

BIRLA CENTRAL LIBRARY

PILANI (RAJASTHAN) R

Class No. 621.38

Book No G2H Vol I

Accession No. 55391

LINE COMMUNICATION

DISTRIBUTION :

**Royal Signals. Scale C.C.
(Manual of Military Publications.)**

W.O.
CODE No.

1698

THE ROYAL SIGNALS

HANDBOOK OF

LINE

COMMUNICATION

*A comprehensive text-book dealing with
the theoretical and practical
aspects of the transmission
of intelligence over lines*

VOLUME I

MCMXLVII

First Published 1947

*Reprinted 1951 Incorporating
Amendments 1, 2, 3 and Errata*

*Fourth impression 1957
Incorporating Supplement*

Crown copyright reserved

Printed and published by
HER MAJESTY'S STATIONERY OFFICE

To be purchased from
York House, Kingsway, London w.c.2
423 Oxford Street, London w^c.1
13A Castle Street, Edinburgh 2
109 St. Mary Street, Cardiff
39 King Street, Manchester 2
Tower Lane, Bristol 1
2 Edmund Street, Birmingham 3
80 Chichester Street, Belfast
or through any bookseller


Price £1 10s. 0d. net

Printed in Great Britain

FOREWORD

A modern text-book covering the theory and practice of line communications has long been required by the Army. This book has been produced at the School of Signals; it is in two volumes, the first volume dealing with the basic theory required for a study of line communications and including a summary of the mathematics necessary for this, the second volume dealing with the practical applications to military line equipments.

The invaluable assistance of the Post Office Engineering Department in the preparation of this book is gratefully acknowledged.

A handwritten signature in black ink, appearing to read "C. R. Williams". The signature is written in a cursive style and is enclosed within a rectangular box that has been drawn around it. The box is slightly larger than the signature and has a thin border.

Major-General,
Director of Signals.

The War Office,
January, 1947.

CONTENTS

VOLUME I

CHAPTER		PAGE
1	AN INTRODUCTION TO LINE COMMUNICATION	1
2	MATHEMATICS	20
3	DIRECT CURRENTS	118
4	ALTERNATING CURRENTS	187
5	AC CIRCUITS	231
6	METAL RECTIFIERS AND POWER SUPPLIES.. .. .	275
7	THERMIONIC VALVES	323
8	VALVE AMPLIFIERS	376
9	FEEDBACK	421
10	OSCILLATORS	463
11	MODULATION	493
12	THE CATHODE RAY OSCILLOSCOPE.. .. .	532
13	FOUR-TERMINAL NETWORKS.. .. .	561
14	ATTENUATION AND ATTENUATORS.. .. .	605
15	FILTERS	635
16	LINE TRANSMISSION	703
17	MATHEMATICAL TREATMENT OF LINE TRANSMISSION.. .. .	749
	APPENDIX I MATHEMATICAL TABLES	774
	APPENDIX II GRAPHICAL CALCULATORS	829
	SUPPLEMENT	843
	INDEX	873

LINE COMMUNICATION

CHAPTER 1

AN INTRODUCTION TO LINE COMMUNICATION

Communication is the conveying of information from one place to another. This may be accomplished in many different ways; for example, by speaking or shouting, by sending a written message, or by flashing a lamp.

To send information from one place to another, three things are necessary: a sending device, a receiving device, and some form of link between the two.

In order to be sent from the transmitter to the receiver, the information must be translated into "signals" that can be passed along the link concerned. In line communication, the signals must be in the form of electric currents that can be transmitted along electrical conductors (referred to as lines), and reconverted into an intelligible form at the receiver. It is the purpose of this book to study the behaviour of electric currents in such lines, and the principles of the various types of terminal equipment.

Line communication is divided into two classes, *viz.* "telegraphy" and "telephony", according to the nature of the signals; the general principles of these two classes will be briefly outlined in the ensuing sections of this chapter.

TELEGRAPHY

Telegraphy may be defined as the art of transmitting messages by means of "code-signals". Telegraph codes suitable for line working are usually built up from two basic conditions, called "mark" and "space". The code-signals representing the various letters of the alphabet, numerals, and punctuation signs, accordingly consist of different combinations of marking and spacing elements.

These signals may be sent by means of a hand-operated key, and received by some instrument for converting them into aural or visual signals that can be translated by a receiving operator; this is called "manual" telegraphy. In "semi-automatic" telegraphy, an operator is again required to manipulate the transmitting

instrument, but at the distant end the signals are received and recorded on paper by a machine that does not necessarily require the continuous presence of an operator. In fully automatic telegraph systems, the actual transmitting and receiving instruments operate without human assistance, the message being fed to the transmitter in the form of a paper tape that is suitably prepared at any convenient time prior to transmission.

Telegraph codes

There are two codes at present in common use for line telegraphy, the Morse code and the Murray code.

The Morse code is the standard code used for manual telegraphy ; it is also extensively used for automatic wireless telegraphy. In it, the signals representing different letters, *etc.*, are, in general, of

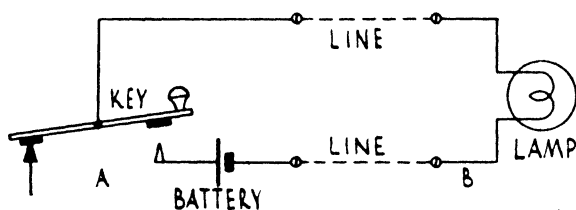


FIG. 1.—Basic telegraph circuit.

different duration, since they consist of different numbers of marking and spacing elements. The latter occur in "groups" as follows :—

- (a) A single marking element, called a "dot".
- (b) Three successive marking elements (with no interval between them), forming a long marking signal called a "dash".
- (c) A single spacing element (equal in length to a dot), to separate the dots and dashes forming a character.
- (d) Three successive spacing elements, to separate the letters of a word.
- (e) Five successive spacing elements, to separate words.

The Murray code was especially designed for automatic working, and it differs basically from the Morse code in that every group in it consists of the same number (five) of elements, each of which may be either mark or space.

This code is used in the teleprinter, but in addition, special "start" and "stop" elements are used at the beginning and end of each group to separate the letters of a word. A special group has to be used to separate words.

Basic telegraph circuit

A simple telegraph circuit is shown in Fig. 1. A key and battery are connected to one end *A* of a line, and a lamp to the other end *B*. When the key is not pressed, the battery is disconnected from the

line, and the lamp will not light ; this is the " spacing condition ". Depression of the key will connect the battery to the line, and the lamp will light ; this is the " marking condition ". The Morse code may therefore be used to convey intelligence from *A* to *B*.

Practical developments

Since watching the lamp would be very tiring for the receiving operator, the lamp might be replaced by some device that would produce two different sounds, or alternatively sound and no sound, to represent the marking and spacing conditions. Alternatively, a permanent record of the received signals could be made by arranging an electro-magnet to deflect a pen over a moving paper tape. This would then leave a trace as in Fig. 2*a* if the pen were to be deflected sideways, or as in Fig. 2*b* if up-and-down. The latter form of trace gave rise to the terms " mark " and " space ".

For higher operating speeds an automatic or semi-automatic system must be used. An example of the latter is the teleprinter ; a " typewriter pattern " keyboard is provided, and when any key

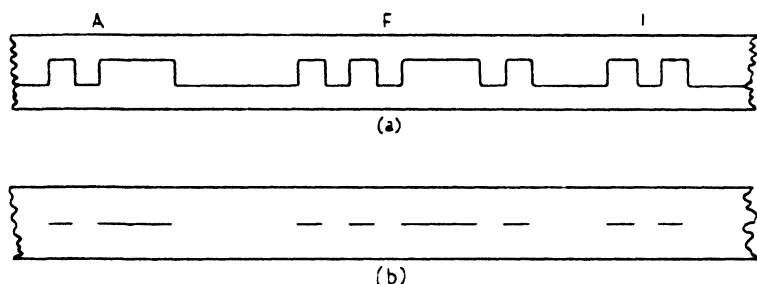


FIG. 2.—Recorded telegraph signals.

is depressed the appropriate groups of the Murray code are sent to line. The receiver converts the code-groups into mechanical movements that select and print the corresponding characters. By providing a transmitter and a receiver at each end, the simultaneous transmission of messages in the two directions can be obtained.

TELEPHONY

Telephony is the transmission of sound—in particular, speech—to a distant place. In the case of line telephony, the mechanical energy of the speaker's voice is made to control electric currents having similar characteristics. At the receiving station, these currents are reconverted into sound waves similar to those originated by the speaker.

Sound

Sound consists of air vibrations, which spread out in all directions from the source. The latter is usually a vibrating body—such as

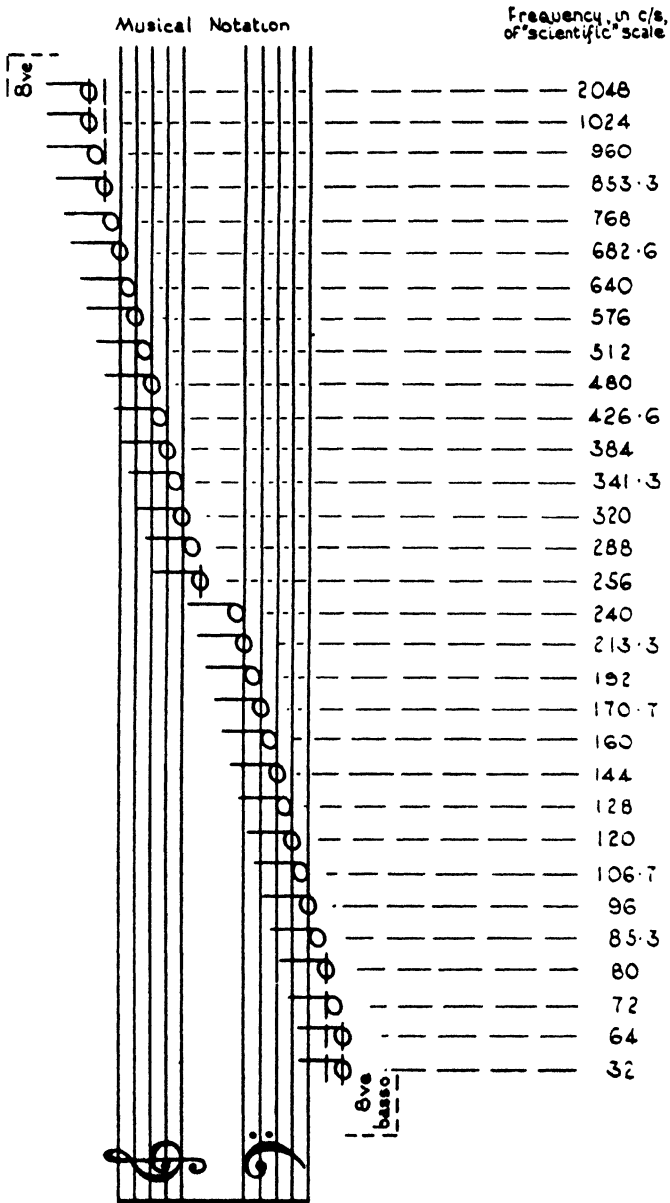


FIG. 3.—Scientific musical scale.

the human vocal chords—which causes the adjacent air to vibrate in a like manner. The vibrations then spread out, at a speed of roughly 1,100 feet per second, causing all near-by air particles to oscillate longitudinally about their original positions. It must be noted that it is the vibrations, and not the air itself, which spread out from the source. When these vibrations reach any light free-to-move object, they will cause it to vibrate in a similar manner. If this object be the diaphragm of a person's ear, the vibration will give him the "sensation" of sound, the loudness depending on the amplitude of the vibrations.

The pitch of a sound depends on the "frequency" of the vibrations—that is to say, the number of vibrations per second; the greater the frequency, the higher the pitch. The ear can hear sounds of frequencies from about 20 to 20,000 cycles per second, the exact audible limits varying from person to person. However, if only the frequencies ranging from 300 to 2,000 c/s are received, the speech will still be intelligible although its quality will be changed. Fig. 3 shows the frequencies of the various notes of the "scientific" musical scale.

Waveform

The simplest form of vibration is the rather dull and insipid note produced by a tuning fork. This sound is called a "pure" tone, since it consists of a "sinusoidal" vibration of one frequency only, and can be represented by a "sine" curve, as in Fig. 4*a*. In general, however, the vibrations corresponding to the tones of musical instruments and speech are somewhat more complex (Fig. 4, *b* to *e*), but can be analysed into a "fundamental" vibration—of a frequency determining the pitch of the note—together with a number of higher-frequency "harmonics" that determine the quality or "timbre" of the sound. Each of these harmonics is a simple (sinusoidal) vibration of frequency equal to a multiple of the frequency of the fundamental, and it is the relative proportions of the various harmonics which distinguish between the tones of, say, a violin and a trumpet, both playing the same note of the scale, or between the various sounds that occur in speech, or between different people's voices. If a telephone circuit limits the transmitted frequency band to 300–2,000 c/s, the higher harmonics will be lost, and although speech will still be perfectly intelligible, this distinction will be lost, and it may be difficult to recognise the voice of the person speaking at the other end.

Basic telephone circuit

Fig. 5 shows a simple telephone system. The battery passes a current through the microphone, along the line, and through the receiver at the distant station. The microphone (see Fig. 6) is in effect a resistance that varies according to the position of its diaphragm. Sound vibrations falling on the diaphragm cause it to move forwards and backwards, and so cause corresponding changes

TELEPHONY

in resistance. The current in the line will therefore vary at the frequency of the sound vibration, and in a manner representing the timbre of the sound. The receiver (Fig. 7) consists of an iron diaphragm in front of an electro-magnet, towards which it is attracted; being held round the rim, it is drawn in at the centre

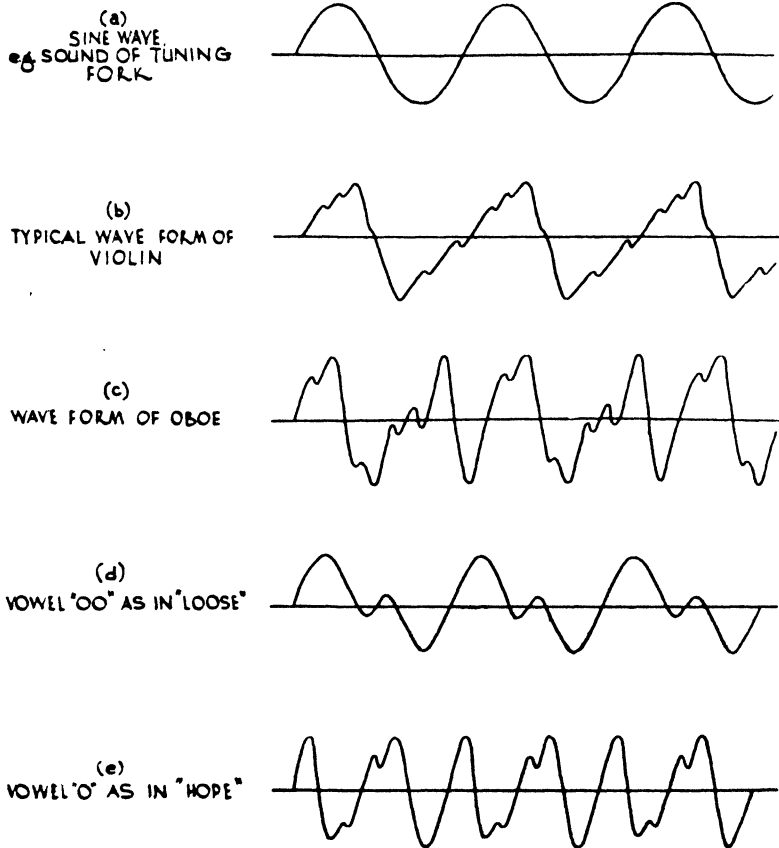


FIG. 4.—Typical waveforms.

towards the magnet. The strength of the attraction, and therefore the extent of the movement, depends on the current through the coils of the electro-magnet. Hence the diaphragm will move forwards and backwards in accordance with the current changes, and, in moving, will give rise to sound waves similar to those falling on the microphone at the far (transmitting) end of the line.

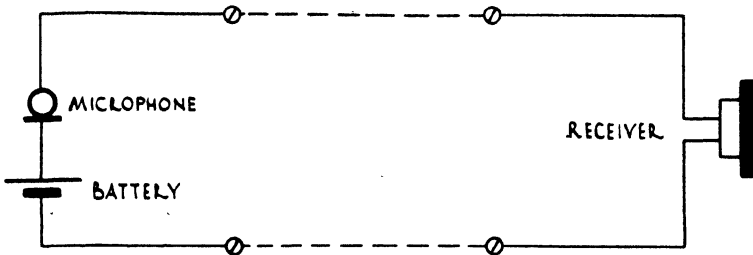


FIG. 5.—Simple telephone circuit.

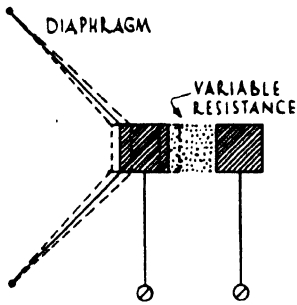


FIG. 6.—Microphone.

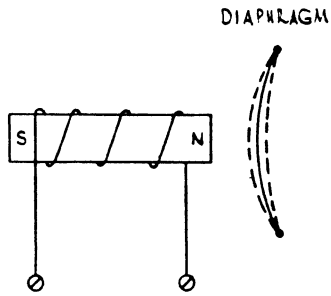


FIG. 7.—Telephone receiver.

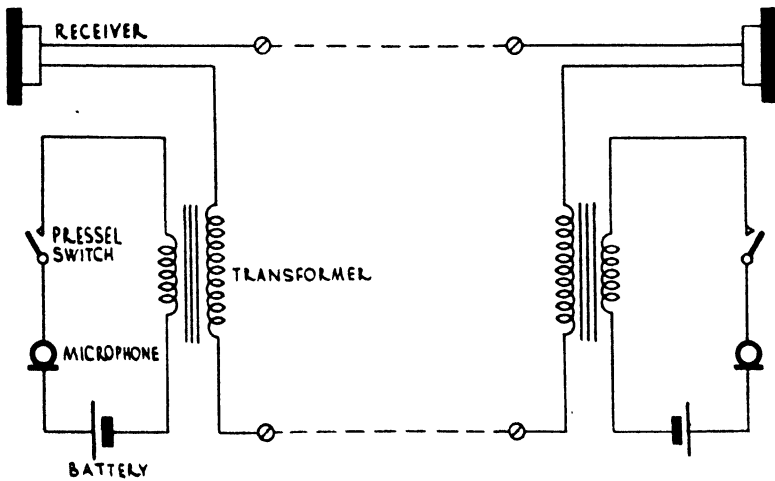


FIG. 8.—Basic telephone circuit.

Practical developments

While the circuit of Fig. 5 would be quite satisfactory for working over a short line, it would be useless on a long line with appreciable resistance, since the changes in resistance of the microphone would be negligible compared with the resistance of the line, and so the changes in current would be barely perceptible. The difficulty is overcome in practice by the use of a transformer, as in Fig. 8. This consists of two windings round a common core. The first is connected to the battery and microphone, and is of low resistance, so that the changes in resistance of the microphone can cause a large change in current round this circuit; this winding is called the "primary". The second winding consists of a large number of turns, so that the changes in primary current will induce into it the optimum voltage for driving the current through the line to operate the receiver at the distant end; this is called the "secondary" winding. Over short distances, an instrument such as this will work satisfactorily with "earth return"—that is to say, with one of the two line wires replaced by a good connection to the

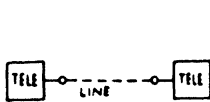


FIG. 9.—Two telephones connected by a line.

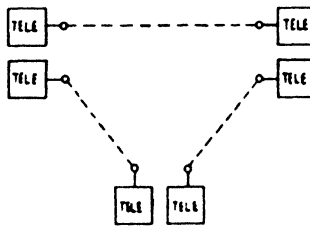


FIG. 10.—Three stations with independent telephones between each.

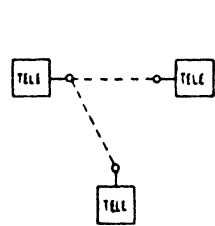


FIG. 11.—Three telephones with party line connection.

ground at each end. In addition to what is shown in the basic circuit of Fig. 8, telephones normally have some means of "calling", or attracting the attention of the person at the other end, as, for example, a magneto generator, operation of which rings a bell on the distant instrument.

An important refinement usually incorporated is some form of "anti-sidetone" circuit, to prevent speech, and any other noises picked up by one's own microphone, from being heard in one's own receiver. This device is particularly advantageous when listening to weak signals in a noisy place.

EXCHANGES

The simplest possible telephone system consists of two telephones connected by a line as in Fig. 9. This is quite a suitable arrangement if two subscribers wish to speak to one another and to no one else. If three people wish to be interconnected, so that each can

converse privately with either of the other two, this can be arranged by repeating the simple lay-out, as shown in Fig. 10. This is uneconomical in equipment, however, since six telephones are needed to interconnect three subscribers.

If the subscribers are interconnected as shown in Fig. 11, only three telephones are used instead of six. This is not altogether satisfactory, however, because when any two of the three subscribers are conversing, the third can listen to the conversation; also, when one subscriber rings to attract the attention of another, the bell of the third subscriber rings too.

The switchboard

In practice, it is usually necessary for a subscriber to be able to speak privately with any one of a number of other subscribers. A flexible system is therefore needed whereby any subscriber's telephone can be connected at will to that of any other subscriber. The simple lay-outs described above are not suitable for this, and in practice this facility is provided by a "switchboard"; this is a piece of apparatus to which all the subscribers' instruments are connected (Fig. 12), and by means of which a switchboard operator can inter-connect any two subscribers. Many switchboards also provide for calls in which more than two subscribers are connected together.

By means of "junction" lines between switchboards, a subscriber connected to one switchboard can be connected through to a subscriber on another, as shown in Fig. 13. Moreover, two such junction lines can be connected together, as in Fig. 14; a subscriber on one switchboard can thus be connected "through" another switchboard, so that he can speak to any subscriber on any subsequent switchboard.

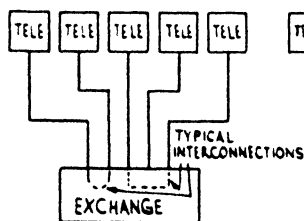


FIG. 12.—Telephones connected to exchange.

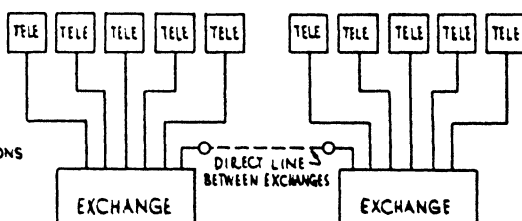


FIG. 13.—Two interconnected exchanges.

Larger switchboards (as distinct from portable field switchboards) generally have a certain amount of associated equipment separate from the switchboard itself. This includes such items as batteries, frames on which the lines are terminated, fuses and other protective devices, testing apparatus, *etc.* The term "exchange" is used to denote the switchboard together with all its associated equipment.

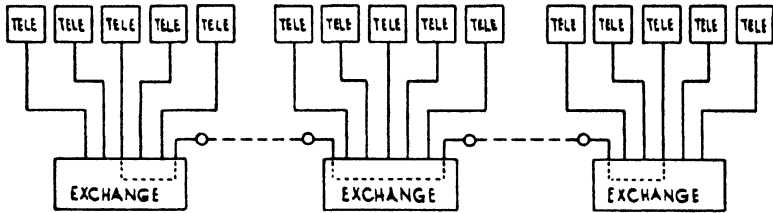


FIG. 14.—Call through three exchanges.

Requirements of switchboards

(a) Subscribers must be able to attract the attention of the switchboard operator; one "calling indicator" is accordingly provided at the switchboard for each subscriber's line, and subscribers are provided with some means of sending a calling signal which will make the indicator operate.

(b) The switchboard operator must be able to attract the attention of any subscriber; each subscriber is therefore provided with a bell, or other form of alarm, that can be operated by a calling signal from the switchboard operator, and the switchboard must include a means of sending this signal.

(c) The switchboard operator must be able to connect any two or more subscribers' instruments together. This is sometimes done by keys on smaller switchboards but is more often effected by means of "cords", with plugs at the end, which the operator can insert into "jacks" connected to the various subscribers' lines.

(d) The subscribers must be able to inform the switchboard operator when they have finished their conversation, so that he can disconnect them. They do this by sending a "clearing signal", to operate some form of clearing or "supervisory" indicator at the switchboard.

(e) The switchboard operator must be able to speak to, and hear, any subscriber; he is therefore provided with a telephone that he can connect to any subscriber's line.

(f) The switchboard operator must be able to monitor, or "listen in to", any conversation without interfering with it, both to make sure that the call is really "through", and also to find out whether the subscribers have finished, since clearing signals may not always be given. He must therefore be able to connect his telephone to the subscribers' lines during a conversation.

(g) All the above requirements must also be satisfied when the "subscriber" is another exchange to which a direct line is provided.

Exchange signalling

From a technical point of view, the simplest method of calling a telephone exchange is the "magneto" system. In this system, the subscriber operates a magneto generator, which provides

sufficient power to operate the indicator at the switchboard. For signalling from subscriber to switchboard, this system suffers from the great disadvantage that if a subscriber fails to "ring off", there is nothing to tell the switchboard operator that the conversation has been concluded. Calling from the switchboard to the subscriber is, however, normally effected by the magneto system, since the ringing-off difficulty does not apply there, and a bell is the most satisfactory method of attracting a subscriber's attention. Another system sometimes used is the "buzzer"; in this system, a buzzer operated by the calling subscriber sends to line an alternating current that can operate an indicator at the exchange, or cause a buzz in the receiver at the distant end.

To avoid the need for ringing off, the "central battery signalling" (CBS) systems were developed. In these, raising the handset of the subscriber's telephone from its cradle or hook operates a switch and completes a DC circuit *via* the line, so that the battery at the exchange can operate the calling indicator. This is known as "loop" calling. The cord circuit includes a "supervisory" indicator, arranged to attract the operator's attention when the handset is replaced on its cradle, so that the subscriber does not have to ring off. Frequently, two supervisory indicators are provided, one connected to the line of each of the two subscribers conversing, so that independent supervision of each subscriber's actions is obtained; if one supervisory indicator operates, and not the other, then the operator knows that the one subscriber has replaced his handset, but that the other has not, and probably requires attention.

A diagram showing the basic circuits of various exchange systems will be found in Chapter 19, Vol. II.

The CB and automatic systems

In all the telephone systems considered above, batteries are required at each subscriber's instrument for the microphone circuit. In the case of large permanent installations this arrangement is undesirable, since it is necessary for a mechanic periodically to change the batteries at all the subscribers' telephones—which may be scattered over a large area. Several types of "common battery" (CB) systems have been developed, in which one large battery at the exchange is used to provide the energising current for all the subscribers' microphones; there are then no components in the subscribers' instruments that should, in the normal course of events, ever require attention. The lines between the subscribers and the exchange have to be of fairly low resistance. The system is therefore unsuitable for subscribers situated far from the exchange, and they will have to use CBS type instruments, which work quite satisfactorily on CB exchanges. In all CB systems, the exchange is called by means of a loop between the two legs of the line, as in CBS systems, and the subscriber is called by means of a generator and bell.

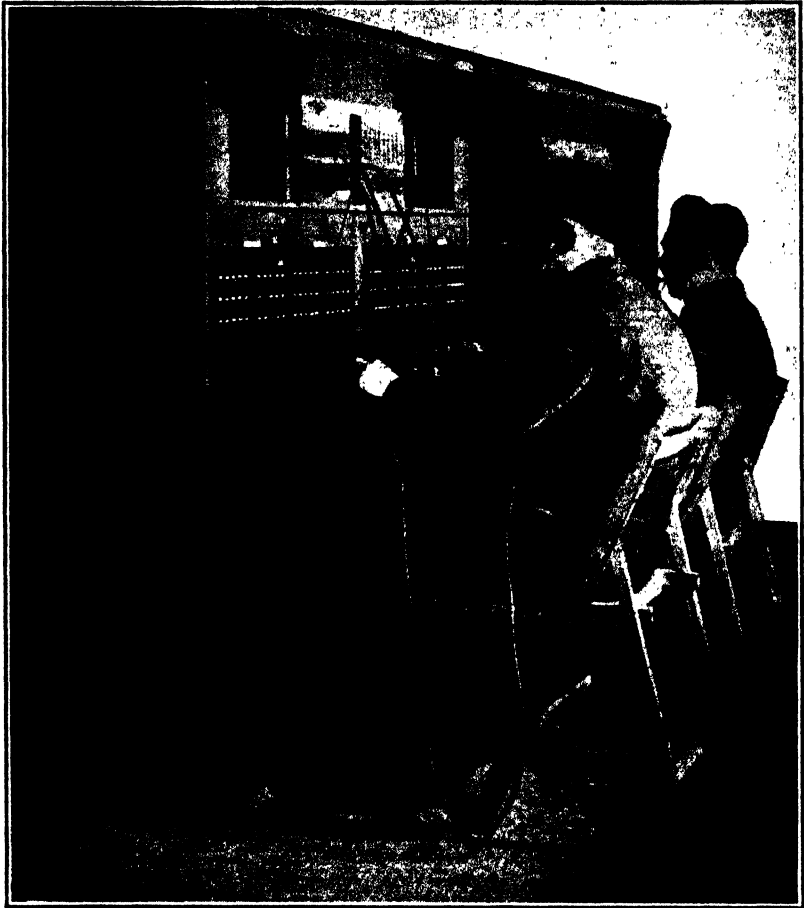


PLATE 1.—Army magneto exchange.

In automatic systems, raising of a subscriber's handset from its cradle loops the line, and causes him to be connected on to a "selector". "Dialling" any digit interrupts this loop a corresponding number of times, causing the selector to step up and round and to connect the subscriber to a further selector. This process is repeated for the second and subsequent digits, connecting the calling subscriber to the line of the subscriber whose number he has dialled. But before making this connection, the final selector connects the called subscriber's line to a power-driven ringing generator; when the called subscriber raises his handset from its cradle, his line is disconnected from the generator, and connected through to the calling subscriber. When the calling subscriber replaces his handset the selectors return to their normal position in readiness to deal with another call.

LONG LINES AND REPEATERS

Attenuation, distortion and interference

A line "attenuates" the signals passed along it; that is to say, the signals reaching the receiving end are weaker than those transmitted from the sending end, owing to power losses in the line itself. The attenuation increases as the length of the line is increased, and on long lines the received signals may be so weak as to be useless unless some steps are taken to make up for the attenuation by amplification; this is done by means of "repeaters". In addition to attenuation, distortion and interference must be considered.

"Distortion" is said to occur in a line or in any piece of equipment when the signal leaving it is not identical in "form" or character (though not necessarily in magnitude) with that entering it. The attenuation of a line increases with frequency, and consequently the higher-frequency components of a signal are weakened more than the lower. Since the relative proportions of the various components of a signal determine its character, this variation of attenuation with frequency constitutes a form of distortion (attenuation-distortion) which, if not corrected, may render the received signal unintelligible. The required correction is effected by means of "equalisers".

Any line picks up noise from nearby power lines, *etc.*, and also "cross-talk" from neighbouring telephone and telegraph circuits. On a long line, the amplitude of such interference might be sufficient to "drown" the signals. Both forms of interference are in general much less in the case of metallic circuits than in the case of those using earth return, and can be greatly reduced by ensuring a symmetrical disposition of the two legs of the line.

Repeaters

To compensate for the power loss in a long line, "repeaters" can be employed to "boost up" the weakened signal currents.

Normally, two amplifiers will be required at each repeater, one for each direction of transmission; these are usually called "send" and "receive", or the "up-to-down" and "down-to-up", amplifiers, to distinguish between them. Also, some form of "separating device" will be required between the telephone and the amplifiers to isolate the input circuit of the one amplifier from the output of the other, as in Fig. 15. The commonest form of separating device is the "hybrid transformer". If this isolation is not effected on both sides of the amplifiers, then a signal from one of the telephones, after amplification by the "send" amplifier, will reach the input side of the "receive" amplifier; after further amplification by this, it will get back to the input of the send amplifier, and the amplifiers will "sing" or "howl".

Repeaters must be spaced at intervals along the line. If one large amplifier were to be used at the transmitting end of the line,

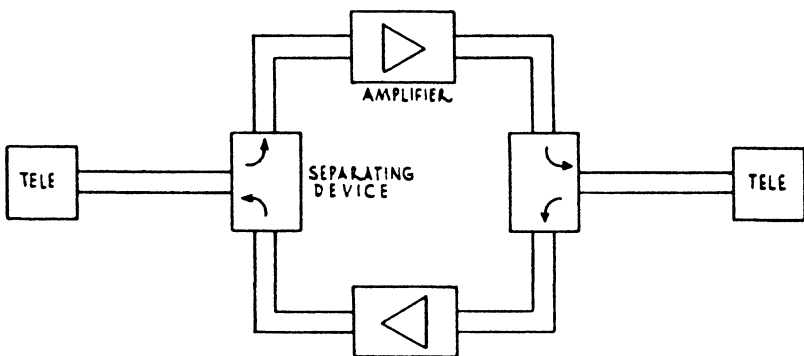


FIG. 15.—Telephone repeater.

its output would be so great that (a) it would cause severe interference to other circuits, and (b) the cost of the amplifier would be enormous. On the other hand, if all the amplification were to be concentrated at the receiving end of the line, the signal currents reaching the amplifier would, in the case of long lines, be much smaller than the noise and cross-talk currents picked up by the line; these would therefore obliterate the signal. By careful repeater spacing, however, the effects of line attenuation can be satisfactorily overcome, while the effects of noise and cross-talk can usually be reduced to negligible proportions.

Two- and four-wire circuits

It will be seen from Fig. 15 that whereas there are only two wires from the telephone, there are four wires between the amplifiers and the "separating device". On a long line requiring a number of repeaters, there are therefore two possible methods of working:

Two-wire Circuit.—Two wires can be run between repeaters, each of which will then have to contain two "separating devices", one on each side of the amplifiers, as in Fig. 16.

Four-wire Circuit.—By running four wires between repeaters, as in Fig. 17, only the two terminal repeaters need contain any separating devices; intermediate repeaters will each have two amplifiers, one for transmission in each direction, and these two amplifiers will be completely separate electrically, since different pairs of wires are used for the two directions.

Whereas the two-wire circuit is more economical in lines, a four-wire circuit requires, in general, fewer repeaters for a given

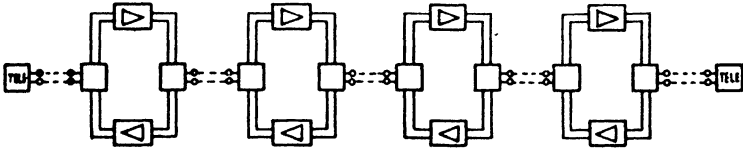


FIG. 16.—Two-wire repeatered circuit.

length of line, is easier to set up and maintain, and is more stable under varying line conditions. Electrically, the four-wire circuit is therefore preferable, particularly on long lines, but the economy in lines afforded by two-wire repeatered circuits is such that these are frequently used for military purposes.

Signalling over repeatered circuits

Speech amplifiers cannot deal with the low-frequency calling signals from a magneto generator, and repeaters must incorporate additional apparatus when generator signalling is used. Alternatively, the generator signals may be converted at the terminals into

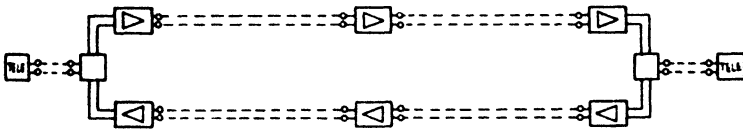


FIG. 17.—Four-wire repeatered circuit.

tones lying within the speech range, which can then be amplified by the same apparatus as the speech. This latter method is known as "voice-frequency" signalling.

Equalisers

Equalisers are electrical networks designed to counteract the attenuation distortion occurring in any part of a circuit. They do this, either by introducing additional attenuation at those frequencies at which the attenuation is least, so that the overall attenuation is independent of frequency; or else by increasing the amplification in a repeater at those frequencies at which the attenuation is

greatest. Equalisers are usually included in repeaters, as well as in terminal equipment, so that the distortion, in the same way as the attenuation, can be corrected all along the line, before it can reach too serious a value.

SIMULTANEOUS TRANSMISSION OF SEVERAL MESSAGES OVER ONE LINE

Particularly in rear areas, very large numbers of telephone conversations are frequently required between different HQs, and a single line between the respective exchanges, such as that shown in Fig. 13, would therefore be totally inadequate. Owing to the time and the volume of stores required to install several lines, special forms of apparatus are often used that enable a line to handle more than one telephone or telegraph message at a time. This is particularly desirable in the case of long repeated lines.

Superposing

"Superposing" is the direct connection of more than one telephone or telegraph instrument on to one line, and there are several simple methods of doing this. The simplest method is direct "series" superposition of a telegraph on to a telephone circuit, as in Fig. 18. This method is very restricted in its application. It depends on the principle that the telephone is unaffected by the DC and very low-frequency AC used by the telegraph

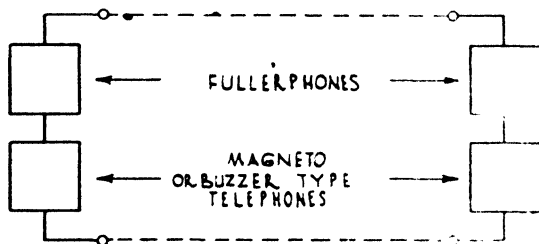


FIG. 18.—Series superposing.

instrument, and that the telegraph instrument is not affected by the alternating currents of the frequencies used by the telephone. This arrangement cannot be used when working to an exchange employing direct current in the line (*i.e.* a CB or CBS exchange). The telephone instrument used must be capable of passing the direct current required by the telegraph instrument.

The only telegraph instrument suitable is the Fullerphone. Even using this instrument, there will be a certain amount of interference to the Fullerphone each time the buzzer or ringing magneto of the telephone is operated.

Phantom working

Phantom working is a more satisfactory method of superposing. In earth-return phantom working, one telephone circuit is obtained in the usual way between the two wires of the line, so that current goes out on one wire and returns by the other. The second instrument is connected between the centre-point of this "physical"

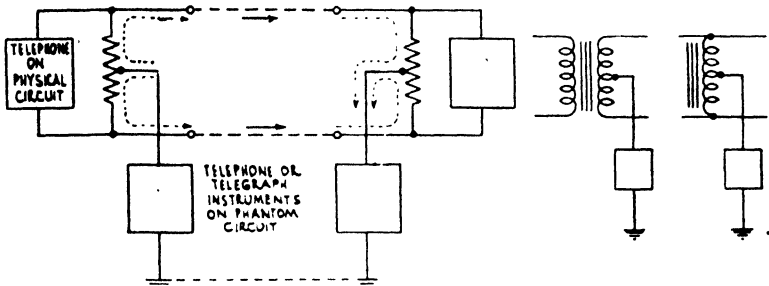


FIG. 19.—Earth-return phantom superposing. FIG. 20.—Phantom connections.

circuit and earth, as in Fig. 19, so that the current divides equally between the two wires—going out on both wires in parallel, and returning *via* the earth; this latter is called the "earth-return phantom" circuit. Fig. 20 shows two methods that can be used to obtain the centre-tap on the physical circuit.

While there is usually no appreciable interference between the physical and the phantom circuits on a pair, the earth-return phantom circuit tends to pick up a lot of noise and interference, since it uses an earth return. On long lines, earth-return phantom circuits are not satisfactory as high-grade speech circuits. They are, however, frequently used in forward areas, and are sometimes

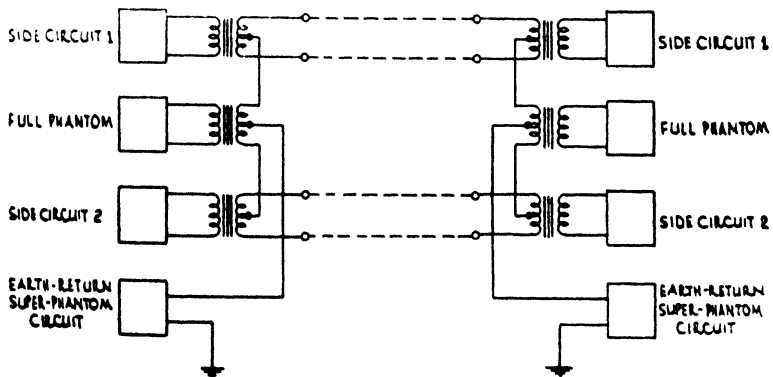


FIG. 21.—Full phantom working, with earth-return superphantom circuit.

used for "maintenance telephones" between repeater stations, to provide communication between the station mechanics.

An improvement on the earth-return phantom circuit just described is the "full phantom" circuit, in which the "phantom" telephone is connected between the centre-taps of two physical circuits, as in Fig. 21. An "earth-return super-phantom" circuit (sometimes known as double-phantom or ghost circuit) can then be added between the centre-tap of the full-phantom circuit and earth. The full-phantom circuit avoids interference from earth currents, but is suitable for high-grade speech circuits only when the two pairs on which it is superposed are of low capacity and are balanced with respect to each other as well as to earth. It is unsuitable for use on star quad cable, which has a relatively high capacity, but it may be used on multiple twin cables and "square-formation" permanent (overhead) line. Nevertheless, a high-grade circuit is obtained from a full phantom only when the physical pairs are very carefully balanced; the earth-return super-phantom circuit is clearly just as subject to interference from earth currents and cross-talk as the simple earth-return phantom.

V.F. telegraphy

The transmitted signals of the telegraph systems so far described have too low a frequency to be amplified conveniently by a valve amplifier in the same way that speech is amplified by a repeater. If, however, the telegraph signals are converted into "tone" within the speech range, they can then be sent over an ordinary telephone circuit and through the speech amplifiers. This method of transmitting telegraph signals is called "voice frequency" (VF) telegraphy.

It is possible to send these "voice frequency tone" signals over the same line as a telephone conversation, and at the receiving end to separate the VF tone from the speech so that there is no mutual interference. The use of this principle will thus permit one speech and one telegraph circuit to work simultaneously over one pair of lines. Although the advantages of this over phantom working are not at first apparent, it may be said that satisfactory operation of the telegraph equipment is possible over much greater distances. Also, in the case of a line sufficiently long to require a repeater for the telephone circuit, the ordinary telephone repeater will amplify the telegraph tone as well as the speech, with no modification at all, whereas with phantom working, a separate repeater would be necessary for the telegraph signals.

Alternatively, it is possible to send a number of different VF tones over the line instead of speech, thus forming a multi-channel VF telegraph system. As many as eighteen such VF channels may be employed over a telephone circuit (assuming, of course, the appropriate equipment at each end), and the advantages of the use of VF telegraphy then become apparent. In rear areas, where there is a vast amount of administrative traffic to be passed, one telephone

can be replaced by a number of telegraph instruments (*e.g.* teleprinters).

Carrier telephony

In carrier telephony, the signals from the transmitting telephone are altered in such a way that they can be passed over the same line as signals from an ordinary telephone, separated from these at the receiving end, and then altered back into normal type telephone currents similar to those leaving the transmitting instrument. This "alteration" consists in moving bodily the whole frequency band occupied by the speech signals to a higher position in the frequency spectrum (say, 3,000 to 6,000 c/s), so that whereas a line used for normal telephony has to pass only frequencies between 0 and 3,000 c/s, a line carrying one "physical" and one "carrier" telephone channel, would have to pass all frequencies between 0 and 6,000 c/s. Carrier telephone systems are therefore more stringent in their line requirements than ordinary telephone circuits.

In multi-channel carrier systems, the signals from each channel transmitter are raised to successively higher frequency bands, and consequently the lines for use with such equipment must be even more carefully chosen. This will be realised when it is stated that under certain conditions, a four-channel carrier telephone system may transmit frequencies up to 50,000 c/s.

Clearly, since all the channels of a multi-channel carrier telephone system are suitable for telephony, they are also suitable for VF telegraphy, and it is common practice to operate a six-channel VF telegraph system over one channel of a four-channel carrier telephone system; this then provides three telephone and six teleprinter circuits.

CHAPTER 2

MATHEMATICS

In order to understand many of the principles of line communication, some knowledge of mathematics is essential. This chapter contains a summary of the simpler branches of mathematics with which the reader is expected to have some acquaintance. The chapter is divided into two parts. Part I contains a summary of algebra and trigonometry, leading up to vectors and complex numbers. Part II includes the elements of calculus and hyperbolic functions, and is intended for those who wish to make a more detailed study of the subject.

Tables of logarithms, trigonometrical functions, *etc.*, will be found at the end of this volume (page 775).

Mathematical symbols

$=$	is equal to . . .
\equiv	is equivalent to . . .
\approx	is approximately equal to . . .
\neq	is not equal to . . .
\rightarrow	tends to <i>or</i> approaches . . .
$>$	is greater than . . .
\geq	is greater than or equal to . . .
\gg	is very much greater than . . .
\nlessgtr	is not greater than . . .
$<$	is less than . . .
\leq	is less than or equal to . . .
\ll	is very much less than . . .
\nlessgtr	is not less than . . .
\sim	the positive difference between . . .
$\sqrt{\quad}$	the square root of . . .
$\sqrt[n]{\quad}$	the <i>n</i> th root of . . .
\sphericalangle	a positive angle; that is, an angle measured in an anti-clockwise direction.
\sphericalangle	a negative angle; that is, an angle measured in a clockwise direction.

PART I

ELEMENTARY MATHEMATICS

Areas, surfaces and volumes

	<i>Surfaces</i>	<i>Volumes</i>
Sphere	$4.\pi.r^2$	$\frac{4}{3}.\pi.r^3$
Cone	$\pi.r.l + \pi r^2$	$\frac{1}{3}.\pi.r^2.h$
Cylinder	$2\pi rh + 2\pi r^2$	$\pi r^2 h$
Triangular prism	$h(a + b + c) + 2\Delta$	$\Delta . h$
Cuboid	$2ab + 2bc + 2ca$	$a . b . c$
	<i>Areas</i>	
Circle	πr^2	
Sector	$\frac{1}{2}r^2\theta = \frac{\pi}{360}r^2 . \varphi^\circ$	
Parallelogram	$hb = b.c.\sin A$	
Trapezium	$\frac{1}{2}h(x + y)$	
Triangle	$\frac{1}{2}hb = \frac{1}{2}b.c.\sin A$ $= \sqrt{s(s-a)(s-b)(s-c)}$	
where :	r = radius l = slant height h = perpendicular distance between faces x, y, a, b, c = sides s = semi-perimeter = $\frac{1}{2}(a + b + c)$ θ = angle in radians φ° = angle in degrees Δ = area of triangle	

Pythagoras' Theorem

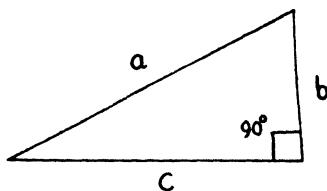


FIG. 22.—Pythagoras' Theorem.

In any right-angled triangle:—

$$a^2 = b^2 + c^2 \tag{1}$$

where a is the length of the hypotenuse (*i.e.* the side opposite the right-angle), and b and c are the lengths of the other two sides.

Indices

a raised to the power n , written as " a^n ", is defined as a multiplied by itself n times,

$$\text{i.e.} \quad a^n = a \times a \times a \times a \dots \text{to } n \text{ factors} \quad (2)$$

$$\text{Thus} \quad 2^4 = 2 \times 2 \times 2 \times 2 = 16$$

In such cases, n and 4 are known as indices.

Multiplication.— $a^n \times a^m = a^{n+m}$; i.e., to multiply powers of the same number, the indices are added.

From this, it can be seen that $a^0 = 1$; for $a^n \times a^0 = a^{n+0} = a^n$, i.e., multiplying by a^0 leaves the value unchanged,

$$\therefore a^0 \text{ must be equal to } 1.$$

$(a^n)^m = a^{nm}$, i.e., when a power is itself raised to a power, the two indices are multiplied.

$(ab)^n = a^n b^n$, i.e., when the product of two numbers is raised to a power, the result is equal to the product of the two numbers each raised to that power.

$$\left. \begin{aligned} a^{-n} &= \frac{1}{a^n} \text{ (for } a^{-n} \times a^n = a^{-n+n} = a^0 = 1) \\ \frac{1}{a^n} &= \sqrt[n]{a}, \text{ for } \left(\frac{1}{a^n}\right)^n = a^{-n} = a \end{aligned} \right\} (3)$$

Note in particular that $\sqrt{ab} = \sqrt{a} \times \sqrt{b}$, and that $\sqrt{\frac{a}{b}} = \frac{\sqrt{a}}{\sqrt{b}}$

Surds.—A square root that cannot be further reduced is called a surd, e.g., $\sqrt{2}$, $\sqrt{3}$, $\sqrt{5}$.

$$\sqrt{8} \text{ is not a surd, as it can be reduced to } 2 \times \sqrt{2}.$$

Rationalization

Evaluation of expressions such as $\frac{1}{\sqrt{2}}$ is difficult, since it involves division by a decimal. If top and bottom are both multiplied by $\sqrt{2}$, the value will be unaltered,

$$\therefore \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{2}} \times \frac{\sqrt{2}}{\sqrt{2}} = \frac{\sqrt{2}}{2} = \frac{1.414}{2} = 0.707,$$

and calculation is thus simplified.

Similarly, $\frac{1}{\sqrt{3}-\sqrt{2}}$ can be simplified by turning the bottom line into the difference of two squares:—

$$\frac{1}{\sqrt{3}-\sqrt{2}} = \frac{1}{\sqrt{3}-\sqrt{2}} \times \frac{\sqrt{3}+\sqrt{2}}{\sqrt{3}+\sqrt{2}} = \frac{\sqrt{3}+\sqrt{2}}{(\sqrt{3})^2 - (\sqrt{2})^2}$$

$$\begin{aligned}
 &= \frac{\sqrt{3} + \sqrt{2}}{3 - 2} = \sqrt{3} + \sqrt{2} \\
 &= 1.732 + 1.414 = 3.146
 \end{aligned}$$

Example.—
$$\frac{1}{\sqrt{1+x^2}+x} = \frac{1}{\sqrt{1+x^2}+x} \times \frac{\sqrt{1+x^2}-x}{\sqrt{1+x^2}-x}$$

$$= \sqrt{1+x^2}-x \quad \text{Ans.}$$

Useful factorisations

$$a^2 - b^2 = (a + b)(a - b) \quad (4)$$

$$a^3 - b^3 = (a - b)(a^2 + ab + b^2) \quad (5)$$

$$a^3 + b^3 = (a + b)(a^2 - ab + b^2) \quad (6)$$

$$a^4 + a^2b^2 + b^4 = (a^2 - ab + b^2)(a^2 + ab + b^2) \quad (7)$$

Simultaneous equations

If there are n unknowns to be evaluated, there must be n equations. The procedure for solution is to reduce to $n - 1$ equations with $(n - 1)$ unknowns, and to continue this process until only one equation containing one unknown is left. The latter is a simple equation which can be solved at once; the other unknowns may then be found by working back through the equations.

Example.—

Solve

$$\begin{aligned}
 x + y - z &= 1 && (i) \\
 2x + y + z &= 6 && (ii) \\
 x + 2y + 2z &= 9 && (iii)
 \end{aligned}$$

Adding equations (i) and (ii) :—

$$\begin{aligned}
 x + y - z &= 1 && (i) \\
 2x + y + z &= 6 && (ii) \\
 \hline
 3x + 2y &= 7 && (iv)
 \end{aligned}$$

Multiplying equation (i) by 2, and adding to equation (iii) :—

$$\begin{aligned}
 2x + 2y - 2z &= 2 && (i) \times 2 \\
 x + 2y + 2z &= 9 && (iii) \\
 \hline
 3x + 4y &= 11
 \end{aligned}$$

Subtracting equation (iv) from (v) :—

$$\begin{aligned}
 3x + 4y &= 11 && (v) \\
 3x + 2y &= 7 && (iv) \\
 \hline
 &&&
 \end{aligned}$$

$$\begin{aligned}
 &2y = 4 && \therefore y = 2 \\
 \therefore \text{From (iv),} &3x + 4 = 7 && \therefore x = 1 \\
 \text{From (i)} &1 + 2 - z = 1 && \therefore z = 2 \\
 \text{Thus :—} &\left. \begin{array}{l} x = 1 \\ y = 2 \\ z = 2 \end{array} \right\} \text{Ans.}
 \end{aligned}$$

Quadratic equations

Quadratic equations, *i.e.*, those of the form $ax^2 + bx + c = 0$, may be solved by three methods:—

- (a) Factorisation.
- (b) Completing the square.
- (c) Formula.

(a) *Factorisation.*—If the equation can be factorised by inspection as $(lx + m) \cdot (px + q) = 0$, the roots are $x = -\frac{m}{l}$ and $x = -\frac{q}{p}$.

Example.—

$$\begin{aligned} \text{Solve } 3x^2 + 7x - 6 &= 0 \\ \therefore (3x - 2)(x + 3) &= 0 \\ \therefore x &= \frac{2}{3} \text{ or } -3 \quad \text{Ans.} \end{aligned}$$

(b) *Completing the square.*—Rearrange the equation to give a perfect square in terms of x , and take the positive and negative roots.

Example.—

$$x^2 + 4x + 2 = 0$$

Divide if necessary to make the coefficient of x^2 equal to 1, and then rearrange so that only terms containing x^2 and x appear on the left-hand side, *e.g.*, $x^2 + 4x = -2$.

Add (half the coefficient of x)² to each side:—

$$\begin{aligned} x^2 + 4x + 4 &= -2 + 4 \\ \therefore x^2 + 4x + 4 &= 2 \\ \therefore (x + 2)^2 &= 2 \\ \therefore x + 2 &= \pm \sqrt{2} \\ \text{i.e. } x &= -2 \pm \sqrt{2} \quad \text{Ans.} \end{aligned}$$

(c) *Formula.*—Apply method (b) to the general equation:—

$$ax^2 + bx + c = 0$$

$$\text{Then } x^2 + \frac{b}{a}x = -\frac{c}{a}$$

Add $\left(\frac{b}{2a}\right)^2$, *i.e.* $\frac{b^2}{4a^2}$ to each side:—

$$\begin{aligned} x^2 + \frac{b}{a}x + \frac{b^2}{4a^2} &= \frac{b^2}{4a^2} - \frac{c}{a} \\ \therefore \left(x + \frac{b}{2a}\right)^2 &= \frac{b^2 - 4ac}{4a^2} \\ \therefore x + \frac{b}{2a} &= \frac{\pm \sqrt{b^2 - 4ac}}{2a} \\ \therefore x &= \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} \quad (8) \end{aligned}$$

This formula gives the two roots of any quadratic equation. Note the three cases :—

$$\begin{aligned} b^2 &> 4ac, \text{ both roots are real,} \\ b^2 &= 4ac, \text{ the roots are equal,} \\ b^2 &< 4ac, \text{ both roots are imaginary.} \end{aligned}$$

Logarithms

Definition.—If $a^x = N$, then $x = \log_a N$ (read as : log, to the base a , of N) ; *i.e.*, the log to base a of N is the power to which a must be raised to produce N .

$$\begin{aligned} \text{e.g.,} \quad 3 &= \log_2 8, \text{ since } 2^3 = 8 \\ \text{similarly,} \quad \frac{1}{3} &= \log_8 2 \\ \text{and} \quad 0.3010 &= \log_{10} 2 \end{aligned}$$

Antilogs.—If $x = \log_a N$ (*i.e.*, $a^x = N$), then $N = \text{antilog}_a x$ (read as : antilog, to base a , of x).

Multiplication by logs.—By definition, if $a^x = N$ and $a^y = M$, then :—

$$\begin{aligned} NM &= a^x \times a^y = a^{x+y}, \\ \text{i.e.,} \quad \log_a (NM) &= x + y = \log_a N + \log_a M. \quad (9) \end{aligned}$$

$$\text{Similarly} \quad \log_a \frac{M}{N} = \log_a M - \log_a N. \quad (10)$$

$$\text{Powers.}— \quad \log_a M^n = n \log_a M \quad (11)$$

$$\log_a \frac{1}{M} = \log_a M^{-1} = -\log_a M. \quad (12)$$

Note that the log of 1, to *any* base, is equal to 0.

Change of base.—

$$\begin{aligned} \text{Let } \log_a N &= x \\ \therefore N &= a^x \end{aligned}$$

Taking logarithms, to base b , of each side :—

$$\begin{aligned} \log_b N &= x \times \log_b a \\ \therefore \log_b N &= \log_b N \times \log_b a \\ \text{i.e.} \quad \log_a N &= \frac{\log_b N}{\log_b a} \quad (13) \end{aligned}$$

Thus the logarithm of a number to base a is equal to the logarithm of the same number to base b , divided by the logarithm of a to base b .

Use of logarithms.—If logarithms of numbers can be found, their use simplifies the processes of multiplication, division, *etc.* For if two numbers M and N have to be multiplied, their logs have to be added, which is a simpler process. For numerical calculations it is most convenient to take 10 as the base. The log of any number

between 1 and 10 will lie between 0 and 1, and the logs of such numbers are given in tables, usually to four figures. The log of *any* number can be found from these.

$$\begin{aligned}\text{Thus } \log_{10} 2 &= 0.3010 \\ \log_{10} 20 &= \log_{10} (2 \times 10) = \log_{10} 2 + \log_{10} 10 \\ &= 0.3010 + 1 = 1.3010\end{aligned}$$

Similarly, $\log_{10} 2000 = 3.3010$.

The number before the decimal point is called the "characteristic": the decimal is called the "mantissa".

The rule for calculating the log, to the base 10, of any number is to find from the tables the log to base 10 of the significant figures; this will give the mantissa. The characteristic is then written down—it will be equal to one less than the number of figures before the decimal point.

Example.—To find $\log_{10} 371.9$.

Look up $\log_{10} 3719$. The tables give the mantissa as 0.5704.

The number of figures before the decimal point is 3

$$\begin{aligned}\therefore \text{the characteristic} &= 2 \\ \therefore \log_{10} 371.9 &= 2.5704. \quad \text{Ans.}\end{aligned}$$

Numbers less than 1.—In this case the log will be negative; to simplify calculation, however, the mantissa is kept positive, and the characteristic is made negative, and numerically equal to one more than the number of noughts after the decimal point.

Thus $\log_{10} 0.03719 = \log_{10} \frac{3.719}{100} = 0.5704 - 2$, which is written $\bar{2}.5704$, the bar over the "2" indicating that this digit is negative.

Multiplication and division.

To multiply, the logs are added.

To divide, the logs are subtracted.

Example.— Evaluate $\frac{13.25 \times 0.00137}{0.1925}$

$$\begin{array}{lll}\text{From the tables:} & \log_{10} 13.25 & = 1.1222 \\ \text{and:} & \log_{10} 0.00137 & = \bar{3}.1367\end{array}$$

$$\begin{array}{lll}\text{On adding:} & \log_{10} (13.25 \times 0.00137) & = \bar{2}.2589 \\ \text{From the tables:} & \log_{10} 0.1925 & = \bar{1}.2844\end{array}$$

$$\text{On subtracting:} \quad \log_{10} \frac{13.25 \times 0.00137}{0.1925} = \bar{2}.9745$$

$$\frac{13.25 \times 0.00137}{0.1925} = \text{antilog}_{10} \bar{2}.9745$$

From the tables, $\text{antilog}_{10} \bar{2}.9745 = 0.0943$. *Ans.*

Indices.—To obtain any power of a number, its log must be multiplied by the power.

Example.— Evaluate $(2 \cdot 38)^7$ by logs.

$$\log_{10} 2 \cdot 38 = 0 \cdot 3766$$

$$\text{Multiplying by } 7: \quad \underline{\quad 7}$$

$$\log_{10} (2 \cdot 38)^7 = \underline{2 \cdot 6362}$$

$$\therefore (2 \cdot 38)^7 = \text{antilog}_{10} 2 \cdot 6362 = 432 \cdot 7 \quad \text{Ans.}$$

Roots are similarly found.

Example.— Evaluate $\sqrt[4]{0 \cdot 0892}$ by logs.

$$\sqrt[4]{0 \cdot 0892} = (0 \cdot 0892)^{\frac{1}{4}}$$

$$\log 0 \cdot 0892 = \bar{2} \cdot 9504.$$

Some way must be found of dividing the $\bar{2}$ by 4. This is done by so expressing it, that the negative portion is a multiple of 4. Thus $\frac{1}{4} \times \bar{2} \cdot 9504 = \frac{1}{4} \times (-4 + 2 \cdot 9504) = -1 + 0 \cdot 7376 = \bar{1} \cdot 7376$

$$\sqrt[4]{0 \cdot 0892} = \text{antilog } \bar{1} \cdot 7376 = 0 \cdot 5466. \quad \text{Ans.}$$

Summations

The sign Σ (Greek capital letter sigma) is used to signify summation, and the limits (if any) over which summation is to be effected are indicated above and below it.

For example :—

$$\sum_{r=1}^{r=n} r^2 = 1^2 + 2^2 + 3^2 + \dots + n^2$$

$$\sum_{r=3}^{r=5} x^2 = 3^2 + 4^2 + 5^2 = 216$$

Arithmetical progression.—e.g., 1, 4, 7, 10, 13,

General form :— $a, (a + d), (a + 2d), \dots$

The r^{th} term is $a + (r - 1)d$

Sum of n terms is : $\sum_{r=1}^{r=n} [a + (r - 1)d] = \frac{1}{2}n [2a + (n - 1)d]$

$$= \frac{1}{2} \times (\text{number of terms}) \times (\text{sum of first and last terms}). \quad (14)$$

Geometrical progression.—e.g., 1, 3, 9, 27, 81,

General form :— a, ax, ax^2, \dots The r^{th} term is ax^{r-1}

Sum of n terms is :— $\sum_{r=1}^{r=n} ax^{r-1} = \frac{a(x^n - 1)}{x - 1}$ (15)

If the numerical value of x is less than 1 (written $|x| < 1$), this sum tends to $\frac{a}{1 - x}$ as the number of terms increases.

Thus the sum of this series to infinity is given by :—

$$\sum_{r=1}^{r=\infty} ax^{r-1} = \frac{a}{1 - x} \quad (16)$$

Miscellaneous summations.

$$\sum_{r=1}^n r^2 = \frac{n}{6}(n+1)(2n+1) \quad (17)$$

$$\sum_{r=1}^n r^3 = \left[\frac{n}{2}(n+1)\right]^2 \quad (18)$$

$$\sum_{r=1}^n r(r+1) = \frac{n}{3}(n+1)(n+2) \quad (19)$$

Means

The arithmetic mean of two quantities a and b is $\frac{a+b}{2}$.

If there are n quantities a, b, c, d, \dots , their arithmetic mean is :—

$$\frac{a + b + c + d + \dots}{n}$$

The geometric mean of two quantities a and b is $\sqrt{a \cdot b}$, i.e., the square root of their product.

Functional notation

Expressions such as $x^2 + 2x + 3$, $x - \frac{1}{x}$, $\sqrt{x^2 - 2}$, are expressions involving x ; that is, their value depends on the value of x . Such expressions are known as "functions" of x .

It is useful to have a general notation for any function of x ; hence a function of x is written as $f(x)$ or $F(x)$ or $\varphi(x)$.

Thus the equation :—

$$y = x^2 + 2x + 3$$

becomes :—

$$y = f(x)$$

where :—

$$f(x) \text{ stands for } x^2 + 2x + 3.$$

This notation is extended to give the value of the function when x assumes some particular value,—e.g., $f(2)$ is the value of $f(x)$ when $x = 2$.

If :—

$$f(x) = x^2 + 2x + 3$$

then :—

$$f(2) = 2^2 + 2 \cdot 2 + 3 = 11.$$

similarly :—

$$f(3) = 3^2 + 2 \cdot 3 + 3 = 18.$$

and :—

$$f(0) = 0 + 0 + 3 = 3.$$

GRAPHS

By drawing two *axes*, the position of any point in a plane may be fixed by its two "co-ordinates". These two axes are known as the x -axis (denoted by Ox), and the y -axis (denoted by Oy). The point O is known as the origin.

If PN is perpendicular to Ox , as shown in Fig. 23, then the “ x -co-ordinate” of P is $ON = x$, and the y -co-ordinate is $NP = y$. The point P is referred to as the point (x, y) . x is considered negative if P lies to the left of Oy ; similarly, y is negative if P is below Ox . Thus to any point in the plane there corresponds one set of two numbers, and vice versa.

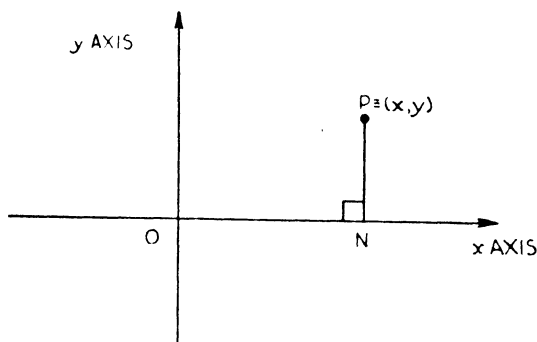


FIG. 23.—Use of co-ordinates x, y to determine position of a point P .

If the values of x and y for the point P are unrestricted, P may be anywhere in the plane. If, however, the values are restricted by stating some definite relationship between them, P can lie only in certain positions. For a normal relationship between x and y (in the form of an equation) P will, in general, lie on a curve; and a curve of some sort exists for every equation. Much information can be obtained from a study of these curves or “graphs”.

There are two types of equation: an “explicit” equation, such as $y = \frac{3x^2 + 5}{1 - x}$, where y is given at once as some “function” of x ; and an “implicit” equation, such as $3x^2y + 5y^3 - 4x = 3$, where y is not given *directly* in terms of x .

Linear equations

An equation of the form $ax + by + c = 0$ always represents a straight line. To draw the line, it is best to find two points on it, and usually the easiest to find are those where $x = 0$ and where $y = 0$.

For example, consider the equation $2x - 3y = 6$.

If $x = 0, y = -2 \quad \therefore (0, -2)$ is on the line.

If $y = 0, x = 3 \quad \therefore (3, 0)$ is on the line.

The graph can now be drawn as a straight line through these two points (Fig. 24).

The graph may be verified; for example, the point $(6, 2)$ should be on it, since $2 \times 6 - 3 \times 2 = 12 - 6 = 6$.

Solution of simultaneous equations.—Graphs may be used to solve simultaneous equations,

$$\text{e.g. } 2x - 3y = 6$$

$$\text{and } x - y = 6.$$

Draw the graph of $x - y = 6$ on the same axes as the first, by drawing a straight line through the points $(6, 0)$ and $(0, -6)$ (Fig. 24).

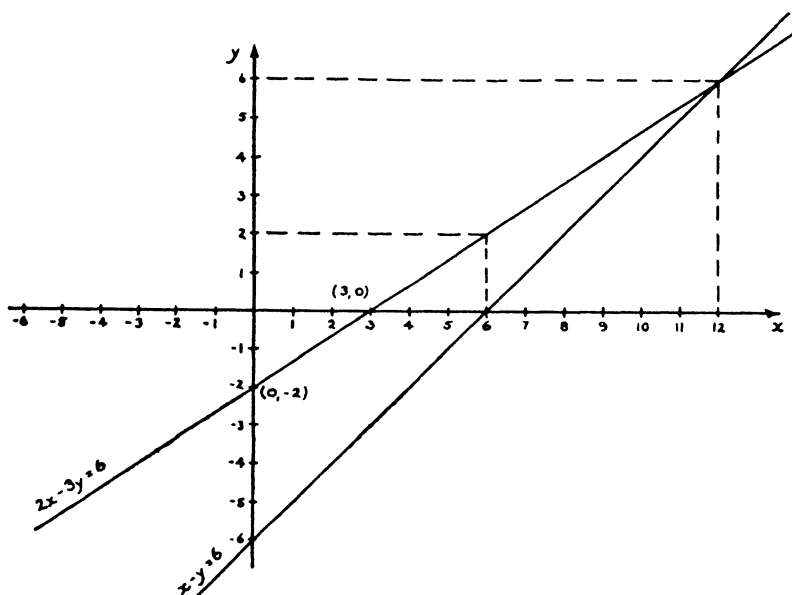


FIG. 24.—Graphs of $x - y = 6$ and $2x - 3y = 6$.

The point which represents the solution of the two equations must satisfy each equation, *i.e.* it must lie on each line. The only point which does this is, of course, the point of intersection—in this case $(12, 6)$. Hence " $x = 12, y = 6$ " is the solution.

Other equations

In some cases, the form of the equation will indicate the shape of the curve. Consider, for example, the equation $x^2 + y^2 = a^2$.

This may be written as $\sqrt{x^2 + y^2} = a$.

But $\sqrt{x^2 + y^2}$ is the distance of the point P from the origin; therefore the equation represents a circle with centre at the origin and radius a .

Similarly $(x - l)^2 + (y - m)^2 = a^2$ is a circle with centre (l, m) and radius a .

Asymptotes

Many curves approach infinity along some straight line, as in Fig. 25.

The straight line is known as an "asymptote": note that a curve which goes to infinity along an asymptote must also return from infinity along it.

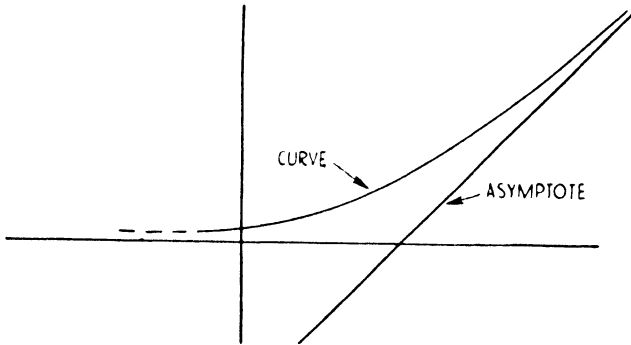


FIG. 25.—Asymptote.

To find the asymptotes of any curve, the condition which makes x or y infinite must first be found; an approximate form of the equation for large values of x or y can then be found.

General rules for plotting curves

1. Plot all points where x or y are zero or infinite.
2. Insert asymptotes, if any, finding out on which side the curve lies.
3. Plot any obviously important points.
4. Note any symmetry that may exist.
5. Avoid giving x or y various numerical values at random.

Example 1.—

Plot the graph of:— $y = x - \frac{1}{x}$

When $x = \pm 1$, $y = 0$, giving two points.

$x = 0$ makes y infinite, hence $x = 0$ is an asymptote. Find on which side of the asymptote the curve lies. If x is slightly greater than zero, y will be large and negative; hence the curve will go to infinity downwards along the right-hand side of the y axis. Similarly, if x is slightly less than zero, y will be large and positive, and the curve will therefore go up to infinity along the left-hand side of the y axis.

When $x \rightarrow \infty$, y also $\rightarrow \infty$, but if x is large $y \approx x$, and hence $y = x$ is an asymptote. By the same method as in the last paragraph, it can be shown that the curve lies below the asymptote if x is positive and above it if x is negative.

Drawing in these points and asymptotes, Fig. 26a is obtained. It can easily be seen that the complete curve will be of the form

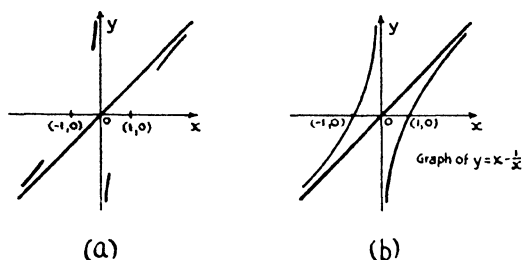


FIG. 26.—Graph of $y = x - \frac{1}{x}$

shown in Fig. 26b. Note that it is in two parts; this curve is known as a hyperbola.

Example 2.—

Plot the graph of:— $y = \frac{x-4}{(x-2)^2(x-3)}$

When $x = 4$, $y = 0$, therefore $(4, 0)$ is on the curve. y also equals 0 if $x \rightarrow \pm \infty$; and, whether x is positive or negative, y will be positive for sufficiently large numerical values of x . Hence $y = 0$ is an asymptote, and the curve is above it on each side.

When $x = 0$, $y = \frac{-4}{-12} = +\frac{1}{3}$, therefore $(0, \frac{1}{3})$ is on the curve.

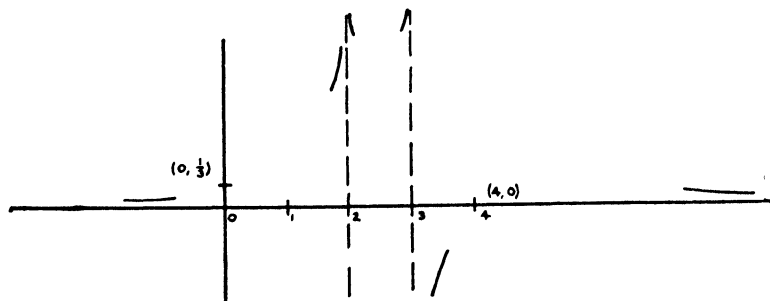


FIG. 27 (a).—Graph of $y = \frac{x-4}{(x-2)^2(x-3)}$

When $x = 2$ or 3 , $y = \infty$, therefore $x = 2$ and $x = 3$ are asymptotes.

If x is just greater or just less than 2 , y is always positive. The curve therefore goes to infinity, and returns, along the positive half of the asymptote $x = 2$.

If x is just less than 3 , y is positive, while if x is just greater than 3 , y is negative; the curve therefore goes up to infinity along the left-hand side of the asymptote $x = 3$, and goes down to "minus infinity" along the right-hand side.

The above fixes the parts of the curve shown in Fig. 27a; from these the rest of the curve can easily be joined up to give Fig. 27b.

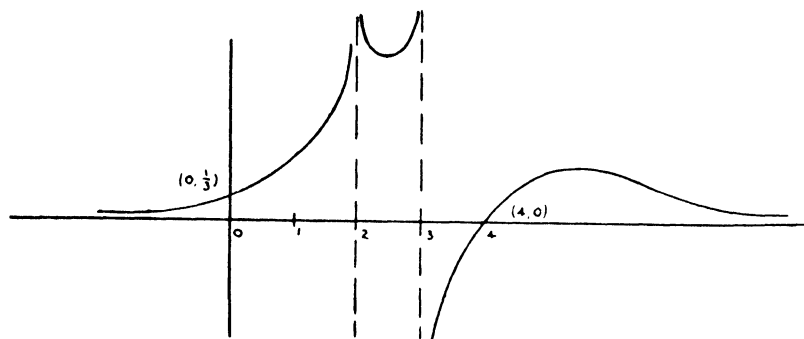


FIG. 27 (b).—Graph of $y = \frac{x-4}{(x-2)^2(x-3)}$

Summary of equations of commonly occurring curves (See Fig. 28)

1. Straight line, parallel to x -axis $y = k$
2. Straight line, of slope m , passing through $(x = 0, y = b)$ $y = mx + b$
3. Straight line, of slope m , passing through $(x = a, y = 0)$ $y = m(x - a)$
4. Straight line, passing through $(x = a, y = 0)$ and $(x = 0, y = b)$ $\frac{x}{a} + \frac{y}{b} = 1$
5. Circle, radius r , centre at the origin $x^2 + y^2 = r^2$
6. Circle, radius r , centre (a, b) $(x - a)^2 + (y - b)^2 = r^2$
7. Ellipse, semi-axes c and d , centre at the origin $\frac{x^2}{c^2} + \frac{y^2}{d^2} = 1$

8. Ellipse, semi-axes c and d , centre (a, b) with axes parallel to the co-ordinate axes :— $\frac{(x - a)^2}{c^2} + \frac{(y - b)^2}{d^2} = 1$
9. Parabola, vertex at the origin, with axis along x -axis :— $y^2 = 4ax$
10. Rectangular hyperbola, with axes as asymptotes, centre at the origin :— $xy = k^2$
11. Hyperbola, with foci on x -axis and centre at the origin :— $\frac{x^2}{a^2} - \frac{y^2}{b^2} = 1$
12. General form of equation of conic section :— $ax^2 + 2hxy + by^2 + 2gx + 2fy + c = 0$

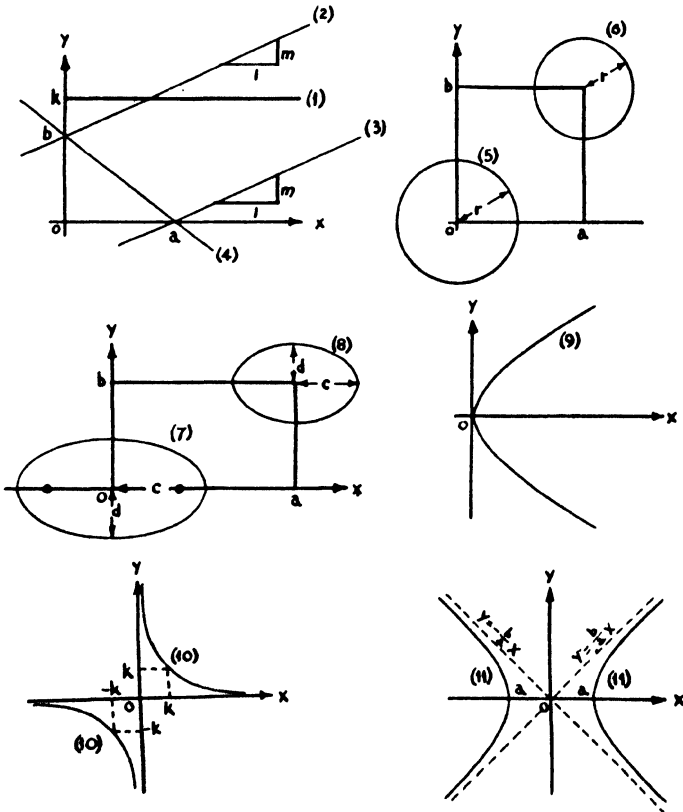


FIG. 28.—Commonly occurring curves.

TRIGONOMETRY

Angular measure

An angle is a measure of rotation ; the usual units are degrees, where one degree is $\frac{1}{360}$ of a complete revolution. As a general rule, angles are measured anti-clockwise from a horizontal reference line, as in Fig. 29, where OA is the reference line, and θ is the angle AOP , shown thus $\sphericalangle AOP$.

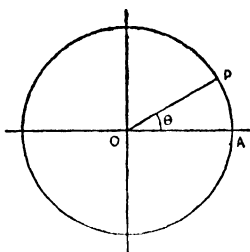


FIG. 29.—Angular measure.

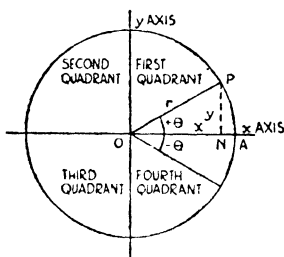


FIG. 30.—The four quadrants and the trigonometrical ratios.

A complete revolution is divided into 4 “quadrants” each of 90° , by two lines at right angles to one another passing through the centre.

In any circle, the length of the arc AP is directly proportional to $\sphericalangle AOP$. As the complete circumference = $2\pi r$, then, by proportion,

$$\text{arc } AP = \frac{2\pi r \theta}{360} \tag{20}$$

where θ is in degrees.

The choice of degrees as units is inconvenient in many theoretical problems ; the unit used in such cases is the “radian”. One radian is defined as the angle subtended at the centre of a circle by an arc whose length is equal to the radius of the circle. Note that $360^\circ = 2\pi$ radians ; this gives 1 radian = $\frac{180}{\pi}$ degrees = $57^\circ 17' 44''$.

Using radians, the arc AP corresponding to an angle θ is :—

$$\text{arc } AP = r \times \theta \tag{21}$$

which is simpler than equation 20 using degrees for units.

The trigonometrical ratios

All right-angled triangles having one angle equal to θ will be similar, and the ratios of their sides will be equal. These ratios are very useful, and form the basis of trigonometry. The definitions of the various ratios hold for all angles, and are as follows.

Draw $\sphericalangle AOP$, and draw PN perpendicular to OA as in Fig. 30.

Let $OP = r$, $PN = y$, and $ON = x$.

The *sine* of the angle θ is then defined as the ratio of the length of PN to that of OP , i.e., $\frac{y}{r}$; this is written as:—

$$\sin \theta = \frac{PN}{OP} = \frac{y}{r} \quad (22)$$

When P lies above the x -axis, y is positive, and therefore $\sin \theta$ is also positive; when P lies below the x -axis, y is negative, and therefore $\sin \theta$ is negative. Note that r is always considered positive.

The *cosine* of the angle θ is defined as the ratio of the length of ON to that of OP , i.e., $\frac{x}{r}$, and is written as:—

$$\cos \theta = \frac{ON}{OP} = \frac{x}{r} \quad (23)$$

Note that $\frac{x}{r}$ is also equal to $\sin\left(\frac{\pi}{2} - \theta\right)$ so that:—

$$\cos \theta = \sin\left(\frac{\pi}{2} - \theta\right) \quad (24)$$

When P lies to the left of Oy , x is negative, and therefore $\cos \theta$ is also negative.

The *tangent* of the angle θ is defined as the ratio of the length of PN to that of ON , i.e., $\frac{y}{x}$; then:—

$$\tan \theta = \frac{PN}{ON} = \frac{y}{x} \quad (25)$$

Note that : $\tan \theta = \frac{\sin \theta}{\cos \theta} \quad (26)$

since $\frac{\sin \theta}{\cos \theta} = \frac{y/r}{x/r} = \frac{y}{x} = \tan \theta$

Signs of the trigonometrical ratios.—If P is below Ox , PN (and therefore $\sin \theta$) will be negative, and if P is to the left of the vertical axis Oy , ON (and therefore $\cos \theta$) will be negative. Thus in the first quadrant, all the ratios are positive. In the second, only the sine is positive; in the third, only the tangent, and in the fourth, only the cosine (*see* Fig. 31). It is important to remember this when calculating ratios of angles outside the first quadrant.

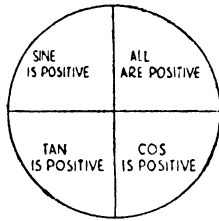


FIG. 31.—Signs of the ratios in the four quadrants.

Three other ratios are :—

$$\text{cosecant } \theta = \text{cosec } \theta = \frac{1}{\sin \theta} = \frac{r}{y} = \sec \left(\frac{\pi}{2} - \theta \right) \quad (27)$$

$$\text{secant } \theta = \sec \theta = \frac{1}{\cos \theta} = \frac{r}{x} = \text{cosec} \left(\frac{\pi}{2} - \theta \right) \quad (28)$$

$$\text{cotangent } \theta = \cot \theta = \frac{1}{\tan \theta} = \frac{x}{y} = \tan \left(\frac{\pi}{2} - \theta \right) \quad (29)$$

Angles greater than 90° ($\frac{\pi}{2}$ radians)

Tables give the values of ratios for angles between 0 and 90° . To calculate ratios of an angle outside this range, it must be written in the form $90^\circ + \theta$, $180^\circ \pm \theta$, $270^\circ \pm \theta$, or $360^\circ \pm \theta$, where θ is an angle between 0 and 90° . One of the following relationships may then be used :—

(a) The ratios of $180^\circ \pm \theta$, $360^\circ \pm \theta$, *etc.*, are the same as the ratios of θ , with a possible change of sign.

(b) For $90^\circ \pm \theta$, $270^\circ \pm \theta$, *etc.*, sin becomes cos, cos becomes sin, tan becomes cot, and so on, with a possible change of sign.

(c) The ambiguity in (a) and (b) as regards the sign can be cleared up by considering the quadrant in which the original angle lies.

Example.—

Find $\sin (180^\circ + \theta)$.

$$\sin (180 + \theta) \text{ from (a) } = \pm \sin \theta.$$

But $180^\circ + \theta$ is in 3rd quadrant,

$$\therefore \sin (180^\circ + \theta) \text{ is negative,}$$

$$\therefore \sin (180^\circ + \theta) = -\sin \theta$$

In practice this process is carried out mentally, thus :—

$$\cos (152^\circ) = \cos (180^\circ - 28^\circ) = -\cos 28^\circ = -0.8829$$

or alternatively :—

$$\cos (152^\circ) = \cos (90^\circ + 62^\circ) = -\sin 62^\circ = -0.8829$$

This is illustrated in Fig. 32, where $OP = 1$.

Obviously, it is easier, if possible, to use the $180^\circ \pm$ and $360^\circ \pm$ forms than the $90^\circ \pm$ and $270^\circ \pm$ as they do not involve any change of ratio.

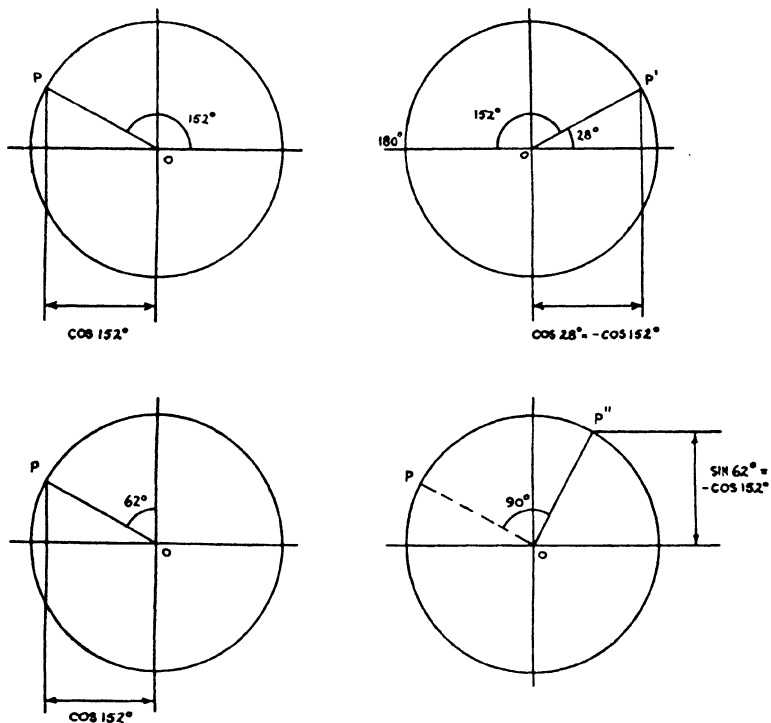


FIG. 32.—Example of ratios outside the first quadrant.

The inverse functions

“The angle whose sine is x ” is written as “ $\sin^{-1} x$ ”; similarly, “ $\cos^{-1} x$ ” means “the angle whose cosine is x ”. It is important not to confuse “ $\sin^{-1} x \equiv$ the angle whose sine is x ” with “ $(\sin x)^{-1} = \left(\frac{1}{\sin x}\right)$ ”. To avoid any possibility of confusion, the inverse ratios are sometimes written as “arc sin”, “arc cos”, *etc.*

Negative angles

Since θ is taken, by convention, as being measured in an anti-clockwise direction from the x -axis, “ $-\theta$ ” represents an angle equal to θ , but measured clockwise from the x -axis, *i.e.*, the same

as $(360^\circ - \theta)$. $\sin(-\theta)$ is therefore equal to $-\sin \theta$,
 $\cos(-\theta) = +\cos \theta$, and $\tan(-\theta) = -\tan \theta$.

Particular angles

The ratios of angles such as $0^\circ, 90^\circ, 180^\circ, \text{etc.}$, also $30^\circ, 45^\circ, 60^\circ$, can be calculated from first principles.

For 0° and 90° , the limiting case of a triangle must be taken, when one side becomes zero and the other two both equal to the radius of the circle. Hence $\cos 0^\circ = \sin 90^\circ = 1$;

$$\sin 0^\circ = \cos 90^\circ = 0 ; \tan 0^\circ = 0 ; \tan 90^\circ = \infty.$$

45° .—If one angle of a right-angled triangle is 45° , the other must also be 45° ; hence the triangle is isosceles—*i.e.*, the two sides adjacent to the right angle are equal. Hence by Pythagoras' theorem, each must be $\frac{1}{\sqrt{2}}$ of the hypotenuse (*see* Fig. 33).

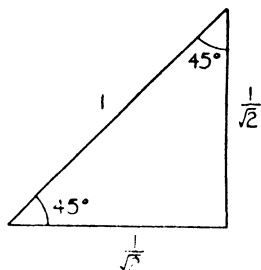


FIG. 33.—The trigonometrical ratios of 45° .

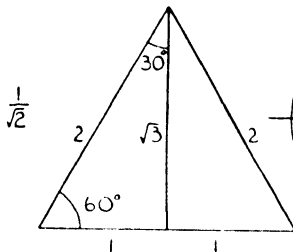


FIG. 34.—The trigonometrical ratios of 30° and 60° .

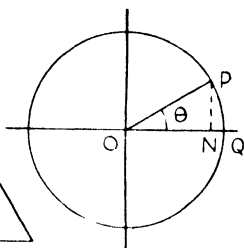


FIG. 35. — The trigonometrical ratios of very small angles.

Thus $\sin 45^\circ = \cos 45^\circ = \frac{1}{\sqrt{2}} = 0.7071$, and $\tan 45^\circ = 1$.

Similarly, by bisecting one of the angles of an equilateral triangle (*see* Fig. 34), it can be shown that :—

$$\sin 30^\circ = \cos 60^\circ = \frac{1}{2} = 0.5 ; \cos 30^\circ = \sin 60^\circ = \frac{\sqrt{3}}{2} = 0.8660$$

$$\tan 30^\circ = \frac{1}{\sqrt{3}} = 0.5774 \qquad \tan 60^\circ = \sqrt{3} = 1.7321$$

Very small angles

Referring to Fig. 35, it can be seen that if θ be very small, the arc PQ ($= OP \cdot \theta$) is roughly equal to PN ($= OP \cdot \sin \theta$). Also ON is roughly equal to OP . For small angles, one can therefore take $\sin \theta$ and $\tan \theta$ as approximately equal to θ (where θ is expressed in radians), and $\cos \theta$ as approximately equal to 1. The smaller the angle, the more accurate is this approximation ; the error is less than 2 per cent. for angles up to 20° for sines, and up to 13° for tangents.

General forms

The angles satisfying the equation :—

$$\sin \theta = x$$

are given by $\theta = n\pi + (-1)^n \sin^{-1} x$

where n is any integer.

Similarly, the angles satisfying the equation :—

$$\cos \theta = x$$

are given by $\theta = 2n\pi \pm \cos^{-1} x$

And the angles satisfying the equation :—

$$\tan \theta = x$$

are given by $\theta = n\pi + \tan^{-1} x$

TABLE I
The trigonometrical ratios for particular angles.

Angle in radians : Angle in degrees :	0	$\frac{\pi}{6}$ 30°	$\frac{\pi}{4}$ 45°	$\frac{\pi}{3}$ 60°	$\frac{\pi}{2}$ 90°	$\frac{2\pi}{3}$ 120°	$\frac{3\pi}{4}$ 135°	$\frac{5\pi}{6}$ 150°	π 180°	$\frac{3\pi}{2}$ 270°	2π 360°
Sine ..	0	$\frac{1}{2}$	$\frac{1}{\sqrt{2}}$	$\frac{\sqrt{3}}{2}$	+1	$\frac{\sqrt{3}}{2}$	$\frac{1}{\sqrt{2}}$	$\frac{1}{2}$	0	-1	0
Cosine ..	1	$\frac{\sqrt{3}}{2}$	$\frac{1}{\sqrt{2}}$	$\frac{1}{2}$	0	$-\frac{1}{2}$	$-\frac{1}{\sqrt{2}}$	$-\frac{\sqrt{3}}{2}$	-1	0	+1
Tangent ..	0	$\frac{1}{\sqrt{3}}$	1	$\sqrt{3}$	∞	$-\sqrt{3}$	-1	$-\frac{1}{\sqrt{3}}$	0	∞	0

Graphs of ratios

It is instructive at this stage to consider the graphs of the ratios ; these are plotted in Fig. 36. Note that $\sin \theta$ and $\cos \theta$ lie between plus and minus one for all angles, but that $\tan \theta$ assumes all values between plus and minus infinity.

Identities

Certain identities connecting the various trigonometrical ratios are important. They are :—

$$\sin^2 \theta + \cos^2 \theta = 1 \quad (30)$$

$$\sec^2 \theta - \tan^2 \theta = 1 \quad (31)$$

$$\operatorname{cosec}^2 \theta - \cot^2 \theta = 1 \quad (32)$$

where θ may be any angle.

These may be proved from Pythagoras' theorem, for, by definition :—

$$\sin \theta = \frac{y}{r} \text{ and } \cos \theta = \frac{x}{r} \text{ (see Fig. 30).}$$

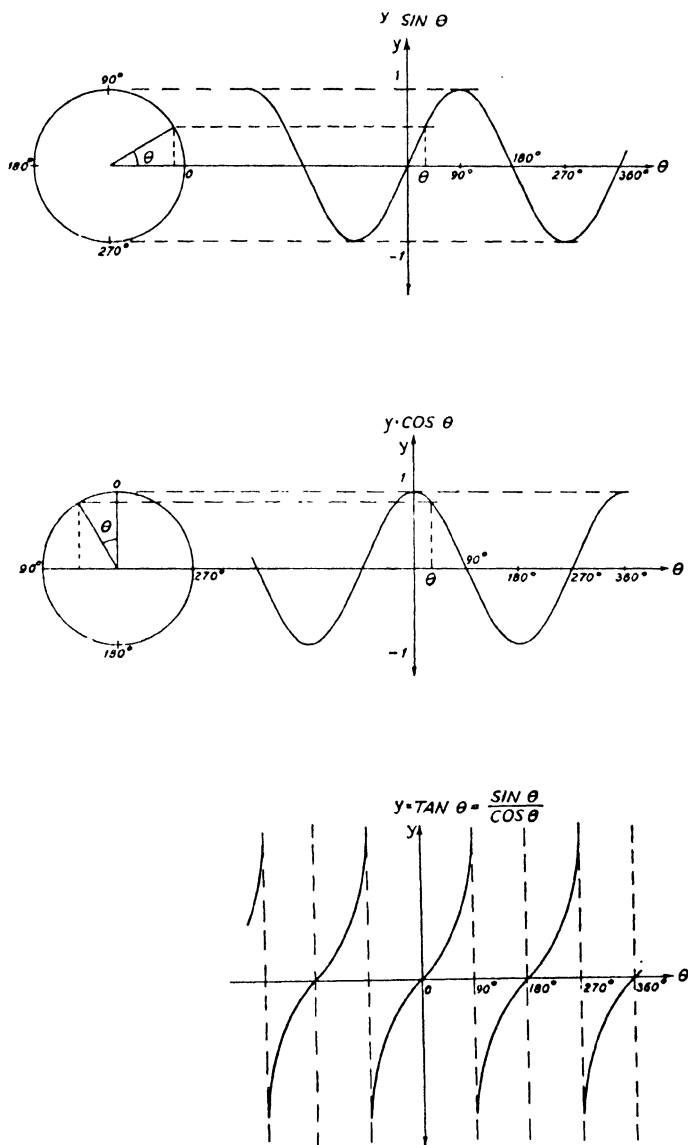


FIG 36.—Graphs of trigonometrical ratios.

But x, y, r are the sides of a right-angled triangle,

$$\therefore x^2 + y^2 = r^2$$

$$\text{i.e., } r^2 \cos^2 \theta + r^2 \sin^2 \theta = r^2$$

$$\text{i.e., } \cos^2 \theta + \sin^2 \theta = 1$$

The other identities are obtained by dividing both sides of this equation by $\cos^2 \theta$ and $\sin^2 \theta$ respectively.

Multiple angle formulae

It is often useful to be able to express the trigonometrical ratios of the sum of two angles in terms of the ratios of each individual angle. This may be done as follows: it will be proved that:—

$$\sin(A + B) = \sin A \cos B + \cos A \sin B.$$

(See Fig. 37)

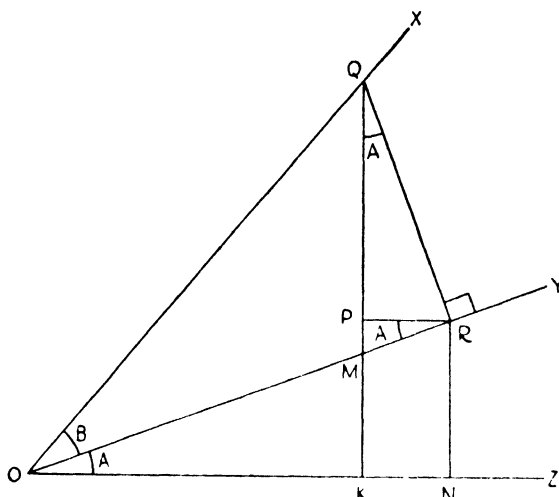


FIG. 37.—Illustrating formula for $\sin(A + B)$

Draw :— $\angle YOZ = A$

$\angle XOY = B$

So $\angle XOZ = A + B$

Q is any point on OX .

Draw QK perpendicular to OZ , cutting OY in M .

“ QR “ “ OY

“ RN “ “ OZ

“ RP “ “ QK

As $\angle K = 90^\circ$, $\angle OMK = 90^\circ - A = \angle QMR$

As $\angle QRM = 90^\circ$, $\angle MQR = 90^\circ - \angle QMR = 90^\circ - (90^\circ - A) = A$

Similarly, it will be seen that $\angle PRM = A$

$$\sin(A + B) = \frac{QK}{OQ} = \frac{QP}{OQ} + \frac{PK}{OQ}$$

But $QP = QR \cos \angle PQR = QR \cos A$

and $PK = RN = OR \sin \angle NOR = OR \sin A$

$$\therefore \sin(A + B) = \frac{QR}{OQ} \cos A + \frac{OR}{OQ} \sin A$$

But $\frac{QR}{OQ} = \sin B$ and $\frac{OR}{OQ} = \cos B$

$$\therefore \sin(A + B) = \sin A \cos B + \cos A \sin B \quad (33)$$

Similarly, it may be shown that :—

$$\sin(A - B) = \sin A \cos B - \cos A \sin B \quad (34)$$

$$\cos(A + B) = \cos A \cos B - \sin A \sin B \quad (35)$$

$$\cos(A - B) = \cos A \cos B + \sin A \sin B \quad (36)$$

By adding (33) and (34) :—

$$2 \sin A \cos B = \sin(A + B) + \sin(A - B) \quad (37)$$

By subtracting (34) from (33) :—

$$2 \cos A \sin B = \sin(A + B) - \sin(A - B) \quad (38)$$

By adding (35) and (36) :—

$$2 \cos A \cos B = \cos(A + B) + \cos(A - B) \quad (39)$$

By subtracting (35) from (36) :—

$$2 \sin A \sin B = \cos(A - B) - \cos(A + B) \quad (40)$$

(37), (38), (39) and (40) are useful for expressing the product of two ratios as the sum of two ratios.

By letting $A = \frac{C + D}{2}$ and $B = \frac{C - D}{2}$, these equations become :—

$$\sin C + \sin D = 2 \sin \frac{C + D}{2} \cos \frac{C - D}{2} \quad (41)$$

$$\sin C - \sin D = 2 \cos \frac{C + D}{2} \sin \frac{C - D}{2} \quad (42)$$

$$\cos C + \cos D = 2 \cos \frac{C + D}{2} \cos \frac{C - D}{2} \quad (43)$$

$$\cos C - \cos D = 2 \sin \frac{C + D}{2} \sin \frac{D - C}{2} = -2 \sin \frac{C + D}{2} \sin \frac{C - D}{2} \quad (44)$$

These formulae are useful for expressing the sum of two ratios as the product of two ratios.

The formulae for $\tan (A \pm B)$ are :—

$$\tan (A + B) = \frac{\tan A + \tan B}{1 - \tan A \tan B} \quad (45)$$

$$\tan (A - B) = \frac{\tan A - \tan B}{1 + \tan A \tan B} \quad (46)$$

Double angle formulae.

By putting $A = B$ in the above, the following expressions are derived for ratios of $2A$:—

$$\sin 2A = 2 \cdot \sin A \cdot \cos A \quad (47)$$

$$\cos 2A = \cos^2 A - \sin^2 A \quad (48)$$

$$\left. \begin{aligned} &= 2 \cos^2 A - 1 \\ &= 1 - 2 \sin^2 A \end{aligned} \right\} \text{ since } \cos^2 A + \sin^2 A = 1$$

$$\tan 2A = \frac{2 \tan A}{1 - \tan^2 A} \quad (49)$$

The following are useful forms of (48) :—

$$\sin^2 A = \frac{1}{2} (1 - \cos 2A) \quad (50)$$

$$\cos^2 A = \frac{1}{2} (1 + \cos 2A) \quad (51)$$

Relationships of this nature facilitate the solution of many problems encountered in telecommunication engineering; this is illustrated by the following examples, which prove three of the relationships used later in this book.

Example 1.—

Express $A \sin \omega t + B \cos \omega t$ in the form :

$$r \cdot \sin (\omega t + \theta)$$

Let :— $A = r \cdot \cos \theta$

and :— $B = r \cdot \sin \theta$

Squaring and adding these two equations,

$$A^2 + B^2 = r^2$$

$$\therefore r = \sqrt{A^2 + B^2}$$

Dividing the second equation by the first,

$$\frac{B}{A} = \tan \theta$$

Then

$$\begin{aligned} A \sin \omega t + B \cos \omega t &= r \cdot \cos \theta \cdot \sin \omega t + r \cdot \sin \theta \cdot \cos \omega t \\ &= r \cdot \sin (\omega t + \theta) \end{aligned}$$

$$= \sqrt{A^2 + B^2} \cdot \sin (\omega t + \theta) \quad \text{Ans.}$$

$$\text{where } \theta = \tan^{-1} \frac{B}{A}$$

Example 2.—

Prove that $\tan^{-1} A + \tan^{-1} B = \tan^{-1} \left(\frac{A + B}{1 - AB} \right)$

Put $x = \tan^{-1} A$, that is, $\tan x = A$

and $y = \tan^{-1} B$, that is, $\tan y = B$

Then

$$\begin{aligned} \tan(\tan^{-1} A + \tan^{-1} B) &= \tan(x + y) \\ &= \frac{\tan x + \tan y}{1 - \tan x \tan y} \\ &= \frac{A + B}{1 - AB} \end{aligned}$$

$$\therefore \tan^{-1} A + \tan^{-1} B = \tan^{-1} \left(\frac{A + B}{1 - AB} \right) \quad \text{Q.E.D.}$$

Similarly it can be proved that:—

$$\tan^{-1} A - \tan^{-1} B = \tan^{-1} \left(\frac{A - B}{1 + AB} \right)$$

Example 3.—Prove that:—

$$\tan^{-1} \frac{1}{A} - \tan^{-1} \frac{1}{B} = \tan^{-1} B - \tan^{-1} A$$

Let:— $A = \tan \theta$, so that $\theta = \tan^{-1} A$

$$\begin{aligned} \text{Then:—} \quad \frac{1}{A} &= \frac{1}{\tan \theta} = \cot \theta \\ &= \tan \left(\frac{\pi}{2} - \theta \right) \end{aligned}$$

$$\begin{aligned} \therefore \tan^{-1} \frac{1}{A} &= \frac{\pi}{2} - \theta \\ &= \frac{\pi}{2} - \tan^{-1} A \end{aligned}$$

$$\text{Similarly} \quad \tan^{-1} \frac{1}{B} = \frac{\pi}{2} - \tan^{-1} B$$

Hence

$$\tan^{-1} \frac{1}{A} - \tan^{-1} \frac{1}{B} = \tan^{-1} B - \tan^{-1} A$$

Triangle formulae

These apply to any triangle having angles A, B, C , and sides a, b, c (see Fig. 38).

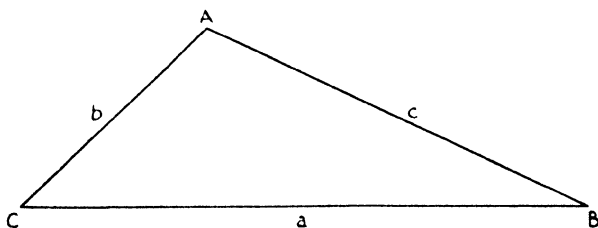


FIG. 38.—Triangle with sides abc and angles ABC .

$$\frac{a}{\sin A} = \frac{b}{\sin B} = \frac{c}{\sin C} \quad (\text{The "sine rule"}) \quad (52)$$

$$a^2 = b^2 + c^2 - 2bc \cos A \quad (\text{The "cosine rule"}) \quad (53)$$

$$b^2 = c^2 + a^2 - 2ca \cos B$$

$$c^2 = a^2 + b^2 - 2ab \cos C$$

$$\tan \left(\frac{A-B}{2} \right) = \frac{a-b}{a+b} \cot \frac{C}{2} \quad \text{etc.} \quad (54)$$

$$\sin \frac{A}{2} = \sqrt{\frac{(s-b)(s-c)}{bc}} \quad \text{etc.} \quad (55)$$

$$\cos \frac{A}{2} = \sqrt{\frac{s(s-a)}{bc}} \quad \text{etc.} \quad (56)$$

$$\sin A = \frac{2}{bc} \sqrt{s(s-a)(s-b)(s-c)} \quad \text{etc.} \quad (57)$$

where $s = \frac{1}{2}(a+b+c)$

Example.—

Given that, in the triangle of Fig. 38, two sides and the included angle are known, find the remaining side and angles; e.g., given $a = 20$, $b = 10$, $C = 40^\circ$, find c , A and B .

Applying the cosine rule (equation 53):—

$$\begin{aligned} c^2 &= a^2 + b^2 - 2ab \cos C \\ &= 20^2 + 10^2 - 2 \cdot 20 \cdot 10 \cos 40^\circ \\ &= 400 + 100 - 400 \cdot 0.7660 \\ &= 500 - 306.4 \\ &= 193.6 \end{aligned}$$

$$\text{i.e.,} \quad c = 13.91. \quad \text{Ans. (i)}$$

Now applying the sine rule (equation 52):—

$$\begin{aligned} \frac{a}{\sin A} &= \frac{b}{\sin B} = \frac{c}{\sin C} \\ \text{i.e.,} \quad \frac{20}{\sin A} &= \frac{10}{\sin B} = \frac{13.91}{\sin 40^\circ} \\ \therefore \sin A &= \frac{20 \sin 40^\circ}{13.91} = \frac{20 \times 0.6428}{13.91} = 0.9241 \\ \therefore A &= 67^\circ 32' \text{ or } 112^\circ 28' \end{aligned}$$

$$\text{Also} \quad \sin B = \frac{10 \sin 40^\circ}{13.91} = 0.4622$$

$$\therefore B = 27^\circ 32' \text{ or } 152^\circ 28'$$

Thus it would appear that there are two triangles having the given properties; but this is not so, for the angles A , B and C of the

triangle must satisfy the relationship : -

$$A + B + C = 180^\circ$$

and the only combination of the above angles which satisfies this result is:—

$$A = 112^\circ 28', B = 27^\circ 32' \text{ Ans. (ii \& iii)}$$

A simpler approach for finding B , having determined two possible values of A , is as follows :—

$$\begin{aligned} B &= 180^\circ - (A + C) \\ \therefore B &= 180^\circ - (67^\circ 32' + 40^\circ) \\ &\text{or } 180^\circ - (112^\circ 28' + 40^\circ) \end{aligned}$$

In this case, the correct pair of values for A and B may be selected by means of the self-evident result, that if a triangle has two unequal angles, the greater angle will be opposite the greater side.

Since $b < c$ it follows that $B < C$

$$\therefore B = 27^\circ 32' \text{ and } A = 112^\circ 28' \text{ Ans. (iii \& ii)}$$

The triangle is therefore uniquely determined as in Fig. 39.

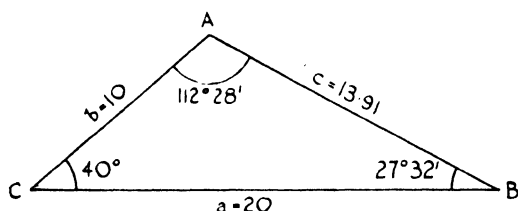


Fig. 39.—Triangle as determined in example.

An alternative approach to the same problem is to employ equation 54.

$$\begin{aligned} \tan \left(\frac{A - B}{2} \right) &= \frac{a - b}{a + b} \cot \frac{C}{2} \\ &= \frac{20 - 10}{20 + 10} \cot \frac{40^\circ}{2} \\ &= \frac{1}{3} \cot 20^\circ = 0.9158 \end{aligned}$$

$$\therefore \frac{A - B}{2} = 42^\circ 29' \text{ (no ambiguity)}$$

But
$$\frac{A + B}{2} = \frac{180^\circ - C}{2} = 70^\circ$$

Hence adding and subtracting gives :

$$A = 112^\circ 29' \text{ and } B = 27^\circ 31' \text{ Ans. (ii \& iii)}$$

Applying the sine rule

$$c = \frac{a \sin C}{\sin A}$$

$$\therefore c = 13.91 \text{ Ans. (i)}$$

BINOMIAL THEOREM

$$\begin{aligned} \text{Expansions such as } (1+x)^2 &= 1 + 2x + x^2 \\ (1+x)^3 &= 1 + 3x + 3x^2 + x^3 \end{aligned}$$

are often useful. A general form of this expansion is given by the Binomial theorem :—

$$(1+x)^n = 1 + nx + \frac{n(n-1)}{1.2}x^2 + \frac{n(n-1)(n-2)}{1.2.3}x^3 + \dots \quad (58)$$

If n is a positive integer, this is true for all values of x . It can be seen that in this case the expansion is finite, the last term being x^n . (The expansions for $(1+x)^2$ and $(1+x)^3$ may be verified.)

If n is not a positive integer, the expansion contains an infinite number of terms. It is then valid only if $-1 < x < 1$ (i.e., $|x| < 1$). In this case a series having an infinite number of terms has a finite sum. Such a series is said to be "convergent".

Factorials.—The terms of this expansion—as well as of many others—can be simplified by using the "factorial" notation. "Factorial n " is written as $\lfloor n$ or $n!$, and is defined as:—

$$\lfloor n \equiv n \times (n-1) \times (n-2) \times \dots \times 4 \times 3 \times 2 \times 1 \quad (59)$$

$$\text{Thus } \lfloor 6 = 6 \times 5 \times 4 \times 3 \times 2 \times 1 = 720$$

$$\lfloor 3 = 3 \times 2 \times 1 = 6$$

$$\lfloor 1 = 1$$

Using this notation, the Binomial expansion of equation 58 can be rewritten as:—

$$(1+x)^n = 1 + nx + \frac{n(n-1)}{\lfloor 2}x^2 + \frac{n(n-1)(n-2)}{\lfloor 3}x^3 + \dots \quad (60)$$

or alternatively:—

$$(1+x)^n = 1 + \frac{\lfloor n}{\lfloor n-1}x + \frac{\lfloor n}{\lfloor 2 \lfloor n-2}x^2 + \frac{\lfloor n}{\lfloor 3 \lfloor n-3}x^3 + \dots \quad (61)$$

Example.—Expand $(1+x)^5$

$$\begin{aligned} (1+x)^5 &= 1 + 5x + \frac{5.4}{1.2}x^2 + \frac{5.4.3}{1.2.3}x^3 + \frac{5.4.3.2}{1.2.3.4}x^4 + \frac{5.4.3.2.1}{1.2.3.4.5}x^5 \\ &= 1 + 5x + 10x^2 + 10x^3 + 5x^4 + x^5 \end{aligned}$$

This may be verified by putting $x = 1$

$$\begin{aligned} \therefore 2^5 &= 1 + 5 + 10 + 10 + 5 + 1 \\ &= 32, \text{ which is true.} \end{aligned}$$

Exponential series

This important series can be derived from the Binomial theorem.

Consider the expansion of $\left(1 + \frac{1}{n}\right)^{nx}$.

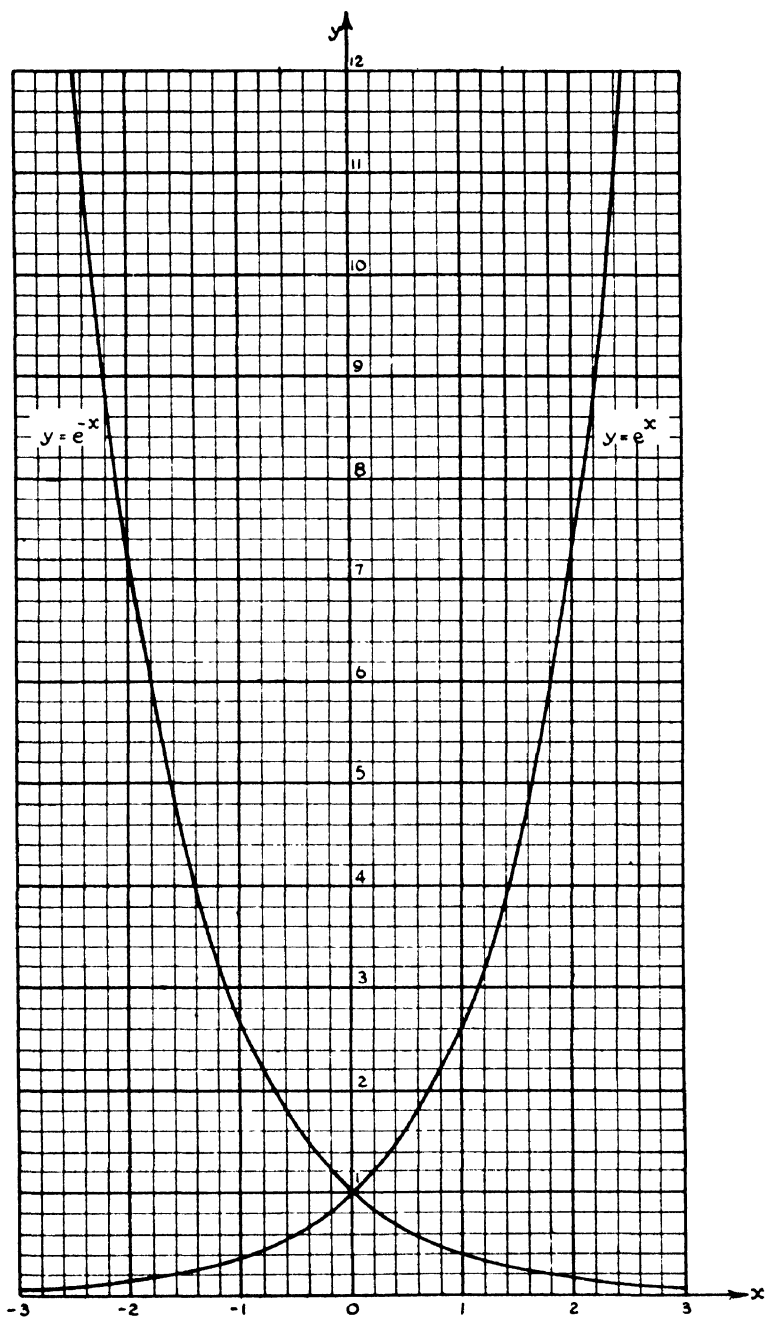


FIG. 40.—Graphs of e^x and e^{-x}

The r^{th} term is $\frac{(nx)(nx-1)(nx-2)\dots(nx-r+1)}{\underline{r}} \times \frac{1}{n^r}$

If n is made very large, each bracket in the numerator $\approx nx$.

Therefore as $n \rightarrow \infty$, the r^{th} term $\rightarrow \frac{x^r}{\underline{r}}$

i.e., when $n \rightarrow \infty$, $\left(1 + \frac{1}{n}\right)^{nx} = 1 + x + \frac{x^2}{\underline{2}} + \dots$ to infinity (62)

or $\text{Limit}_{n \rightarrow \infty} \left[\left(1 + \frac{1}{n}\right)^n\right]^x = 1 + x + \frac{x^2}{\underline{2}} + \dots$

It can be shown that this infinite series is convergent for all values of x .

The last equation can be written as :—

$$e^x = 1 + x + \frac{x^2}{\underline{2}} + \dots \quad (63)$$

where
$$e = \text{Limit}_{n \rightarrow \infty} \left(1 + \frac{1}{n}\right)^n \quad (64)$$

The value of e can be calculated by letting $x = 1$

$$\begin{aligned} \therefore e &= e^1 = 1 + 1 + \frac{1}{\underline{2}} + \frac{1}{\underline{3}} \dots \quad (65) \\ &= 2.71828 \dots \end{aligned}$$

This expansion for e^x is very useful. When dealing with it, it is important to remember that e^x is an ordinary number raised to the power x , and behaves just as any other number. The usefulness of the expansion is that it enables a number raised to a power to be expressed as a series.

The graphs of $y = e^x$ and $y = e^{-x}$ are important; they are given in Fig. 40.

Logarithms to the base e are very important and are known as "Natural" or "Napierian" logarithms. When no base is stated, it may be assumed to be e . Thus "log N " stands for "logarithm of N to the base e ".

$$\log_e N = \frac{\log_{10} N}{\log_{10} e}$$

But $\log_{10} 2.718 = 0.4343$

Thus $\log_e N = \frac{\log_{10} N}{0.4343}$

i.e., $\log_e N = 2.3026 \cdot \log_{10} N \quad (66)$

and $\log_{10} N = 0.4343 \cdot \log_e N \quad (67)$

Logarithms both to the base 10 and to the base e may be found in Appendix I.

VECTORS

Definition

A "vector" is a quantity *possessing both magnitude and direction*. It may be represented by a line whose length and angle with some reference axis correspond to this magnitude and direction. A "scalar", on the other hand, is a *quantity that possesses magnitude alone*. Thus if a man walks four miles East from O to P , and then three miles North from P to Q , the total distance he has covered

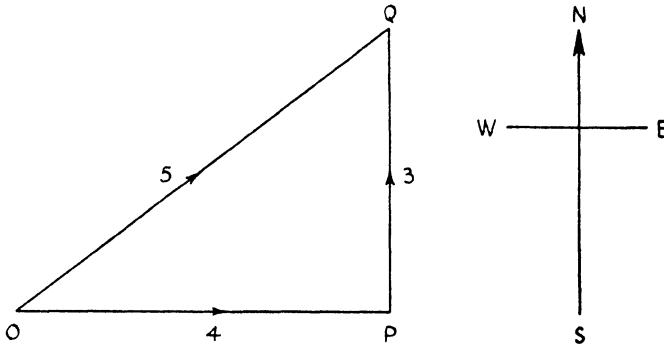


FIG. 41.—Example of vector addition.

is $OP + PQ = 4 + 3 = 7$ miles—a *scalar* quantity. But the distance OQ from his starting point to his destination is 5 miles in the *direction* shown in Fig. 41; this is a *vector* quantity, since it has *direction* as well as magnitude. When it is necessary to emphasize the distinction between scalar and vector quantities, an arrow may be placed over the two letters representing its origin and termination, in order to indicate its direction. Thus, referring to Fig. 41, one could write:—

$$\vec{OP} + \vec{PQ} = \vec{OQ}$$

in place of:— vector OP + vector PQ = vector OQ .

Addition of vectors

The sum of two vectors is defined as the displacement equivalent to the combined effect of the two individual displacements. Thus

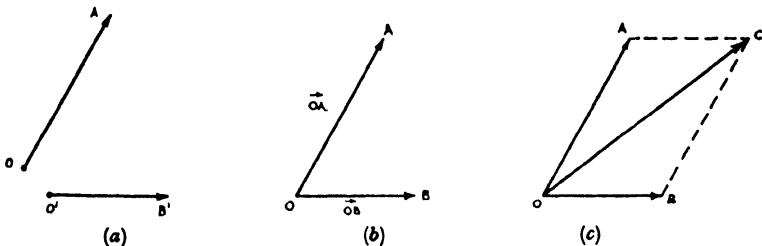


FIG. 42.—Addition of two vectors OA and OB .

in Fig. 41, the sum of the vectors OP and PQ is the vector OQ . In general, two vectors OA and OB (see Fig. 42a) are added by drawing them so that they both emanate from one point, —i.e. as \vec{OA} and \vec{OB} in Fig. 42b. The sum of these two, $\vec{OA} + \vec{OB}$, is the vector OC , which may be obtained either by drawing AC equal in direction and magnitude to OB , or by drawing BC equal in direction and magnitude to OA . In either case, the same point C is arrived at (Fig. 42c), and it can be seen that the figure $OBCA$ is a parallelogram.

This gives the rule for addition of vectors :—

The resultant of two vectors OA and OB is the diagonal through O of the parallelogram having OA and OB as two sides.

To find the magnitude of the resultant OC and the angle θ_1 that it makes with vector OB , drop a perpendicular CD on to OB , as in Fig. 43.

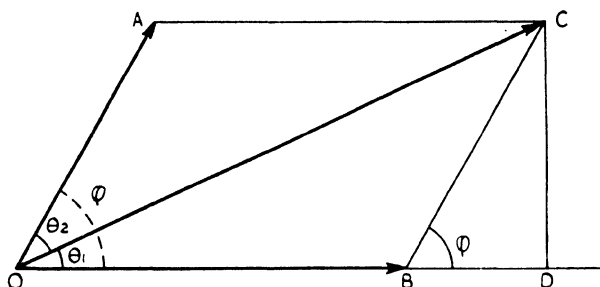


FIG. 43.—Parallelogram for addition of vectors.

Let the angle between vectors OA and OB be φ .

As OA and BC are parallel,

$$\angle DBC = \varphi$$

$$\angle OBC = 180^\circ - \varphi$$

Applying the cosine rule to triangle OBC :—

$$OC^2 = BC^2 + OB^2 - 2BC \cdot OB \cos \angle OBC$$

$$\text{i.e. } OC^2 = OA^2 + OB^2 + 2OA \cdot OB \cos \varphi$$

$$\therefore OC = \sqrt{OA^2 + OB^2 + 2OA \cdot OB \cos \varphi} \quad (68)$$

$$\tan \theta_1 = \frac{CD}{OD}$$

$$= \frac{BC \sin \varphi}{OB + BD}$$

$$= \frac{OA \sin \varphi}{OB + BC \cos \varphi} = \frac{OA \sin \varphi}{OB + OA \cos \varphi} \quad (69)$$

Similarly if θ_2 is the angle between the resultant OC and the vector OA :—

$$\tan \theta_2 = \frac{OB \sin \varphi}{OA + OB \cos \varphi} \quad (70)$$

Negative vectors

To comply with the normal use of + and - signs, the vector " $-OA$ " is defined as that vector which, when added to OA , will produce a zero resultant. (A zero vector has zero magnitude.)

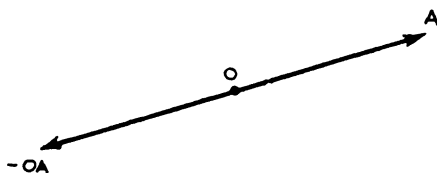


FIG. 44.—Negative vector $-OA$.

From this definition it follows that the vector $-\vec{OA}$ has the same magnitude as \vec{OA} , and the opposite direction (see Fig. 44), so that $-\vec{OA} = \vec{AO}$.

This is equivalent to saying that the minus sign rotates the vector through 180° .

Subtraction of vectors

The result of subtracting a vector OB from a vector OA can be obtained by regarding " $\vec{OA} - \vec{OB}$ " as $\vec{OA} + (-\vec{OB})$, as in Fig. 45.

$$\vec{OA} - \vec{OB} = \vec{OA} + (-\vec{OB}) = \vec{OC}$$

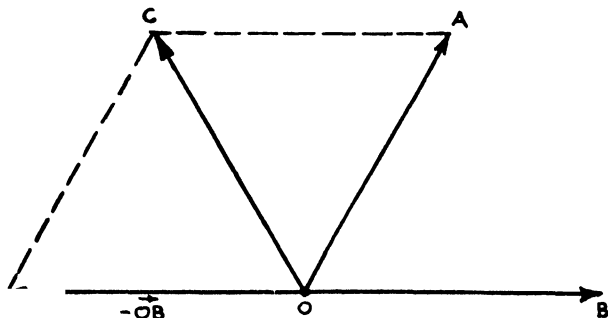


FIG. 45.—Subtraction of vector OB from OA .

Multiplication of a vector by a number

Multiplication has not yet been defined, except that multiplication by " -1 " rotates a vector through 180° . If a vector OP be multiplied by any positive real number n the result is a vector OP' of length equal to $(n \times OP)$ and of the same direction as \vec{OP} . Thus if \vec{OP} is "4 miles eastwards", " $3 \times OP$ " is a distance of twelve miles eastwards (see Fig. 46*b*). If a vector be multiplied by a negative number, its direction is reversed, since $-n = -1 \times n$. Thus " -3 " times the vector OP previously mentioned is the vector OP'' , which is twelve miles westwards (Fig. 46*c*).

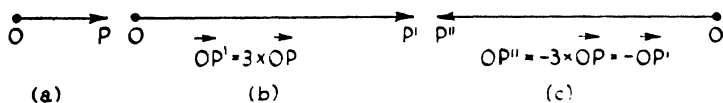


FIG. 46.—Multiplication of a vector.

Rotation of a vector

Since multiplication of a vector by " -1 " rotates it through 180° , it can be seen that multiplying it *twice* by -1 will rotate it through 360° . In general, multiplication by $(-1)^n$ rotates a vector through $(n \times 180^\circ)$ if n is an integer. If this rule is to apply for *all* values of n , then on putting $n = \frac{1}{2}$, multiplication by $(-1)^{\frac{1}{2}}$ must be considered to rotate a vector through $\frac{1}{2} \times 180^\circ = 90^\circ$. $(-1)^{\frac{1}{2}} = \sqrt{-1}$ is denoted by the letter j . The direction taken by convention as positive is anti-clockwise. Multiplication of a vector by j thus rotates it anti-clockwise through 90° .

$\sqrt{-1}$ cannot be evaluated in terms of normal numbers, and it is known as an "imaginary" quantity. It can, however, be

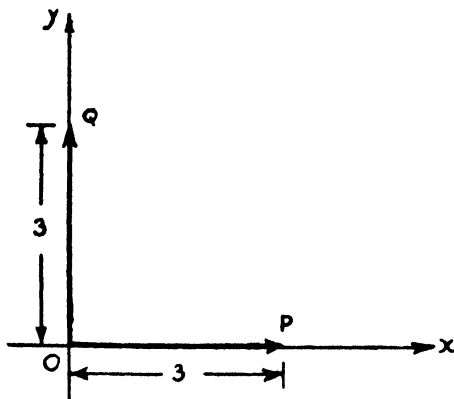


FIG. 47.—Rotation of a vector: $OQ = j.OP$.

dealt with as a normal algebraic quantity. As will be seen, it frequently permits great simplification in calculations.

The important result of the last paragraph is the fact that multiplication by $j = \sqrt{-1}$ rotates a vector anti-clockwise through 90° . It follows that multiplication of a vector by $j^2 = -1$ rotates it through 180° ; by $j^3 = -j = \frac{1}{j}$, through 270° ; and by $j^4 = +1$, through 360° .

This last result provides a convenient way of representing vectors when numerical problems are concerned.

Draw two rectangular axes Ox , Oy , and let the series of real numbers, positive or negative, represent vectors along the x axis; *i.e.*, the number 3 represents a vector of length 3 along Ox (see Fig. 47, where OP represents the vector 3).

Consider now a purely imaginary number such as $j3$. This can be written as $j \times 3$. But the vector 3 is a vector along the x axis of length 3, and multiplication by j rotates the vector through 90° . Therefore the vector $j3$ is a vector of length 3, along OY ; *e.g.* OQ represents the vector $j3$.

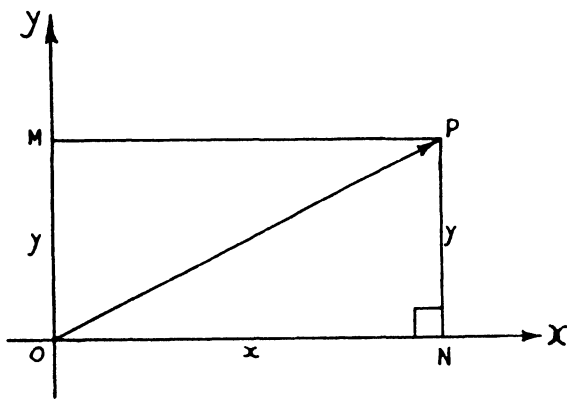


FIG. 48.—Rectangular vector notation.

Rectangular notation

Consider the vector OP (Fig. 48), and drop perpendiculars PN , PM from P to the axes. Let $ON = x$, $OM = y$. Then (x, y) are the co-ordinates of P . The vector OP is the sum of the vectors $ON + OM$ (since $ONPM$ is a parallelogram). But ON has length x and is along the x -axis, therefore it is equal to the vector x . Also, OM has length y and is along the y -axis, and it is consequently equal to the vector jy . Therefore one can write:—

$$\text{Vector } OP = ON + OM = x + jy \quad (71)$$

Hence *any* vector OP may be written in the form $(x + jy)$, where x and y are the co-ordinates of its extremity P . For example, in

Fig. 49, the vectors OA and OB are denoted as the vectors $1 + j3$ and $2 - j2$ respectively.

This method of notation simplifies the addition of vectors, for if the vectors are all in the form $x + jy$ (*i.e.*, real + imaginary terms), the resultant of adding will be found by adding all the real terms and adding all the imaginary terms. For example, in Fig. 49, the sum of $OA = 1 + j3$ and $OB = 2 - j2$ will be $OC = 3 + j1$.

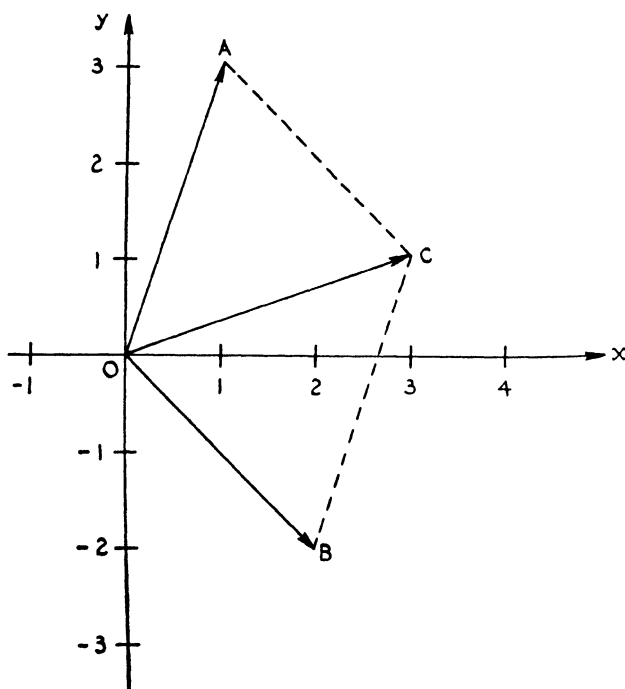


FIG. 49.—Addition of vectors by components.

This may be verified by drawing the parallelogram. Any number of vectors may be added or subtracted in this way.

For a vector to be zero, both the real (x) and the imaginary (y) terms must be equal to 0; and for two vectors to be equal, the real parts of the two vectors must be equal, as also must the imaginary.

Polar notation (modulus and angle)

It has been shown that any vector may be represented by its real and imaginary parts. Alternatively, a vector may be denoted by its length—known as its “modulus”—and the angle it makes with the x -axis—sometimes known as its “argument”. Using this notation, if the vector OP has length r and makes an angle θ with

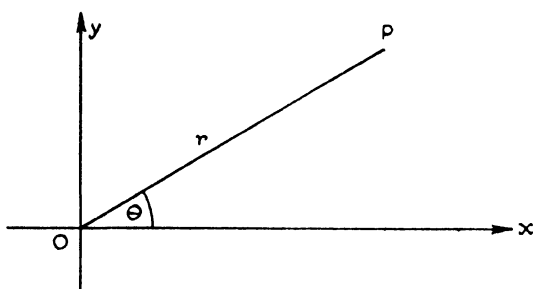


FIG. 50.—Polar vector notation.

the x -axis, it is called the vector $r \angle \theta$ (see Fig. 50);

$$\text{i.e.} \quad \text{Vector } OP = r \angle \theta \quad (72)$$

It should be noted that the modulus of OP is often written as $|OP|$, i.e., $|OP| \equiv r$.

The negative of OP (that is, the vector $-OP$), has the same length (r) as OP , but the reverse direction. It can therefore be expressed as:—

$$\begin{aligned} -OP &= -[r \angle \theta] \\ &= r \angle \pi + \theta \end{aligned} \quad (73)$$

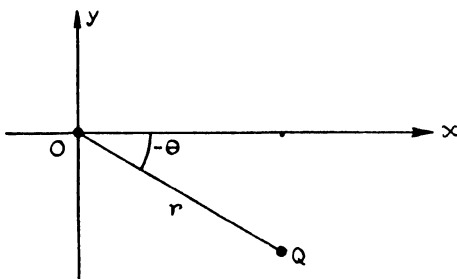


FIG. 51.—Vector with negative angle.

The vector OQ (see Fig. 51) is the vector $r \angle -\theta$. This is sometimes written as the vector $r \sphericalangle \theta$, where $\sphericalangle \theta = \angle -\theta$.

The vector $r \sphericalangle \theta$ should not be confused with the vector $-r \angle \theta$

Thus vector $3 \sphericalangle 45^\circ = 3 \angle -45^\circ = 3 \angle 315^\circ$
 whereas vector $-3 \angle 45^\circ = 3 \angle 180^\circ + 45^\circ = 3 \angle 225^\circ$

Conversion from rectangular notation to polar notation

Using the rectangular notation the vector OP (Fig. 52) is denoted as $x + jy$; while using the polar notation, it is denoted as $r \angle \theta$.

Clearly, simple relationships exist between x , y , r and θ . Using Pythagoras' theorem:—

$$\begin{aligned} |OP|^2 &= r^2 = x^2 + y^2 \\ \therefore |OP| &= r = \sqrt{x^2 + y^2} \end{aligned} \quad (74)$$

e.g., if $OP = 3 + j4$, then $r = \sqrt{9 + 16} = \sqrt{25} = 5$

It is important to remember that $r = \sqrt{x^2 + y^2}$ and not $\sqrt{x^2 + (jy)^2}$.

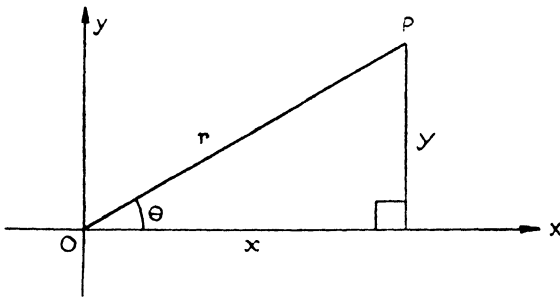


FIG. 52.—Relation between rectangular and polar notation.

The angle θ is best given by the formula:—

$$\tan \theta = \frac{y}{x} \quad (75)$$

This gives θ with a possible error of 180° ; the ambiguity can be overcome by considering in which quadrant the vector lies.

e.g., if $OP = 3 + j4$, $\tan \theta = \frac{4}{3} = 1.33$.

This gives $\theta = 53^\circ 7'$ or $180^\circ + 53^\circ 7'$; as the vector is in the 1st quadrant, the first result is correct, i.e., $\theta = 53^\circ 7'$.

Example.—

Express in polar form the vector:—

$$\begin{aligned} OP &\equiv a + j\sqrt{1-a^2} \\ |OP| &= \sqrt{a^2 + (1-a^2)} = 1 \\ \tan \varphi &= \frac{\sqrt{1-a^2}}{a} \end{aligned}$$

Hence the vector $a + j\sqrt{1-a^2}$ may also be denoted as the vector:

$$1, \tan^{-1} \frac{\sqrt{1-a^2}}{a}. \text{ Ans.}$$

Conversion from polar notation to rectangular notation

If the vector is given in the form $r \angle \theta$, it may easily be rewritten in the rectangular form as $x + jy$.

Referring to Fig. 52 :—

$$\begin{aligned} x &= r \cos \theta \\ y &= r \sin \theta \end{aligned} \tag{76}$$

$$\therefore OP \equiv r \angle \theta \equiv x + jy \tag{77}$$

$$\begin{aligned} &= r \cos \theta + j r \sin \theta \\ &= r (\cos \theta + j \sin \theta) \end{aligned} \tag{78}$$

It is important to note that the form of the vector $r \angle \theta$ is " $r (\cos \theta + j \sin \theta)$ ", and not " $r (\sin \theta + j \cos \theta)$ ". The latter may be rewritten as $r [\cos (90 - \theta) + j \sin (90 - \theta)]$, and it is therefore the vector $r \angle 90^\circ - \theta$.

Example.—

Write the vector $OP = 2 \angle 30^\circ$ in the form $x + jy$.

$$\begin{aligned} OP \equiv r \angle \theta &= 2 \angle 30^\circ \equiv 2 \cos 30^\circ + j \cdot 2 \sin 30^\circ \\ &= \sqrt{3} + j 1. \text{ Ans.} \end{aligned}$$

Multiplication and division of vectors

The process of multiplication using rectangular notation is purely algebraic.

$$\begin{aligned} \text{e.g. } (3 + j4) (1 - j1) &= 3 - j3 + j4 - j^2 4 \\ &= 3 - j3 + j4 + 4 \\ &= 7 + j 1. \end{aligned}$$

In this form, it is not so easy to see what the result means as when the vectors are expressed in polar form; nor, as will be seen, is multiplication of vectors as easy when they are expressed in the rectangular form as when they are expressed in polar form.

Consider the two vectors $OP_1 \equiv r_1 \angle \theta_1$ and $OP_2 \equiv r_2 \angle \theta_2$.

Then $OP_1 \equiv r_1 \angle \theta_1 \equiv r_1 (\cos \theta_1 + j \sin \theta_1)$

and $OP_2 \equiv r_2 \angle \theta_2 \equiv r_2 (\cos \theta_2 + j \sin \theta_2)$

$$\begin{aligned} \therefore OP_1 \times OP_2 &= r_1 r_2 \{ \cos \theta_1 \cos \theta_2 + j \sin \theta_1 \cos \theta_2 + j \cos \theta_1 \sin \theta_2 \\ &\quad + j^2 \sin \theta_1 \sin \theta_2 \} \\ &= r_1 r_2 \{ (\cos \theta_1 \cos \theta_2 - \sin \theta_1 \sin \theta_2) + j (\sin \theta_1 \cos \theta_2 \\ &\quad + \cos \theta_1 \sin \theta_2) \} \\ &= r_1 r_2 \{ \cos (\theta_1 + \theta_2) + j \cdot \sin (\theta_1 + \theta_2) \} \\ &= r_1 r_2 \angle \theta_1 + \theta_2 \end{aligned} \tag{79}$$

This shows that when two vectors are multiplied, using their polar form, the moduli must be multiplied and the angles added. It can be seen that this result agrees with the fact that multiplication

by j rotates through 90° . For $j = 1 \angle 90^\circ$; hence multiplication by j will multiply the modulus by 1 and add 90° to the angle.

In general, multiplication by a vector of the form $1 \angle \theta$ is equivalent simply to a rotation through an angle θ .

When two vectors are divided, the moduli are divided and the angles subtracted.

$$\begin{aligned} \text{Thus the vector } \frac{6 \angle 27^\circ}{3 \angle 11^\circ} &= \frac{6}{3} \angle 27^\circ - 11^\circ \\ &= 2 \angle 16^\circ \end{aligned}$$

Example.—

Find the modulus and angle of $\frac{4 - j3}{2 + j}$

This is in the form of $\left(\frac{\text{vector}}{\text{vector}} \right)$. Its modulus is therefore found by dividing the moduli.

$$\therefore \text{Modulus} = \frac{|4 - j3|}{|2 + j1|} = \frac{\sqrt{4^2 + 3^2}}{\sqrt{2^2 + 1^2}} = \frac{\sqrt{16 + 9}}{\sqrt{4 + 1}} = \frac{\sqrt{25}}{\sqrt{5}} = \sqrt{5}$$

The angle is found by subtraction of the two individual angles :—

$$\begin{aligned} \text{Angle} &= \tan^{-1} \frac{-3}{4} - \tan^{-1} \frac{1}{2} \\ &= -36^\circ 52' - 26^\circ 34' \\ &= -63^\circ 26' \quad \text{Ans.} \end{aligned}$$

Raising vectors to powers

Just as multiplication of vectors can be effected in two different ways, according to whether they are expressed in rectangular or polar co-ordinates, so also can the raising of vectors to powers. When expressed in rectangular co-ordinates, a vector is raised to a power by straightforward algebraic multiplication, thus :—

$$\begin{aligned} (2 + j1)^2 &= (2 + j1) \times (2 + j1) \\ &= 4 + j4 - 1 \\ &= 3 + j4. \end{aligned}$$

From the rules for multiplication and division of vectors, it follows that :—

$$\begin{aligned} [r \angle \theta]^2 &= (r \times r) \angle \theta + \theta = r^2 \angle 2\theta \\ \text{and } [r \angle \theta]^3 &= (r \times r \times r) \angle \theta + \theta + \theta = r^3 \angle 3\theta \\ \text{or } [r \angle \theta]^n &= r^n \angle n\theta \end{aligned} \quad (80)$$

It can be seen that the treatment of vectors in polar notation is much simpler than that of vectors in rectangular notation; since the answers to many vector calculations in electrical work are required in polar form, it is frequently advantageous to convert from rectangular to polar form before raising to powers.

Example.—

Find $(2 + j)^2$

$$\begin{aligned} (2 + j)^2 &= [\sqrt{2^2 + 1^2}, \tan^{-1} \frac{1}{2}]^2 \\ &= [\sqrt{5} / 26^\circ 34']^2 \\ &= (\sqrt{5})^2 / 2 \times 26^\circ 34' \\ &= 5 / 53^\circ 8' \quad \text{Ans.} \end{aligned}$$

As a check that this is the same result as obtained by the algebraic method above, *viz.* $(2 + j)^2 = 3 + j4$:—

$$|3 + j4| = \sqrt{3^2 + 4^2} = \sqrt{9 + 16} = \sqrt{25} = 5$$

and angle $(3 + j4) = \tan^{-1} \frac{4}{3} = \tan^{-1} 1.333 = 53^\circ 8'$

Hence $5 / 53^\circ 8' = 3 + j4$. *Ans.*

Square root of a vector

When a vector is expressed in polar form, its square root can be found by *raising the vector to the power of one-half*, by the method just described ;

for example, $\sqrt{5 / 53^\circ 8'} = [5 / 53^\circ 8']^{\frac{1}{2}} = \sqrt{5} / 26^\circ 34'$.

The square root of a vector expressed in rectangular form may be determined as follows :—

Let $\sqrt{x + jy}$ be $a + jb$

Required to find a and b .

Since $a + jb = \sqrt{x + jy}$

$$\therefore a^2 + 2jab - b^2 = x + jy. \tag{81}$$

Equating real quantities,

$$a^2 - b^2 = x \tag{82}$$

Equating imaginary quantities,

$$2ab = y \tag{83}$$

But :— $(a^2 + b^2)^2 = (a^2 - b^2)^2 + 4a^2b^2$

$$\therefore (a^2 + b^2)^2 = x^2 + y^2$$

$$\therefore a^2 + b^2 = \sqrt{x^2 + y^2} \tag{84}$$

Adding (82) and (84) :—

$$2a^2 = \sqrt{x^2 + y^2} + x$$

$$\therefore a^2 = \frac{\sqrt{x^2 + y^2} + x}{2} \tag{85}$$

Subtracting (82) from (84) :—

$$2b^2 = \sqrt{x^2 + y^2} - x$$

$$b^2 = \frac{\sqrt{x^2 + y^2} - x}{2} \tag{86}$$

Thus a and b are given by (85) and (86).

Example.—

Find $\sqrt{3 + j4}$.

Let $\sqrt{3 + j4} = a + jb$

From (85) :—

$$a^2 = \frac{\sqrt{3^2 + 4^2} + 3}{2}$$

$$\therefore a^2 = 4$$

$$\therefore a = 2$$

From (86) :—

$$b^2 = \frac{\sqrt{3^2 + 4^2} - 3}{2}$$

$$b^2 = 1$$

$$b = 1$$

Thus $\sqrt{3 + j4} = 2 + j1$ Ans.

As mentioned above, it is frequently advantageous to convert a vector to polar co-ordinates before manipulating it, and this example could also have been worked as follows :—

$$\begin{aligned} \sqrt{(3 + j4)} &= \sqrt{[\sqrt{3^2 + 4^2} \angle \tan^{-1} \frac{4}{3}]} \\ &= \sqrt{[5 \angle 53^\circ 8']} \\ &= [5 \angle 53^\circ 8']^{1/2} \\ &= \sqrt{5} \angle 26^\circ 34' \text{ Ans.} \end{aligned}$$

Rationalisation

It is sometimes necessary to eliminate j from the denominator of an expression. This can be done by "rationalisation", *i.e.*, by multiplication of both numerator and denominator by the "conjugate" of the denominator.

The "conjugate" of a vector $r \angle \theta = x + jy$ is that vector which has the same modulus and equal but opposite angle. Thus, the

conjugate of $r \angle \theta$ is $r \angle -\theta$
and the conjugate of $x + jy$ is $x - jy$ (87)

Example.—

Express $\frac{1}{5 - j3}$ in the rectangular form $x + jy$

$$\frac{1}{5 - j3} = \frac{1}{5 - j3} \times \frac{5 + j3}{5 + j3} = \frac{5 + j3}{5^2 - j^2 3^2} = \frac{5 + j3}{25 + 9} = \frac{5}{34} + j\frac{3}{34} \text{ Ans.}$$

It is a good rule to avoid rationalisation unless necessary.

Exponential notation of a vector

As will be seen later (equation 125 p. 91), $\cos \theta + j \sin \theta = e^{j\theta}$. Thus the vector $r \angle \theta \equiv r(\cos \theta + j \sin \theta)$ may be written as the vector $r \cdot e^{j\theta}$.

A further apparent simplification can be carried out by letting $r = e^a$. The vector now becomes $e^a \cdot e^{j\theta} = e^{a+j\theta}$.

By letting $a + j\theta$ equal the complex number γ , say, the vector $r \angle \theta$ may be denoted simply and completely as the vector e^γ . Thus:—

$$OP \equiv r \angle \theta \equiv e^{a+j\theta} = e^\gamma \tag{88}$$

Logarithm of a vector

To find $\log_e [r \angle \theta]$

Rewrite the vector $[r \angle \theta]$ using the exponential notation, as:—

$$[r \angle \theta] = r \cdot e^{j\theta}$$

$$\begin{aligned} \text{Then } \log_e [r \angle \theta] &= \log_e (r \cdot e^{j\theta}) \\ &= \log_e r + \log_e e^{j\theta} \\ &= \log_e r + j\theta \end{aligned} \tag{89}$$

Rotating vectors

Let the vector OP , of length r , rotate in an anti-clockwise direction about a centre O . Then when OP has turned through an angle θ from its horizontal position along Ox (see Fig. 53a), the instantaneous height h of P above Ox is given by:—

$$h = r \sin \theta \tag{90}$$

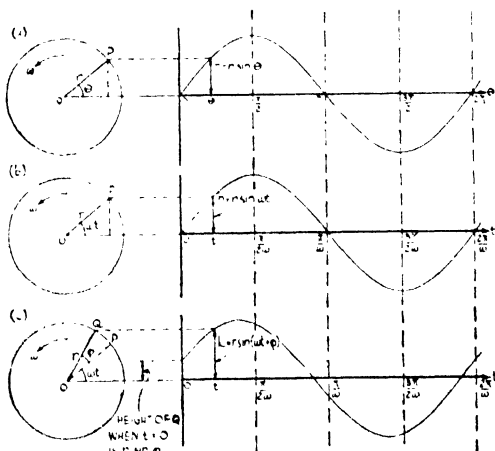


FIG. 53.—Rotating vectors.

If the vertical height h of P be plotted against θ , the resulting curve is as shown on the right of Fig. 53a. Since the one variable (h) is directly proportional to the *sine* of the other (θ), this is called a "sine", or "sinusoidal" curve.

If OP be rotating with a constant angular velocity ω corresponding to f revolutions per second—that is, $\omega = 2\pi f$ radians per second—then the time for one revolution is $\frac{1}{f} = \frac{2\pi}{\omega}$ seconds. After time t , OP will have turned through an angle $\theta = \omega t$, where t is measured from the instant when OP is in the horizontal position along Ox . The vertical height of P at any time t is given by:—

$$h = r \sin \omega t \quad (91)$$

and varies as shown in Fig. 53*b*. Time may, however, be measured from some instant other than that at which OP lies along Ox . Consider a vector OQ that makes an angle φ with OP ; then at the instant $t = 0$, OQ makes an angle φ with Ox , and at any later instant t , OQ will make an angle $(\omega t + \varphi)$ with Ox . The height k of Q at time t is then given by:—

$$k = r \sin (\omega t + \varphi) \quad (92)$$

This is shown in Fig. 53*c*.

Many mechanical and electrical quantities vary with time in a sinusoidal manner, and are represented by equations of the form (92) and by figures similar to Fig. 53. Rotating vectors provide a very convenient method of expressing such sinusoidal waveforms; the addition, subtraction, multiplication and division of sine waves can then be easily achieved by the application of these processes to the rotating vectors, whereas such operations can not so easily be applied to the sine waves themselves.

Addition of two sine waves using rotating vectors

Consider the two sinusoidal waveforms represented by the equations:—

$$\begin{aligned} a &= A \sin \omega t \\ b &= B \sin (\omega t + \varphi) \end{aligned}$$

where a and b represent the instantaneous heights of the two curves at any time t , and A and B are the peak or maximum heights. These two sine waves are illustrated in Fig. 54 *a* and *b* respectively, and they could clearly be added, to give curve (*c*), by the somewhat tedious process of adding the individual heights of the two curves at each instant.

A much easier way of adding the two curves is to draw two vectors $OP \equiv A \angle \omega t$ and $OQ \equiv B \angle \omega t + \varphi$, such that, if they be rotated at constant angular velocity ω , the graphs of the instantaneous heights of P and Q will be identical with the curves to be added. These two vectors (Fig. 55) then represent the two curves, and they may be added by completing the parallelogram. The result (Fig. 56) is a third vector OR which can be denoted by $C \angle \omega t + \theta$, where C and θ are, as shown below, given by:—

$$C = |OR| = \sqrt{A^2 + B^2 + 2AB \cos \varphi} \quad (93)$$

and
$$\theta = \tan^{-1} \left(\frac{B \sin \varphi}{A + B \cos \varphi} \right) \tag{94}$$

This vector OR is the sum of the two vectors OP and OQ , and represents curve $c = C \sin(\omega t + \theta)$ which is the sum of the curves represented by OP and OQ .

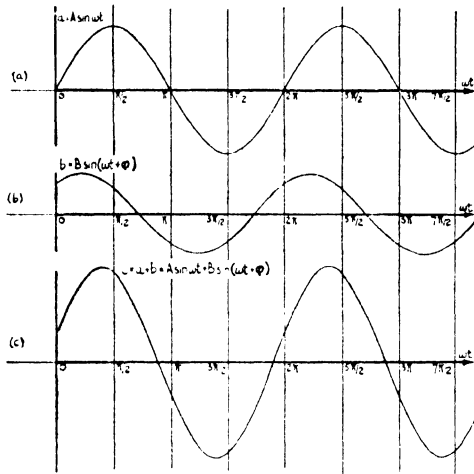


FIG. 54.—Addition of two sine waves.

The values of the modulus C and angle $\angle\theta$ of the resultant vector $OR = OP + OQ$ can be evaluated as follows.

From Fig. 55 :—

$$OP = A \cos \omega t + jA \sin \omega t$$

$$OQ = B \cos (\omega t + \varphi) + jB \sin (\omega t + \varphi)$$

$$OR = OP + OQ$$

$$\therefore OR = \{A \cos \omega t + B \cos (\omega t + \varphi)\} + j \{A \sin \omega t + B \sin (\omega t + \varphi)\}$$

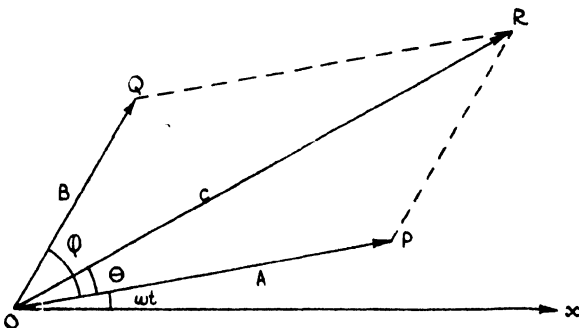


FIG. 55.—Addition of two vectors OP and OQ representing two sine waves.

$$\begin{aligned}
 \therefore |OR|^2 &= \{A \cos \omega t + B \cos(\omega t + \varphi)\}^2 + \{A \sin \omega t + B \sin(\omega t + \varphi)\}^2 \\
 &= \{A^2 \cos^2 \omega t + B^2 \cos^2(\omega t + \varphi) + 2AB \cos(\omega t + \varphi) \cos \omega t\} \\
 &\quad + \{A^2 \sin^2 \omega t + B^2 \sin^2(\omega t + \varphi) + 2AB \sin(\omega t + \varphi) \sin \omega t\} \\
 &= A^2 + B^2 + 2AB \{\cos(\omega t + \varphi) \cos \omega t + \sin(\omega t + \varphi) \sin \omega t\} \\
 &= A^2 + B^2 + 2AB \cos \{(\omega t + \varphi) - (\omega t)\} \\
 &= A^2 + B^2 + 2AB \cos \varphi \\
 \therefore C &= |OR| = \sqrt{A^2 + B^2 + 2AB \cos \varphi} \quad (95)
 \end{aligned}$$

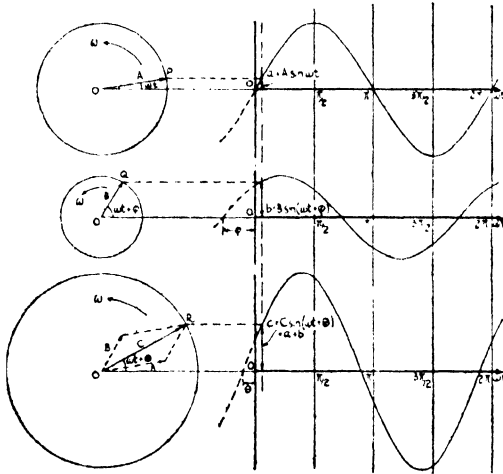


FIG. 56.—Addition of two sine waves by means of rotating vectors

The angle made by OR with Ox at any instant t is $(\omega t + \theta)$, so that, from Fig. 56 :—

$$\tan(\omega t + \theta) = \frac{A \sin \omega t + B \sin(\omega t + \varphi)}{A \cos \omega t + B \cos(\omega t + \varphi)}$$

θ can be expressed as the difference between two angles, *i.e.* :—

$$\tan \theta = \tan \{(\omega t + \theta) - \omega t\}$$

so that :—

$$\begin{aligned}
 \tan \theta &= \frac{\tan(\omega t + \theta) - \tan \omega t}{1 + \tan(\omega t + \theta) \tan \omega t} \\
 \therefore \tan \theta &= \frac{\frac{A \sin \omega t + B \sin(\omega t + \varphi)}{A \cos \omega t + B \cos(\omega t + \varphi)} - \frac{\sin \omega t}{\cos \omega t}}{1 + \frac{A \sin \omega t + B \sin(\omega t + \varphi)}{A \cos \omega t + B \cos(\omega t + \varphi)} \cdot \frac{\sin \omega t}{\cos \omega t}} \\
 &= \frac{B \sin \{(\omega t + \varphi) - \omega t\}}{A (\sin^2 \omega t + \cos^2 \omega t) + B \cos \{(\omega t + \varphi) - \omega t\}} \\
 &= \frac{B \sin \varphi}{A + B \cos \varphi} \quad (96)
 \end{aligned}$$

PART II

MORE ADVANCED MATHEMATICS

DIFFERENTIAL CALCULUS

Differential calculus deals with the *rate of change* of a function : e.g., if $y = f(x)$, by how much will y increase (or decrease) if the value of x is increased by some small amount? For functions in general, the answer will of course depend on the initial value of x . The graphical illustration of this is useful : if the curve $y = f(x)$ is drawn, the rate of change of y will be proportional to the *slope* of the curve. If it is very steep, a small increase in x will produce a proportionately large increase in y ; if the curve is fairly flat, the increase in y will be small. It can be seen that for any curve except a straight line the slope, or rate of change, varies from place to place. Hence, if it is to be measured by considering the ratios of increases in y and x , it is important to see that these increases are small, otherwise their ratio will not give a true idea of the slope of the curve at that point.

These small changes in the values of x and y are usually denoted by δx or δy (alternatively Δx or Δy)—the Greek letter delta signifying “a small change in”.

Note that if δx is small, $(\delta x)^2$ will be even smaller, and can be neglected in comparison with δx . Higher powers of δx are, of course, smaller still.

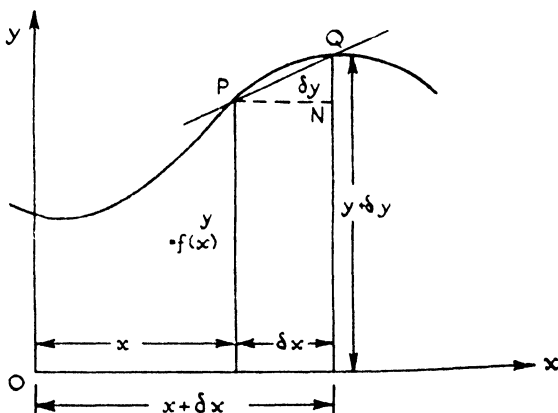


FIG. 57.—Differential notation.

It has been stated that the rate of change, or slope, is given by the ratio of the increases in y and x , or $\frac{\delta y}{\delta x}$ as it would be written. This is illustrated graphically in Fig. 57.

To find the slope at $P \equiv (x, y)$, an adjacent point Q is taken, whose co-ordinates are $(x + \delta x, y + \delta y)$. The ratio $\frac{\delta y}{\delta x}$ will give the tangent of the angle QPN , i.e., the "slope" of the line PQ . It can be seen that if Q is made very close to P , this will give the slope of the curve at P . The conditions for this are that δy and δx both become zero. Although they both become zero, as Q moves up to P , the ratio $\frac{\delta y}{\delta x}$ approaches some finite value, which will be the slope of the curve. This value is denoted by $\frac{dy}{dx}$. In other words, $\frac{dy}{dx}$ is the limit of the ratio $\frac{\delta y}{\delta x}$ as δx (and therefore δy) $\rightarrow 0$, or:—

$$\frac{dy}{dx} = \text{Limit}_{\delta x \rightarrow 0} \frac{\delta y}{\delta x} \quad (97)$$

Hence $\frac{dy}{dx}$ gives the rate of change of y , or the slope, at this point (x, y) . As the slope depends upon the position of the point P , it is obvious that $\frac{dy}{dx}$ must be a function of x . To find the slope at any *particular* point the numerical value of x must be inserted.

Notation

y is a function of x , denoted by $f(x)$. $\frac{dy}{dx}$ is a function of x , and is denoted by $f'(x)$; this is called the "first derivative", or "differential coefficient", of $f(x)$, i.e. :—

$$\frac{dy}{dx} = f'(x) \quad (98)$$

This is sometimes written as $\frac{d}{dx}f(x)$

Calculation of $f'(x)$ ("differentiation")

$f'(x)$ has been defined as the limit of $\frac{\delta y}{\delta x}$ when δx tends to zero. This indicates the method of calculation.

$$\text{At } P, \quad y = f(x) \quad (i)$$

At Q , x increases to $x + \delta x$, and as a result, y increases to $y + \delta y$.

$$\therefore \quad y + \delta y = f(x + \delta x) \quad (ii)$$

This is the condition that Q shall lie on the curve.

Subtracting equation (i) from equation (ii) :—

$$\delta y = f(x + \delta x) - f(x)$$

$$\text{Hence} \quad \frac{\delta y}{\delta x} = \frac{f(x + \delta x) - f(x)}{\delta x}$$

$$\begin{aligned}
 \text{Thus } f'(x) &= \frac{dy}{dx} \\
 &= \text{Limit}_{\delta x \rightarrow 0} \frac{\delta y}{\delta x} \\
 &= \text{Limit}_{\delta x \rightarrow 0} \frac{f(x + \delta x) - f(x)}{\delta x} \quad (99)
 \end{aligned}$$

This is the basic formula from which all derivatives are calculated.

Example :—

Take a particular case, say $y = x^2$, and find the slope of this curve at the point (x, y) .

$$\begin{aligned}
 f(x) &= x^2 \\
 \text{From above, } \frac{dy}{dx} &= \text{Limit}_{\delta x \rightarrow 0} \frac{f(x + \delta x) - f(x)}{\delta x} \\
 \text{Now } \frac{\delta y}{\delta x} &= \frac{(x + \delta x)^2 - x^2}{\delta x} \\
 &= \frac{x^2 + 2x \cdot \delta x + \delta x^2 - x^2}{\delta x} \\
 &= 2x + \delta x
 \end{aligned}$$

Note that no approximations have been made.

But $\frac{dy}{dx}$ is the limit of $\frac{\delta y}{\delta x}$ when $\delta x \rightarrow 0$
and equals the limit of $2x + \delta x$ when $\delta x \rightarrow 0$

$$\therefore \frac{dy}{dx} = 2x$$

Thus the slope of $y = x^2$ at any point is equal to $2x$ (e.g., at the point $(3, 9)$, the slope is $2 \times 3 = 6$).

Derivative of x^n

$$\begin{aligned}
 \text{Let } f(x) &= x^n \\
 \text{Then } \frac{\delta y}{\delta x} &= \frac{(x + \delta x)^n - x^n}{\delta x}
 \end{aligned}$$

That is :—

$$\frac{\delta y}{\delta x} = \frac{x^n \left(1 + \frac{\delta x}{x}\right)^n - x^n}{\delta x}$$

Expand $\left(1 + \frac{\delta x}{x}\right)^n$ by the Binomial theorem, where n and x may have any value, since $\left|\frac{\delta x}{x}\right| < 1$.

$$\frac{\delta y}{\delta x} = \frac{x^n \left\{ 1 + n \cdot \frac{\delta x}{x} + \frac{n(n-1)}{2} \left(\frac{\delta x}{x}\right)^2 + \dots \right\} - x^n}{\delta x}$$

$$\therefore \frac{\delta y}{\delta x} = \frac{\left\{ x^n + n\delta x \cdot x^{n-1} + \frac{n(n-1)}{2} (\delta x)^2 x^{n-2} + \dots \right\} - x^n}{\delta x}$$

$$= nx^{n-1} + \frac{n(n-1)}{2} x^{n-2} \delta x + \dots$$

All terms after the second involve powers of δx greater than the first, and may be neglected when $\delta x \rightarrow 0$.

$$\therefore \frac{dy}{dx} = \text{Limit}_{\delta x \rightarrow 0} \frac{\delta y}{\delta x} = nx^{n-1}$$

$$\text{i.e., } \frac{d}{dx}(x^n) = nx^{n-1} \quad (100)$$

e.g., as already proved, $\frac{d}{dx} x^2 = 2x$.

Example.—

Differentiate $\frac{1}{\sqrt{x}}$ with respect to x .

$$\text{Let } y = \frac{1}{\sqrt{x}} = x^{-\frac{1}{2}}$$

$$\therefore \frac{dy}{dx} = -\frac{1}{2}x^{-\frac{3}{2}} \quad \text{Ans.}$$

Constants

The equation $y = C$, where C is a constant, represents a straight line parallel to the x -axis. The slope is zero, so that:—

$$\text{If } y = C$$

$$\text{Then } \frac{dy}{dx} = \frac{d}{dx}(C) = 0 \quad (101)$$

Multiplication by a constant.—If the function is multiplied by some constant, the constant remains after differentiation; for example, the slope of the curve $y = 5x^3$ is five times as great as that of $y = x^3$.

$$\text{Thus if } y = 5x^3$$

$$\frac{dy}{dx} = 5 \times 3x^2 = 15x^2$$

Products

Consider $y = f(x) = u \cdot v$, where u and v are both functions of x .

$$\text{Then } \frac{\delta y}{\delta x} = \frac{(u + \delta u)(v + \delta v) - uv}{\delta x}$$

$$= \frac{uv + u \cdot \delta v + v \cdot \delta u + \delta u \cdot \delta v - uv}{\delta x}$$

$$= u \cdot \frac{\delta v}{\delta x} + v \cdot \frac{\delta u}{\delta x} + \frac{\delta u \cdot \delta v}{\delta x}$$

As δx tends to zero, so also will δu and δv . The term $\frac{\delta u \cdot \delta v}{\delta x}$ will then be small and may be neglected.

$$\frac{dy}{dx} = \text{Limit}_{\delta x \rightarrow 0} \frac{\delta y}{\delta x} = u \cdot \frac{dv}{dx} + v \cdot \frac{du}{dx}$$

$$\text{i.e., } \frac{d}{dx}(u \cdot v) = u \cdot \frac{dv}{dx} + v \cdot \frac{du}{dx} \quad (102)$$

Example.—

Find $\frac{dy}{dx}$ when $y = (x^2 + 3)(2x - 1) = u \cdot v$,

where $u = x^2 + 3$ and $v = 2x - 1$.

$$\begin{aligned} \frac{dy}{dx} &= (x^2 + 3) \times 2 + 2x \cdot (2x - 1) \\ &= 2x^2 + 6 + 4x^2 - 2x \end{aligned}$$

$$\therefore \frac{dy}{dx} = 6x^2 - 2x + 6 \quad \text{Ans.}$$

Quotients

In a similar manner to the above, it may be shown that if $y = \frac{u}{v}$, where u and v are both functions of x , then :—

$$\frac{dy}{dx} = \frac{d}{dx} \left(\frac{u}{v} \right) = \frac{v \frac{du}{dx} - u \frac{dv}{dx}}{v^2} \quad (103)$$

Example.—

Find $\frac{dy}{dx}$ when $y = \frac{x^2 - 1}{x + 2}$

In this case $u = x^2 - 1$ and $v = x + 2$

$$\frac{dy}{dx} = \frac{(x + 2) \cdot 2x - (x^2 - 1) \cdot 1}{(x + 2)^2}$$

$$\therefore \frac{dy}{dx} = \frac{x^2 + 4x + 1}{(x + 2)^2} \quad \text{Ans.}$$

Trigonometrical functions

To take another particular case, let $y = \sin x$. It is required to find the slope of this curve at the point (x, y) .

$$f(x) = \sin x$$

$$\frac{dy}{dx} = \text{Limit}_{\delta x \rightarrow 0} \frac{f(x + \delta x) - f(x)}{\delta x}$$

$$= \text{Limit}_{\delta x \rightarrow 0} \frac{\sin(x + \delta x) - \sin x}{\delta x}$$

$$= \text{Limit}_{\delta x \rightarrow 0} \frac{\sin x \cos \delta x + \cos x \sin \delta x - \sin x}{\delta x}$$

When $\delta x \rightarrow 0$, $\cos \delta x \rightarrow 1$ and $\sin \delta x \rightarrow \delta x$

$$\therefore \frac{dy}{dx} = \frac{\sin x \cdot 1 + \cos x \cdot \delta x - \sin x}{\delta x} = \cos x$$

$$\text{Thus } \frac{d}{dx}(\sin x) = \cos x \quad (104)$$

This result may be verified by reference to Fig. 58.

When $x = 0$, $y = \sin x = 0$, $\cos x = 1$, and the slope of $y = \sin x$ is a maximum.

When $x = 90^\circ$, $y = \sin x = 1$, $\cos x = 0$, and the slope of $y = \sin x$ is also zero.

When $x = 180^\circ$, $y = \sin x = 0$, $\cos x = -1$, and the slope of $y = \sin x$ is a maximum in a negative direction.

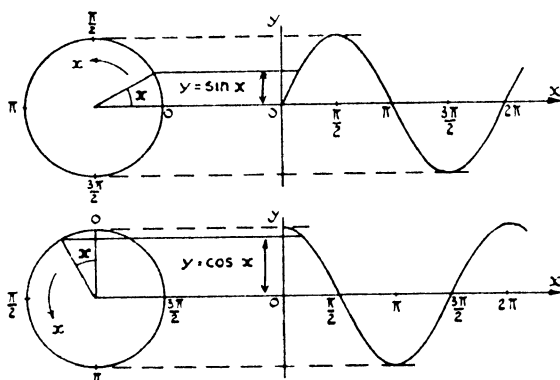


FIG. 58.—Graphs of $y = \sin x$ and $y = \frac{d}{dx} \sin x = \cos x$.

It has been shown that the differential coefficient of $\sin x$ is $\cos x$. In a similar manner it may be shown that the differential coefficient of $\cos x$ is $-\sin x$.

Consider the differential coefficient of $\tan x$.

$$\text{Let } y = \tan x$$

$$\therefore y = \frac{\sin x}{\cos x}$$

This may be considered as a quotient. Hence:—

$$\begin{aligned} \frac{dy}{dx} &= \frac{\cos x \frac{d(\sin x)}{dx} - \sin x \frac{d(\cos x)}{dx}}{\cos^2 x} \\ &= \frac{\cos^2 x + \sin^2 x}{\cos^2 x} \\ &= \frac{1}{\cos^2 x} = \sec^2 x \end{aligned}$$

$$\text{Thus } \frac{d}{dx} (\tan x) = \sec^2 x \quad (105)$$

The derivatives of other trigonometrical functions may be calculated in a similar manner. Some of the more important ones

are listed in Table II; a further list of derivatives is given in Appendix I.

TABLE II
Differential coefficients of the trigonometrical ratios

y	$\frac{dy}{dx}$
$\sin x$	$\cos x$
$\cos x$	$-\sin x$
$\tan x$	$\sec^2 x$
$\cot x$	$-\operatorname{cosec}^2 x$
$\sec x$	$\sec x \cdot \tan x$
$\operatorname{cosec} x$	$-\operatorname{cosec} x \cdot \cot x$

Inverse functions

The differentiation of an inverse function (such as $\sin^{-1} x$ or $\tan^{-1} x$) is interesting. Consider :—

$$y = \sin^{-1} x$$

$\frac{dy}{dx}$ cannot be found at once; rewrite the equation as :—

$$x = \sin y$$

Then $\frac{dx}{dy} = \cos y$

$\therefore \frac{dy}{dx} = \frac{1}{\cos y}$

Now $\cos y = \sqrt{1 - \sin^2 y} = \sqrt{1 - x^2}$

$\therefore \frac{dy}{dx} = \frac{1}{\sqrt{1 - x^2}}$

Similarly, if $y = \tan^{-1} x$

$$x = \tan y$$

$$\frac{dx}{dy} = \sec^2 y$$

$$\frac{dy}{dx} = \frac{1}{\sec^2 y}$$

$$= \frac{1}{1 + \tan^2 y}$$

$$= \frac{1}{1 + x^2}$$

Thus $\frac{d}{dx} (\tan^{-1} x) = \frac{1}{1 + x^2}$ (106)

Sum of terms and series

If $y = f(x)$ is given as a sum of a number of terms, $\frac{dy}{dx}$ is found by adding the derivatives of each term taken individually.

$$\begin{aligned}\text{Thus, if } y &= 5x^2 + 3x + 7 \\ \frac{dy}{dx} &= (5 \times 2x) + 3 + 0 \\ &= 10x + 3\end{aligned}$$

Exponential and logarithmic functions

The derivative of an exponential function may be found by expressing it as a series; each term of the series can then be differentiated, and the resulting derivatives added.

$$\text{Thus if :— } y = e^x$$

It can be expressed as :—

$$\begin{aligned}y &= 1 + x + \frac{x^2}{2} + \frac{x^3}{3} + \frac{x^4}{4} + \dots \\ \therefore \frac{dy}{dx} &= 0 + 1 + \frac{2x}{2} + \frac{3x^2}{3} + \frac{4x^3}{4} + \dots \\ &= 0 + 1 + x + \frac{x^2}{2} + \frac{x^3}{3} + \dots \\ &= e^x\end{aligned}$$

$$\text{Thus } \frac{d}{dx}(e^x) = e^x \quad (107)$$

Using this result, one can find the derivative of $\log_e x$.

$$\text{For, if } y = \log_e x$$

$$\text{Then :— } x = e^y$$

$$\begin{aligned}\therefore \frac{dx}{dy} &= \frac{d}{dy}(e^y) \\ &= e^y\end{aligned}$$

$$\begin{aligned}\therefore \frac{dy}{dx} &= \frac{1}{e^y} \\ &= \frac{1}{x}\end{aligned}$$

This gives the important relationship that :—

$$\frac{d}{dx}(\log_e x) = \frac{1}{x} \quad (108)$$

Function of a function

$$y = F[f(x)]$$

Each function is differentiated and the results multiplied :—

$$\frac{dy}{dx} = F'[f(x)] \times f'(x) \quad (109)$$

This can be extended for functions of a function of a function.

Example 1.—

Differentiate $\sin x^2$ with respect to x .

This is a function (sin) of a function of x , (x^2).

First differentiate $\sin x^2$ with respect to x^2 , giving $\cos x^2$.

Next differentiate x^2 with respect to x , giving $2x$.

Then the differential coefficient of $\sin x^2$ with respect to x is :—

$$\cos x^2 \times 2x = 2x \cdot \cos x^2 \quad \text{Ans.}$$

Example 2.—

Find $\frac{dy}{dx}$ when $y = \sqrt{x^3 - 3x}$

Differentiate the $\sqrt{\quad}$, giving $\frac{1}{2}(x^3 - 3x)^{-1}$

Differentiate $x^3 - 3x$, giving $3x^2 - 3$

$$\therefore \frac{dy}{dx} = \frac{1}{2}(x^2 - 1)(3x^2 - 3)^{-1} \quad \text{Ans.}$$

Example 3.—

$$\begin{aligned} y &= e^{3x^2} \\ \frac{dy}{dx} &= e^{3x^2} \cdot \frac{d}{dx}(3x^2) \\ &= 6x \cdot e^{3x^2} \quad \text{Ans.} \end{aligned}$$

Example 4.—

$$y = \log \tan \sqrt{x^2 + 1}. \quad \text{Find } \frac{dy}{dx}.$$

This is a function (log) of a function (tan) of a function ($\sqrt{\quad}$) of the function ($x^2 + 1$), which is a function of x .

Differentiating $\log \tan \sqrt{x^2 + 1}$ with respect to $\tan \sqrt{x^2 + 1}$
gives :— $\frac{1}{\tan \sqrt{x^2 + 1}}$

Differentiating $\tan \sqrt{x^2 + 1}$ with respect to $\sqrt{x^2 + 1}$
gives :— $\sec^2 \sqrt{x^2 + 1}$

Differentiating $\sqrt{x^2 + 1}$ with respect to $(x^2 + 1)$
gives :— $\frac{1}{2}(x^2 + 1)^{-1}$

Differentiating $(x^2 + 1)$ with respect to x
gives :— $2x$.

$$\begin{aligned} \text{Hence } \frac{d}{dx}(\log \tan \sqrt{x^2 + 1}) &= \frac{1}{\tan \sqrt{x^2 + 1}} \times \sec^2 \sqrt{x^2 + 1} \\ &\quad \times \frac{1}{2}(x^2 + 1)^{-1} \times 2x \\ &= \frac{x}{\sqrt{x^2 + 1} \sin \sqrt{x^2 + 1} \cos \sqrt{x^2 + 1}} \quad \text{Ans.} \end{aligned}$$

Successive differentiation

If $\frac{dy}{dx}$ is itself differentiated with respect to x , the result is

written $\frac{d^2y}{dx^2}$ or $f''(x)$. This gives the rate of change of the slope of $f(x)$, and is known as the *second* derivative or differential coefficient. Similarly subsequent derivatives may be found; their calculation involves no new principles.

Example.—

Find the third derivative of $y = x^3 \sin x$.

$$\frac{dy}{dx} = 3x^2 \cdot \sin x + x^3 \cos x$$

$$\begin{aligned} \frac{d^2y}{dx^2} &= 6x \sin x + 3x^2 \cos x + 3x^2 \cos x - x^3 \sin x \\ &= 6x \sin x + 6x^2 \cos x - x^3 \sin x \end{aligned}$$

$$\begin{aligned} \frac{d^3y}{dx^3} &= 6 \sin x + 6x \cos x + 12x \cos x - 6x^2 \sin x - x^3 \cos x \\ &\quad - 3x^2 \sin x \\ &= 6 \sin x + 18x \cos x - 9x^2 \sin x - x^3 \cos x. \quad \text{Ans.} \end{aligned}$$

Maxima and Minima

Since $\frac{dy}{dx}$ gives the slope of $f(x)$ at any point, it can be used to find the points where y is a maximum or minimum; for at these points the curve is horizontal, *i.e.* the slope is zero. The values of x that make y a maximum or minimum will therefore be the roots of the equation $f'(x) = 0$.

To decide whether any particular root of this equation gives a maximum or minimum, two methods may be used.

1.—Find $\frac{dy}{dx}$ for values of x just above and below that giving $f'(x) = 0$. If it is positive below and negative above, the curve will be as Fig. 59, *i.e.* a maximum. If it is negative below and positive above, the point will be a minimum.

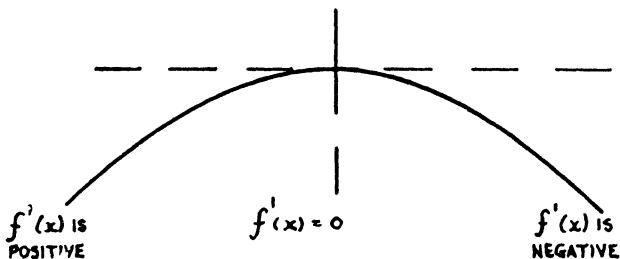


FIG. 59.—Curve with maximum.

It is possible sometimes for the slope to have the same sign before and after. In this case the curve is as shown in Fig. 60, and the point is neither a maximum nor a minimum, but is a "point of inflection".

2.—For a maximum, the slope is positive before and negative after—*i.e.*, the slope is decreasing; therefore the rate of change of slope is negative. $\frac{d^2y}{dx^2}$ is therefore negative. Similarly at a minimum, $\frac{d^2y}{dx^2}$ is positive. Hence an alternative way is to find $\frac{d^2y}{dx^2}$ at the point; if it is negative the point is a maximum, if positive it is a minimum. If $\frac{d^2y}{dx^2} = 0$, the curve may be of the form shown in Fig. 60.

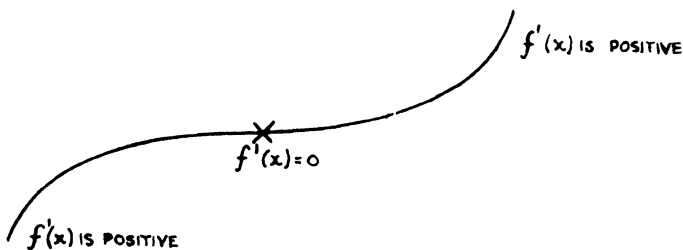


FIG. 60.—Curve with point of inflection.

Example 1.—

Consider the curve :—

$$y = x^4 - 5x^2 + 4$$

$$\frac{dy}{dx} = 4x^3 - 10x$$

∴ Maxima or minima occurs if $4x^3 - 10x = 0$.

i.e., if $x = 0$ or $\pm \sqrt{\frac{5}{2}}$.

Now determine whether these points are maxima or minima.

Method 1.—

Consider the point $x = 0$; just before, $\frac{dy}{dx}$ is positive; just after, it is negative.

Therefore $x = 0$ is a maximum.

Consider the point $x = +\sqrt{\frac{5}{2}}$; just before, $\frac{dy}{dx}$ is negative; just after, it is positive.

Therefore $x = +\sqrt{\frac{5}{2}}$ is a minimum.

Consider the point $x = -\sqrt{\frac{5}{2}}$; just before, $\frac{dy}{dx}$ is negative; just after, it is positive.

Therefore $x = -\sqrt{\frac{5}{2}}$ is also a minimum.

Method 2.—

$$\frac{d^2y}{dx^2} = 12x^2 - 10$$

At $x = 0$, this is negative, therefore at $x = 0$ the curve has a maximum.

At $x = \pm\sqrt{\frac{5}{2}}$, this is positive, therefore at these points the curve has minima.

Thus the curve has a maximum at $x = 0$, and minima at $x = +\sqrt{\frac{5}{2}}$ and at $x = -\sqrt{\frac{5}{2}}$.

The curve is shown in Fig. 61.

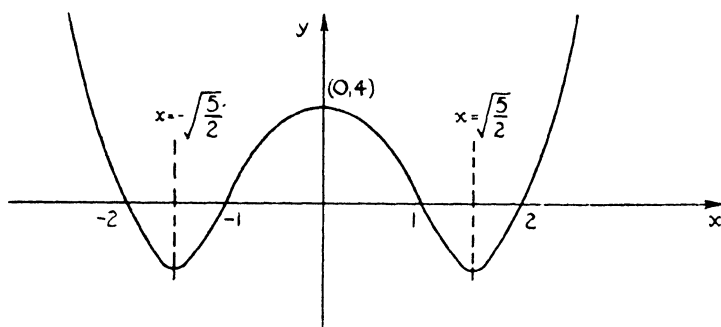


FIG. 61.—Graph of $y = x^4 - 5x^2 + 4$.

Example 2.—

What positive value of L will make

$\sqrt{(R^2 + \omega^2L^2)(G^2 + \omega^2C^2)} + RG - \omega^2LC$
a maximum or minimum?

Putting $y = \sqrt{(R^2 + \omega^2L^2)(G^2 + \omega^2C^2)} + RG - \omega^2LC$

$$\frac{dy}{dL} = \frac{1}{2} \frac{\sqrt{G^2 + \omega^2C^2}}{\sqrt{R^2 + \omega^2L^2}} \times 2\omega^2L - \omega^2C$$

For y to be a maximum or minimum, $\frac{dy}{dL} = 0$

$$\therefore \sqrt{\frac{G^2 + \omega^2C^2}{R^2 + \omega^2L^2}} = \frac{C}{L}$$

$$\text{i.e., } \frac{G^2 + \omega^2C^2}{R^2 + \omega^2L^2} = \frac{C^2}{L^2}$$

i.e., $L^2G^2 = R^2C^2$

or $L = \frac{RC}{G}$

This gives the value of L for y to be a maximum or minimum. It can be shown by differentiating again that this value of L gives a *minimum* value to y .

Differentiation of a vector

Vectors and complex numbers are differentiated in the same manner as other functions. If, however, the vector is given in polar form as r/θ , it must first be written in rectangular co-ordinate or in exponential form—*i.e.*, as $r \cos \theta + jr \sin \theta$ or as $r.e^{j\theta}$.

Consider the differential coefficient, with respect to t , of the rotating vector:—

$$OP = r/\omega t + \varphi \tag{110}$$

(a) This vector may be expressed in rectangular co-ordinates as:—

$$OP = r \cos (\omega t + \varphi) + jr \sin (\omega t + \varphi) \tag{111}$$

$$\begin{aligned} \text{Then } \frac{d}{dt}(OP) &= \frac{d}{dt} \left\{ r \cos (\omega t + \varphi) \right\} + j \cdot \frac{d}{dt} \left\{ r \sin (\omega t + \varphi) \right\} \\ &= r \cdot \frac{d}{dt} \cos (\omega t + \varphi) + \cos (\omega t + \varphi) \frac{dr}{dt} \\ &\quad + jr \cdot \frac{d}{dt} \sin (\omega t + \varphi) + j \sin (\omega t + \varphi) \frac{dr}{dt} \end{aligned}$$

In the case under consideration, $\frac{dr}{dt} = 0$; that is, the amplitude of the vector is not changing. Therefore:—

$$\begin{aligned} \frac{d}{dt}(OP) &= -\omega r \sin (\omega t + \varphi) + 0 + j\omega r \cos (\omega t + \varphi) + 0 \\ &= j\omega \{ r \cos (\omega t + \varphi) + jr \sin (\omega t + \varphi) \} \\ &= j\omega \cdot OP. \end{aligned}$$

(b) Alternatively, the vector OP may be expressed in exponential form as:—

$$\begin{aligned} OP &= r \cdot e^{j(\omega t + \varphi)} \tag{112} \\ &= r \cdot e^{j\omega t} \cdot e^{j\varphi} \\ &= (e^{j\omega t}) \cdot (r \cdot e^{j\varphi}) \end{aligned}$$

$$\begin{aligned} \text{Then } \frac{d}{dt}(OP) &= (r \cdot e^{j\varphi}) \frac{d}{dt} e^{j\omega t} + e^{j\omega t} \frac{d}{dt} (r \cdot e^{j\varphi}) \\ &= r \cdot e^{j\varphi} j \omega \cdot e^{j\omega t} + 0 \\ &= j\omega r \cdot e^{j\omega t} \cdot e^{j\varphi} \\ &= j\omega \cdot OP, \text{ as before.} \end{aligned}$$

Partial differentiation

Frequently a dependent variable is a function of two or more independent variables; for example, the volume V of a cylinder is determined by both the radius r and the length h , and one can write :—

$$V = f(r, h) \quad (113)$$

In order to determine the rate at which V increases or decreases when one of the independent variables changes, the other independent variable must be kept constant throughout the calculation. Thus, while determining the rate at which the volume of a cylinder varies with radius, the length h must be kept constant. A derivative of a variable with respect to one of several independent variables is known as a "partial derivative", and is represented by the symbol " ∂ " to distinguish it from the " d " in the ordinary derivative $\frac{dy}{dx}$. Then :—

$\frac{\partial V}{\partial r}$ = the rate at which V increases with respect to r , when all other relevant independent variables (e.g., h) are kept constant.

$\frac{\partial V}{\partial h}$ = the rate at which V increases with respect to h , when all other relevant independent variables (e.g., r) are kept constant.

Partial derivatives are evaluated in the normal manner, all variables other than the two concerned being treated as constants. Thus, for example,

$$\text{if : } V = \pi r^2 h \quad (114)$$

$$\text{Then } \frac{\partial V}{\partial r} = 2\pi r h \quad (115)$$

$$\text{and } \frac{\partial V}{\partial h} = \pi r^2 \quad (116)$$

If a small change δh is made in the value of h , whilst r is kept constant, the corresponding change δV is given by :—

$$\delta V \simeq \frac{\partial V}{\partial h} \delta h$$

Similarly, for a change δr in the value of r , h being kept constant :—

$$\delta V \simeq \frac{\partial V}{\partial r} \delta r$$

In general, if r and h are changed simultaneously, then :—

$$\delta V \simeq \frac{\partial V}{\partial r} \delta r + \frac{\partial V}{\partial h} \delta h$$

Second-order partial derivatives may be evaluated as follows. In the case of a function of two independent variables, e.g., $V = f(r, h)$,—there are four second-order partial derivatives, viz. :—

$\frac{\partial^2 V}{\partial r^2}$ = the rate at which $\frac{\partial V}{\partial r}$ increases with respect to r when h is kept constant.

$\frac{\partial^2 V}{\partial h^2}$ = the rate at which $\frac{\partial V}{\partial h}$ increases with respect to h when r is kept constant.

$\frac{\partial^2 V}{\partial r \partial h}$ = the rate at which $\frac{\partial V}{\partial h}$ increases with respect to r when h is kept constant.

$\frac{\partial^2 V}{\partial h \partial r}$ = the rate at which $\frac{\partial V}{\partial r}$ increases with respect to h when r is kept constant.

Taking as an example the function $V = \pi r^2 h$, the second-order partial derivatives are found as follows :—

$$\frac{\partial^2 V}{\partial r^2} = \frac{\partial}{\partial r} \left(\frac{\partial V}{\partial r} \right) = \frac{\partial}{\partial r} (2\pi r h) = 2\pi h$$

$$\frac{\partial^2 V}{\partial h^2} = \frac{\partial}{\partial h} \left(\frac{\partial V}{\partial h} \right) = \frac{\partial}{\partial h} (\pi r^2) = 0$$

$$\frac{\partial^2 V}{\partial r \partial h} = \frac{\partial}{\partial r} \left(\frac{\partial V}{\partial h} \right) = \frac{\partial}{\partial r} (\pi r^2) = 2\pi r$$

$$\frac{\partial^2 V}{\partial h \partial r} = \frac{\partial}{\partial h} \left(\frac{\partial V}{\partial r} \right) = \frac{\partial}{\partial h} (2\pi r h) = 2\pi r.$$

It will be noted that, in this simple case, $\frac{\partial^2 V}{\partial r \partial h} = \frac{\partial^2 V}{\partial h \partial r}$, a result that is true for all those functions of two independent variables which are likely to be encountered by the student.

INTEGRAL CALCULUS

Integration

Integration is the reverse process to differentiation.

If $\frac{dy}{dx} = f'(x)$

then y is the "integral" of $f'(x)$.

This is written as :—

$$y = \int f'(x) dx$$

There is no complete set of rules for integration. In fact, in certain cases, the results are unknown. The process depends upon remembering the results of differentiation.

Consider the integral of x^n .

From a knowledge of differentiation :—

$$\frac{d}{dx} (x^{n+1}) = (n+1) x^n$$

Hence $\frac{d}{dx} \left(\frac{1}{n+1} \cdot x^{n+1} \right) = \frac{n+1}{n+1} x^n = x^n$

Thus $\int x^n dx = \frac{1}{n+1} x^{n+1} + C$ (117)

The constant C occurs in the complete integral; for, when differentiated, any constant becomes zero.

Equation 117 is true in all cases except when $n = -1$.

It will be remembered that :

$$\frac{d}{dx} (\log_e x) = \frac{1}{x}$$

$$\text{Hence} \quad \int x^{-1} dx = \log_e x + C \quad (118)$$

Example.—

Integrate $5x^3 + 3$.

The x^3 must have come from an x^4 term; x^4 itself when differentiated produces $4x^3$ and not $5x^3$. Hence the integral of the first term must be $\frac{5}{4}x^4$. The integral of the second term is similarly $3x$. The complete integral is $\frac{5}{4}x^4 + 3x + C$. *Ans.*

Consider the integral of $(ax + b)^n$.

$$\frac{d}{dx} (ax + b)^{n+1} = a(n+1)(ax + b)^n$$

$$\text{Hence} \quad \frac{d}{dx} \left\{ \frac{1}{a(n+1)} (ax + b)^{n+1} \right\} = (ax + b)^n$$

$$\text{Thus} \quad \int (ax + b)^n dx = \frac{1}{a(n+1)} (ax + b)^{n+1} + C \quad (119)$$

Example.—

Integrate $(2x + 3)^4$.

The answer may be written down straight away from equation 119.

$$\begin{aligned} \int (2x + 3)^4 dx &= \frac{1}{2 \times 5} (2x + 3)^5 + C \\ &= \frac{1}{10} \cdot (2x + 3)^5 + C \quad \text{Ans.} \end{aligned}$$

The general rule for integration is to manipulate the integral into such a form that it is directly integrable using equations 117, 118 or 119.

Expansion

Frequently an expression can be converted into an integrable form by expanding.

Consider the integral of $(x^2 + 3)(x - 5)$.

$$\begin{aligned} \int (x^2 + 3)(x - 5) dx &= \int (x^3 - 5x^2 + 3x - 15) dx \\ &= \frac{x^4}{4} - \frac{5}{3}x^3 + \frac{3}{2}x^2 - 15x + C. \end{aligned}$$

Integrals resulting in logs

If an expression $\log_e f(x)$ is differentiated, the result is $\frac{f'(x)}{f(x)}$ and any expression of this form may be integrated directly as

$\log_e f(x)$. That is, if the numerator of an expression is the differential coefficient of the denominator, then the integral is the logarithm (to base e) of the denominator.

Consider the integral of $\tan x$.

$$\int \tan x \, dx = \int \frac{\sin x}{\cos x} \, dx = -\int \frac{(-\sin x)}{\cos x} \, dx = -\log_e \cos x + C$$

Example.—

Integrate
$$\frac{12x + 4}{3x^2 + 2x + 6}$$

In this case the numerator is twice the differential coefficient of the denominator.

$$\begin{aligned} \int \frac{12x + 4}{3x^2 + 2x + 6} \, dx &= 2 \int \frac{6x + 2}{3x^2 + 2x + 6} \, dx \\ &= 2 \log_e (3x^2 + 2x + 6) + C. \quad \text{Ans.} \end{aligned}$$

Partial fractions

When the denominator of an expression may be factorised, the integral may often be found by rearranging the expression as partial fractions.

Consider the integral of $\frac{x + 1}{x^2 + 5x + 6}$

$$\frac{x + 1}{x^2 + 5x + 6} = \frac{x + 1}{(x + 3)(x + 2)} = \frac{2}{x + 3} - \frac{1}{x + 2}$$

Thus
$$\begin{aligned} \int \frac{x + 1}{x^2 + 5x + 6} \, dx &= \int \left[\frac{2}{x + 3} - \frac{1}{x + 2} \right] \, dx \\ &= \int \frac{2}{x + 3} \, dx - \int \frac{1}{x + 2} \, dx \\ &= 2 \log_e (x + 3) - \log_e (x + 2) + C \\ &= \log_e \frac{(x + 3)^2}{(x + 2)} + C \end{aligned}$$

Integration by parts

This is the converse of the rule for differentiating a product, and is used when the expression consists of the product of two different types of function of x , e.g. $x^3 \log_e x$.

It will be remembered that :

$$\frac{d}{dx} (uv) = u \frac{dv}{dx} + v \frac{du}{dx} \quad (\text{where } u \text{ and } v \text{ are functions of } x)$$

$$\therefore uv = \int \left(u \cdot \frac{dv}{dx} \right) dx + \int \left(v \cdot \frac{du}{dx} \right) dx$$

Let $w = \frac{dv}{dx} \quad \therefore v = \int w \cdot dx$

$$\text{Hence } u \int w \cdot dx = \int u \cdot w \cdot dx + \int \left(\int w \cdot dx \cdot \frac{du}{dx} \right) dx$$

$$\therefore \int u \cdot w \cdot dx = u \int w \cdot dx - \int \left(\int w \cdot dx \cdot \frac{du}{dx} \right) dx \quad (120)$$

Expressed in words, equation 120 becomes: *the integral of a product equals the first term times the integral of the second term, minus the integral of (the integral of the second term times the differential of the first).*

Consider the integral of $x^3 \log_e x$.

Since the differential coefficient of $\log_e x$ is known, but the integral of $\log_e x$ has not yet been encountered, take $w = x^3$ and $u = \log_e x$.

$$\begin{aligned} \text{Hence } \int x^3 \cdot \log_e x \, dx &= \int \log_e x \cdot x^3 \, dx \\ &= \log_e x \cdot \int x^3 \, dx - \int \left(\int x^3 \, dx \cdot \frac{d}{dx} \log_e x \right) dx \\ &= \log_e x \cdot \frac{x^4}{4} - \int \left(\frac{x^4}{4} \cdot \frac{1}{x} \right) dx \\ &= \frac{x^4}{4} \log_e x - \int \frac{x^3}{4} \, dx \\ &= \frac{x^4}{4} \log_e x - \frac{x^4}{16} \end{aligned}$$

For the complete solution a constant C must be added.

$$\text{Hence } \int x^3 \cdot \log_e x \, dx = \frac{x^4}{4} \log_e x - \frac{x^4}{16} + C$$

This method may be used to determine the integral of $\log_e x$ by letting:—

$$w = 1 \text{ and } u = \log_e x$$

$$\begin{aligned} \text{Hence } \int \log_e x \, dx &= \log_e x \cdot \int 1 \, dx - \int \left(\int 1 \, dx \cdot \frac{d}{dx} \log_e x \right) dx \\ &= x \log_e x - \int x \cdot \frac{1}{x} \, dx \\ &= x \log_e x - x \end{aligned}$$

Adding a constant for the complete solution gives:—

$$\int \log_e x \, dx = x \log_e x - x + C.$$

Trigonometrical transformations

Products and powers of \sin and \cos may be integrated by changing to the form $\sin nx$ and $\cos nx$.

Consider the integral of $\sin^3 x$.

This cannot be integrated in its present form, hence apply the identity :—

$$\cos 2x = 1 - 2 \sin^2 x$$

Thus $\sin^2 x = \frac{1}{2}(1 - \cos 2x)$

Hence
$$\begin{aligned} \int \sin^2 x \, dx &= \int \frac{1}{2}(1 - \cos 2x) \, dx = \frac{1}{2} \int (1 - \cos 2x) \, dx \\ &= \frac{1}{2} \int 1 \, dx - \frac{1}{2} \int \cos 2x \, dx \\ &= \frac{x}{2} - \frac{\sin 2x}{4} + C \end{aligned}$$

Integration by substitution

The process of integration may frequently be simplified by making a substitution. Such a substitution may be either algebraic or trigonometric. It is important to remember that the “ dx ” term must be converted into terms of the new variable.

Algebraic substitutions.—Consider the integral of $x(4 - 2x^2)^6$

This may be determined by making an algebraic substitution.

Let $4 - 2x^2 = u$

Then $-4x \, dx = du$

Hence
$$\begin{aligned} \int x(4 - 2x^2)^6 \, dx &= \int -\frac{1}{4} u^6 \, du \\ &= -\frac{u^7}{28} + C \\ &= -\frac{(4 - 2x^2)^7}{28} + C \end{aligned}$$

Trigonometrical substitutions.—If the expression to be integrated contains :

- (i) $\sqrt{a^2 - x^2}$, put $x = a \sin \theta$ or $x = a \cos \theta$
- (ii) $\sqrt{a^2 + x^2}$, put $x = a \tan \theta$
- (iii) $\sqrt{x^2 - a^2}$, put $x = a \sec \theta$

Consider the integral of $\frac{1}{\sqrt{a^2 - x^2}}$

This root can conveniently be removed by putting $x = a \sin \theta$, so that :—

$$\sqrt{a^2 - x^2} = \sqrt{a^2 - a^2 \sin^2 \theta} = \sqrt{a^2 \cos^2 \theta} = a \cos \theta.$$

The “ dx ” has to be turned into an expression involving θ .

As $x = a \sin \theta$

$\therefore \frac{dx}{d\theta} = a \cos \theta$

$\therefore dx = a \cos \theta d\theta$

(This line can be obtained without the intermediate step.)

Hence
$$\int \frac{dx}{\sqrt{a^2 - x^2}} = \int \frac{a \cos \theta d\theta}{a \cos \theta} = \int 1 \cdot d\theta = \theta + C$$

But $\sin \theta = \frac{x}{a} \quad \therefore \theta = \sin^{-1} \frac{x}{a}$

Thus $\int \frac{dx}{\sqrt{a^2 - x^2}} = \sin^{-1} \frac{x}{a} + C$

Example.—

Find the integral of $\frac{\sqrt{16 - x^2}}{x^2}$

Put $x = 4 \cos \theta, \quad \therefore \theta = \cos^{-1} \frac{x}{4}$
 $\therefore dx = -4 \sin \theta d\theta.$

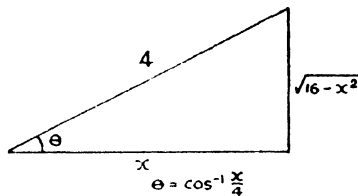


FIG. 62.

In addition, from Fig. 62 :—

$$\sin \theta = \frac{\sqrt{16 - x^2}}{4}, \quad \cos \theta = \frac{x}{4}, \quad \tan \theta = \frac{\sqrt{16 - x^2}}{x}$$

$$\begin{aligned} \text{Hence } \int \frac{\sqrt{16 - x^2}}{x^2} dx &= \int \frac{\sqrt{16 - 16 \cos^2 \theta}}{16 \cos^2 \theta} \cdot -4 \sin \theta d\theta \\ &= - \int \frac{\sin^2 \theta}{\cos^2 \theta} d\theta \\ &= - \int \frac{1 - \cos^2 \theta}{\cos^2 \theta} d\theta \\ &= - \int \sec^2 \theta d\theta + \int 1 d\theta \\ &= - \tan \theta + \theta + C \\ &= - \frac{\sqrt{16 - x^2}}{x} + \cos^{-1} \frac{x}{4} + C \quad \text{Ans.} \end{aligned}$$

Area under a curve

The area $OMPN$ under the curve $y = f(x)$ and bounded by the axes and the ordinate NP is a function of x (the co-ordinate of P) (see Fig. 63). The area cannot be found at once, but its derivatives can. For if x is increased to $(x + \delta x)$, the area A increases by an element δA , which is equal to the area $PP'N'N$. To a first approximation, this is equal to $y \cdot \delta x$.

$$\therefore \delta A = y \delta x \quad \text{or} \quad \frac{\delta A}{\delta x} = y$$

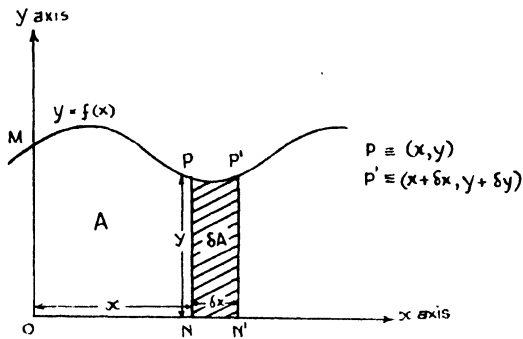


FIG. 63.—Infinitely small portion of the area under a curve.

∴ taking the limit as $\delta x \rightarrow 0$, the inaccuracy disappears and :—

$$\frac{dA}{dx} = y = f(x)$$

or

$$A = \int f(x) dx \quad (121)$$

Hence the area of a curve up to the point x is found by integrating,

Definite integrals

Normally, the area is required between two ordinates, as at x_1 and x_2 in Fig. 64. This is found by calculating the area up to x_2 and subtracting from it the area up to x_1 . If $A = \int f(x) dx$,

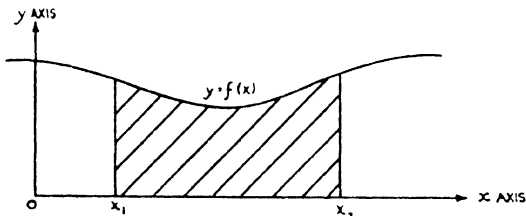


FIG. 64.—Finite area under a curve.

the notation used for this is $[A]_{x_1}^{x_2}$ i.e., the value of A when $x = x_2$ minus the value of A when $x = x_1$. This is also written $\int_{x_1}^{x_2} f(x) dx$, and is known as a definite integral.

Note that as a result of subtraction the constant of integration disappears.

Example.—

Find the area under the curve $y = 3x^2 + 8x + 7$ from $x = 1$ to $x = 2$, i.e., $\int_1^2 (3x^2 + 8x + 7) dx$

Evaluating the definite integral :—

$$\begin{aligned}\text{Required area} &= [x^3 + 4x^2 + 7x]_1^8 \\ &= (8 + 16 + 14) - (1 + 4 + 7) = 38 - 12 = 26\end{aligned}$$

Substitutions in definite integrals.—Note that if the variable is changed in order to simplify the integration, the answer need not be turned back into terms of the original variable, provided that the limits are changed to correspond with the substitution.

Example.—

Find the area of the circle $x^2 + y^2 = r^2$. It is easiest to calculate the area of one quadrant, taking $y = \sqrt{r^2 - x^2}$ from $x = 0$ to $x = r$, i.e., $\int_0^r \sqrt{r^2 - x^2} dx$

A substitution has to be made :—

$$\text{let } x = r \sin \theta$$

$$\therefore dx = r \cos \theta d\theta$$

$$\text{and } \sqrt{r^2 - x^2} = \sqrt{r^2 - r^2 \sin^2 \theta} = r \cos \theta$$

Therefore the integral is $\int_{x=0}^{x=r} r \cos \theta \cdot r \cos \theta d\theta = r^2 \int_{x=0}^{x=r} \cos^2 \theta d\theta$

The limits are in terms of x , and must be changed to θ .

$x = r$ corresponds to $\theta = \frac{\pi}{2}$; $x = 0$ to $\theta = 0$.

$$\therefore \text{area} = r^2 \int_0^{\frac{\pi}{2}} \cos^2 \theta d\theta$$

To integrate $\cos^2 \theta$, use the identity $\cos^2 \theta = \frac{1}{2} (1 + \cos 2\theta)$

$$\begin{aligned}\therefore \int &= \frac{1}{2} r^2 \int_0^{\frac{\pi}{2}} (1 + \cos 2\theta) d\theta \\ &= \frac{r^2}{2} \left[\theta + \frac{\sin 2\theta}{2} \right]_0^{\frac{\pi}{2}} \\ &= \frac{r^2}{2} \left[\frac{\pi}{2} + 0 - 0 - 0 \right] \\ &= \frac{\pi r^2}{4}\end{aligned}$$

This is the area of $\frac{1}{4}$ of the circle. Hence the total area = πr^2 .

Mean height of curve.—The mean height of a curve is obtained by finding the area of the curve and dividing it by the length of the base.

Example.—

Find the mean height of the curve $y = A^2 \sin^2 \theta$. If this curve be drawn, it is seen to extend along the θ -axis from $-\infty$ to $+\infty$. It is, however, *recurrent*, so that it is sufficient to consider the portion of the curve between $\theta = 0$ and $\theta = 2\pi$; outside these limits, the curve merely repeats the cycle of values it assumes within them. Its mean height can therefore be found by finding the area over one complete cycle (e.g., from $\theta = 0$ to $\theta = 2\pi$, or equally, from $-\pi$ to $+\pi$, or from -2π to 0) and dividing by the length of the base (2π).

$$y = A^2 \sin^2 \theta$$

\therefore the area over one cycle is given by

$$\begin{aligned} \int_0^{2\pi} y \, d\theta &= \int_0^{2\pi} A^2 \sin^2 \theta \, d\theta \\ &= \frac{1}{2} A^2 \int_0^{2\pi} (1 - \cos 2\theta) \, d\theta \\ &= \frac{1}{2} A^2 \left[\theta \right]_0^{2\pi} - \frac{1}{2} A^2 \left[\frac{1}{2} \sin 2\theta \right]_0^{2\pi} \\ &= \frac{1}{2} A^2 [2\pi - 0] - \frac{1}{2} A^2 [0 - 0] \\ &= \pi A^2 \end{aligned}$$

The mean height h of the curve is therefore:—

$$\begin{aligned} h &= \frac{\pi A^2}{2\pi} \\ &= \frac{A^2}{2} \end{aligned}$$

This might also be expressed by saying that $\frac{A^2}{2}$ is the mean or average value of the quantity $A^2 \sin^2 \theta$.

CIRCULAR AND HYPERBOLIC FUNCTIONS

Maclaurin's theorem

Many functions of x can be expanded as a series of powers of x (e.g., $(1+x)^n$, e^x , etc.). Maclaurin's theorem enables an expansion to be found for a general function of x , i.e., $y = f(x)$.

$$\text{Let } f(x) = A_0 + A_1 x + A_2 x^2 + A_3 x^3 + A_4 x^4 + \dots$$

Differentiating:—

$$\begin{aligned} f'(x) &= A_1 + 2 \cdot A_2 x + 3 \cdot A_3 x^2 + 4 \cdot A_4 x^3 + \dots \\ f''(x) &= 2 \cdot A_2 + 2 \cdot 3 \cdot A_3 x + 3 \cdot 4 \cdot A_4 x^2 + \dots \\ f'''(x) &= 2 \cdot 3 \cdot A_3 + 2 \cdot 3 \cdot 4 \cdot A_4 x + \dots \\ f''''(x) &= 2 \cdot 3 \cdot 4 \cdot A_4 + \dots \end{aligned}$$

This is true for all values of x , hence, when $x = 0$:—

$$A_0 = f(0)$$

$$A_1 = f'(0)$$

$$A_2 = \frac{f''(0)}{2} = \frac{f''(0)}{\underline{2}}$$

$$A_3 = \frac{f'''(0)}{2 \cdot 3} = \frac{f'''(0)}{\underline{3}}$$

$$A_4 = \frac{f''''(0)}{2 \cdot 3 \cdot 4} = \frac{f''''(0)}{\underline{4}}$$

Thus

$$f(x) = f(0) + x f'(0) + \frac{x^2}{\underline{2}} f''(0) + \frac{x^3}{\underline{3}} f'''(0) + \frac{x^4}{\underline{4}} f''''(0) + \dots \quad (122)$$

where $f''(0)$, *etc.*, means the value of $f''(x)$, *etc.*, when $x = 0$. This is known as "*Maclaurin's theorem*".

If no derivatives of $f(x)$ vanish, this expansion will involve an infinite number of terms. The reader should verify that it holds for $(1+x)^n$ and e^x .

Circular functions

A number of important series can be obtained from this theorem.

Take, for example, $f(x) = \sin x$. To find the series, one must calculate the successive derivatives, and their value when $x = 0$.

$$\begin{aligned} f(x) &= \sin x & \therefore & f(0) = 0 \\ f'(x) &= \cos x & \therefore & f'(0) = 1 \\ f''(x) &= -\sin x & \therefore & f''(0) = 0 \\ f'''(x) &= -\cos x & \therefore & f'''(0) = -1 \\ f''''(x) &= \sin x & \therefore & f''''(0) = 0, \text{ etc.} \end{aligned}$$

Hence the series is :—

$$\sin x = x - \frac{x^3}{\underline{3}} + \frac{x^5}{\underline{5}} - \frac{x^7}{\underline{7}} + \dots \quad (123)$$

Similarly

$$\cos x = 1 - \frac{x^2}{\underline{2}} + \frac{x^4}{\underline{4}} - \frac{x^6}{\underline{6}} + \dots \quad (124)$$

Since $e^x = 1 + x + \frac{x^2}{\underline{2}} + \frac{x^3}{\underline{3}} + \dots$

the expansion for e^{jx} is :—

$$e^{jx} = 1 + jx + \frac{(jx)^2}{\underline{2}} + \frac{(jx)^3}{\underline{3}} + \dots$$

$$\therefore e^{jx} = 1 + jx - \frac{x^2}{2} - j\frac{x^3}{3} + \frac{x^4}{4} + j\frac{x^5}{5} - \frac{x^6}{6} \dots$$

$$\therefore e^{jx} = (1 - \frac{x^2}{2} + \frac{x^4}{4} \dots) + j(x - \frac{x^3}{3} + \frac{x^5}{5} \dots)$$

Hence $e^{jx} = \cos x + j \sin x$ (125)

Similarly $e^{-jx} = \cos x - j \sin x$ (126)

This shows that the trigonometrical ratios can be treated from an algebraical aspect as well as from a geometrical aspect. It is possible to prove trigonometrical identities from these results, e.g., multiplying together the two equations just obtained gives:—

$$1 = \cos^2 x + \sin^2 x$$

Both $\cos x$ and $\sin x$ may be obtained as expressions involving e by adding and subtracting these two equations. From $\cos x$ and $\sin x$, expressions for $\sec x$, $\operatorname{cosec} x$, $\tan x$, and $\cot x$ follow.

Thus:—

$$\cos x = \frac{e^{jx} + e^{-jx}}{2} \tag{127}$$

$$\sin x = \frac{e^{jx} - e^{-jx}}{j2} \tag{128}$$

Hence $\tan x = -j \cdot \frac{(e^{jx} - e^{-jx})}{(e^{jx} + e^{-jx})}$ (129)

$$\sec x = \frac{2}{e^{jx} + e^{-jx}} \tag{130}$$

$$\operatorname{cosec} x = \frac{j2}{e^{jx} - e^{-jx}} \tag{131}$$

$$\cot x = j \frac{e^{jx} + e^{-jx}}{e^{jx} - e^{-jx}} \tag{132}$$

Hyperbolic functions

It has been shown that $\cos x = \frac{e^{jx} + e^{-jx}}{2}$. The value of $\frac{e^x + e^{-x}}{2}$ is also important, and this is known as “cosh x ”, or the “hyperbolic cosine” of x .

Thus: $\cosh x = \frac{e^x + e^{-x}}{2}$ (133)

Similarly: $\sinh x = \frac{e^x - e^{-x}}{2}$ (134)

Whence: $\cosh x + \sinh x = e^x$ (135)

and $\cosh x - \sinh x = e^{-x}$ (136)

These hyperbolic functions bear the same relation to a hyperbola as sine and cosine do to a circle (see Appendix I).

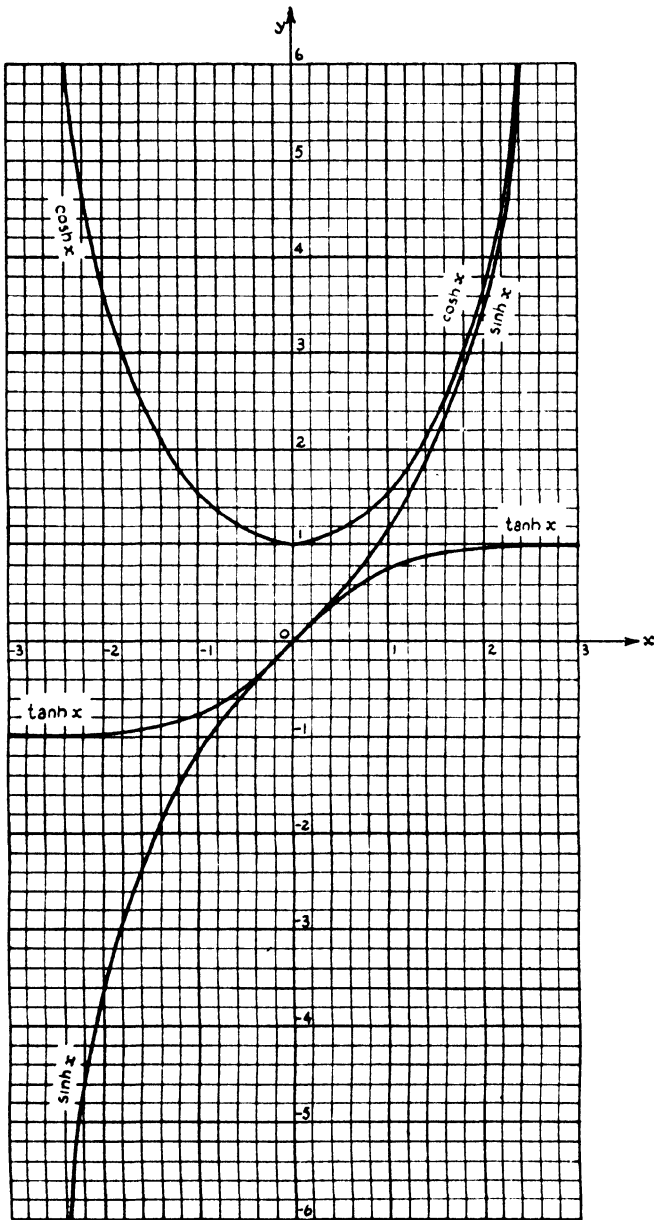


FIG. 65.—Graphs of the hyperbolic functions $\sinh x$, $\cosh x$ and $\tanh x$.

Since :—
$$e^x = 1 + x + \frac{x^2}{2} + \frac{x^3}{3} + \frac{x^4}{4} + \dots$$

and
$$e^{-x} = 1 - x + \frac{x^2}{2} - \frac{x^3}{3} + \frac{x^4}{4} - \dots$$

it follows that the series for the hyperbolic functions are :—

$$\cosh x = 1 + \frac{x^2}{2} + \frac{x^4}{4} + \dots \tag{137}$$

$$\sinh x = x + \frac{x^3}{3} + \frac{x^5}{5} + \dots \tag{138}$$

From the definitions, it can be seen that the following conversion rules apply :—

Circular to hyperbolic

Hyperbolic to circular

$$\sin x = -j \cdot \sinh jx \tag{139} \qquad \sinh x = -j \cdot \sin jx \tag{143}$$

$$\cos x = \cosh jx \tag{140} \qquad \cosh x = \cos jx \tag{142}$$

$$\sin jx = j \cdot \sinh x \tag{141} \qquad \sinh jx = j \cdot \sin x \tag{144}$$

$$\cos jx = \cosh x \tag{142} \qquad \cosh jx = \cos x \tag{140}$$

Tanh x is defined as
$$\frac{\sinh x}{\cosh x} = \frac{e^x - e^{-x}}{e^x + e^{-x}} = \frac{e^{2x} - 1}{e^{2x} + 1} \tag{145}$$

therefore
$$\tanh x = \frac{-j \sin jx}{\cos jx} = -j \tan jx \tag{146}$$

and
$$\tan x = -j \tanh jx \tag{147}$$

Fig. 65 gives the graphs of the hyperbolic functions.

Note that $\cosh x$ is always greater than 1, and that $\tanh x$ lies between +1 and -1; and that, unlike circular functions, hyperbolic functions are not periodic.

coth x is defined as
$$\frac{\cosh x}{\sinh x} = \frac{1}{\tanh x} = \frac{e^x + e^{-x}}{e^x - e^{-x}} = \frac{e^{2x} + 1}{e^{2x} - 1} \tag{148}$$

sech x is defined as
$$\frac{1}{\cosh x} = \frac{2}{e^x + e^{-x}} \tag{149}$$

cosech x is defined as
$$\frac{1}{\sinh x} = \frac{2}{e^x - e^{-x}} \tag{150}$$

Hyperbolic identities

Hyperbolic identities are similar to the corresponding circular identities, and may be readily deduced from them. As a general rule, identities hold if “ $-\sinh^2$ ” is written instead of “ \sin^2 ”, and “ \cosh^2 ” instead of “ \cos^2 ”.

Thus
$$\cos^2 x + \sin^2 x = 1$$
 becomes
$$\cosh^2 x - \sinh^2 x = 1 \tag{151}$$

and
$$\cos 2x = \cos^2 x - \sin^2 x$$
 becomes
$$\cosh 2x = \cosh^2 x + \sinh^2 x \tag{152}$$

$$= 2 \cosh^2 x - 1 \tag{153}$$

$$= 1 + 2 \sinh^2 x \tag{154}$$

It can be shown that :—

$$\sinh (A + B) = \sinh A \cosh B + \cosh A \sinh B \quad (155)$$

$$\sinh (A - B) = \sinh A \cosh B - \cosh A \sinh B \quad (156)$$

$$\cosh (A + B) = \cosh A \cosh B + \sinh A \sinh B \quad (157)$$

$$\cosh (A - B) = \cosh A \cosh B - \sinh A \sinh B \quad (158)$$

Dividing equation 155 by equation 157 gives :—

$$\tanh (A + B) = \frac{\tanh A + \tanh B}{1 + \tanh A \tanh B} \quad (159)$$

Dividing equation 156 by equation 158 gives :—

$$\tanh (A - B) = \frac{\tanh A - \tanh B}{1 - \tanh A \tanh B} \quad (160)$$

Putting $A = B = x$ in equation 155 gives :—

$$\sinh 2x = 2 \cdot \sinh x \cdot \cosh x \quad (161)$$

Putting $A = B = x$ in equation 157 gives equation 152 above.

It will be noted that :—

$$\begin{aligned} \tanh x &= \frac{\sinh x}{\cosh x} \\ &= \frac{2 \cdot \sinh^2 x}{2 \cdot \sinh x \cdot \cosh x} \\ &= \frac{\cosh 2x - 1}{\sinh 2x} \end{aligned} \quad (162)$$

All the above identities may be verified using equations 133 and 134.

Differentiation of hyperbolic functions

The differential coefficients of hyperbolic functions can easily be obtained by using the exponential form of the functions. Thus, for example :—

$$\begin{aligned} \frac{d}{dx} (\sinh x) &= \frac{d}{dx} \left(\frac{e^x - e^{-x}}{2} \right) \\ &= \frac{d}{dx} \left(\frac{1}{2} e^x - \frac{1}{2} e^{-x} \right) \\ &= \frac{1}{2} e^x + \frac{1}{2} e^{-x} \\ &= \frac{e^x + e^{-x}}{2} \\ &= \cosh x \end{aligned} \quad (163)$$

Some of the more important derivatives are given in Table III while a further list is given in Appendix I.

TABLE III
Differential coefficients of some hyperbolic functions

y	$\frac{dy}{dx}$
$\sinh x$	$\cosh x$
$\cosh x$	$\sinh x$
$\tanh x$	$\operatorname{sech}^2 x$
$\coth x$	$-\operatorname{cosech}^2 x$
$\operatorname{sech} x$	$-\operatorname{sech} x \tanh x$
$\operatorname{cosech} x$	$-\operatorname{cosech} x \coth x$
$\sinh^{-1} x$	$\frac{1}{\sqrt{1+x^2}}$
$\cosh^{-1} x$	$\frac{1}{\sqrt{x^2-1}}$
$\tanh^{-1} x$	$\frac{1}{1-x^2}$

Complex hyperbolic functions

Expressions such as $\cosh (\alpha + j\beta)$ are often encountered in transmission theory. Their values can be calculated from first principles and tables.

If $\sinh (\alpha + j\beta) = A + jB$, one can find A and B in terms of α and β .

$$\begin{aligned} \text{For } A + jB &= \sinh (\alpha + j\beta) \\ &= \sinh \alpha \cosh j\beta + \cosh \alpha \sinh j\beta \\ &= \sinh \alpha \cos \beta + j \cosh \alpha \sin \beta \end{aligned}$$

Equating real and imaginary parts :—

$$A = \sinh \alpha \cos \beta$$

and $B = \cosh \alpha \sin \beta$

Similarly, if $\cosh (\alpha + j\beta) = A + jB$, one can find A and B in terms of α and β .

$$\begin{aligned} A + jB &= \cosh (\alpha + j\beta) \\ &= \cosh \alpha \cosh j\beta + \sinh \alpha \sinh j\beta \\ &= \cosh \alpha \cos \beta + j \sinh \alpha \sin \beta. \end{aligned}$$

Equating real and imaginary parts :—

$$A = \cosh \alpha \cos \beta$$

and $B = \sinh \alpha \sin \beta$

Example 1.—Evaluate $\cosh \left(3 + j\frac{\pi}{4} \right)$

$$\begin{aligned} \cosh \left(3 + j\frac{\pi}{4} \right) &= \cosh 3 \cosh j\frac{\pi}{4} + \sinh 3 \sinh j\frac{\pi}{4} \\ &= \cosh 3 \cos \frac{\pi}{4} + j \sinh 3 \sin \frac{\pi}{4} \\ &= 10.07 \times 0.7071 + j 10.02 \times 0.7071 \\ &= 7.12 + j 7.07 \end{aligned}$$

Example 2.—Show that $\tanh\left(\alpha + j\frac{\pi}{2}\right) = \coth \alpha$

$$\begin{aligned}\sinh\left(\alpha + j\frac{\pi}{2}\right) &= \sinh \alpha \cosh j\frac{\pi}{2} + \cosh \alpha \sinh j\frac{\pi}{2} \\ &= \sinh \alpha \cos \frac{\pi}{2} + j \cosh \alpha \sin \frac{\pi}{2} \\ &= j \cosh \alpha\end{aligned}$$

and

$$\begin{aligned}\cosh\left(\alpha + j\frac{\pi}{2}\right) &= \cosh \alpha \cosh j\frac{\pi}{2} + \sinh \alpha \sinh j\frac{\pi}{2} \\ &= \cosh \alpha \cos \frac{\pi}{2} + j \sinh \alpha \sin \frac{\pi}{2} \\ &= j \sinh \alpha\end{aligned}$$

$$\therefore \tanh\left(\alpha + j\frac{\pi}{2}\right) = \frac{\sinh\left(\alpha + j\frac{\pi}{2}\right)}{\cosh\left(\alpha + j\frac{\pi}{2}\right)} = \frac{j \cosh \alpha}{j \sinh \alpha} = \coth \alpha \quad \text{Q.E.D.}$$

The converse of this type of problem is less simple—*i.e.*, given $\tanh(\alpha + j\beta) = A + jB$, find α and β .

$$\text{If} \quad \tanh(\alpha + j\beta) = A + jB,$$

$$\text{then} \quad \tanh(\alpha - j\beta) = A - jB,$$

since if an identity is true for $+j$, it is also true for $-j$.

$$\begin{aligned}\tanh[(\alpha + j\beta) + (\alpha - j\beta)] &= \frac{\tanh(\alpha + j\beta) + \tanh(\alpha - j\beta)}{1 + \tanh(\alpha + j\beta) \cdot \tanh(\alpha - j\beta)} \\ \therefore \quad \tanh 2\alpha &= \frac{A + jB + A - jB}{1 + (A + jB)(A - jB)} \\ &= \frac{2A}{1 + A^2 + B^2}\end{aligned}$$

Also

$$\begin{aligned}\tanh[(\alpha + j\beta) - (\alpha - j\beta)] &= \frac{\tanh(\alpha + j\beta) - \tanh(\alpha - j\beta)}{1 - \tanh(\alpha + j\beta) \cdot \tanh(\alpha - j\beta)} \\ \therefore \quad \tanh 2j\beta &= \frac{A + jB - A + jB}{1 - (A + jB)(A - jB)} \\ &= \frac{2jB}{1 - A^2 - B^2}\end{aligned}$$

$$\therefore \quad -j \tanh 2j\beta = \frac{2B}{1 - A^2 - B^2}$$

$$\therefore \quad \tan 2\beta = \frac{2B}{1 - A^2 - B^2}$$

Thus
$$\tanh 2\alpha = \frac{2A}{1 + A^2 + B^2} \tag{164}$$

and
$$\tan 2\beta = \frac{2B}{1 - (A^2 + B^2)} \tag{165}$$

Those roots for β must be chosen for which $\tan \beta$ has the same sign as B .

If the hyperbolic function of a complex number is required in the polar form $r \angle \theta$, the following identities may be used :—

$$\sinh(\alpha + j\beta) = \sqrt{\sinh^2 \alpha + \sin^2 \beta} \angle \tan^{-1}(\coth \alpha \cdot \tan \beta) \tag{166}$$

$$\cosh(\alpha + j\beta) = \sqrt{\sinh^2 \alpha + \cos^2 \beta} \angle \tan^{-1}(\tanh \alpha \cdot \tan \beta) \tag{167}$$

These identities may be verified as follows :—

Let $\sinh(\alpha + j\beta)$ equal a vector $r \angle \theta$.

$$\begin{aligned} \sinh(\alpha + j\beta) &= \sinh \alpha \cdot \cosh j\beta + \cosh \alpha \cdot \sinh j\beta \\ &= \sinh \alpha \cdot \cos \beta + j \cosh \alpha \cdot \sin \beta \end{aligned}$$

$$\begin{aligned} \therefore r^2 &= \sinh^2 \alpha \cdot \cos^2 \beta + \cosh^2 \alpha \cdot \sin^2 \beta \\ &= \sinh^2 \alpha \cdot (1 - \sin^2 \beta) + (1 + \sinh^2 \alpha) \cdot \sin^2 \beta \\ &= \sinh^2 \alpha - \sinh^2 \alpha \cdot \sin^2 \beta + \sin^2 \beta + \sinh^2 \alpha \cdot \sin^2 \beta \\ &= \sinh^2 \alpha + \sin^2 \beta \end{aligned}$$

$$\therefore r = \sqrt{\sinh^2 \alpha + \sin^2 \beta}$$

$$\begin{aligned} \text{Also } \theta &= \tan^{-1} \left(\frac{\cosh \alpha \cdot \sin \beta}{\sinh \alpha \cdot \cos \beta} \right) \\ &= \tan^{-1}(\coth \alpha \cdot \tan \beta) \end{aligned}$$

Similarly, letting $\cosh(\alpha + j\beta)$ equal $r \angle \theta$,

$$\begin{aligned} \cosh(\alpha + j\beta) &= \cosh \alpha \cdot \cosh j\beta + \sinh \alpha \cdot \sinh j\beta \\ &= \cosh \alpha \cdot \cos \beta + j \cdot \sinh \alpha \cdot \sin \beta \end{aligned}$$

$$\begin{aligned} \therefore r^2 &= \cosh^2 \alpha \cdot \cos^2 \beta + \sinh^2 \alpha \cdot \sin^2 \beta \\ &= (1 + \sinh^2 \alpha) \cdot \cos^2 \beta + \sinh^2 \alpha \cdot (1 - \cos^2 \beta) \\ &= \cos^2 \beta + \sinh^2 \alpha \cdot \cos^2 \beta + \sinh^2 \alpha - \sinh^2 \alpha \cdot \cos^2 \beta \\ &= \sinh^2 \alpha + \cos^2 \beta \end{aligned}$$

$$\therefore r = \sqrt{\sinh^2 \alpha + \cos^2 \beta}$$

$$\begin{aligned} \text{and } \theta &= \tan^{-1} \left(\frac{\sinh \alpha \cdot \sin \beta}{\cosh \alpha \cdot \cos \beta} \right) \\ &= \tan^{-1}(\tanh \alpha \cdot \tan \beta) \end{aligned}$$

Alternatively, the following identities may be used :—

$$\sinh(\alpha + j\beta) = \sqrt{\cosh^2 \alpha - \cos^2 \beta} \angle \tan^{-1}(\coth \alpha \cdot \tan \beta) \tag{168}$$

$$\cosh(\alpha + j\beta) = \sqrt{\cosh^2 \alpha - \sin^2 \beta} \angle \tan^{-1}(\tanh \alpha \cdot \tan \beta) \tag{169}$$

DIFFERENTIAL EQUATIONS

A differential equation is an equation involving unknown quantities and their derivatives.

$$\text{e.g.} \quad \frac{d^2y}{dx^2} + 5\frac{dy}{dx} + 4y = 0$$

$$\text{and} \quad x^2 \frac{dy}{dx} = \sin x.$$

A solution of the equation is a function whose derivatives satisfy the equation.

Equations containing first derivatives are known as "first-order" equations; equations containing first and second derivatives are known as "second-order" equations, and so on. In general, there will be one indeterminate constant in the solution of an equation containing only first derivatives, two for an equation containing second derivatives, and so on.

Solution of equations of the first order and first degree

If the first order equation (containing only $\frac{dy}{dx}$) can be manipulated into the form $f(x) dx = F(y) dy$, it may be solved by direct integration.

$$\text{Example.}— \quad 2y + 3\frac{dy}{dx} = 4$$

$$\therefore \quad 3\frac{dy}{dx} = 4 - 2y$$

$$\therefore \quad \frac{dy}{y-2} = -\frac{2}{3} dx$$

Integrating :—

$$\log_e (y - 2) = -\frac{2}{3} x + \log_e C \quad (\text{where } C \text{ is a constant})$$

$$\therefore \quad y - 2 = C e^{-\frac{2x}{3}}$$

$$\text{or} \quad y = 2 + C e^{-\frac{2x}{3}} \quad \text{Ans.}$$

Linear equations of the first order, of the general form:—

$$\frac{dy}{dx} + Py = Q, \quad (170)$$

where P and Q may be functions of x , may be solved by multiplying through by e raised to the power of the integral, with respect to x , of the coefficient of y , i.e. by $e^{\int P dx}$.

$$\therefore e^{\int P dx} \cdot \frac{dy}{dx} + y P e^{\int P dx} = Q e^{\int P dx}$$

The left-hand side of the equation is the differential coefficient with respect to x of the product of $e^{\int P dx}$ and y .

$$\therefore \frac{d}{dx} (e^{\int P dx} \cdot y) = Q e^{\int P dx}$$

Integrating :—

$$y \cdot e^{\int P dx} = \int [Q e^{\int P dx}] dx + C \quad (171)$$

Example.—

$$\text{Solve} \quad \frac{dy}{dx} - 2y = e^{3x}$$

Multiply both sides by e^{-2x} , which is e raised to the power of the integral, with respect to x , of (-2) .

$$\therefore e^{-2x} \left(\frac{dy}{dx} - 2y \right) = e^{-2x} \cdot e^{3x}$$

$$\therefore \frac{d}{dx} (e^{-2x} \cdot y) = e^x$$

Integrating :—

$$e^{-2x} \cdot y = e^x + C$$

$$\therefore y = e^{2x} (e^x + C) \quad \text{Ans.}$$

Solution of linear equations having constant coefficients

The equations considered here are linear equations of any order having constant coefficients, *i.e.*, equations of the form :—

$$p_n \frac{d^n y}{dx^n} + p_{n-1} \frac{d^{n-1} y}{dx^{n-1}} + \dots + p_1 \frac{dy}{dx} + p_0 y = f(x) \quad (172)$$

where p_n etc. are constants.

The simple case where $f(x) = 0$ will be considered first, *e.g.* :—

$$\frac{d^3 y}{dx^3} + 7 \frac{d^2 y}{dx^2} + 9 \frac{dy}{dx} - y = 0$$

The general form of such a linear equation is :—

$$p_n \frac{d^n y}{dx^n} + p_{n-1} \frac{d^{n-1} y}{dx^{n-1}} + \dots + p_1 \frac{dy}{dx} + p_0 y = 0 \quad (173)$$

It can be shown that the general solution to this equation is :—

$$y = A_1 e^{m_1 x} + A_2 e^{m_2 x} + \dots + A_n e^{m_n x} \quad (174)$$

where m_1, m_2, \dots, m_n are the solutions of the equation :—

$$p_n m^n + p_{n-1} m^{n-1} + \dots + p_1 m + p_0 = 0$$

Note that this general solution contains n arbitrary constants.

Example 1.—

$$\text{Solve} \quad \frac{d^3 y}{dx^3} - 4 \frac{dy}{dx} = 0$$

$m_1, m_2,$ and m_3 will be the roots of:—

$$m^3 - 4m = 0$$

i.e. of $m(m-2)(m+2) = 0$

$\therefore m = 0, 2, \text{ or } -2.$

Therefore the general solution is:—

$$y = Ae^0 + Be^{2x} + Ce^{-2x}$$

$$= A + Be^{2x} + Ce^{-2x}$$

Since $e^{2x} = \cosh 2x + \sinh 2x$ and $e^{-2x} = \cosh 2x - \sinh 2x$, this may be written as:—

$$y = A + B(\cosh 2x + \sinh 2x) + C(\cosh 2x - \sinh 2x)$$

$$= A + D \cosh 2x + E \sinh 2x \quad \text{Ans.}$$

where $D = B + C$, and $E = B - C$

Example 2.—

An important example in transmission theory is:—

$$\frac{d^2y}{dx^2} - \gamma^2y = 0$$

The solution as above is:—

$$y = Ae^{\gamma x} + Be^{-\gamma x}$$

$$= C \cosh \gamma x + D \sinh \gamma x \quad \text{Ans.}$$

where $C = A + B$, and $D = A - B$

Example 3.—

In some cases the roots may be imaginary, as in this example:—

$$\frac{d^2y}{dx^2} + 9y = 0$$

m_1 and m_2 are the roots of:—

$$m^2 + 9 = 0$$

$\therefore m = \pm j3$

Therefore the general solution is:—

$$y = Ae^{j3x} + Be^{-j3x}$$

$$= A(\cos 3x + j \sin 3x) + B(\cos 3x - j \sin 3x)$$

$$= C \cos 3x + jD \sin 3x \quad \text{Ans.}$$

where $C = A + B$, and $D = A - B$

Consider now an equation of the form:—

$$\frac{d^2y}{dx^2} + P \frac{dy}{dx} + Qy = f(x)$$

where P and Q are constants.

The complete solution to the equation may be written as:—

$$y = u + v$$

where u is any function whatever that satisfies the equation, and v is the general solution to the equation:—

$$\frac{d^2y}{dx^2} + P \frac{dy}{dx} + Qy = 0$$

u is called the "particular integral", and
 v is called the "complementary function".

Example.—

$$\text{Solve : } \frac{d^2y}{dx^2} + \frac{dy}{dx} - 6y = x^2$$

To find the complementary function.—Consider the equation :—

$$\begin{aligned} \frac{d^2y}{dx^2} + \frac{dy}{dx} - 6y &= 0 \\ m^2 + m - 6 &= 0 \\ (m + 3)(m - 2) &= 0 \end{aligned}$$

Hence $y = Ae^{-3x} + Be^{2x}$

This is the complementary function.

To find the particular integral.—

Let $y = H + Kx + Lx^2$ be one solution to the equation.

Then $\frac{dy}{dx} = K + 2Lx$

and $\frac{d^2y}{dx^2} = 2L$

These derivatives must satisfy the original equation ;

$$\therefore 2L + (K + 2Lx) - 6(H + Kx + Lx^2) = x^2$$

$$\therefore 2L + K + 2Lx - 6H - 6Kx - 6Lx^2 = x^2$$

Thus equating coefficients gives :—

$$L = -\frac{1}{6}; \quad K = -\frac{1}{18}; \quad H = -\frac{7}{108};$$

Hence the particular integral = $-\frac{1}{108}(7 + 6x + 18x^2)$

The complete solution is therefore :—

$$y = A \cdot e^{-3x} + B \cdot e^{2x} - \frac{1}{108}(7 + 6x + 18x^2)$$

HARMONIC ANALYSIS

Fourier's Theorem

Any single-valued periodic function $y = f(t)$ having a period 2π may be expressed in the form :—

$$y = c + A_1 \sin(\omega t + \varphi_1) + A_2 \sin(2\omega t + \varphi_2) + A_3 \sin(3\omega t + \varphi_3) + \dots \quad (175)$$

$$\begin{aligned} \text{Since } A \sin(\omega t + \varphi) &= A \sin \omega t \cos \varphi + A \cos \omega t \sin \varphi \\ &= a \sin \omega t + b \cos \omega t \end{aligned}$$

where $a = A \cos \varphi$ and $b = A \sin \varphi$,

this expansion may be expressed as :—

$$\begin{aligned} y &= c + a_1 \sin \omega t + a_2 \sin 2\omega t + a_3 \sin 3\omega t + \dots \\ &\quad + b_1 \cos \omega t + b_2 \cos 2\omega t + b_3 \cos 3\omega t + \dots \quad (176) \end{aligned}$$

In order to use this expression to analyse a complex waveform, it is necessary to determine the coefficients c , a_1 , a_2 , . . . and b_1 , b_2 , This is done by multiplying both sides of equation 176 by a suitable factor and integrating between the limits 0 and 2π . If the multiplying factor is correctly chosen, all terms vanish except those which will give the required coefficient. The vanishing of the unknown terms depends on certain definite integrals:—

Integrals of harmonic functions.

$$(a) \int_0^{2\pi} \cos nx \, dx = \frac{1}{n} \left[\sin nx \right]_0^{2\pi} = \frac{1}{n} [0 - 0] \\ = 0 \quad (n \text{ is any integer}) \quad (177)$$

$$(b) \int_0^{2\pi} \sin nx \, dx = -\frac{1}{n} \left[\cos nx \right]_0^{2\pi} = -\frac{1}{n} [1 - 1] \\ = 0 \quad (n \text{ is any integer}) \quad (178)$$

$$(c) \int_0^{2\pi} \sin mx \cos nx \, dx = \int_0^{2\pi} \left\{ \frac{1}{2} \sin (m+n)x + \frac{1}{2} \sin (m-n)x \right\} dx \\ = 0 \quad (m \text{ and } n \text{ are any integers}) \quad (179)$$

$$(d) \int_0^{2\pi} \cos mx \cos nx \, dx = \int_0^{2\pi} \left\{ \frac{1}{2} \cos (m+n)x + \frac{1}{2} \cos (m-n)x \right\} dx \\ = 0 \quad (m \text{ and } n \text{ are any unequal integers}) \quad (180)$$

$$(e) \int_0^{2\pi} \sin mx \sin nx \, dx = \int_0^{2\pi} \left\{ \frac{1}{2} \cos (m-n)x - \frac{1}{2} \cos (m+n)x \right\} dx \\ = 0 \quad (m \text{ and } n \text{ are any unequal integers}) \quad (181)$$

$$(f) \int_0^{2\pi} \cos^2 nx \, dx = \int_0^{2\pi} \left\{ \frac{1}{2} \cos 2nx + \frac{1}{2} \right\} dx \\ = \pi \quad (n \text{ is any integer}) \quad (182)$$

$$(g) \int_0^{2\pi} \sin^2 nx \, dx = \int_0^{2\pi} \left\{ \frac{1}{2} - \frac{1}{2} \cos 2nx \right\} dx \\ = \pi \quad (n \text{ is any integer}) \quad (183)$$

Determination of the coefficients

To find c .—Integrate both sides of equation 176 with respect to ωt between the limits 0 and 2π .

$$\int_0^{2\pi} y \, d(\omega t) = c \int_0^{2\pi} d(\omega t) + a_1 \int_0^{2\pi} \sin \omega t \cdot d(\omega t) \\ + a_2 \int_0^{2\pi} \sin 2\omega t \cdot d(\omega t) + \dots \\ + b_1 \int_0^{2\pi} \cos \omega t \cdot d(\omega t) \\ + b_2 \int_0^{2\pi} \cos 2\omega t \cdot d(\omega t) + \dots$$

$$\begin{aligned}
&= c \int_0^{2\pi} d(\omega t) + 0 \\
&\qquad\qquad\qquad + 0 + \dots \\
&\qquad\qquad\qquad + 0 \\
&\qquad\qquad\qquad + 0 + \dots \\
\therefore \int_0^{2\pi} y d(\omega t) &= c \int_0^{2\pi} d(\omega t) \\
&= c \left[\omega t \right]_0^{2\pi} \\
&= 2\pi c \\
\therefore c &= \frac{1}{2\pi} \int_0^{2\pi} y d(\omega t) \tag{184}
\end{aligned}$$

It will be noted that c is the mean value of y between the limits 0 and 2π .

To find a_n , the series must be multiplied by some factor such that on integrating between the limits 0 and 2π , all terms vanish except that containing a_n . This may be accomplished by multiplying the series by $\sin n\omega t$ and integrating with respect to ωt between limits 0 and 2π .

$$\begin{aligned}
\int_0^{2\pi} y \sin n\omega t \cdot d(\omega t) &= c \int_0^{2\pi} \sin n\omega t \cdot d(\omega t) \\
&\quad + a_1 \int_0^{2\pi} \sin \omega t \sin n\omega t \cdot d(\omega t) \\
&\quad + a_2 \int_0^{2\pi} \sin 2\omega t \sin n\omega t \cdot d(\omega t) + \dots \\
&\quad + a_n \int_0^{2\pi} \sin^2 n\omega t \cdot d(\omega t) + \dots \\
&\quad + b_1 \int_0^{2\pi} \cos \omega t \sin n\omega t \cdot d(\omega t) \\
&\quad + b_p \int_0^{2\pi} \cos 2\omega t \sin n\omega t \cdot d(\omega t) + \dots \\
&= 0 \\
&\quad + 0 + 0 + 0 \dots + a_n \cdot \pi + 0 \dots \\
&\quad + 0 + 0 + 0 \dots \\
&= a_n \cdot \pi
\end{aligned}$$

$$\text{Hence} \qquad a_n = \frac{1}{\pi} \int_0^{2\pi} y \sin n\omega t \cdot d(\omega t) \tag{185}$$

where n is any positive integer.

In this case, it will be noticed that a_n is twice the mean value of $y \sin n\omega t$ between the limits of 0 and 2π .

To find b_n , the series is multiplied and integrated in a similar manner, the necessary factor being $\cos n\omega t$. The series then becomes :—

$$\begin{aligned}
 \int_0^{2\pi} y \cos n\omega t \cdot d(\omega t) &= c \int_0^{2\pi} \cos n\omega t \cdot d(\omega t) \\
 &+ a_1 \int_0^{2\pi} \sin \omega t \cos n\omega t \cdot d(\omega t) \\
 &+ a_2 \int_0^{2\pi} \sin 2\omega t \cos n\omega t \cdot d(\omega t) + \dots \\
 &+ b_1 \int_0^{2\pi} \cos \omega t \cos n\omega t \cdot d(\omega t) \\
 &+ b_2 \int_0^{2\pi} \cos 2\omega t \cos n\omega t \cdot d(\omega t) + \dots \\
 &+ b_n \int_0^{2\pi} \cos^2 n\omega t \cdot d(\omega t) + \dots \\
 &= 0 \\
 &\quad + 0 + 0 + 0 \dots \\
 &\quad + 0 + 0 + 0 \dots + b_n \cdot \pi + 0 \dots \\
 &= b_n \cdot \pi \\
 \therefore b_n &= \frac{1}{\pi} \int_0^{2\pi} y \cos n\omega t \cdot d(\omega t) \tag{186}
 \end{aligned}$$

where n is any positive integer.

Thus b_n is twice the mean value of $y \cos n\omega t$ between the limits 0 and 2π .

Analysis of a square waveform

Fig. 66 shows a square waveform; this is a single-valued periodic function of ωt , having a period 2π , and it may therefore be analysed by Fourier's Theorem.

From $\omega t = 0$ to $\omega t = \pi$, the equation to the function is $y = d$

From $\omega t = \pi$ to $\omega t = 2\pi$, the equation to the function is $y = 0$

Let the function, expressed as a harmonic series, be :—

$$\begin{aligned}
 y &= c + a_1 \sin \omega t + a_2 \sin 2\omega t + a_3 \sin 3\omega t + \dots \\
 &\quad + b_1 \cos \omega t + b_2 \cos 2\omega t + b_3 \cos 3\omega t + \dots
 \end{aligned}$$

To find c .—

$$c = \frac{1}{2\pi} \int_0^{2\pi} y d(\omega t) = \frac{1}{2\pi} \int_0^{\pi} y d(\omega t) + \frac{1}{2\pi} \int_{\pi}^{2\pi} y d(\omega t)$$

$$\therefore c = \frac{1}{2\pi} \cdot d \cdot \pi + 0 = \frac{d}{2}$$

From inspection of Fig. 66, it can be verified that the mean value of y is $\frac{d}{2}$.

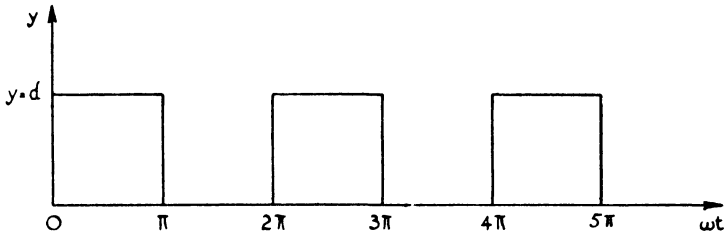


FIG. 66.—Square waveform always above t axis.

To find a_n .—

$$\begin{aligned} a_n &= \frac{1}{\pi} \int_0^{2\pi} y \sin n\omega t \cdot d(\omega t) \\ &= \frac{1}{\pi} \left[\int_0^\pi d \sin n\omega t \cdot d(\omega t) + \int_\pi^{2\pi} 0 \cdot \sin n\omega t \cdot d(\omega t) \right] \\ &= \frac{1}{\pi} \left[\frac{-d \cos n\omega t}{n} \right]_0^\pi \\ &= \frac{d}{n\pi} (1 - \cos n\pi) \end{aligned}$$

When n is odd, $(1 - \cos n\pi) = 2$

When n is even, $(1 - \cos n\pi) = 0$

Thus :—

$$a_1 = \frac{2d}{\pi}, a_2 = 0$$

$$a_3 = \frac{2d}{3\pi}, a_4 = 0$$

To find b_n .—

$$\begin{aligned} b_n &= \frac{1}{\pi} \int_0^{2\pi} y \cos n\omega t \cdot d(\omega t) \\ &= \frac{1}{\pi} \left[\int_0^\pi d \cos n\omega t \cdot d(\omega t) + \int_\pi^{2\pi} 0 \cdot \cos n\omega t \cdot d(\omega t) \right] \\ &= \frac{1}{\pi} \left[\frac{d \sin n\omega t}{n} \right]_0^\pi \\ &= 0 \end{aligned}$$

All cosine terms are thus zero.

The required equation to the function is therefore:—

$$y = \frac{d}{2} + \frac{2d}{\pi} \left\{ \sin \omega t + \frac{1}{3} \sin 3 \omega t + \frac{1}{5} \sin 5 \omega t + \frac{1}{7} \sin 7 \omega t + \dots \right\} \quad (187)$$

A curve frequently encountered in communications engineering is that shown in Fig. 67. This is similar in general form to the one

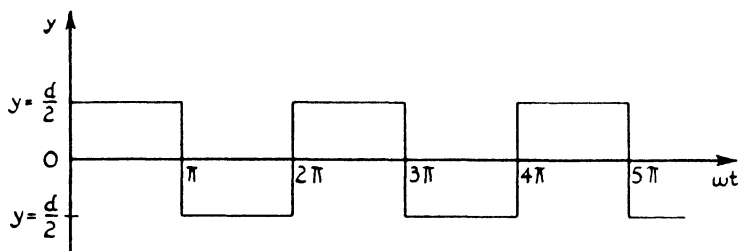


FIG. 67.—Square waveform with zero constant term.

shown in Fig. 66, and represented by equation 187, but it is symmetrical about the time axis ($0-\omega t$); the first term $\left(\frac{d}{2}\right)$ therefore does not appear in its equation, which is:—

$$y = \frac{2d}{\pi} \left(\sin \omega t + \frac{1}{3} \sin 3 \omega t + \frac{1}{5} \sin 5 \omega t + \dots \right) \quad (188)$$

Graphical application

Equations 184, 185 and 186 give the coefficients c , a_n and b_n in the Fourier series represented by equation 176 for any single-valued function. They can be applied, however, only when the function is known analytically—as, for example:—

$$\begin{aligned} \text{from} & \quad 0 \text{ to } t_1, & y &= f_1(t) \\ \text{from} & \quad t_1 \text{ to } t_2, & y &= f_2(t) \\ \text{from} & \quad t_2 \text{ to } \frac{2\pi}{\omega}, & y &= f_3(t) \end{aligned}$$

Sometimes the function to be expressed as a Fourier series is known graphically but not analytically, and in such cases an approximate graphical method of analysis must be applied. Any number k of ordinates at intervals of $\frac{2\pi}{k}$ are drawn, and the heights

$y_0, y_1, y_2, \dots, y_{k-1}$ of each ordinate measured. The larger the number of ordinates drawn, the closer will the approximation be; the order n of the highest harmonic that can be calculated with reasonable accuracy by means of a k -ordinate analysis is given by:—

$$n = \frac{k-2}{2}$$

Equation 184 can then be rewritten as :—

$$c = \frac{1}{k} (y_0 + y_1 + y_2 + \dots + y_{k-1})$$

$$\therefore c = \frac{1}{k} \sum_{m=0}^{m=k-1} y_m \tag{189}$$

and equation 185 can be written as :—

$$\begin{aligned} a_n &= \frac{1}{\pi} \int_0^{2\pi} y \sin n\omega t \cdot d(\omega t) \\ &= 2 \times \text{average ordinate of the curve } y \sin n\omega t \\ &\simeq \frac{2}{k} \times \text{sum of } k \text{ ordinates} \\ &= \frac{2}{k} \left(y_0 \sin \frac{2\pi \cdot 0n}{k} + y_1 \sin \frac{2\pi \cdot 1n}{k} + y_2 \sin \frac{2\pi \cdot 2n}{k} \right. \\ &\qquad \qquad \qquad \left. + \dots + y_{k-1} \sin \frac{2\pi (k-1)n}{k} \right) \\ &= \frac{2}{k} \sum_{m=0}^{m=k-1} y_m \sin mn \frac{2\pi}{k} \end{aligned} \tag{190}$$

Similarly

$$b_n = \frac{2}{k} \sum_{m=0}^{m=k-1} y_m \cos mn \frac{2\pi}{k} \tag{191}$$

12-ordinate analysis.—

If twelve ordinates are taken, ($k = 12$), as in Fig. 68, they must

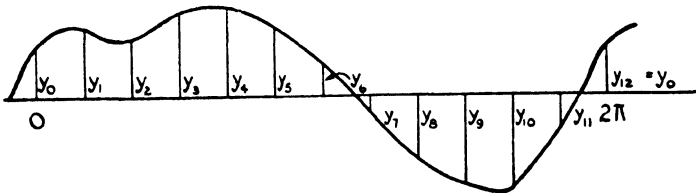


FIG. 68.—12-ordinate analysis.

be spaced at $\frac{2\pi}{12}$, or 30° . Then :—

$$\begin{aligned} a_n &= \frac{1}{6} \left\{ y_0 \sin 0n \frac{\pi}{6} + y_1 \sin 1n \frac{\pi}{6} + y_2 \sin 2n \frac{\pi}{6} + \dots \right. \\ &\qquad \qquad \qquad \left. + y_{11} \sin 11n \frac{\pi}{6} \right\} \end{aligned} \tag{192}$$

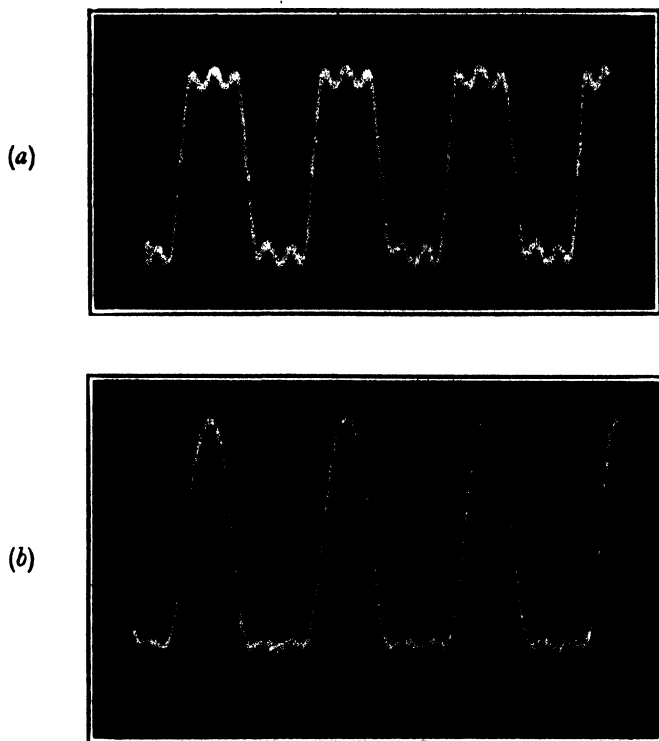


PLATE 2.—Oscillograms showing component sine waves and resultant wave forms.

$$\text{and } b_n = \frac{1}{6} \left\{ y_0 \cos 0n \frac{\pi}{6} + y_1 \cos n \frac{\pi}{6} + y_2 \cos 2n \frac{\pi}{6} + \dots + y_{11} \cos 11n \frac{\pi}{6} \right\} \quad (193)$$

Hence the early coefficients in the series of equation 176 become:—


$$c = \frac{1}{12} \{ y_0 + y_1 + y_2 + y_3 + y_4 + y_5 + y_6 + y_7 + y_8 + y_9 + y_{10} + y_{11} \} \quad (194)$$

$$a_1 = \frac{1}{6} \{ (y_3 - y_9) + 0.866 (y_2 + y_4 - y_8 - y_{10}) + 0.5 (y_1 + y_5 - y_7 - y_{11}) \} \quad (195)$$

$$a_2 = \frac{0.866}{6} \{ (y_1 + y_2 + y_7 + y_8) - (y_4 + y_5 + y_{10} + y_{11}) \} \quad (196)$$

$$a_3 = \frac{1}{6} \{ (y_1 + y_5 + y_9) - (y_3 + y_7 + y_{11}) \} \quad (197)$$

(c)

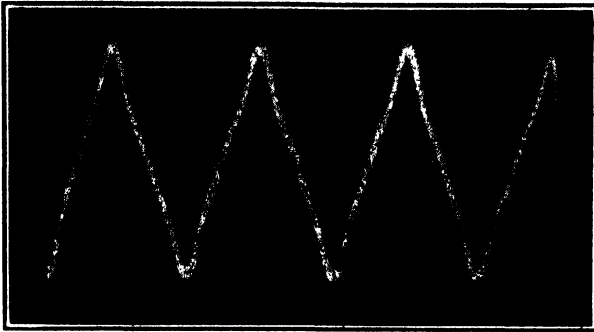

(d)

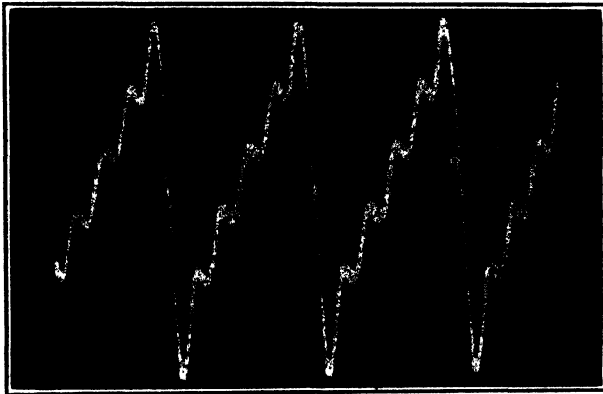


PLATE 2.—Oscillograms showing component sine waves and resultant wave forms

$$a_4 = \frac{0.866}{6} \{(y_1 + y_4 + y_7 + y_{10}) - (y_2 + y_5 + y_8 + y_{11})\} \quad (198)$$

$$a_5 = \frac{1}{6} \{(y_3 - y_9) + 0.866 (y_8 + y_{10} - y_2 - y_4) + 0.5 (y_1 + y_5 - y_7 - y_{11})\} \quad (199)$$

$$b_1 = \frac{1}{6} \{(y_0 - y_6) + 0.866 (y_1 + y_{11} - y_5 - y_7) + 0.5 (y_2 + y_{10} - y_4 - y_8)\} \quad (200)$$

$$b_2 = \frac{1}{6} \{(y_0 - y_3 + y_6 - y_9) + 0.5 (y_1 + y_5 + y_7 + y_{11}) - 0.5 (y_2 + y_4 + y_8 + y_{10})\} \quad (201)$$

$$b_3 = \frac{1}{6} \{(y_0 + y_4 + y_8) - (y_2 + y_6 + y_{10})\} \quad (202)$$


$$b_4 = \frac{1}{6} \{(y_0 + y_3 + y_6 + y_9) - 0.5 (y_1 + y_2 + y_4 + y_5 + y_7 + y_8 + y_{10} + y_{11})\} \quad (203)$$

$$b_5 = \frac{1}{6} \{(y_0 - y_6) + 0.866 (y_5 + y_7 - y_1 - y_{11}) + 0.5 (y_2 + y_{10} - y_4 - y_8)\} \quad (204)$$

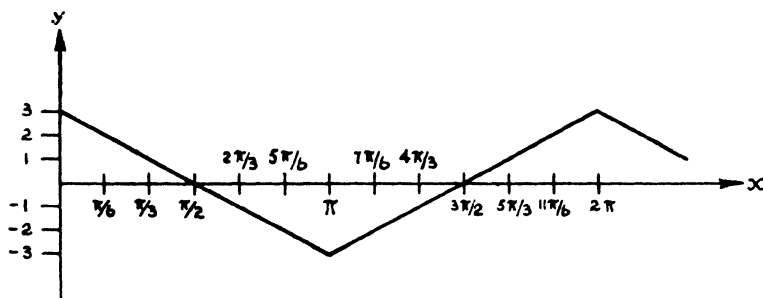
Example.—

Express as a Fourier series the curve shown in Fig. 69*a*.
Applying a 12-ordinate analysis :—

$$\begin{array}{ll}
 y_0 = 3 & y_7 = -2 \\
 y_1 = 2 & y_8 = -1 \\
 y_2 = 1 & y_9 = 0 \\
 y_3 = 0 & y_{10} = 1 \\
 y_4 = -1 & y_{11} = 2 \\
 y_5 = -2 & y_{12} = y_0 = 3 \\
 y_6 = -3 &
 \end{array}$$



(a)

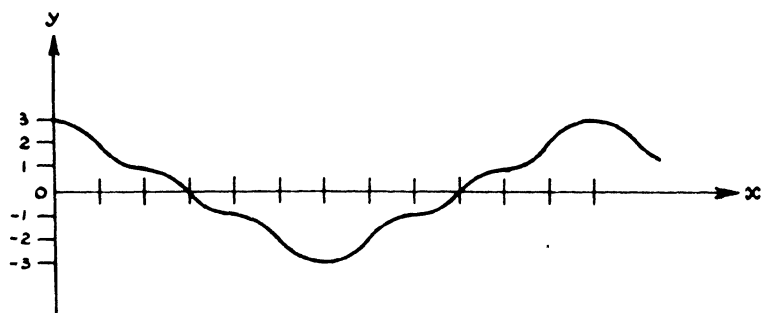

(b)

FIG. 69.—Example of Fourier analysis.

Then, from equations 194 to 204 :—

$$c = \frac{1}{12} \{3 + 2 + 1 + 0 - 1 - 2 - 3 - 2 - 1 + 0 + 1 + 2\} = 0$$

$$a_1 = \frac{1}{6} \{ (0 - 0) + 0.866 (1 - 1 + 1 - 1) + 0.5 (2 - 2 + 2 - 2) \} = 0$$

$$a_2 = \frac{0.866}{6} \{ (2 + 1 - 2 - 1) - (-1 - 2 + 1 + 2) \} = 0$$

$$a_3 = \frac{1}{6} \{ (2 - 2 + 0) - (0 - 2 + 2) \} = 0$$

$$a_4 = \frac{0.866}{6} \{ (2 - 1 - 2 + 1) - (1 - 2 - 1 + 2) \} = 0$$

$$a_5 = \frac{1}{6} \{ (0 - 0) + 0.866 (-1 + 1 - 1 + 1) + 0.5 (2 - 2 + 2 - 2) \} = 0$$

$$b_1 = \frac{1}{6} \{ (3 + 3) + 0.866 (2 + 2 + 2 + 2) + 0.5 (1 + 1 + 1 + 1) \} = \frac{1}{6} \{ 6 + 6.93 + 2 \} = 2.49$$

$$b_2 = \frac{1}{6} \{ (3 - 3) + 0.5 (2 - 2 - 2 + 2) - 0.5 (1 - 1 - 1 + 1) \} = 0$$

$$b_3 = \frac{1}{6} \{ (3 - 1 - 1) - (1 - 3 + 1) \} = 0.333$$

$$b_4 = \frac{1}{6} \{ (3 + 0 - 3 + 0) - 0.5 (2 + 1 - 1 - 2 - 2 - 1 + 1 + 2) \} = 0$$

$$b_5 = \frac{1}{6} \{ (3 + 3) + 0.866 (-2 - 2 - 2 - 2) + 0.5 (1 + 1 + 1 + 1) \} = \frac{1}{6} \{ 6 - 6.93 + 2 \} = 0.178$$

Thus the curve is represented approximately by a series, the first three terms of which are (see Fig. 69b) :—

$$y = 2.49 \cos x + 0.333 \cos 3x + 0.178 \cos 5x + \dots$$

Input-output curves

Many pieces of equipment used in communication engineering have a non-linear characteristic ; that is to say, the output is not directly proportional to the input, so that the waveform of the output differs from that of the input.

The input-output characteristic of many items of equipment can be represented by a line *PQ* (see Fig. 70) such that, if any input, represented by a distance *Oa* along one axis *Ox*, be projected on to it at *N*, the projection *Ob* of *N* on to *Oy* represents the output. If *PQ* is a straight line, the output will be identical in waveform to the input, but if *PQ* is curved, the output waveform will differ from the input waveform. This difference in waveform corresponds to the generation of harmonics of the fundamental input frequency, and can be analysed by considering the output waveform produced when a sinusoidal input is applied.

Fig. 71 shows a sine wave so applied to a curve *PQ* that the projection of the peaks of the wave coincide with the ends *P* and *Q* of the curve. The axis of the sine wave is extended to meet *PQ* at *O*, and a line *AOB* drawn at right angles to this axis with *OA* = *OB* = amplitude of sine wave. If 12 ordinates *q*₁ *q*₂ . . . are shown on

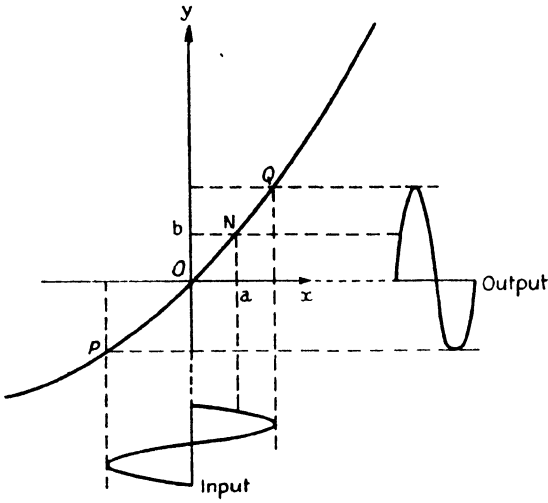


FIG. 70.—Typical input-output curve showing non-linearity.

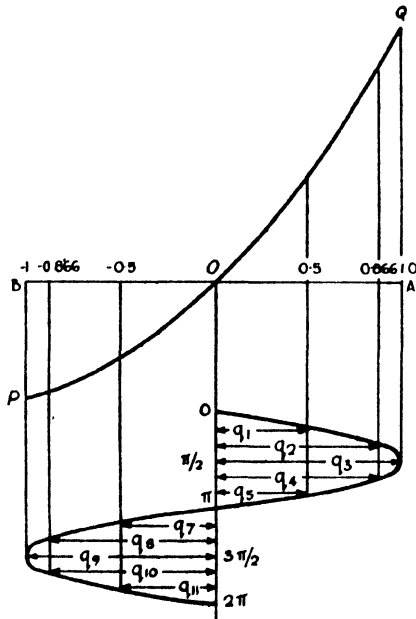


FIG. 71.—Application of 12-point analysis to input-output curve.

the sine wave at intervals of $\frac{2\pi}{12}$, it can be seen that :—

$$\left. \begin{aligned}
 q_0 = q_6 = q_{12} &= 0 \\
 q_1 = q_5 = OA \sin 30^\circ &= 0.5 OA \\
 q_2 = q_4 = OA \sin 60^\circ &= 0.866 OA \\
 q_3 &= OA \\
 q_7 = q_{11} = OA \sin 210^\circ &= -0.5 OA \\
 q_8 = q_{10} = OA \sin 270^\circ &= -0.866 OA \\
 q_9 &= -OA
 \end{aligned} \right\} (205)$$

An input-output curve PQ can thus be analysed by marking off, along the input axis, distances equal to ± 0.5 , ± 0.866 , and ± 1 times the amplitude of the input under consideration, and by measuring the heights $h_1, h_2, \text{etc.}$, of the curve at these points. If desired, the horizontal line AB may be taken not through O , but lower, so that all the heights h appear positive; the mean value term (c in equation 176) is then increased by h' , where h' is the distance from O to AB , but the other terms in the series are unaffected.

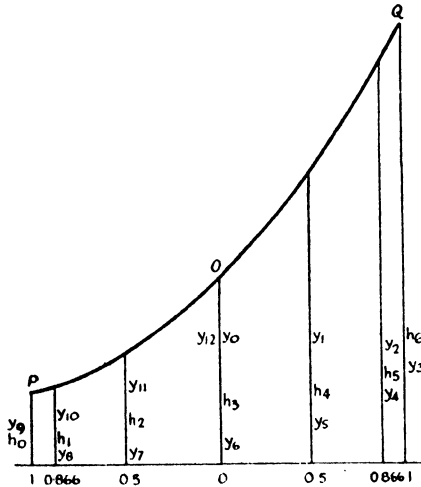


FIG. 72.—12-point analysis of input-output curve.

The coefficients of the terms in equation 176 can be found from equations 194 to 204. The notation of Fig. 72 gives :—

$$\left. \begin{aligned}
 y_0 = y_6 = y_{12} &= h_3 \\
 y_1 = y_5 &= h_4 \\
 y_2 = y_4 &= h_5 \\
 y_3 &= h_6 \\
 y_7 = y_{11} &= h_2 \\
 y_8 = y_{10} &= h_1 \\
 y_9 &= h_0
 \end{aligned} \right\} (206)$$

With this notation, these coefficients are:—

$$c = \frac{1}{12} \{(h_0 + h_6) + 2(h_1 + h_2 + h_3 + h_4 + h_5)\} \quad (207)$$

$$a_1 = \frac{1}{6} \{(h_4 + h_6) - (h_0 + h_2) + 1.732(h_5 - h_1)\} \quad (208)$$

$$a_3 = \frac{1}{6} \{(h_0 - h_6) + 2(h_4 - h_2)\} \quad (209)$$

$$a_5 = \frac{1}{6} \{(h_6 - h_0) + (h_4 - h_2) + 1.732(h_1 - h_5)\} \quad (210)$$

$$b_3 = \frac{1}{6} \{(h_2 + h_4 - h_5 - h_1) + 2h_3\} \quad (211)$$

$$b_4 = \frac{1}{6} \{(h_0 + 2h_3 + h_6) - (h_1 + h_2 + h_4 + h_5)\} \quad (212)$$

$$a_2 = a_4 = b_1 = b_3 = b_5 = 0 \quad (213)$$


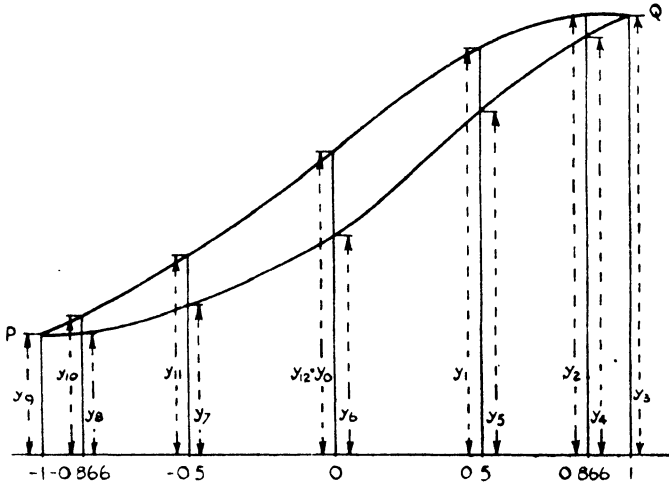


FIG. 73.—12-point analysis of input-output loop.

In certain cases, the input-output relationship must be represented not by a single line PQ , but by a closed loop. In such cases, equations 206 (and, therefore, 207 to 213) do not hold, but equations 194 to 204 may be applied, where $y_1, y_2, etc.$, have the meanings indicated in Fig. 73.

Particular cases of symmetry

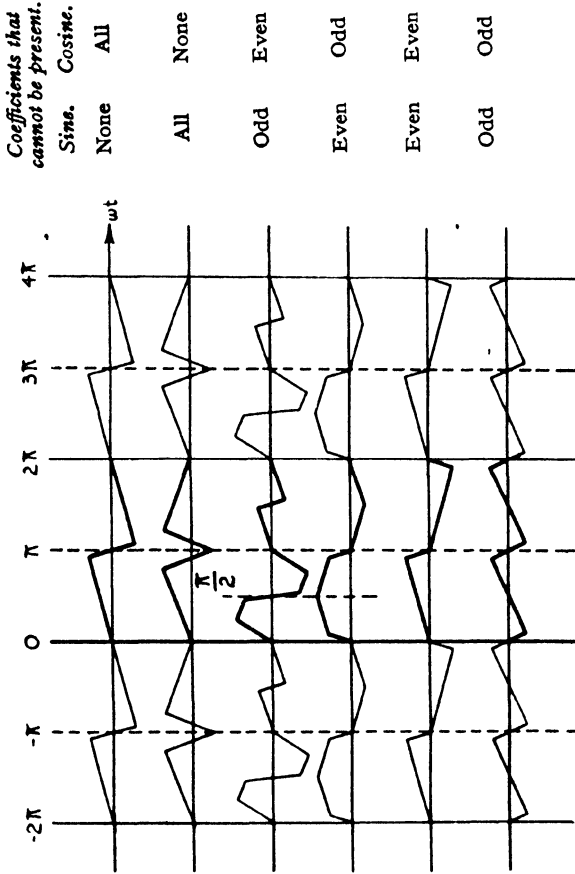In many cases, examination of the symmetrical properties of a curve may avoid the necessity for calculating the values of *all* the coefficients, since some of these may be seen, from inspection of the curve, to be zero. Fig. 74 gives the most important cases of symmetry.



Symmetry.

(a) Skew-symmetrical about $\omega t = 0$

$$\text{i.e. } f(\omega t) = -f(-\omega t)$$

(b) Symmetrical about $\omega t = 0$

$$\text{i.e. } f(\omega t) = +f(-\omega t)$$

(c) Skew-symmetrical about $\omega t = \pm \frac{\pi}{2}$

$$\text{i.e. } f(\omega t) = -f(\pi - \omega t)$$

(d) Symmetrical about $\omega t = \pm \frac{\pi}{2}$

$$\text{i.e. } f(\omega t) = +f(\pi - \omega t)$$

(e) Both half-cycles of same form,

$$\text{but with } f(\omega t) = -f(\pi + \omega t)$$

(f) Both half-cycles of same form ;

$$\text{but with } f(\omega t) = +f(\pi + \omega t)$$

[This is really a double-frequency waveform, since the fundamental frequency ($n = 1$) is excluded.]

FIG. 74.—Particular cases of symmetry in Fourier analysis.

Coefficients that cannot be present.

Sine. Cosine.

None All

All None

Odd Even

Even Odd

Even Even

Odd Odd

A curve is said to be *symmetrical* about a line $\omega t = k$ if its shape to the left of that line is a "mirror image" of its shape to the right of it; while it is *skew-symmetrical* about that line if its shape to the left of it is the same as that to the right, but inverted about the horizontal (ωt) axis. If the curve is symmetrical about $y = 0$ (as it is, of necessity, in cases (a), (c) and (d)), then the constant a_0 is zero. In other cases it may be necessary to subtract the component $y = a_0$ before the above conditions of skew-symmetry can be realised.

If a curve exhibits symmetry about two points, each of these will impose a limitation on the coefficients that may be present. The square waveform (Fig. 67) exhibits symmetry about $\omega t = \pm \frac{\pi}{2}$ and skew-symmetry about $\omega t = 0$. Its series therefore contains only *odd sine terms*.

Analysis of typical waveforms

(a) *Saw-toothed.*—

$$y = \frac{2d}{\pi} \left\{ \sin x - \frac{1}{2} \sin 2x + \frac{1}{3} \sin 3x - \dots \right\}$$

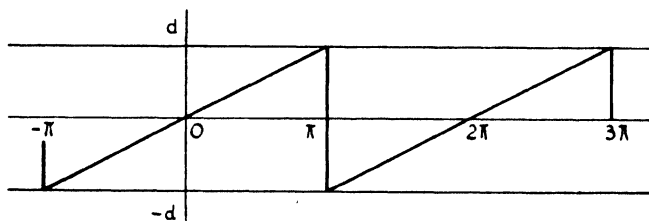


FIG. 75.—Analysis of saw-toothed waveform.

(b) *Modified saw-toothed.*—

$$y = \frac{d}{4} - \frac{2d}{\pi^2} \left\{ \cos x + \frac{\cos 3x}{3^2} + \frac{\cos 5x}{5^2} + \dots \right\} + \frac{d}{\pi} \left\{ \sin x - \frac{\sin 2x}{2} + \frac{\sin 3x}{3} - \dots \right\}$$

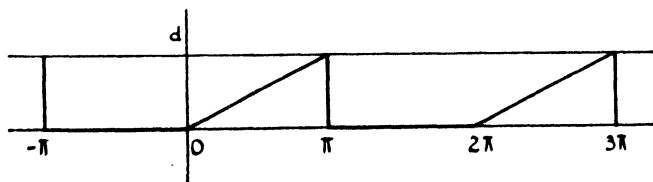


FIG. 76.—Analysis of modified saw-toothed waveform.

(c) *Triangular.*—

$$y = \frac{8d}{\pi^2} \left\{ \cos x + \frac{\cos 3x}{3^2} + \frac{\cos 5x}{5^2} + \dots \right\}$$

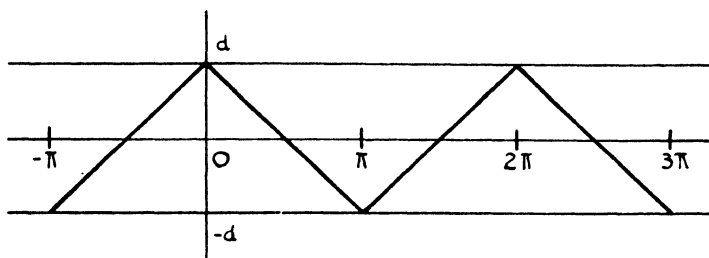


FIG. 77.—Analysis of triangular waveform.

(d) *Half-wave rectifier output.*—

$$y = \frac{2d}{\pi} \left\{ \frac{1}{2} + \frac{\pi}{4} \sin x - \frac{1}{1.3} \cos 2x - \frac{1}{3.5} \cos 4x - \frac{1}{5.7} \cos 6x - \dots \right\}$$

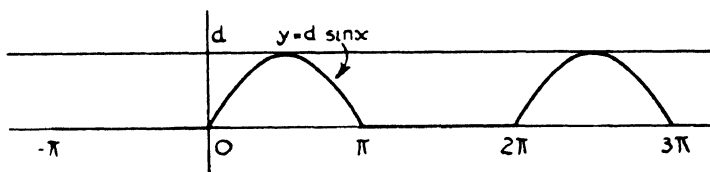


FIG. 78.—Analysis of half-wave rectifier output.

(e) *Full-wave rectifier output.*—

$$y = \frac{4d}{\pi} \left\{ \frac{1}{2} - \frac{1}{1.3} \cos 2x - \frac{1}{3.5} \cos 4x - \frac{1}{5.7} \cos 6x - \dots \right\}$$

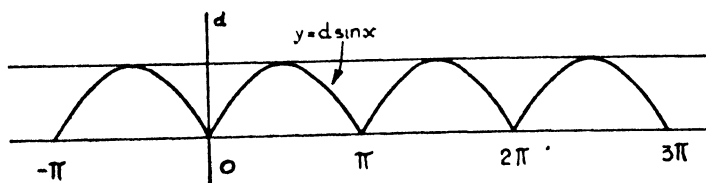


FIG. 79.—Analysis of full-wave rectifier output.

CHAPTER 3

DIRECT CURRENTS

This chapter summarises some of the important principles of elementary electricity and magnetism that are applicable to line communication, and is intended for revision.

Electric currents are intimately concerned with the structure of matter, and the answer to the question "What is electricity?" cannot be given without some knowledge of this structure. A very brief description of the molecules and atoms from which all matter is built up will therefore be given.

The smallest particle of any substance that can exist independently and still retain the characteristics of that substance is called a "molecule" of that substance. Each molecule is built up from a number of chemical elements, the smallest particle of each element being known as an atom of that element. Table IV gives a list of most of the known elements. The existence of molecules and atoms as the fundamental particles of matter has been accepted since the eighteenth century, but it was not until the present century that a satisfactory picture of the structure of the atom was provided.

Atomic structure

The atom of any particular element is now believed to consist of a positively-charged "nucleus" surrounded by a number of "planetary electrons". These planetary electrons behave as extremely small negative charges rotating in orbits of various sizes around the central nucleus which constitutes almost the entire mass of the atom. The epithets "positively-" and "negatively-charged" were originally used to express the fact that two similarly "charged" bodies (*e.g.*, both positive) repel each other, whereas two bodies of opposite charge (one positive, one negative) attract each other. The electron is considered to be the fundamental electric charge, a negatively charged body being one having a surplus of electrons, and a positively charged body being one having a deficit of them.

The charge of the electron is extremely small; the practical unit of electrical charge or "quantity of electricity", the coulomb, is equivalent to a definite, very large, number of electrons (actually about 6.28×10^{18}).

TABLE IV
Atomic weights and numbers

Element	Symbol	Atomic number	Atomic weight	Element	Symbol	Atomic number	Atomic weight
Actinium ..	Ac	89	c.227	Neodymium ..	Nd	60	144.27
Aluminium ..	Al	13	26.97	Neon ..	Ne	10	20.18
Antimony ..	Sb	51	121.76	Nickel ..	Ni	28	58.69
Argon ..	A	18	39.94	Niobium ..	No	41	92.91
Arsenic ..	As	33	74.91	Nitrogen ..	N	7	14.01
Barium ..	Ba	56	137.36	Osmium ..	Os	76	190.2
Beryllium ..	Be	4	9.02	Oxygen ..	O	8	16.00
Bismuth ..	Bi	83	209.00	Palladium ..	Pd	46	106.7
Boron ..	B	5	10.82	Phosphorus ..	P	15	31.02
Bromine ..	Br	35	79.92	Platinum ..	Pt	78	195.23
Cadmium ..	Cd	48	112.41	Polonium ..	Po	84	210
Caesium ..	Cs	55	132.91	Potassium ..	K	19	39.10
Calcium ..	Ca	20	40.08	Praeseodymium	Pr	59	140.92
Carbon ..	C	6	12.00	Protoactinium	Pa	91	231
Cerium ..	Ce	58	140.13	Radium ..	Ra	88	226.05
Chlorine ..	Cl	17	35.46	Radon ..	Rn	86	222
Chromium ..	Cr	24	52.01	Rhenium ..	Re	75	186.31
Cobalt ..	Co	27	58.94	Rhodium ..	Rh	45	102.91
Copper ..	Cu	29	63.57	Rubidium ..	Rb	37	85.48
Dysprosium ..	Dy	66	162.46	Ruthenium ..	Ru	44	101.7
Erbium ..	Er	68	167.20	Samarium ..	Sm	62	150.43
Europium ..	Eu	63	152.0	Scandium ..	Sc	21	45.10
Fluorine ..	F	9	19.00	Selenium ..	Se	34	78.96
Gadolinium ..	Gd	64	156.9	Silicon ..	Si	14	28.06
Gallium ..	Ga	31	69.72	Silver ..	Ag	47	107.88
Germanium ..	Ge	32	72.60	Sodium ..	Na	11	23.00
Gold ..	Au	79	197.2	Strontium ..	Sr	38	87.63
Hafnium ..	Hf	72	178.6	Sulphur ..	S	16	32.06
Helium ..	He	2	4.00	Tantalum ..	Ta	73	180.88
Holmium ..	Ho	67	163.5	Tellurium ..	Te	52	127.61
Hydrogen ..	H	1	1.008	Terbium ..	Tb	65	159.2
Indium ..	In	49	114.76	Thallium ..	Tl	81	204.39
Iodine ..	I	53	126.92	Thorium ..	Th	90	232.12
Iridium ..	Ir	77	193.1	Thulium ..	Tm	69	169.4
Iron ..	Fe	26	55.84	Tin ..	Sn	50	118.70
Krypton ..	Kr	36	83.7	Titanium ..	Ti	22	47.90
Lanthanum ..	La	57	138.92	Tungsten ..	W	74	183.92
Lead ..	Pb	82	207.22	Uranium ..	U	92	238.07
Lithium ..	Li	3	6.94	Vanadium ..	V	23	50.95
Lutecium ..	Lu	71	175.0	Xenon ..	Xe	54	131.3
Magnesium ..	Mg	12	24.32	Ytterbium ..	Yb	70	173.04
Manganese ..	Mn	25	54.93	Yttrium ..	Y	39	88.92
Mercury ..	Hg	80	200.61	Zinc ..	Zn	30	65.38
Molybdenum ..	Mo	42	95.95	Zirconium ..	Zr	40	91.22

The number of planetary electrons in each atom varies with the element ; hydrogen, the lightest, has only one ; helium has two ; lithium three ; and so on up to uranium, which has 92. Elements heavier than uranium are known to exist, and are classified under the general heading of " trans-uranic " elements. Thus according to

the element considered, the atom will contain between 1 and 90-odd units of negative charge. A complete atom, however, is electrically neutral, these negative charges being counteracted by equal positive charges in the nucleus. The number of such charges is known as the "atomic number" of the element (*see* Table IV).

The nucleus contains a number of particles called "protons"; a proton has a weight roughly 1,840 times that of the electron, and has a charge equal to that of the electron but opposite in sign. But in all atoms (except hydrogen) the weight of the planetary electrons together with that of the (equal number of) protons in the nucleus does not account for the whole weight of the atom. The weight of an atom (*i.e.*, atomic weight) is normally measured with reference to the atom of oxygen, which is assumed to have a weight of 16.00. The original theory assumed that the additional mass was due to equal number of protons and electrons added to the nucleus; the charge of each additional electron would balance that of each additional proton, and the net charge on the atom would still be zero. This theory was modified, however, in 1932 by the discovery of the "neutron"; this is a particle of mass roughly equal to that of the proton, but with zero charge. On the new theory, each additional proton with its associated electron is believed to be replaced by a neutron.

In the ordinary state, many elements consist of a mixture of "isotopes". These are atoms having the same atomic number but different atomic weights, and they are caused by different numbers of neutrons in the nucleus. The various isotopes of an element have identical chemical, but differing physical, properties.

Thus an atom is now assumed to consist of a nucleus of protons and neutrons, with planetary electrons (equal in number to the protons in the nucleus, and to the atomic number of the element) rotating in orbits around it.

Other particles are also known to exist, such as the positron and the mesotron, but these are less important.

It has been seen that an atom is normally electrically neutral. When an atom or molecule contains a surplus or deficiency of electrons, it is said to have been ionised. If an excess of electrons occurs, the atom or molecule will exhibit the properties of a negatively-charged particle; in such a state it is known as a "negative ion". If, however, a deficiency of electrons occurs, the atom or molecule will exhibit the properties of a positively-charged particle, and is known as a "positive ion".

The electric current

It has been seen that the electrons rotate in orbits around the nucleus, and these orbits are maintained by the electrostatic attraction between the electrons and the nucleus. Electrons in the outer orbits, being further from the nucleus, are held more loosely; in fact, in certain substances, such as metals, transfer of

these outer electrons between adjacent atoms is continually taking place. Such substances are called "conductors". If electrons are removed, by external means, from one end of a conductor, these loosely held electrons will be attracted towards that end, and a resultant motion of electrons will ensue. This flow of electrons constitutes an electric current. Substances in which the electrons are tightly bound to their parent nuclei will not permit such a flow of electrons; these substances are called "insulators".

To take a specific case, a simple cell consists of a copper rod or "electrode" and a zinc electrode inserted in dilute sulphuric acid. When the electrodes are connected externally by a metallic wire, it is found that an electric current flows due to chemical action

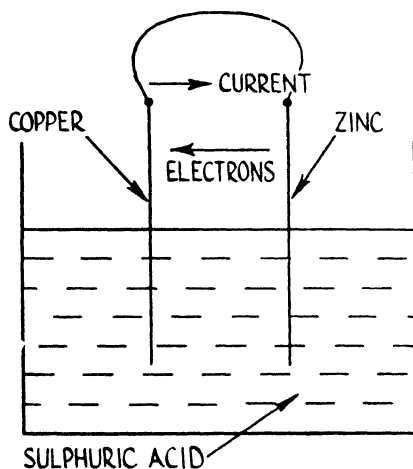


FIG. 80.—Simple cell.

between the electrodes and the acid. Consider the current flowing through this wire. It was originally assumed that "electricity" flowed from the copper electrode to the zinc; for this reason, the copper electrode was called the "positive", and the zinc the "negative". Thus "conventional current" flows from the positive electrode (copper) to the negative (zinc), although it is now known that what is actually happening is that a movement of the loosely held orbital electrons in the wire is taking place in the direction of zinc to copper. Thus one may say that electrons are flowing from the zinc to the copper. It is important to note that nearly all the laws of electricity are worded on the basis of "conventional current flow", as they were stated before electrons had been discovered.

The practical unit of current is the "ampere", which is equal to a rate of movement of electric charge of one coulomb per second (a flow of 6.28×10^{18} electrons per second).

More exactly, any movement of electric charge constitutes an electric current. In addition to a movement of electrons, a current

may be produced by a movement of positively and negatively charged ions.

By convention, the direction of flow of an electric current is determined by considering the flow to be due to positively charged particles. Thus, although a flow of electricity from point *A* to point *B* may be due to positively charged ions moving from *A* to *B*, it may also be due to negatively charged particles such as electrons or negative ions flowing from *B* to *A* (see Fig. 81).

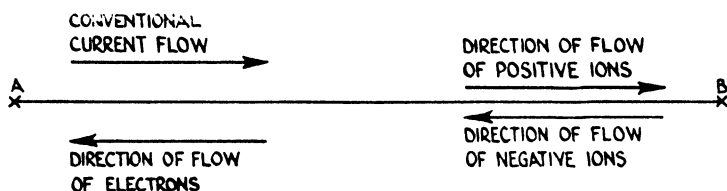


FIG. 81.—Direction of flow of electrons or ions to give flow of current.

The passage of electricity may occur :--

(a) through a conductor such as a metal due to the movement of the loosely held outer electrons of the atoms ;

(b) through a vacuum or gas due to the movement of electrons ;

(c) through a gas due to a movement of the ionised gas molecules ;

(d) through a liquid due to the ionisation of certain molecules, particularly those of acids and salts in solution, and the movement of the resulting ions.

Electro-motive force and potential difference

It is convenient to regard an " electric pressure " as being set up between the electrodes of a cell ; this pressure is known as " electro-motive force " (EMF). It is dependent solely upon the chemical constitution of the cell, and it exists even when the connecting wire is removed, *i.e.*, when no current is flowing. In the example given above, the copper electrode is said to be at a " higher potential " than the zinc, so that a " potential difference " (PD) exists between the two ends of the wire joining the electrodes. It is this PD which causes the current to flow through the wire from the point of higher to the point of lower potential, and it is the EMF of the cell which produces this PD. The practical unit used both for EMF and for PD is the " volt ", which is $\frac{1}{1.0186}$ of the EMF of a standard Weston cadmium cell at a temperature of 20° C. A more rigid definition of this and other electrical units is given on page 131.

Conductors and insulators

It has been seen that conductors are those substances that permit the movement of electrons from atom to atom through them

when a potential difference is applied; the ease with which electrons can be removed from their orbits by such a PD varies as from substance to substance. An insulator or non-conductor, on the other hand, is a substance in which the outer orbital electrons are tightly held to the atomic nuclei and will not break away on the application of a potential difference. If a PD is maintained between the ends of an insulator, the orbital electrons will be pulled over towards the point of higher potential, and the result will be a distortion of the electron orbits. This hypothesis will be used later to explain certain phenomena in connection with dielectric materials.

RESISTANCE

The distinction between conductors and insulators is not well defined, and there are many substances that may be regarded either as poor conductors or as poor insulators. In fact, all substances offer some "resistance" to the movement of electrons through them, and the magnitude of this resistance varies from a very low value in the case of a good conductor, through intermediate values for poor conductors and poor insulators, to a high value in the case of good insulators. The precise meaning of electrical resistance, and the unit in which it is measured, are explained in the next paragraph.

Ohm's Law

As a result of practical measurement, it was found by Ohm that :—

In any conductor, the ratio between the potential difference across it and the current flowing through it is a constant, provided that the physical conditions of the conductor, such as temperature, remain unchanged.*

This constant is termed the "resistance" of the conductor, and the practical unit is the "Ohm". This is defined as follows :—

If a PD of 1 volt across a conductor causes a current of 1 ampere to flow through it, then the resistance of that conductor is 1 ohm.

Using this definition, it follows that :—

$$\frac{E}{I} = R \quad (1)$$

where E is potential difference in volts,
 I is the current in amperes,
 and R is the resistance in ohms.

*There are a few exceptions which are dealt with in Chapter 6, but which need not be considered at this stage. The statement made here is true for all pure metals and alloys.

It is this mathematical expression which is usually known as "Ohm's Law", and it is often quoted in the equivalent forms:

$$E = IR \quad (2)$$

or

$$I = \frac{E}{R} \quad (3)$$

Resistances in series

With resistances in series, the current will be the same in each. Applying Ohm's law to each in turn:—

$$E_1 = IR_1$$

$$E_2 = IR_2$$

$$E_3 = IR_3$$

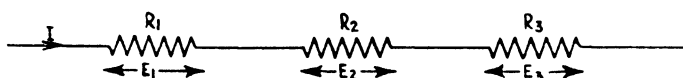


FIG. 82.—Resistances in series.

∴ The total potential difference E is:—

$$\begin{aligned} E &= E_1 + E_2 + E_3 \\ &= IR_1 + IR_2 + IR_3 \end{aligned}$$

But if R is resultant resistance, then by Ohm's law:—

$$E = IR$$

$$IR = IR_1 + IR_2 + IR_3$$

or

$$R = R_1 + R_2 + R_3 \quad (4)$$

Resistances in parallel

The potential difference across all three resistances is the same, *viz.*, the PD E volts between A and B . The total current I is given by:—

$$I = I_1 + I_2 + I_3$$

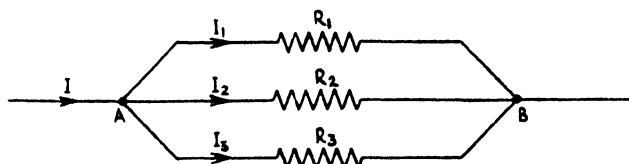


FIG. 83.—Resistances in parallel.

Applying Ohm's law to each resistance in turn:—

$$I = \frac{E}{R_1} + \frac{E}{R_2} + \frac{E}{R_3}$$

But if R is the resultant resistance, then by Ohm's law:—

$$I = \frac{E}{R}$$

$$\therefore \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \quad (5)$$

When two resistances are in parallel it will be noted that:—

since $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$

$\therefore R = \frac{R_1 R_2}{R_1 + R_2}$ (6)

The reciprocal of resistance is often termed the “conductance”, and is measured in mhos (sometimes called reciprocal ohms); that is:—

$$G \text{ (in mhos)} = \frac{1}{R \text{ (in ohms)}}$$

Then for conductances in parallel, the total conductance G is:—

$$G = G_1 + G_2 + G_3 + \dots \quad (7)$$

Specific resistance

The resistance of a conductor depends both on its dimensions and on the material of which it is made, and it is desirable to compare the resistive properties of materials in some way that is independent of the dimensions of the conductor. The “specific resistance” of a material (also known as resistivity) is defined as *the resistance between the opposite faces of a 1 cm. cube of the material*, and is measured in “ohms per cm. cube”. Then the resistance R of a conductor of that material is given by:—

$$R = \frac{\rho l}{A} \quad (8)$$

where l is the length of the conductor (in cm.),

A is the area of the conductor (in sq. cm.),

and ρ is the specific resistance of the material.

The reciprocal of specific resistance or resistivity is specific conductance or conductivity, which is measured in mhos per cm. cube.

Temperature Coefficient of resistance

As a general rule the specific resistance of a metallic conductor increases with rise in temperature. The following equation gives the relationship between the resistance, R_t at $t^\circ\text{C}$ and the resistance R_0 at 0°C ., for a very wide range of temperature.

$$R_t = R_0 (1 + \alpha t + \beta t^2) \quad (9)$$

where α and β are constants for the metal concerned. Over a moderate range of temperature, say 0° to 100°C ., the constant β , which is very small, has negligible effect, and the equation:—

$$R = R_0 (1 + \alpha t) \quad (10)$$

is sufficiently accurate. α is called the temperature coefficient of resistance. Table V gives average values of ρ and α .

TABLE V
Specific resistances and temperature coefficients

Metal.	Specific resistance ρ (ohms per cm. cube)	Temperature coefficient of resistance α
Copper ..	1.6×10^{-6}	0.004
Iron ..	9.8×10^{-6}	0.006
Manganin ..	44.0×10^{-6}	0.00002

Kirchhoff's laws

These two laws are of universal application in the treatment of electrical networks. For the purpose of this section, a network will be defined as any number of resistances and batteries connected together to form an electrical circuit.

Law 1.—The algebraic sum of currents meeting at any point in a network is zero.

Law 2.—The algebraic sum of the products of current and resistance in each conductor of a closed circuit is equal to the algebraic sum of the EMFs in that circuit.

The first law merely states that the current entering a point is equal to the current leaving it. This is equivalent to saying that there is no accumulation of charge at the point. The second law can be verified by application of Ohm's law, the term algebraic merely signifying that, if clockwise currents or EMFs are considered as positive, then anti-clockwise ones must be treated as negative. The law therefore states that the algebraic sum of EMFs and PDs in any closed circuit is zero.

Example.—

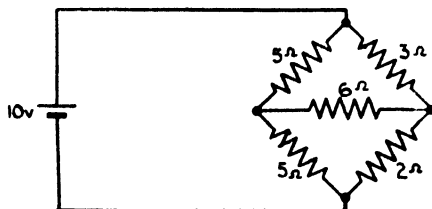


FIG. 84 (a)

The network shown in Fig. 84a has a potential of 10v applied to it from a battery that has no internal resistance. Find the current in the centre arm (6 ohms).

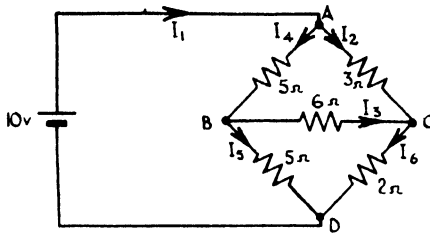


FIG. 84 (b)

Fig. 84b shows the circuit with the currents indicated as I_1 to I_6 .

But by Kirchhoff's first law, the currents leaving the point A are equal to the currents entering,

$$\begin{aligned} \therefore I_4 &= I_1 - I_2 \\ \text{Similarly at } B \quad I_5 &= I_4 - I_3 \\ &= I_1 - I_2 - I_3 \\ \text{and at } C \quad I_6 &= I_2 + I_3. \end{aligned}$$

To check these results, the current leaving D

$$\begin{aligned} &= I_5 + I_6 \\ &= I_1 - I_2 - I_3 + I_2 + I_3 \\ &= I_1 \end{aligned}$$

This must be correct, since I_1 was originally the current in this circuit.

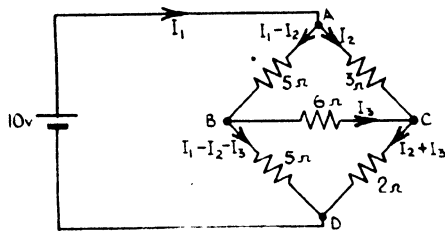


FIG. 84 (c)

Using these results (see Fig. 84c), the unknown quantities are now reduced to three—namely, I_1 , I_2 and I_3 —and it will be necessary to obtain three equations by application of Kirchhoff's second law to the network. At least one of these equations must contain the battery EMF.

Consider ACB . This is a closed network, and therefore Kirchhoff's second law may be applied to it:—

$$3I_2 - 6I_3 - 5(I_1 - I_2) = 0,$$

there being no applied EMF.

On simplifying this,

$$5I_1 - 8I_2 + 6I_3 = 0 \quad (i)$$

Consider BCD :—

$$6I_3 + 2(I_2 + I_3) - 5(I_1 - I_2 - I_3) = 0$$

Simplifying, $5I_1 - 7I_2 - 13I_3 = 0 \quad (ii)$

Consider outer network, ACD and battery :—

$$3I_3 + 2(I_2 + I_3) = 10$$

Simplifying, $5I_2 + 2I_3 = 10 \quad (iii)$

From equations (i) and (ii) :—

$$I_2 - 19I_3 = 0$$

$$I_2 = 19I_3$$

Substitute for I_2 in equation (iii) :—

$$5(19I_3) + 2I_3 = 10$$

$$I_3 = \frac{10}{97}$$

$$= 0.103 \text{ amps } Ans.$$

Measurement of resistance

There are three simple methods of measuring resistance, namely, by voltmeter and ammeter, by substitution, and by Wheatstone's bridge.

1. *Voltmeter and ammeter.*—A suitable voltage is applied to either of the networks shown in Fig. 85*a* and 85*b*. From the readings of the two meters, the value of R can be calculated by

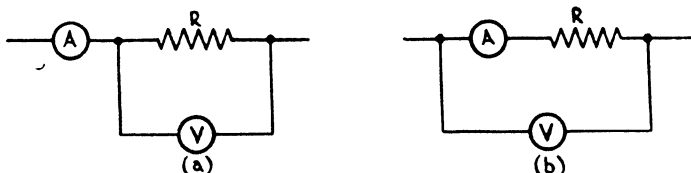


FIG. 85.—Measurement of resistance by voltmeter and ammeter method.

Ohm's law. Errors are introduced in both methods, since in (a) the ammeter reading includes the current through the voltmeter, and in (b) the voltmeter reading includes the voltage drop across the ammeter. If the resistances of the meters are known, correction can, however, be made. The resistance of a voltmeter is usually known more accurately than that of an ammeter, and also it is usually high compared with the resistance to be measured; method (a) is therefore preferable in most cases.

2: *By substitution.*—Connect the resistance R to be measured in series with a galvanometer and battery. Note the deflection obtained. Replace R by a calibrated resistance r and vary it until

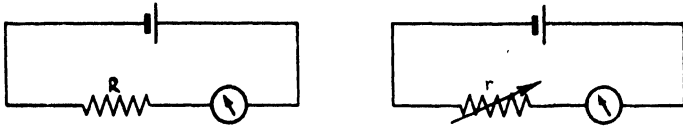


FIG. 86.—Measurement of resistance by substitution.

the galvanometer gives the same deflection as before ; the value of r is then equal to R .

Wheatstone's bridge

The bridge method for comparing and measuring resistances is very widely used and, though it will be considered here only from the DC aspect, its application is of great importance in AC work as well.

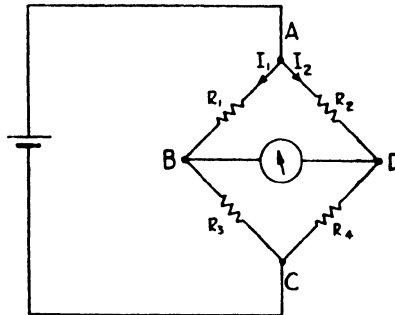


FIG. 87.—Measurement of resistance by Wheatstone's bridge.

Consider the condition of the network illustrated that will give no deflection in the galvanometer, *i.e.* no current in BD . This means that B and D are at the same potential or, in other words, the PD across AB = the PD across AD .

$$\therefore I_1 R_1 = I_2 R_2$$

$$\therefore \frac{I_1}{I_2} = \frac{R_2}{R_1}$$

Since there is no current in BD , then by applying Kirchoff's first law to the point B , the current in BC must be I_1 . Similarly, the current in DC is I_2 .

As before, the PD across BC = the PD across DC .

$$\therefore I_1 R_3 = I_2 R_4$$

$$\therefore \frac{I_1}{I_2} = \frac{R_4}{R_3}$$

Hence
$$\frac{R_2}{R_1} = \frac{R_4}{R_3}$$

This gives the condition that the bridge shall be balanced.

Therefore, if this condition can be reached, a simple relationship is set up between all four resistances; if the ratio $\frac{R_2}{R_1}$ and the value of R_3 are known, it is easy to calculate R_4 . This system is used in the metre bridge and in the Post-Office box. In the former, the known resistance is fixed and the ratio is varied; in the latter, the ratio is fixed and the known resistance is varied. Each gives a high degree of accuracy.

ELECTRICAL UNITS

In addition to the "practical" system of units, which is used for everyday electrical work and of which some examples have already been given, there exist three other systems of units. Two of these, the "electrostatic" and the "electromagnetic", are "absolute" systems based on theoretical considerations; while not used for practical measurements, they are none the less important to a study of electrical theory. The other system of units is the "international", which forms a standard against which the practical units can be compared.

Electrostatic units (ESU)

The "electrostatic unit of charge" is defined as *that charge which, when placed 1 cm. distant from an exactly similar charge in a vacuum, repels it with a force of 1 dyne.* Measurement of charge is simply a measurement of the number of electrons. If the electron had been discovered before the ESU of charge was defined, the electron might equally well have been made the basic unit of charge in theoretical considerations.

$$1 \text{ ESU of charge} \approx 2.09 \times 10^9 \text{ electrons.}$$

Electric current is measured as a rate of flow of charge (or electrons). The "electrostatic unit of current" is defined as *a rate of flow of one ESU of charge per second.*

Electric potential is a measure of the potential energy at a point due to its position in an electrostatic field. The actual value of the potential at a point, like all potential energies, is purely relative, and only the *potential difference* between two points is completely determinable. The "electrostatic unit of potential" is defined as *the potential difference that exists between two points when the work done in taking one ESU of charge from one point to the other is one erg [1 erg = 1 dyne-cm.].*

Electromagnetic units (EMU)

For completeness, the principal electromagnetic units will now be defined, although these will not be referred to again until later in the chapter. The basis of the electromagnetic system of units is the force between magnetic poles, just as the basis of the electrostatic system is the force between electric charges.

Current is measured in terms of the electromagnetic field it produces. The "electromagnetic unit of current" is defined as *that current which, when flowing in a circular loop of wire of radius 1 cm., produces at the centre a magnetic field of 2π dynes per unit pole.*

The "electromagnetic unit of electric charge" is defined as *that charge which is transferred past a point of a conductor when a current of one EMU flows for one second.*

The "electromagnetic unit of potential" is defined as *that potential difference which exists between two points when the work done in taking one EMU of charge from one point to the other is one erg.*

Practical units

Neither the electrostatic system nor the electromagnetic system of units is completely satisfactory as a means of expressing practical electrical measurements, since certain of these units are inconveniently large, others much too small. The fundamental practical units are rigidly defined as follows:--

$$1 \text{ Ampere} = 10^{-1} \text{ EMU of current } [\approx 3 \times 10^9 \text{ ESU of current}] \quad (11)$$

$$1 \text{ Volt} = 10^8 \text{ EMU of potential } [\approx \frac{1}{300} \text{ ESU of potential}] \quad (12)$$

$$1 \text{ Coulomb} = 10^{-1} \text{ EMU of charge } [\approx 3 \times 10^9 \text{ ESU of charge}] \quad (13)$$

These definitions were resolved in 1908 by an International Conference, which decided that the fundamental practical units should be based on the electromagnetic rather than on the electrostatic system. The connections quoted above between the practical units and the ESU are sufficiently accurate for almost all purposes.

International units

The international units were defined at the conference previously mentioned, in terms of the measurable physical quantities of mass, distance, and time. They are used as a basis of comparison and legislation. At the same time, their values correspond very closely with the fundamental practical units.

The "international ohm" is defined as *the resistance offered to an unvarying electric current by a column of mercury at 0° C. , 14.4521 grammes in mass, of a constant cross-section, and of length 106.300 cms.*

The advantage of such a unit lies in the fact that it has a definite physical interpretation.

The *international ampere* is defined in terms of an electro-chemical phenomenon, namely that if two electrodes are immersed in a solution of silver nitrate and a potential difference is maintained between them, a current will flow and silver will be deposited on the negative (lower potential) electrode. The rate of deposit of

silver is proportional to the current flowing. The definition is framed as follows :—

The "international ampere" is *that unvarying electric current which, when passed through an aqueous solution of silver nitrate, in accordance with an authorised specification, deposits silver at the rate of 0.0011180 grammes per second.*

The "international volt" is *that potential difference which must be applied across a conductor whose resistance is one international ohm in order to produce a current of one international ampere.*

POWER

Consider a conductor having a potential difference of e ESU between its two ends. The statement that the PD has this value is, by definition, equivalent to saying that the work done in passing one ESU of charge from one end of the conductor to the other is e ergs. The work done in passing a charge of q ESU will therefore be qe ergs. But if this process takes a time t secs, then

$$q = it \text{ where } i \text{ is the current in ESU}$$

$$\therefore \text{ Work done} = e it \text{ ergs.} \quad (14)$$

Now let the PD be E volts and the current I amps. Then for all practical purposes $e = \frac{E}{300}$ and $i = 3 \times 10^9 I$

$$\therefore \text{ The work done} = EIt \times 10^7 \text{ ergs} \quad (15)$$

But 10^7 ergs = 1 joule (practical unit of work)
and work done = EIt joules.

Power is the rate of doing work, *i.e.* :—

$$\text{Power} = EI \text{ joules per second.} \quad (16)$$

The unit of power is called the "watt".

$$1 \text{ watt} = 1 \text{ joule/second} \quad (17)$$

$$1 \text{ Kilowatt} = 1,000 \text{ joules/second} \quad (18)$$

$$1 \text{ kW-hour} = 1,000 \times 3,600 \text{ joules} \quad (19)$$

$$1 \text{ Horse power} = 746 \text{ watts} \quad (20)$$

$$= 550 \text{ ft.-lb./sec.} \quad (21)$$

$$4.18 \text{ joules} = 1 \text{ calorie of heat energy.} \quad (22)$$

The formula for power may be adapted as required, by using Ohm's law.

$$i.e., \quad \text{Power} = E \times I \text{ watts} \quad (23)$$

$$= \frac{E^2}{R} \text{ watts} \quad (24)$$

$$= I^2 R \text{ watts} \quad (25)$$

Maximum power transfer theorem (DC case)

Consider a battery or generator of EMF E and internal resistance r , supplying current to a load R .

By Ohm's law :—

$$I = \frac{E}{R + r}$$

Therefore the power P supplied to the load R is :—

$$\begin{aligned} P &= I^2 R \\ &= E^2 \cdot \frac{R}{(R + r)^2} \end{aligned}$$

It is required to find the value of R that will enable maximum power to be taken from the generator. Therefore in the expression

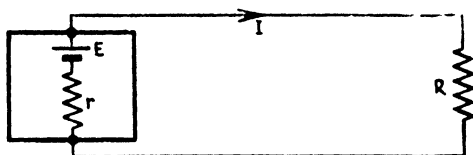


FIG. 88.—Maximum power transfer (DC case).

above, E and r will be considered constant and the expression differentiated with respect to R :—

$$\begin{aligned} P &= E^2 \cdot \frac{R}{(R + r)^2} \\ \frac{dP}{dR} &= E^2 \left[\frac{(R + r)^2 - 2R(R + r)}{(R + r)^4} \right] \\ &= E^2 \left[\frac{r - R}{(R + r)^3} \right] \end{aligned}$$

For a maximum or minimum value, $\frac{dP}{dR} = 0 \quad \therefore R = r$ (26)

It may be verified, by a second differentiation, that $R = r$ gives a *maximum* value of P . This therefore gives the theorem :—
Maximum power is transferred from a generator to the load when the resistance of the load is equal to the resistance of the generator.

ELECTROSTATICS AND CAPACITY

In order to study the problem of capacity it is necessary first of all to consider electrostatics in a little more detail. The basis of electrostatics is "Coulomb's Law" concerning the force of repulsion between two like charges of q_1 and q_2 ESU respectively at a distance d cms. apart :—

$$F = \frac{q_1 \times q_2}{k d^2} \text{ dynes,} \quad (27)$$

where k is the "dielectric constant" of the medium separating

the charges. This constant is unity for a vacuum (and approximately so for air) and this law is the basis on which the ESU of charge was defined.

Field strength, potential difference, and potential

The "field strength" F at a point is *the force in dynes that would act on a positive unit charge placed at that point*. Field strength is measured in dynes per unit charge.

The "potential difference" between two points is *the work done (in ergs) in moving a unit positive charge from one point to the other*.

The "potential" at a point is *the work done (in ergs) in moving a unit positive charge from infinity to the point*. That is to say, it is the potential difference between the particular point and some reference point remote from the field.

Potential at a point distant r cm. from a point charge

The potential at the point B , distant r cm. from a charge q ESU (see Fig. 89), is the work done in moving a unit positive charge from

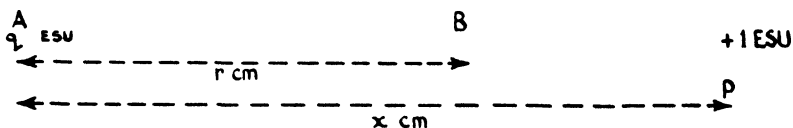


FIG. 89.—Potential at a distance from a point charge.

infinity to the point B . Suppose that the unit charge has been moved to a point P distant x cm. from A . The field strength at P is

$$F = \frac{q \times 1}{kx^2} \text{ dynes per unit charge}$$

If the unit charge is moved a small distance δx towards B it will experience a force resisting this motion, and the force may be taken as constant and equal to $\frac{q}{kx^2}$ dynes over the *small* distance δx .

The work done in this short distance is $\frac{q}{kx^2} \delta x$ ergs.

The work done in bringing the unit charge from infinity to the point B , r cm. from q , is the summation of this work over the total distance, and this is equal to:—

$$\int_r^\infty \frac{q}{kx^2} dx, \text{ so that:—}$$

$$E = \left[-\frac{q}{kx} \right]_r^\infty,$$

$$\therefore E = \frac{q}{kr} \text{ ESU} \quad (28)$$

Since the field strength at B is :—

$$F = \frac{q}{kr^2}$$

it is seen that in this particular case :—

$$F = - \frac{dE}{dr} \quad (29)$$

i.e., Field strength = - potential gradient.

This is a completely general result, true for any electrostatic field.

Potential of an isolated conducting sphere carrying a charge

Consider a metal sphere carrying a charge of q ESU and of radius a cms. This sphere is to be imagined as completely isolated ; that is, infinitely remote from any distorting fields. Under these conditions the charge will be distributed equally over the whole surface of the sphere, and it can be shown that, at an external point such as P , this distributed charge will have exactly the same effect as a charge q ESU concentrated at the centre of the sphere.

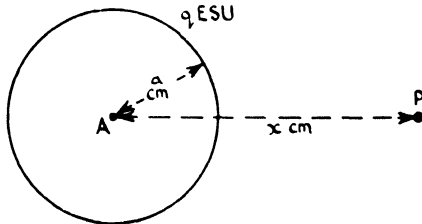


FIG. 90.—Point P distant x cm from charged sphere.

The potential at the surface of the sphere is then the potential at a point distant a cms. from a point charge q ESU,

$$\text{i.e.,} \quad E = \frac{q}{ka} \text{ ESU}$$

$$\therefore \quad \frac{q}{E} = ka \quad (30)$$

The interpretation of this result is that in the case of an isolated charged sphere the ratio of charge to potential is a constant depending only on the dimensions of the sphere and nature of the surrounding medium. This constant is called the "Capacity" of the sphere, and in a vacuum ($k = 1$) is numerically equal to the radius of the sphere in centimetres.

In general, for any insulated conductor, the ratio of charge to potential is a constant, depending only on the shape and dimensions of the conductor and on the nature of the surrounding medium. This ratio is called the capacity of the conductor, and denoting it by C :—

$$C = \frac{Q}{E} \quad (31)$$

Capacity has the dimensions of a length, and the electrostatic unit of capacity is the centimetre. If Q is measured in coulombs and E in volts, then the capacity C in farads is :—

$$C \text{ (farads)} = \frac{Q \text{ (coulombs)}}{E \text{ (volts)}} \quad (32)$$

Thus a conductor is said to have a capacity of one farad if a charge of one coulomb raises its potential by one volt.

$$1 \text{ farad} = 9 \times 10^{11} \text{ ESU of capacity.} \quad (33)$$

One farad is therefore the capacity of an isolated sphere of radius 9×10^{11} cms. in a vacuum, *i.e.*, 5.6×10^6 miles radius. Clearly such a unit is much too large for practical purposes and the unit usually employed is the "micro-farad" (μF).

$$1 \mu\text{F} = 10^{-6} \text{ farads} = 9 \times 10^5 \text{ ESU of capacity.} \quad (34)$$

Smaller capacities are sometimes expressed in "micro-micro-farads" ($\mu\mu\text{F}$) or pica-farads (pF).

$$1 \mu\mu\text{F} = 10^{-6} \mu\text{F} = 10^{-12} \text{ farads} = 0.9 \text{ ESU of capacity.} \quad (35)$$

Capacity of a parallel plate condenser

Consider an isolated sphere of radius r cms. carrying a charge q ESU (Fig. 91). It has been seen that the potential is $\frac{q}{kr}$ ESU and the capacity is kr ESU.

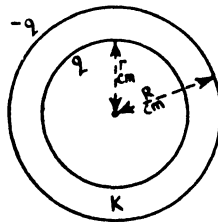


FIG. 91.—Capacity between two concentric spheres.

Now suppose that the sphere is surrounded by another concentric conducting sphere of radius R cms. The potential of the outer sphere will be $\frac{q}{kR}$ ESU. If now the outer sphere is earthed it takes on an induced charge $-q$ and its potential falls to zero; that is to say, its potential is $+\frac{q}{kR}$ due to the charge on the inner sphere, and $-\frac{q}{kR}$ due to its own induced charge. But the potential inside a hollow conductor due to a charge on its surface is everywhere the same as the potential of the surface. Therefore due to the induced charge, the potential of the inner sphere is $-\frac{q}{kR}$. The effect of the two charges together is to give the outer sphere zero potential and

the inner sphere a potential $\left(\frac{q}{kr} - \frac{q}{kR}\right)$, the first term being due to the original charge, and the second term due to the induced charge on the outer sphere.

The potential difference between the spheres is :—

$$E = \frac{q}{kr} - \frac{q}{kR} = \frac{q}{k} \left(\frac{1}{r} - \frac{1}{R} \right) \text{ ESU}$$

The capacity of the system is :—

$$C = \frac{q}{E} = \frac{k}{\frac{1}{r} - \frac{1}{R}} \text{ ESU}$$

$$\therefore C = \frac{kRr}{R-r} \text{ ESU} \quad (36)$$

The capacity per unit area of the inner sphere is therefore

$$\frac{kR}{(R-r)4\pi r} \text{ ESU}$$

From this result can be deduced the capacity of a flat parallel plate condenser. For suppose that r and R are both infinitely large but that their difference $R - r = d$ is finite.

The capacity per unit area of the inner sphere becomes

$$\begin{aligned} \text{Limit}_{r \rightarrow \infty} \frac{kR}{(R-r)4\pi r} &= \text{Limit}_{r \rightarrow \infty} \frac{k(r+d)}{d4\pi r} \\ &= \frac{k}{4\pi d} \end{aligned}$$

This is the capacity of a parallel plate condenser per unit area.

If A sq. cms. is the area of the plates,

$$C = \frac{kA}{4\pi d} \text{ ESU} \quad (37)$$

In air $k \simeq 1$

$$\therefore C_{\text{air}} \simeq \frac{A}{4\pi d}$$

This result may be obtained more easily if "Coulomb's Theorem" is assumed. This theorem is a basic theorem of electrostatics. It states that *the field strength just outside the surface of a conductor is $F = \frac{4\pi\sigma}{k}$ where σ is the charge density at that point of the surface (charge per unit area) and k is the dielectric constant of the surrounding medium. Moreover, the direction of the field is normal to the surface.*

Let the area of each plate be A sq. cms. It will be assumed that the area of the plates is large compared with the distance d cms. between them, so that there is everywhere between the plates a uniform normal electric field of strength F , say.

If E_p is the potential at a point such as P (Fig. 92) and the field strength is F ,

$$\text{then} \quad F = - \frac{dE_p}{dx}$$

$$\therefore E_p = - \int F dx$$

and the PD between the plates is:—

$$E = - \int_d^0 F dx = Fd$$

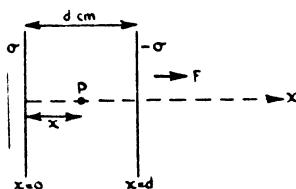


FIG. 92.—Capacity between two flat parallel plates.

But F is everywhere constant, and by Coulomb's Theorem, near the surface, $F = \frac{4\pi\sigma}{k}$.

$$\therefore E = \frac{4\pi\sigma d}{k} \quad \text{ESU}$$

But the total charge on each plate is numerically:—

$$q = \sigma A \quad \text{ESU}$$

$$C = \frac{q}{E} = \frac{kA}{4\pi d} \quad \text{ESU}$$

Capacity between two co-axial cylinders

To find an expression for the capacity of a condenser whose plates are co-axial cylinders, (see Fig. 93), of radii r and R , (e.g., the capacity of a co-axial cable).

It is necessary first to consider the electrostatic field at a distance x cms. from a uniformly distributed line charge of λ ESU per cm.

Consider the field due to a length ds of the charge:—

$$dF = \frac{\lambda ds}{kx^2 \sec^2 \theta}$$

and the component perpendicular to the line charge is:—

$$dF_n = \frac{\lambda \cdot ds}{kx^2 \sec^2 \theta} \cos \theta$$

But

$$ds = d(x \cdot \tan \theta) = x \cdot \sec^2 \theta d\theta$$

$$\therefore dF_x = \frac{\lambda \cdot \cos \theta \cdot d\theta}{r^2}$$

and the total field due to a line of infinite length having a charge λ per cm. is :—

$$\begin{aligned} F &= \frac{\lambda}{kx} \int_{-\frac{\pi}{2}}^{+\frac{\pi}{2}} \cos \theta \, d\theta = \frac{\lambda}{kx} [\sin \theta]_{-\frac{\pi}{2}}^{+\frac{\pi}{2}} \\ &= \frac{2\lambda}{kx} \text{ dynes per unit charge.} \end{aligned}$$

Now consider a long cylinder of radius r cms., and carrying a charge λ ESU per cm. of its length. At points outside the cylinder,

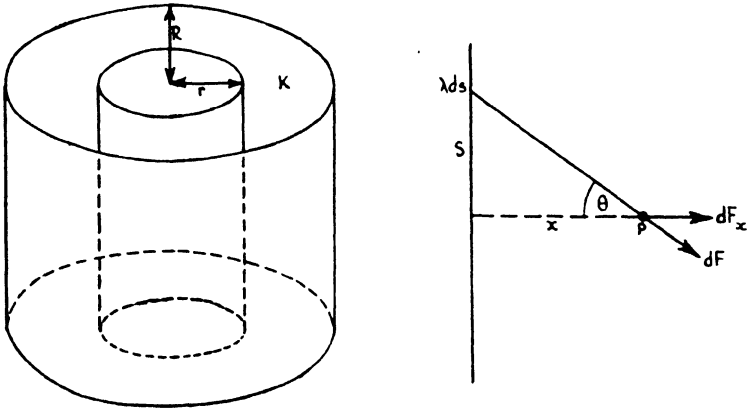


FIG. 93.—Capacity between two coaxial cylinders.

the charge will behave like a line charge λ per cm. along the axis of the cylinder, and the field at a point distant x cms. from the axis will be $\frac{2\lambda}{kx}$ ESU. The potential at such a point is therefore :—

$$E = - \int F \cdot dx = - \frac{2\lambda}{k} \int \frac{1}{x} dx = - \frac{2\lambda}{k} \log_e x$$

The potential at the inner plate is therefore $-\frac{2\lambda}{k} \log_e r$,

and the potential at the outer plate is $-\frac{2\lambda}{k} \log_e R$.

The potential difference is therefore $\frac{2\lambda}{k} \log_e \left(\frac{R}{r} \right)$; but the charge per unit length is λ ESU, therefore the capacity per unit length is :—

$$C = \frac{k}{2 \log_e \left(\frac{R}{r} \right)} \text{ ESU per cm} \quad (38)$$

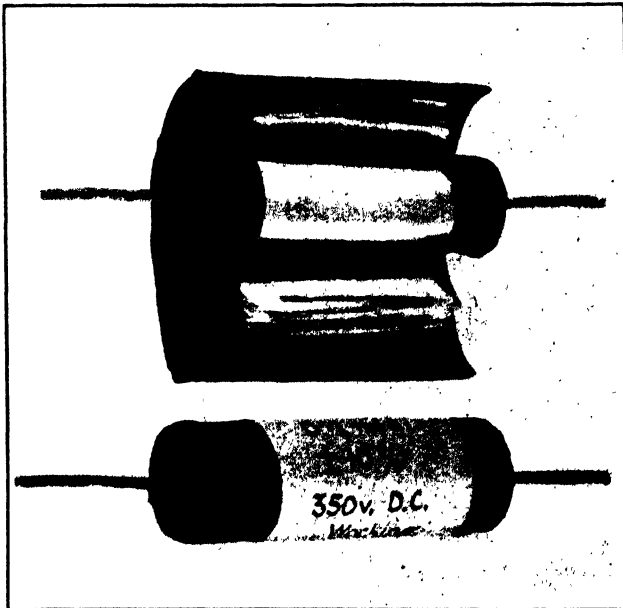
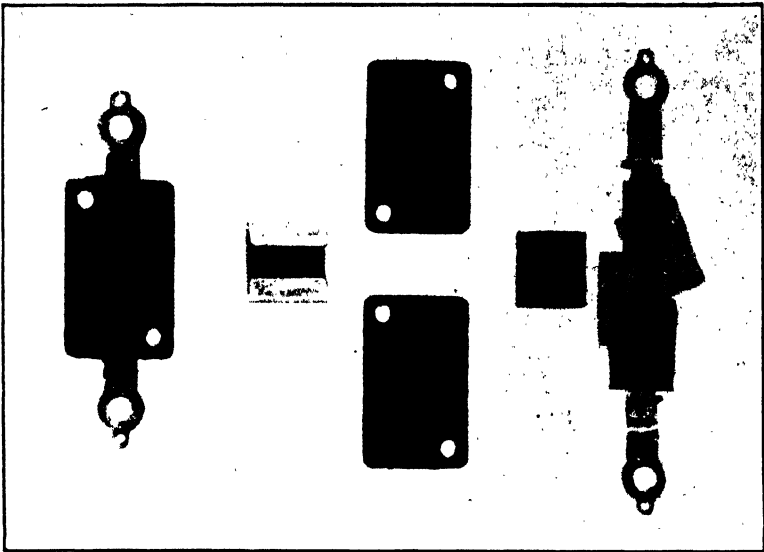


PLATE 3.—Mica and paper condensers showing construction.

Capacity between two parallel wires

If two wires both have radius a , and their centres are separated by a distance c (see Fig. 94), it can be shown that the capacity

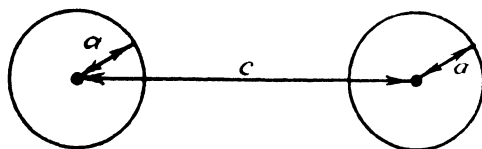


FIG. 94.—Capacity between two parallel wires.

between the wires is given by :—

$$\begin{aligned}
 C &= \frac{k}{4 \log_e \left(\frac{c}{a} \right)} \text{ ESU per cm.} \\
 &= \frac{0.01941k}{\log_{10} \left(\frac{c}{a} \right)} \mu\text{F per mile}
 \end{aligned}
 \tag{39}$$

provided that $a \ll c$.

Dielectric constant

The " dielectric constant " k of a material may be defined as *the ratio of the capacity of a condenser employing that material as dielectric to the capacity of an exactly similar condenser but employing a vacuum as the dielectric.*

Some typical values of dielectric constants are given in Table VI:—

TABLE VI.
Dielectric constants.

Medium	Dielectric constant
Paxolin	5 to 8
Ebonite	2.7 to 2.9
Mica	5.7 to 7
Polythene	2.2 to 2.4
Paraffin wax	2 to 2.3
Air	1.0006
Vacuum	1

From the formula for the capacity of a parallel plate condenser it will be seen that to give a large value of capacity the conditions are : large area plates, small separation between plates, and a high dielectric constant.

Dielectrics

It has already been mentioned that when an electrostatic field is applied to a dielectric there is a distortion of the electron orbits due to the interaction of the field and the orbital electrons. This results in a mechanical stress being set up in the dielectric, and a dielectric in this condition is said to be "polarised". This hypothesis explains all the phenomena associated with dielectrics.

If a condenser is charged and then discharged, and is then left for a short time with the plates open-circuited, it is found that it again becomes charged to a small extent. This charge, which is of the same polarity as the original charge, is called the "residual charge", and is due to the slow return of the polarised dielectric to its normal unpolarised condition.

When a dielectric is polarised, there is a nett transfer of electrons in the direction opposite to that of the applied field. This transfer of electrons gives rise to a "displacement current", and the mechanical stress produces heat in the dielectric. This heat produced indicates a power loss known as "dielectric loss".

If a condenser is subjected to a very high voltage, "dielectric breakdown" may occur. This is due to the large field overcoming the forces holding the electrons in their orbits; the electrons break away, and the dielectric becomes a conductor. With solid dielectrics the damage caused is permanent, and the condenser becomes useless. In the case of liquid and gaseous dielectrics, sparking occurs, but as soon as the peak voltage has passed, the dielectric "heals up" and recovers its normal properties. The ability of a material to resist breakdown is known as its "dielectric strength", and is measured in terms of the voltage at which breakdown occurs. Such figures are useful only for rough comparison, since they depend on the thickness of the sample and on the conditions under which the test is made. Considerations of dielectric strength are mainly the concern of the power engineer.

The type of condenser used for any particular purpose depends largely on two factors: the capacity required, and the maximum voltage to which the condenser will be subjected. Air condensers can be used for capacities up to $0.001 \mu\text{F}$ ($1,000 \mu\mu\text{F}$), but they are bulky and are used only where a variable condenser is required. Ceramic condensers cover a similar range, $5 \mu\mu\text{F}$ to $1,000 \mu\mu\text{F}$, for fixed condensers. Mica condensers are normally used over a range from $50 \mu\mu\text{F}$ to $0.01 \mu\text{F}$. Paper condensers cover the range from $0.0001 \mu\text{F}$ to $8 \mu\text{F}$. Where possible, paper condensers are used for economic reasons; but since the dielectric strength of mica is approximately ten times that of paper, a paper condenser of say $0.01 \mu\text{F}$ for 1,000 V. working might be larger and more expensive than a similarly rated mica condenser.

Electrolytic condensers

If two aluminium plates are immersed in a suitable electrolyte

such as a borax solution, the application of a direct voltage will cause a current to flow. This current rapidly diminishes to a small value due to the formation of a thin insulating film of aluminium oxide on the positive electrode. Owing to the extreme thinness of this film (0.01 to 0.05×10^{-3} cm.), a high capacity will exist between the positive electrode and the solution. This arrangement forms the basis of electrolytic condensers enabling

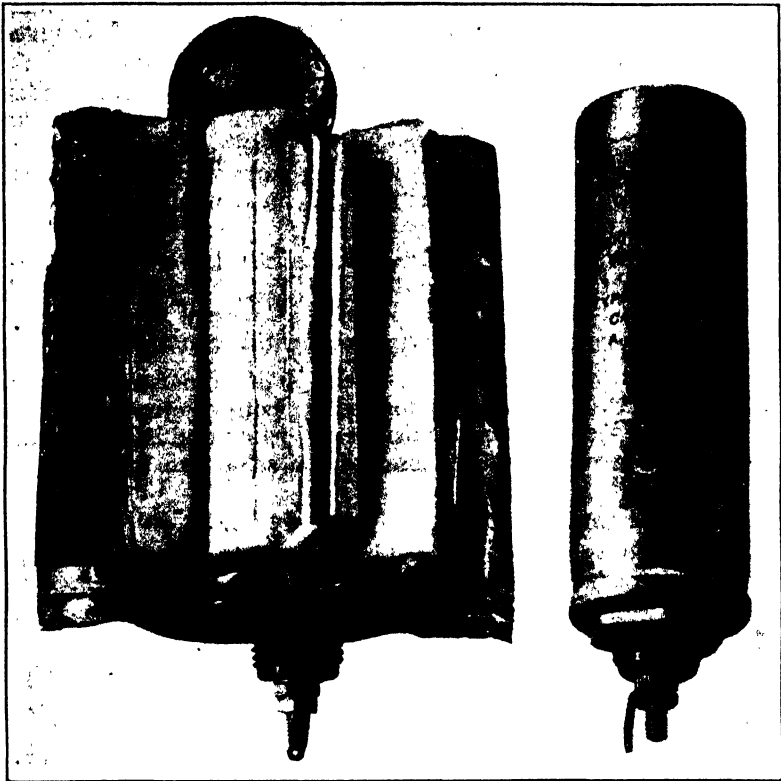


PLATE 4.—Electrolytic condenser.

large values of capacity to be obtained in a small volume and at low cost.

Most electrolytic condensers require the presence of a polarising direct current to maintain the film, and such condensers can be used only in circuits where the peak value of the alternating voltage is less than that of the superimposed direct voltage.

The dielectric strength of the oxide film is high, and condensers can be made to withstand voltages up to 500–700 V. The rated voltage of a condenser is always slightly less than that of the forming

voltage. Above this voltage, the leakage current becomes excessive, and perforations of the film may occur.

A film of electrolyte is always present, so that any perforation that may occur can be immediately resealed. The nature of the electrolyte may vary, giving three different types:—

(a) The "wet" electrolytic condenser. In this type, the anode is suspended in the centre of a cylindrical container which forms the cathode, and a liquid electrolyte is used. The shape of the anode is designed to give a large surface area, thus increasing the capacity, while the liquid electrolyte gives the advantage of quick resealing after a breakdown.

(b) The "semi-dry" electrolytic condenser. The electrodes take the form of long strips of aluminium foil, the dielectric film having been formed on the anode. These are rolled together, being separated usually by a cotton gauze impregnated with the electrolyte. The roll is mounted in an aluminium or bakelite container.

(c) The "dry" electrolytic condenser. The construction is similar to that of the semi-dry type, but a material is added to the electrolyte to make it solid at normal temperatures. This is the most common type used in this country.

Reversible electrolytic condensers consist of ordinary electrolytic condensers with an oxide film formed on both electrodes. They are thus equivalent to two condensers in series, and have half the capacity of an ordinary condenser of the same size.

Condensers in parallel

When condensers are connected in parallel, they have a common voltage, but each has its own charge.

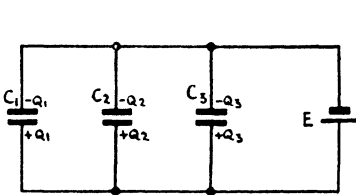


FIG. 95.—Condensers in parallel.

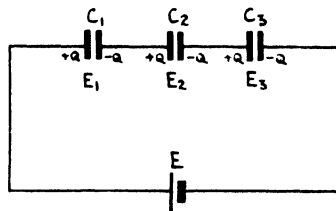


FIG. 96.—Condensers in series.

The total charge

$$Q = Q_1 + Q_2 + Q_3$$

∴

$$\frac{Q}{E} = \frac{Q_1}{E} + \frac{Q_2}{E} + \frac{Q_3}{E}$$

∴

$$C = C_1 + C_2 + C_3 \quad (40)$$

Condensers in series

A charge $+Q$ on the left-hand plate of C_1 will induce $-Q$ on the second plate, this causes $+Q$ on C_2 , and so on. Thus all the

condensers have the same *charge*, which is equal to the total charge :—

$$\begin{aligned}
 Q &= Q_1 = Q_2 = Q_3 \\
 \text{But } E &= E_1 + E_2 + E_3 \\
 \therefore \frac{Q}{C} &= \frac{Q_1}{C_1} + \frac{Q_2}{C_2} + \frac{Q_3}{C_3} \\
 \therefore \frac{1}{C} &= \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \tag{41}
 \end{aligned}$$

Charge and discharge of a condenser

Consider a series circuit of battery, condenser, resistance and key as shown in Fig. 97. The left-hand plate of the condenser will

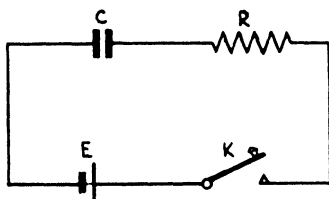


FIG. 97.—Circuit for charging a condenser *C* through a resistance *R*.

be at the same potential as the negative plate of the battery, and on closing the key the whole of the EMF will drive a current through *R* to charge the condenser. The magnitude of this current is dependent on *R*.

Immediately *C* commences to acquire a charge, the charging current will drop, and therefore the PD across *R* will fall. This process continues so that, as the charge in the condenser approaches its full value, the charging current becomes less and less. By continuation of this argument it may be shown that, in theory, the condenser will take an infinite time to become fully charged. This deduction is proved mathematically below.

At any instant, *t* seconds after closing the key,
 let *v* be the PD across the condenser,
i be the charging current,
q be the charge on the condenser.

$$\begin{aligned}
 \text{Then } i &= \frac{dq}{dt} \\
 &= \frac{d(Cv)}{dt} \\
 \text{But } i &= \frac{\text{PD across } R}{R} \\
 &= \frac{E - v}{R}
 \end{aligned}$$

$$\therefore \frac{E - v}{R} = C \frac{dv}{dt}$$

$$\frac{dv}{dt} + v \cdot \frac{1}{CR} = \frac{E}{CR}$$

Multiply by $e^{\frac{t}{CR}}$:—

$$\frac{dv}{dt} \cdot e^{\frac{t}{CR}} + \frac{v}{CR} \cdot e^{\frac{t}{CR}} = \frac{E}{CR} \cdot e^{\frac{t}{CR}}$$

The left-hand side of this equation is the differential coefficient of $v \cdot e^{\frac{t}{CR}}$, so that this equation can be written as :—

$$\frac{d}{dt} \left[v \cdot e^{\frac{t}{CR}} \right] = \frac{E}{CR} \cdot e^{\frac{t}{CR}}$$

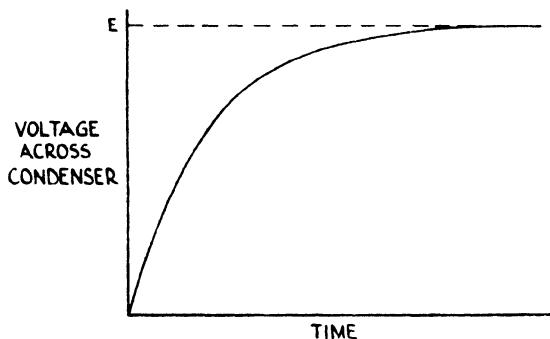


FIG. 98.—Graph showing charging of condenser.

Integrating :—

$$v \cdot e^{\frac{t}{CR}} = E \cdot e^{\frac{t}{CR}} + K, \text{ where } K \text{ is a constant,}$$

$$\therefore v = E + K \cdot e^{-\frac{t}{CR}}$$

But when $t = 0$, $v = 0$, hence K may be determined :—

$$K = -E$$

$$\text{Thus } v = E \left(1 - e^{-\frac{t}{CR}} \right) \quad (42)$$

From this formula it will be seen that, as t increases, v becomes nearer and nearer to E but will not reach it until, t being infinite, the factor $e^{-\frac{t}{CR}}$ becomes zero. A graph showing the voltage across the condenser increasing exponentially with time is given in Fig. 98.

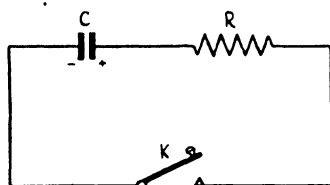


FIG. 99.—Circuit for discharging a condenser C through a resistance R .

If the battery is now removed and the key again closed, the condenser starts to discharge. At first, the PD across the condenser driving the discharge current through R is equal to E ; but as soon as the condenser partly discharges, this PD drops, and the current (*i.e.* the rate of discharge) drops. The curve of the discharge is again exponential, and theoretically the condenser never fully discharges.

The current i is now decreasing, so that :—

$$i = - \frac{dq}{dt}$$

$$= - C \frac{dv}{dt}$$

Also
$$i = \frac{\text{PD across } R}{R}$$

$$= \frac{v}{R}$$

$$\therefore \frac{v}{R} = - C \frac{dv}{dt}$$

$$\therefore \frac{dv}{dt} + \frac{1}{CR} \cdot v = 0$$

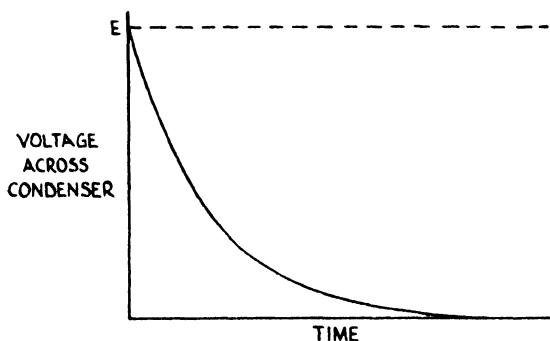


FIG. 100.—Graph showing discharge of condenser.

$$\therefore \frac{dv}{dt} e^{\frac{t}{CR}} + \frac{1}{CR} v \cdot e^{\frac{t}{CR}} = 0$$

$$\therefore \frac{d}{dt} \left(v \cdot e^{\frac{t}{CR}} \right) = 0$$

$$\therefore v \cdot e^{\frac{t}{CR}} = K, \text{ where } K \text{ is a constant}$$

$$\therefore v = K \cdot e^{-\frac{t}{CR}}$$

When $t = 0$, $v = E$, hence K may be determined :—

$$K = E$$

$$\text{Thus } v = E \cdot e^{-\frac{t}{CR}} \quad (43)$$

The graph of this function gives therefore the discharge curve of the condenser, and is shown in Fig. 100.

Time constant

In the design of electrical apparatus, it is often required to produce a resistance-capacity circuit with a definite time of discharge or charge. It has been shown that theoretically this time is infinite,

TABLE VII
Condenser charge and discharge

% divergence from total charge or discharge	Time of Charge or Discharge
1.8%	4 CR secs.
3.1%	3.5 CR secs.
5.0%	3 CR secs.
8.3%	2.5 CR secs.
13.5%	2 CR secs.
37 %	1 CR secs.

but the practical aspect will now be considered. From equations 42 and 43 for v , it is noticed that the rate of charge or discharge is dependent on the product CR . This product is therefore termed the "time constant" of the circuit.

(a) Charge: When $t = CR$ secs.

$$v = E (1 - e^{-1})$$

$$= 63\% E.$$

(b) Discharge: When $t = CR$ secs.

$$v = E \cdot e^{-1}$$

$$= 37\% E$$

That is, when C and R are in farads and ohms respectively, the product CR gives the time in seconds for the condenser (*a*) to charge up to 63 per cent. of full charge, or (*b*) to discharge from full charge to 37 per cent. of full charge. Table VII shows how this time constant is utilised in designing practical circuits when a certain margin is permissible between the total charge or discharge and that actually reached after a given time.

Example.—A condenser-resistance circuit is required to have discharge time of 150 milliseconds. A 5 per cent. margin is allowable. (Condenser must be at least 95 per cent. discharged in the 150 milliseconds.)

From table, for a 5 per cent. margin,

$$3 CR = 0.150 \text{ secs.}$$

$$\therefore CR = 0.050 \text{ secs.}$$

Choosing $C = 0.1 \mu\text{F}$ as a suitable condenser,

$$R = \frac{0.050}{0.1 \times 10^{-6}} \text{ ohms} = 0.5 \text{ Megohm. Ans.}$$

MAGNETISM

Certain specimens of magnetite, an ore of iron mined in various parts of the world, are called natural magnets or lodestones, and possess the following properties :—

- (a) they attract small fragments of iron and steel ;
- (b) when suitably suspended, they come to rest in a definite position relative to the points of the compass ;
- (c) they are able to confer both these properties on certain other materials, notably iron, steel, nickel and cobalt.

These properties have been known from the earliest times, but it was not until very much later that it was found that these properties could be artificially imparted to steel and iron by means of an electric current.

Magnets may be classified as permanent magnets and electro-magnets. Permanent magnets are made of steel or such alloys as cobalt steel, and once magnetised they retain their magnetic properties for a long period under normal conditions. Electromagnets are made with a core of soft iron or of iron alloys such as permalloy (iron-nickel), and have the property that, although more easily magnetised, they lose their magnetic properties almost immediately when the magnetising influence is removed.

Permanent magnets

Fig. 101 represents a rectangular bar magnet that will attract fragments of iron brought near either end, and will exert a force of either repulsion or attraction on other magnets in the vicinity. The influence of the magnet may be detected in the surrounding space in various ways, and it is found to vary inversely with the square of the distance from the magnet. To account for this

phenomenon, the magnet is said to establish a magnetic field, which is represented by the curved lines (lines of force) in Fig. 101. This method of representing the magnetic field is merely a convention adopted to give a simple pictorial representation of the influence of the magnet in the surrounding space.

Ewing has shown that the behaviour of permanent magnets and magnetic materials may be explained on the assumption that they are made up of a very large number of small cuboids, each of which has the properties of a permanent magnet. In the unmagnetised material, these small magnets have a random orientation, and the specimen shows no resultant magnetic properties. Magnetisation has the effect of orientating the small magnets along an axis, called the magnetic axis, which joins those two points near the ends of the

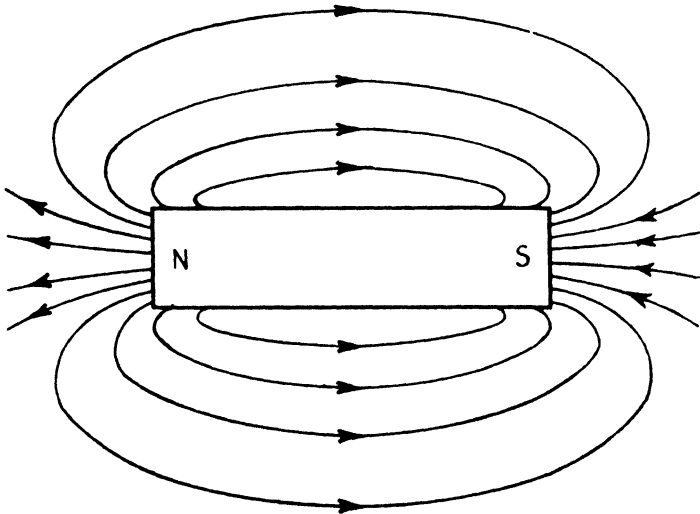
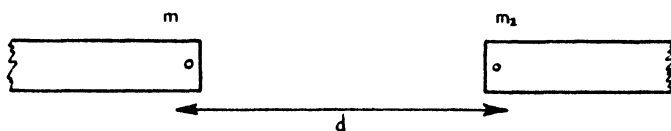


FIG. 101.—Field round a bar magnet.

magnet where the effect of the magnetic field appears to be concentrated; these points are known as poles. Every magnet is assumed to possess two poles, a north-seeking pole, which experiences a force of attraction towards the Earth's north magnetic pole, and a south-seeking pole, which is attracted to the Earth's south magnetic pole. These poles cannot, of course, be isolated, since two unlike poles comprise a magnet and an isolated pole has no physical meaning. It is possible, however, to visualise an isolated pole by considering a magnet that is so long, that the influence of the unwanted pole is negligible in the vicinity of the pole being examined. On this basis, careful experiment has shown that the force between two such poles is directly proportional to the "strength" m of each pole, and inversely proportional to the square of the distance d between the poles (see Fig. 102),

FIG. 102.—Force between two magnetic poles distant d apart.

i.e.,
$$\text{Force} \propto \frac{mm_1}{d^2}$$

In this connection, the strength of a magnetic pole is merely a theoretical idea, but it can be given a physical meaning by defining a unit magnetic pole as follows.

A "unit magnetic pole" is that pole which, when separated by one centimetre (in vacuo) from an exactly similar pole, repels it with a force of one dyne.

The law for the force of repulsion then becomes :—

$$\text{Force} = \frac{mm_1}{\mu d^2} \text{ dynes} \quad (44)$$

where d is the distance between the poles in centimetres, and μ is a property of the surrounding medium, known as its permeability ($\mu = 1$ for a vacuum, and is approximately equal to 1 for air). For convenience, north-seeking poles are assumed to have a positive pole strength, and south-seeking poles a negative pole strength. Thus, for unlike poles, the force is a negative repulsion, *i.e.*, an attraction.

The "field strength" at a point is the force that would be experienced by a unit north-seeking pole placed at that point. It is a vector, denoted by H , and its magnitude is measured in dynes per unit pole, gauss, or occasionally oersteds.

The force experienced by a pole of strength m will be Hm dynes. A magnet of pole strength m and length l cms. set at right angles

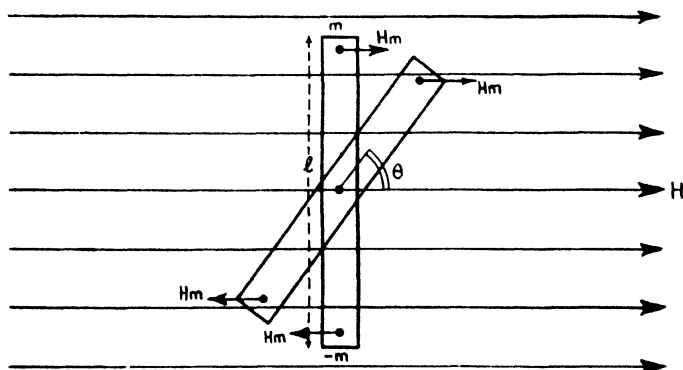


FIG. 103.—Magnetic moment.

to a uniform magnetic field of strength H gauss will therefore experience a turning moment Hml centimetre-dynes tending to align it with the magnetic field. When the magnet makes an angle θ with the field (see Fig. 103), the turning moment is reduced to $Hml \sin \theta$, which vanishes when $\theta = 0$.

The product ml is known as the "magnetic moment" of the magnet, and is *the turning moment that is experienced by the magnet when placed at right angles to a uniform magnetic field of unit strength.*

Magnetic flux and lines of induction

From equation 44, the force between two poles, one a unit pole, the other of strength m , at a distance d cms. apart, is:—

$$\text{Force} = \frac{m}{\mu d^2} \text{ dynes.}$$

This, by definition, is the field strength at a point d cms. from an isolated pole of strength m ,

$$\text{i.e.} \quad H = \frac{m}{\mu d^2} \text{ gauss.}$$

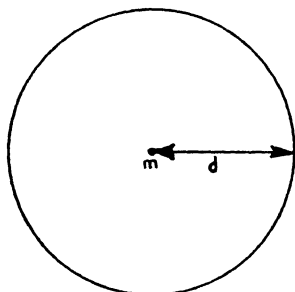


FIG. 104.—Sphere of radius d surrounding isolated pole m .

Thus, the field strength in this simple case depends on the permeability of the medium, and this is true in the general case, for a complex magnetic field may be built up of fields due to simple poles. It is convenient to have a notation for expressing magnetic effects that is independent of the permeability of the medium. This is done by using a theoretical concept, lines of induction, defined as follows:—

All lines of induction leave every unit north-seeking pole and enter every unit south-seeking pole.

The total number of lines of induction in a magnetic system is called the "flux", represented by the letter Φ . The flux density B is the flux per unit area, and is expressed in lines per square centimetre. Thus $\Phi = B.A$, where A is the cross-sectional area normal to the lines of induction.

The fact that B , like Φ , is a vector may be seen from the

fact that it is the number of lines per square cm. crossing a surface that is orientated in a particular way ; it may therefore be regarded as having direction as well as magnitude.

Consider an imaginary spherical surface of radius d cms. having an isolated pole of strength m at its centre (Fig. 104). Then since by definition $4\pi m$ lines of induction leave this pole, and can only terminate in an unlike pole (assumed very remote), all these lines must cross the imaginary surface. Since the pole is isolated, it may be assumed that the lines will be symmetrically distributed, giving a flux density of :—

$$B = \frac{4\pi m}{4\pi d^2} \text{ lines per square cm., i.e., } B = \frac{m}{d^2} = \mu \frac{m}{\mu d^2} = \mu H.$$

Thus in the particular case of an isolated pole, $B = \mu H$. This is true in the general case, since a complex field may be regarded as being built up of simple poles.

Hence flux, flux density, and field strength are connected by the relationship :—

$$\Phi = A.B = A\mu H \tag{45}$$

Note that in a vacuum ($\mu = 1$) B and H are vectors of equal magnitude ; they have always the same direction, and the lines of induction and lines of force may be considered to be identical. This is approximately true for air.

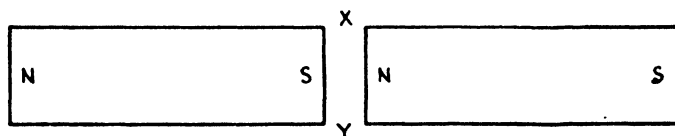


FIG. 105.—Bar magnet cut in half along XY .

Suppose that a bar magnet of pole strength m is divided by a cut XY (see Fig. 105) at right angles to its magnetic axis. The result will be two bar magnets of pole strength m . That is to say, the left-hand face of the gap will be a south pole and the right-hand face a north pole. The "intensity of magnetisation" I of the magnet in the region of this gap is defined as *the pole strength of either face divided by the area of the face*. I is a vector, since it is associated with direction, the imaginary cut having been made at right angles to the magnetic axis. The magnitude of I is measured in unit poles per square cm.

Behaviour of soft iron in a magnetic field

Consider a bar of soft iron of permeability μ placed in a uniform magnetic field of strength H gauss ; for simplicity, the bar is placed with its length in the direction of the field. It is observed in practice that the soft iron becomes magnetised, with north and south poles as shown in Fig. 106, the axis of the resultant magnet being in the direction of the magnetising field.

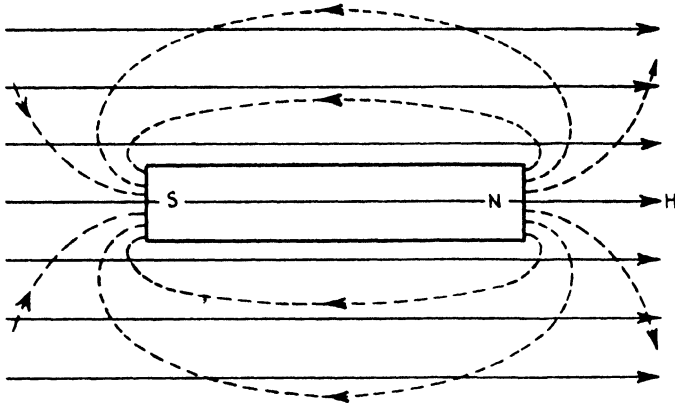


FIG. 106.—Soft iron bar in magnetic field.

The field in the vicinity of the soft iron may be predicted by considering lines of induction. The lines of induction due to the uniform field H may be represented by straight parallel lines, those due to the induced magnetism of the soft iron will be as shown dotted in Fig. 106.

The resultant lines of induction are as shown in Fig. 107, and may be found by considering the two fields of Fig. 106 superposed. Clearly at the ends of the magnet the induction due to the two component fields is additive, whilst at the sides they are in opposition. The soft iron is therefore seen to have the effect of concentrating the lines of induction so that they pass through the soft iron in preference to passing through the air.

Now suppose that a minute gap XY is cut at right angles to the magnetic axis and that the intensity of magnetisation in this region is I . Let the pole strength of the faces of the gap be m and the

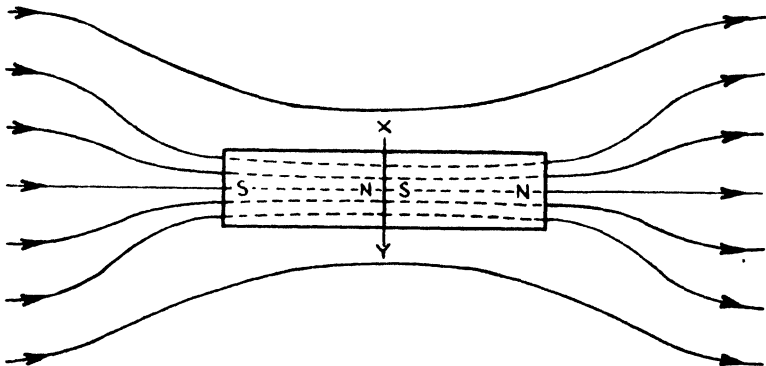


FIG. 107.—Magnetic field around soft iron bar.

area a sq. cms. Then by definition, $I = \frac{m}{a}$, but 4π lines of induction leave every unit north pole on the left side of the gap and enter every unit south pole on the right-hand side. The total flux in the gap due to the induced magnetism of the soft iron is $4\pi m$, and the flux density due to the induced magnetism is $\frac{4\pi m}{a} = 4\pi I$.

The total flux density in the gap, however, contains a component due to the original magnetising field H and numerically equal to H . Thus the total flux density is given by:—

$$B = H + 4\pi I \tag{46}$$

This result has been obtained in the special case of a bar of soft iron in a uniform magnetic field; it may, however, be extended to any shaped piece of iron in any type of field, since the iron may be regarded as made up of a large number of very small bars, for each of which the field may be regarded as uniform.

Dividing equation 46 by H :—

$$\frac{B}{H} = 1 + 4\pi \frac{I}{H}$$

i.e.,

$$\mu = 1 + 4\pi k \tag{47}$$

where k is defined as the "susceptibility" of the iron and gives a measure of the ease with which it may be magnetised by induction. Equation 47 shows that susceptibility and permeability are related.

Hysteresis

Fig. 108 shows the cycle followed by the magnetic flux (B) produced by a bar as the magnetising field (H) is varied. Starting

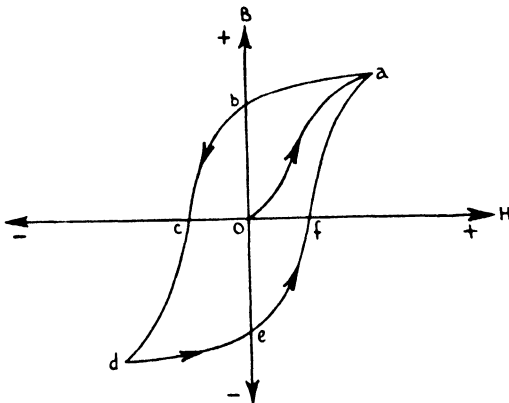


FIG. 108.—Hysteresis cycle.

with zero field and the iron demagnetised (point O), the field is gradually increased in the positive direction. At first the magnetisation is slow, then increases rapidly until, having almost reached

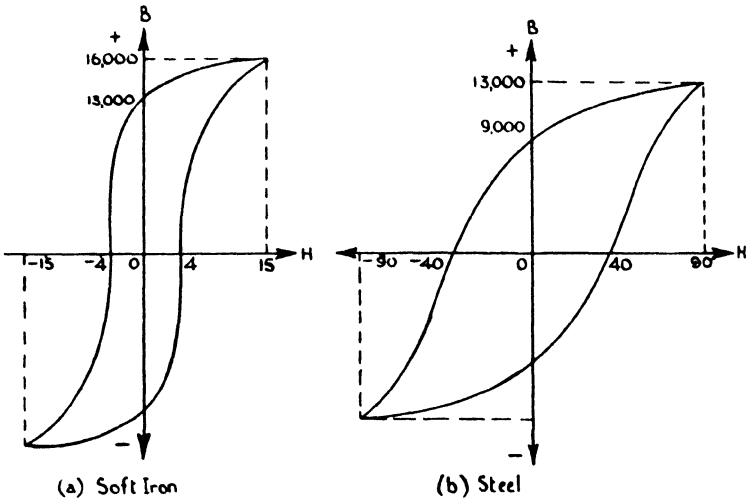


FIG. 109.—B-H or hysteresis curves for soft iron and steel.

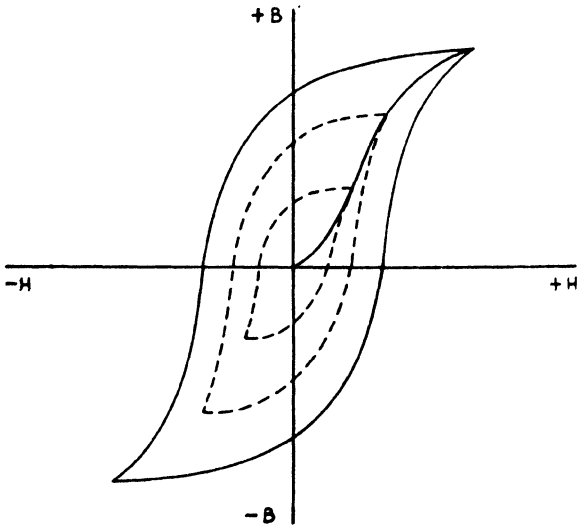


FIG. 110.—Effect of degree of magnetisation on hysteresis loop.

saturation point, the rate of change of flux drops.

The magnetising field is now reduced ; the flux, however, does not follow the original curve, but decreases far more slowly until, when the field is fully removed, the iron has an amount of residual magnetism represented by Ob . Reversing the magnetising field eventually removes all the magnetism (point c) and then remagnetises the iron in the reverse direction, until another saturation point is reached at d . Returning the field to zero and then increasing it in the original direction will complete the cycle. The outer curve ($a b c d e f a$) so traced will be followed for all future magnetising cycles.

It will be observed from the diagram that, after the initial magnetisation, the flux may be considered as lagging behind the field ; this phenomenon is termed " hysteresis ".

The distance Ob on the curve is a measure of the " retentivity " of the iron, while the distance Oc , *i.e.*, the field required to demagnetise, is a measure of the " coercivity ". These two qualities vary for different magnetic materials ; curves for soft iron and steel are shown in Fig. 109.

Fig. 110 shows hysteresis curves for a specimen using different degrees of magnetisation.

Hysteresis power loss

The hysteresis loop has a further quantitative interest since it can be shown, as below, that the energy expended in performing one cycle of magnetisation is represented by the area enclosed by the curve. Thus it can be seen that more work is done in the case of steel than in the case of soft iron. This is what would be expected from the known qualities of these two metals.

This work is of importance in such apparatus as the transformer, where repeated cycles are made, for the power loss caused by hysteresis is wasted as heat.

The most convenient method of producing the reversals of magnetic field is the use of the solenoid. The hysteresis loss in a sample of magnetic material placed at the centre of a solenoid will therefore be considered.

The field (H) at the centre of the solenoid is given by the formula:—

$$H = 4\pi Ni = \frac{4\pi T i}{l} \quad (\text{This result is verified on page 163.})$$

Where T is the total number of turns,

N is the number of turns per unit length,

i is the current in the solenoid (in EMU),

and l is the length (in cm.).

$$\therefore i = \frac{l}{4\pi T} \times H$$

The total flux Φ through the solenoid is $B \cdot A$, where A is the cross-sectional area, and the EMF induced (see p. 167) is:—

$$e = - T \times \frac{d(BA)}{dt} \text{ (in EMU)}$$

$$\therefore e = - T \times A \frac{dB}{dt}$$

The work done to complete the hysteresis cycle is done against this EMF,

$$\begin{aligned} \therefore \text{instantaneous power} &= - e \times i \\ &= \left(TA \cdot \frac{dB}{dt} \right) \times \left(\frac{l}{4\pi T} \cdot H \right) \\ &= \frac{Al}{4\pi} \times H \frac{dB}{dt} \end{aligned}$$

The work dW done in a small time dt is:—

$$dW = \frac{Al}{4\pi} \times H \frac{dB}{dt} \cdot dt$$

$$\text{Total work done } W \text{ is } W = \frac{Al}{4\pi} \times \int H dB \quad (48)$$

and it will be noticed that the integral included in the last equation is the area of the hysteresis loop. This is illustrated in Fig. 111.

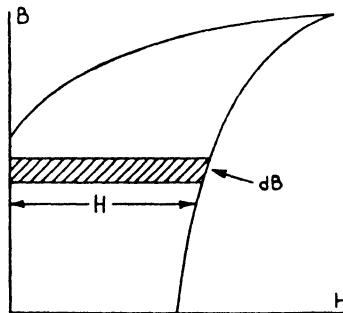


FIG. 111.—Calculation of power loss due to hysteresis.

Furthermore, Al is the volume of the sample,

$$\therefore \text{the work done per c.c.} = \frac{\text{Area of loop}}{4\pi} \quad (49)$$

If B and H are in the units of lines per sq. cm., this expression will give the work in ergs per c.c. per cycle.

Now, as already stated, this work done against hysteresis is, in practice, a loss of power and therefore of much importance. If the shape of the loop is known, then the area will give a value for this loss. This method is not suitable for use on machines and an

approximate method devised by Steinmetz is preferable. Steinmetz discovered that the hysteresis loss P_H per c.c. per cycle was very closely given by the formula $P_H = \eta B_{max}^{1.6}$ ergs, where η is a constant called the "hysteresis coefficient" and whose value depends upon the material, and B_{max} is the maximum flux density during the cycle. Hence the loss in a core of volume V c.c. over f cycles is given by :—

$$\begin{aligned} \text{Work done} &= \eta \cdot B_{max}^{1.6} \cdot V \cdot f \text{ ergs} \\ &= \eta \cdot V \cdot f \cdot B_{max}^{1.6} \times 10^{-7} \text{ joules.} \end{aligned}$$

If f cycles per second is the frequency, then this loss occurs each second, and :—

$$\text{Hysteresis power loss} = \eta \cdot V \cdot f \cdot B_{max}^{1.6} \times 10^{-7} \text{ watts} \quad (50)$$

Dia- and para-magnetism

The type of magnetism already dealt with, which is the most important, is called *ferromagnetism*. There are, however, two other classifications which deserve brief mention here. They are *diamagnetism* and *paramagnetism*.

If a material has a permeability of less than 1, it is said to be *diamagnetic*; if the permeability is greater than 1, the material is said to be *paramagnetic*. Examples of each are shown in Table VIII.

TABLE VIII
Diamagnetic and paramagnetic substances

Diamagnetic substances	Paramagnetic substances
Bismuth	Liquid Oxygen
Water	Air
Quartz	Palladium
Lead	Platinum
Copper	Aluminium
Hydrogen	Oxygen

The permeability of all these substances is very near unity, however; for example, μ for platinum is 1.000017, and for bismuth 0.99996. To the paramagnetic substances may be added a class of certain ions that show far stronger paramagnetism when in the form of salts or in solution. Thus some copper salts have values of μ around 1.75.

The ferromagnetic substances (nickel, cobalt and iron) have far higher permeabilities, from 250 up to many thousands, and may be considered as extreme cases of paramagnetism.

Fig. 112 shows $B-H$ and $\mu-H$ curves for a typical ferro-magnetic material. It will be seen that μ is by no means constant.

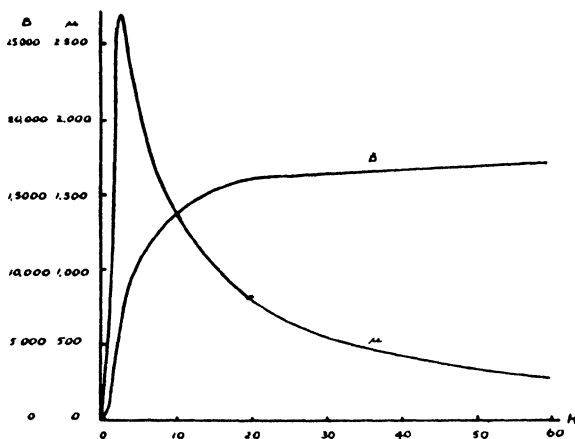


FIG. 112.—Typical $\mu-H$ and $B-H$ curves.

ELECTROMAGNETISM AND INDUCTANCE

The magnetic field due to a current in a straight wire is circular around the wire, and its direction is clockwise when viewed in the direction in which the current is flowing. The field strength at P

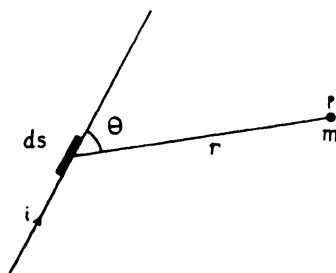


FIG. 113.—Field distant r from a wire carrying current

due to a short section of wire ds carrying a current i (Fig. 113) is given by Laplace's Law :—

$$H = \frac{i \cdot ds \cdot \sin \theta}{r^2} \text{ gauss} \quad (51)$$

Where i is the current,
 ds is the length of the segment of wire,
 θ is the angle between segment of wire and line to P ,
 r is the distance from segment to P .

Field at centre of coil

By Laplace's Law, the force on a unit pole at the centre of a coil in vacuo due to current i flowing through a small segment ds of that coil (see Fig. 114) is given by :—

$$f = \frac{id s}{r^2} \text{ dynes}$$

∴ The total force on the unit pole due to the whole coil is :—

$$\begin{aligned} F &= \Sigma f \\ &= \int_0^{2\pi r} \frac{id s}{r^2} \\ &= \frac{2\pi i}{r} \text{ dynes} \end{aligned}$$

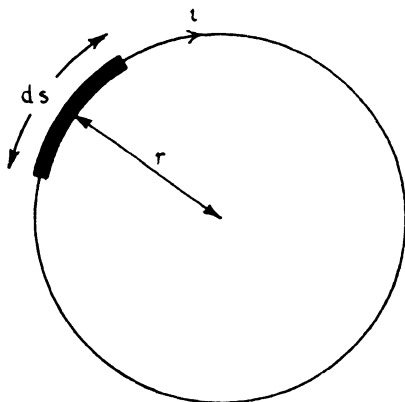


FIG. 114.—Field at centre of a coil.

Thus, if i is the current in EMU (defined on page 131), the field strength is :—

$$H = \frac{2\pi i}{r} \text{ gauss}$$

Since 1 EMU of current = 10 amps,

$$H = \frac{2\pi I}{10r} \text{ gauss} \quad (52)$$

where I is in amperes.

For a coil of T turns,

$$H = \frac{2\pi I T}{10r} \text{ gauss} \quad (53)$$

∴ The flux at the centre of the coil is therefore given by :—

$$\Phi = A \mu H = \frac{2\pi A \mu}{10r} \cdot T \cdot I \quad (54)$$

showing that the flux is directly proportional to the current.

Field at centre of solenoid

Consider the case of a solenoid. Referring to Fig. 115, P is a point on the axis of a long solenoid, and AB is one turn of that solenoid.

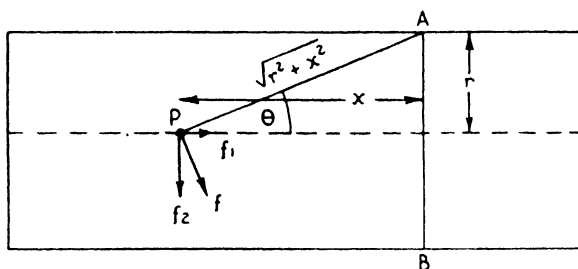


FIG. 115.—Force on unit pole at centre of solenoid, due to one turn.

Then the force f on a unit pole at P due to a segment ds of AB is:—

$$f = \frac{i ds}{r^2 + x^2}$$

But this force can be resolved into two components, f_1 and f_2 , in the directions shown, so that:—

$$f_1 = \frac{i \cdot ds}{r^2 + x^2} \sin \theta$$

$$f_2 = \frac{i \cdot ds}{r^2 + x^2} \cos \theta$$

To find the field at P due to the turn AB , the forces f must be summed over the complete turn. The components f_2 will clearly have a zero resultant, but:—

$$\begin{aligned} \Sigma f_1 &= \Sigma \frac{i \cdot ds}{r^2 + x^2} \sin \theta \\ &= \frac{2\pi r \cdot i \cdot \sin \theta}{r^2 + x^2} \text{ dynes} \end{aligned}$$

But
$$\sin \theta = \frac{r}{\sqrt{r^2 + x^2}}$$

hence
$$\Sigma f_1 = \frac{2\pi r \cdot i \cdot \sin \theta}{r^2 + x^2} = \frac{2\pi r^2 i}{(r^2 + x^2)^{\frac{3}{2}}} \text{ dynes} \quad (55)$$

This is the force at P due to one turn; the summation for the whole solenoid is now required.

The field strength at P due to a small segment of solenoid dx long is:—

$$h = \frac{2\pi r \cdot i \cdot \sin \theta}{r^2 + x^2} \cdot N dx \text{ gauss}$$

where N is number of turns per unit length, *i.e.*, per centimetre.

But $dx = AC = \frac{AE}{\sin \theta}$ as $d\theta \rightarrow 0$

$$= \frac{\sqrt{r^2 + x^2}}{\sin \theta} \cdot d\theta$$

$\therefore h = \frac{2\pi r \cdot i}{\sqrt{r^2 + x^2}} \cdot N d\theta$

$$= 2\pi Ni \cdot \sin \theta \cdot d\theta \text{ gauss} \tag{56}$$

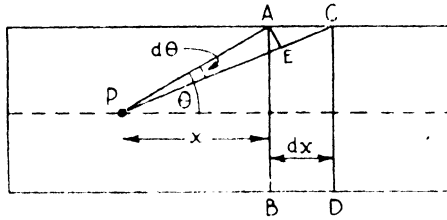


FIG. 116.—Force on unit pole at centre of solenoid, due to whole winding

If a long solenoid is considered, then the limits of θ are 0 and π , so that :—

Resultant field strength at P is :—

$$H = \int_0^\pi 2\pi Ni \times \sin \theta d\theta$$

$$= 2\pi Ni [-\cos \theta]_0^\pi$$

$$= 4\pi Ni \text{ gauss}$$

This is with i in EMU. With I in amperes, the field strength at the centre of the solenoid is

$$H = \frac{4\pi NI}{10} \text{ gauss.} \tag{57}$$

Note.—To obtain this result, it was necessary to assume a *long* solenoid, *i.e.*, long compared with its radius. If, in practice, this could not be assumed, then the limits of θ would need to be applied afresh to equation 56.

Force on a conductor

So far, the force on a magnetic pole due to a current has been considered ; but if the conductor exerts a force on the magnet, then the magnet must exert an equal but opposite force on the conductor. The direction of this force is shown in Fig. 117, and is given by *Fleming's left-hand rule* :—

Extend the thumb and first two fingers of the left hand mutually

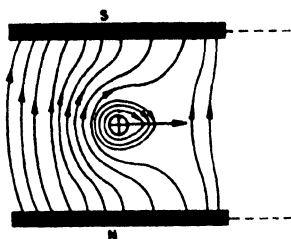


FIG. 117.—Force on current-carrying conductor in magnetic field.

at right angles. Place first finger in direction of field, second finger in direction of current; the thumb then gives the direction of the force acting on the conductor (see Fig. 118). The strength of this force can be calculated by applying Laplace's Law.

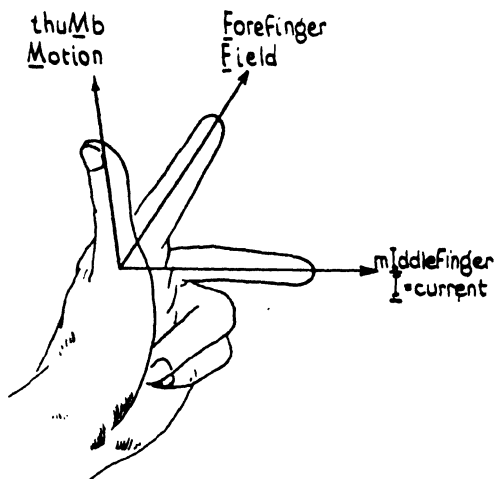


FIG. 118.—Fleming's left-hand rule.

Consider a magnetic pole of strength m , r cm. from a small segment of wire dl long, and carrying a current i EMU (see Fig. 119). The force on a pole m due to a current i is given by:—

$$F = \frac{m \cdot i \cdot dl}{r^2} \text{ dynes.}$$

The reaction on the conductor due to the magnetic pole must also be equal to $\frac{m \cdot i \cdot dl}{r^2}$ dynes.

But $\frac{m}{r^2}$ is the field strength at the conductor.

Therefore the force on a conductor of length dl in a field of strength H is $H \cdot i \cdot dl$ dynes.

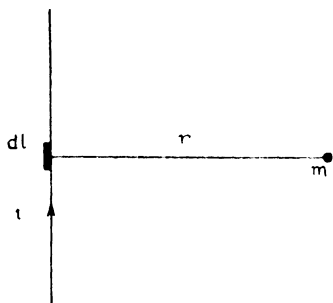


FIG. 119.—Pole distant r from current-carrying conductor.

If the field is uniform over the whole length l of the conductor, then :—

$$\text{Force} = \frac{H I l}{10} \text{ dynes} \quad (58)$$

where I is in amperes.

Force on a coil in a magnetic field

Now consider a rectangular coil suspended in a uniform field, and carrying a current of I amps.

With the field into the paper the forces acting on the sides of the rectangle are as shown.

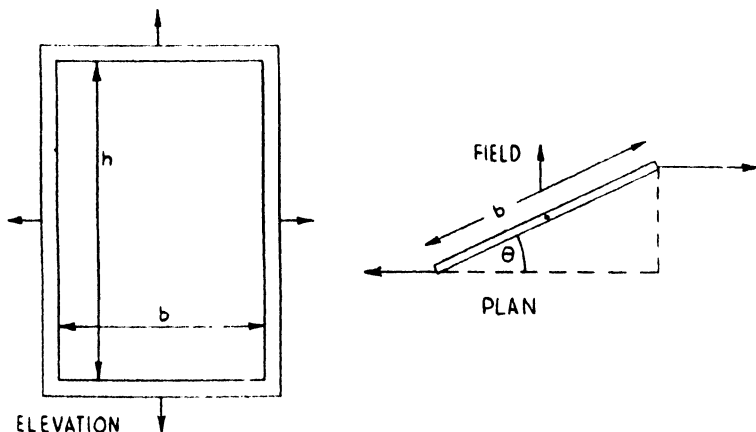


FIG. 120.—Rectangular coil in uniform magnetic field

If the coil is now rotated through an angle θ about its vertical axis the two horizontal forces will form a couple which will tend to turn it back to its original position.

$$\text{Force on one conductor} = \frac{HIh}{10} \text{ dynes.}$$

$$\therefore \text{Couple on coil} = \frac{HIh b \sin \theta}{10} \text{ dyne-cm.}$$

$$\text{But} \quad hb = \text{area, } A, \text{ of coil}$$

$$\therefore \text{Couple on coil of } T \text{ turns} = \frac{HIAT}{10} \sin \theta \text{ dyne-cm.} \quad (59)$$

Electromagnetic induction

Two convenient laws state the theory of electromagnetic induction very concisely:—

Faraday's Law.—When the magnetic flux through a circuit is changing, an induced EMF is set up, and its magnitude is proportional to the rate of change of flux.

Lenz's Law.—The EMF induced in any circuit is always in such a direction that its effect tends to oppose the motion or change producing it.

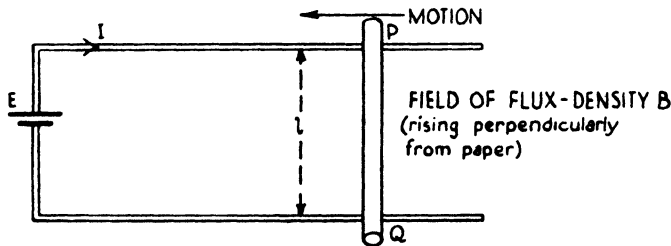


FIG. 121.—Bar moving in magnetic field.

Consider the circuit shown in Fig. 121, composed of heavy-gauge conductors of negligible resistance, with a magnetic field having a flux-density B acting at right angles to the page.

Due to the force produced by the magnetic flux and the current i EMU through PQ , the bar PQ will be pulled along the parallel bars towards the left.

Let it move a distance dx in time dt .

Then the rate of change of flux-linkages is $B \cdot l \cdot \frac{dx}{dt}$

Now in moving the conductor, work is done.

$$\text{The force} = Bil \text{ dynes}$$

$$\therefore \text{the work done} = Bil \cdot dx \text{ ergs.}$$

This work is done by energy from the cell necessary to overcome the back EMF caused by motion.

Let the back EMF = e EMU

Then the work done = $-ei dt$ ergs

$\therefore Bil dx = -ei dt$

or $e = -Bl \cdot \frac{dx}{dt} = -\frac{d\Phi}{dt}$ EMU (60)

\therefore the induced EMF in EMU = - Rate of change of flux-linkages.

Hence the induced EMF in volts = - Rate of change of flux-linkages $\times 10^{-8}$.

Fleming's right-hand rule

The direction of the induced EMF in such a case may be deduced by Lenz's Law. A convenient method of determining the direction of motion is given by Fleming's right-hand rule :—

Extend the thumb and first two fingers of the right hand mutually at right angles. Place first finger in direction of field, thumb in direction of motion; the second finger will then give the direction of the induced EMF, and of the resulting current in a closed circuit (see Fig. 122).

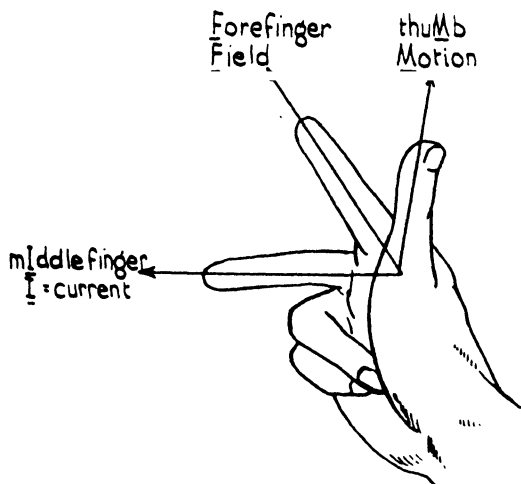


FIG. 122.—Fleming's right-hand rule.

Rotation of a coil in a uniform field

Consider a rectangular coil rotating at angular velocity ω radians per second, as shown in Fig. 123.

Then the velocity of one side of the coil is $\omega \frac{b}{2}$ as shown.

Velocity at right angles to field = $\omega \frac{b}{2} \sin \theta$ where $\theta = \omega t$, i.e. the angle turned through after time t .

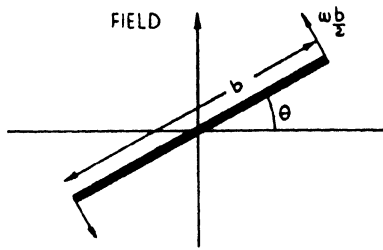


FIG. 123.—Coil rotating in uniform magnetic field.

$$\begin{aligned} \text{Rate of change of flux-linkages} &= -2 \left(\omega \frac{b}{2} \sin \theta \right) hB \\ &= -\omega BA \sin \theta \end{aligned}$$

where h is the height of the coil

B is the flux density

A is the coil area $= bh$.

Induced EMF in 1 turn $= -$ Rate of change of flux-linkages $\times 10^{-8}$ volts

$$= +\omega BA \sin \theta \cdot 10^{-8} \text{ volts.}$$

Induced EMF in coil of T turns

$$= \omega BAT \sin \theta \cdot 10^{-8} \text{ volts} \quad (61)$$

Thus it is seen that the EMF varies with $\sin \theta$. It will be zero, therefore, when $\theta = 0$, *i.e.* when the coil is at right angles to the field; and a maximum when θ is 90° , *i.e.* when the coil is parallel to the field. The value of the EMF at the different positions is shown in Fig. 124 by a sine wave of amplitude $\omega BAT \cdot 10^{-8}$ volts.

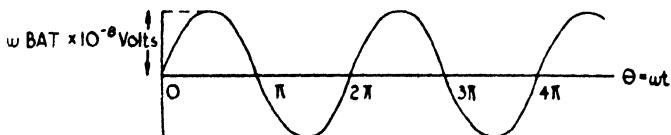


FIG. 124.—Sinusoidal EMF induced into coil of Fig. 123.

The instantaneous value of the EMF is seen from equation 61 to be $e = \omega BAT \sin \omega t \cdot 10^{-8}$ volts. This is of the form:—

$$e = E_{\max} \sin \omega t \quad (62)$$

where

$$E_{\max} = \omega BAT \cdot 10^{-8} \text{ volts.} \quad (63)$$

The coil described above is the simplest form of “alternating current” generator, and equation 62 will be seen in Chapter 4 to be of fundamental importance in the study of AC.

Inductance

In the preceding sections induced EMFs due to change of flux in a coil have been considered. In each case the flux considered was due to some external field. When a current flows through a coil, however, it sets up a field of its own, and any change in this current alters this field. So without external aid a changing flux is obtained in the coil, and an induced EMF is therefore set up in such a direction as to tend to maintain the flux at its original density. This is termed "self-induction".

A coil has a self-inductance (L) of 1 henry when a change of current of 1 ampere per second induces a back EMF of 1 volt. Hence it follows that the back EMF is:—

$$e \text{ (in volts)} = -L \text{ (in henries)} \times \frac{dI}{dt} \text{ (in amps/sec.)} \quad (64)$$

The negative sign is introduced because, when $\frac{dI}{dt}$ is positive, *i.e.*, when the current is increasing, the induced EMF e will be opposing the applied EMF.

$$\text{From (64):} \quad e = -L \frac{dI}{dt}$$

$$\text{From (60):} \quad e = -T \frac{d\Phi}{dt} 10^{-8}$$

$$\therefore \quad L = T \frac{d\Phi}{dI} 10^{-8}$$

$$\frac{d\Phi}{dI} = \frac{2\pi A\mu}{10r} \cdot T = \frac{\Phi}{I} \quad (\text{from eq. 54})$$

$$\therefore \quad L = \frac{\Phi T}{I} \times 10^{-8} \text{ henries} \quad (65)$$

i.e., self-inductance = flux-turns per ampere $\times 10^{-8}$.

Again, the field in the centre of a long solenoid is given by:—

$$H = \frac{4\pi TI}{10l} \text{ gauss}$$

$$\therefore \quad \text{Flux } \Phi = \frac{4\pi TI \mu A}{10l} \text{ lines}$$

$$\text{and} \quad L = \frac{4\pi T^2 \mu A}{10l} \times 10^{-8} \text{ henries} \quad (66)$$

This last expression shows that the inductance of a long solenoid can be calculated from the purely physical dimensions:—

Number of turns,	T
Length,	l
Permeability of core material,	μ
and Cross-sectional area,	A

Mutual inductance

In the case of self-induction, the change of flux was caused by current variation in the same coil. This change of flux may

however, be caused by current variations in a second coil that is linked with the first magnetically. The induced EMF is then due to "mutual induction".

Two coils have a mutual inductance (M) of 1 henry when a change of 1 ampere per second in one produces an EMF of 1 volt in the other. Hence it follows that the induced EMF is:—

$$e_2 \text{ (in volts)} = M \text{ (in henries)} \times \frac{dI_1}{dt} \text{ (amps/sec.)}.$$

As before, it can be shown that:—

Mutual inductance = Flux-turns in secondary per ampere in primary $\times 10^{-8}$

$$\text{and} \quad M = \frac{4\pi T_1 T_2 \mu A}{10l} \times 10^{-8} \text{ henries} \quad (67)$$

For this to be true, however, the two coils must be fully linked magnetically. Otherwise the field, $\frac{4\pi TI}{10l}$, due to the primary, may not link with the whole of the secondary, and the derivation of the formula would be false.

Inductance of two parallel wires

The inductance of two parallel wires, radius a , distance between centres c , is given by:—

$$L = 0.1609 + 1.481 \log_{10} \frac{c-a}{a} \text{ mH per mile loop} \quad (68)$$

Construction of inductances

For air-cored inductances, formulae can be used to determine the number of turns T required, but it is usually simpler in practice to use trial and error methods. Turns can be added or removed to alter the inductance L , remembering that L varies as T^2 . The same methods apply to iron-cored inductances, although in this case the inductance can also be varied by adjusting the air-gap in the core.

Example.—Using a former $\frac{1}{2}$ inch square, length of winding $\frac{1}{2}$ inch, find how many turns are required for an inductance of 1 mH (air cored).

$$L = \frac{4\pi T^2 A}{10^9 \cdot l} \text{ henries}$$

where l is the length in cm.

$$= 2.54 \frac{4\pi T^2 A'}{10^6 \cdot l'} \text{ mH}$$

where l' is the length in ins., and A' is the area in sq. ins.

$$\text{In this case,} \quad A' = \frac{1}{4}, \quad l' = \frac{1}{2}, \quad L = 1.$$

$$\text{Hence,} \quad 1 = \frac{2.54 \times 4\pi \times T^2 \times \frac{1}{4}}{10^6 \cdot \frac{1}{2}}$$

$$\therefore T^2 = \frac{10^6 \cdot 4}{2 \times 2 \cdot 54 \times 4\pi} = 251^2$$

251 turns are therefore required.

Such an inductance was constructed and found to have an inductance of 1·002 mH.

Circuits containing inductance and resistance

When the key is depressed in a circuit as shown in Fig. 125, the battery tries to drive a current of strength $\frac{E}{R}$ through the circuit, but owing to the inductance L the current is initially

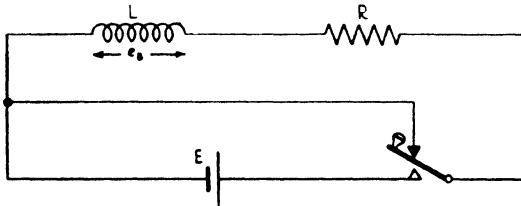


FIG. 125.—Application of EMF to inductance and resistance in series.

zero and slowly builds up to this value. The growth of current is comparable with the charging of a condenser discussed earlier.

Let the rate of change of current be $\frac{di}{dt}$

The back EMF $e_B = -L \frac{di}{dt}$

But $i = \frac{E + e_B}{R}$

$\therefore e_B = -E + iR$

Equating the two values of e_B :—

$$-E + iR = -L \frac{di}{dt}$$

$\therefore \frac{di}{dt} + \frac{iR}{L} = \frac{E}{L}$

Multiply by $e^{\frac{Rt}{L}}$:—

$$\frac{di}{dt} \cdot e^{\frac{Rt}{L}} + i \cdot \frac{R}{L} \cdot e^{\frac{Rt}{L}} = \frac{E}{L} \cdot e^{\frac{Rt}{L}}$$

$$\therefore \frac{d}{dt} [i \cdot e^{\frac{Rt}{L}}] = \frac{E}{L} \cdot e^{\frac{Rt}{L}}$$

$$\therefore i \cdot e^{\frac{Rt}{L}} = \frac{E}{R} \cdot e^{\frac{Rt}{L}} + K$$

(where K is a constant)

$$\therefore i = \frac{E}{R} + K \cdot e^{-\frac{Rt}{L}}$$

When $t = 0$, $i = 0$, hence K may be determined :—

$$K = -\frac{E}{R}$$

$$\therefore i = \frac{E}{R} \left(1 - e^{-\frac{Rt}{L}}\right) \quad (69)$$

This, then, is the equation for the graph shown in Fig. 126.

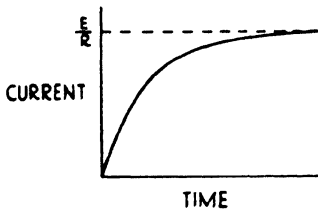


FIG. 126.—Graph showing growth of current in L-R circuit.

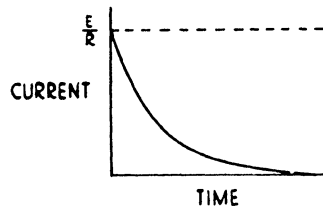


FIG. 127.—Graph showing decay of current in L-R circuit.

If the key in the above circuit is now released, the current tends to cease, but it is partially maintained by the back EMF, so that it dies away exponentially.

$$\text{Again } e_b = -L \frac{di}{dt}$$

$$\text{But } i = \frac{e_b}{R}$$

$$\therefore e_b = iR$$

$$\therefore iR = -L \frac{di}{dt}$$

$$\therefore \frac{di}{i} = -\frac{R}{L} dt$$

Integrating :—

$$\log_e i = -\frac{Rt}{L} + K$$

$$\begin{aligned} \text{or} \quad & i = Ke^{-\frac{R}{L}t} \\ \text{When } t = 0, \quad & i = \frac{E}{R} \\ \therefore \quad & K = \frac{E}{R} \\ \text{Thus} \quad & i = \frac{E}{R} \cdot e^{-\frac{R}{L}t} \end{aligned} \quad (70)$$

and this is the equation for the graph of Fig. 127 showing the gradual decrease of current.

Time constant

The time-constant of a circuit containing inductance and resistance is equal to $\frac{L}{R}$. If L is expressed in henries and R in ohms, $\frac{L}{R}$ is equal to the time in seconds for the current to reach 63 per cent. of its final value when the circuit is closed; or for the current to fall to 37 per cent. of its initial value when the circuit is broken. (Compare this with the time-constant CR for a circuit containing inductance and capacity, CR being the time for the *charge* on the condenser to reach 63 per cent. of its final value, or fall to 37 per cent. of its maximum value.)

DC METERS

Meters may be roughly divided into two classes :—

- (1) Voltmeters,
- (2) Ammeters.

A voltmeter is always placed in parallel with the circuit, being connected to the two points between which the potential difference is to be measured. Therefore, to prevent disturbance of current distribution in the circuit, the voltmeter must have a high resistance. Ammeters, on the other hand, are placed in series with the circuit, and, for a similar reason, must have a low resistance.

Most meters are designed as sensitive milliammeters, and adapted as voltmeters and ammeters by the inclusion of series resistances or parallel shunts.

Moving coil meters

The principle underlying the operation of this type of meter is that expounded in the last section. A coil is suspended in a strong magnetic field, and, when a current I flows, it is turned by a couple of strength

$$\frac{HIA l \sin \theta}{10} \text{ dyne-cm.}$$

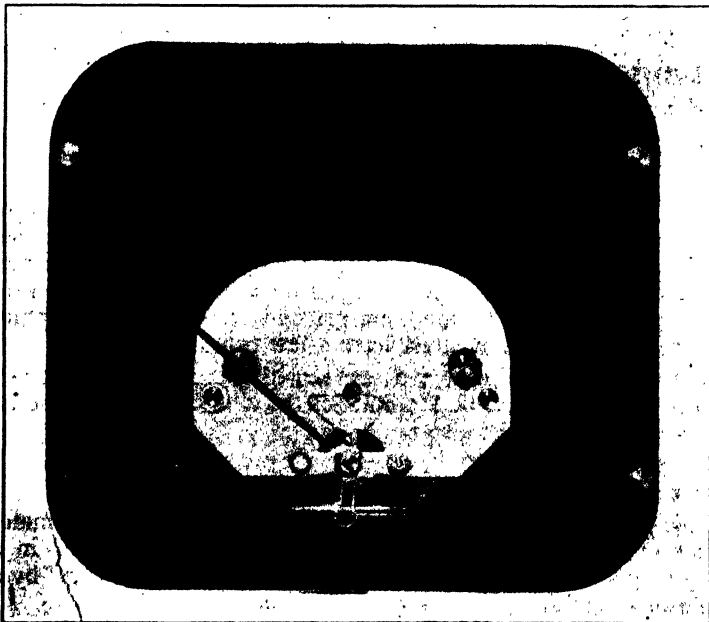
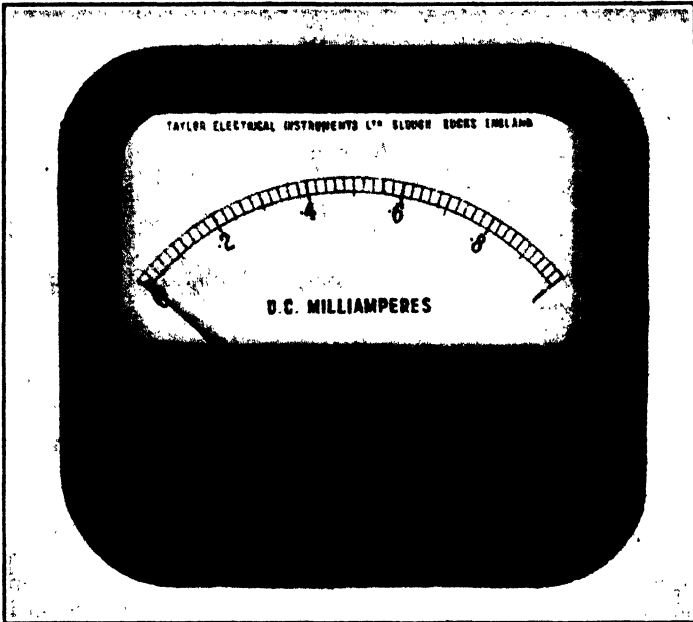


PLATE 5.—Moving coil meter.

The field is supplied by a large permanent magnet as shown in Fig. 128, and, by placing a soft iron cylinder between the pole pieces, which are themselves shaped, this field is made radial. This means that whatever the position of the coil, $\sin \theta = 1$, and the turning couple is always constant and of value equal to $\frac{HIA\tau}{10}$ dyne-cm.

A restoring couple is supplied by a phosphor-bronze suspension or a spring. The latter is the more common in the normal portable

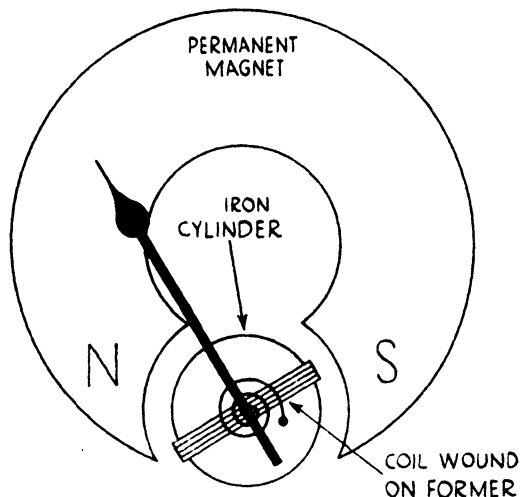


FIG. 128.—Moving coil meter.

type of meter. This restoring couple is directly proportional to the deflection, *i.e.* $= k\theta$, where k is a constant. Therefore at equilibrium position

$$k\theta = \frac{HIA\tau}{10}$$

$$\therefore I = \frac{10 \cdot k}{HAT} \theta$$

$$= K \cdot \theta$$

The deflection is thus proportional to the current, so giving a linear scale.

The coil gains momentum as it swings towards this position and, to prevent this momentum causing unwanted oscillation about the equilibrium point, "damping" is introduced by winding the coil on a metal former. As the coil rotates, eddy currents are induced into this former, using up the kinetic energy of the system. When the coil reaches its equilibrium position it has no energy to swing further, and the turning and restoring couples are balanced, so that efficient damping is obtained.

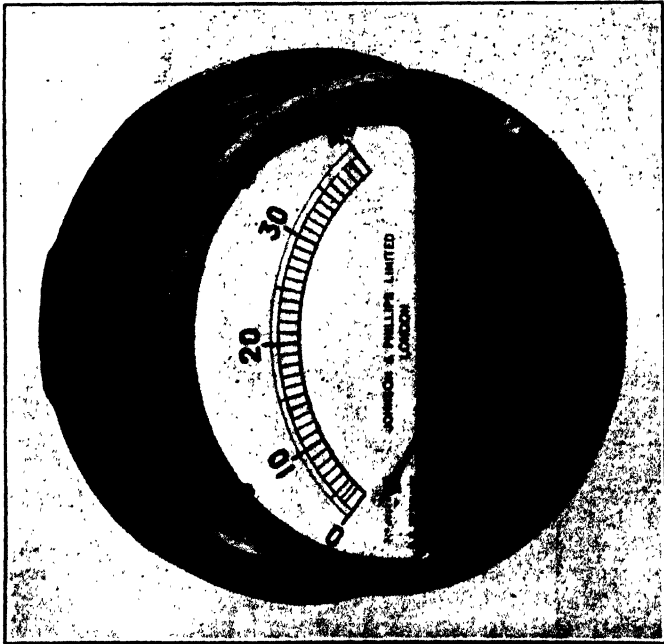
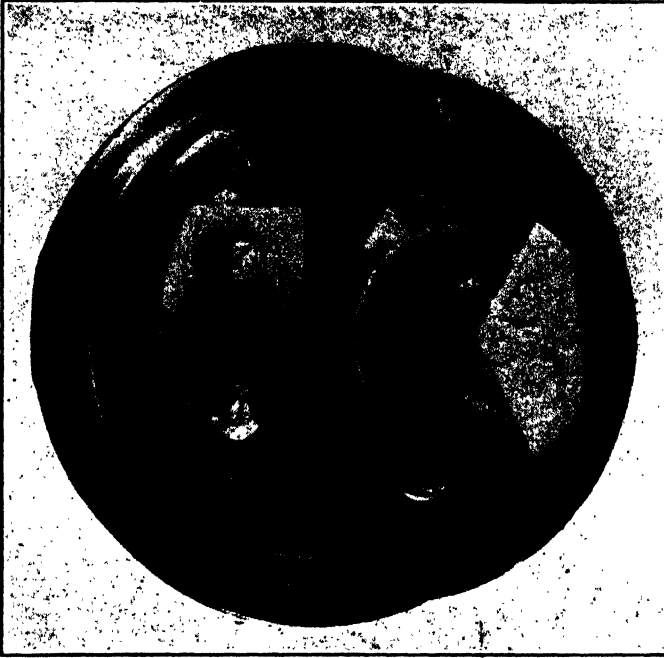


PLATE 6.—Moving iron meter—repulsion type.

"Ballistic" meters discard this damping and the coil is wound on a light non-metallic former. They are used to measure discharge or similar short-duration currents, when the initial swing of the meter is proportional to the quantity of electricity passed.

The moving coil milliammeter may be used as a voltmeter when a series resistance is connected. For use as an ammeter a shunt must be connected in parallel with the meter.

The passage of current through the coil raises its temperature and alters its resistance. It is normal therefore to fit a "swamp" resistance in series with the coil. The resistance being of a metal having a low temperature coefficient, such as manganin, varies little, and thus reduces the effect of temperature on the meter as a whole.

In the case of an ammeter, the meter and swamp are connected in series, and the shunt is connected in parallel across both.

Moving iron meters

This type of meter is usually made in one of two designs; the first is illustrated in Fig. 129. The current to be measured is passed through the coil and sets up a magnetic field. This magnetises the soft iron and draws it into the centre of the coil.

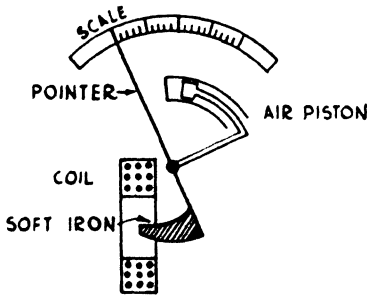


FIG. 129.—Attraction type moving iron meter.

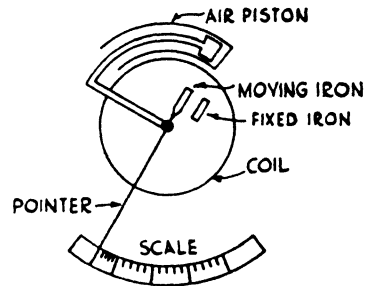


FIG. 130.—Repulsion type moving iron meter.

The force acting on the iron is dependent on the magnetism of the iron and on the field of the coil, both of which are proportional to the current, so that it is not directly proportional to the current but is proportional to the square of the current. Therefore, unlike that of the moving coil meter, the scale is not linear, but an approximately linear scale can be produced by careful shaping of the iron.

The restoring couple is supplied by a spring or sometimes by gravity. The damping is almost invariably obtained by the use of an air piston or "dashpot".

The second type, illustrated in Fig. 130, is often known as the "repulsion" type meter.

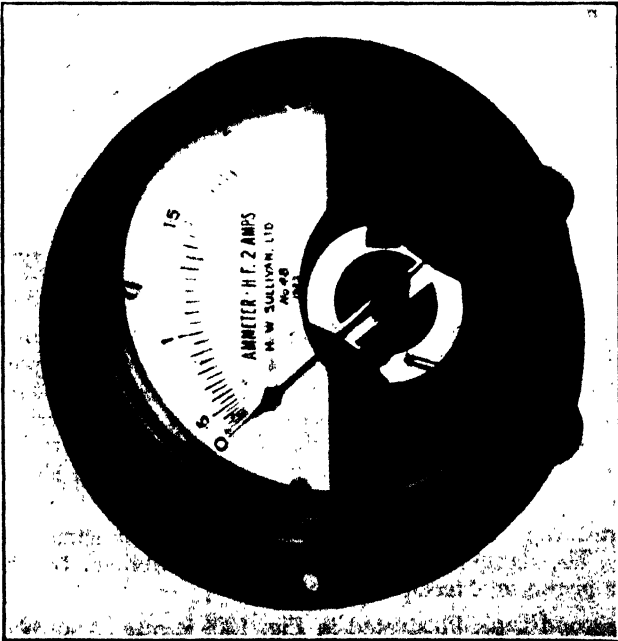
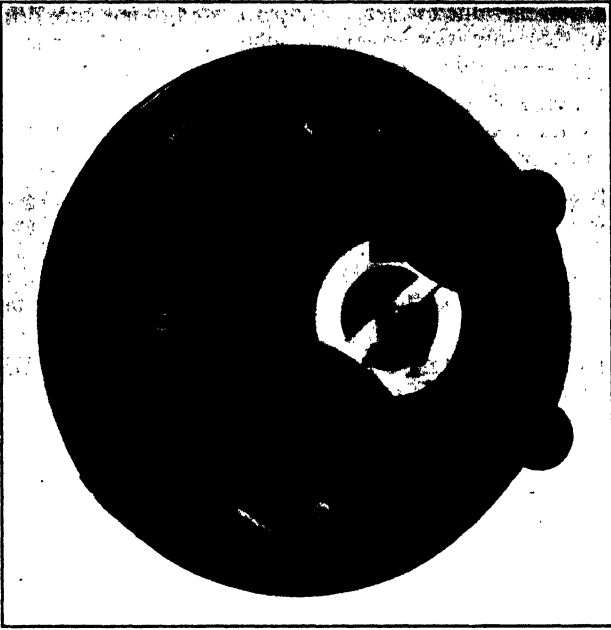


PLATE 7.—Hot-wire meter.

Two iron bars are situated axially in a short solenoid. One is fixed, while the other is movable and attached to a pivot that also carries the pointer. When current flows through the coil the bars are equally magnetised and repel each other. The repulsion gives a deflection on the scale which is calibrated for direct reading. The repulsion is proportional to the product of the pole strengths of each magnet and therefore to I^2 , giving again a non-linear scale.

Similar restoring and damping systems are used as in the previous type.

By varying the type of wire used in the coil the resistance of the meter can be varied, and so both voltmeters and ammeters can be made without need for any shunt or swamp resistances.

Both types of moving iron meters are susceptible to stray magnetic fields, and, since these would naturally cause deflection, good screening is necessary. Hysteresis also affects the readings, in that a higher reading will be given for decreasing currents than for increasing currents, while the retentivity will give a small deflection when no current is flowing. These defects are now reduced by the use of the alloy "mumetal", which has a hysteresis loss small enough to be neglected. By these means the moving iron meter can be made very accurate; and, owing to its robustness, it is more suitable for certain purposes than the moving coil meter. A further advantage is that the deflection is proportional to the square of the current, and this fact enables it to be used for AC as well as DC (*see* Chapter 6).

Hot-wire meters

Passage of current through a resistance wire causes generation of heat, and the wire expands with the resultant temperature rise.

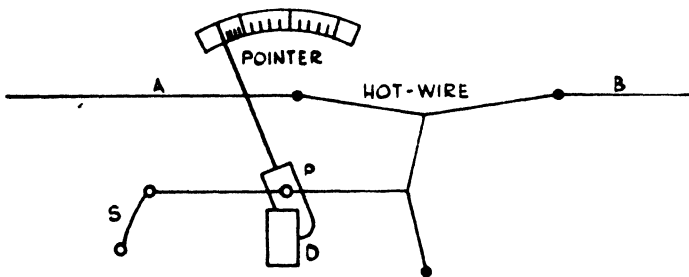


FIG. 131.—Hot-wire meter.

It can be shown that the expansion is proportional to the square of the current flowing, and this is the principle adopted in hot-wire meters, though due to practical factors the increase in length is not exactly proportional to I^2 . Each meter must therefore be individually calibrated.

Fig. 131 shows the essential features. The current to be measured passes through the hot-wire from *A* to *B*. The hot-wire

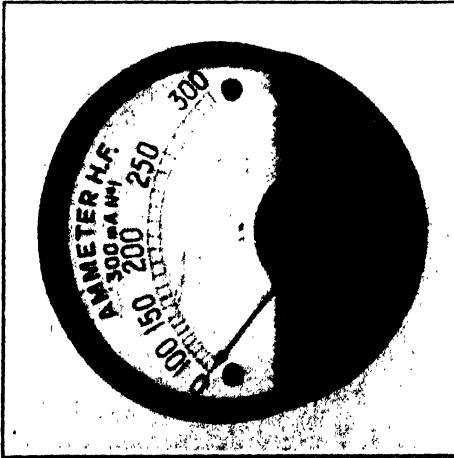
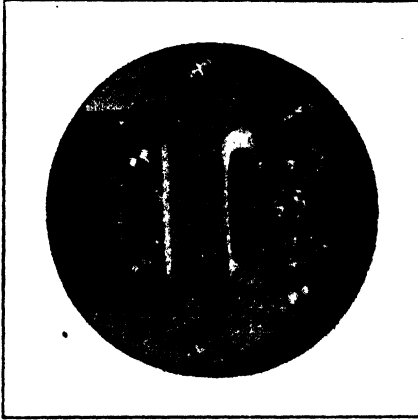


PLATE 8.—Thermo-couple meter.

is usually made of manganin, since the resistance of this metal varies little over the temperature range employed. The resultant sag in the hot-wire is taken up by tension applied from a phosphor-bronze spring *S*, through a silk thread that passes round pulley *P* and is attached to the top of *S*. Movement of the silk thread, due to change in the length of the hot-wire, rotates the pulley, and the scale is calibrated to read the current directly.

Damping is provided by a light aluminium plate, attached to the pointer, passing between the poles of a permanent magnet *D*. Contraction of the wire should return the meter to zero after use, but in practice this is not always the case and adjustments to the hot-wire have to be made. This fact, together with its high power consumption, its mechanical frailness, and its liability to damage from overload, renders its use unsuitable in many cases, but, like the moving iron meter, it has the advantage that it can be used for both DC and AC measurements.

Thermo-couple meters

The basic fact used in the construction of these meters was discovered as far back as 1806 and is known after the discoverer as the Seebeck effect.

If a circuit comprised of different metals is at one temperature throughout, there is no resultant EMF. If, however, one junction between two dissimilar metals is at a different temperature from

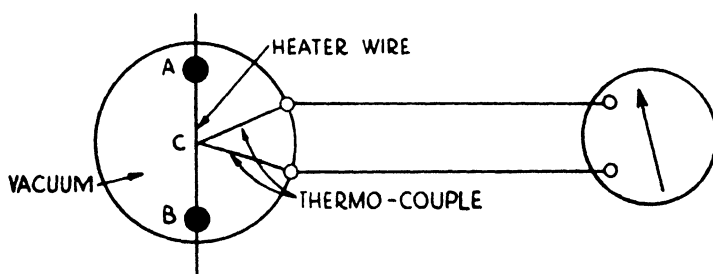


FIG. 132.—Thermo-couple meter.

the remainder of the circuit, an EMF is set up and a current will flow; this EMF is known as a "thermo-electric" EMF. This phenomenon can easily be demonstrated, using two dissimilar metals such as copper and iron, but the usual "thermo-electric couple", as it is called, used in such meters consists of bismuth and antimony, as this combination gives a large EMF, although numerous other combinations may be used.

As the temperature of the thermo-couple is increased, the EMF at first increases; but, after a certain rise in temperature, it ceases to increase and, finally, decreases until it reaches zero and starts to build up again with reversed polarity. It follows that only the

first portion (that of EMF increasing with temperature) can be used for thermo-electric meters.

The construction of the meter is shown diagrammatically in Fig. 132.

The current to be measured passes between *A* and *B*, raising the temperature of the heater wire. Attached to the centre of *AB* is the thermo-junction and, as the temperature of this junction increases, so the EMF across the couple rises; the resultant current is passed through an ordinary DC meter, usually of moving coil type. The meter is calibrated to read directly the current flowing in the external circuit of which the heater wire *AB* forms a part.

This type of meter is suitable for both AC and DC. It is so built that the couple is neatly encased in the ammeter case, and it often resembles an ordinary moving coil meter, though, as it depends for operation on heating effect, its scale is non-linear.

Shunt and series resistances

If a meter has been designed as a sensitive milliammeter, the use of shunts (in parallel) and series resistances is essential if the meter is to be used as an ammeter or voltmeter.

The principle is as follows: if a meter reads up to 100 mA and it is required to use it for measurements up to 1 ampere, then the inference is that, when 1 ampere passes through the circuit, only 100 mA must pass through the meter. This will give full-scale deflection, and recalibration will enable direct reading of the currents to the higher limit. Only 100 mA pass through the meter, therefore 900 mA must pass through shunt. Thus, the required shunt = $\frac{1}{9}G$, where *G* is the resistance of the meter.

The principle of voltmeter and series resistance is similar, and is illustrated in the following example:—

Q. A meter of resistance 40 ohms gives a deflection of one scale division for a current of 1 milliampere. Find the series resistance required to change it into a voltmeter reading 1 volt per scale division.

$$A. \text{ Voltage across meter for 1 scale division deflection} = \frac{40}{1,000} \text{ V.}$$

But this must be the voltage across the meter when 1 volt is applied across the meter and series resistance,

$$\begin{aligned} \therefore \text{ Series resistance} &= 40 \times \frac{\text{voltage across series resistance}}{\text{voltage across meter}} \text{ ohms} \\ &= 40 \times \frac{1,000 - 40}{40} \text{ ohms} = 960 \text{ ohms.} \end{aligned}$$

Some meters are provided with a set of shunts and series resistances so that their ranges and uses can be varied. As an

example, consider the meter shown in Fig. 133*a*, having an internal resistance of $200\ \Omega$, and giving full-scale deflection when the current flowing through it is $0.75\ \text{mA}$; this corresponds to a voltage of $150\ \text{mV}$ across the meter.

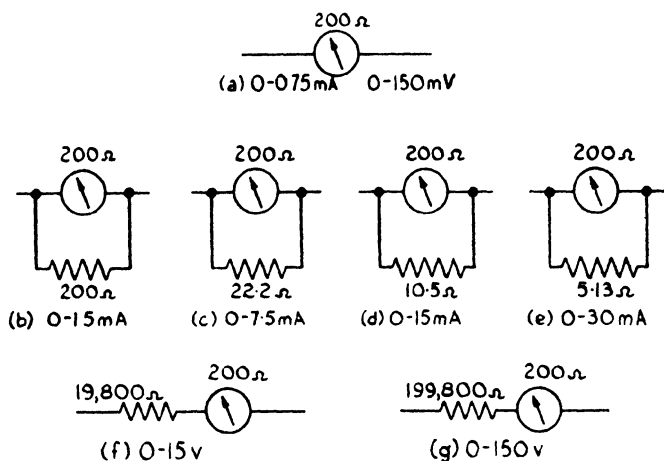


FIG. 133.—Multi-purpose meter.

The range may be extended as follows :—

- 0—1.5 mA using a shunt of $200\ \Omega$
- 0—7.5 mA using a shunt of $22.2\ \Omega$
- 0—15 mA using a shunt of $10.5\ \Omega$
- 0—30 mA using a shunt of $5.13\ \Omega$
- 0—15 V using a series resistance of $19,800\ \Omega$
- 0—150 V using a series resistance of $199,800\ \Omega$.

CIRCUITS CONTAINING INDUCTANCE, CAPACITY AND RESISTANCE


It is interesting to consider the behaviour of the current in the circuit of Fig. 134 after the key is closed. It will be seen that there are three distinct cases, depending on the relative values of R , L and C . A differential equation is obtained by writing down an equation for the current i seconds after closing the key.

The voltage across C is $\frac{q}{C}$, and has polarity as shown.

At $t=0$, $q=0$, since the condenser is initially discharged, and $i=0$.

The voltage across L is $-L\frac{di}{dt}$, measured in the direction of i , and therefore Kirchhoff's Law gives :—

$$E - L\frac{di}{dt} - \frac{q}{C} = iR \quad (71)$$

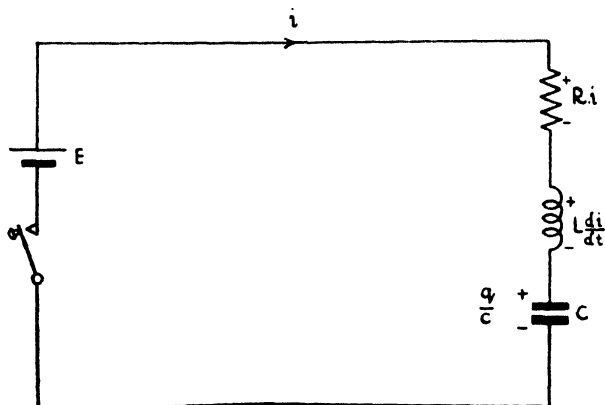FIG. 134.—Application of F.M.F. to R , L and C in series.

To eliminate the variable q from the equation, differentiate both sides with respect to t and put $\frac{dq}{dt} = i$, giving:—

$$-L \frac{d^2 i}{dt^2} - \frac{i}{C} = R \frac{di}{dt}$$

or

$$\frac{d^2 i}{dt^2} + \frac{R di}{L dt} + \frac{i}{LC} = 0 \quad (72)$$

The solution of this equation is:—

$$i = Ae^{m_1 t} + Be^{m_2 t},$$

where m_1 and m_2 are the roots of the equation:—

$$m^2 + m \frac{R}{L} + \frac{1}{LC} = 0$$

The roots are:—

$$m = -\frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}}$$

That is, $m = -a \pm b$, where $a = \frac{R}{2L}$ and $b = \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}}$

Hence, the general solution to equation 72 is:—

$$i = Ae^{(-a+b)t} + Be^{(-a-b)t} \quad (73)$$

Case 1.—

$$\frac{R^2}{4L^2} > \frac{1}{LC} \quad \therefore b \text{ is real.}$$

Equation 73 gives:—

$$\begin{aligned} i &= e^{-at} (Ae^{bt} + Be^{-bt}) \\ &= e^{-at} (F \cosh bt + G \sinh bt) \end{aligned} \quad (74)$$

To determine the value of F and G , put $t = 0$.

This must give $i = 0$, hence $F = 0$.

Also, from equation 71 :—

$$\frac{di}{dt} = \frac{E}{L} \text{ when } t = 0$$

Differentiating equation 74 with $t = 0$ and $F = 0$:

$$\frac{E}{L} = \left(\frac{di}{dt} \right)_{t=0} = bG$$

$$\therefore G = \frac{E}{bL}$$

Equation 74 now becomes :—

$$i = \frac{E}{bL} e^{-at} \sinh bt \quad (75)$$

The way in which i varies with t is shown in Fig. 135

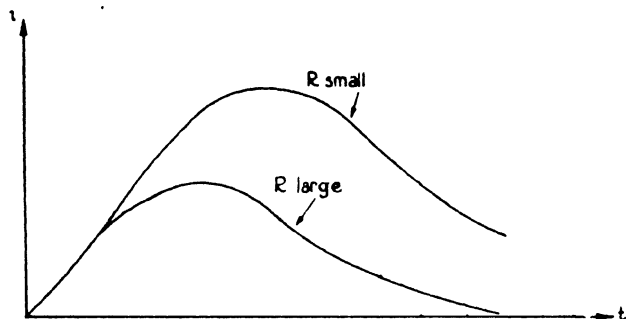


FIG. 135.—Current in circuit of Fig. 134 when $\frac{R^2}{4L^2} > \frac{1}{LC}$.

Case 2.—

$$\frac{R^2}{4L^2} = \frac{1}{LC} \quad \therefore b = 0$$

The solution of equation 72 in this case is :—

$$i = (A + Bt) e^{-at}$$

When $t = 0, i = 0, \therefore A = 0$

Hence $i = Bte^{-at}$

As before, when

$$t = 0,$$

$$\frac{di}{dt} = \frac{E}{L}$$

$$\therefore B = \frac{E}{L}$$

Thus,

$$i = \frac{Et}{L} e^{-at} \quad (76)$$

This curve is of similar shape to those in Fig. 135.

Case 3.—

$$\frac{R^2}{4L^2} < \frac{1}{LC} \quad \therefore b \text{ is imaginary}$$

$$\text{Let } b = j\omega, \text{ so that } \omega = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$

Equation 73 gives :—

$$i = e^{-at} (F \cos \omega t + G \sin \omega t)$$

and, as before, by considering $t = 0$, F and G may be evaluated, giving :—

$$i = \frac{E}{\omega L} e^{-at} \sin \omega t$$

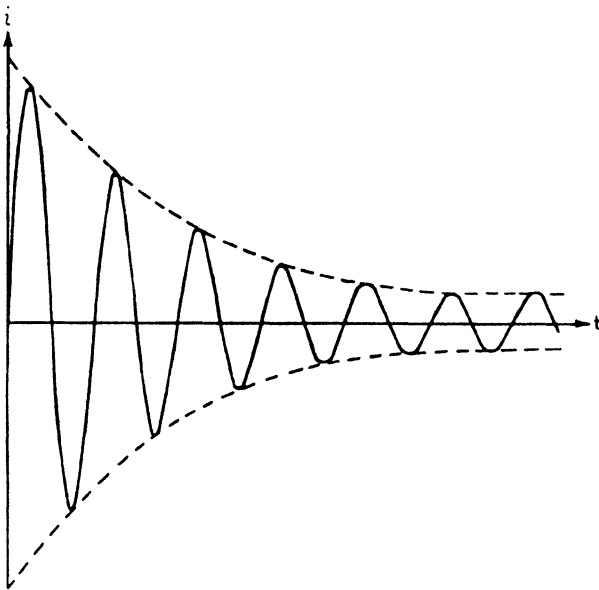


FIG. 136.—Current in circuit of Fig. 134 when $\frac{R^2}{4L^2} < \frac{1}{LC}$.

This shows that i has an exponentially decaying sinusoidal waveform, as shown in Fig. 136. Damped oscillations occur in this circuit at a frequency f given by :—

$$f = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$

This is known as the "natural resonant frequency" of the circuit. The rate of damping is proportional to a , i.e., $\frac{R}{2L}$, and will be least when R is small.

CHAPTER 4

ALTERNATING CURRENTS

DC theory deals with the behaviour of currents and voltages that are constant in magnitude and direction; AC theory deals with currents and voltages that are not constant, but that vary through some particular cycle of values which is repeated continuously at some fixed rate. The rate of repetition is called the "frequency" and is measured in cycles per second. Fig. 137 shows the graph of such a waveform; the vertical axis represents voltage, and the horizontal axis, time.

It can be seen that the complete voltage cycle extends from *A* to *B*, where it is repeated. The duration of each cycle in this case is $\frac{1}{100}$ th sec., and hence there are 100 cycles in one second, *i.e.*, the "frequency" is 100 cycles/second. The frequency may

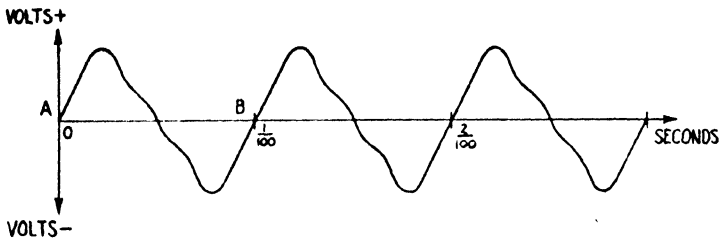


Fig. 137.—Typical alternating current waveform.

have any value up to infinity. For convenience this range can be roughly divided up into bands. Frequencies below 100 cycles/second are normally used for commercial power distribution; for example, in this country the supply frequency is usually 50 cycles/second. The next band is the "audio" frequency band, *i.e.*, the range of the human ear. The exact limits of this vary with individuals, but lie between 20 c/s and 20 kc/s (20,000 cycles/second); many people cannot hear above 10 kc/s. The frequency determines the "pitch" of a note; for example, middle "C" on a piano is taken, using the scientific scale, as 256 cycles/second. An increase in pitch of one octave is equivalent to *doubling* the frequency. Faithful reproduction of speech or music would demand a system that could work from 20 cycles/second to 20 kc/s; it is possible, however, to obtain satisfactory intelligibility of speech if frequencies between 300 and 2,000 cycles/second are reproduced. Above this range are

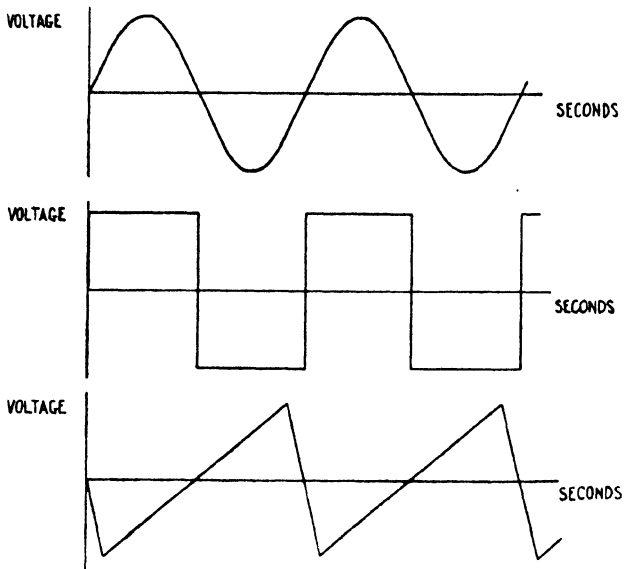


FIG. 138.—Alternating voltages having (a) sinusoidal, (b) square, and (c) triangular waveforms.

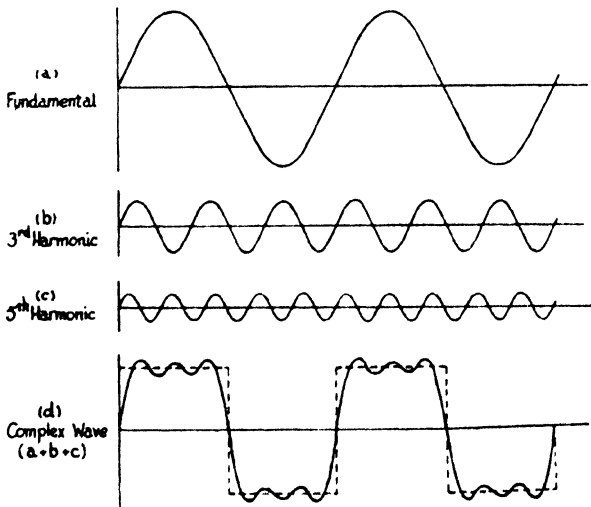


FIG. 139.—Addition of fundamental sine wave, with third and fifth harmonics, to give an approximation to a square waveform.

the frequencies used for carrier telephony and wireless—up to several thousand megacycles—and these are further sub-divided.

The shape or “ waveform ” of an alternating voltage or current is just as important as the frequency. Fig. 138 shows three voltages that have the same frequency but have different waveforms.

Since any recurrent waveform may have to be dealt with, the problem is to develop a general theory that can be applied to any particular case, and Fourier's theorem provides the solution.

Fourier's theorem

The mathematical aspect of Fourier's theorem has been dealt with in Chapter 2. In words, this theorem states that *any recurrent waveform of frequency f can be resolved into the sum of a number of sinusoidal waveforms having frequencies $f, 2f, 3f, \dots$. The number of sine waves may be finite or infinite.*

An alternative way of stating the theorem is to state that any steady note can be split up into a fundamental and “ harmonics ”. The fundamental has frequency f , the second harmonic has frequency $2f$, the third harmonic has frequency $3f$, and so on. Sounds produced by the human voice or musical instruments nearly always contain a large number of harmonics.

This theorem thus reduces any waveform to a number of sine waves. The square wave, for example, consists of a fundamental and all the *odd* harmonics up to infinity: suppose the amplitude of the fundamental is 1, then the amplitude of the third harmonic will be $\frac{1}{3}$, that of the fifth will be $\frac{1}{5}$, and so on. Fig. 139 shows the result of taking up to the 5th harmonic; it will be seen that this gives a good approximation to a square wave.

The general theory developed in this chapter will therefore be based on the assumption that the waveform is sinusoidal. The behaviour of other types of waveform can be investigated by applying Fourier's theorem and the Superposition theorem (see Chapter 5).

SINUSOIDAL WAVEFORMS

Fig. 140 shows the graph of $e = E_{\max} \sin 2\pi ft$. This is known as a sinusoidal waveform or sine wave, and it has been shown in

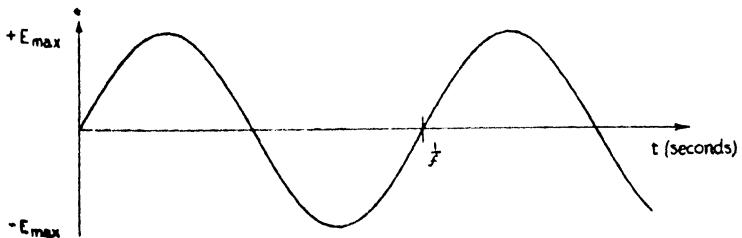


FIG. 140.—Graph of $e = E_{\max} \sin 2\pi ft$.

Chapter 3 that it is the form of voltage produced in a loop of wire rotated with a constant speed of rotation in a uniform magnetic field (the simple alternator).

From the equation it can be seen that the first cycle ends when

$$2\pi ft = 2\pi \text{ (radians) ;}$$

that is, after a time $t = \frac{1}{f}$ seconds.

Hence the "periodic time" of one cycle is $\frac{1}{f}$ seconds, and therefore there are f cycles per second; *i.e.*, f is the frequency.

It can also be seen (remembering that the maximum value of $\sin \theta$ is 1) that the maximum value of e is E_{\max} . Hence

$$e = E_{\max} \sin 2\pi ft$$

is the equation of a sinusoidal EMF whose peak value is E_{\max} and whose frequency is f . " e " represents the value of the EMF at any time t , and is known as the "instantaneous" value. Similarly $i = I_{\max} \sin 2\pi ft$ represents a sinusoidal current. The function need not necessarily be " $\sin 2\pi ft$ ", since " $\cos 2\pi ft$ ", or " $\sin (2\pi ft + \varphi)$ ", or " $A \sin 2\pi ft$ ", all represent sinusoidal waveforms.

Angular velocity

The voltage produced by a coil of wire rotating in a linear magnetic field has been shown to be $e = E_{\max} \sin 2\pi ft$, where f is the speed of rotation in revolutions/second. If the angular velocity ω (in radians/sec.) is taken as determining the speed, the equation becomes $e = E_{\max} \sin \omega t$; for there are 2π radians to one revolution, and hence f revolutions/second corresponds to $2\pi \times f$ radians/sec.

That is,
$$\omega = 2\pi f \quad (1)$$

In AC problems it is often more convenient to deal with ω than with f , principally because the three symbols $2\pi f$ can be replaced by the single symbol ω .

At this stage it is worth mentioning certain approximations that can be made in calculations where extreme accuracy is not required. It will be found that $f = 800$ c/s gives $\omega = 5,025$ radians/second, and this can normally be taken as 5,000, the error being only $\frac{1}{2}$ per cent. Similarly $f = 1,600$ c/s gives $\omega \approx 10,000$ radians/second, and so on. These approximations will be made in this chapter, and are worth remembering.

Mean and RMS values

The mean value of any expression of the form $E_{\max} \sin \omega t$ is zero over an indefinite period of time. It will be assumed when dealing with *any* waveform that the mean value is zero; otherwise it can be regarded as containing a DC component, which must be dealt with separately.

It was shown in connection with DC (Chapter 3) that the power or heating effect of a voltage or current depended upon its *square*. This applies also to AC, but the square of a sine wave will vary from

instant to instant ; it is, in fact, not the *instantaneous* value of the square that is important, but its *mean* value. It can be seen at once that this mean value will not be zero, for a *square* is always positive. This mean value is most conveniently expressed in the form of a voltage E such that E^2 is equal to the mean value of e^2 . In this case E is the square root of the mean value of e^2 , and is therefore called the *Root Mean Square* (RMS) value of the alternating voltage ; it is that steady voltage which would give the same mean power effect as the alternating voltage. A similar definition applies to RMS values for alternating currents. These values are written as E_{RMS} and I_{RMS} . This is to distinguish these values from maximum values (E_{max} and I_{max}) and instantaneous values (e and i).

The value of E_{RMS} will now be calculated in terms of E_{max} . The first step is to calculate the mean value of e^2 ; this can be done by calculus, or more simply as follows :—

$$e = E_{max} \sin \omega t$$

$$\therefore e^2 = E_{max}^2 \sin^2 \omega t$$

The mean value of $\sin^2 \omega t$ is not obvious, but a useful trigonometric formula gives :—

$$\sin^2 \theta = \frac{1}{2} (1 - \cos 2\theta)$$

Applying this formula :—

$$e^2 = E_{max}^2 \times \frac{1}{2} (1 - \cos 2\omega t)$$

$$= \frac{E_{max}^2}{2} - \frac{E_{max}^2}{2} \cos 2\omega t$$

Considering the right-hand side, the first term is constant and its mean value is equal to $\frac{E_{max}^2}{2}$. The second term has a sine wave-form, and its mean value over a period of time is zero.

$$\therefore \text{The mean value of } (e^2) = \frac{E_{max}^2}{2}$$

Now $E_{RMS} = \sqrt{\text{mean value of } e^2}$

$$\therefore E_{RMS} = \frac{E_{max}}{\sqrt{2}} \quad (2)$$

which gives the RMS value in terms of the peak value.

$$\text{Similarly } I_{RMS} = \frac{I_{max}}{\sqrt{2}} \quad (3)$$

Alternating voltages and currents are usually measured by their RMS values ; it is important to remember this, as all insulation must be able to withstand the *peak* voltage. For example, the normal 230 volt mains supply has a peak voltage of $\sqrt{2} \times 230 = 325.3$ volts.

AC + DC.—If both AC and DC flow through a circuit at the same time, the RMS value of the resultant is $\sqrt{I_{DC}^2 + I_{RMS}^2}$ where I_{DC} is the DC component, and I_{RMS} is the RMS value of the AC component. The proof is similar to that given above.

Mean and average values.—The mean value of any expression of the form $e = E_{max} \sin \omega t$ (which has been seen to be zero over an indefinite period of time) is usually called the “average” value of e . The term “mean value of e ” is frequently used to represent the “mean value of $|e|$ ”, which in the case of a sine wave can be shown to be equal to $\frac{2}{\pi} \cdot E_{max} = 0.637 \cdot E_{max}$.

Form factor.—The ratio of the RMS value to the mean value of a current or voltage is called the “form factor” of the waveform in question. In the case of a sine wave:—

$$\text{Form factor} = \frac{0.707 \cdot E_{max}}{0.637 \cdot E_{max}} = 1.11$$

Phase

Two wave-forms of the same frequency may not reach similar points of a cycle (*e.g.*, peak values) at the same time. The amount by which they are out of step is called the “difference in phase”, and is just as important as the magnitude when comparing two wave-forms. Phase difference is normally expressed as the angle by which one wave is ahead of, or behind, the other. In Fig. 141, for example,

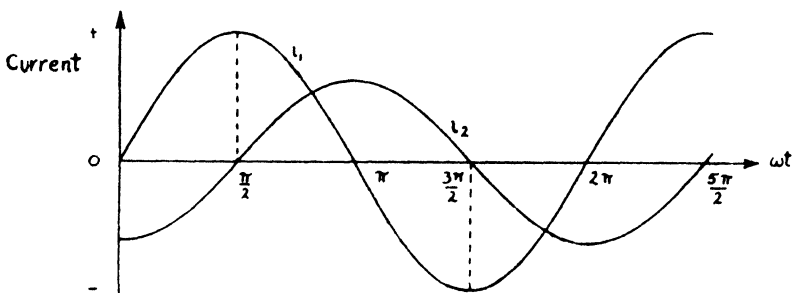


FIG. 141.—Two currents 90° out of phase.

the larger curve is 90° (or $\frac{\pi}{2}$ radians) ahead of the smaller one. This can be seen from the fact that the larger one is initially zero, but the smaller one is zero and increasing in the same direction 90° later.

The difference in phase between two voltages or currents can easily be seen from the equations.

For example, $e = E_{max} \sin(\omega t + \phi)$ represents a wave that is ϕ radians ahead of the wave $e' = E'_{max} \sin \omega t$.

Note that the voltage $e = E_{\max} \sin \omega t$ is 90° behind the voltage $e' = E'_{\max} \cos \omega t$, since $\cos \omega t = \sin(\omega t + 90^\circ)$.

Sum of two sine waves of same frequency

The sum of two sinusoidal wave-forms of the same frequency is a third sinusoidal wave-form having the same frequency.

This can be proved in two ways.

(a) Draw the graphs of the two, and add up point by point. The resultant will be a sine wave of the same frequency.

(b) Proof from equations:—

Let voltages be $e_1 = E_{1\max} \sin \omega t$

and $e_2 = E_{2\max} \sin(\omega t + \varphi)$

$$= E_{2\max} \sin \varphi \cos \omega t + E_{2\max} \cos \varphi \sin \omega t$$

$$\therefore e_1 + e_2 = (E_{1\max} + E_{2\max} \cos \varphi) \sin \omega t + E_{2\max} \sin \varphi \cos \omega t$$

Now any expression of the form $A \sin \omega t + B \cos \omega t$ can be written as:—

$$A \sin \omega t + B \cos \omega t$$

$$= \sqrt{A^2 + B^2} \left(\frac{A}{\sqrt{A^2 + B^2}} \sin \omega t + \frac{B}{\sqrt{A^2 + B^2}} \cos \omega t \right)$$

$$= \sqrt{A^2 + B^2} \sin(\omega t + \theta)$$

$$\text{where } \tan \theta = \frac{B}{A}, \sin \theta = \frac{B}{\sqrt{A^2 + B^2}}, \text{ and } \cos \theta = \frac{A}{\sqrt{A^2 + B^2}}$$

Hence $e_1 + e_2$

$$= \sqrt{(E_{1\max} + E_{2\max} \cos \varphi)^2 + E_{2\max}^2 \sin^2 \varphi} \sin(\omega t + \theta)$$

$$= \sqrt{E_{1\max}^2 + E_{2\max}^2 + 2E_{1\max} E_{2\max} \cos \varphi} \sin(\omega t + \theta) \quad (4)$$

$$\text{where } \theta = \tan^{-1} \frac{E_{2\max} \sin \varphi}{E_{1\max} + E_{2\max} \cos \varphi}$$

This is a sine wave of the same frequency as e_1 and e_2 .

Representation by rotating vector

Neither the graphical nor the trigonometrical method of representing AC is entirely satisfactory, particularly when relative phase or addition has to be shown. It will now be shown that any sinusoidal alternating current or voltage can be represented as part of a rotating vector.

Consider the expression $e = E_{\max} \sin \omega t$. To calculate e from first principles, the value of $\sin \omega t$ at any instant has to be found. This is done, as in trigonometry, by drawing the angle ωt anti-clockwise from a starting line, and dropping a perpendicular (see Fig. 142).

The angle $\angle PON = \omega t$. Then $\frac{NP}{OP} = \sin \omega t$.

To calculate $e = E_{\max} \sin \omega t$, make $OP = E_{\max}$.

Then $PN = E_{\max} \sin \omega t$

$\therefore PN = e$

A moment later, ωt will have altered, but E_{\max} is constant and therefore OP remains the same length. This is represented by Fig. 143.

In all cases, e is equal to PN ; if P falls below the horizontal axis, e is negative.

If the figure is drawn for successive instants, the line OP will rotate about O at a constant angular velocity ω . As both the length and the direction of OP are important, it must be regarded

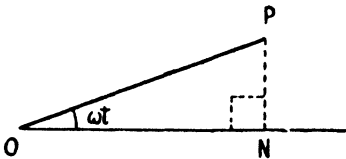


FIG. 142.—Representation of sinusoidal voltage by rotating vector OP .

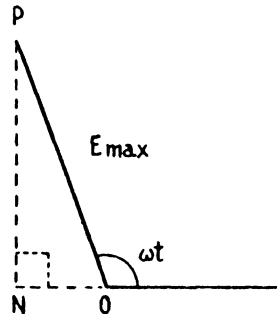


FIG. 143.—Representation of sinusoidal voltage by rotating vector OP .

as a vector, and e is equal to its vertical component. Note that e is only *part* of the vector; in practice it is easier to deal with a complete vector than with any particular part, and it is for this reason that vectors are so important in AC theory. The reason is easy to see: e itself is a *varying* quantity, but the complete vector has *constant* amplitude and *constant* angular velocity.

The representation of AC by vectors may be summarised as follows: any sinusoidal alternating EMF of peak value E_{\max} and angular velocity ω may be represented by the vertical component of a rotating vector whose length is equal to E_{\max} and whose angular velocity is equal to ω . It can be seen that the frequency of the alternating voltage is equal to the speed of rotation of the vector measured in *revolutions per second*.

A similar definition applies to currents.

Note that the *horizontal* component could equally well have been taken.

Illustration of phase difference

Consider the voltage $e_2 = E_{\max} \sin(\omega t + \phi)$. This is the vertical part of a vector whose length is E_{\max} and whose angle

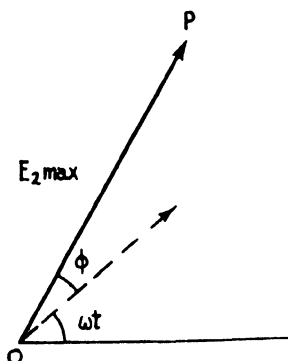


FIG. 144.—Representation of sinusoidal voltage e_2 by rotating vector OP .

is $\omega t + \phi$. To draw the vector, the angle ωt would be drawn as before, and the constant angle ϕ added to it, as in Fig. 144.

If this vector and the vector representing $e_1 = E_{1max} \sin \omega t$ are drawn on the same diagram for different values of ωt , Fig. 145 is obtained.

Note that E_{1max} and E_{2max} remain in the same *relative* position, rotating together at the same speed. In AC problems it is sufficient to consider vectors in one position only, and to simplify calculation a position is usually chosen in which one of the vectors is horizontal. Thus the two voltages would appear as in Fig. 146.

It is important to remember, when dealing with these "vector diagrams", as they are called, that although drawn in one fixed position, the vectors are rotating at a constant angular velocity ω ; and that the instantaneous voltages are the vertical components of the vectors at any instant. The direction of rotation is anti-

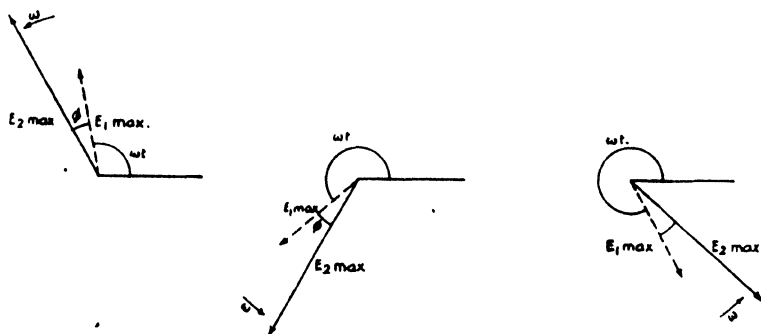


FIG. 145.—Representation of two sinusoidal voltages e_1 and e_2 by rotating vectors.

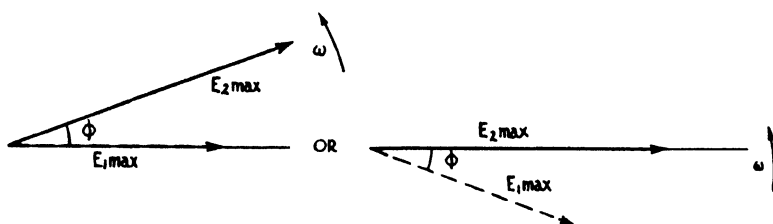


FIG. 146.—Vector representation of the two voltages e_1 and e_2 .

clockwise, as shown in Fig. 146. It will be noted that a vector diagram is the best way of showing the phase difference between two waveforms.

Addition of voltages

The problem of addition and subtraction, already solved by two methods, is much simplified by using vectors. To find the sum of $e_1 = E_{1,max} \sin \omega t$ and $e_2 = E_{2,max} \sin (\omega t + \phi)$ it is necessary to find the *sum of the vertical components of two vectors*. This, of course, is equal to the *vertical component of the sum of the two vectors*—in other words, if the two vectors are drawn and added, the resultant vector will represent the sum of the two voltages.

This is shown in Fig. 147.

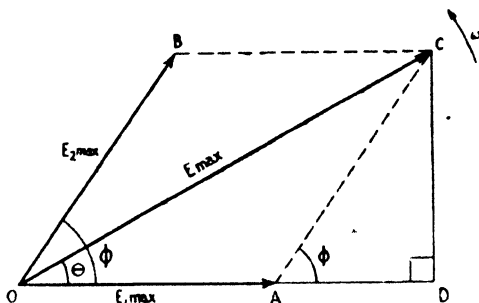


FIG. 147.—Addition of two out-of-phase voltages by rotating vectors.

Since $E_{1,max}$ and $E_{2,max}$ rotate together, E_{max} will rotate at the same speed and the figure will not change its shape; hence E_{max} has the same frequency as $E_{1,max}$ and $E_{2,max}$.

Applying the cosine formula to the triangle OAC :—

$$OC = \sqrt{OA^2 + AC^2 - 2.OA.AC \cos (180^\circ - \phi)}$$

$$\text{i.e. } E_{max} = \sqrt{E_{1,max}^2 + E_{2,max}^2 + 2E_{1,max}E_{2,max} \cos \phi} \quad (5)$$

Dropping a perpendicular CD on to OA ,

$$\tan \theta = \frac{CD}{OA + AD}$$

$$\therefore \theta = \tan^{-1} \frac{E_{2\max} \sin \varphi}{E_{1\max} + E_{2\max} \cos \varphi} \quad (6)$$

It will be seen from this that the use of vectors provides an easy way of determining the sum of two alternating voltages. Subtraction is done by subtracting the vectors. It is most important to note that (unless they happen to be in phase) alternating voltages *cannot be added directly*; that is, the peak or RMS values cannot be added. Addition or subtraction *must* be done vectorially.

AC CIRCUITS

The next problem is to consider the behaviour of alternating currents and voltages in various circuits, consisting of combinations of inductance, capacity and resistance. It will be shown that in these circuits a sinusoidal voltage produces a sinusoidal current of the same frequency, and *vice versa*. The current and voltage will not, in general, be in phase; the phase and magnitude relationships for particular circuits will now be determined.

Resistance, capacity and inductance

Resistance.—Let a voltage $e = E_{\max} \sin \omega t$ be applied to a resistance R (see Fig. 148).

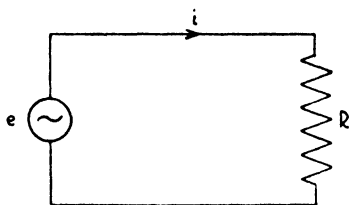


FIG. 148.—Alternating voltage applied to resistance.

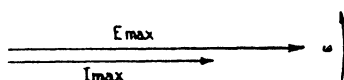


FIG. 149.—Current through resistance in phase with the applied voltage.

Ohm's law applies at any instant; hence i can be determined from the equation $e = iR$ or $i = \frac{E_{\max}}{R} \sin \omega t$.

Hence i is a sinusoidal alternating current, in phase with e and having the same frequency. The peak value of i is $I_{\max} = \frac{E_{\max}}{R}$.

The two relationships are therefore:—

(a) e and i are in phase.

$$(b) \frac{E_{\max}}{I_{\max}} = R. \quad (7)$$

The vector diagram is therefore as shown in Fig. 149, where the two vectors have been separated for clarity.

Inductance.—Let $e = E_{\max} \sin \omega t$ be applied to an inductance L (see Fig. 150). The resistance of the inductance is taken as zero.

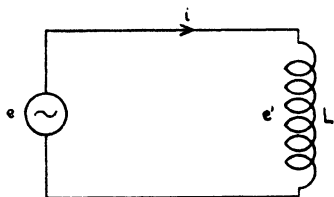


FIG. 150.—Alternating voltage applied to an inductance.

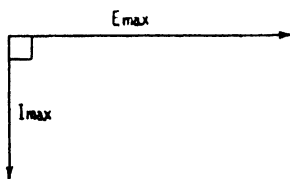


FIG. 151.—Current through inductance lagging 90° behind applied voltage.

The EMF induced across the inductance, e' , is given by $-L \frac{di}{dt}$.

Applying Kirchhoff's second law:—

$$e + e' = 0$$

$$\therefore e - L \frac{di}{dt} = 0$$

$$\therefore \frac{di}{dt} = \frac{e}{L} = \frac{E_{\max}}{L} \sin \omega t$$

Integrating with respect to t ,

$$i = \frac{-E_{\max}}{\omega L} \cos \omega t$$

This can be written as:—

$$i = \frac{+E_{\max}}{\omega L} \sin \left(\omega t - \frac{\pi}{2} \right)$$

which shows that:—

(a) i is 90° behind e .

(b) $I_{\max} = \frac{E_{\max}}{\omega L}$. (8)

The vector diagram is shown in Fig. 151.

Capacity.—Let $e = E_{\max} \sin \omega t$ be applied to a condenser of capacity C (see Fig. 152).

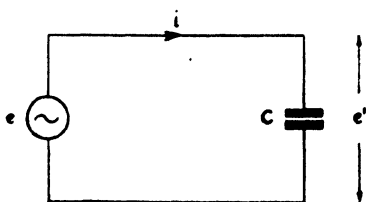


FIG. 152.—Alternating voltage applied to condenser.

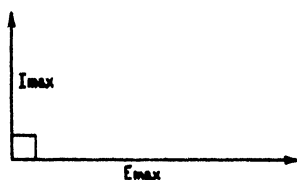


FIG. 153.—Current through condenser leading the applied voltage by 90° .

Measured in the direction of i , $e' = -\frac{q}{C} = -\frac{1}{C} \int idt$

(Note the minus sign: if i is positive, e' is in opposition to i .)

Applying Kirchhoff's second law:—

$$e + e' = 0$$

$$\therefore e = \frac{1}{C} \int idt$$

$$\therefore \int idt = CE_{\max} \sin \omega t$$

Differentiating with respect to t ,

$$i = \omega CE_{\max} \cos \omega t$$

This may be written as:—

$$i = \omega CE_{\max} \sin \left(\omega t + \frac{\pi}{2} \right)$$

showing that:—

(a) i is 90° ahead of e .

(b) $I_{\max} = \omega CE_{\max}$.

(9)

The vector diagram is shown in Fig. 153.

Current-voltage relationships in AC circuits

All DC theory, including, in particular, Kirchhoff's laws, is based upon the fact that $E \div I$ is a constant and is equal to the resistance R . A similar relationship is required for AC if the same methods are to apply. But, taking instantaneous values, $e \div i$ will vary from 0 to $\pm\infty$ if the two are not in phase, so the law does not hold in its original form.

Consider, however, the result of dividing the *vectors* representing e and i . Denoting these vectors by E and I , then $\frac{E}{I}$ will be a vector; let it be the vector $Z = |Z| / \varphi$. To divide these vectors, divide the lengths and subtract the angles;

$$\text{then } |Z| = \frac{|E|}{|I|} = \frac{E_{\max}}{I_{\max}},$$

which is constant. Also, the angle φ will be equal to the angle between E and I , that is, the phase angle, which is also constant. Provided, then, that vectors are used throughout, the relationship $\frac{E}{I} = Z$ holds for AC, just as $\frac{E}{I} = R$ applies to DC. The vector Z is called the *impedance vector*, impedance being, in a sense, the AC equivalent of resistance, since it represents the total opposition of the circuit to current. Note that although E and I are rotating vectors, Z is fixed.

Since, in practical problems, alternating voltages and currents are measured by their RMS values, it is convenient to let the magnitudes of the vectors employed correspond to these RMS values.

Hence let

$$|E| = E_{RMS}$$

and

$$|I| = I_{RMS}$$

By so doing, the vector approach will yield an RMS answer. This convention will be used throughout this book. When no ambiguity is likely to arise between the vector and its modulus, the modulus sign may be omitted and the RMS voltages and currents represented by E and I .

The procedure for AC problems is first to find an expression for Z . The vector Z is of no use except as a means to an end: its modulus, however, gives the ratio between peak (or RMS) values: $\frac{E_{\max}}{I_{\max}} = \frac{E_{\text{RMS}}}{I_{\text{RMS}}} = |Z|$; and its angle gives the phase angle by which the voltage leads the current. If the angle is negative, the current is ahead of the voltage.

The value of $|Z|$ is the impedance of the circuit in ohms. Z , being a vector, can be expressed in the "j" notation as $R + jX$; then R is the resistive part of the impedance, and X the reactive part, called the "reactance". The expression $\frac{1}{Z}$ is called the "admittance", and may be denoted by Y . It, also, is a vector.

The impedance Z of any circuit can be calculated, provided that the impedance of each of the three fundamental components R , L and C is known; these three cases will now be dealt with.

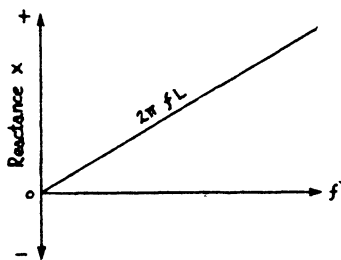


FIG. 154.—Reactance of an inductance.

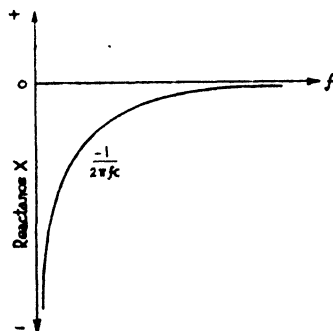


FIG. 155.—Reactance of a condenser.

Resistance (see Fig. 148).—

$$|Z| = \frac{E_{\max}}{I_{\max}} = R; \quad \text{angle } \varphi = 0^\circ;$$

$$\therefore Z = R \angle 0^\circ = R \quad (10)$$

Hence the vector impedance of a resistance is a real number equal to its resistance, and does not vary with frequency.

Inductance (see Fig. 150).—

$$|Z| = \frac{E_{\max}}{I_{\max}} = \omega L; \quad \text{angle } \varphi = +90^\circ;$$

$$\therefore Z = \omega L \angle 90^\circ = j\omega L = j2\pi fL \quad (11)$$

Hence the vector impedance of an inductance is a pure imaginary quantity, whose magnitude increases with frequency. The reactance $X_L = \omega L = 2\pi fL$, and varies with frequency as in Fig. 154.

Capacity (see Fig. 152).—

$$|Z| = \frac{E_{\max}}{I_{\max}} = \frac{1}{\omega C}; \quad \text{angle } \phi = -90^\circ$$

$$\therefore Z = \frac{1}{\omega C} \angle -90^\circ$$

$$= \frac{-j}{\omega C} = \frac{1}{j\omega C} \quad (12)$$

These two expressions are equivalent, but *it will be found, as a general rule, that the first is the more useful if the condenser is in a series circuit, and the second if it is in a parallel circuit.*

It will be seen that the vector impedance of a capacity is a pure imaginary quantity, whose magnitude decreases with frequency.

The reactance $X_C = \frac{-1}{\omega C} = \frac{-1}{2\pi fC}$ (see Fig. 155).

The three results just obtained are important, as they form the basis of all AC theory. It is possible from them to calculate the impedance of any network; for when dealing with vectors the same methods can be employed as in DC. If, for instance, impedances are connected in series, the total impedance is found by adding the *vector* impedances. It is most important to note that impedances cannot be added unless they are in vector form. Similarly, if impedances are connected in parallel, the total impedance may be found by adding the *vector* admittances.

Calculation of impedance of simple circuits

The simplest type of problem is the calculation of the impedance of a given circuit at some frequency. Two answers are generally required: the impedance in ohms, and the phase angle between current and voltage—that is, $|Z|$, and the angle ϕ . The angle ϕ is normally assumed to lie in either the first or the fourth quadrant. The steps in this type of problem are as follows:—

(a) Draw the circuit, inserting the impedances as vectors. If numerical values are given, simplify each impedance as far as possible. It is usually best *not* to eliminate fractions.

(b) Find total *vector* impedance by applying the same methods as for DC problems. Simplify the answer if possible.

(c) Find $|Z|$. From this, if the applied RMS voltage is given, the RMS current may be found, or *vice versa*, by

remembering that $|Z| = \frac{E}{I} = \frac{E_{\max}}{I_{\max}}$.

(d) Find the angle ϕ . Hence the phase relationship between e and i is determined. Remember that if ϕ is negative the current is ahead of the voltage.

Two examples will illustrate this method.

Example 1.—A general problem without numerical values. An inductance and resistance are connected in series; find the impedance at any frequency, and the phase angle.

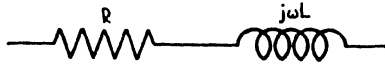


FIG. 156.—Inductance in series with resistance.

Step a.—Consider Fig. 156.

Note that the impedance of the inductance has been written in vector form as $j\omega L$.

Step b.—The two impedances, as vectors, are R and $j\omega L$. They are in series, so the total impedance is found by adding:—

$$Z = R + j\omega L$$

Steps c and d.*—

$$\text{Hence } |Z| = \sqrt{R^2 + \omega^2 L^2} \quad \text{Ans. (i)}$$

$$\text{and } \tan \varphi = \frac{\omega L}{R} \quad \text{Ans. (ii)}$$

Since φ is positive, the current lags on the voltage.

The answers just obtained are general, and could be applied to a particular case by substituting numerical values. As, however, there are so many possible combinations of R , L and C , it is impossible to remember all the necessary formulae, and it is better to work out each example from first principles.

Example 2.—Find the current flowing in the circuit of Fig. 157, and calculate its phase with respect to the voltage.

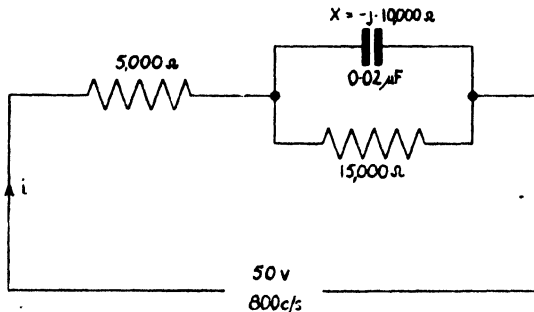


FIG. 157.—Circuit containing resistance in parallel with capacity, in series with another resistance.

Step a.—The impedance of the condenser must be written as a vector. The two possible expressions are $\frac{-j}{\omega C}$ and $\frac{1}{j\omega C}$, and since this is a parallel circuit, the second expression will be used

* See conversion from rectangular to polar vector notation, p. 58.

here. Numerical values are now inserted, remembering that $f = 800$ gives $\omega = 5,000$. Then,

$$\frac{1}{j\omega C} = \frac{100 \times 10^6}{j \times 5 \times 10^3 \times 2} = \frac{10^8}{j \cdot 10^4} = \frac{10^4}{j} = -j \cdot 10,000$$

Step b.—To find the total impedance, the impedance of the parallel circuit must first be found. Remembering that:—

$$\frac{1}{Z_r} = \frac{1}{Z_1} + \frac{1}{Z_2}, \text{ so that } Z_r = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2}}$$

this is given by:—

$$Z_r = \frac{1}{\frac{1}{15,000} + \frac{j}{10^4}}$$

Bringing the bottom line over a common denominator:—

$$Z_r = \frac{1}{\frac{2 + j3}{30,000}} = \frac{3 \times 10^4}{2 + j3}$$

The total impedance Z is this in series with $5,000 \Omega$

$$\therefore Z = 5 \times 10^3 + \frac{3 \times 10^4}{2 + j3}$$

Always remove common factors where possible; in this case take out 5×10^3 , giving:—

$$Z = 5 \times 10^3 \left[1 + \frac{3 \times 2}{2 + j3} \right]$$

Simplifying the expression in the bracket,

$$Z = 5 \times 10^3 \left[\frac{2 + j3 + 6}{2 + j3} \right]$$

$$\therefore Z = 5 \times 10^3 \times \frac{(8 + j3)}{(2 + j3)} \quad (i)$$

This is the answer in its simplest form. It is *not* usual to rationalise at this stage, for although it is easy in this case, it usually leads to much unnecessary additional work.

Step c.—Find $|Z|$. Z consists of a number of vectors multiplied together or divided; to find its modulus, the separate moduli must be multiplied or divided. The factor 5×10^3 of course remains unchanged, as can be seen by regarding it as a vector.

$$\begin{aligned} \text{Hence } |Z| &= 5 \times 10^3 \times \frac{|8 + j3|}{|2 + j3|} \\ &= 5 \times 10^3 \times \frac{\sqrt{64 + 9}}{\sqrt{4 + 9}} \end{aligned}$$

$$\therefore |Z| = 5 \times 10^3 \sqrt{\frac{73}{13}}$$

As the impedance itself is not required, this answer is not worked out at this stage. The current is calculated by remembering that

$$|Z| = \frac{E}{I}$$

Now $E = 50$ volts,

$$\begin{aligned} \therefore I &= \frac{50}{|Z|} = \frac{50}{5 \times 10^3} \sqrt{\frac{13}{73}} \text{ amps} \\ &= 10 \sqrt{\frac{13}{73}} \text{ mA} \\ &= 4.2 \text{ mA} \quad \text{Ans. (i)} \end{aligned}$$

Step d.—Find the angle φ . Z consists of a number of vectors multiplied together or divided, and its angle is found by adding or subtracting the individual angles.

$$\begin{aligned} \text{Hence from (i)} \quad \varphi &= \tan^{-1}\left(\frac{3}{8}\right) - \tan^{-1}\left(\frac{3}{2}\right) \\ &= \tan^{-1}(0.375) - \tan^{-1}(1.5) \\ &= 20^\circ 33' - 56^\circ 18' \quad (\text{these values being chosen} \\ &\quad \text{because } 8 + j3 \text{ and } 2 + j3 \\ &\quad \text{both lie in the first quadrant}) \\ &= -35^\circ 45' \quad \text{Ans. (ii)} \end{aligned}$$

The negative sign shows that i leads e , as is to be expected in a capacitive circuit.

i is therefore a current of 4.2 mA, leading the voltage by $35^\circ 45'$.

Calculation of frequency or component values in simple circuits

In some problems, the impedance is given and either the frequency or one of the component values is required. Each problem must be treated on its merits, but two examples are given to illustrate typical methods.

Example 1 (see Fig. 158).—Find the frequency.

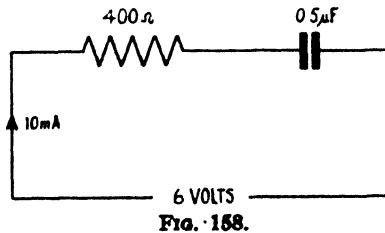


FIG. 158.

As the voltage and current are given, the impedance can be found:—

$$|Z| = \frac{E}{I} = \frac{6 \times 1,000}{10} = 600 \text{ ohms}$$

To obtain an equation for f , an expression is first found for the impedance of the resistance and condenser in series.

Step a.—Consider Fig. 159.

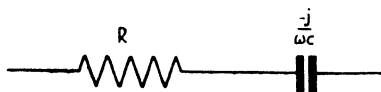


FIG. 159.

Step b.— $Z = R - \frac{j}{\omega C}$

Step c.— $|Z| = \sqrt{R^2 + \frac{1}{\omega^2 C^2}}$

Applying this expression to the example:—

$$600 = \sqrt{(400)^2 + \frac{(10^6)^2}{\omega^2 \times (0.5)^2}}$$

Squaring both sides:—

$$36 \times 10^4 = 16 \times 10^4 + \frac{10^{12} \times 4}{\omega^2}$$

$$\therefore \frac{4 \times 10^{12}}{\omega^2} = 20 \times 10^4$$

$$\therefore \omega^2 = \frac{4 \times 10^{12}}{20 \times 10^4} = 2 \cdot 10^7$$

$$\therefore \omega = \sqrt{2 \times 10^7} = 10^3 \cdot \sqrt{20}$$

Thus $f = \frac{\omega}{2\pi} = \frac{10^3 \cdot \sqrt{20}}{2\pi}$
 $= 712 \text{ c/s } \textit{Ans.}$

Example 2 (see Fig. 160).—

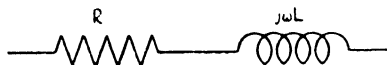


FIG. 160.

$|Z|$ is given as 500Ω at 800 c/s (i.e., $\omega = 5 \times 10^3$) (i)

$|Z|$ is given as 800Ω at $1,600 \text{ c/s}$ (i.e., $\omega = 10^4$) (ii)

Find R and L .

It is first necessary to calculate the impedance of a resistance and inductance in series.

Step a.—Write the impedance of L as $j\omega L$

Step b.—The total impedance $Z = R + j\omega L$

Step c.— $|Z| = \sqrt{R^2 + \omega^2 L^2}$

Apply this to the problem, giving two equations:—

(i) becomes: $500 = \sqrt{R^2 + 25 \cdot 10^6 L^2}$ (iii)

and (ii) becomes: $800 = \sqrt{R^2 + 100 \cdot 10^6 L^2}$ (iv)

Squaring each side of these two equations:—

(iii) becomes: $25 \cdot 10^4 = R^2 + 25 \cdot 10^6 L^2$ (v)

and (iv) becomes: $64 \cdot 10^4 = R^2 + 100 \cdot 10^6 L^2$ (vi)

Subtract, $39 \cdot 10^4 = 75 \cdot 10^6 L^2$ (vii)

$\therefore L^2 = \frac{39 \cdot 10^4}{75 \cdot 10^6}$

$\therefore L = \frac{1}{10} \sqrt{\frac{39}{75}}$ Henries
 $= 100 \sqrt{\frac{39}{75}}$ mH
 $= \frac{100}{5} \sqrt{\frac{39}{3}}$ mH
 $= 20 \sqrt{13}$ mH
 $= 72$ mH *Ans. (ii)*

Now find R .

Multiplying equation (v) by 3:—

$$75 \cdot 10^4 = 3R^2 + 75 \cdot 10^6 L^2$$

Equation (vii):—

$$39 \cdot 10^4 = 75 \cdot 10^6 L^2$$

Subtracting:—

$$3R^2 = 36 \cdot 10^4$$

$\therefore R^2 = 12 \cdot 10^4$

$\therefore R = 346$ ohms. *Ans. (i)*

More complicated circuits

In more complicated circuits, all currents and voltages will be written down as vectors. These vectors are in fact rotating, but as only their *relative* positions are important, it is permissible to consider them in any position and regard them as fixed. The position is generally chosen so that one of the vectors becomes horizontal—it will then be used as a reference. An example illustrates this.

Example.—See Fig. 161.

Find the current x .

It will be noted that, in the general case, the same graphical symbol is used for all impedances, irrespective of whether they are resistive, inductive, or capacitive.

In this example, the impedances have already been expressed

as vectors. To solve the problem, it will be most convenient to take the EMF of 6 volts as the reference vector ; it thus becomes the vector $6\angle 0$. Let the total generator current be y , so the current in the central arm is $(y - x)$. x and y are both vectors, and x is required. There are two unknowns, so two equations must be found : these are obtained by applying Kirchoff's law round the two small closed networks.

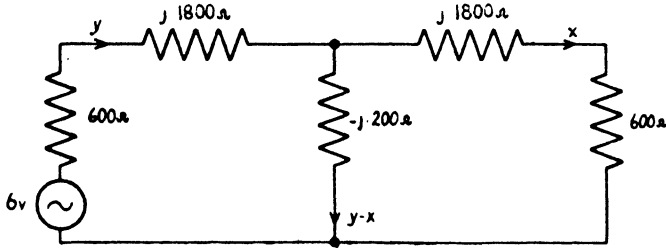


FIG. 161.

Left-hand network :—

$$6 = y (600 + j1800 - j200) + j200x$$

$$\therefore 6 = y (600 + j1600) + j200x \tag{i}$$

Right-hand network :—

$$0 = x (j1800 + 600 - j200) + j200y$$

$$0 = y.j200 + x (600 + j1600)$$

$$0 = jy + x (3 + j8)$$

$$y = jx (3 + j8) \tag{ii}$$

Substitute (ii) in (i) to eliminate y :—

$$6 = jx [(3 + j8) (600 + j1600) + 200]$$

$$= 200jx [1 + (3 + j8)^2] = 200jx [1 + 9 - 64 + j48]$$

$$\therefore x = \frac{6}{j200 (j48 - 54)} = \frac{6}{200 (-48 - j54)} = \frac{-1}{200 (8 + j9)}$$

This gives x in vector form. Its modulus will give the current in amps :

$$|x| = \frac{1}{200\sqrt{64 + 81}} \text{ amp} = \frac{1000}{200\sqrt{145}} \text{ mA} = 0.42 \text{ mA. Ans. (i)}$$

Its angle will be the angle by which x is ahead of the 6 volts,

$$i.e. \quad 180^\circ - \tan^{-1} \frac{9}{8} = 180^\circ - \tan^{-1} 1.125 = 180^\circ - 48^\circ 22'$$

$$= 131^\circ 38' \text{ Ans. (ii)}$$

(The "180°" is the angle corresponding to the " - 1 " in the numerator.)

POWER IN AC CIRCUITS

In DC, the power developed in any circuit is equal to the product of the voltage across it and the current through it. In AC, the *instantaneous power* is equal to the product of the instantaneous values of voltage and current, so that :—

$$p = e \times i \quad (13)$$

The instantaneous power is of little practical value : the important quantity is the “ true power ”, which is defined as the *average value* of the power over a period of time, and is measured in watts. The product of the RMS values $E \times I$ is called the *apparent power* ; it might at first sight appear likely that this would give the true power, but it will be seen shortly that this is not so.

Calculation of true power in any circuit

Take the general case of a circuit where the voltage and current are out of phase by an angle φ , so that :—

$$e = E_{\max} \sin \omega t \quad (14)$$

$$\text{and } i = I_{\max} \sin (\omega t + \varphi) \quad (15)$$

(φ may be negative, but this does not affect the answer).

The instantaneous power is given by :—

$$\begin{aligned} p &= E_{\max} \sin \omega t \times I_{\max} \sin (\omega t + \varphi) \\ &= E_{\max} I_{\max} \sin \omega t \sin (\omega t + \varphi) \end{aligned}$$

The true value of power P is the mean value of this ; to calculate it, the formula $2 \sin A \sin B = \cos (A - B) - \cos (A + B)$ is used.

$$\text{This gives } p = \frac{E_{\max} \times I_{\max}}{2} [\cos \varphi - \cos (2\omega t + \varphi)]$$

Consider the expression inside the bracket. The first term is constant, and its mean value over any period of time is $\cos \varphi$. The second term is a sinusoidal waveform, and its mean value is zero.

Hence $P = \text{mean value of } p$

$$= \frac{E_{\max} \times I_{\max}}{2} \cos \varphi$$

$$\text{i.e. } P = E \times I \cos \varphi \quad (16)^*$$

$$\text{since } E = \frac{E_{\max}}{\sqrt{2}} \text{ and } I = \frac{I_{\max}}{\sqrt{2}} \quad \text{from (2) and (3)}$$

This shows that the true power depends not only on the values of the current and voltage, but also on their relative phase. $\cos \varphi$ is called the “ power factor ” of the load. Note that for a resistance the power factor is unity, and the true power is equal to the apparent power. For a pure reactance (inductance or capacity) $\varphi = 90^\circ$ and $\cos \varphi = 0$, and so a *pure reactance cannot absorb power* ; this is a most important fact.

*If E and I refer to the corresponding rotating vectors then equation 16 becomes $P = |E| \cdot |I| \cdot \cos \varphi$ (see p. 199).

The equation just proved can be written as :—

True power = Apparent power \times power factor.

If the impedance of the load can be written as :—

$$Z = R + jX$$

then the power factor is given by :—

$$\cos \varphi = \frac{R}{\sqrt{R^2 + X^2}} = \frac{R}{|Z|} \quad (17)$$

Alternative forms of the expression can be calculated. Thus :—

$$\begin{aligned} P &= EI \cos \varphi = E \cdot I \cdot \frac{R}{|Z|} \\ &= I^2 |Z| \cos \varphi = I^2 R = \frac{E^2 R}{|Z|^2} = \frac{E^2}{|Z|^2} \cdot \cos \varphi \quad (18) \end{aligned}$$

Of these different forms, $P = I^2 R$ is perhaps the most useful.

Note that the expression $P = \frac{E^2 R}{|Z|^2}$ is *not* the same as the formula $P = \frac{E^2}{R}$ in DC, which applies only to a pure resistance.

As $I \cos \varphi$ is that component of I which is in phase with E , true power can be taken as the product of voltage and the in-phase component of current; or equally as the product of current and the in-phase component of voltage. This method is often useful in AC power questions.

A few examples will illustrate typical methods.

Example 1.—See Fig. 162. Find the total power in watts.

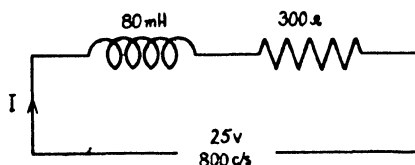


FIG. 162.

The current I will be calculated, and the formula $I^2 R$ applied. To calculate I , $|Z|$ must first be found.

$$f = 800 \quad \therefore \omega = 5000$$

The impedance of the inductance

$$X_L = j\omega L = j \times 5000 \times \frac{80}{1000} = j400$$

$$\therefore |Z| = 100 \sqrt{9 + 16} = 100 \sqrt{25} = 500$$

$$\therefore I = \frac{E}{|Z|} = \frac{25}{500} = \frac{1}{20}$$

$$\begin{aligned} \therefore P &= I^2 R = \frac{1}{400} \times 300 \\ &= 0.75 \text{ watts.} \end{aligned}$$

The following is an alternative method:—

Taking the 25 volts as a reference vector, the current $I = \frac{25}{100(3 + j4)}$. The power is equal to 25 times the in-phase component of i ; this can be found by rationalisation:—

$$I = \frac{25}{100(3^2 + 4^2)}(3 - j4) = \frac{3}{100} - j \frac{4}{100}$$

The first term is the in-phase component, and the second, being multiplied by j , is 90° out of phase. The power is therefore:—

$$P = \frac{3}{100} \times 25 = 0.75 \text{ watt. } \textit{Ans.}$$

Example 2.—See Fig. 163.

Find the total power.

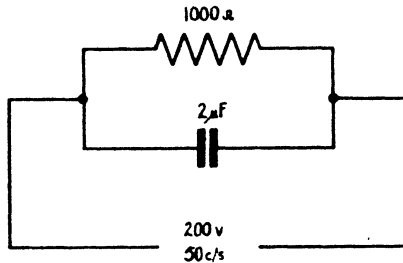


FIG. 163.

The answer should be obvious: the condenser takes no power, and the power in the resistance is calculated from the voltage across it:—

$$P = \frac{E^2}{R} = \frac{4 \times 10^4}{10^3} = 40 \text{ watts}$$

and this is the total power.

Example 3.—A 250 volt 500 c/s motor takes 1kW at a power factor of 0.8 lagging.

(i) What current does it take?

(ii) What condenser must be placed in parallel to bring the power factor to unity?

(iii) What will then be the total supply current?

$$(a) \quad 1000 = EI \cos \varphi = 250 \times I \times 0.8.$$

$$\therefore I = 5 \text{ amps. } \textit{Ans. (i)}$$

The in-phase component of this current is

$$I \cos \varphi = 5 \times 0.8 = 4 \text{ amps}$$

and the 90° out-of-phase component is

$$I \sin \varphi = I \sqrt{1 - \cos^2 \varphi} = 5 \sqrt{1 - 0.64} = 3 \text{ amps.}$$

(b) To bring the power factor to unity, a condenser must be added that will take a current of 3 amps, 90° ahead of the voltage.

It must therefore have a reactance of $\frac{250}{3}$ ohms.

$$\therefore \frac{1}{\omega C} = \frac{10^6}{2\pi \times 500 \times C} = \frac{250}{3} \quad (\text{with } C \text{ in } \mu\text{F})$$

$$\begin{aligned} \therefore C &= \frac{3 \times 10^6}{250 \times 1000\pi} = \frac{12}{\pi} \\ &= 3.82 \mu\text{F} \quad \text{Ans. (ii)} \end{aligned}$$

(c) The total line current will then be merely the in-phase component—that is, 4 amps. *Ans. (iii)*

Note that by adding a condenser to increase the power factor, the total current has been decreased. Fig. 164 shows the vector diagrams with and without the condenser.

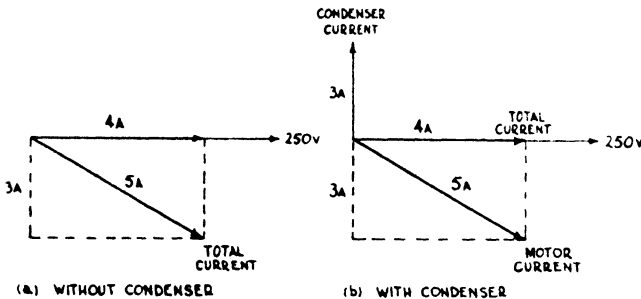


FIG. 164.—Effect of power-factor correcting condenser.

With large electrical installations, particular attention has to be paid to the power factor; the nearer it approaches unity, the smaller is the total current, and the smaller the loss in the distribution lines.

RESONANCE

In AC circuits (apart from those consisting of pure resistances), the current and voltage are usually out of phase. Under certain conditions, however, they may be in phase, and the circuit behaves as a resistance. This phenomenon is known as resonance: for a given circuit it would normally occur at only a finite number of frequencies—usually one, in the simplest cases. It is possible, however, to find circuits that resonate at all frequencies.

A two-terminal network containing reactance is said to resonate when the voltage across it and current through it are in phase.

This is the general definition of resonance; resonance should not be confused with the condition for maximum or minimum impedance, though this often occurs at or near resonance.

A few particular circuits will now be considered. It is normally required to calculate the frequency at which a given circuit will

resonate, though it is also often necessary to calculate the value of one or more of the components that will make a circuit resonate at a given frequency. The impedance at resonance is important and will be found in each case. The resonant frequency is denoted by f_0 , and the corresponding angular velocity by ω_0 .

General rules for finding the condition for resonance

To find the condition for resonance, it is necessary simply to write down the impedance Z , and to state the condition that this shall be resistive (*i.e.*, real). This can be done in a variety of ways, all of which are worth bearing in mind.

If Z is in the form $[r, \theta]$, the resonant condition is $\theta = 0$.

If Z is in the form $R + jX$, the resonant condition is $X = 0$.

If $Y = Z^{-1}$ is in the form $G + jB$, the resonant condition is $B = 0$.

If Z is in the form $\frac{A + jB}{C + jD}$, the resonant condition is $\frac{B}{A} = \frac{D}{C}$.

(This last condition is equivalent to saying that the numerator and denominator have equal angles and hence that the angle of Z is 0.) From the condition for resonance, the resonant frequency can be calculated.

Series resonance

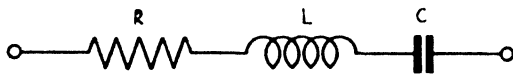


FIG. 165.—Series resonant circuit.

In Fig. 165, the impedance is:—

$$\begin{aligned} Z &= R + j\omega L - \frac{j}{\omega C} \\ &= R + j\left(\omega L - \frac{1}{\omega C}\right) \end{aligned} \quad (19)$$

The condition for resonance is:—

$$\begin{aligned} \omega L - \frac{1}{\omega C} &= 0 \\ \therefore \omega^2 &= \frac{1}{LC} \\ \text{Thus } \omega &= \omega_0 = \frac{1}{\sqrt{LC}}, \text{ or } f = f_0 = \frac{1}{2\pi\sqrt{LC}} \end{aligned} \quad (20)$$

From equation 19, it can be seen that the impedance at resonance (when $X = 0$) is equal to R .

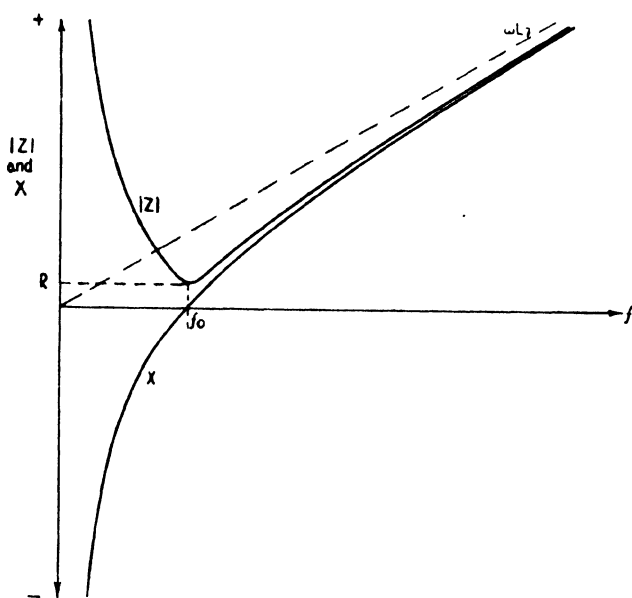


FIG. 166.—Variation of impedance and reactance with frequency for a series circuit.

Note that at any other frequency, the magnitude of the impedance is :—

$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} \quad (21)$$

which is always greater than R . Hence the impedance is a *minimum* at resonance. Fig. 166 shows how the impedance and reactance vary with frequency.

Voltages in series resonance circuits

Let a voltage E be applied to the above circuit at its resonant frequency. Consider the voltage across the condenser (E_c) or inductance (E_L); this is calculated from the total current.

$$I = \frac{E}{R}, \text{ and } E_L = I \times \omega_0 L$$

$$\therefore E_L = E \times \frac{\omega_0 L}{R}$$

Denote $\frac{\omega_0 L}{R}$ by the letter Q .

$$\text{Then } E_L = Q \times E$$

Similarly, $E_o = \frac{I}{\omega_o C} = I\omega_o L$, since, at resonance, $\frac{1}{\omega_o C} = \omega_o L$

$$\therefore E_o = E_L = Q \times E \quad (22)$$

$Q = \frac{\omega_o L}{R}$ may often be very large; if R is the resistance of the inductance only, Q may have values up to several hundred. Hence the voltage across the inductance or condenser may be several hundred times the voltage across the whole circuit. This important property of series resonant circuits is of wide application in communication engineering, as it provides a simple means of discriminating between different frequencies. If a constant voltage at

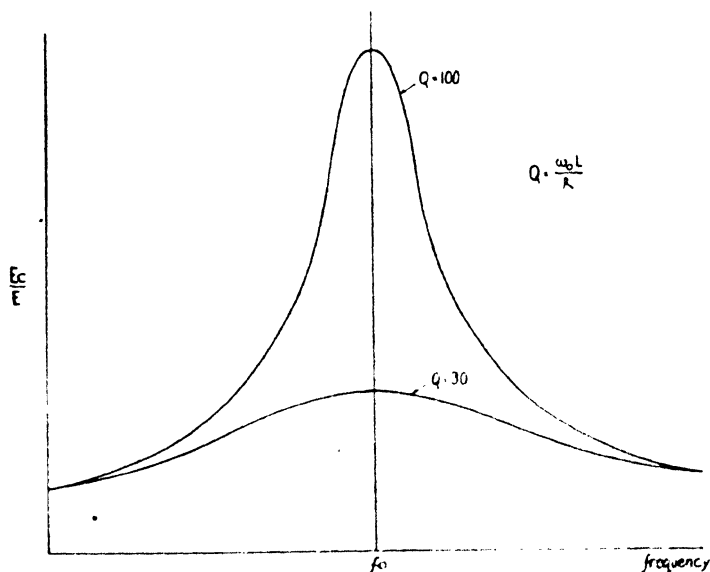


FIG. 167.—Variation with frequency of voltage across condenser of Fig. 165 for constant applied voltage.

varying frequency is applied to the circuit, the voltage across, say, the condenser will reach a maximum just below the resonant frequency, but if Q is large the difference between the two frequencies is small. Fig. 167 shows the variation of $\frac{E_o}{E}$ with frequency.

$$\begin{aligned} \text{The ratio } \frac{E_o}{E} &= \frac{|\text{condenser impedance}|}{|\text{total impedance}|} \\ &= \frac{1}{\omega C \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} \end{aligned}$$

Let this equal n . The maximum value of n^2 will occur at the same frequency as that of n .

$$\begin{aligned} \therefore \quad \eta^2 &= \frac{1}{\omega^2 C^2 \left(R^2 + \omega^2 L^2 - \frac{2L}{C} + \frac{1}{\omega^2 C^2} \right)} \\ &= \frac{1}{\omega^2 C^2 \left(R^2 - \frac{2L}{C} \right) + \omega^4 L^2 C^2 + 1} \end{aligned}$$

To find the frequency that makes η^2 a maximum, differentiate (for simplicity, with respect to ω^2) and put $\frac{d(\eta^2)}{d(\omega^2)} = 0$.

$$\frac{d(\eta^2)}{d(\omega^2)} = \frac{- [C^2 (R^2 - \frac{2L}{C}) + 2\omega^2 L^2 C^2]}{[\omega^2 C^2 (R^2 - \frac{2L}{C}) + \omega^4 L^2 C^2 + 1]^2}$$

$$\therefore \quad 2\omega^2 L^2 C^2 = -C^2 \left(R^2 - \frac{2L}{C} \right)$$

$$\therefore \quad \omega^2 L^2 = \frac{L}{C} - \frac{R^2}{2}$$

$$\begin{aligned} \therefore \quad \omega^2 &= \frac{1}{LC} - \frac{R^2}{2L^2} \\ &= \omega_0^2 - \frac{R^2}{2L^2} = \omega_0^2 \left(1 - \frac{R^2}{2\omega_0^2 L^2} \right) \\ &= \omega_0^2 \left(1 - \frac{1}{2Q^2} \right) \text{ since } Q = \frac{\omega_0 L}{R} \end{aligned}$$

$$\therefore \quad \omega = \omega_0 \cdot \sqrt{1 - \frac{1}{2Q^2}}, \quad \therefore f = f_0 \cdot \sqrt{1 - \frac{1}{2Q^2}} \quad (23)$$

f is therefore less than f_0 ; but if Q is large (>10 , say), the term $\frac{1}{2Q^2} \cong 0$ and $f \cong f_0$.

Parallel resonance (anti-resonance)

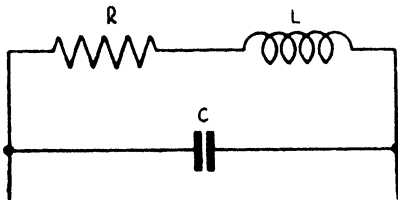


FIG. 168.—Parallel circuit containing R , L and C .

The case of a pure inductance in parallel with a condenser is not considered, as in practice an inductance always possesses resistance. The circuit to be dealt with is shown in Fig. 168.

The impedance is given by :—

$$\frac{1}{Z} = \frac{1}{R + j\omega L} + j\omega C$$

The simplest way of determining the condition for resonance is by rationalisation.

$$\frac{1}{Z} = \frac{R - j\omega L}{(R + j\omega L)(R - j\omega L)} + j\omega C$$

$$\therefore Y = Z^{-1} = \frac{R}{R^2 + \omega^2 L^2} + j\omega \left[C - \frac{L}{R^2 + \omega^2 L^2} \right] \quad (24)$$

The condition for resonance is that the “ j ” term is equal to zero.

$$\text{This will occur when } C = \frac{L}{R^2 + \omega^2 L^2} \quad (25)$$

$$R^2 + \omega^2 L^2 = \frac{L}{C}$$

$$\omega^2 L^2 = \frac{L}{C} - R^2$$

$$\omega^2 = \frac{1}{LC} - \frac{R^2}{L^2}$$

$$\omega = \omega_0 = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$\text{and} \quad f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} \quad (26)$$

The impedance at resonance is given by equation 24 when the “ j ” term is put equal to zero.

$$\begin{aligned} \therefore \frac{1}{Z} &= \frac{R}{R^2 + \omega_0^2 L^2} \\ &= \frac{R}{\frac{L}{C}} \quad (\text{from equation 25}) \end{aligned}$$

$$\therefore Z = \frac{L}{CR} \quad \text{at resonance} \quad (27)$$

Note that if R is very small, Z will be very large, tending to infinity as R approaches zero.

If R is small, there is a useful approximation to this formula or Z .

$$\text{For} \quad \frac{1}{Z} = \frac{R}{R^2 + \omega_0^2 L^2}, \text{ as above,}$$

$$\therefore Z = R + \frac{\omega_0^2 L^2}{R}$$

Neglecting the first term :—

$$Z \simeq \frac{\omega_0^2 L^2}{R} = \frac{\omega_0 L}{R} \cdot \omega_0 L = Q \cdot \omega_0 L \quad (28)$$

where $Q = \frac{\omega_0 L}{R}$, as for series resonance. If Q is large, it can be seen that the impedance of the circuit at resonance is much greater than the impedance of the inductance.

It can be shown that, if Q is large, $|Z|$ is a maximum at resonance. In theory, the maximum value occurs at a frequency

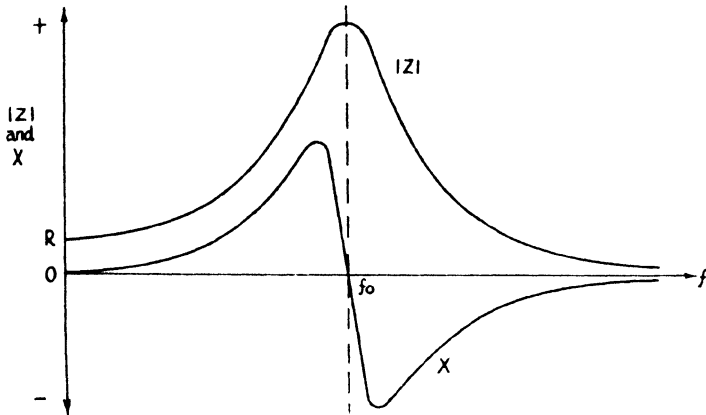


FIG. 169.—Variation of impedance and reactance for a parallel circuit.

just above the resonant frequency, but the difference between the two frequencies is small. Fig. 169 shows how the impedance and reactance vary with frequency.

Currents in parallel resonant circuit

Let the total current through the circuit be I at the resonant frequency; consider the current through the condenser (I_C) or inductance (I_L).

This can be found from the voltage across the circuit, which is equal to the product of I and the impedance at resonance,

$$\begin{aligned} \text{i.e.,} \quad E &= I \cdot \frac{L}{CR} \\ I_C &= E \cdot \omega_0 C = \frac{IL}{CR} \times \omega_0 C = I \times \frac{\omega_0 L}{R} \\ &= Q \cdot I \end{aligned} \quad (29)$$

If Q is large, it can be shown that I_L is also roughly equal to $Q \times I$.

Hence in a parallel resonant circuit, the current through either arm is much greater than the total current.

A few examples will illustrate the application of these formulae.

Example 1.—Find the series and parallel resonant frequencies of a condenser of $0.005 \mu\text{F}$ and an inductance of 100 mH whose resistance is 500 ohms . Find also the impedance at resonance of the parallel circuit.

Here $L = 0.1$, $C = 5 \times 10^{-9}$, and $R = 500$

For series resonance,

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{10^{-1} \times 5 \times 10^{-9}}} = \frac{10^5}{2\pi\sqrt{5}}$$

$$= 7119 \text{ c/s} \quad \text{Ans. (i)}$$

For parallel resonance,

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} = \frac{1}{2\pi} \sqrt{\frac{10^{10}}{5} - 25 \times 10^4 \times 10^2}$$

$$= \frac{1}{2\pi} \sqrt{10^8 (2000 - 25)} = \frac{10^4}{2\pi} \sqrt{1975}$$

$$= 7073 \text{ c/s} \quad \text{Ans. (ii)}$$

The impedance at resonance = $\frac{L}{CR}$

$$= \frac{10^9}{10 \times 5 \times 500} = \frac{10^6}{25} = 40,000 \text{ ohms.} \quad \text{Ans. (iii)}$$

Note that although R is not small (Q is about 10), the difference between the two resonant frequencies is small.

Example 2.—A coil of inductance 1 H and resistance 300 ohms resonates with a series condenser at 500 c/s . What voltage will appear across the condenser if 10 volts is applied to the circuit (a) at 500 c/s ? (b) at 1000 c/s ?

The value of the condenser is not required, and need not be found for this problem.

At 500 c/s , the reactance of the inductance will be $j2\pi fL = j1000\pi$. The condenser must therefore have a reactance of $-j1000\pi$ at 500 c/s .

$$Q = \frac{2\pi fL}{R} = \frac{1000\pi}{300}$$

If 10 volts is applied to the whole circuit, the voltage across C will be:—

$$10 \times Q = \frac{1000\pi}{30} = 104.5 \text{ volts.} \quad \text{Ans. (i)}$$

At 1000 c/s , the reactance of L will have doubled, $= j2000\pi$ and the reactance of C will have halved, $= -j500\pi$

$$\therefore \text{total impedance} = 300 + j2000\pi - j500\pi = 300 + j1500\pi$$

$$= 300 (1 + j5\pi)$$

$$\therefore |Z| = 300 \sqrt{1 + 25\pi^2}$$

The voltage across the condenser will be equal to the product of total current and impedance of the condenser, *i.e.*, $\frac{10}{|Z|} \times 500\pi$

$$= \frac{10 \times 500\pi}{300\sqrt{1 + 25\pi^2}} = \frac{50\pi}{3\sqrt{1 + 246}} = \frac{50\pi}{3\sqrt{247}} = 3.33 \text{ volts Ans. (ii)}$$

This example gives a good illustration of the "magnification" effect of a series circuit.

Selectivity of resonant circuits

Series and parallel resonant circuits can be used to pick out signals at their resonant frequency. Consider Fig. 170.

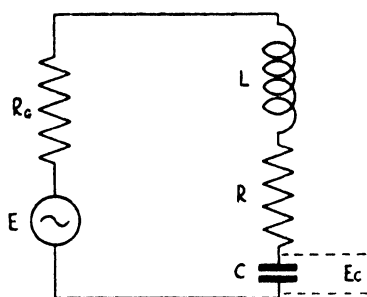


FIG. 170.—Generator connected to series resonant circuit.

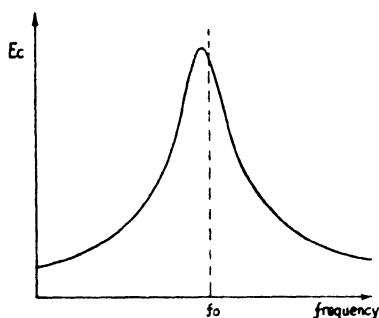


FIG. 171.—Variation with frequency of voltage across condenser of Fig. 165 for constant applied voltage, when generator impedance is low.

Suppose that a generator of constant voltage E and internal impedance R_g is connected to a series circuit, and that the frequency of E is varied. Consider the voltage E_c across C . As the frequency is varied, the total impedance of L , C and R will vary; if R_g is always small compared with this impedance, the voltage across L , C and R will be approximately equal to E . At resonance E_c will be approximately equal to $Q \cdot E$. The variation of E_c with f is shown in Fig. 171. It can be seen that it reaches a sharp maximum just below resonance—the circuit is "selective".

Consider the same circuit but with R_g large. If the impedance of L , C and R is always very small compared with R_g , the current in the circuit will be approximately equal to $\frac{E}{R_g}$ at all frequencies. In this case, the voltage across C will drop steadily with frequency, as shown in Fig. 172.

This circuit is clearly not selective. It will thus be seen that a series circuit will operate satisfactorily as a selective circuit

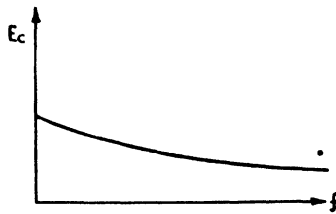


FIG. 172.—Variation with frequency of voltage across condenser of Fig. 165 for constant applied voltage, when generator impedance is high.

only if supplied from a generator having a low internal impedance.

Fig. 173 shows a parallel circuit. Consider the voltage E' across this circuit when it is connected to the generator. Suppose that E is kept constant and the frequency is varied. If R_g is small at all frequencies compared with the impedance of the parallel circuit, then E' will be approximately equal to E , and the circuit will not be selective. If, however, R_g is always large compared with the impedance of the circuit, then the current flowing will always be approximately equal to $\frac{E}{R_g}$. In this case, E' will be proportional to the impedance of the parallel circuit, and will therefore be a maximum at resonance as shown in Fig. 174.

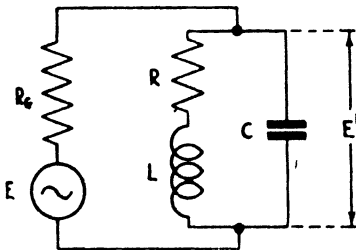


FIG. 173.—Generator connected to parallel resonant circuit.

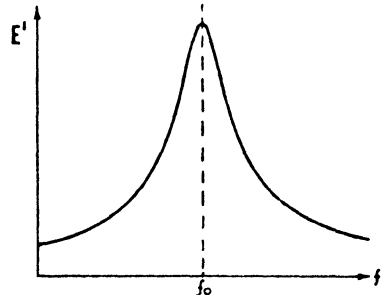


FIG. 174.—Voltage across parallel resonant circuit.

Hence the parallel circuit is selective only if supplied from a generator having a high internal impedance.

Parallel circuit resonant at all frequencies

An example of a circuit that resonates at all frequencies will now be given. It is of wide application in the design of constant-impedance reactive networks. Consider the circuit shown in Fig. 175.

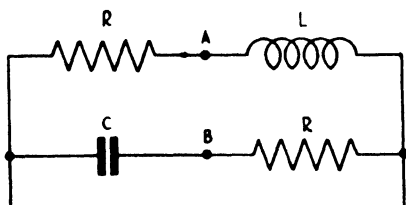


FIG. 175.—Parallel circuit with equal resistance in both arms.

Note that the two resistances are equal. The condition of resonance will first be obtained.

$$\frac{1}{Z} = \frac{1}{R + j\omega L} + \frac{1}{R - \frac{j}{\omega C}} = \frac{R - \frac{j}{\omega C} + R + j\omega L}{(R + j\omega L)\left(R - \frac{j}{\omega C}\right)}$$

$$\therefore \frac{1}{Z} = \frac{2R + j\left(\omega L - \frac{1}{\omega C}\right)}{R^2 + \frac{L}{C} + jR\left(\omega L - \frac{1}{\omega C}\right)} \quad (30)$$

The condition for resonance is that the numerator and denominator should have the same angle.

$$i.e. \quad \frac{\left(\omega L - \frac{1}{\omega C}\right)}{2R} = \frac{R\left(\omega L - \frac{1}{\omega C}\right)}{R^2 + \frac{L}{C}}$$

Cross-multiplying :—

$$\left(\omega L - \frac{1}{\omega C}\right)\left(R^2 + \frac{L}{C}\right) = 2R^2\left(\omega L - \frac{1}{\omega C}\right)$$

$$\therefore \left(\omega L - \frac{1}{\omega C}\right)\left(R^2 - \frac{L}{C}\right) = 0$$

$$\text{This is satisfied if } \omega L = \frac{1}{\omega C} \quad (31)$$

$$\text{or} \quad R^2 = \frac{L}{C} \quad (32)$$

Consider equation 31. This gives the normal frequency of resonance. At this frequency the impedance, from equation 30,

will be $\frac{R^2 + \frac{L}{C}}{2R} = \frac{R}{2} + \frac{L}{2CR}$. This result is of no particular interest.

Consider equation 32. This is a relationship between the components of the circuit that would not normally be satisfied. It does not, however, involve frequency, and hence if it were

satisfied the circuit would be resonant at all frequencies; for if $R^2 = \frac{L}{C}$, equation 30 can be written as:—

$$Z = \frac{R^2 + R^2 + Rj\left(\omega L - \frac{1}{\omega C}\right)}{2R + j\left(\omega L - \frac{1}{\omega C}\right)} = \frac{R\left[2R + j\left(\omega L - \frac{1}{\omega C}\right)\right]}{2R + j\left(\omega L - \frac{1}{\omega C}\right)} = R \quad (33)$$

Hence if $R^2 = \frac{L}{C}$, the impedance of this circuit is equal to R at all frequencies. It can now be seen why this circuit is so important—for although it contains reactances, its impedance is constant and resistive at all frequencies.

It is worth noting that $R^2 = \frac{L}{C}$ is the condition that the bridge formed by the four components should be balanced; hence if this is true there will be no voltage across AB (see Fig. 175, p. 221).

The same results hold if any two impedances Z_1 and Z_2 are substituted for L and C provided that $Z_1 Z_2 = R^2$. Impedances that satisfy this condition are known as “inverse impedances with respect to R ”.

Reactance sketches

Reactance sketches may be employed to determine the resonant frequency of a network. The impedance (Z) of any circuit may be written in the form:—

$$Z = R + jX \quad (34)$$

where R is the resistance and X the reactance.

The admittance (Y) of the circuit is defined as the reciprocal of the impedance and is also complex,

$$\text{i.e.} \quad Y = \frac{1}{Z} = G + jB \quad (35)$$

where G is the “conductance” and B the “susceptance” of the circuit. (The susceptance is sometimes represented by S instead of B .)

From equations 34 and 35:—

$$G + jB = \frac{1}{R + jX} = \frac{R - jX}{R^2 + X^2}$$

$$\therefore \quad G = \frac{R}{R^2 + X^2} \quad (36)$$

$$\text{and} \quad B = \frac{-X}{R^2 + X^2} \quad (37)$$

$$\text{Also} \quad R + jX = \frac{1}{G + jB} = \frac{G - jB}{G^2 + B^2}$$

$$\therefore R = \frac{G}{G^2 + B^2} \tag{38}$$

$$\text{and } X = \frac{-B}{G^2 + B^2} \tag{39}$$

In the case of series resonance, the condition for resonance was taken as the condition for zero reactance, *i.e.* $X = 0$; and this condition gives series resonance whether resistance is present or not. From equation 37, the susceptance at resonance is zero unless the resistance of the series circuit is also zero.

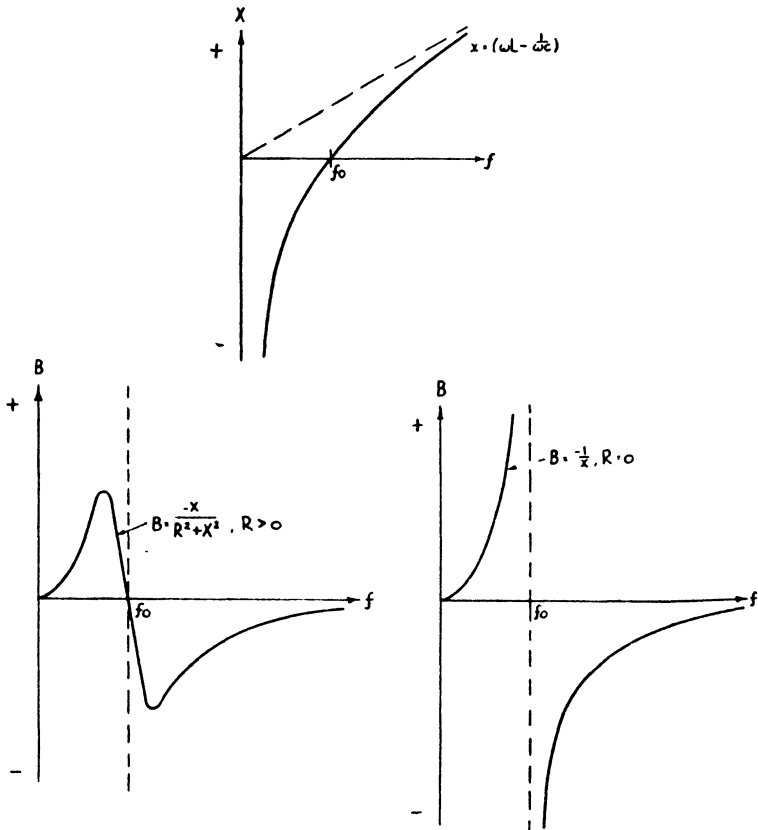


FIG. 176.—Variation of reactance and susceptance with frequency for a series circuit.

In the case of parallel resonance, the condition for resonance was found by equating to zero the imaginary part of $\frac{1}{Z}$; that is, the condition is one of zero susceptance. This condition $B = 0$ gives parallel resonance whether resistance is present or not.

The general shape of these curves (Figs. 176 and 177) should be

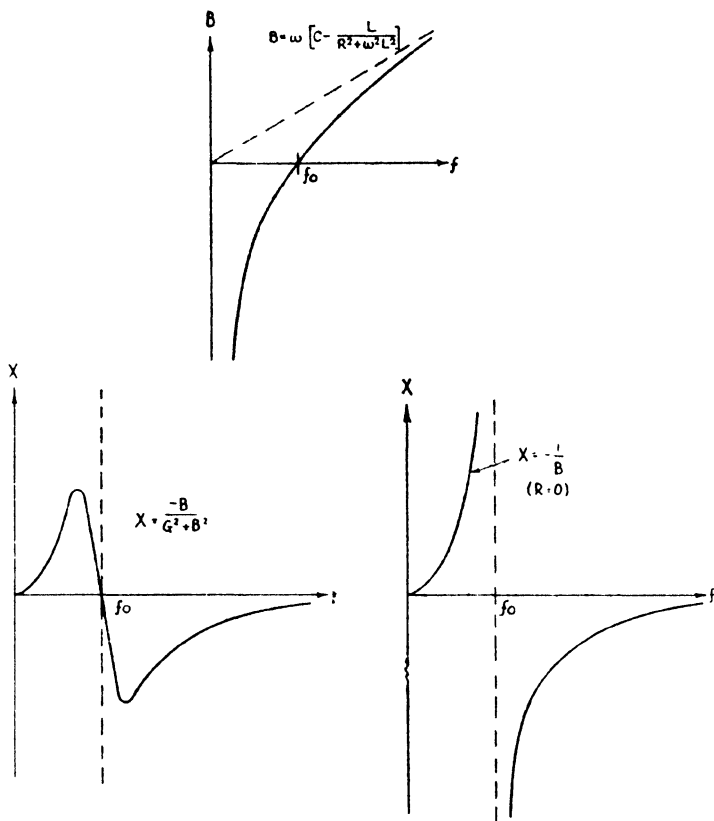


FIG. 177.—Variation of susceptance and reactance with frequency for a parallel circuit.

memorised as they are extremely useful in exploring the behaviour of filters and other complex networks. As an example of the use to which these curves can be put, consider a circuit that has more than one resonant frequency.

Circuit having two resonant frequencies

Consider the circuit in Fig. 178. If this circuit is treated by the normal method:—

$$Z = \frac{\frac{-j}{\omega C} \left\{ R + j \left(\omega L - \frac{1}{\omega C} \right) \right\}}{R + j \left(\omega L - \frac{2}{\omega C} \right)}$$

$$\begin{aligned}
 &= \frac{-j}{\omega C} [\omega CR + j(\omega^2 LC - 1)] \\
 &= \frac{-j}{\omega C} [\omega CR + j(\omega^2 LC - 1)] [\omega CR - j(\omega^2 LC - 2)] \\
 &= \frac{\omega^2 C^2 R^2 + (\omega^2 LC - 2)^2}{\omega^2 C^2 R^2 + (\omega^2 LC - 2)^2}
 \end{aligned}$$

The reactance is given by :—

$$X = \frac{-1}{\omega C} [\omega^2 C^2 R^2 + (\omega^2 LC - 1)(\omega^2 LC - 2)] \tag{40}$$

This is zero if :—

$$\omega^4 L^2 C^2 - \omega^2 (3LC - C^2 R^2) + 2 = 0$$

This has two positive roots :—

$$\omega = \sqrt{\frac{(3L - CR^2) \pm \sqrt{(3L - CR^2)^2 - 8L^2}}{2L^2 C}} \tag{41}$$

Thus the circuit has two resonant frequencies, at both of which the reactance is zero. It can be shown that where a circuit has

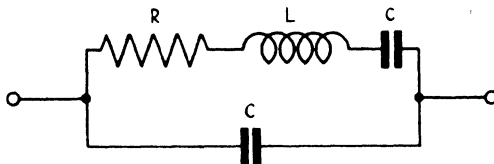


FIG. 178.—Simple circuit having two resonant frequencies.

more than one resonant frequency, series and parallel resonances must occur alternately. This will not be proved, but a method for exploring the resonances by means of reactances sketches will be given.

Consider the circuit of Fig. 178, but suppose that the resistance $R = 0$.

Fig. 179 shows how the reactance-frequency sketch is built up ; (a) and (b) show the susceptance-frequency sketches for the two arms of the circuit, and (c) shows the susceptance sketch of the whole circuit, being the sum of the susceptances of the two parallel arms. Finally (d) shows the reactance-frequency sketch obtained from (c) by the relationship $X = -\frac{1}{B}$ which holds for pure reactances. The frequency f_1 , for which the reactance is zero, is a series resonance ; the frequency f_2 , which gives infinite reactance, is a parallel resonance. The presence of a small resistance in the circuit will in general alter the *value* of these resonant frequencies, but it will not alter the *order* in which they occur.

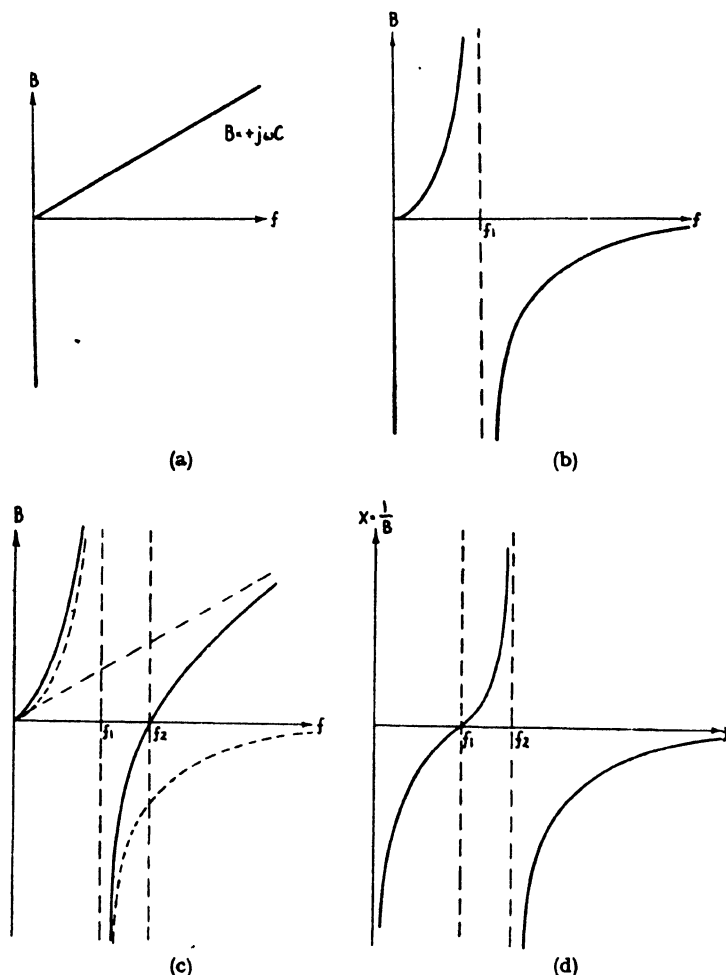


FIG. 179.—Method for obtaining the reactance frequency curves of the circuit of Fig. 178 (assuming $R = 0$).

Thus the lower frequency :—

$$f_1 = \frac{1}{2\pi} \sqrt{\frac{(3L - CR^2) - \sqrt{(3L - CR^2)^2 - 8L^2}}{2L^2C}} \quad (42)$$

gives series resonance, and the upper frequency :—

$$f_2 = \frac{1}{2\pi} \sqrt{\frac{(3L - CR^2) + \sqrt{(3L - CR^2)^2 - 8L^2}}{2L^2C}} \quad (43)$$

gives parallel resonance.

Summary of conditions for resonance, for maximum and minimum impedance, and for maximum voltages and currents

$$\omega_0 = 2\pi \times \text{series resonant frequency} = \frac{1}{\sqrt{L_0 C_0}}$$

L_0 = value of inductance (L) to give series resonant condition.

C_0 = value of capacity (C) to give series resonant condition.

$$Q = \frac{\omega_0 L_0}{R}$$

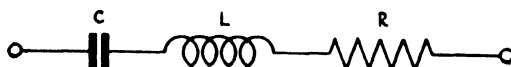


FIG. 180.—Series resonant circuit.

1. *Series circuit, with R assumed constant (Q varies with ω).—*

(a) Condition for resonance :—

$$\omega^2 LC = 1 \tag{44}$$

(b) Condition for minimum impedance on varying L , C or ω :—

$$\omega^2 LC = 1 \tag{45}$$

(c) Condition for maximum voltage across L , with constant applied voltage :—

(i) If ω be varied :

$$\omega^2 = \frac{1}{LC \left(1 + \frac{R^2 C}{2L}\right)} = \omega_0^2 \cdot \left(1 + \frac{1}{2Q^2}\right)^{-1} \tag{46}$$

(ii) If L be varied :

$$L = \frac{1}{\omega^2 C} + CR^2 = L_0 \left(1 + \frac{1}{Q^2}\right) \tag{47}$$

(iii) If C be varied :

$$C = \frac{1}{\omega^2 L} = C_0 \tag{48}^*$$

(d) Condition for maximum voltage across C , with constant applied voltage :—

(i) If ω be varied :

$$\omega^2 = \frac{1}{LC} - \frac{R^2}{2L^2} = \omega_0^2 \cdot \left(1 - \frac{1}{2Q^2}\right) \tag{49}$$

(ii) If L be varied :

$$L = \frac{1}{\omega^2 C} = L_0 \tag{50}^*$$

* *i.e.*, as for resonance.

(iii) If C be varied :

$$C = \frac{L}{R^2 + \omega^2 L^2} = C_0 \left(1 + \frac{1}{Q^2}\right)^{-1} \quad (51)$$

2. Series circuit, with Q assumed constant (R varies with ω).—

(a) Condition for resonance :—

$$\omega^2 LC = 1 \quad (52)$$

(b) Condition for minimum impedance :—

(i) If ω be varied :

$$\omega^2 = \frac{1}{LC} \cdot \left(1 + \frac{1}{Q^2}\right)^{-1} = \omega_0^2 \left(1 + \frac{1}{Q^2}\right)^{-1} \quad (53)$$

(ii) If L be varied :

$$L = \frac{1}{\omega^2 C} \left(1 + \frac{1}{Q^2}\right)^{-1} = L_0 \left(1 + \frac{1}{Q^2}\right)^{-1} \quad (54)$$

(iii) If C be varied :

$$C = \frac{1}{\omega^2 L} = C_0 \quad (55)^*$$

(c) Condition for maximum voltage across L , with constant applied voltage :—(i) If ω be varied :

$$\omega^2 = \frac{1}{LC} = \omega_0^2 \quad (56)^*$$

(ii) If L be varied :

$$L = \frac{1}{\omega^2 C} = L_0 \quad (57)^*$$

(iii) If C be varied :

$$C = \frac{1}{\omega^2 L} = C_0 \quad (58)^*$$

(d) Condition for maximum voltage across C , with constant applied voltage :—(i) If ω be varied :

$$\omega^2 = \frac{1}{LC} \left(1 + \frac{1}{Q^2}\right)^{-1} = \omega_0^2 \left(1 + \frac{1}{Q^2}\right)^{-1} \quad (59)$$

(ii) If L be varied :

$$L = \frac{1}{\omega^2 C} \left(1 + \frac{1}{Q^2}\right)^{-1} = L_0 \left(1 + \frac{1}{Q^2}\right)^{-1} \quad (60)$$

(iii) If C be varied :

$$C = \frac{1}{\omega^2 L} \left(1 + \frac{1}{Q^2}\right)^{-1} = C_0 \left(1 + \frac{1}{Q^2}\right)^{-1} \quad (61)$$

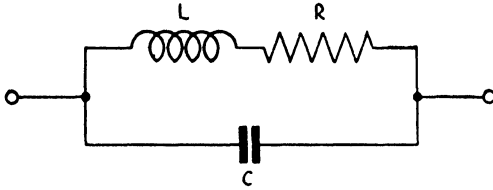


FIG. 181.—Parallel resonant circuit.

3. Parallel circuit, with R assumed constant (Q varies with ω).—

(a) Condition for resonance :—

$$\omega^2 = \frac{1}{LC} - \frac{R^2}{L^2} = \omega_0^2 \left(1 - \frac{1}{Q^2}\right) \quad (62)$$

(b) Condition for maximum impedance :—

(i) If ω be varied :

$$\omega^2 = \frac{1}{LC} \sqrt{1 + \frac{2R^2C}{L}} - \frac{R^2}{L^2} = \omega_0^2 \left[\sqrt{1 + \frac{2}{Q^2}} - \frac{1}{Q^2} \right] \quad (63)$$

(ii) If L be varied :

$$L = \frac{1}{2\omega^2C} + \frac{1}{2\omega} \sqrt{\frac{1}{\omega^2C^2} + 4R^2} = L_0 \cdot \frac{1}{2} \left[\sqrt{1 + \frac{4}{Q^2}} + 1 \right] \quad (64)$$

(iii) If C be varied :

$$C = \frac{L}{R^2 + \omega^2L^2} = C_0 \cdot \left(1 + \frac{1}{Q^2}\right)^{-1} \quad (65)^*$$

(c) Condition for maximum current through L , with constant total current :—

(i) If ω be varied :

$$\omega^2 = \frac{1}{LC} - \frac{R^2}{2L^2} = \omega_0^2 \cdot \left(1 - \frac{1}{2Q^2}\right) \quad (66)$$

(ii) If L be varied :

$$L = \frac{1}{\omega^2C} = L_0 \quad (67)$$

(iii) If C be varied :

$$C = \frac{L}{R^2 + \omega^2L^2} = C_0 \cdot \left(1 + \frac{1}{Q^2}\right)^{-1} \quad (68)^*$$

(d) Condition for maximum current through C , with constant total current :—

(i) If ω be varied :

$$\omega^2 = \omega_0^2 \cdot \frac{1}{2} \left[\sqrt{1 + \frac{2}{Q^2}} + 1 \right] \quad (69)$$

(ii) If L be varied :

$$L = L_0 \cdot \frac{1}{2} \left[\sqrt{1 + \frac{4}{Q^2}} + 1 \right] \quad (70)$$

* i.e., as for resonance.

(iii) If C be varied :

$$C = \frac{1}{\omega^2 L} = C_0 \quad (71)$$

4. *Parallel circuit, with Q assumed constant (R varies with ω).—*

(a) Condition for resonance :—

$$\omega^2 = \frac{1}{LC} - \frac{R^2}{L^2} = \omega_0^2 \left(1 - \frac{1}{Q^2}\right) \quad (72)$$

(b) Condition for maximum impedance :—

(i) If ω be varied :

$$\omega^2 = \frac{1}{LC} \left(1 + \frac{1}{Q^2}\right)^{-1} = \omega_0^2 \left(1 + \frac{1}{Q^2}\right)^{-1} \quad (73)$$

(ii) If L be varied :

$$L = \frac{1}{\omega^2 C} = L_0 \quad (74)$$

(iii) If C be varied :

$$C = \frac{L}{R^2 + \omega^2 L^2} = C_0 \left(1 + \frac{1}{Q^2}\right)^{-1} \quad (75)^*$$

(c) Condition for maximum current through L , with constant total current :—(i) If ω be varied :

$$\omega^2 = \frac{1}{LC} \left(1 + \frac{1}{Q^2}\right)^{-1} = \omega_0^2 \left(1 + \frac{1}{Q^2}\right)^{-1} \quad (76)$$

(ii) If L be varied :

$$L = \frac{1}{\omega^2 C} \left(1 + \frac{1}{Q^2}\right)^{-1} = L_0 \left(1 + \frac{1}{Q^2}\right)^{-1} \quad (77)^*$$

(iii) If C be varied :

$$C = \frac{1}{\omega^2 L} \left(1 + \frac{1}{Q^2}\right)^{-1} = C_0 \left(1 + \frac{1}{Q^2}\right)^{-1} \quad (78)^*$$

(d) Condition for maximum current through C , with constant total current :—(i) If ω be varied :

$$\omega^2 = \frac{1}{LC} = \omega_0^2 \quad (79)$$

(ii) If L be varied :

$$L = \frac{1}{\omega^2 C} = L_0 \quad (80)$$

(iii) If C be varied :

$$C = \frac{1}{\omega^2 L} = C_0 \quad (81)$$

* *i.e.*, as for resonance.

CHAPTER 5

AC CIRCUITS

GENERAL NETWORK THEOREMS

An "electrical network" may be defined as being *any electrical circuit containing impedances and generators*. A simple network may consist of a single closed circuit (or mesh), as in Fig. 182, whereas more complex networks may consist of a number of meshes that are interdependent, as in Fig. 183.

The current through, and the voltage across, any impedance of a network may be determined by the application of Ohm's and Kirchhoff's Laws, but, in the case of a complex network, the process

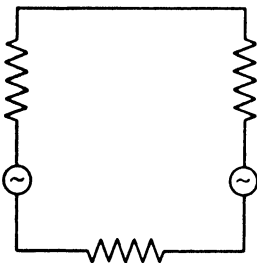


FIG. 182.—Simple electrical network (single mesh).

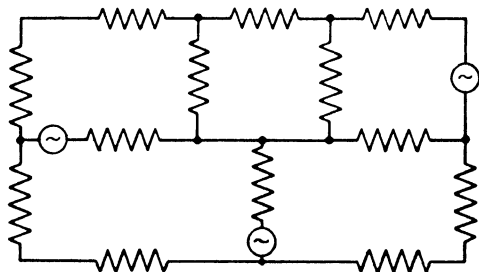


FIG. 183.—More complex electrical network.

is lengthy and tedious, owing to the need for solving a large number of simultaneous equations. A number of network theorems have therefore been formulated to provide certain simplifications in the calculations.

Certain of these theorems have universal application, whereas others are restricted to circuits containing "linear" impedances. A "linear impedance" may be defined as *any impedance that obeys Ohm's Law*; that is to say, any impedance for which the potential drop across it is proportional to the current flowing through it. Resistances, inductances and condensers fall into this category, whereas metal rectifiers and thermionic valves do not.

Superposition theorem

If a network of linear impedances contains more than one generator, the current flowing at any point is the vector sum of the currents that would flow at that point if each generator were considered separately

with all other generators replaced at the time by impedances equal to their internal impedances.

This follows from the linearity of Ohm's Law. For suppose the network consists of n meshes; Kirchhoff's Laws will give a set of n linear equations such as:—

$$E_1 = Z_{11}I_1 + Z_{12}I_2 + \dots + Z_{1n}I_n$$

$$E_2 = Z_{21}I_1 + Z_{22}I_2 + \dots + Z_{2n}I_n$$

.....

$$E_n = Z_{n1}I_1 + Z_{n2}I_2 + \dots + Z_{nn}I_n$$

These may be solved, giving a set of relations:—

$$I_1 = A_{11}E_1 + A_{12}E_2 + \dots + A_{1n}E_n$$

$$I_2 = A_{21}E_1 + A_{22}E_2 + \dots + A_{2n}E_n$$

.....

$$I_n = A_{n1}E_1 + A_{n2}E_2 + \dots + A_{nn}E_n$$

where the A s are coefficients depending on the Z s, but independent of the E s and I s.

The theorem follows, from the linearity of these equations.

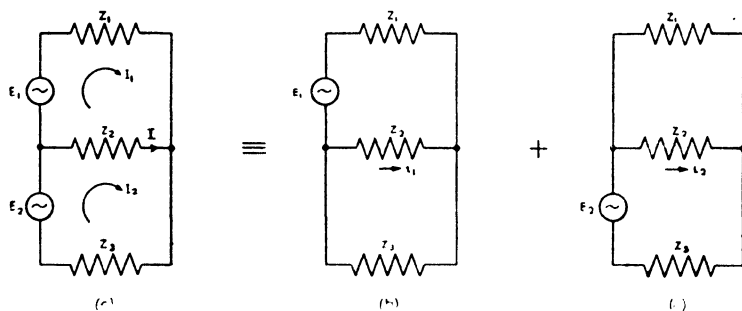


FIG. 184.—Equivalent circuits illustrating superposition theorem.

Fig. 184 shows the superposition theorem applied to solve a simple problem. It is required to find the current I flowing in the impedance Z_2 . This will first be solved by the application of Kirchhoff's Laws.

(a) *By Kirchhoff's Laws.*—Considering cyclic currents I_1 and I_2 as in Fig. 184a, the required current $I = I_2 - I_1$, and Kirchhoff's first law is satisfied.

By Kirchhoff's second law:—

$$I_1(Z_1 + Z_2) - I_2Z_2 = E_1$$

and

$$-I_1Z_2 + I_2(Z_2 + Z_3) = E_2$$

Solving these equations gives:—

$$I_1 = \frac{E_1(Z_2 + Z_3) + E_2Z_2}{Z_2Z_3 + Z_2Z_1 + Z_1Z_2}$$

$$I_2 = \frac{E_1 Z_2 + E_2(Z_1 + Z_2)}{Z_2 Z_3 + Z_3 Z_1 + Z_1 Z_2}$$

$$\therefore I = I_2 - I_1 = \frac{[E_1 Z_2 + E_2(Z_1 + Z_2)] - [E_1(Z_2 + Z_3) + E_2 Z_2]}{Z_2 Z_3 + Z_3 Z_1 + Z_1 Z_2}$$

$$\text{i.e. } I = \frac{E_2 Z_1 - E_1 Z_3}{Z_2 Z_3 + Z_3 Z_1 + Z_1 Z_2}$$

(b) By the superposition theorem (see Fig. 184, b and c).—

$$I = i_1 + i_2$$

$$\text{But } i_1 = \frac{-E_1}{Z_1 + \frac{Z_2 Z_3}{Z_2 + Z_3}} \times \frac{Z_3}{Z_2 + Z_3} = \frac{-E_1 Z_3}{Z_2 Z_3 + Z_3 Z_1 + Z_1 Z_2}$$

$$\text{and } i_2 = \frac{E_2}{Z_3 + \frac{Z_1 Z_2}{Z_1 + Z_2}} \times \frac{Z_1}{Z_1 + Z_2} = \frac{E_2 Z_1}{Z_2 Z_3 + Z_3 Z_1 + Z_1 Z_2}$$

$$\text{Therefore } I = i_1 + i_2 = \frac{E_2 Z_1 - E_1 Z_3}{Z_2 Z_3 + Z_3 Z_1 + Z_1 Z_2}$$

In this example there is little to choose between the two methods; but in a more complicated example the superposition method is often easier than the method using Kirchhoff's Laws.

Thévenin's theorem

The current in a load impedance connected to two terminals *a* and *b* of a network of impedances and generators is the same as if this load impedance were connected to a simple constant-voltage generator, whose EMF is the open-circuit voltage measured across *a* and *b*, and whose internal impedance is the impedance of the network looking back into the terminals *a* and *b* with all generators replaced by impedances equal to their internal impedances.

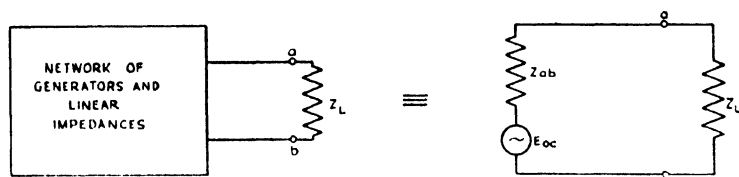


FIG. 185.—Equivalent circuits illustrating Thévenin's theorem.

Fig. 185 shows Thévenin's theorem (sometimes also called "Pollard's theorem") in diagrammatic form. E_{oc} is the open-circuit voltage across terminals *a b* (i.e. with Z_L disconnected), and Z_{ob} is the impedance measured looking into terminals *a b* with all generators replaced by impedances equal to their internal impedances.

Example.—A network consisting of generators and impedances has two output terminals (see Fig. 186a). The following observations are made at these terminals:—

- (a) Open-circuit voltage 100 volts;
- (b) current 2 amps with terminals short-circuited;
- (c) current 1.77 amps in a $10\ \Omega$ resistance connected across the terminals.

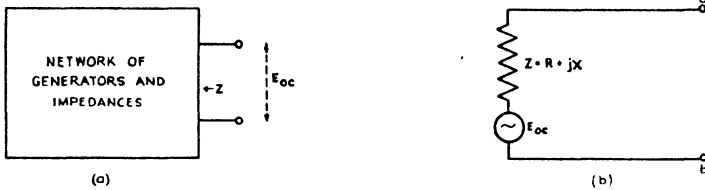


FIG. 186.—Example to illustrate use of Thévenin's theorem.

Find the current that will flow in a $50\ \Omega$ resistance connected across the terminals.

The first step is to establish the equivalent circuit. This, by Thévenin's theorem, is the generator of Fig. 186b, where $E_{oc} = 100$ volts by (a) above.

To find $Z = R + jX$, use the data (b) and (c).

$$(b) \text{ gives } \frac{100}{\sqrt{R^2 + X^2}} = 2$$

$$\therefore \frac{100^2}{4} = R^2 + X^2 \quad (i)$$

$$(c) \text{ gives } \frac{100}{\sqrt{(R + 10)^2 + X^2}} = 1.77$$

$$\therefore \frac{100^2}{3.132} = R^2 + X^2 + 20R + 100 \quad (ii)$$

$$\text{From (i) and (ii) } 20R + 100 = \frac{100^2}{3.132} - \frac{100^2}{4}$$

$$= 100^2 \times \frac{0.87}{4 \times 3.13}$$

$$\therefore R = \frac{500 \times 0.87}{4 \times 3.13} - 5$$

$$= 35 - 5$$

$$= 30 \text{ ohms}$$

$$\text{From (i) } R^2 + X^2 = 2500$$

$$\therefore X^2 = 2500 - 900 = 1600$$

$$\therefore X = 40 \text{ ohms}$$

$$\therefore Z = 30 + j40$$

With a resistive load of 50Ω ,

$$I = \frac{100}{\sqrt{80^2 + 40^2}} = \frac{100}{40\sqrt{5}} = 1.12 \text{ amps. Ans.}$$

Norton's theorem

The current in a load impedance connected to two terminals a and b of a network consisting of generators and impedances is the same as if this load impedance were connected to a constant-current generator, whose generated current is equal to the short-circuit current measured at a-b, and having infinite internal impedance, but placed in parallel with an impedance equal to the impedance of the network looking back into the terminals a and b with all generators replaced by impedances equal to their internal impedances.

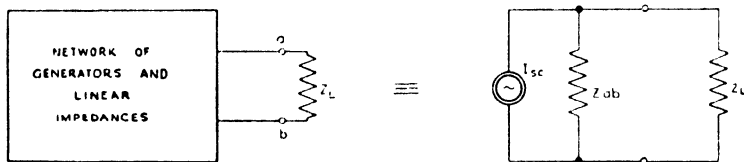


FIG. 187.—Equivalent circuits illustrating Norton's theorem.

This theorem is similar to Thévenin's theorem in that it enables a complicated network to be replaced by a single generator and impedance. In this case, however, the generator is of the constant-current type, and the impedance is in shunt with it, whilst in the case of Thévenin's theorem the equivalent generator is of the constant-voltage type, in series with an impedance. The equivalent circuits given by Thévenin's and Norton's theorem yield exactly the same current and voltage in the load impedance, and are therefore effectively identical to one another. In any particular problem, either theorem can therefore be used.

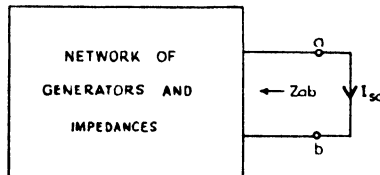


FIG. 188.—Derivation of constant-current generator.

In most cases Thévenin's theorem is the easier to apply, although when the network impedance is high compared with the load impedance, the constant-current generator concept (Norton's theorem) may simplify calculations—as in the equivalent circuit for a pentode valve amplifier, see page 361.

Fig. 187 shows Norton's theorem in diagrammatic form. I_{sc} is the current that flows when terminals a and b are short-circuited, and Z_{ab} is the impedance measured looking into terminals a and b with all generators replaced by impedances equal to their internal impedances (see Fig. 188).

Compensation theorem

Any impedance in a network can be replaced by a generator of zero internal impedance and of EMF equal to the instantaneous potential difference across the replaced impedance.

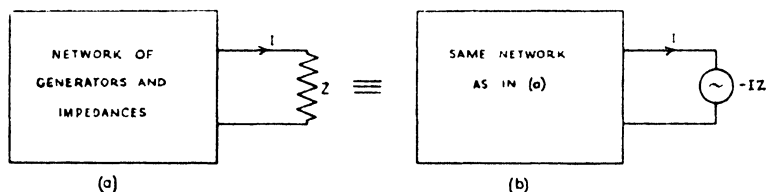


FIG. 189.—Equivalent circuits illustrating the compensation theorem.

Fig. 189 shows a network of impedances and generators, together with the particular impedance Z , that is to be replaced, considered as the load. The network may be completely solved by using Kirchhoff's Laws; in particular the equation for the right-hand mesh will be:—

$$\sum Z_1 I_1 + ZI = \sum E_1$$

where the summation extends over a number of unspecified impedances in the right-hand mesh.

If the circuit of Fig. 189a is solved by Kirchhoff's Laws, the equations will be exactly the same as for Fig. 189b, with the exception of the equation for the right-hand mesh which becomes:—

$$\sum Z_1 I_1 = -ZI + \sum E_1$$

Thus all the equations are identical for the two networks, and so also are the currents and voltages throughout the two networks; that is, the networks are equivalent.

It will be noticed that there is no restriction in this theorem on the types of impedance in the network; the impedances may in fact be linear or non-linear.

Maximum power transfer theorem

This theorem states that, given a generator with internal impedance Z_0/φ , the maximum power will be obtained from it if a load having the conjugate impedance $Z_0/-\varphi$ is connected across it. If the modulus alone can be varied, the power will be a maximum if the moduli of the load and generator impedances are equal, irrespective of the value of φ . This will now be proved.

Let a load of impedance Z_L/θ be connected across the generator as in Fig. 190.

The problem is to determine the values of Z_L and θ to give maximum power in the load.

The first step is to calculate the power in the load. It has been seen that the vector r/θ is equivalent to the vector $r(\cos \theta + j \sin \theta)$, (see Chapter 2). Thus the total impedance is:—

$$Z = Z_g \angle \varphi + Z_L \angle \theta = (Z_g \cos \varphi + Z_L \cos \theta) + j(Z_g \sin \varphi + Z_L \sin \theta) \quad (1)$$

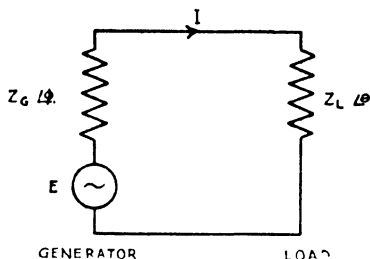


FIG. 190.—Maximum power transfer; generator connected to load.

$$\begin{aligned} \therefore |Z|^2 &= (Z_g \cos \varphi + Z_L \cos \theta)^2 + (Z_g \sin \varphi + Z_L \sin \theta)^2 \\ &= Z_g^2(\cos^2 \varphi + \sin^2 \varphi) + Z_L^2(\cos^2 \theta + \sin^2 \theta) \\ &\quad + 2Z_g Z_L (\cos \varphi \cos \theta + \sin \varphi \sin \theta) \\ &= Z_g^2 + Z_L^2 + 2Z_g Z_L \cos(\varphi - \theta) \end{aligned} \quad (2)$$

$$|I| = \frac{|E|}{|Z|}$$

and:—

$$\begin{aligned} P &= |I|^2 \times (\text{the resistive part of the load impedance}) \\ &= |I|^2 Z_L \cos \theta \end{aligned}$$

$$\begin{aligned} \therefore P &= \frac{|E|^2}{|Z|^2} Z_L \cos \theta \\ &= \frac{|E|^2 Z_L \cos \theta}{[Z_g^2 + Z_L^2 + 2Z_g Z_L \cos(\varphi - \theta)]} \end{aligned} \quad (3)$$

Consider first the variation of Z_L with θ constant. P will be a maximum when:—

$$\frac{dP}{dZ_L} = 0$$

$$\text{Now } P = \frac{|E|^2 Z_L \cos \theta}{Z_g^2 + Z_L^2 + 2Z_g Z_L \cos(\varphi - \theta)} = \frac{|E|^2 \cos \theta}{\frac{Z_g^2}{Z_L} + Z_L + 2Z_g \cos(\varphi - \theta)}$$

$$\therefore \frac{dP}{dZ_L} = \frac{-|E|^2 \cos \theta \left[\frac{-Z_\theta^2}{Z_L^2} + 1 \right]}{\left[\frac{Z_\theta^2}{Z_L} + Z_L + 2Z_\theta \cos(\varphi - \theta) \right]^2} \quad (4)$$

This is equal to zero if $Z_L^2 = Z_\theta^2$, and, since Z_L is positive, this gives $Z_L = Z_\theta$.

As $\frac{dP}{dZ_L}$ is positive when $Z_L < Z_\theta$ and negative when $Z_L > Z_\theta$,

this gives a maximum value to P . Hence the power is a maximum when the moduli of the generator and load impedances are equal.

Now consider variations of θ , with Z_L constant.

$$P = \frac{|E|^2 Z_L \cos \theta}{Z_\theta^2 + Z_L^2 + 2Z_\theta Z_L \cos(\varphi - \theta)}$$

$$\frac{dP}{d\theta} = \frac{|E|^2 Z_L [-\sin \theta \{Z_\theta^2 + Z_L^2 + 2Z_\theta Z_L \cos(\varphi - \theta)\} - \cos \theta \times 2Z_\theta Z_L \sin(\varphi - \theta)]}{[Z_\theta^2 + Z_L^2 + 2Z_\theta Z_L \cos(\varphi - \theta)]^2}$$

$$= \frac{-|E|^2 Z_L [(Z_\theta^2 + Z_L^2) \sin \theta + 2Z_\theta Z_L \sin \varphi]}{[Z_\theta^2 + Z_L^2 + 2Z_\theta Z_L \cos(\varphi - \theta)]^2} \quad (5)$$

This is zero if $\sin \theta = -\sin \varphi \times \frac{2Z_\theta Z_L}{Z_\theta^2 + Z_L^2}$, and, as before, this gives a maximum value to P .

The power will be an absolute maximum if both conditions are satisfied simultaneously, *i.e.* $Z_L = Z_\theta$, and $\sin \theta = -\sin \varphi$, or $\theta = -\varphi$; thus the load for maximum power is $Z_\theta \angle -\varphi$.

Writing the generator impedance is in the form $R + jX$, the load for maximum power is $R - jX$; that is, the generator and load impedances are conjugates.

It should be noted that this theorem applies to variation in *load* impedance. If the generator impedance is variable, maximum power will be transferred when $Z_\theta = 0 - jX_L$.

THE DECIBEL

Power ratios

Line communication is concerned with the transmission of AC power from one point to another, and the various lines and pieces of equipment that constitute a communication system introduce gains and losses of power.



FIG. 191.—Network connecting a generator and a load.

Consider a network connecting a generator to a load. Let the input power be P_1 and the output power be P_2 . The ratio of output power to input power is then $\frac{P_2}{P_1}$. The network may introduce a loss, in which case $\frac{P_2}{P_1}$ will be less than unity; or it may introduce a gain (e.g. an amplifier), in which case $\frac{P_2}{P_1}$ will be greater than unity.

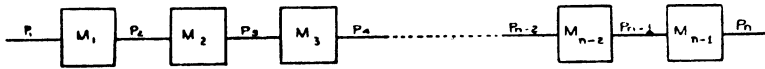


FIG. 192.—Series of networks in tandem.

If a number of such networks are connected in tandem as in Fig. 192, and the individual power ratios are known, the overall power ratio $\frac{P_n}{P_1}$ is obtained by multiplying together the individual power ratios. This follows from the fact that:—

$$\begin{aligned} \frac{P_n}{P_1} &= \frac{P_2}{P_1} \times \frac{P_3}{P_2} \times \frac{P_4}{P_3} \times \dots \times \frac{P_n}{P_{n-1}} \\ &= M_1 \times M_2 \times M_3 \times \dots \times M_{n-1} \end{aligned}$$

where $M_1, etc.$, are the individual power ratios.

Example.—

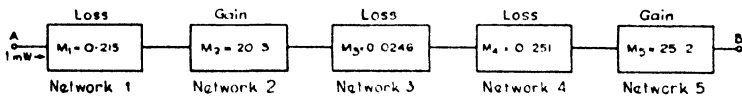


FIG. 193.

Consider Fig. 193. Five networks are inserted in tandem between A and B. The individual power ratios are:—

- $M_1 = 0.215$ (a loss)
- $M_2 = 20.3$ (a gain)
- $M_3 = 0.0246$ (a loss)
- $M_4 = 0.251$ (a loss)
- $M_5 = 25.2$ (a gain)

Find the power at B if 1 mW of power is applied to A.

Overall power ratio = $0.215 \times 20.3 \times 0.0246 \times 0.251 \times 25.2$
 = 0.679 (a loss)

Thus if 1 mW is applied to *A*, the output power at *B* will be 0.679 mW. *Ans.*

Logarithmic units

In a complex system containing a large number of component circuits each contributing a gain or loss, calculation of the overall power ratio may become extremely laborious. To simplify this calculation, the individual power ratios are expressed in a logarithmic unit, enabling addition to be employed in place of multiplication. The logarithmic unit employed is the "decibel" (abbreviated to db), and power gain or loss *D* of a network expressed in this unit is defined as:—

$$D = 10 \log_{10} \frac{P_2}{P_1} \quad (6)$$

where P_2 = output power
 and P_1 = input power.

If $\frac{P_2}{P_1}$ is less than unity, then $10 \log_{10} \frac{P_2}{P_1}$ will be negative. A negative sign thus indicates a power loss, and a positive sign a gain.

It should be noted that, since:—

$$10 \log_{10} \frac{P_2}{P_1} = -10 \log_{10} \frac{P_1}{P_2} \quad (7)$$

the numerical answer will be the same no matter whether $\frac{P_2}{P_1}$ or $\frac{P_1}{P_2}$ is considered, but to obtain the correct sign $\frac{P_2}{P_1}$ must be considered.

The following examples given in Table IX show how power ratios can be expressed in decibels.

TABLE IX
 Power ratios expressed in decibels

Input	Output	Ratio	Gain in db (negative sign indicates a loss)
2 mW	2000 mW	$\frac{2000}{2} = 1000$	$10 \log_{10} 1000 = 10 \times 3 = 30$ db
3 mW	600 mW	$\frac{600}{3} = 200$	$10 \log_{10} 200 = 10 \times 2.301 = 23.01$ db
5 mW	500 mW	$\frac{500}{5} = 100$	$10 \log_{10} 100 = 10 \times 2 = 20$ db
20 mW	2000 mW	$\frac{2000}{20} = 100$	$10 \log_{10} 100 = 10 \times 2 = 20$ db
2 mW	20 mW	$\frac{20}{2} = 10$	$10 \log_{10} 10 = 10 \times 1 = 10$ db
40 mW	200 mW	$\frac{200}{40} = 5$	$10 \log_{10} 5 = 10 \times 0.699 = 6.99$ db
3 W	6 W	$\frac{6}{3} = 2$	$10 \log_{10} 2 = 10 \times 0.301 = 3.01$ db
10 mW	12.6 mW	$\frac{12.6}{10} = 1.26$	$10 \log_{10} 1.26 = 10 \times 0.10 = 1$ db
500 mW	5 mW	$\frac{5}{500} = \frac{1}{100}$	$10 \log_{10} \left(\frac{1}{100}\right) = 10 \times -\log_{10} 100 = 10 \times (-2) = -20$ db
100 mW	21.6 mW	$\frac{21.6}{100} = 0.216$	$10 \log_{10} 0.216 = 10(-0.335) = 10(-1+0.335) = -6.65$ db

Expression of absolute power level using the decibel notation

The decibel is fundamentally a unit of power *ratio* and not of absolute power; but if some standard reference level of power be assumed, then any absolute power can be expressed as so many db above or below this reference standard. While various other standards may occasionally be encountered, the standard adopted in Britain and America is 1 mW (0.001 W). Using this

TABLE X

Absolute powers expressed in dbm

Powers expressed in decibels referred to 1 mW.			
1	$\mu\mu\text{W}$ - 90 dbm	1 mW	0 dbm
10	$\mu\mu\text{W}$ - 80 "	2 mW	+ 3 "
100	$\mu\mu\text{W}$ - 70 "	4 mW	+ 6 "
0.001	μW - 60 "	5 mW	+ 7 "
0.01	μW - 50 "	8 mW	+ 9 "
0.1	μW - 40 "	10 mW	+ 10 "
1.0	μW - 30 "	20 mW	+ 13 "
2	μW - 27 "	40 mW	+ 16 "
4	μW - 24 "	50 mW	+ 17 "
5	μW - 23 "	80 mW	+ 19 "
8	μW - 21 "	100 mW	+ 20 "
10	μW - 20 "	200 mW	+ 23 "
20	μW - 17 "	400 mW	+ 26 "
40	μW - 14 "	500 mW	+ 27 "
50	μW - 13 "	800 mW	+ 29 "
80	μW - 11 "	1000 mW	+ 30 "
100	μW - 10 "	1 W	+ 30 "
200	μW - 7 "	2 W	+ 33 "
400	μW - 4 "	4 W	+ 36 "
500	μW - 3 "	5 W	+ 37 "
800	μW - 1 "	8 W	+ 39 "
		10 W	+ 40 "
		100 W	+ 50 "
		1 kW	+ 60 "
		10 kW	+ 70 "
		100 kW	+ 80 "

standard, any power P can be expressed as $10 \log_{10} \left(\frac{P}{1 \text{ mW}} \right)$ db referred to 1 mW. Thus one can express 1 watt as $10 \log_{10} \left(\frac{1.000}{1} \right) = 30$ db above the standard 1 mW, or "+ 30 db with respect to 1 mW". Similarly, $5 \mu\text{W}$ can be expressed as $10 \log_{10} \left(\frac{5}{10000} \right) = -23$ db with respect to 1 mW (*i.e.*, 23 db below 1 mW). The expression "db with respect to 1 mW" or "db referred to 1 mW" is usually abbreviated to "dbm"; other abbreviations sometimes met are "db wrt 1 mW", "db ref 1 mW", and "vu" (voice unit).

Thus $20 \text{ dbm} \equiv 20 \text{ db wrt } 1 \text{ mW} \equiv 20 \text{ db ref } 1 \text{ mW} \equiv 20 \text{ vu}$
 $= 20 \text{ db with respect to } 1 \text{ mW}$
 $= 100 \text{ mW}.$

Conversion of decibels to power ratios

The conversion of power ratios expressed in decibels (and of powers expressed in dbm) to actual power ratios (and actual powers) is effected by exactly the reverse process from that used for expressing power ratios in decibels (and actual powers in dbm).

$$10 \log_{10} \frac{P_2}{P_1} = D \quad (8)$$

(quoted)

$$\therefore \log_{10} \frac{P_2}{P_1} = \frac{D}{10}$$

$$\therefore \frac{P_2}{P_1} = \text{antilog} \left(\frac{D}{10} \right) \quad (9)$$

Example 1.—

What power, in watts, is represented by 25 dbm ?

$$\frac{P}{1 \text{ mW}} = \text{antilog} \frac{25}{10} = \text{antilog } 2.5 = 316.2$$

$$P = 316.2 \text{ mW}$$

$$= 0.316 \text{ W } \textit{Ans.}$$

Example 2.—

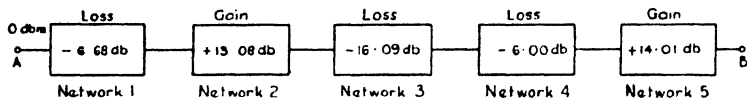


FIG. 194.

Consider Fig. 194. Five networks are inserted in tandem between *A* and *B*. The decibel gains and losses of the individual networks are :—

Network 1	-	6.68 db
Network 2	+	13.08 db
Network 3	-	16.09 db
Network 4	-	6.00 db
Network 5	+	14.01 db

Find the power at *B* if 0 dbm is applied to *A*.

$$\text{Total decibel gain or loss} = -6.68 + 13.08 - 16.09 - 6.00 + 14.01$$

$$= -1.68 \text{ db}$$

$$\text{Power at } B = 0 - 1.68 \text{ dbm}$$

$$= -1.68 \text{ dbm. } \textit{Ans.}$$

This is the decibel approach to the example given on page 239 ; it should be noted that -1.68 dbm corresponds to a power of 0.679 milliwatts .

Current and voltage ratios

When it is desired to compare the powers developed in two *equal resistors* it is sufficient to measure the two voltages or the two currents; then the power ratio in decibels is equal to twenty times the logarithm (to base 10) of the current or voltage ratio.

Consider two equal resistors of R ohms, carrying currents of RMS values I_1 and I_2 , and having voltages across them of RMS values E_1 and E_2 respectively. Then the powers developed in these two resistors are :—

$$P_1 = E_1 I_1 = R \cdot I_1^2 = \frac{1}{R} \cdot E_1^2$$

$$\text{and } P_2 = E_2 I_2 = R \cdot I_2^2 = \frac{1}{R} \cdot E_2^2$$

The ratio between these two powers is therefore :—

$$\frac{P_2}{P_1} = \frac{E_2 I_2}{E_1 I_1} = \left(\frac{I_2}{I_1}\right)^2 = \left(\frac{E_2}{E_1}\right)^2$$

Or, expressing this in decibels,

$$\begin{aligned} D &= 10 \log_{10} \left(\frac{P_2}{P_1}\right) = 10 \log_{10} \left(\frac{I_2}{I_1}\right)^2 \\ &= 20 \log_{10} \left(\frac{I_2}{I_1}\right) \end{aligned} \quad (10)$$

$$\begin{aligned} \text{and } D &= 10 \log_{10} \left(\frac{P_2}{P_1}\right) = 10 \log_{10} \left(\frac{E_2}{E_1}\right)^2 \\ &= 20 \log_{10} \left(\frac{E_2}{E_1}\right) \end{aligned} \quad (11)$$

Thus the power ratio in decibels is equal to $20 \log_{10}$ (current ratio) = $20 \log_{10}$ (voltage ratio), *provided that the two resistances are equal* through which the two currents I_1 and I_2 (or across which the two voltages E_1 and E_2) are measured.

Currents through Impedances.—When it is required to compare the powers in two impedances by measurement of the currents through them, it is desirable that their resistive components be equal since, in this case, the power ratio will be equal to the (current ratio)². This may be verified as follows :—

Let the two impedances be :—

$$\begin{aligned} Z_1 &\equiv |Z_1| \angle \varphi_1 \equiv R_1 + jX_1 \\ \text{and } Z_2 &\equiv |Z_2| \angle \varphi_2 \equiv R_2 + jX_2 \end{aligned}$$

Let the magnitudes of the currents flowing in Z_1 and Z_2 be I_1 and I_2 respectively.

The power ratio is :—

$$\frac{P_2}{P_1} = \frac{I_2^2 R_2}{I_1^2 R_1} \quad (12)$$

Hence when

$$R_1 = R_2$$

$$\frac{P_2}{P_1} = \left(\frac{I_2}{I_1}\right)^2$$

Voltagcs across Impedances.—When considering the voltage across two impedances the (voltage ratio)² will be equal to the power ratio if the conductive components be equal. This may be verified as follows :—

Let the impedances be :—

$$Z_1 \equiv |Z_1| \angle \varphi_1 \equiv R_1 + jX_1$$

and

$$Z_2 \equiv |Z_2| \angle \varphi_2 \equiv R_2 + jX_2$$

Let their admittances be :—

$$Y_1 \equiv |Y_1| \angle -\varphi_1 \equiv G_1 + jB_1$$

and

$$Y_2 \equiv |Y_2| \angle -\varphi_2 \equiv G_2 + jB_2$$

Power

$$P_1 = I_1^2 R_1 = \frac{E_1^2}{Z_1^2} \cdot Z_1 \cos \varphi_1$$

$$= \frac{E_1^2}{Z_1} \cos \varphi_1$$

$$= E_1^2 Y_1 \cos \varphi_1$$

$$= E_1^2 G_1$$

Similarly

$$P_2 = E_2^2 G_2$$

The power ratio is :—

$$\frac{P_2}{P_1} = \frac{E_2^2 G_2}{E_1^2 G_1} \tag{13}$$

Hence when

$$G_1 = G_2$$

$$\frac{P_2}{P_1} = \left(\frac{E_2}{E_1}\right)^2$$

TRANSFORMERS

Two or more coils possessing mutual inductance form a transformer. At audio and power frequencies, iron cores are generally used and the mutual inductance is large. At higher frequencies iron cores cannot be used and the coupling is smaller; such transformers are most conveniently considered as coupled circuits. The behaviour of iron-cored transformers is most easily seen by considering first a "perfect" or "ideal" transformer, that is, one with no losses. The losses that occur in practical transformers can then be considered separately.

The "perfect" transformer

Consider first a transformer with zero winding resistance, an infinite primary inductance, and such that all flux produced by the primary cuts the secondary, and vice versa. This is known as a perfect transformer. Its behaviour may be explained by a vector diagram. As the flux is the only link between primary

and secondary, it is chosen as the reference vector (it can be represented by a vector as it varies sinusoidally).

Conditions on no-load

First consider the transformer with a constant alternating voltage E_1 applied to the primary, and the secondary open-circuited — *i.e.* off load (*see* Fig. 195*a*). Let the primary and secondary turns be T_1 and T_2 respectively. The current that flows will be infinitely small, due to the large inductance of the primary; this will be 90° behind the voltage E_1 . The magnetic flux Φ in the iron core will be in phase with this current, hence Φ is 90° behind E_1 . The flux, however, will still be finite, and the vector diagram is as shown in Fig. 195*b*.

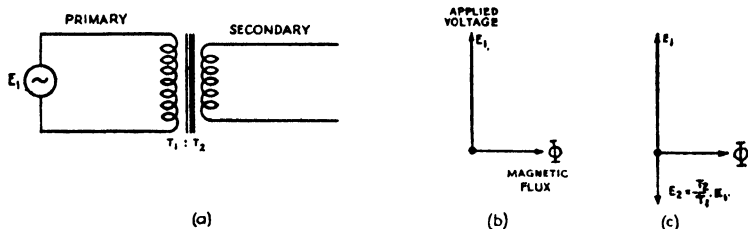


FIG. 195.—Transformer on no-load (*i.e.*, open-circuit).

The next result is one of fundamental importance, upon which is based the whole of transformer theory. It is as follows:—

If the applied voltage E_1 is constant, then the flux Φ is constant.

Since sine curves are being dealt with, the term “constant” refers to the amplitude of the waveform, *i.e.* the moduli of the corresponding vectors.

As it is always assumed that the applied voltage is constant, it will be seen that the flux must remain constant, whatever load may be connected to the secondary. The proof of the statement just made is as follows:—

If there is no resistance in the transformer, the applied EMF must be exactly equal and opposite to the back-EMF developed across the primary. Hence, as E_1 is constant, the back-EMF must be constant. But the back-EMF is proportional to the rate of change of flux; the flux must therefore be such that its rate of change is a sine-wave of constant amplitude. Thus the flux itself must be a sinusoidal waveform of constant amplitude, *i.e.* the flux is constant.

Returning to the perfect transformer, with voltage E_1 applied to the primary, the secondary voltage E_2 can be calculated. For E_2 is produced by the flux cutting the secondary turns, and as the flux is the same for primary and secondary, the primary and secondary induced voltages will be proportional to the primary

turns T_1 and the secondary turns T_2 respectively. But the primary induced voltage is the back-EMF in the primary, which is equal and opposite to E_1 . Hence the secondary voltage is of magnitude E_2 , such that

$$\frac{E_1}{E_2} = \frac{T_1}{T_2} \quad (14)$$

Also, E_2 is in phase with the back-EMF in the primary, *i.e.* 180° out of phase with the applied primary voltage. This result is also true when any load is connected across the secondary. The vector diagram is shown in Fig. 195c.

The derivation of the name "transformer" will now be clear: by choosing a suitable ratio for $\frac{T_1}{T_2}$ we can transform an alternating voltage to any other required voltage of the same frequency.

Conditions on load

It has been shown so far that as soon as a voltage is applied to the primary a voltage appears across the secondary, and a small amount of primary current flows (infinitely small if the transformer is perfect). It now remains to study the action when a load impedance is connected across the secondary. Assume that this

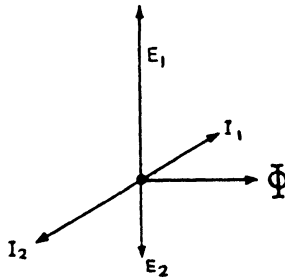


FIG. 196.—Vector diagram for perfect transformer on load.

impedance is given; the secondary voltage is constant and known, and hence the magnitude and phase of the secondary current can be calculated.

Insert this on the vector diagram; Fig. 196 shows the case for a load with a positive reactance, so that I_2 lags behind E_2 . It is here that the constancy of the flux Φ must be taken into account, for the effect of this current I_2 on the flux will be considerable. Some action must take place to nullify this effect: in fact, a primary current I_1 flows.

If I_1 is to have the opposite effect to I_2 , it must be 180° out of phase. Its magnitude is determined by the fact that the two effects are to be equal. Now the effect of a current I on flux is proportional to $I \times T$, where T is the number of turns through which it flows. As the effect of I_1 and I_2 must be equal, $I_1 T_1$ and $I_2 T_2$ must be equal.

$$\begin{aligned} \therefore I_1 T_1 &= I_2 T_2 \\ \therefore \frac{I_1}{I_2} &= \frac{T_2}{T_1} \end{aligned} \tag{15}$$

In other words, the current ratio is the inverse of the turns ratio, *i.e.* the winding with the fewer turns carries the larger current. Fig. 196 shows the vector diagram.

Note that the angle between E_2 and I_2 is equal to the angle between E_1 and I_1 , *i.e.* if the load on the secondary takes a lagging current, the transformer will take a lagging current from the supply. This can be put in another way by saying that the power factor is the same for primary and secondary.

It has been shown that $\frac{E_1}{E_2} = \frac{T_1}{T_2}$, and that $\frac{I_2}{I_1} = \frac{T_1}{T_2}$; hence $\frac{E_1}{E_2} = \frac{I_2}{I_1}$

$$\therefore E_1 \cdot I_1 = E_2 \cdot I_2$$

The input power = $E_1 I_1 \cos \varphi_1$, where $\cos \varphi_1$ is the input power factor; and the output power = $E_2 I_2 \cos \varphi_2$, where $\cos \varphi_2$ is the output power factor. But $\varphi_1 = \varphi_2$, so that $\cos \varphi_1 = \cos \varphi_2$, and it has just been proved that $E_1 I_1 = E_2 I_2$

$$\therefore \text{Input power} = \text{Output power} \tag{16}$$

Thus the perfect transformer introduces no loss, and the efficiency is 100 per cent. In practice, efficiencies of 95 per cent. can easily be obtained in power transformers, and audio-frequency transformers frequently have a loss of less than $\frac{1}{2}$ db.

Impedance transformation

With the secondary off load, the primary of a perfect transformer takes no current; that is to say, its input impedance is infinite. When a load is connected to the secondary, the input or

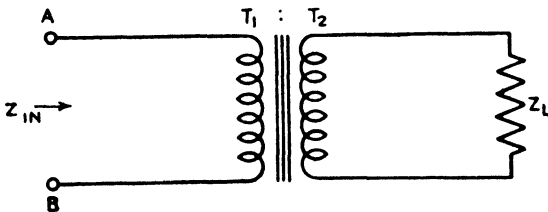


FIG. 197.—Impedance-transforming property of a transformer.

primary impedance Z_{IN} is not infinite, but depends upon the load Z_L in the secondary (*see* Fig. 197). The relationship between Z_{IN} and Z_L is most important, and will now be derived.

From equations 14 and 15,

$$\frac{E_1}{E_2} = \frac{T_1}{T_2} \text{ and } \frac{I_2}{I_1} = \frac{T_1}{T_2}$$

$$\begin{aligned}
 \therefore \quad & \frac{E_1 I_2}{E_2 I_1} = \frac{T_1^2}{T_2^2} \\
 \therefore \quad & \frac{E_1}{I_1} = \frac{T_1^2}{T_2^2} \frac{E_2}{I_2} \\
 \text{But} \quad & \frac{E_1}{I_1} = Z_{IN} \text{ and } \frac{E_2}{I_2} = Z_L \\
 \therefore \quad & \frac{Z_{IN}}{Z_L} = \frac{T_1^2}{T_2^2} \\
 & Z_{IN} = \frac{T_1^2}{T_2^2} \times Z_L \qquad (17)
 \end{aligned}$$

This means that the impedance Z_{IN} across AB in Fig. 197 will be $\frac{T_1^2}{T_2^2} \times Z_L$. It should be noted that the transformer *alters the modulus of an impedance but not its angle*. Thus, if Z_L is a condenser, the impedance across AB will be capacitive.

If T_1 is greater than T_2 , the input impedance Z_{IN} will be greater than Z_L ; if T_1 is less than T_2 , the input impedance Z_{IN} will be less than Z_L . Note that the impedance ratio is the *square* of the turns ratio.

This property of a transformer is known as "impedance transformation"; it is very useful for connecting together two circuits (*e.g.* lines) of different impedance to satisfy the condition for maximum power transference.

From this result, it can be seen that a series impedance Z in the secondary can be transferred to the primary as an impedance $Z \times \frac{T_1^2}{T_2^2}$ without affecting the behaviour of the circuit, *e.g.*, the two circuits in Fig. 198 are equivalent as far as AC is concerned.

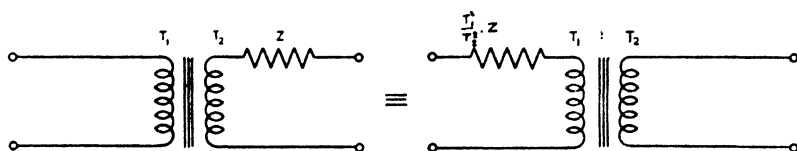


FIG. 198.—Secondary impedance transferred to primary.

In the same way, an impedance could, if desired, be transferred from primary to secondary by multiplying by $\frac{T_2^2}{T_1^2}$. This method often simplifies the solution of problems involving transformers.

Example 1.—Find the power dissipated in the load of the transformer shown in Fig. 199*a*.

This will be achieved by finding the secondary current i and using the formula $P = i^2 R = 400i^2$. To find i , the equivalent circuit of Fig. 199*b* is used.

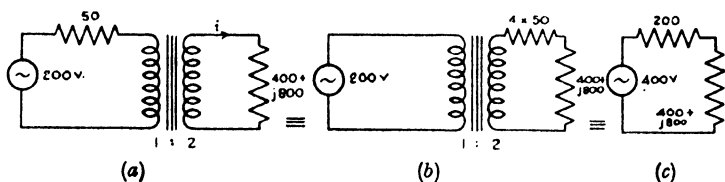


FIG. 199.

The 50 ohms has been transferred to the secondary as $4 \times 50 = 200$ ohms. The transformer with 200v on the primary is equivalent to a generator of 400v, by Thévenin's theorem, so that a further equivalent circuit is as shown in Fig. 199*c*.

Total impedance $Z = 600 + j800 = 200(3 + j4)$

$$|Z| = 200\sqrt{3^2 + 4^2} = 1000 \text{ ohms}$$

$$\therefore i = \frac{400}{1000} = 0.4 \text{ amps}$$

$$\therefore P = 400 \times i^2 = 0.16 \times 400 = 64 \text{ watts.}$$

Example 2.—Find the equivalent input capacity of the transformer in Fig. 200.

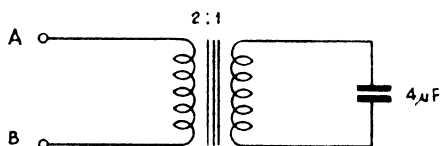


FIG. 200.

It is easy to be caught out by a simple example such as this, by saying that the answer is $16\mu\text{F}$. This, of course, is *not* the correct answer.

The impedance across AB is $2^2 = 4$ times the impedance of the $4\mu\text{F}$ condenser. To *multiply* the *impedance* of a condenser by 4, its *capacity* must be *divided* by four. The correct answer is therefore $1\mu\text{F}$.

Transformers and maximum power transfer

The maximum power transfer theorem stated (p. 236) that, to obtain maximum power from a generator of internal impedance $Z_g \angle \phi$, a load of impedance $Z_o \angle -\phi$ must be connected; and that if the two angles cannot be made equal and opposite, the maximum power under these circumstances will be obtained when the moduli of the two impedances are equal.

This does not answer the problem in its practical form: usually

the impedance of the generator and of the load are both given, and it is required to connect the two together to obtain maximum power transfer. This process is known as "impedance matching", and is carried out by using a transformer of suitable turns ratio. It was shown above that a transformer alters the modulus of an impedance by a factor $\frac{T_1^2}{T_2^2}$ but does not affect the angle. Hence if the impedances of the load and of the generator are given, a transformer can be used to satisfy the first condition of the maximum power transfer theorem (moduli equal), but not the second (angles equal and opposite). If, as is often the case, the two impedances are resistive, the second condition is automatically satisfied, as both angles are equal to zero.

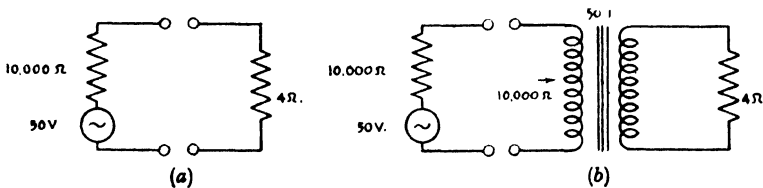


FIG. 201.—Example to illustrate impedance matching, using a transformer.

Fig. 201 illustrates a typical example: the load and generator are given in Fig. 201a.

If the connection was made direct, the power developed in the 4 ohms would be negligible. A transformer is therefore inserted; if the impedances are to match, $\frac{T_1^2}{T_2^2}$ will have to equal $\frac{10,000}{4}$;

$$\therefore \frac{T_1^2}{T_2^2} = \frac{10,000}{4} = 50^2$$

This transforms the 4 ohms up to 10,000, as shown in Fig. 201b, and maximum power will be transferred.

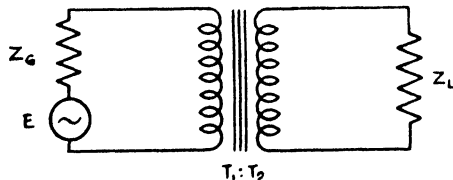


FIG. 202.—Impedance matching, using a transformer (general case).

If the generator impedance is Z_g , and the load impedance is Z_L (see Fig. 202), the turns ratio will be given by:—

$$\frac{T_1}{T_2} = \sqrt{\frac{|Z_g|}{|Z_L|}} \quad (18)$$

Example.—

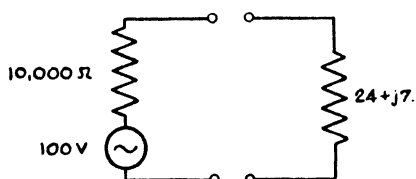


FIG. 203.

The generator and load are as given in Fig. 203. Calculate :—

(a) The power in the load if connected directly to the generator.

(b) The turns ratio of transformer for maximum power transfer, and the power so transferred.

(c) The power that would be transferred if the second condition of the maximum power transfer theorem could be satisfied (*i.e.* angles equal and opposite).

(a) Total impedance = $10,024 + j7$. To slide-rule accuracy, this is equal to 10,000.

$$\begin{aligned} \therefore I &= \frac{100}{10^4} \\ &= \frac{1}{100} \text{ amp} \end{aligned}$$

$$\begin{aligned} \therefore P &= I^2 R = \frac{1}{10^4} \times 24 \text{ watts} \\ &= 2.4 \text{ milliwatts } \textit{Ans.} \end{aligned}$$

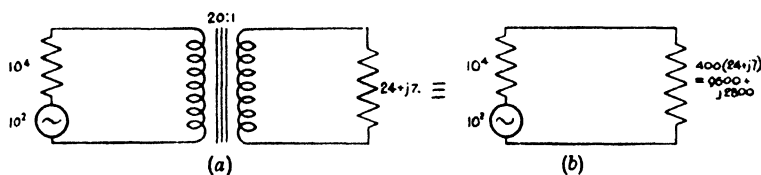


FIG. 204.

(b) The modulus of the load impedance Z_L is :—

$$\begin{aligned} |Z_L| &= \sqrt{24^2 + 7^2} \\ &= 25 \end{aligned}$$

$$\therefore \frac{T_1^2}{T_2^2} = \frac{10^4}{25}$$

$$\therefore \frac{T_1}{T_2} = 20 : 1$$

To find the power transferred, find the equivalent circuit ; this is shown in Fig. 204.

Note that the transferred impedance is *not* 10^4 ohms—although its modulus will be 10^4 ohms. It must be transferred as a vector, *i.e.* as $9600 + j \cdot 2800$.

$$\begin{aligned} \text{Total impedance} &= 10^4 + 9600 + j \cdot 2800 = 19,600 + j \cdot 2800 \\ &= 2800 (7 + j \cdot 1) \end{aligned}$$

$$\therefore I = \frac{100}{2800 \cdot |7 + j \cdot 1|} = \frac{1}{28\sqrt{50}} \text{ amp}$$

\therefore Power transferred

$$P = I^2 R = \frac{1}{28^2 \times 50} \times 9600 = \frac{12}{49} \text{ watts}$$

$$\text{i.e. } P = 245 \text{ mW } \textit{Ans.}$$

(c) In this case, the load would be 10^4 (both angles = 0)

$$\therefore \text{Total impedance} = 2 \times 10^4$$

$$\therefore I = \frac{10^2}{2 \times 10^4} = \frac{1}{200}$$

$$\begin{aligned} \therefore P &= I^2 R = \frac{1}{4 \times 10^4} \times 10^4 \\ &= 250 \text{ mW } \textit{Ans.} \end{aligned}$$

This shows that by using a transformer, the transferred power in this particular case is increased more than 100 times.

Note that satisfying the second condition produced a further power increase of only about 2 per cent.

Transformers with more than two windings

The same theory applies as for ordinary transformers—*i.e.*, voltages are proportional to turns, and the total effect of all currents on the flux is zero.

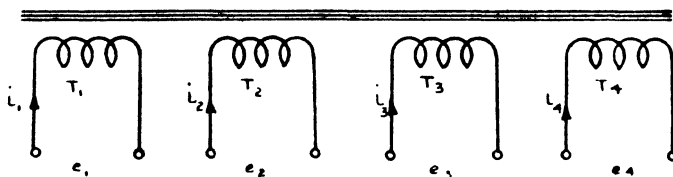


FIG. 205.—Transformer with more than two windings.

Consider Fig. 205, which shows a transformer with four windings. The equations are :—

The transformer voltage equation :—

$$\frac{e_1}{T_1} = \frac{e_2}{T_2} = \frac{e_3}{T_3} = \frac{e_4}{T_4} \quad (19)$$

and the transformer current equation :—

$$i_1 T_1 + i_2 T_2 + i_3 T_3 + i_4 T_4 = 0 \quad (20)$$

It is not usually possible to introduce the idea of transferred impedances, and problems are best tackled from first principles and the application of Kirchoff's law.

Example.—A three-winding transformer having turns t , t , and $n \cdot t$, is connected, as in Fig. 206, to three impedances R , S , and Q , and to a generator A that produces a current I . Find the current x flowing through R .

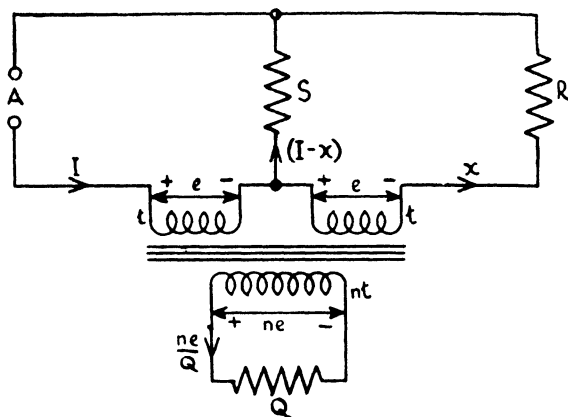


FIG. 206.—Example of three-winding transformer.

Let the voltage appearing across one of the transformer windings with t turns be e ; the voltages across the other windings can then be written in at once by applying the transformer voltage equation (equation 19), since the turns ratios are known. Note that instantaneous polarities for the voltages, as for the currents, have been inserted.

The current through the impedance Q can be found at once from the voltage across it: this current is $\frac{ne}{Q}$, as shown in the figure.

The transformer current equation (equation 20) then becomes:—

$$\frac{ne}{Q} \cdot nt = I \cdot t + x \cdot t$$

$$\therefore e = I \cdot \frac{Q}{n^2} + x \cdot \frac{Q}{n^2} \tag{i}$$

Applying Kirchoff's law to the right-hand mesh (*i.e.* that including S and R),

$$e = S(I - x) - R \cdot x$$

$$\therefore e = I \cdot S - x \cdot (S + R) \tag{ii}$$

Solving for x by subtracting equation (i) from equation (ii):—

$$0 = I \left(S - \frac{Q}{n^2} \right) - x \left(S + R + \frac{Q}{n^2} \right)$$

$$\therefore x = I \cdot \frac{\left(S - \frac{Q}{n^2}\right)}{\left(S + R + \frac{Q}{n^2}\right)}$$

Note that $x = 0$ if $\frac{Q}{n^2} = S$.

LOSSES AND EQUIVALENT CIRCUITS

Up to this point it has been assumed that the transformer was perfect, but in practice there will be losses. The various types of loss and their effect will now be considered; the most convenient way of doing this is by drawing an equivalent circuit.

The losses are divided into four groups: Iron losses (in the core), copper losses (in the windings), flux leakage losses, and self-capacity.

Iron losses

(a) *Magnetising current.*—If the inductance of the primary is not infinite, current will flow in the primary when the secondary is off load; it is this current that produces the flux Φ . As Φ is constant for all loads, this current will also be constant, and must be added to the total current on load. It will be 90° behind the primary voltage E_1 , and is therefore represented in the equivalent circuit as being caused by an inductance L_p across the primary (see Fig. 207a). This is, of course, the inductance measured across the primary with the secondary off load, and should be as large as possible. It is drawn on the equivalent circuit across one side of the transformer only. As it is a reactance, it does not introduce a *power* loss.

(b) *Eddy current loss.*—The alternating flux, as well as producing voltages in the windings, produces voltages in the metal of the core, causing eddy currents to circulate. As the core material has resistance, this effect is equivalent to a small extra resistive load on the transformer, and it is constant with the flux. This loss is reduced by using insulated laminations for the core, thereby giving the core a very high resistance to eddy currents.

(c) *Hysteresis loss.*—Due to hysteresis, losses occur in the process of magnetising the core. These are *power* losses which appear in the form of heat. As power can be represented as occurring in a resistance and not in a reactance, this loss is equivalent to a small extra resistive load, which is constant with flux.

Eddy current and hysteresis losses combine to form a single resistive load on the supply. As this load is constant with flux, and therefore with applied primary voltage, it will be represented by a resistance R_0 across the primary (see Fig. 207a); and as the loss is small, this resistance will be large.

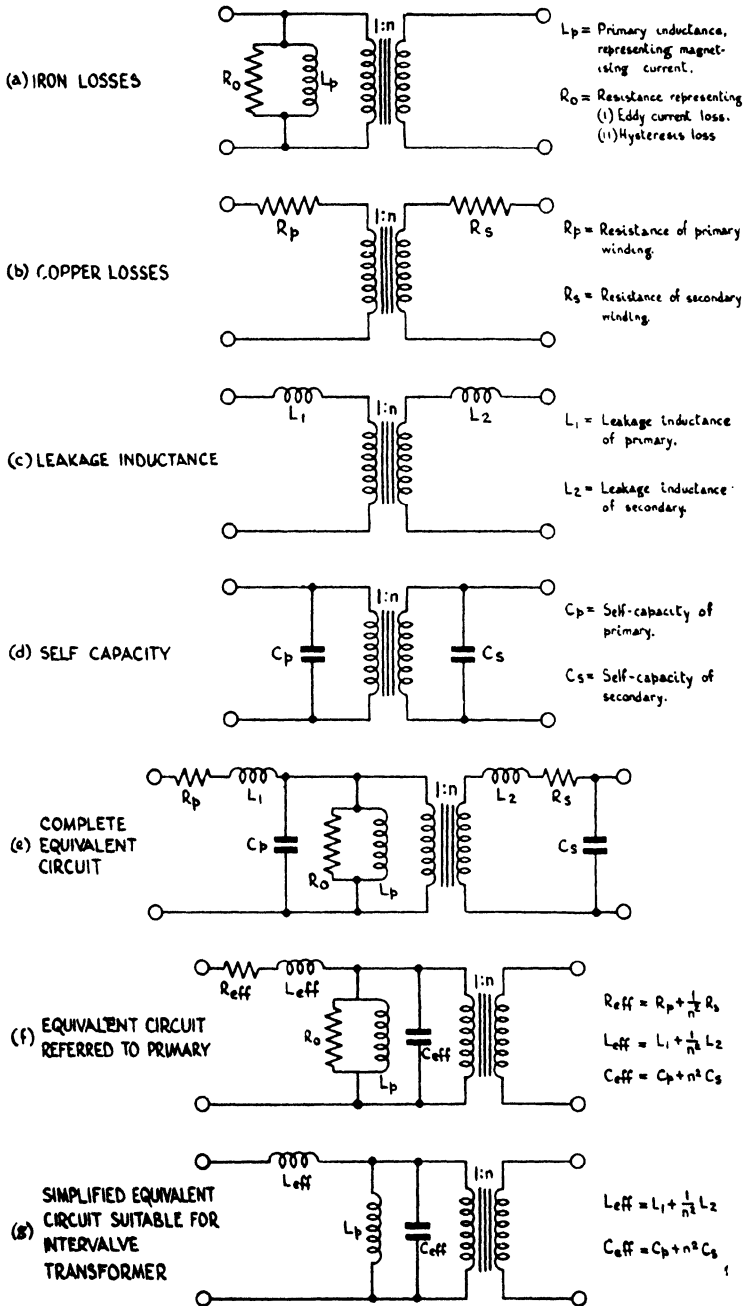


Fig. 207.—Equivalent circuits for transformers having losses.

Copper losses

These are due simply to the DC resistance of the windings, and are represented by the resistances R_p and R_s in Fig. 207*b*. The loss due to these is an " I^2R " loss, which increases with the square of the load current.

Flux leakage losses

It has been assumed that all the flux produced by the primary cuts the secondary turns; in practice a small amount will not. It will however cut the primary turns, and so produce self-inductance. The effect of flux leakage in the primary can be represented by a small series inductance L_1 , as shown in Fig. 207*c*. There will similarly be flux leakage between the secondary and the primary represented by L_2 .

Self-capacity of windings

The presence of internal winding capacities may have to be taken into consideration. These are of no importance at power frequencies, but they have a large effect on the behaviour of the transformer at audio frequencies. They can be represented by condensers C_p and C_s across primary and secondary, as in Fig. 207*d*.

Complete equivalent circuit

The equivalent circuit for a transformer, including all the above losses, is therefore as shown in Fig. 207*e*.

It is often convenient to simplify the circuit of Fig. 207*e* by transferring L_2 , R_s and C_s to the primary, where they become $\frac{T_1^2}{T_2^2} L_2$, $\frac{T_1^2}{T_2^2} R_s$, and $\frac{T_1^2}{T_2^2} C_s$. They can then be combined with L_1 , R_p and C_p to give what are known as the effective leakage inductance, resistance and capacity, referred to the primary—that is, L_{eff} , R_{eff} , and C_{eff} in Fig. 207*f*. Alternatively, L_1 , R_p , and C_p could, if desired, be transferred to the secondary.

The complete equivalent circuit can be further simplified by neglecting any losses that may be small. Thus in the case of transformers used in valve amplifiers, the resistance of the windings is usually very small, as also are the eddy current and hysteresis losses. In such cases, R_p , R_s and R_o can be omitted, and the equivalent circuit, referred to the primary, is then as shown in Fig. 207*g*.

TRANSFORMERS WITH SMALL COUPLING

A transformer can be regarded as two windings possessing self and mutual inductance; this is indeed the most satisfactory way of dealing with transformers in which the coupling is small.

It has been seen in Chapter 3 (page 170) that if two circuits have mutual inductance M , a current i_1 in the primary will induce

a voltage $\frac{M di_1}{dt}$ in the secondary. If there is also a current i_2 flowing in the secondary, it will produce a voltage $-L_s \frac{di_2}{dt}$ in the secondary due to self-inductance. If both i_1 and i_2 are flowing, their effects on flux are additive, so their induced voltages are additive. Hence the total induced voltage in the secondary is :—

$$e_2 = M \frac{di_1}{dt} - L_s \frac{di_2}{dt} \tag{21}$$

Similarly,

$$e_1 = M \frac{di_2}{dt} - L_p \frac{di_1}{dt} \tag{22}$$

These equations apply for any waveform of current. Dealing with pure sine-waves only, and using the vector representation, it has already been seen that $-L_p \frac{di_1}{dt}$ becomes $-j\omega L_p i_1$; similarly $M \frac{di_2}{dt}$ becomes $j\omega M i_2$. Hence the equations for induced voltages become :—

$$e_2 = j\omega M i_1 - j\omega L_s i_2 \tag{23}$$

$$e_1 = j\omega M i_2 - j\omega L_p i_1 \tag{24}$$

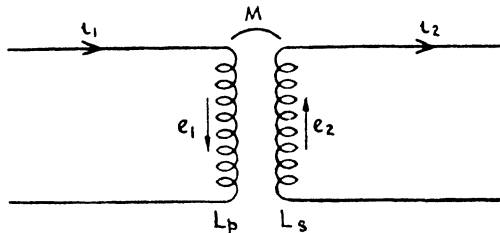


FIG. 208.—Transformer represented by two coupled circuits.

Fig. 208 shows the sense in which these induced voltages are measured.

Suppose now an external voltage E is applied to the primary, and an impedance Z is connected across the secondary. The effective primary impedance will now be calculated (see Fig. 209).

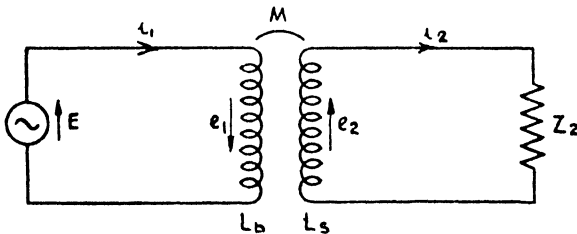


FIG. 209.—Transformer of Fig. 208 connected between generator and

The equations 23 and 24 hold. Apply Kirchhoff's Law to the primary :—

$$\begin{aligned} E + e_1 &= 0 \\ \therefore E &= -e_1 = -j\omega M i_2 + j\omega L_p i_1 \quad (\text{from 24}) \\ \therefore E &= j\omega L_p i_1 - j\omega M i_2 \end{aligned} \quad (25)$$

Apply Kirchhoff's Law to the secondary :—

$$\begin{aligned} e_2 &= i_2 Z_2 \\ \therefore j\omega M i_1 - j\omega L_s i_2 &= i_2 Z_2 \\ \therefore j\omega M i_1 &= i_2 (Z_2 + j\omega L_s) = i_2 Z_s \\ \therefore i_2 &= \frac{j\omega M i_1}{Z_s} \end{aligned} \quad (26)$$

where $Z_s = Z_2 + j\omega L_s =$ total secondary impedance.

Eliminating i_2 from 25 and 26 gives :—

$$\begin{aligned} E &= j\omega L_p i_1 - j\omega M \left(\frac{j\omega M i_1}{Z_s} \right) \\ \therefore E &= j\omega L_p i_1 + \frac{\omega^2 M^2}{Z_s} i_1 \\ \text{Primary impedance } Z_p &= \frac{E}{i_1} = j\omega L_p + \frac{\omega^2 M^2}{Z_s} \end{aligned} \quad (27)$$

The second term is known as the "reflected impedance" from the secondary.

It can be shown that the result given in equation 27 reduces to $Z_p = \frac{T_1^2}{T_2^2} Z_2$ if the transformer is perfect—a result already obtained on page 248. For, if the transformer is perfect, L_p and L_s tend to infinity. $M^2 \rightarrow L_p L_s \rightarrow \infty$, and $\frac{L_p}{L_s} \rightarrow \frac{T_1^2}{T_2^2}$

Equation 27 gives :—

$$\begin{aligned} Z_p &= j\omega L_p + \frac{\omega^2 M^2}{Z_s} \\ &= j\omega L_p + \frac{\omega^2 M^2}{j\omega L_s + Z_2} \\ &= \frac{-\omega^2 L_p L_s + \omega^2 M^2 + j\omega L_p Z_2}{j\omega L_s + Z_2} \end{aligned} \quad (28)$$

But $L_p L_s = M^2$

$$\therefore Z_p = \frac{j\omega L_p Z_2}{j\omega L_s + Z_2} \quad (29)$$

As $L_s \rightarrow \infty$, Z_2 can be neglected in the denominator.

$$\text{Hence } Z_p = \frac{L_p}{L_s} Z_2 = \frac{T_1^2}{T_2^2} \cdot Z_2 \quad (30)$$

Equation 17 is thus verified.

MAINS TRANSFORMERS**The core**

As mains transformers deal only with a low-frequency supply, usually 50 c/s, iron cores may be used. These are laminated to reduce eddy currents and related losses, each lamination being insulated by a coating of shellac or similar substance. The shape is normally as shown in Fig. 210, and suitable proportions are

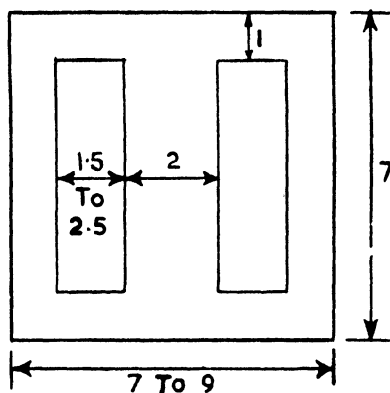


FIG. 210.—Typical transformer core stamping.

indicated. The core material is usually a silicon-steel alloy, such as stalloy, which has a high permeability and high resistivity, and consequently low losses.

The stack, or thickness, should be between 1 and $1\frac{1}{2}$ times the width of the centre limb. This permits ease of winding and is not thin enough to depreciate the transformer efficiency.

The optimum effective core area—*i.e.* the cross-sectional area of the centre limb—is given approximately by:—

$$A = \frac{\sqrt{W}}{5.58} \text{ sq. in.}$$

where W = volt-amperes output.

The windings

The windings are usually of insulated copper wire, and are made around the centre limb of the core, the other limbs serving to complete the magnetic circuit and so reduce its reluctance. The normal form of insulation for the wire is enamel, and the layers are interleaved with paper. To simplify construction, however, silk or cotton covered wire may be used and in this case interleaving will not be necessary. Some thicker insulation should be provided between the separate windings and between the core and the first layer.

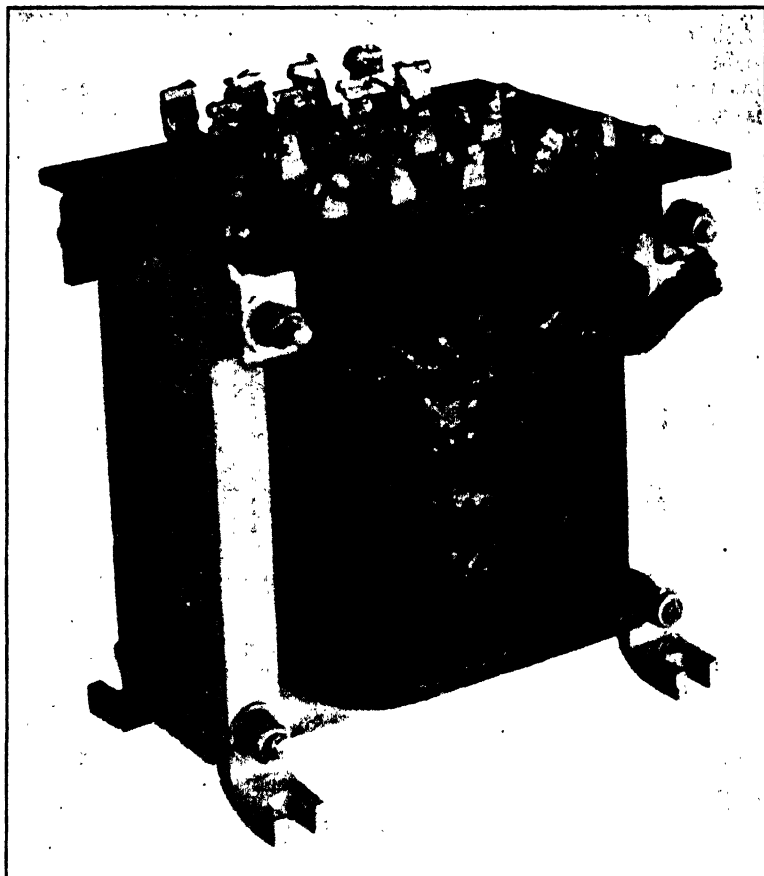


PLATE 9.—Mains transformer.

The number of turns required on the primary is given by the formula

$$N = \frac{0.225 \times 10^8 E}{f B_{max} A}$$

where

E = primary voltage

f = frequency in c/s

B_{max} = maximum AC flux density

and

A = cross-sectional area of core in sq. inches.

Power loss and temperature rise

It should be noted that with mains transformers, considerable power may be transferred; as the efficiency of an average transformer is about 90 per cent., the power wasted in the transformer and converted to heat energy may be quite large. This wasted energy is reduced to a minimum by the choice of a suitable gauge of wire for the primary and secondary windings; a very thin wire would give too great a resistance and cause too great a heat loss, with excessive rise in temperature and disastrous results. The standard upon which choice of wire should be based is that the gauge of wire for both windings should have a cross-sectional area of 1200 to 1500 circular mils per ampere. The following table has been drawn up to enable the correct gauge to be found at a glance :—

TABLE XI
Current-carrying capacity of copper wires

Current in Amperes	Required area in circular mils	Appropriate Wire Size S.W.G.	Ohms per 1000 feet at 60° F.
0·001	1·2	49	7,077
0·01	12·0	43	786
0·1	120·0	31	76
0·5	600·0	22	13·0
1·0	1200·0	20	7·9
2·0	2400	17	3·25
3·0	3600	16	2·49
4·0	4800	15	1·97
5·0	6000	14	1·59
6·0	7200	13	1·20
7·0	8400	13	1·20
8·0	9600	12	0·94
9·0	10,800	12	0·94
10·0	12,000	11	0·76
12·0	14,400	10	0·62
15·0	18,000	9	0·49
20·0	24,000	8	0·40
25·0	30,000	7	0·33

Notes.—A circular mil is the area of a circle of diameter 0·001 inch.

A check that the temperature rise will not be excessive can be obtained by adding the copper and iron losses and dividing the sum by the total surface area of the transformer. If the loss per square inch is less than 0·5 watts, then the temperature rise on load should not exceed 40° C. and operation will be satisfactory.

AUDIO FREQUENCY TRANSFORMERS

Line transformers

Line transformers are used to match lines, say, to 600 ohms for connecting to exchanges, *etc.* The primary inductance L_p must be large compared with 600 ohms at all frequencies transmitted, to prevent it causing a shunt loss in a 600 ohms circuit; it is therefore usually of the order of 1H. As power is to be transmitted, the winding resistances must be small; generally several hundred turns of medium gauge wire are used on a stalloy core with no air-gap. This gives a sufficiently large inductance, and a resistance on the 600-ohm side of less than 200 ohms. The disadvantage of this is the low saturation-level for the core, which prevents the transformer from being used with any large polarising DC or with 17 c/s AC ringing. If the latter is required, more turns must be used on a large core.

LETTER.	IMPEDANCE RATIO	
	LINE	EQUIPMENT
A	1	: 1
B	1.6	: 1
C	2.6	: 1
D	0.62	: 1
E	0.38	: 1
F	0.286	: 1
G	0.133	: 1
H	2	: 1
I	0.5	: 1


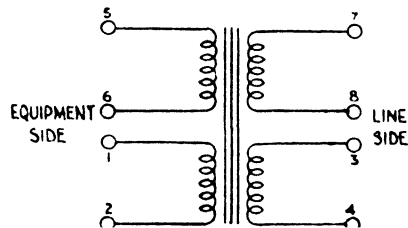


FIG. 211.—Line transformers, Types 48 and 50.


Line transformers are usually of the P.O. type 48 or 50. The type 48 will not pass 17 c/s ringing, whereas the type 50 will. The *impedance* ratio is indicated by a suffix in accordance with Fig. 211.

Amplifier input transformers

This covers transformers used for amplifiers, *etc.*, which work with a very large impedance across the secondary (such as the grid circuit of a valve). The primary impedance must be high in most cases (about 30H at audio frequencies if a very large input impedance is required), but as there is usually no polarising DC, this can be obtained by using a core with a large permeability—*e.g.* “radio-metal” or “mumetal”—with several thousand turns. If a large step-up ratio is required, the number of turns on the secondary must be very large. The secondary resistance is not important, as no current is flowing. The limiting factors are the secondary self-capacity referred to the primary, and leakage inductance, both of which increase rapidly with the number of turns. This gives a limit of about 1 : 5 if a large input impedance is desired; if the primary inductance can be dropped to, say, 1H, ratios up to 1 : 20

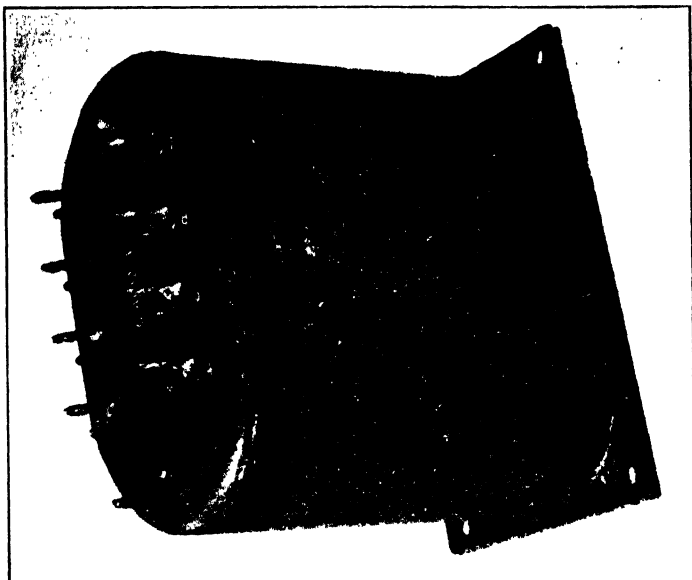

Type 50.

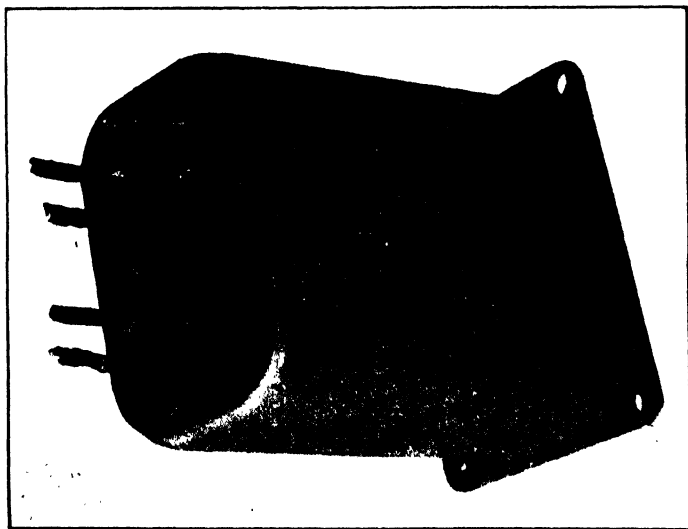

Type 48.

PLATE 10.—Line transformer.

can be obtained. The secondary capacity will resonate at some frequency with the leakage inductance, and if the secondary capacity is large, this resonance will occur within the frequency range of the amplifier, causing a peak in the response. This usually happens at about 10 kc/s.

Fig. 212 shows the equivalent circuit; in (b) the irrelevant components have been omitted. It will be seen that when L and C resonate, the voltage across C will be large, producing a peak in

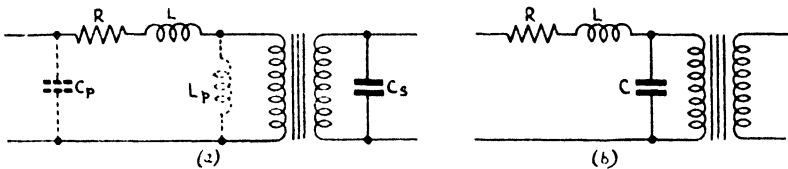


FIG. 212.—Equivalent circuit of input transformer.

the response. This can be damped by increasing (artificially) the resistance R , either by a series resistance in the primary or a resistance across the secondary. Above this resonant frequency the response drops, due to the shunting effect of C .

Interval transformers

These are similar to input transformers except that DC usually flows through the primary, and the primary inductance *must* be large as it represents the anode load on the first stage (see p. 390). This requires a core with an air-gap to prevent saturation, and a larger number of turns on the primary. This reduces the turns ratio to a maximum of about 1 : 3½.

Amplifier output transformers

These usually carry DC in the primary, and the primary inductance must be large compared with the load reflected from the secondary. As power is being transferred, the resistance of the windings must be low. The primary usually has several thousand turns of fine copper wire (30–40 S.W.G.), and the secondary is determined by the output impedance. The core is of stalloy or radiometal, with an air gap.

Auto-transformers

An auto-transformer is one in which the primary is part of the secondary, or vice versa (see Fig. 213).

The same formulae for voltage and current ratio still apply,

$$\text{i.e. } \frac{E_1}{E_2} = \frac{T_1}{T_2} = \frac{I_2}{I_1}.$$

Its main advantage is the fact that losses are reduced. For the current flowing through the secondary is, from Fig. 213, $(I_2 - I_1)$. This is less than I_2 , and hence causes smaller copper and flux leakage losses. This is particularly noticeable when $\frac{T_1}{T_2} \approx 1$, when

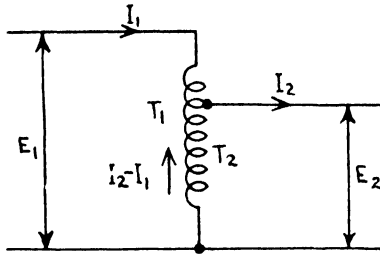


FIG. 213.—Auto-transformer.

I_1 and I_2 will be almost equal and the losses very small. Hence auto-transformers are most useful when a small turns ratio is required.

Fig. 214 shows a particularly useful form of auto-transformer used when it is desired to change the impedance of a circuit, and

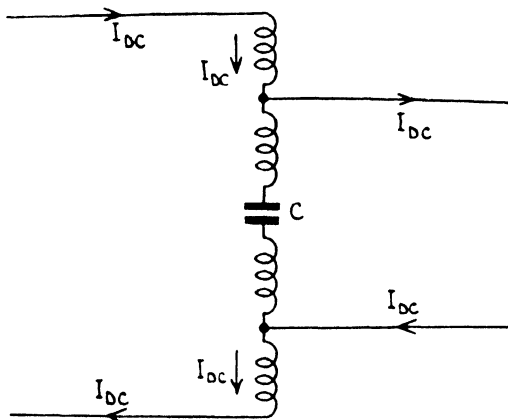


FIG. 214.—Auto-transformer with blocking condenser at centre tap.

yet still provide a DC path, say, for signalling or DC testing. The condenser C prevents a DC short-circuit being placed across the circuit by the transformer winding.

Core materials

1. *Iron*.—The maximum permeability depends on the purity, and is of the order of 10,000 to 20,000. Saturation level is high. Hysteresis and eddy-current losses are high.

2. *Silicon-iron alloys*.—Losses smaller than iron. Stalloy (4 per cent. silicon) is the most common type. Maximum permeability is about 15,000.

3. *Nickel-iron alloys*.—These alloys are characterised by low saturation level and high permeability at low flux densities.

Permalloy.—78 per cent. nickel, permeability up to 100,000.

Hypernik.—50 per cent nickel, similar to permalloy, but losses are smaller and saturation level is higher.

Mumetal.—73 per cent. nickel, 22 per cent. iron, 5 per cent. copper. High permeability, low hysteresis and eddy-current losses, low saturation level.

Radiometal.—Similar to mumetal, but with lower eddy-current losses and lower initial permeability.

Perminvar.—45 per cent. nickel, 30 per cent. iron, 25 per cent. copper. Constant permeability at low fluxes. Negligible hysteresis loss. Loses characteristics if not carefully treated.

4. *Cobalt alloys*.

Permendur.—50 per cent. iron, 50 per cent. cobalt. Has high permeability at high flux densities.

Pure iron is seldom used in transformers. Silicon-iron is used mainly in mains transformers and power transformers at audio frequencies, and also for smoothing chokes, etc. It is also used for interstage transformers carrying a polarising DC current.

Nickel-iron alloys are used principally for audio frequency transformers working at low voltages (such as found in telephony). Their high initial permeability enables large inductance values to be obtained without an excessive number of turns.

Cobalt alloys. Permendur is used chiefly for telephone receivers, etc., where the flux density is high.

At high carrier frequencies, thin nickel-iron stampings are generally used. Where losses must be kept to a minimum, toroidal dust cores can be used.

Distortion due to B-H curve

If a sinusoidal voltage is applied to a transformer, it follows from the basic theory that the flux must be sinusoidal. If no saturation takes place in the core, the B-H curve is linear, and the magnetising current will also be sinusoidal. If, however, saturation does occur, to maintain a sinusoidal flux the magnetising current cannot also be sinusoidal, but must increase when saturation occurs at each half cycle. A typical waveform is illustrated in Fig. 215.

This clearly causes distortion. If no DC is present, only *odd* harmonics will be produced. If two frequencies are applied simultaneously, this will lead to cross-modulation. As both these effects are undesirable, it is most important that hysteresis and saturation should be reduced to a minimum in audio frequency transformers.

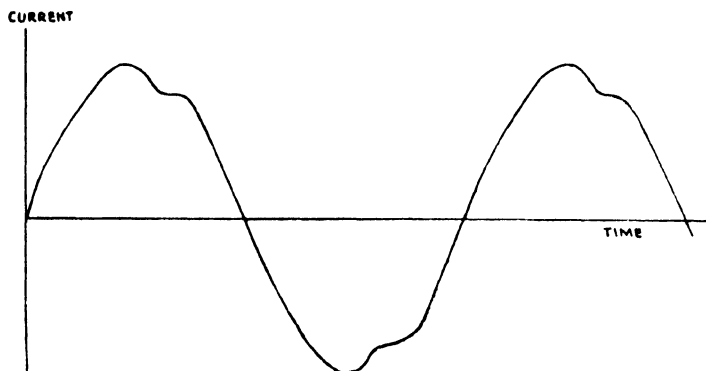


FIG. 215.—Typical waveform of transformer magnetising current for sinusoidal EMF of sufficient amplitude to cause saturation on peaks.

Interwinding capacities

To ensure that two halves of a winding are symmetrical about the centre point, special precautions have to be taken when winding the transformer, for not only must the two halves of the winding have exactly the same number of turns and resistance, but all capacities must also be balanced. The most convenient way of doing this is by winding the two windings together (*i.e.* two wires side by side) and connecting as in Fig. 216.

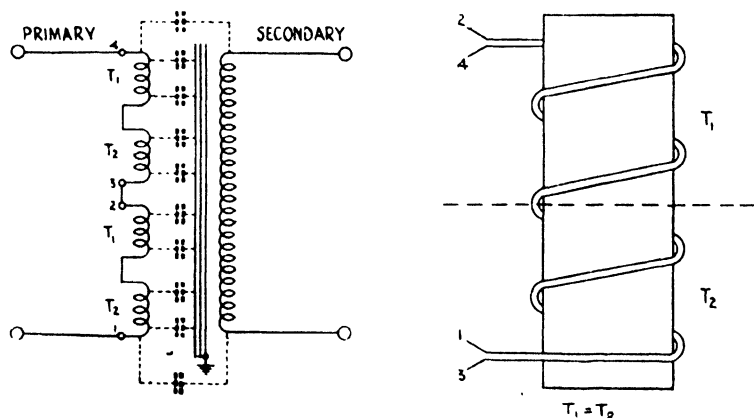


FIG. 216.—Method of balancing interwinding capacities.

It is sometimes also important that the capacity from primary to secondary should be kept to a minimum. This is done by inserting an earthed screen between the windings, increasing their capacity to earth but reducing the capacity between the two. The screen usually consists of a copper sheet covering the winding; the ends should overlap, but must not make electrical contact, since this would give the effect of a short-circuited turn.

BRIDGE CIRCUITS

The principle of the direct current Wheatstone's bridge (*see* page 129) can be extended to alternating current bridge circuits. Not only are these useful for measuring unknown impedances, but also some forms of AC bridge can be used for measuring frequency, while others find special applications in the circuits of telecommunication equipment.

General case of AC bridge

Let four impedances be connected as in Fig. 217, and an alternating voltage applied between *A* and *B*; then the bridge formed by these four impedances is said to be balanced when the instantaneous PD between *C* and *D* is always zero. If the applied voltage

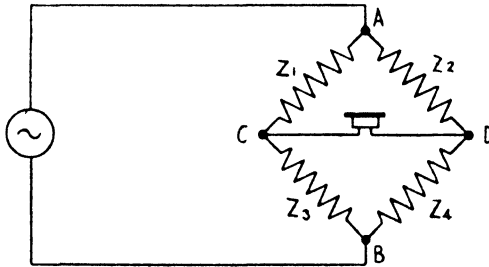


FIG. 217.—General case of AC bridge.

is of audible frequency, the balance condition can conveniently be found by adjusting one or more of the impedances for minimum sound intensity in a telephone receiver connected between *C* and *D*.

The condition for balance is found in the same way as for the Wheatstone's bridge, and is

$$Z_1 Z_4 = Z_2 Z_3 \quad (31)$$

This is a vector equation, since Z_1 , Z_2 , Z_3 , and Z_4 are impedances having both modulus and angle. If the impedances are written in the form $|Z| \angle \varphi$, this equation becomes:—

$$\begin{aligned} (|Z_1| \angle \varphi_1) \cdot (|Z_4| \angle \varphi_4) &= |Z_2| \cdot (\angle \varphi_2) \cdot (|Z_3| \angle \varphi_3) \\ \text{i.e. } |Z_1| \cdot |Z_4| \angle \varphi_1 + \varphi_4 &= |Z_2| \cdot |Z_3| \angle \varphi_2 + \varphi_3 \quad (32) \end{aligned}$$

This is equivalent to the two conditions:—

$$|Z_1| \cdot |Z_4| = |Z_2| \cdot |Z_3| \quad (33)$$

and

$$\angle \varphi_1 + \varphi_4 = \angle \varphi_2 + \varphi_3 \quad (34)$$

Both these conditions must be satisfied for a true balance to be obtained; two adjustments therefore have to be made, so that the bridge may be balanced with respect to both magnitude and phase angle (or, what amounts to the same thing, with respect to both resistance and reactance).

Impedance bridges

If one of the impedances in a balanced bridge is unknown, its value can be calculated from those of the other three, by equations 33 and 34. Frequently, however, it is desired to know the resistance and the inductance or capacity of a circuit component (e.g. a coil) rather than its impedance at one particular frequency. If the frequency of the supply is known, these can be calculated from the measured impedance.

Bridges that balance at all frequencies

When the equations of balance for certain bridges are solved for the values of the circuit constants (R and L or C) rather than of the impedance, the frequency f_0 of the applied EMF vanishes from the equations, and the required values are given in terms of the resistance, inductance, and capacity of the three known arms of the bridge. Bridges in which this occurs are said to be "independent of frequency"; they are particularly suitable for measurements of R , L , and C , since the frequency of the supply need not be accurately known, and a balance obtained at one frequency will hold at any other (provided that the circuit constants of the four bridge arms do not vary with frequency).

Bridges that balance at only one frequency

A bridge in which the frequency of the applied EMF does not vanish from the balance equations when they are solved for the circuit constants R and L or C is said to be "dependent on frequency". A balance obtained at one frequency on such a bridge will not, in general, hold at any other frequency, and hence if the values of the circuit constants of all four arms of the bridge are known, the frequency of the applied EMF may be calculated. A bridge of this type can therefore be used to measure frequency, in which case it is called a "frequency bridge".

Simplification of general case

In order to simplify the circuit, and to reduce the number of variables in the equations, it is usual in practice to make two arms

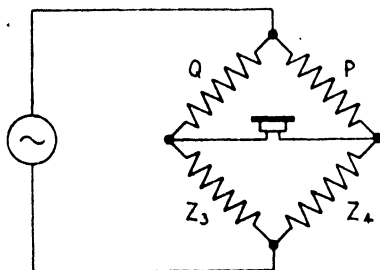


FIG. 218.—AC bridge with two adjacent impedances replaced by pure resistances.

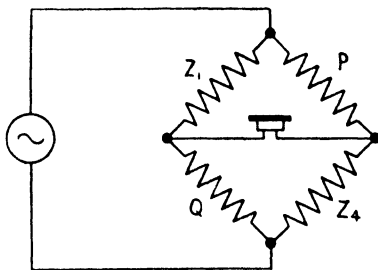


FIG. 219.—AC bridge with two opposite impedances replaced by pure resistances.

of an AC bridge purely resistive—say, for example, $Z_1 = Q$ and $Z_2 = P$, as in Fig. 218, or $Z_3 = Q$ and $Z_4 = P$, as in Fig. 219. The conditions of balance (equations 33 and 34) thus become:—

For Fig. 218:—

$$Q \cdot |Z_4| = P \cdot |Z_3|$$

i.e. $|Z_4| = \frac{P}{Q} \cdot |Z_3|$

and $\varphi_4 = \varphi_3$

and for Fig. 219:—

$$|Z_1| \cdot |Z_4| = P \cdot Q$$

i.e. $|Z_4| = \frac{PQ}{|Z_1|}$

and $\varphi_4 = -\varphi_1$

It can be seen that two conditions are still necessary for a balance to be obtained.

Adjustment of bridges

The two adjustments necessary to balance an AC bridge are not, in general, independent. It is necessary, therefore, to adjust one control until approximately minimum output is obtained from the detector (*e.g.* the telephone receiver in Fig. 217), then to adjust the other; and to repeat this process until the output cannot be further reduced.

Certain bridges have been developed in which one control governs the resistive balance, and the other the reactive; while in other bridges, one control enables the modulus of the impedances to be balanced, and the other the phase angle. Even in these bridges the adjustments of the two controls are not completely independent, and the procedure for balancing given above should be followed if accurate results are to be obtained.

Example of an AC bridge balancing at only one frequency (Series resonance bridge)

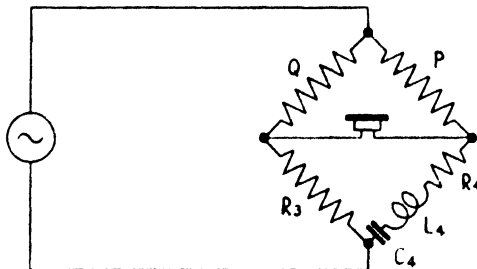


FIG. 220.—Series resonance bridge.

The condition for balance, from equation 32, is:—

$$Q \left[R_4 + j \left(\omega L_4 - \frac{1}{\omega C_4} \right) \right] = P R_3$$

$$\therefore QR_4 = PR_3 \quad \text{and} \quad \omega^2 L_4 C_4 = 1$$

This bridge can be used to measure an unknown inductive impedance ($R_4 + j\omega \cdot L_4$) if P and Q are fixed known resistors, and R_3 and C_4 are variable components whose values are known. Then :—

$$R_4 = \frac{P}{Q} \cdot R_3 \quad \text{and} \quad L_4 = \frac{1}{\omega^2 C_4}$$

It can also be used to measure an unknown frequency if the value of the inductance L_4 is known. The frequency is then given by :—

$$\omega^2 = \frac{1}{L_4 C_4}, \quad \text{or} \quad f = \frac{1}{2\pi\sqrt{L_4 C_4}}$$

The accurate adjustment of R_3 is necessary to obtain zero output in the telephone receiver, although R_3 does not appear in the formula for frequency.

Example of an AC bridge balancing at all frequencies (Maxwell bridge)

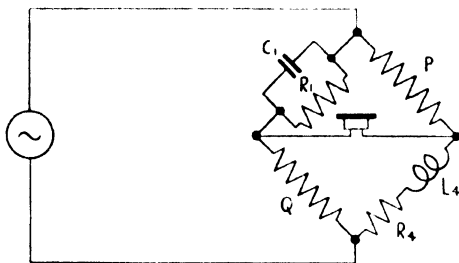


FIG. 221.—Maxwell bridge.

The condition for balance is :—

$$PQ = (R_4 + j\omega L_4) \cdot \frac{1}{\frac{1}{R_1} + j\omega C_1}$$

$$\text{i.e.} \quad \frac{PQ}{R_1} + j\omega C_1 PQ = R_4 + j\omega L_4$$

$$\text{i.e.} \quad R_4 = \frac{PQ}{R_1} \quad \text{and} \quad L_4 = PQC_1$$

This bridge also can be used for measuring an unknown inductance, and it has the advantage that the frequency at which the balance is made need not be known accurately. It could, clearly, not be used to measure frequency.

The Wien frequency bridge

An interesting and useful bridge is shown in Fig. 222.

Note that in the lower arms the two resistances and condensers are equal.

The condition for balance is :—

$$\frac{2P}{\frac{1}{R} + j\omega C} = P \left(R + \frac{1}{j\omega C} \right)$$

$$\therefore 2P = P \left(R + \frac{1}{j\omega C} \right) \left(\frac{1}{R} + j\omega C \right)$$

$$\therefore 2P = P \left[1 + 1 + j \left(\omega CR - \frac{1}{\omega CR} \right) \right]$$

$$\therefore \omega CR = \frac{1}{\omega CR}$$

$$\therefore \omega^2 = \frac{1}{C^2 R^2}$$

Thus the bridge balances if $f = \frac{1}{2\pi CR}$

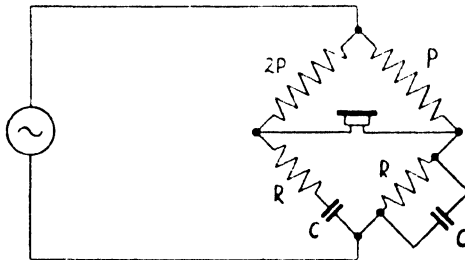


FIG. 222.—AC bridge (Wien) for measuring unknown audio frequencies.

This balances at one frequency only. If both resistances are made to vary simultaneously the bridge can be calibrated to measure frequency. The capacities C are normally fixed, but may be changed simultaneously to another fixed value to alter the frequency range of the bridge.

Summary of frequently used bridges

A table of the most useful impedance bridges is given on pages 272A and B, together with the equations by which one can calculate the value of the unknown impedance $Z = |Z|/\varphi = R + jX = \frac{1}{G + jB}$. These equations are obtained by substituting the appropriate values of $R_1, Z_1, etc.$, in equations 33 and 34, and are given in polar co-ordinate form $|Z|/\varphi$ in columns (f) and (g), and also in rectangular component form $R + jX$ in columns (h) and (j). From the latter, the values of resistance and inductance or capacity that give this impedance are calculated and are given in column (d).

In some cases the expressions for R and X are somewhat involved, while those for the corresponding admittance $Y = Z^{-1} = G + jB$ given in columns (k) and (l) are more manageable. In these cases, the impedance Z is more easily represented as a reactance ($j\omega L$ or $\frac{1}{j\omega C}$) in parallel with a resistance r (see column (c)).

The lamp bridge

The lamp bridge is used to indicate when a voltage departs from a preset value, or to maintain a voltage at a preset value. It depends for its action on the fact that the resistance of a lamp increases as the current through it is raised.

The basic circuit is shown in Fig. 223, where R_1 , R_2 and R_3 are normal resistances whose values are (for all practical purposes) independent of the current through them, and where R_4 is a lamp.

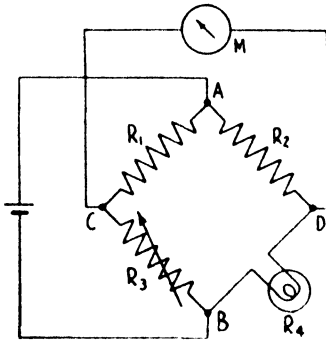


FIG. 223.—Lamp bridge: calibration on DC from battery.

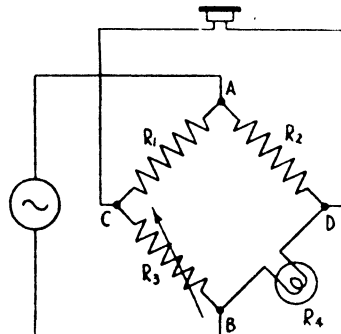


FIG. 224.—Lamp bridge: calibration on audio frequency.

With the standard voltage E applied between terminals A and B , R_3 is adjusted so that the bridge is balanced and the meter reads zero. Then $R_1R_4 = R_2R_3$.

If the voltage applied between A and B rises above the standard value E , the current both through R_1 and R_3 and through R_2 and R_4 increases. The increased current through R_4 raises its temperature, and therefore its resistance. The bridge then becomes unbalanced, and the potential of D rises above that of C , so that the meter M deflects. Similarly, if the applied voltage falls below the standard value E , the resistance of R_4 drops and causes the potential of D to drop below that of C ; the meter M then deflects in the opposite direction.

If the applied voltage be alternating, then the output across CD will again be zero when the bridge is balanced; if it be of audible frequency, this condition can conveniently be detected by means of a telephone receiver, as shown in Fig. 224. The terminals

A and *B* can then be connected to any EMF that it is desired to adjust to the same value E ; the amplitude of this EMF is then adjusted until no tone is heard in the receiver. This balance is independent of frequency.

When the EMF applied to *AB* is lower than E , then the voltage appearing across *CD* is in phase with it; and if it is higher than E , then this voltage is 180° out of phase with it. While this phase change is not evident from the headphones, it can be used automatically to control the output of an oscillator (*see* page 477).

CHAPTER 6

METAL RECTIFIERS AND POWER SUPPLIES

METAL RECTIFIERS

Rectification is the process of converting an alternating current into a direct current. This can be done by the use of the diode valve, which possesses the property of passing current only from the anode to the cathode. A valve, however, is not mechanically strong, and it requires an external power supply for its filament or heater circuit ; as an alternative, there are now two types of metal rectifier, the copper oxide rectifier and the selenium rectifier. Early metal rectifiers were large and cumbersome, but with subsequent development, they are now compact, robust, and efficient, and have become the accepted means of rectification in the majority of smaller power packs.

The copper oxide metal rectifier is made by coating one side of a copper disc with a layer of red cuprous oxide. The layer, being obtained by heat treatment, is very hard. This combination offers a low resistance to current flowing from the oxide to the copper, but an extremely high resistance to current flowing from the metal to the oxide.

The selenium type of metal rectifier is a more recent development. The selenium layer may be formed on almost any type of metal surface, but the one most commonly employed is nickel-plated steel. This layer of selenium is then sprayed with a low melting point tin alloy which forms the "counter-electrode" and makes the assembly mechanically sound.

Considerable research has been carried out to discover exactly where the asymmetrical resistance is introduced. The metals and alloys are all linear resistances and the oxide, though having non-linear resistance, is not asymmetric. The all-important asymmetry of the rectifier is thus assumed to be due to a layer existing between the cuprous oxide and the copper in the first case, and between the selenium and the counter-electrode in the second. This is termed the "barrier-layer" and, though its existence has not yet been definitely proved, it gives a satisfactory explanation of the rectifier action.

As, in practice, the "forward" resistance is not zero and the "backward" resistance is not infinite, considerable heat is evolved during operation, and, if no adequate cooling is provided, the resulting temperature rise will cause decrease of both forward and

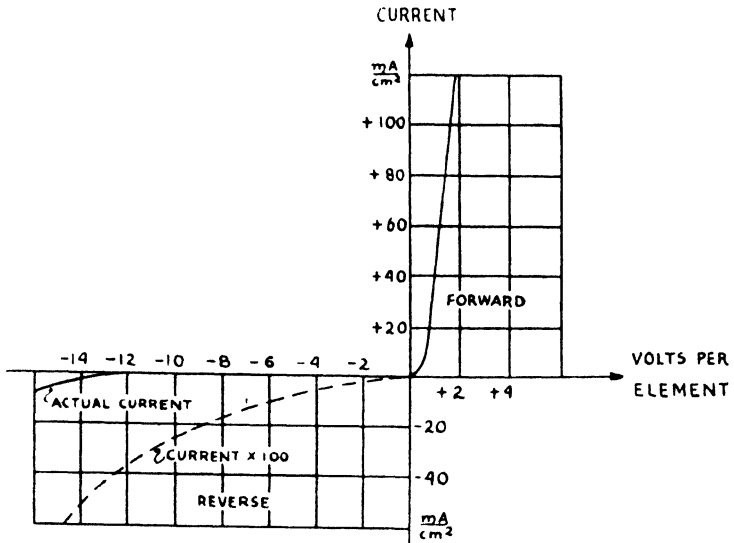


FIG. 225.—Characteristic of current against applied voltage for a typical selenium rectifier.

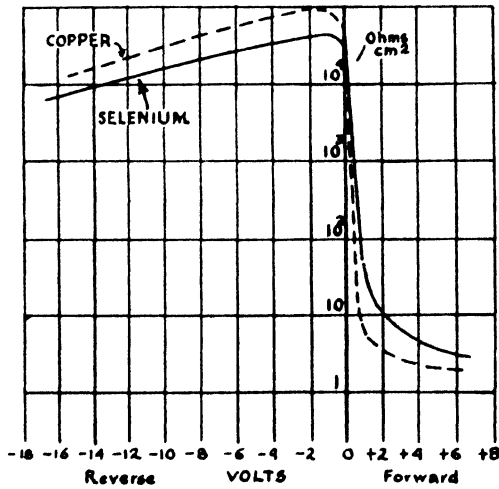


FIG. 226.—Resistance-voltage curves.

reverse resistances of both types of rectifier, thus altering their performance. An excessive rise may cause permanent damage to the rectifier.

For these reasons, rectifiers are designed for working at a certain ambient temperature, usually in the region of 30° C., and to stand a temperature rise of some 40° C. without great depreciation. An excessive rise in temperature is frequently prevented by the provision of cooling fins; a free circulation of air round the rectifier is always desirable, and in the case of large power plants this air circulation may be improved by the provision of fans.

Characteristics of metal rectifiers

It has been stated briefly that the rectifier offers a low impedance to current flowing in the forward direction and a high impedance to current in the reverse direction. This property is demonstrated more fully by the characteristic curves.

Fig. 225 shows the characteristic curve of a typical selenium rectifier. The broken curve shows the current (to 100 times the scale), when voltage is applied in the reverse direction. It illustrates clearly the very high resistance of the rectifier in this direction, and how it is reduced with increase of voltage. At reverse voltages higher than 18 volts, the rectifier may be considered to pass current, and hence for rectifiers working with higher voltages it will be necessary to use two or more such elements in series.

The copper oxide rectifier has a similar characteristic but may be considered to pass current after 8 volts per element in the reverse direction instead of the 18 volts for the selenium element.

In the forward direction, elements have a high impedance until the applied voltage is above $\frac{1}{2}$ volt per section for the copper oxide type, or $\frac{1}{3}$ volt for the selenium type. This property finds application in such apparatus as the acoustic shock absorbers fitted across some telephone receivers.

The above current-voltage characteristic can be translated into resistance values, and the resistance-voltage curve is thus obtained (*see* Fig. 226).

The copper oxide rectifier

Most of the qualities of this rectifier have been enumerated, but little has been said about its actual construction. This is illustrated diagrammatically in Figs. 227 and 228.

In the manufacturing process, rings or discs, about 1 mm. thick, of highly refined copper are heated in air to a temperature just above 1000° C. until a layer of cuprous oxide about 0.1 mm. thick has formed on the surface. The crystal structure of the oxide layer is modified by annealing processes, after which the discs are cooled. A thin film of black cupric oxide has by then formed over the red cuprous oxide, and has to be removed by chemical treatment.

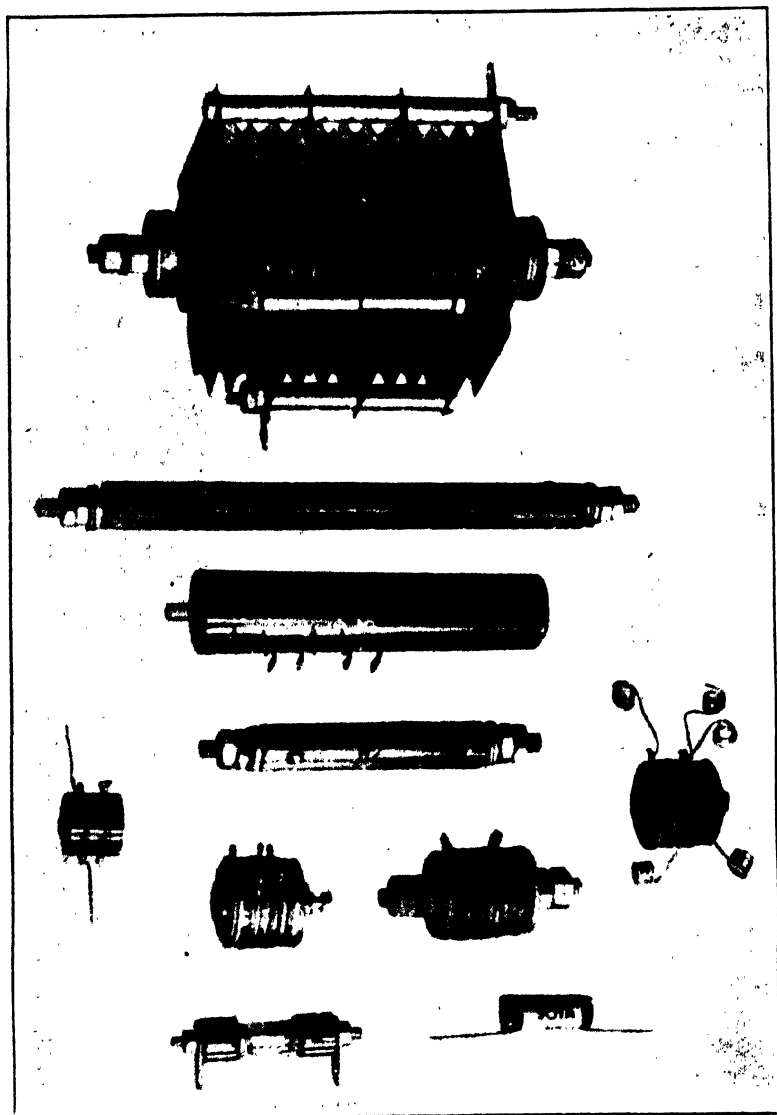


PLATE 11.—Copper oxide rectifiers

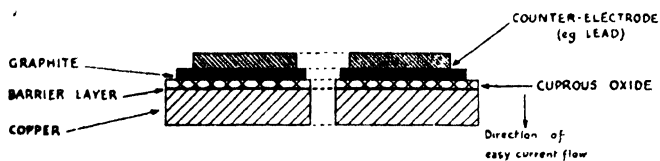


FIG. 227.—Copper-oxide rectifier element (passes conventional current $\text{Cu}_2\text{O} \rightarrow \text{Cu}$).

The cuprous oxide is painted with an aqueous suspension of colloidal graphite and finally covered by the "counter-electrode"—a soft metal (*e.g.* lead) plate or coating.

Copper oxide rectifier elements are rarely used singly owing to the limited reverse voltage that they will stand (6 to 8 v). They are usually connected in series, and must be maintained under

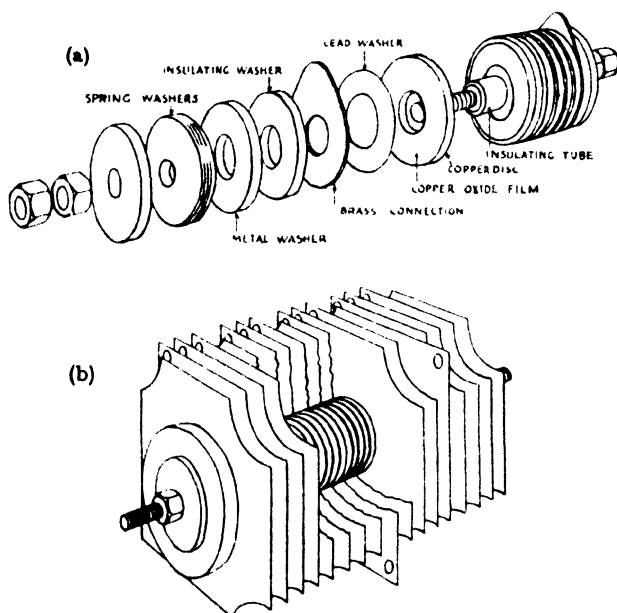


FIG. 228.—Copper-oxide rectifiers (a) without cooling fins, (b) with cooling fins.

a pressure of 50–60 lb. per square inch to ensure good contact between the lead, graphite and cuprous oxide. This last requirement complicates maintenance, since removal of the pressure tends to change the rectifier characteristics. Thus if one element breaks down, it will probably be found necessary to replace the whole series.

The selenium rectifier

Selenium rectifiers are usually formed on a nickel-plated steel surface. Selenium is applied to the base and, by heating in a hot press at about 130°C ., is formed into a homogeneous layer about 0.1 mm. thick. The temperature is raised to $180\text{--}215^{\circ}\text{C}$., changing the selenium into a grey crystalline form. A low melting point

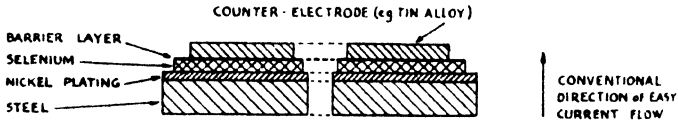


FIG. 229.—Selenium rectifier element.

alloy is now sprayed on to the selenium layer to act as a counter-electrode, and the manufacture is completed by an electrical forming process which considerably increases the reverse resistance.

The selenium rectifier does not require high pressure to ensure contact between the component layers and can thus be easily dismantled and repaired (contrast with the copper oxide rectifier).

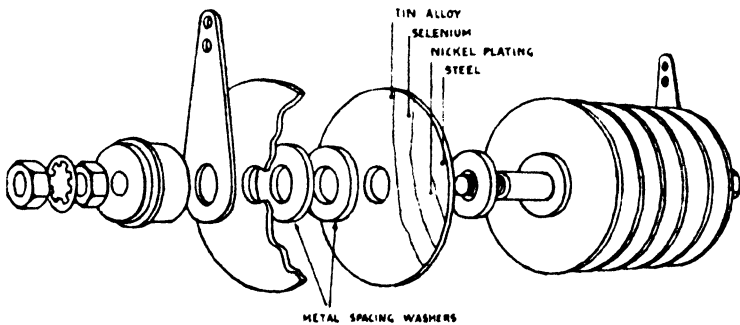


FIG. 230.—Selenium rectifier.

The lack of pressure enables the separate elements to be spread out, so that the steel plates can act as their own cooling fins.

One peculiar characteristic of the selenium rectifier is that, if it has been employed in the forward direction or with low voltage in the reverse direction, and is then suddenly required to operate with a high reverse voltage, an abnormally high reverse current will flow for an instant; after this, the rectifier resistance increases and the current is cut down to the value normally corresponding to that applied voltage.

SELENIUM RECTIFIER

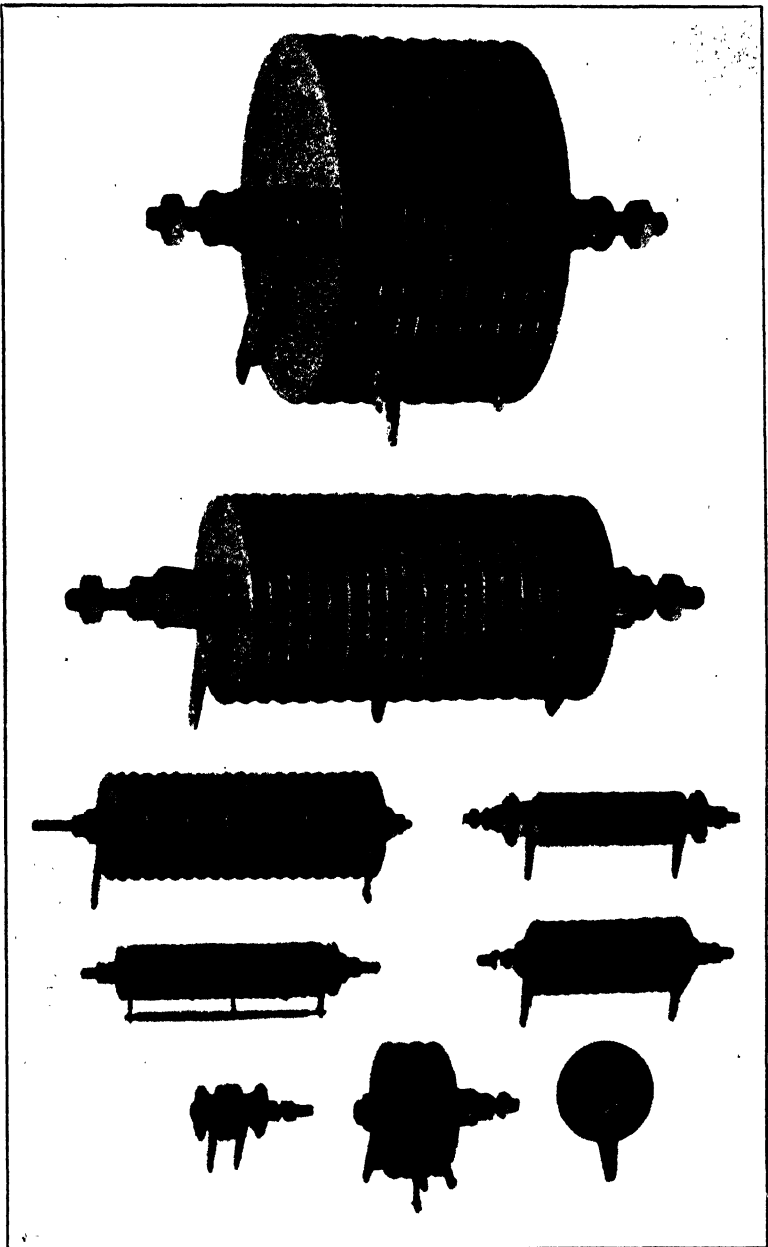


PLATE 12.—Selenium rectifiers.

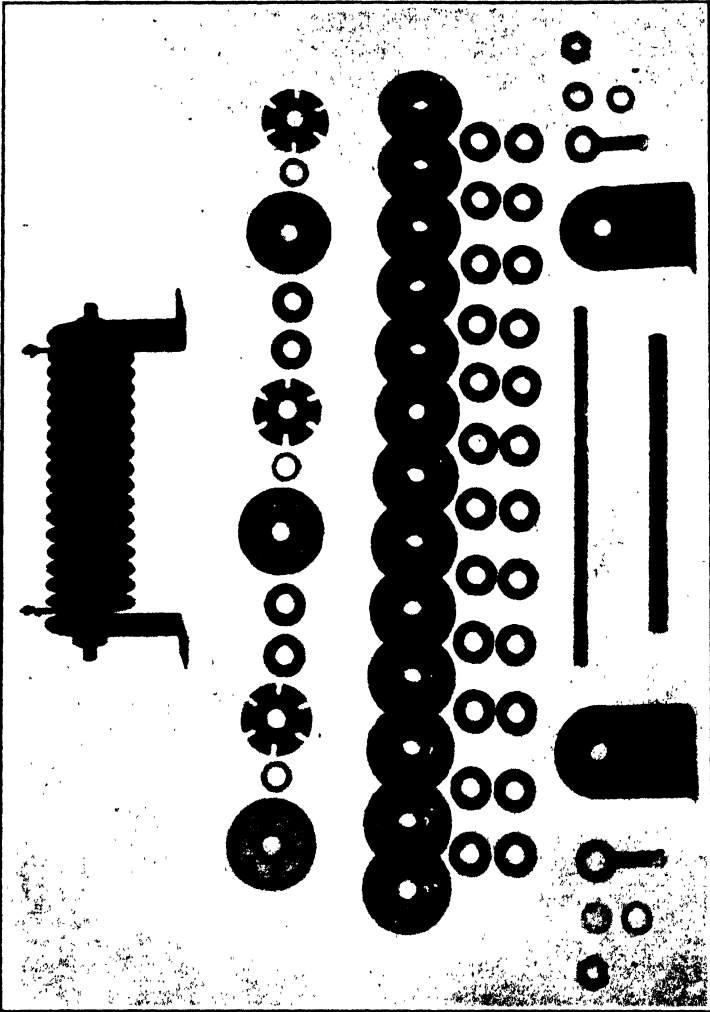


PLATE 13.—Selenium rectifier employing spring spacers, showing component parts.

Effect of temperature

The forward and backward resistances of both types of rectifier drop with increase in temperature ; this is illustrated in Figs. 231

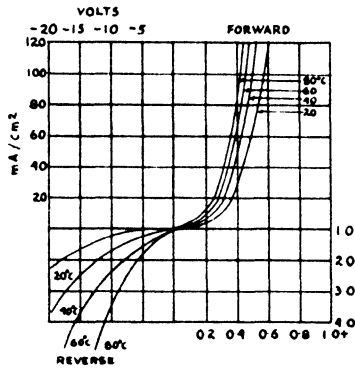


FIG. 231.—Effect of temperature on copper-oxide rectifier.

and 232. This determines the permissible current for a given power dissipation. Selenium rectifiers should be kept below 85° C., and copper oxide rectifiers below 55° C. This corresponds to a forward current of ½ to 1 amp per sq. in., though this value may be increased to 2-3 amps if special cooling arrangements are made.

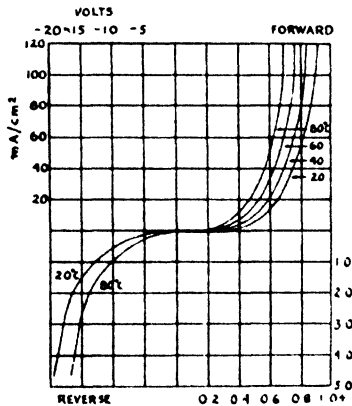


FIG. 232.—Effect of temperature on selenium rectifier.

Marking of rectifiers

Two alternative symbols for a rectifier are shown in Fig. 233a and b. The arrow shows the forward direction of "conventional" current flow ; the rectifier resistance is smaller in this direction.

RECTIFICATION CIRCUITS

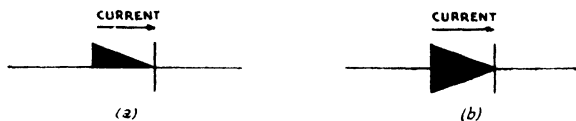


FIG. 233.—Standard symbols for rectifier, showing direction of conventional current flow.

The marking of the rectifier itself is shown in Fig. 234*a* and *b*. At first sight this may seem misleading; it should be remembered that the “+” or RED terminal of a rectifier is the terminal at which the current *leaves* the rectifier.

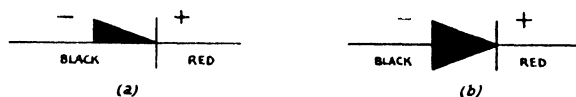


FIG. 234.—Symbols for rectifier, showing standard labelling of terminals.

Self-capacity of rectifiers

All rectifiers possess a certain amount of self-capacity, which is of some importance. For both types of rectifier, it is approximately $0.02 \mu\text{F}$ per sq. cm. of plate area, and is independent of frequency.

RECTIFICATION CIRCUITS

Half-wave rectification

The simplest method of rectifying an alternating current is to use a half-wave rectifier circuit.

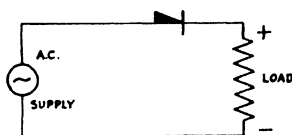


FIG. 235.—Series half-wave rectifier circuit.

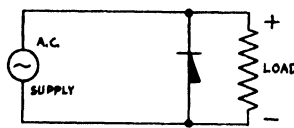


FIG. 236.—Shunt half-wave rectifier circuit.

Fig. 235 shows a circuit suitable for half-wave rectification; the half-cycle flowing clockwise in the load circuit will pass, while the anti-clockwise half-cycle will be impeded by the reverse resistance of the rectifier. Fig. 236 shows a circuit which will obtain a similar result; but, this time, the rectifier short-circuits the load during the forward half-cycle, and it is the reverse half-cycle which, finding high resistance in the rectifier, passes to the load.

The circuit shown in Fig. 235 will operate only if the AC source provides a path for DC. This is not essential for the circuit shown in Fig. 236. The load impedance should be less than the reverse impedance of the rectifier in Fig. 235, and greater than the forward impedance in Fig. 236.

In these two systems the output is as shown in Fig. 237.



FIG. 237.—Output from half-wave rectifier.

This constitutes a wastage of half the voltage supplied, and the system is only used when very little power output is required. The frequencies contained in the output are the supply frequency and its even harmonics.

Full-wave rectification

In other cases full-wave rectification is used (see Fig. 238).

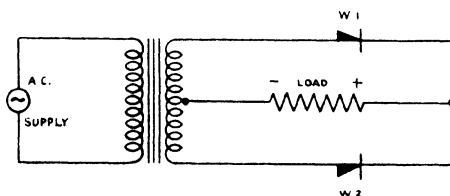


FIG. 238.—Full-wave rectifier circuit.

Each half-cycle is now utilised. On one half-cycle, current will flow through rectifier W_1 to load. On the other half-cycle, current will flow via W_2 to the load. The direction of current through the load will be the same for both half-cycles. But though "full-wave" rectification is now obtained, only half of the voltage across the transformer secondary is being applied to the load, and the provision of a centre-tap to the transformer is essential. The high voltage necessary across the secondary winding of the transformer may be a source of danger.

The "bridge" circuit

To avoid these difficulties, a rectifier bridge may be used as shown in Fig. 239.

The half-cycle of AC flowing clockwise around the circuit finds a low impedance in rectifiers W_1 and W_2 , and it therefore

flows through the load from right to left. The next half-cycle, flowing anti-clockwise, finds a low resistance path through rectifiers W_4 and W_1 , so that the current through the load is again from right to left.

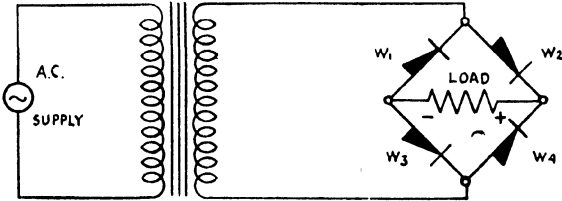


FIG. 239.—Bridge rectifier circuit.

The current reaching the load is now of the form shown in Fig. 240. The output contains even harmonics of the supply frequency, but no fundamental.

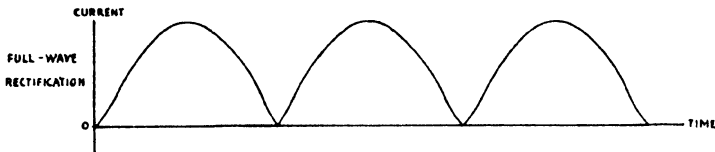


FIG. 240.—Output from full-wave rectifier.

This bridge circuit is generally used in cases where currents of 0.5 amp and upwards are required.

Voltage doubler circuits

If a high voltage and small current output is required, a voltage doubler circuit may be employed. Fig. 241 shows a typical full-wave voltage doubler circuit.

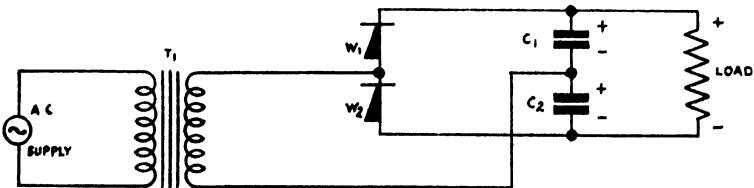


FIG. 241.—Full-wave voltage doubler circuit.

Consider a half-cycle that makes the top of the secondary coil of T_1 positive, and the bottom negative. Current will flow through rectifier W_1 , charging the condenser C_1 to the voltage of the supply. During the next half-cycle the condenser C_2 will be charged and, as both condensers are charged as shown, the final voltage across

the load will be twice that of the supply. This will apply, however, only if the load is taking no current; current drain will prevent the condensers from reaching their full charge, and the voltage will in practice never be quite double that of the supply. The percentage by which it falls short of the double value will depend upon the current drain, and the circuit is normally used only when the current drain is very small.

A modified form of the full-wave voltage doubler circuit* is shown in Fig. 242a.

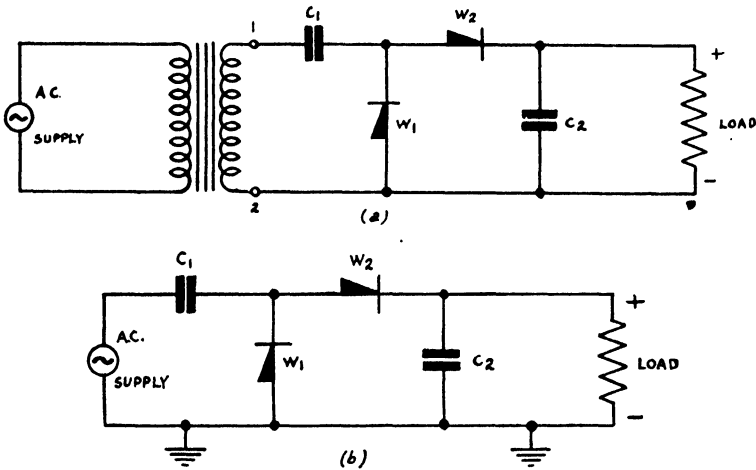


FIG. 242.—Modified full-wave voltage doubler circuit.

Consider a half-cycle that makes terminal 1 of the transformer secondary negative, and 2 positive. Current will flow through rectifier W_1 and charge condenser C_1 , but, owing to the low impedance offered by the rectifier W_1 and the high impedance of rectifier W_2 , no current reaches the load. During the next half-cycle, rectifiers W_1 and W_2 have high and low impedances respectively. The voltage already across condenser C_1 , plus the voltage across the secondary, is therefore applied across condenser C_2 and the load. Thus, though in the first half-cycle no voltage was applied to the load, in the second half-cycle twice the voltage is applied, utilising the charge obtained from the first.

Condenser C_2 acts as a "reservoir"; that is, it stores the charge and maintains the voltage across the load during the half-cycles charging condenser C_1 .

The above circuit is often used when one side of the supply and one side of the load are both earthed. In this case the transformer may be dispensed with, as in Fig. 242b.

* In American literature, this is often known as a "half-wave" voltage doubler circuit.

Two voltage doubler circuits may be arranged in the form of a voltage quadrupler, as in Fig. 243.

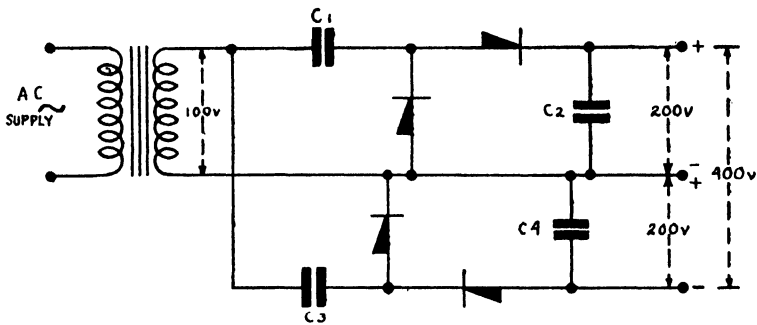


FIG. 243.—Full-wave voltage quadrupler circuit.

Such circuits are successful only when the current taken is extremely small.

AC METERS

It is clear that meters will be required for making measurements of alternating currents and voltages. Various forms of DC meters have already been described; the effect of AC on these will be considered.

Moving coil meters

The deflection is proportional to the current i ; if i is an alternating current of very low frequency the meter will be able to follow the alternations, and will move from side to side about the zero mark. If, however, the frequency is high, the meter will be unable to follow the variations but will read the average value of the current—*i.e.* zero. Hence a pure alternating current will not deflect a moving coil meter, which is therefore of no application in AC measurements. On the other hand, if a current consists of DC plus an alternating component, a moving coil meter in the circuit will read the DC and be unaffected by the AC—a useful property.

Moving iron meters

The deflection of a moving iron meter is proportional to i^2 , and for a DC meter the scale is calibrated to read the square root of this, *i.e.* to give a direct reading of current. If i is an alternating current of a sufficiently high frequency the meter will give a steady deflection proportional to the mean value of i^2 . This is not zero, but is equal to $[I_{RMS}]^2$, and hence the scale will read I_{RMS} —the root mean square value of the current. Hence moving iron meters will respond to AC, and will give a reading of the RMS value. If the current consists of AC and DC, the meter will read $\sqrt{I_{DC}^2 + I_{RMS}^2}$.

The operation of these meters is satisfactory at mains frequencies, but they are seldom used for audio-frequency work. Their principal disadvantage is low sensitivity.

Hot-wire and thermo-couple meters

These both depend upon the heating effect of the current, and hence operate satisfactorily from AC, giving readings of RMS values. Their main advantage is that they can measure AC at any frequency, but they suffer from the disadvantage that they have a very small overload safety margin—the majority of meters of this type being permanently damaged by a 50 per cent. overload.

Rectifier meters

It has been seen that certain types of meters operate directly from AC; more commonly, however, the AC is rectified and measured on a DC meter. Using metal rectifiers, this method is satisfactory up to frequencies of about 100 kc/s, and enables a

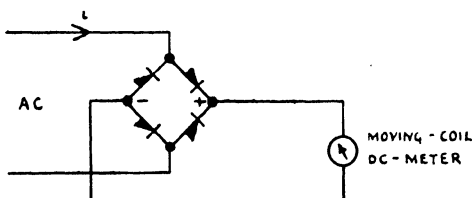


FIG. 244.—Bridge rectifier applied to meter.

moving-coil DC meter to be used with consequent high sensitivity. It is usual to employ a full-wave rectifier bridge for this purpose, consisting of copper oxide elements, the circuit being as shown in Fig. 244.

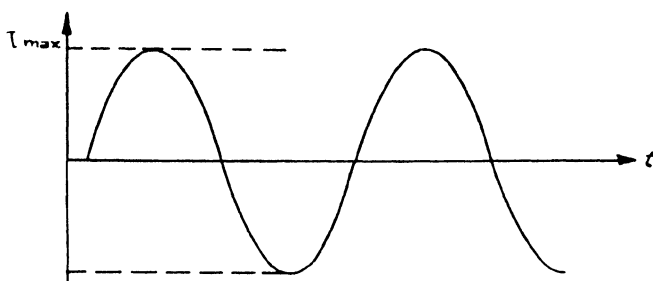


FIG. 245.—Sinusoidal alternating current applied to rectifier.

It is important to know what relationship exists between the alternating current or voltage and the meter deflection. It will be shown that the deflection is directly proportional to the alternating current, but not to the alternating voltage. Suppose the current i is of the form shown in Fig. 245—a sine wave, of peak value I_{max} .

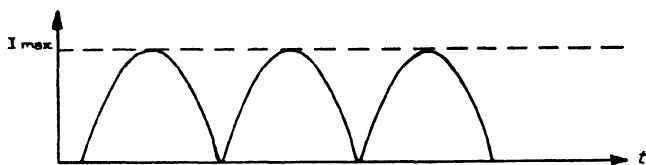


FIG. 246.—Rectified current applied to meter.

The rectified current will be of the form shown in Fig. 246.

The peak value will be I_{max} , for in a metal rectifier working below overload point the leakage current is negligible—less than 1 per cent. The meter deflection will be proportional to the mean value of this waveform; it can be shown that (for a sine wave) this is equal to $0.637 I_{max} = 0.9I$, where I = RMS value of alternating current. Hence the reading of a DC meter would have to be multiplied by 1.11 to give the RMS value of the current, or alternatively the scale could be recalibrated. Note that the meter scale will still be linear—*i.e.* the deflection is directly proportional

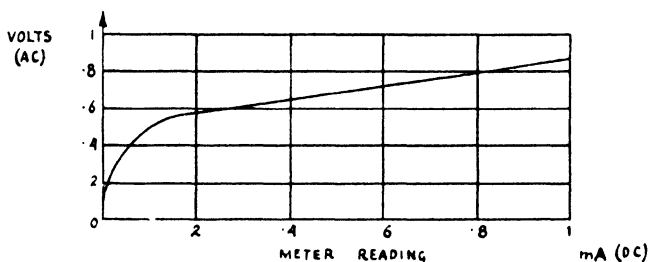


FIG. 247.—Voltage drop across AC meter and rectifier.

to the alternating current. It is most important, however, to note that, although no *current* is lost in the rectifier, a *voltage* drop is introduced. This voltage drop does not vary *linearly* with the current, so that the total impedance of rectifier plus meter is *not constant*. Fig. 247 shows the voltage drop across meter plus rectifier for a typical 1 mA rectifier meter with a coil resistance of 100 ohms.

This means that if the meter is used to measure the voltage across its terminals (*i.e.* is used as a voltmeter) the scale will not be linear at the bottom end.

Rectifier voltmeters

It has just been shown that, as the impedance of a rectifier meter varies with the current through it, it cannot be used as a voltmeter without recalibration. This is true only when small voltages have to be measured; when large voltages are to be measured, a large dropping resistance must be put in series with the meter, and this will "swamp" any variations in the impedance

of the meter, and hence give a linear scale. Thus, for example, with a 1 mA meter used to give a full-scale deflection (FSD) on 100 volts the drop across the rectifier plus meter is less than 1 volt, so the error cannot be greater than 1 volt on the scale.

Calculation of resistances for voltmeter

If the voltage drop across rectifier plus meter at full scale deflection is known, this can be subtracted from the required full-scale deflection voltage to give the required voltage drop in the series resistance. This resistance can then be calculated as follows:—

$$R = \frac{\text{Required voltage drop}}{1.11 \times \text{meter FSD current (DC)}}$$

(The denominator is of course the *alternating* current required for full-scale deflection.)

For example: consider the 1 mA meter already mentioned: a full-scale deflection is required on 10 volts.

At full-scale deflection the meter voltage drop is, from Fig. 247, about 0.86 volt. Hence 9.14 volts must be dropped in the series resistor at full-scale deflection, *i.e.* when the direct current is 1 mA and the alternating current is 1.11 mA (RMS).

$$\text{Hence } R = \frac{9.14 \times 1000}{1.11} = 8227 \text{ ohms.}$$

The circuit is therefore as shown in Fig. 248.

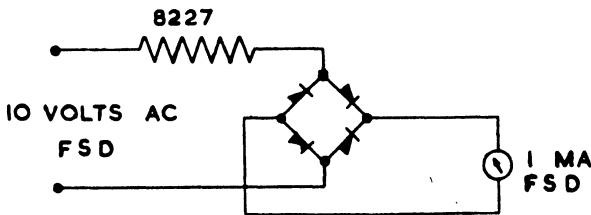


FIG. 248.—Use of series resistance with rectifier-type milliammeter to measure voltage.

Note that there will be an appreciable error at low voltages, as 8227 ohms is not very large compared with the meter impedance. Thus when the meter reads 0.2, the alternating current flowing will be 0.222 mA, giving a drop of 1.83 volts across the 8227 ohms resistor. The voltage across the meter is (from Fig. 247) 0.57 volts, so the terminal voltage is $1.83 + 0.57 = 2.4$, and not 2. In this case it would be necessary to provide another scale on the meter, or a calibration chart, for accurate measurements. Suppose, however, that the same meter was required to give full-scale deflection on 100 volts; the voltage drop in the meter at full-scale deflection is 0.9 volts, so $R = \frac{(100 - 0.9)}{1.11} \times 1000 = 89,190$ ohms.

In this case, when the meter reads 0·2 and the alternating current is 0·222, the voltage drop across R is 19·8, and that across the meter is 0·57, so the terminal voltage is 20·4, corresponding to an error of about 2 per cent. In this case the scale is reasonably accurate, and recalibration is probably unnecessary.

High current ranges

The range of a DC milliammeter is increased by the use of shunts; in AC meters, however, as the impedance varies with current, the multiplying factor of a shunt would also vary, and the meter would require separate scales for each range. For this reason, shunts are seldom found in AC meters; current transformers are used instead. For example, suppose the 1 mA meter is required to read 100 mA; the turns ratio can be calculated as follows (see Fig. 249).

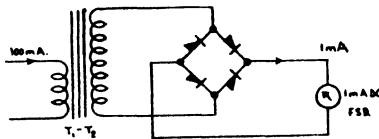


FIG. 249.—Use of current transformer to measure large currents.

The secondary alternating current required to produce 1 mA DC is 1·11 mA AC (RMS) and this is required when the primary current is 100 mA.

$$\text{Hence } \frac{T_1}{T_2} = \frac{1 \cdot 11}{100} = 1 : 90.$$

Similarly, to read 1 amp, the ratio would be 1 : 900. The most important point in current transformer design is to keep the iron losses to a minimum. In the example given, the secondary would in practice probably be wound with 900 turns, giving 10 and 1 turns for the 100 mA and 1 amp primaries respectively. For measurements of larger currents, the primary often consists of a straight bar of metal with the secondary wound toroidally round it.

It is most important to ensure that the meter is never disconnected from the secondary while the primary current is flowing; for its removal might well increase the primary impedance 100 times, with a corresponding rise in secondary voltage. In many instances this is sufficient to destroy the transformer. If the meter were disconnected but the rectifier left in circuit, the rectifier would certainly be burned out.

Low voltage meters

It has been seen that rectifier meters do not give linear scales at low voltages. This can be overcome by using a transformer to step up the voltage and inserting a large resistance in series with the meter. Linearity is thus obtained, but at the expense of sensitivity.

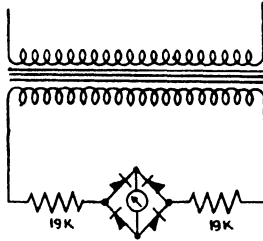


FIG. 250.—Use of voltage transformer.

An example of this is the decibel-meter (Fig. 250), which has to give a full-scale deflection on 0.775 volt. Here, a step-up ratio of about 1 : 2 is used, with a $40\mu\text{A}$ FSD meter and 38,000 ohms in series.

Frequency errors

For rectifier meters without transformers, these are negligible up to 100 kc/s. The performance of transformer meters depends on the design and construction of the transformer, but the response can usually be made flat over the audio-frequency range.

Temperature errors

These affect principally the voltage drop across the rectifiers, and can therefore be neglected in those circuits where this voltage drop is made to have little effect.

FURTHER APPLICATIONS OF RECTIFIERS

Biasing of rectifiers

It has been seen that the resistance of a rectifier depends on the DC voltage applied to it. When a DC voltage is applied in such

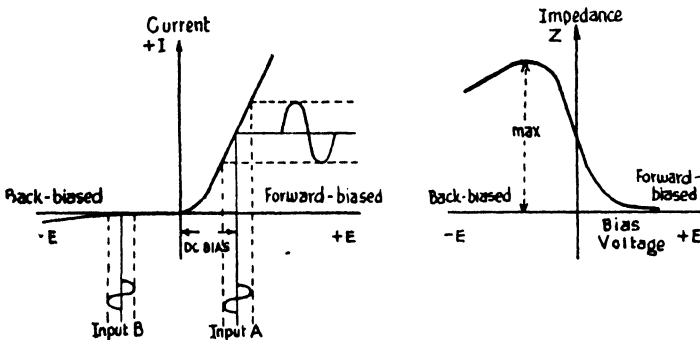


FIG. 251.—Variation of rectifier impedance with bias.

a direction that the rectifier offers a low resistance, the rectifier is said to be "forward-biased." If the voltage is reversed, the rectifier is said to be "back-biased."

Consider, in addition to a large forward-biasing voltage, the application of a small AC voltage (input *A*, Fig. 251). The current flowing will contain a large alternating component, and the rectifier therefore offers a low impedance to the AC voltage. The magnitude of this impedance depends on the slope of the current-voltage characteristic curve of the rectifier, and hence on the DC biasing voltage.

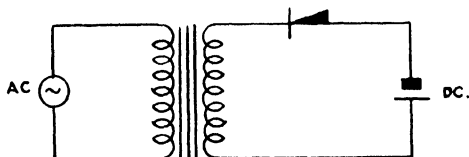


FIG. 252.—Method of applying AC and DC independently to a rectifier.

If the DC biasing voltage is now changed, so that the rectifier is back-biased, and the same alternating voltage again applied (input *B*), very little current will flow, and the alternating component will be negligible. The rectifier therefore offers a high impedance to the AC voltage under these conditions.

Fig. 251 also shows the variation of impedance with bias voltage, it being noted that the rectifier offers its maximum impedance when an optimum bias voltage is applied.

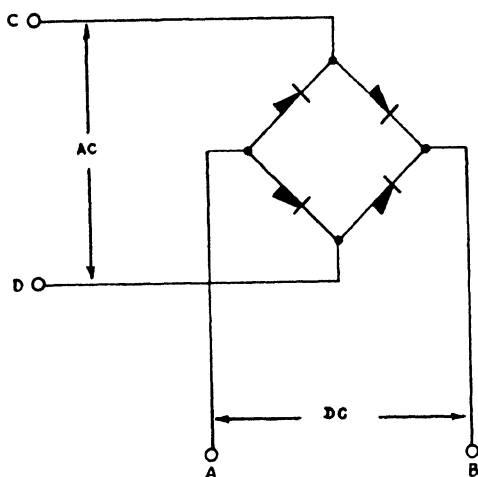


FIG. 253.—Alternative method of applying AC and DC independently to a rectifier network.

One of the many ways of applying AC and DC separately to a rectifier is shown in Fig. 252. Another commonly found method is shown in Fig. 253; this circuit is in fact a full-wave rectifier bridge, but it is more convenient not to regard it as such. Clearly, if the DC bias is applied with *A* positive and *B* negative, the

rectifiers will all be forward-biased, and the AC impedance across CD will be low. If, however, B is positive and A is negative, the rectifiers will all be back-biased, and the AC impedance will be high.

These elementary circuits form the basis of many ingenious devices employed in line communication. Some common examples will now be considered.

Variable attenuators

A typical variable attenuator circuit is shown in Fig. 254. The input is applied across a "bridge" circuit having a rectifier W_1 in one arm, and a $250\ \mu\text{F}$ condenser in the other. The output from the other diagonal of the bridge appears across $A-B$. If W_1 is back-biased, its impedance is high, and is balanced roughly by the $250\ \mu\text{F}$ condenser; in this case little output will appear across $A-B$, and the attenuation will be high. If W_1 is forward-biased, the bridge will be unbalanced, and the attenuation low.

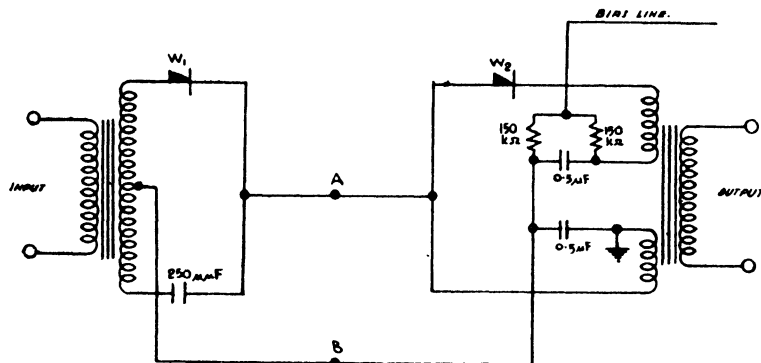


FIG. 254.—Typical variable attenuation circuit.

The output across $A-B$ is applied to another bridge circuit consisting of a rectifier W_2 , balanced in this instance by a short-circuit in the opposite arm. The other diagonal of this bridge is connected through a transformer to the attenuator output. This second bridge is roughly balanced when W_2 is forward-biased. Hence, for high overall attenuation, W_1 must be back-biased and W_2 forward-biased. For low attenuation, these biases must be reversed. By adjusting the bias to intermediate values, any desired attenuation may be obtained.

This is effected by applying a voltage to the "bias line". If the DC paths are traced out, it will be seen that a positive potential to earth on the bias line causes W_1 to conduct and W_2 to be back-biased, giving low attenuation. On the other hand, a negative potential on the bias line reverses the biases, and gives high attenuation. The attenuation may thus be varied by adjusting the DC bias voltage.

Voltage limiters

Voltage limiters are designed to prevent the voltage at a point in a circuit from exceeding a certain peak value. This peak value is usually quite small, the commonest form of voltage limiter being the "crash limiter" used across telephone receivers. In its simplest form, this consists of two rectifiers back to back (*see*

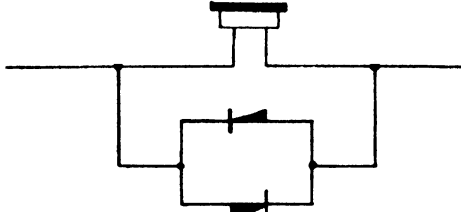


FIG. 255.—Use of rectifier as voltage limiter.

Fig. 255). When the voltage across the receiver exceeds 0.25 volt, the forward resistance of one or other rectifier drops, and shunts the receiver. This has the effect of limiting the voltage at that point.

It is possible to control the voltage at which limiting takes place by applying an initial DC back-bias to each rectifier, as in

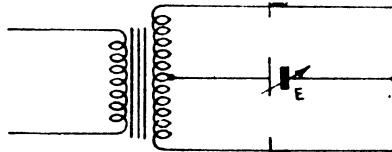


FIG. 256.—Biased voltage limiter.

Fig. 256. Here the voltage across each rectifier is E volts back-bias, plus the alternating voltage across half the transformer secondary. When the alternating voltage exceeds E , limiting will occur. By varying E , the level at which limiting occurs may be adjusted.

Certain materials have an impedance that drops as the applied voltage is increased in either direction, and these also are used as limiters. An example of this is the "ATMITE*" disc used in certain three-channel carrier telephone systems. Its current-voltage and impedance-voltage characteristics are shown in Fig. 257*a* and *b*.

Fig. 258 shows such a disc used as a voltage limiter at the input to the modulator on a multi-channel carrier telephone system. Its function is to prevent overloading of the transmitting equipment and consequent distortion; the effect on intelligibility is negligible. When the level of the input is 1 mW, the disc has high impedance and its shunting effect is nil. As the level increases, however, the resistance of the disc decreases and its shunt effect limits the level passing through the pad to the modulator.

* ATMITE is a Trade Mark owned by Automatic Telephone & Electric Co., Ltd., and is used by them to denote the particular non-linear resistance material which they market.

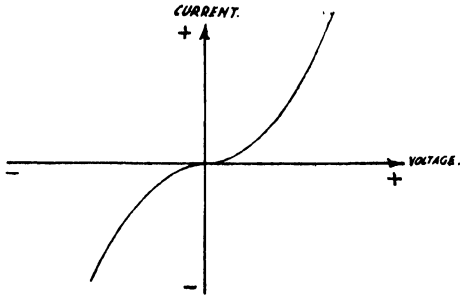


FIG. 257a.—Current-voltage characteristic of an ATMITE disc.

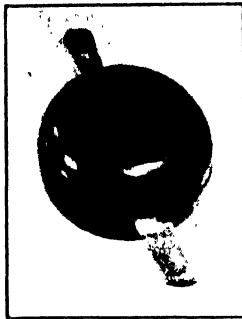


PLATE 14.—ATMITE disc.

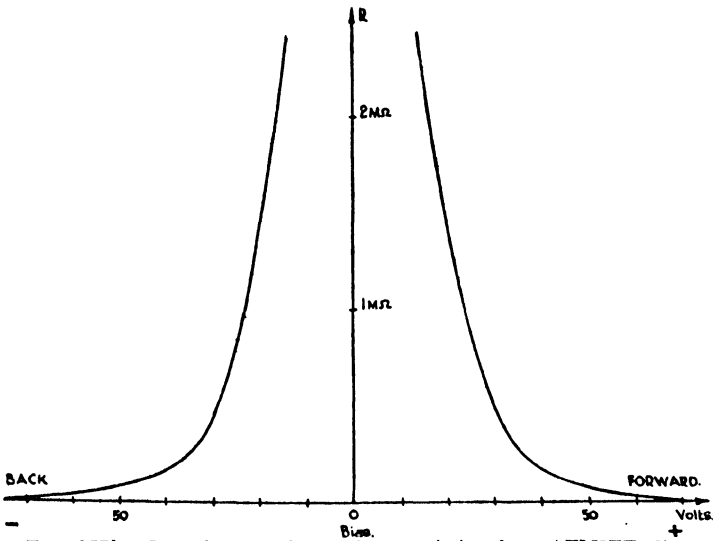


FIG. 257b.—Impedance voltage characteristic of an ATMITE disc,

LIMITERS

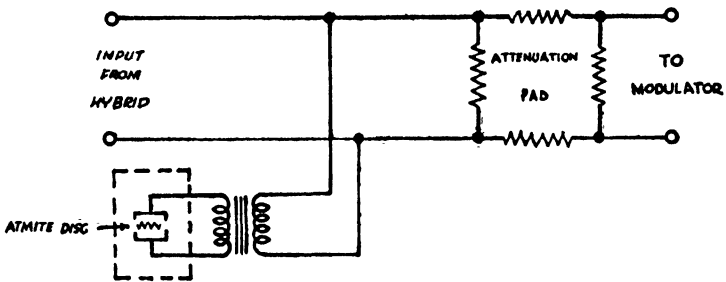


FIG. 258.—Use of ATMITE disc as voltage limiter.

The action of the limiter can best be seen from Fig. 259, which shows the voltage passing to the pad plotted against the voltage applied from a circuit having an impedance of 600 ohms, with the limiter in and out of circuit.

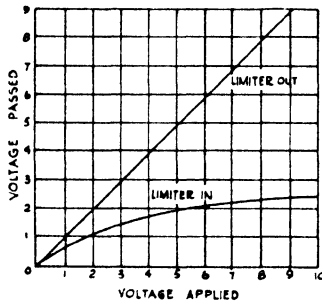


FIG. 259.—Action of ATMITE disc voltage limiter.

To show that the ATMITE disc causes little distortion, the output of a normal buzzer unit is given in Fig. 260. Fig. 260a shows the output of the buzzer, and Fig. 260b shows the same output after passing the limiter.

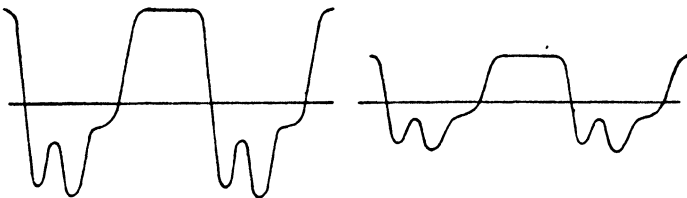


FIG. 260.—Effect of ATMITE disc on output of buzzer unit (obtained from CRO traces).

In addition to its use as a limiter, an ATMITE disc is occasionally used as a spark quench across relay contacts. By reducing voltage surges, it prevents sparking.

Relay slugging

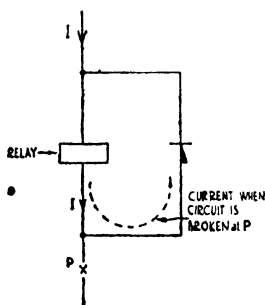


FIG. 261.—Rectifier as relay slug.

A rectifier in shunt with a relay coil can be used to make the relay slow-to-release. Consider Fig. 261; in the normal condition, with the relay operated, the rectifier is connected in such a direction that it will not shunt the relay. Without the rectifier, if the relay circuit be broken at P , the relay would release quickly. With the rectifier in place, however, the inductance of the relay tends to maintain a current through the low resistance of the rectifier. Until this current dies down, the relay will not release.

Meter shunts

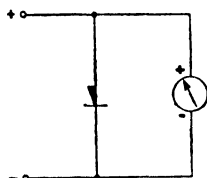


FIG. 262.—Rectifier as meter shunt.

Connected across a meter, a rectifier will act as a shunt whose resistance drops as the applied voltage increases. This has the effect of closing up the top end of the meter scale. With care, an approximately logarithmic scale can be obtained.

POWER SUPPLIES

Equipment in which thermionic valves are used always requires a DC high tension (HT) supply. This is not usually immediately available, but has to be derived from some other source—either AC mains or a low-voltage DC battery. For this purpose, some sort

of power supply unit has to be used. It is essential that the HT provided should have a minimum amount of AC present, and that the DC voltage should not vary appreciably when the current taken from the supply changes. The first problem (reducing the "ripple") is referred to as "smoothing"; the second (keeping the output voltage constant) is referred to as "regulation". These problems will now be discussed, together with various forms of power supplies.

Smoothing circuits

The output from a rectifier has been seen to consist of pulses of DC, and these can be shown, by Fourier's analysis, to consist of a steady DC component, equal to the mean value of the pulses, plus a large number of alternating components. For half-wave rectification, the DC component is equal to $\frac{1}{\pi}$ times the peak value of the pulses, and for full-wave rectification it is twice this value (see page 117). The alternating components, however, form a ripple that would be detrimental to the operation of most line equipment, and they are therefore removed by means of low-pass filters having a cut-off frequency lower than the lowest ripple frequency. These filters normally consist of one or more sections, each section comprising a choke or inductance in series with the rectifier output, and a condenser in parallel with the output, as shown in Fig. 263.

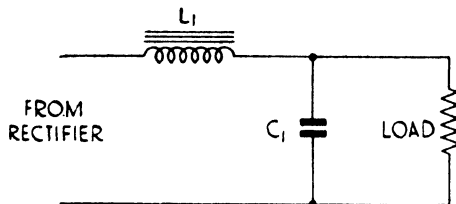


FIG. 263.—Single section choke-input filter.

The theory of filters is dealt with in Chapter 15, but the operation of the smoothing filter now under discussion may be understood by considering the choke and condenser to form a potentiometer across the rectifier output. At zero frequency (*i.e.*, for DC) the inductance offers a low impedance (merely that of its DC resistance), while the condenser offers an infinite impedance; the whole of the DC voltage developed by the rectifier is therefore applied to the load, and this voltage is equal to the mean value of the rectifier output. At the frequencies of the various ripple components, however, the inductance offers a high impedance, and the condenser a low impedance; only a fraction of the ripple voltage thus appears across the condenser, and therefore across the load. If particularly good smoothing is required, two or more such sections in tandem may be employed, as in Fig. 264.

If a "reservoir" condenser is connected in shunt across the rectifier output before the first choke, as C_1 in Figs. 266 and 268, the resulting smoothing network is called a "condenser-input" filter. On no load, a condenser-input filter gives a larger output voltage

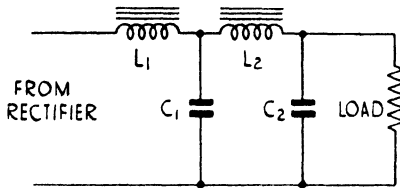


FIG. 264.—Double section choke-input filter.

than a choke-input filter. This is because, on no load, the condenser charges up to the peak (not the mean) voltage of the pulses; and, retaining this voltage from the peak of one pulse to the next, gives a DC output voltage that is equal to the *peak* value of the alternating voltage applied to the rectifier. On load, the condenser partially discharges through the load during the periods between pulses (see Fig. 265), and the mean DC output voltage drops. Thus the condenser-input filter gives a higher output voltage on light loads than the choke-input filter, but the "regulation" is not so good; that is to say, the DC output voltage drops appreciably with increase

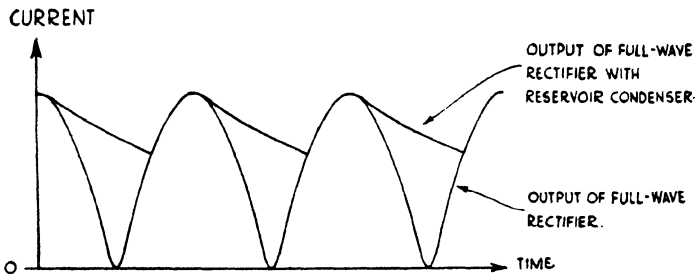


FIG. 265.—Output of full-wave rectifier with reservoir condenser.

in load. The condenser-input filter has the advantage that the reservoir condenser itself assists in the smoothing, and hence a reservoir condenser followed by *one* choke-and-condenser section will give a degree of smoothing comparable with that obtained from *two* choke-input sections.

The values of the components for filters of either the choke-input or the condenser-input type can be calculated by the following empirical methods.

Design of condenser-input filters

(1) For half-wave rectifiers

(a) Knowing V (the RMS voltage across secondary of transformer), and V_0 (the required direct voltage across the

load), calculate $\frac{V_0}{V}$. Let the required direct current through the load be I_0 . Calculate R ($= \frac{V_0}{I_0}$).

(b) Using graph *a* of Fig. 267, read off $\omega C_1 R$ ($\omega = 2\pi \times$ supply frequency), and thus obtain the value of C_1 .

(c) From graph *b* of Fig. 267, read off the percentage ripple $\frac{V_R}{V_0}$ across C_1 . (V_R is the RMS ripple voltage.)

(d) Calculate L_2 and C_2 from the formula:—

$$\frac{\text{Per cent. ripple across } C_2}{\text{Per cent. ripple across } C_1} = \frac{1}{\omega^2 L_2 C_2}$$

the aim being to reduce the percentage ripple across C_2 to a minimum (e.g. 0.2 to 0.3 per cent. if possible).

Units used are ohms, farads, and henries.

(2) For full-wave rectifiers

(a) Knowing V , V_0 , and I_0 , calculate $\frac{V_0}{V}$ and R .

(b) Using graph *a* of Fig. 269, read off $\omega C_1 R$ ($\omega = 2\pi \times$ supply frequency) and thus obtain the value of C_1 .

(c) From graph *b* of Fig. 269, read off the percentage ripple across C_1 .

(d) Calculate L_2 and C_2 from the following formula:—

$$\frac{\text{Per cent. ripple across } C_2}{\text{Per cent. ripple across } C_1} = \frac{1}{4 \omega^2 L_2 C_2}$$

the aim being to reduce the ripple across C_2 to a minimum.

In step (d) for the full-wave rectifier, the “ $4 \omega^2$ ” is introduced because the ripple frequency is now twice that of the supply.

Design of choke-input filters

Consider the single-section filter shown in Fig. 263. Using a full-wave rectifier circuit, the values of L_1 and C_1 can be obtained from the formula:—

$$\text{Percentage ripple at output} \approx \frac{144}{L_1 C_1}$$

This is an approximate formula, but the values obtained will give suitable smoothing for 100 c/s ripple. If the ripple frequency is not 100 c/s, then values obtained for L_1 and C_1 should be multiplied by $\frac{100}{f}$, where f is the actual ripple frequency.

Condenser values so obtained are in microfarads, and inductance values in henries.

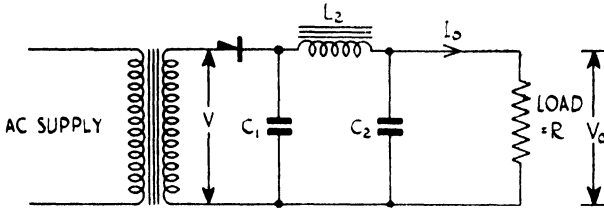


FIG. 266.—Half-wave rectifier with condenser-input filter.

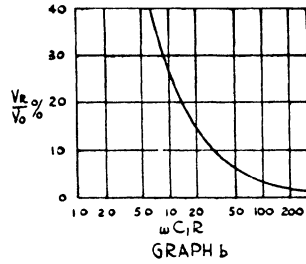
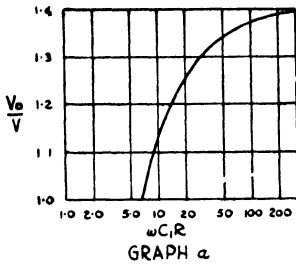


FIG. 267.—Design data for a condenser-input filter for use with a half-wave rectifier.

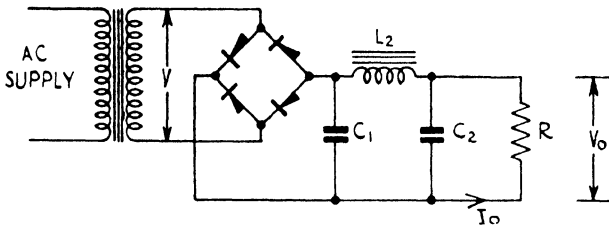


FIG. 268.—Full-wave (bridge) rectifier with condenser-input filter.

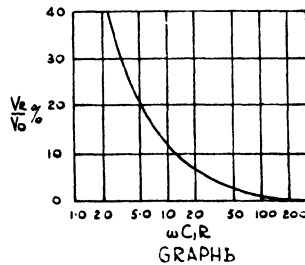
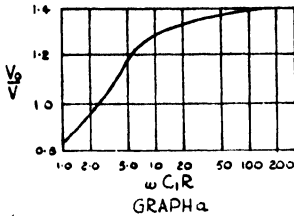


FIG. 269.—Design data for a condenser-input filter for use with a full-wave rectifier, assuming a fundamental ripple frequency of 100 c/s.

The distribution of inductance and capacity (only the product L_1C_1 has been obtained) depends on the size of choke to be fitted. There is a critical value to L_1 , however, and a choke of lower value will lack the good voltage regulation which is the advantage of filters of this type.

$$L \quad (\text{in henries}) \simeq \frac{\text{load resistance (in ohms)}}{1000}$$

To obtain a small percentage ripple it is better to use a double section filter, as component sizes would be more economical.

The values of L_1 , L_2 , C_1 and C_2 can be obtained from the formula :

$$\text{Percentage ripple in output} \simeq \frac{1350}{L_1L_2(C_1 + C_2)^2}$$

This again gives merely a guiding relationship between the various components, and actual values will be chosen to prevent too great a voltage drop and to give suitable and economical components. The units are capacity in microfarads and inductance in henries.

Resonance.—If series resonance occurs in L_1 and C_1 of the filter, large alternating voltages will build up and the reverse of smoothing will result. To avoid this, the product of the inductance in henries times the capacity in microfarads should not be lower than 5 in the case of a 50 c/s supply. For this supply frequency, resonance occurs when $L_1C_1 = 2.53$, but a large safety margin is essential.

POWER SUPPLIES WORKING FROM DC

The preceding paragraphs have shown how a power supply can be made to operate from AC mains. If, however, the source of power is a low-voltage DC battery, some means must be found of stepping this up to the required HT voltage. The two most common ways of doing this are by using either a vibrator or a rotary transformer.

Vibrators

A vibrator is used to change the DC to a low-voltage AC supply, which can be stepped up by a transformer and dealt with as before. The way in which a vibrator does this is described below.

The shunt-drive type vibrator

Fig. 270a shows the simplified circuit of a shunt-drive type vibrator. In the "idle" position, the armature does not make with either contact; but when the DC supply is connected, magnetising current flows through the coil attracting the armature to the top contact. This results in DC flowing through the top half of the transformer primary winding. At the same time this contact shorts out the operating coil, and after the magnetic flux has decayed the armature is released; the momentum of the latter carries it past its central position and on to the bottom contact. DC now passes through the lower half of the transformer in the

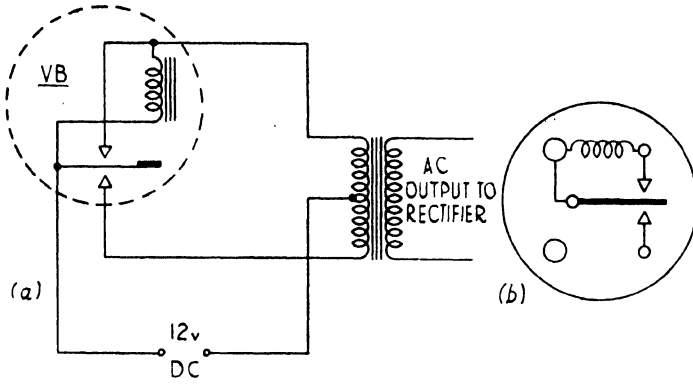


FIG. 270.—Shunt-drive type vibrator.

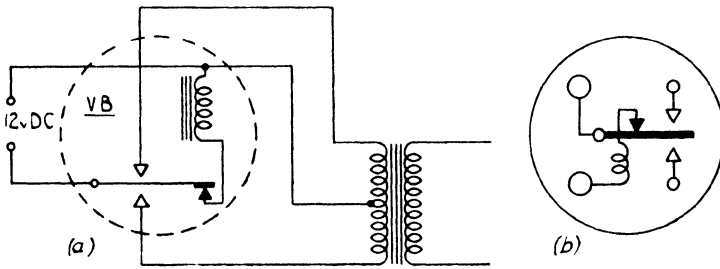


FIG. 271.—Series drive type vibrator.

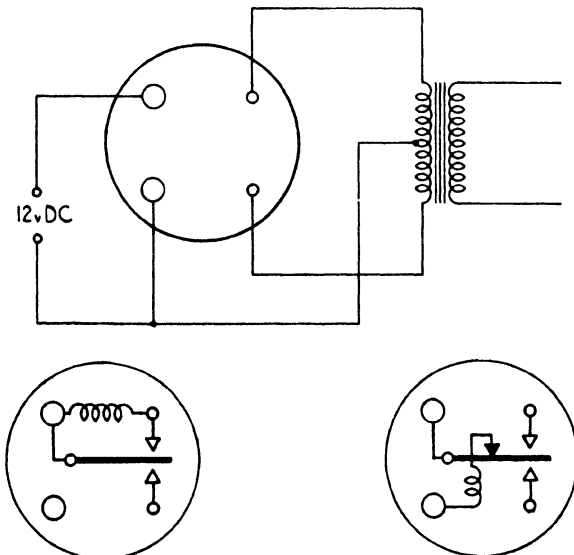


FIG. 272.—Circuit for shunt or series drive vibrator.

reverse direction to the previous pulse. Thus, there occurs, in the transformer, a reversal comparable with the two halves of a cycle of AC. Meanwhile the coil is again magnetised, and the armature keeps vibrating between the contacts until the DC supply is disconnected. The constant reversals in the primary induce an alternating EMF into the secondary; if a suitable turns ratio be chosen, the required HT voltage is obtained, and can be rectified as described in previous sections. Fig. 270*b* shows the diagrammatic representation of the shunt-drive type vibrator.

The series-drive type vibrator

In this later type of vibrator, the coil is in series with a third contact that is making with the armature in the rest position (*see* Fig. 271*a*). When the supply is connected, current flows through the coil and causes attraction of the armature. The armature then makes contact with the upper contact and DC flows through the top half of the transformer primary. This movement also breaks the circuit of the coil, so that the armature is released; and it therefore travels back through its rest position and, owing to its momentum, continues on to the lower contact. The armature is now in contact with both the lower interrupter contact and the coil contact. Thus a DC pulse passes through the lower half of the transformer and the coil is energised once more. The armature returns to the top contact and the cycle begins again.

The current in the primary thus consists of reversals of DC which, as before, have the same effect as ordinary AC and produce the required high alternating voltage across the secondary.

Fig 271*b* shows the diagrammatic representation of the series-drive type vibrator.

Vibrator circuit arrangements

In the case of the shunt-drive type of vibrator, although four pins are fitted on the base, only three are used, whereas in the series-drive type all four pins are employed; circuits may, however, be so arranged that either type may be inserted (*see* Fig. 272).

When the vibrator contacts make and break the DC circuit, heavy induced voltages are set up which may cause sparking at and damage to these contacts. To remove this possibility spark quench condensers are fitted between the armature and the two contacts, as shown in Fig. 273*a*. A typical value for these condensers is 0.01 μ F. Sometimes a "buffer" condenser is fitted across the secondary of the transformer, as shown in Fig. 273*b*. The action of this buffer condenser is principally to improve the commutation, thereby increasing the efficiency and prolonging the contact life, but it also performs the function of the spark quench condensers, as it offers an easy path for the heavy surges.

Synchronous vibrators

The synchronous, or self-rectifying, vibrator circuit is arranged to reverse the polarity of the secondary at the same instants as

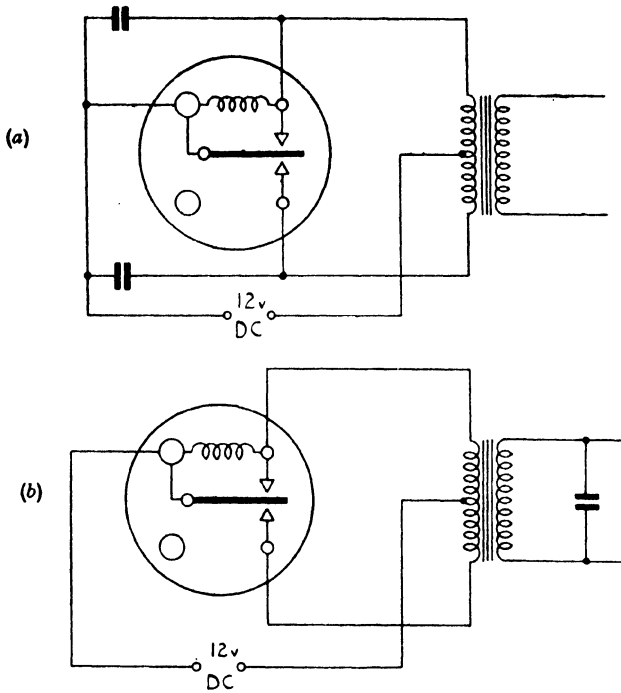


FIG. 273.—Vibrator circuit showing :—(a) spark quench condensers. (b) buffer condenser.

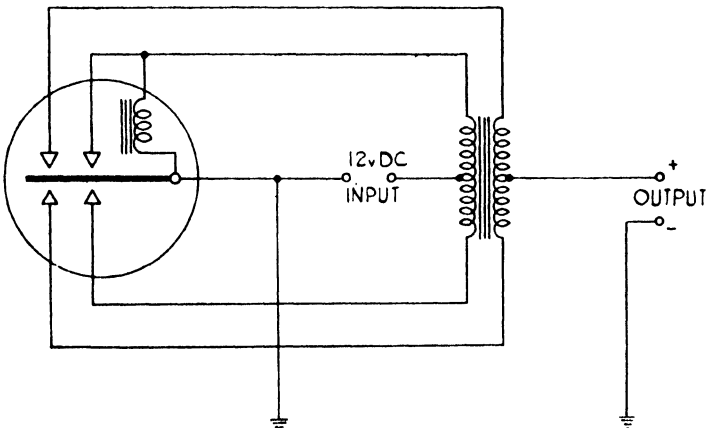


FIG. 274.—Synchronous vibrator.

the reversals occur in the vibrator. The output is therefore rectified and consists of pulsating DC which can be smoothed by the circuits already covered.

The main difference from the non-rectifying vibrator circuit is the provision on the vibrator of additional contacts, which are connected to the terminals of the secondary coils (*see* Fig. 274). When the armature makes with the lower contacts DC builds up through the lower half of transformer primary, inducing an EMF in the lower half of the secondary. By controlling the polarity of the LT supply, it can be arranged that the centre tap of the secondary assumes a positive potential with respect to the lower terminal which is now earthed through the vibrator. The next induced EMF, due to the break of this DC and the make of the DC in the other half of primary, will be reversed; but, owing to the change-over of the secondary contacts, it will be taken from the top half of the secondary, so that the centre tap remains of positive polarity.

Thus by synchronising the change-over contacts, pulsating DC is obtained in the output, the centre tap of the secondary winding being the positive terminal. This type of vibrator assembly, by avoiding the need for rectifiers, is economical, eliminates the loss of energy in the rectifiers, and eliminates the rectifiers as a source of faults. This last advantage is, however, off-set by the fact that synchronous vibrators are more liable to faults than non-synchronous, and the overall fault-liability of both systems is about equal.

The contacts of the synchronous vibrator are slightly staggered so that the secondary contacts break a little before the primary and make a little after. This removes the danger of the secondary surge, due to the primary break, being passed to the output with the wrong polarity.

Radio interference suppression

The transient voltage surges in vibrator circuits contain radio frequency noise components, which cause interference in any near-by radio equipment. This noise cannot be controlled by the spark quench or buffer condensers, and other means of avoiding it must therefore be incorporated. The methods of suppression used in the past have not been standardised, and the circuits used are those which were found most suitable in the particular cases. The methods adopted incorporate:—

- (1) Shielding—both magnetic and electrostatic;
- (2) Good earthing;
- (3) RF filtering in the leads to and from the vibrators.

All these combined give fair, but not full, suppression of the interference.

Fig. 275 shows an example of such a unit, typical values being:—

C_1	..	0.1 μ F		C_2	..	0.25 μ F
L_1	..	75.0 mH		L_2	..	32 μ H

Radio frequencies set up at the contact of the vibrator driving

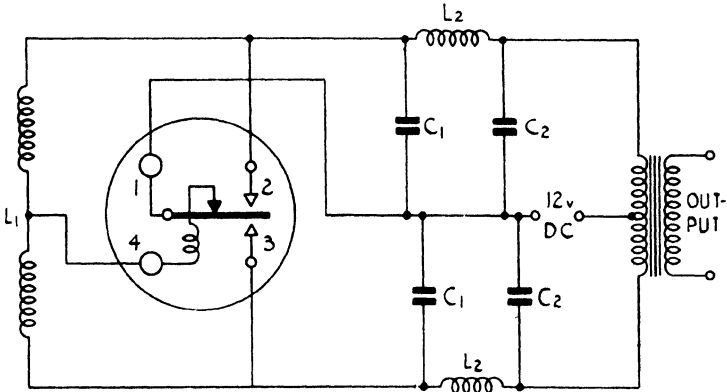


FIG. 275.—Radio interference suppression.

coil are suppressed by L_1 , while those from the main contacts are suppressed by the low-pass filter formed by L_2 , C_1 , and C_2 , which has a cut-off frequency well below 1 Mc/s.

Equally as important as the filter is the thorough shielding of the power supply and its connecting leads, since even a small piece of wire or metal will radiate sufficiently to cause interference in a sensitive receiver.

Mechanical construction of vibrators

The metal can of the vibrator supplies the requisite screening, while in the later models it also provides hermetic sealing. Without

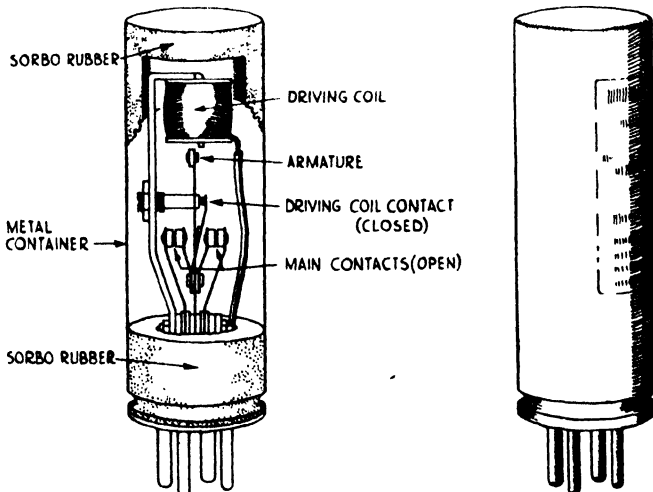


FIG. 276.—Construction of series-drive type vibrator

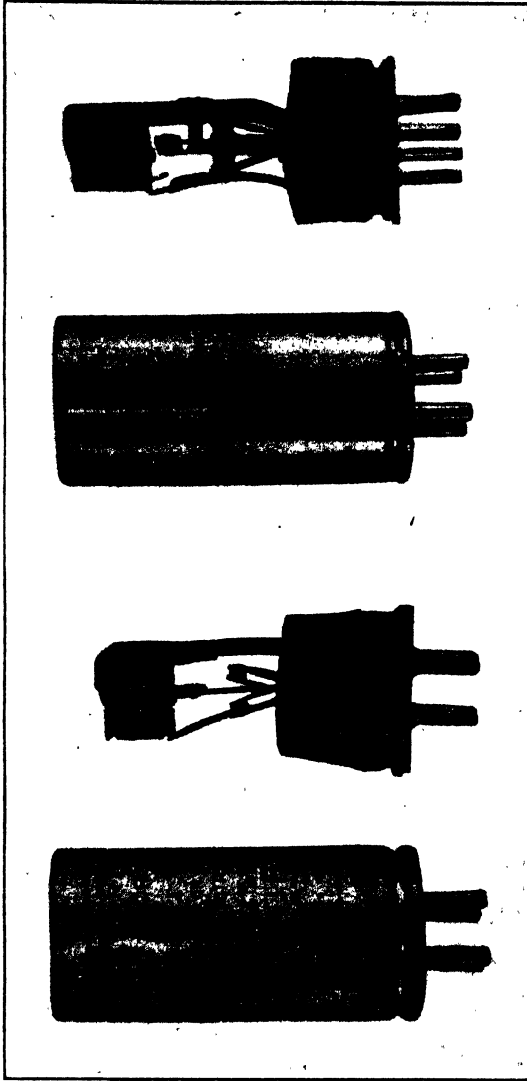


PLATE 15.—Vibrators.

this latter the vibrator may easily stop in a humid or rarefied atmosphere. In the tropics, damp entering the can forms a film on the contacts which prevents metallic contact ; thus no current can flow and the vibrator stops. In rarefied atmosphere the vibrator contacts start sparking at low voltages, so that the contacts deteriorate. Both of these difficulties are removed by hermetic sealing. When stoppages occur due to humidity a cure, though drastic, can be effected by force-driving the vibrator off 230 volts AC mains in series with a 30 watt lamp. This voltage breaks down the film, and the contacts are cleared for normal operation.

The frequency of the vibrator reed is not standardised, but, in the types used by the army, is of the order of 100 c/s. It is governed principally by the mechanical inertia of the reed and the electrical characteristics of the coil ; and thus, in the miniature vibrators now being developed, a higher frequency is used.

Rotary transformers

Rotary transformers consist in effect of a DC motor and generator, with their armatures coupled mechanically. The motor works from a low-voltage supply, usually 12 volts or 24 volts, and the generator is designed to produce the required HT voltage.

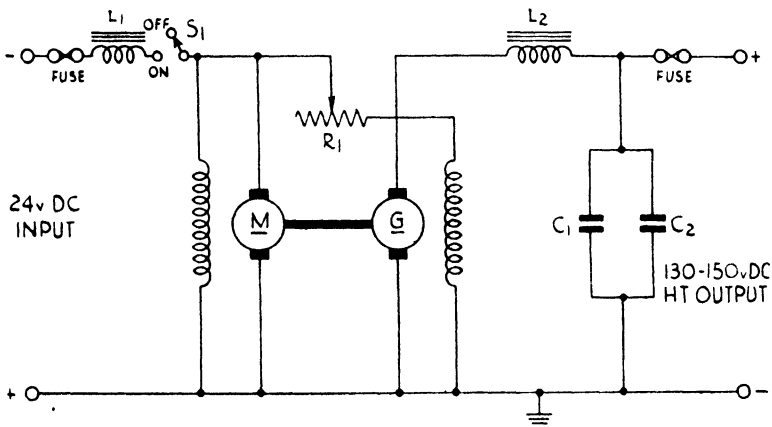


FIG. 277.—Circuit of rotary transformer.

In some cases, the two armatures are wound together and work in the same field. In other cases, the two fields are quite separate ; an example of this type will now be considered.

The output of the supply is :—

HT 130–150 volts, maximum drain 285 milliamps.

It is designed to operate from 24 volts DC.

Fig. 277 shows the circuit of the rotary transformer. L_1 is a choke fitted to prevent AC caused by commutator ripple from

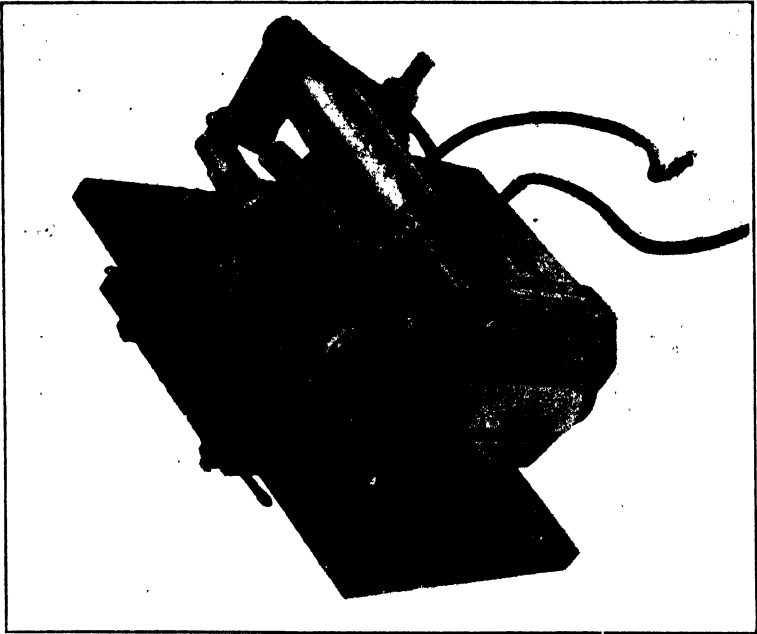


PLATE 16.—Carbon pile regulator.

feeding back to the supply and thus rendering it noisy. L_2 , C_1 , and C_2 form the smoothing circuit. The output voltage is controlled by R_1 , which varies the current in the field coil of the generator.

If required, a carbon pile regulator may be fitted to ensure a constant HT voltage output for all loads up to the maximum.

Fig. 278 shows the circuit of such a regulator, and Fig. 279 a diagrammatic arrangement of its mechanical construction.

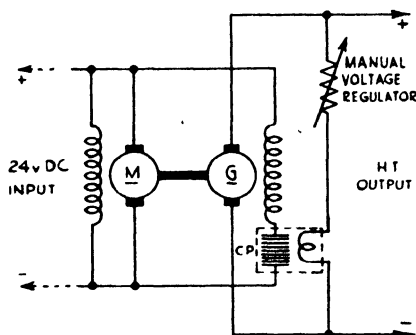


FIG. 278.—Regulation by use of carbon pile.

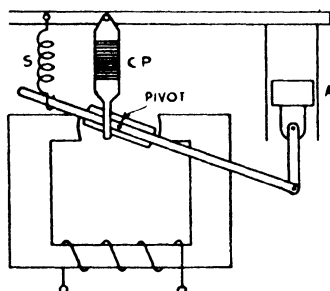


FIG. 279.—Carbon pile regulator.

The carbon pile consists of a stack of carbon plates, the resistance of which is varied by the pressure exerted on it. Normally it is held under pressure by the spring S ; but when HT is being supplied, current flows through the coil of the electro-magnet, and the field between the pole-pieces tends to rotate the soft iron armature against the tension of the spring, and increases the resistance of the carbon pile.

In operation a state of stability is reached, and the carbon pile will be under a certain pressure due to the normal value of output voltage. When the load current increases, the HT voltage tends to fall, due to the increased armature voltage drop. This drop in voltage output causes less current through the electro-magnet of the carbon pile regulator and therefore decreased resistance. The resultant increase in generator field current produces the required increase in generator EMF.

POWER SUPPLY UNITS

The main parts of any power supply have now been considered; to illustrate their use, several complete power supply units will be discussed.

Example 1

A power supply unit providing $80 + 80$ volts and 12 volts DC, from either 12-volt DC or AC mains.

The design (Fig. 280) is conventional; the AC is rectified by a voltage doubler circuit, and the output smoothed by reservoir condensers. The LT supply is rectified by a full-wave bridge, and again smoothed by a reservoir condenser. A high degree of smoothing is not required for either supply.

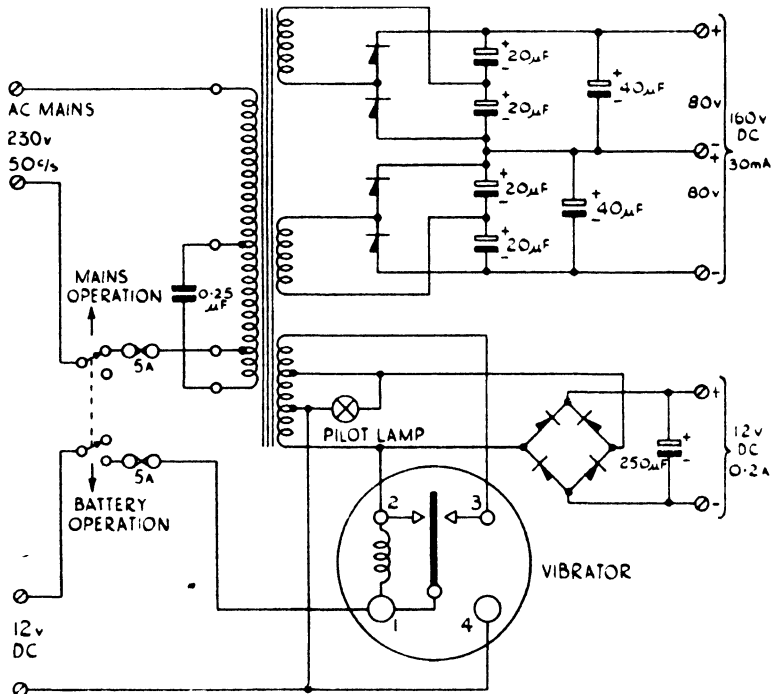


Fig. 280.—Power supply circuit providing 80 + 80 V, and 12 V DC from AC mains or from 12 V DC.

When working off a 12-volt battery, the LT terminals will not be used, since 12-volt DC may be obtained directly from the battery. The 0.25 μF condenser forms a buffer condenser for the vibrator.

Example 2

A power supply unit providing 130 volts HT and 24 volts LT from AC mains, with arrangements for a standby supply.

This unit (see Fig. 281) is designed to work off various supply voltages, the mains being connected to the appropriate terminals on the terminal strip shown on the left of the diagram. The neon lamp lights when the mains supply is in use. The remainder of the circuit is standard, apart from the relay *A* and the AC contactor switch *CS*. These cause automatic change-over to the standby supply, should the mains supply fail.

Relay *A* is across the HT supply and is normally operated. This causes operation of *CS*, placed across the LT supply, and this contactor completes the circuit for normal working. Should the LT fail, *CS* releases; should the HT fail, *A* releases, again causing *CS*

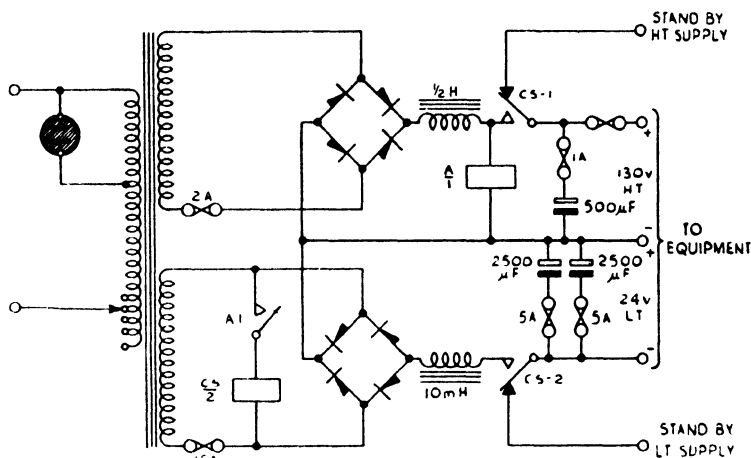


Fig. 281.—Power supply unit providing 130V HT and 24V LT from AC mains, with provision for standby supply.

to release. Thus, if either supply fails, the contacts of *CS* will release, thereby connecting the standby supply to the output terminals.

The outputs of this supply unit are :—

LT : 24 volts, 3 to 11 amps.

HT : 130 volts, 150–600 milliamps.

Example 3

A power supply unit providing 12 + 12 volts DC, at 6 amps, from AC mains.

This unit (*see* Fig. 282) is designed for use off 50 c/s AC mains, the necessary stepping up from the lower voltage supplies being achieved by an auto-transformer. The two subsequent pairs of transformers each change the single-phase input to a three-phase output which is designed to give a steadier rectified voltage than that possible with rectified single-phase voltages. The output is then fed to two sets of terminals; the first through a smoothing circuit to give an output suitable for telegraph supply, and the second without any smoothing giving a supply suitable for driving a motor. This double source prevents interference from the motor feeding back to the telegraph circuit. The output voltage in each case is 12 + 12.

POWER SUPPLY UNITS

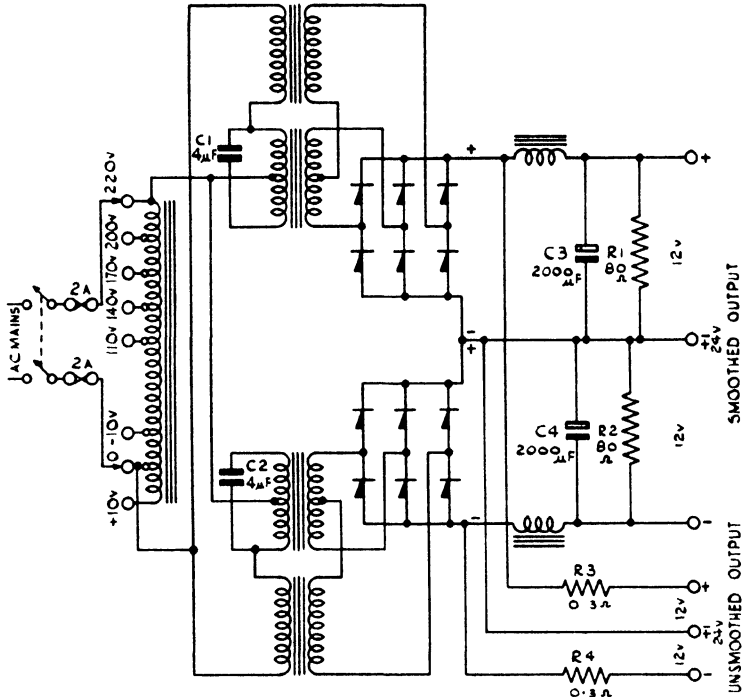


FIG. 282.—Power supply unit providing 12 V + 12 V DC at 6 amps, from AC mains.

To understand the conversion to three-phase, consider the circuit of Fig. 283. The transformer T_1 has an inductive primary impedance that is largely resistive on full load. On no-load, its impedance is largely inductive, so that I will lag behind V_1 by

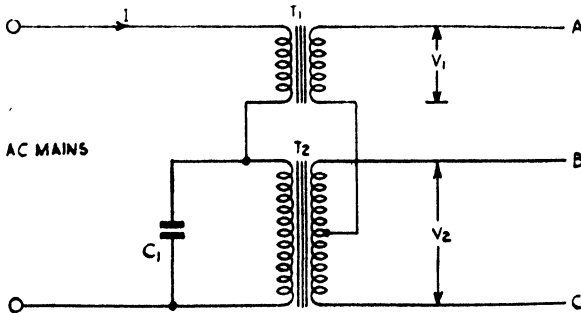


FIG. 283.—Method of obtaining three-phase supply.

almost 90° . Taking the supply current as reference vector, Fig. 284 shows the voltage across T_1 on full load; the arrow shows how the voltage vector rotates as the load is reduced.

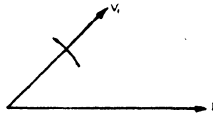


FIG. 284.—Vector diagram for voltage across primary of T_1 on full load.

Consider now the lower transformer; if C_1 is sufficiently large, the parallel combination of T_2 and C_1 will have a capacitive impedance, so that V_2 will lag behind the mains current I , as shown in Fig. 285. By a suitable adjustment of C_1 , V_2 can be made to lag behind V_1 by exactly 90° on full load.

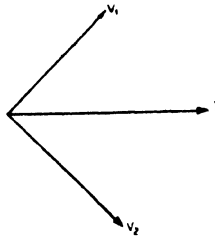


FIG. 285.—Vector diagram for voltage across primary of T_2 on full load.

Consider now the voltages of the three terminals A , B , and C relative to the mid-point O of the transformer T_2 . The voltages V_1 and V_2 are redrawn in Fig. 286, with V_1 as reference vector, and this is the voltage of A (relative to O). The voltage of B is in phase with

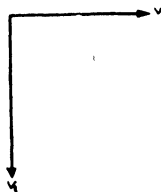


FIG. 286.—Vector relationship between voltages across the two transformer primaries on full load.

V_2 , but equal in magnitude to $\frac{1}{2}V_2$; and the voltage of C is 180° out of phase with V_2 and equal in magnitude to $\frac{1}{2}V_2$ (see Fig. 287a). The voltages between the three terminals A , B , and C (which are shown in their cyclic order in Fig. 287b), are therefore given by:—

$$V_{AB} = V_{AO} + V_{OB} = -V_{OA} + V_{OB} = -V_1 + \frac{1}{2}V_2$$

$$V_{BO} = V_{BO} + V_{OC} = -V_{OB} + V_{OC} = -\frac{1}{2}V_2 - \frac{1}{2}V_2 = -V_2$$

$$V_{CA} = V_{CO} + V_{OA} = -V_{OC} + V_{OA} = +\frac{1}{2}V_2 + V_1 = V_1 + \frac{1}{2}V_2$$

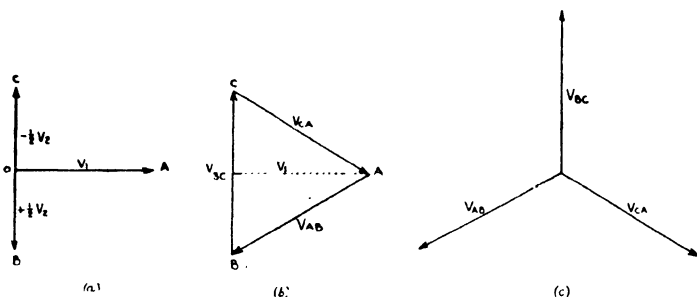


FIG. 287.—Complete voltage vector diagram for three-phase conversion.

It can be seen that if $\frac{1}{2}V_2 = \frac{1}{\sqrt{3}}V_1$, i.e. if $V_1 = \frac{\sqrt{3}}{2}V_2$, then the triangle will be equilateral; this relationship can be satisfied by suitable choice of transformer turns ratios. The three points A , B and C then form a three-phase supply, the vector voltages between AB , BC , and CA being equal in magnitude. If the vectors representing these voltages are drawn in "star" form, as in Fig. 287c, it can be more clearly seen that they are separated by angles of 120° .

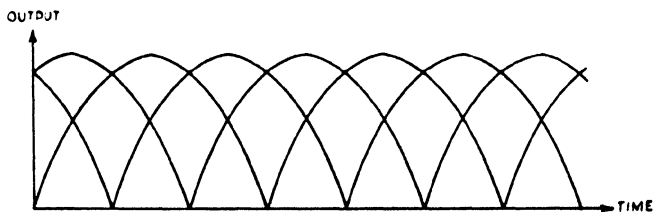


FIG. 288.—Output from three-phase full-wave rectifier.

This three-phase supply is applied to a full-wave bridge rectifier, the output voltage of which is equivalent to the combined effect of three single-phase rectified outputs differing by 120° . This gives a wave-form as shown in Fig. 288.

It can be seen that the lowest frequency present is six times the supply frequency, and hence smoothing is a simpler problem than with a single-phase supply.

This, however, is not the most important advantage of this system; it has also a constant output voltage at all loads. In a normal rectified power supply, the output voltage drops as the load is increased, due to resistance losses in transformers and smoothing circuits, and increased drops in the rectifier. In this case, however, the circuit is designed to give efficient conversion to three-phase at full load. As the load drops, the voltages V_1 and V_2 vary in magnitude and phase, which causes the rectified voltage to drop. If this drop as the load is reduced is made to balance the decreased resistive drop, a constant output voltage can be obtained for wide variations of load. This does not apply at zero load, so to prevent any trouble arising from this, a constant initial load is provided by the two 80-ohm resistances across the output. The net result is a constant output voltage for all loads up to 6 amps.

CURRENT AND VOLTAGE STABILISERS

In many circuits, it is necessary that the voltages and currents applied to the equipment be kept within close limits, while the supply may fluctuate over a wide range. For this reason, many stabilising devices have been developed.

Current stabilisers—the barretter

Current stabilisers are designed so that an increase in the current through them causes an increase of their resistance. If therefore they are placed in series with the load, their effect will be to stabilise the value of the current.

The most common form is the barretter, which is a lamp with a special filament—usually pure iron drawn to a fine wire—in a bulb

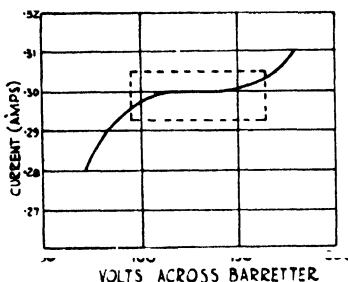


FIG. 289.—Typical voltage-current characteristic of barretter.

filled with hydrogen. The reasons for gas filling are to prevent oxidation of the filaments and to permit rapid removal of heat and therefore speedy stabilisation.

Fig. 289 shows the voltage-current characteristic of a typical

barretter working at 0·3 amps over a voltage range of 95 to 165 volts. This voltage range is called the working or "barretting" range of the barretter, and varies with the different designs. The working current level can be altered by design between limits of 0·2 amp and several amps. The former limit is governed by the possible fineness of the wire filament, while the latter is governed by the physical size of the lamp, a large size being necessary to dissipate the heat produced. This heat will be wastage of power and, as this is never desirable, the use of a barretter should always be carefully considered before adoption.

In operation, the barretter should be allowed ample air-circulation, as the ambient temperature naturally affects its working. It should also be removed or shielded from any strong magnetic field, as this would induce noise into the circuit.

Voltage stabilisers

In contrast to the current stabiliser, whose impedance increases with current, voltage stabilisers have an impedance which decreases with increase of voltage. For this reason they are used in parallel with the load. When the supply voltage increases, the impedance of the stabiliser will drop owing to the increased voltage across it.


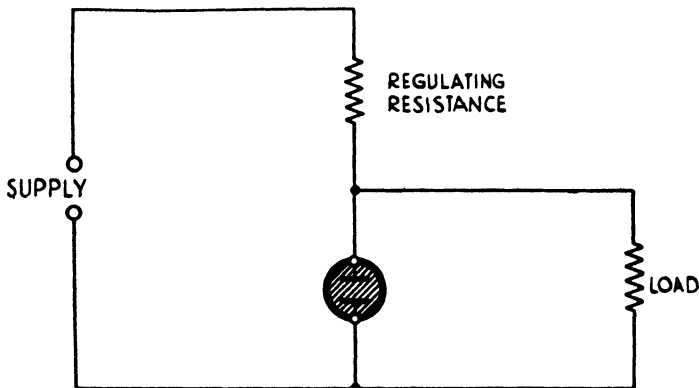


FIG. 290.—Voltage stabiliser circuit.

This causes a greater proportion of the current to flow through the stabiliser and less through the load. A circle of changes will therefore be set up which will tend to keep a constant voltage across the load, and therefore a constant current through it.

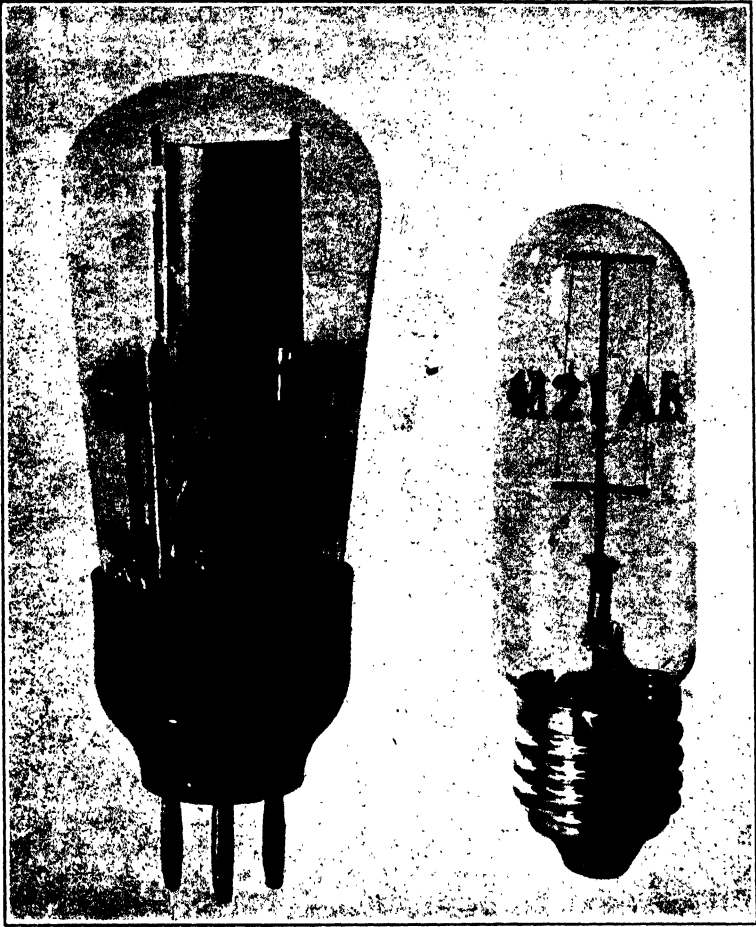A common type of voltage stabiliser is the cold-cathode neon tube. The epithet "cold-cathode" is given because the cathode requires no heater current. The voltage builds up across the electrodes until it is high enough to cause the tube to "strike". This striking voltage may be anything from 80 to 180 volts, and is usually about 100 volts in the case of the tubes used in line equipment.



(a) PLATE 17.—(a) Neon stabiliser.
(b) Barretter.

Once the tube has "struck", its resistance falls abruptly from infinity to a very low value, so that the direct application of the striking voltage would cause a very large discharge current—large enough, in fact, to cause destruction of the tube. To avoid this, a resistance is connected in series with the tube as in Fig. 290, thus limiting the current.

Increase of voltage above the striking point causes a further decrease in the impedance of the neon tube. Therefore more of the supply voltage will appear across the regulating resistance, while that across the neon tube and the load will tend to be unchanged

CHAPTER 7

THERMIONIC VALVES

THERMIONIC EMISSION

The phenomenon of current flow in an electrical conductor has been explained by the hypothesis that in a conductor, certain electrons in the outer orbits of the component atoms are comparatively loosely held to their parent nuclei, and that when an electrostatic field is superimposed on the conductor, a drift of the so-called "conductor electrons" results. This drift of electrons will be from the low potential to the high potential part of the electrostatic field, and will correspond to an electric current in the reverse direction.

When a metal is heated, the normal random motion of the conductor electrons is intensified, and at very high temperatures electrons will tend to leave the surface of the conductor altogether. This phenomenon is called "thermionic emission"—the name meaning simply the emission of electrons due to the application of heat—and on this phenomenon depends the operation of thermionic valves. A valve consists of a suitably heated "cathode", or emitter of electrons, together with one or more electrodes for collecting the electrons emitted, and for controlling and utilising the resulting flow of electrons.

In order to use a heated metal as a source of electrons, the cathode must be enclosed in an evacuated envelope. This is necessary for two reasons: firstly, most metals oxidise rapidly when heated to a high temperature in air; and secondly, if air (or any other gas) were present in the envelope, the emitted electrons, having attained sufficient velocity to leave the cathode, would collide with the molecules of the gas, causing ionisation of the gas and producing undesired results.

The cathode

The cathode may either be "directly heated", by constructing it in the form of a wire and passing an electric current through it, in which case it is called a "filament"; or it may be "indirectly heated", by making it in the form of a cylinder round a "heater wire" through which the heating current is passed. The heater of an indirectly heated valve is electrically insulated from the cathode, but is so attached to it mechanically that almost all the heat generated by the heater passes to the cathode. To permit this

passage of heat, the insulation between heater and cathode must be chosen and designed with its thermal behaviour as the primary consideration, and it is usually weak electrically. For this reason, care must be taken not to allow too high a potential difference to be developed between heater and cathode, or the insulation will break down. The maximum permissible heater-cathode voltage for most small valves is usually of the order of 100 volts.

Indirectly heated valves have three main advantages over the directly heated type. Firstly, there is a thermal reservoir effect between heater and cathode, due to the high thermal capacity of the insulation, so that the cathode remains at a constant temperature even when AC is used for the heater, whereas the temperature of the filament of a directly heated valve heated by AC varies between wide limits at twice the AC supply frequency. Owing to its thermal capacity, the cathode may take several minutes to reach its final working temperature, though it usually approaches this temperature after about 30 seconds. Secondly, since the cathode is electrically isolated from the heater, greater flexibility in circuit design is possible; in particular, several valves can be operated from the same heater supply, and yet have their cathodes connected to any desired points in their respective circuits without mutual interaction. Thirdly, since no heating current is passed through the cathode itself, the whole of the latter is at the same potential.

Cathode construction

The metal originally used for directly heated cathodes was tungsten, either pure or containing about one per cent. of thorium oxide, but the temperatures required were high, so also was the heating current. Most cathodes in use to-day (except in high-power radio transmitting valves) are of the oxide coated type; these give emission of electrons at dull red heat, and are economical in supply power. Directly heated filaments of this type consist simply of a wire of nickel, tungsten or nickel alloy coated with a preparation of barium, strontium or calcium oxides. The indirectly heated cathodes consist of a nickel tube coated with oxide forming the cathode, and inside this tube, and insulated from it, is a stout tungsten wire that forms the heater.

THE DIODE

The subsequent motion of the free electrons that surround the cathode as the result of thermionic emission may be influenced by electrostatic fields applied by means of further "electrodes". Thermionic valves are classified according to the number of electrodes they possess, the simplest being the two-electrode valve or "diode".

The diode consists of a cathode (either directly or indirectly heated) surrounded by a second electrode, the anode (or plate). Fig. 291 shows the assembly of the two types of diode, and the conventional symbol associated with each. Fig. 291*a* shows a

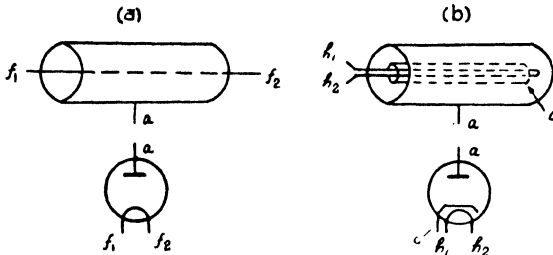


FIG. 291.—Arrangement of electrodes in a diode :
 (a) directly heated ; (b) indirectly heated.

directly heated valve with a filament f_1f_2 and an anode a , whilst Fig. 291*b* shows an indirectly heated valve having a heater h_1h_2 , a cathode c , and an anode a .

Space-charge

The rate of emission of electrons into the free space surrounding the cathode may be considered to be constant since it depends principally on the temperature of the cathode. What happens to these electrons afterwards depends on the electrostatic potential of the anode relative to the cathode. If the anode is made negative with respect to the cathode, the emitted electrons will be repelled

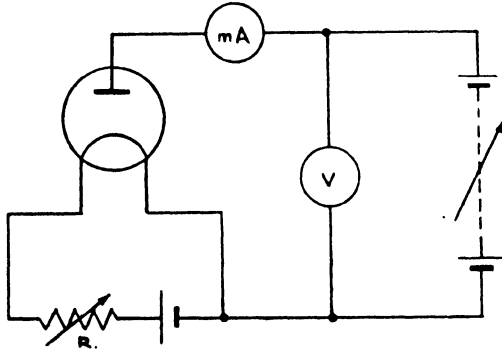


FIG. 292.—Circuit for plotting characteristic curves of a diode.

back into the cathode, and no current will flow between anode and cathode. If the anode is maintained at a positive potential relative to the cathode (Fig. 292), emitted electrons will be attracted towards the anode. The rate of arrival of electrons at the anode, that is, the anode or plate current, is, however, limited by the negative "space-charge" produced by the electrons in transit between cathode and anode. The number of electrons in transit at any instant is just sufficient to produce a negative space-charge which neutralises the attraction of the anode on the electrons just about to leave the cathode. All electrons emitted in excess of this number are at once repelled back into the cathode. Where the anode

current is limited by space-charge, it will be dependent on anode potential, and is substantially independent of the rate of emission of electrons by the cathode. Fig. 293 shows graphically the relationship between anode potential and anode current for a diode, and Fig. 294 shows the effect of the space-charge on the potential gradient in the valve.

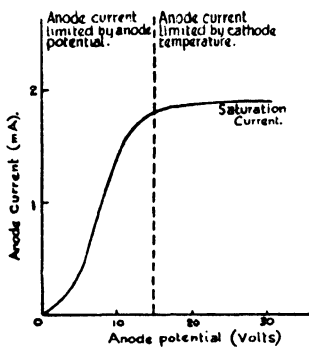


FIG. 293.—Relationship between anode potential and anode current for a diode.

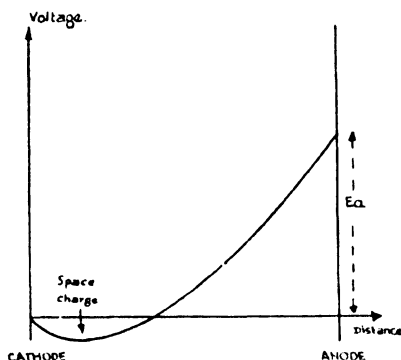


FIG. 294.—Potential gradient in a diode, showing effect of space-charge.

The lower part of the curve in Fig. 293, corresponding to space-charge limitation of the anode current, can be represented by a three-halves power law, *i.e.* by:—

$$I_a = k \cdot E_a^{\frac{3}{2}} \quad (1)$$

where k is a constant depending on the construction of the valve.

As the anode potential is raised, a point is eventually reached where the space-charge effect produced by all the electrons emitted is not sufficient to balance the attraction due to the anode, and the anode current will be largely independent of the anode voltage, but will be determined by the rate of emission of electrons from the cathode and therefore by the temperature of the cathode.

The upper portion of the curve of Fig. 293 shows this condition.

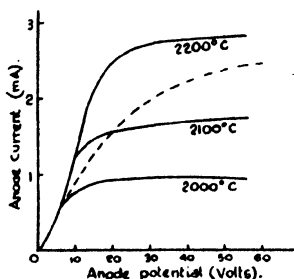


FIG. 295.—Effect of cathode temperature on characteristic curves of a diode.

The limiting value of the anode current (that is, the value above which it is impossible to increase the anode current by increasing the anode voltage) is called the "saturation current", and the valve, in this condition, is said to be "saturated".

Fig. 295 shows how the saturation current is increased by raising the temperature of the cathode (by increasing the heater current). The curve of Fig. 293 and the solid curves of Fig. 295 are plotted for a tungsten emitter; thoriated tungsten gives curves of the same general shape, but in the case of oxide coated cathodes, saturation takes place much more gradually, as shown by the dotted curve of Fig. 295.

It has been stated that the electrons emitted from a heated

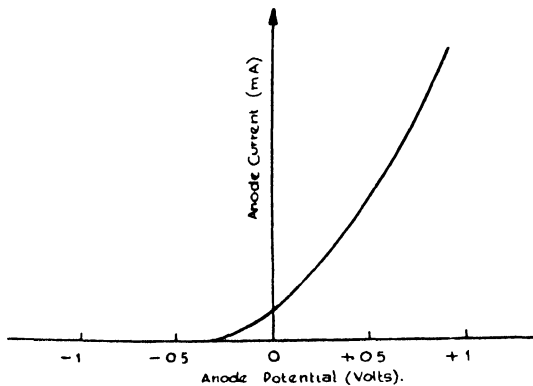


FIG. 296.—Characteristic of a diode for very small anode potentials.

cathode form a space-charge around it, and are attracted to the anode only when a positive anode voltage is applied. This is not strictly accurate, for some of the emitted electrons may have a sufficiently high initial velocity to enable them to reach the anode. This causes a small anode current to flow when the anode voltage is zero, or even slightly negative, as illustrated in Fig. 296. This current ceases to flow when the anode potential is made slightly more negative—the negative voltage on the anode necessary to reduce the current to zero being normally less than 1 volt.

Rectification using a diode

Fig. 297 shows the characteristic curve of a diode plotted for negative as well as positive anode potentials. It will be seen from this curve that the diode is a non-linear impedance of the same type as the metal rectifiers discussed in Chapter 6, except that the diode current falls to zero and does not increase in the reverse direction when a reverse voltage is applied.

Fig. 298 shows a diode used in a half-wave rectifier circuit. The operation of this circuit should be perfectly clear if it is

remembered that the diode will pass current from anode to cathode, but not from cathode to anode. It will be noted that in this circuit, an AC supply is used for a directly heated cathode; this is quite usual in diodes used for power supplies, but is not often employed

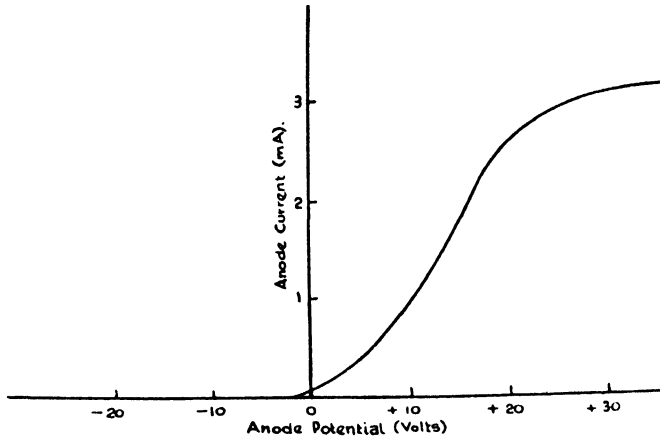


FIG. 297.—Characteristic of a diode for negative and positive anode potentials.

in the case of directly heated valves used for other purposes because it tends to give rise to excessive mains hum.

Fig. 299 shows a double-diode used in a full-wave rectifier circuit. A double-diode is a pair of diodes contained in the same envelope. In this example, the two diodes are sharing a common cathode, which is directly heated.

Fig. 300 shows a pair of diodes used in a full-wave rectifying and voltage-doubling circuit. The diodes shown here are indirectly heated, and it is easily seen that the two cathodes are at different potentials. If, therefore, the two valves are combined into a double-diode, separate cathodes will be necessary. If directly heated diodes are used for this circuit, a separate filament supply must, for the same reason, be used for each one.

THE TRIODE

The diode, which is the simplest form of thermionic valve, is limited to a single function, namely rectification. In the "triode", the flow of electrons from cathode to anode is controlled by means of an additional electrode interposed between the cathode and the anode (see Fig. 301). This electrode, which is called the "grid" on account of the form taken in early examples of such valves, is in the form of an open mesh. The grid is normally operated at a negative potential relative to the cathode, and so it attracts no electrons to itself, so that no grid current flows; but it tends to repel those electrons which are being attracted to the anode.

The number of electrons reaching the anode is determined mainly by the electrostatic field near the cathode, and hardly

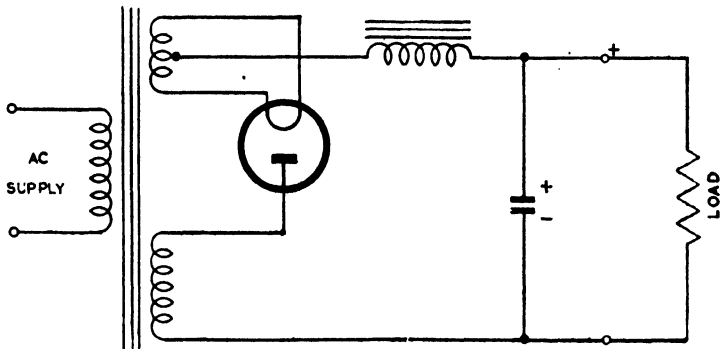


FIG. 298.—Half-wave rectification using a diode.

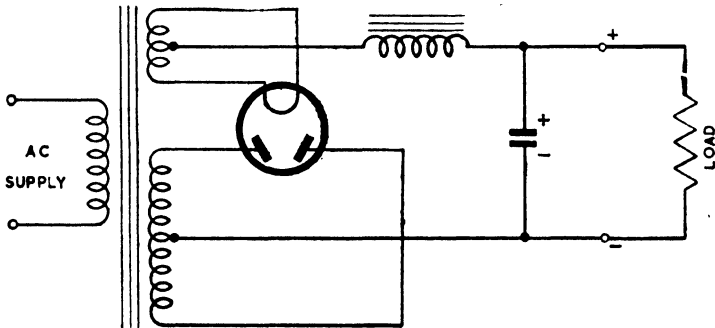


FIG. 299.—Full-wave rectification using a double-diode.

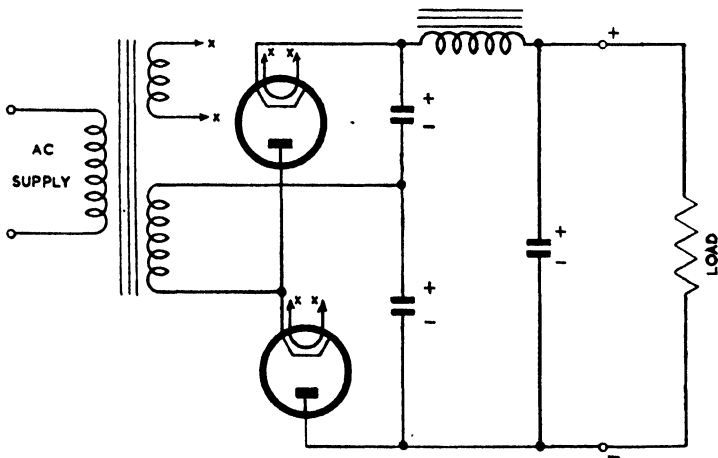


FIG. 300.—Full-wave rectification with voltage doubling using two diodes.

at all by the field in the rest of the space between the cathode and anode; for, near the cathode, the electrons are travelling slowly compared with those which have already moved some distance towards the anode, and the electron density in the inter-electrode space will be high near the cathode, decreasing

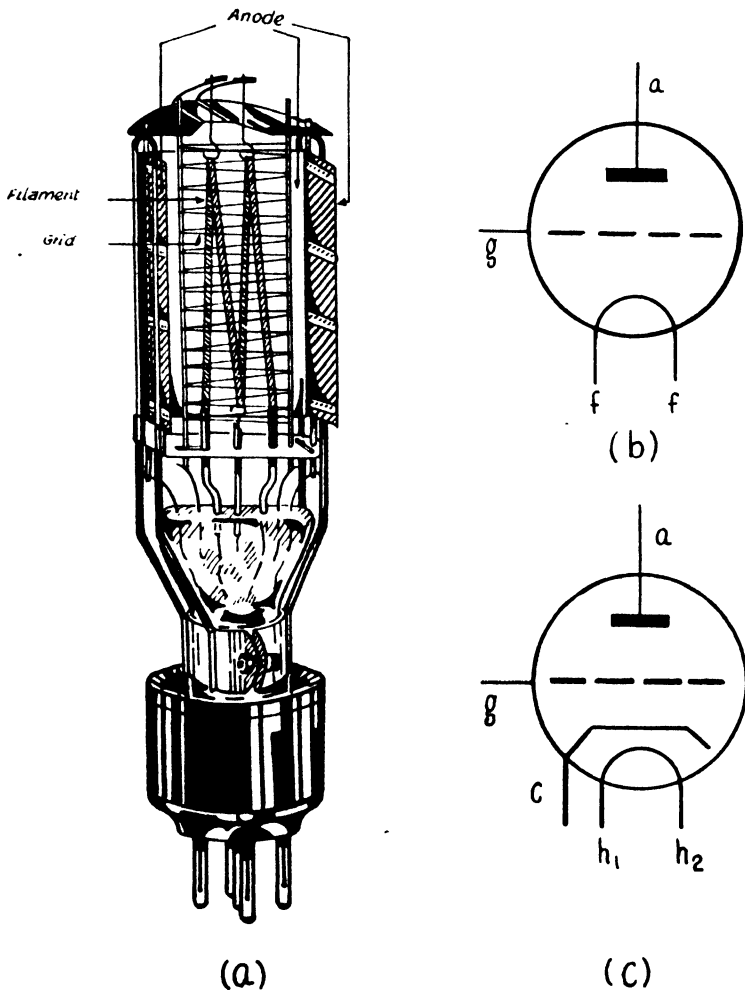


FIG. 301.—Arrangement of electrodes in a triode.

towards the anode. The total space-charge will be concentrated near the cathode, since once an electron has left this region it contributes to the space-charge for only a very brief interval of time. Thus the space current in a triode is determined by the

electrostatic field near the cathode produced by the combined effect of anode and grid potentials.

For a symmetrical grid structure it can be shown that the electrostatic field near the cathode is proportional to $\left(E_g + \frac{E_a}{\mu}\right)$ where E_g and E_a are the grid and anode potentials respectively and μ is a constant determined by the geometry of the valve. The total space current I , varies with $\left(E_g + \frac{E_a}{\mu}\right)$ in exactly the same way that anode current varies with anode voltage for the diode; that is, over the lower part of the curve (for small values of I),—

$$I_s = K \left(E_g + \frac{E_a}{\mu}\right)^{\frac{3}{2}} \quad (2)$$

K being a constant, determined by the dimensions of the valve, and $\left(E_g + \frac{E_a}{\mu}\right)$ being positive.

In general I_s is the sum of the anode current I_a and the grid current I_g , but if the grid is maintained at a sufficiently negative potential with respect to cathode, the grid current is zero since no electrons emitted by the cathode will go to the grid.

Thus for negative grid potential and $\left(E_g + \frac{E_a}{\mu}\right)$ positive :—

$$I_s = K \left(E_g + \frac{E_a}{\mu}\right)^{\frac{3}{2}} \quad (3)$$

for small values of I_s .

Under the same conditions, but with $\left(E_g + \frac{E_a}{\mu}\right)$ negative, I_s will be zero, since the electrostatic field near the cathode will then be such as to repel all the emitted electrons back into the cathode.

VALVE CONSTANTS AND CHARACTERISTIC CURVES

Equation 3 is a mathematical expression connecting I_s , E_g and E_a . It is always convenient to interpret such a result in a graphical form, but here, since there are three variables, this could only be done completely by plotting a series of points in three dimensions using three axes, mutually at right angles, for I_s , E_g and E_a . These points could then be joined to form a surface, the "characteristic surface" of the triode. Such a surface is drawn in perspective in Fig. 302.

Instead of plotting such a surface, certain characteristic curves may be derived; these are of two main types, the mutual and the anode characteristics.

Mutual characteristics

A surface such as that shown in Fig. 302 gives a complete picture of the interconnection between I_s , E_g and E_a ; that is to say

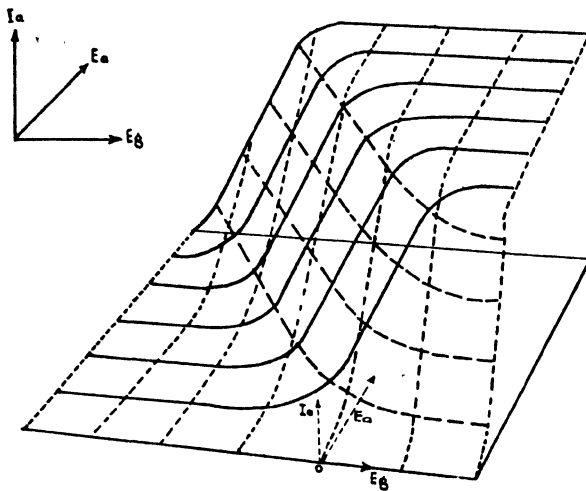


FIG. 302.—Characteristic surface for a triode

on such a surface all three quantities are continuously variable. Now suppose instead that a spot value of E_a , say $E_a = 50$ volts, is taken, and, with E_a kept constant at this value, the variation of I_a with E_g is plotted. The resultant two-dimensional curve will be a cross-section of the characteristic surface taken perpendicular to the axis of E_a through the point $E_a = 50$ volts. Similarly, curves may be plotted showing the connection between I_a and E_g for other values of E_a . The result is a family of mutual characteristics as shown in Fig. 303.

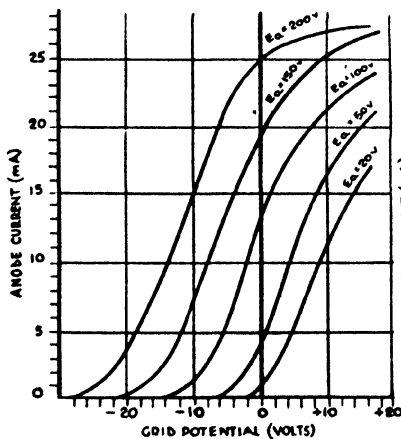


FIG. 303.—Family of mutual characteristics of a triode.

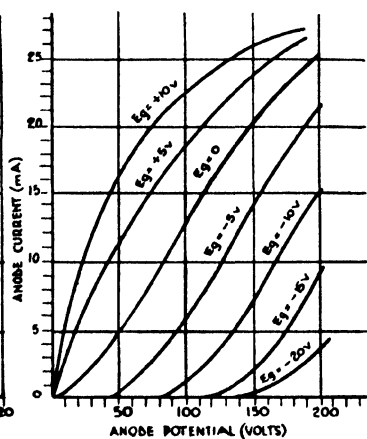


FIG. 304.—Family of anode characteristics of a triode.

This family of curves is equivalent to Fig. 302 except that it gives a picture that is discontinuous as far as E_a is concerned; it can never give a complete representation, but the picture may be made as detailed as required by interpolating for E_a between the curves. It will be noted that the curves have been extended into the region of positive grid potential. When the grid is slightly positive it will, owing to its open construction, attract only a negligible proportion of the total number of electrons emitted from the cathode, and the anode current will still be substantially equal to the total space current. A similarity is seen between the shape of these mutual characteristics and the shape of the diode characteristic shown in Fig. 293. The flattening of the curves for higher values of anode current is in both cases due to the saturation effect; that is, the total emission current fixes an upper limit for the anode current. The point on a mutual characteristic where the anode current becomes zero is called "cut-off", and the corresponding value of E_g is the "cut-off bias". The value E_{c0} of the cut-off bias is clearly seen from equation 3 to be $E_{c0} = -\frac{E_a}{\mu}$.

Anode characteristics

Another family of curves, the anode characteristics, may be derived by choosing fixed values of E_g , and plotting the variations of I_a with E_a . The result will be another set of cross-sections of Fig. 302, this time taken perpendicular to the axis of E_g .

This family of anode characteristics (Fig. 304) is also equivalent to Fig. 302, but this time the discontinuities occur in the values of E_g , and if a more detailed picture is required, it is necessary to interpolate for values of E_g between these curves. In the case of Fig. 304, the curves have not been drawn for sufficiently high values of anode current and anode voltage to show the effects of saturation, but these are similar to the case of the mutual characteristics; namely, that the anode current has an upper limit determined by the emission current, and all the curves will eventually flatten out at this value.

Amplification factor (μ)

The symbol μ has already been introduced as a constant depending solely on the geometry of the valve, and such that the electrostatic field near the cathode is proportional to $\left(E_g + \frac{E_a}{\mu}\right)$.

It is in fact defined as the ratio of the relative effectiveness of the grid and anode voltages in producing electrostatic fields at the surface of the cathode, or (what clearly comes to the same thing) in producing anode current over that range where the anode current is limited by the space charge. In the practical case, due to slight asymmetry of the grid structure and to the necessity of having supporting wires, μ can no longer be considered a pure geometrical constant, but it will vary slightly with anode and grid voltages

and with the emission current. Nevertheless it is defined as follows:—

Amplification factor μ is the ratio of the relative effectiveness of the grid voltage, to that of the anode voltage, in controlling the anode current.

$$\mu = \frac{\frac{\partial I_a}{\partial E_g}}{\frac{\partial I_a}{\partial E_a}}$$

That the amplification factor μ defined in this way is equivalent to the μ of equations 2 and 3 on page 331 may be seen by partial differentiation of equation 3. Thus:—

$$\frac{\partial I_a}{\partial E_g} = \frac{3}{2}K \left(E_g + \frac{E_a}{\mu} \right)^{\frac{1}{2}}$$

and
$$\frac{\partial I_a}{\partial E_a} = \frac{3}{2}K \left(E_g + \frac{E_a}{\mu} \right)^{\frac{1}{2}} \cdot \frac{1}{\mu}$$

giving again:—
$$\mu = \frac{\frac{\partial I_a}{\partial E_g}}{\frac{\partial I_a}{\partial E_a}}$$

To avoid using partial derivatives, the amplification factor μ can be defined in terms of the voltage increments, δE_g and δE_a , in grid and anode potentials respectively, that keep the plate current constant. Thus an increase δE_a in anode potential gives an increase δI_a in anode current, with grid potential constant at E_g ; and it requires an increase $-\delta E_g$ (a decrease) in grid potential to restore the anode current to its original value, with anode potential constant at $E_a + \delta E_a$.

In this case the amplification factor is defined as:—

$$\mu = \frac{\delta E_a}{\delta E_g} \quad (4)$$

It has been stated that in the practical valve, μ will depend very slightly on the operating conditions due to asymmetry of the grid, but for the most part it may be taken as a constant except for a tendency to become lower as cut-off is approached.

Mutual conductance g (sometimes represented by g_m , G_m , or S)

The mutual conductance g (sometimes referred to as trans-conductance) is defined as the rate of change of plate current with respect to change of grid potential.

i.e.
$$g = \frac{\partial I_a}{\partial E_g}$$

Or, using the approximate notation of finite increments, if an increment δE_g in grid potential causes an increase δI_a in anode current, when the anode voltage is kept constant,

$$g = \frac{\delta I_a}{\delta E_g} \quad (5)$$

Mutual conductance has the dimensions of a conductance and is expressed either in micromhos (μmho) or more commonly in milliamps per volt. It will be seen from equation 5 that g is the gradient or slope of the mutual characteristic. Since the mutual characteristics (see Fig. 303) are approximately straight and parallel over most of their length, g is substantially independent of operating conditions, except for a decrease near cut-off. In certain valves, however, the grid is made definitely asymmetrical, with a view to causing a large variation in mutual conductance under different operating conditions. Such a valve is called a "variable- μ " valve and will be discussed later (p. 360).

AC resistance R_a (or ρ)

The anode characteristic resistance (also called the internal resistance or the internal impedance) is defined as the rate of change of anode potential with respect to change in anode current.

$$R_a = \frac{\partial E_a}{\partial I_a}$$

Or, if an increment δE_a in anode potential causes an increase δI_a in anode current, when the grid potential is kept constant,

$$R_a = \frac{\delta E_a}{\delta I_a} \quad (6)$$

R_a has the dimensions of a pure resistance and is measured in ohms (or megohms). It is the reciprocal of the slope of the anode characteristic, and where the anode characteristics are straight and parallel it will be constant (see Fig. 304).

It is important to notice that the AC resistance is concerned only with the ratio of *changes* of anode potential to *changes* in anode current, and *not* with the ratio of *total* anode potential to *total* anode current. This is also true of g and μ .

Reference is frequently made to "low impedance" and "high impedance" valves. A low impedance valve is a valve having a small value of R_a , whereas a high impedance valve has a high value of R_a .

Relation between μ , g and R_a

The three valve constants μ , g and R_a are not independent, but as may be seen from equations 4, 5 and 6, they are connected by the relation:—

$$\mu = R_a \times g \quad (7)$$

where g is in mhos, and not in mA/V.

Derivation of valve constants from characteristics

The valve constants μ , g and R_a may all be derived under given operating conditions from a study of *either* a set of mutual characteristics *or* a set of anode characteristics.

Fig. 305 shows a set of mutual characteristic curves for a CV 1664 (AR13), a low-impedance triode.

Suppose the operating conditions are given as $E_a = 130$ volts, $E_g = -4.5$ volts. From the curve corresponding to $E_a = 130$ volts it can be seen that $E_g = -4.5$ volts gives $I_a = 6.5$ mA (point P, Fig. 305).

Now keeping E_a constant at 130 volts (that is, remaining on the same curve), it can be seen that a change of 1.5 volt in grid potential to -3 volts gives an increase in anode current to 10.25 mA (point Q, Fig. 305).

$$\text{i.e.} \quad \delta E_g = 1.5 \text{ volt, and } \delta I_a = 3.75 \text{ mA}$$

$$\text{Therefore} \quad g = 2.5 \text{ mA/volt}$$

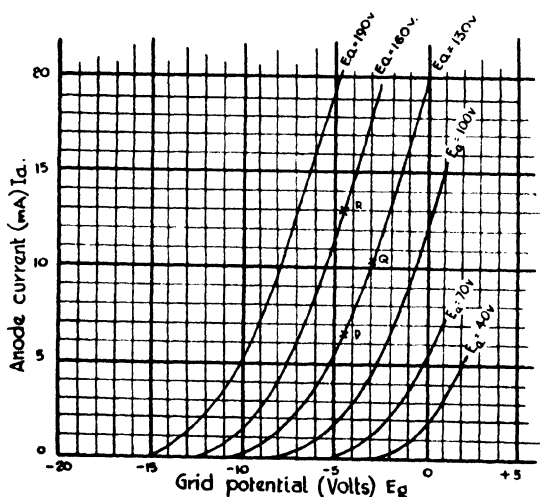


FIG. 305.—Mutual characteristics of a triode (CV 1664).

Now going back to the initial operating point, *i.e.* $E_a = 130$ volts, $E_g = -4.5$ volts, $I_a = 6.5$ mA, and keeping E_g constant at -4.5 volts, a change in E_a involves leaving the curve corresponding to $E_a = 130$ volts; but considering the curve corresponding to $E_a = 160$ volts, it can be seen that the anode current for $E_a = 160$ volts and $E_g = -4.5$ volts is 13 mA (point R), so that an increase of 30 volts in E_a gives an increase of 6.5 mA in I_a , provided E_g is constant at -4.5 volts.

$$\text{i.e.} \quad \delta E_a = 30 \text{ volts,} \quad \delta I_a = 6.5 \text{ mA}$$

$$\text{Thus} \quad R_a = \frac{30}{6.5 \times 10^{-3}} = 4600 \Omega$$

$$\text{Since} \quad \mu = R_a \times g$$

$$\mu = 4600 \times \frac{2.5}{1000} \text{ (g reduced to amps/volt, i.e. mhos)}$$

$$\text{i.e.} \quad \mu = 11.5$$

Now consider Fig. 306, which shows a set of anode characteristics for the same valve. Suppose the operating point is given as $E_g = -4.5$ volts, $E_a = 130$ volts. From the curves, $I_a = 6.5$ mA (point S).

Now keeping E_g constant, an increase in E_a from 130 volts to 160 volts gives an increase in I_a from 6.5 mA to 13.0 mA (point T).

i.e. $\delta E_a = 30$ volts $\delta I_a = 6.5$ mA

Thus $R_a = \frac{30}{6.5 \times 10^{-3}} = 4600$ ohms.

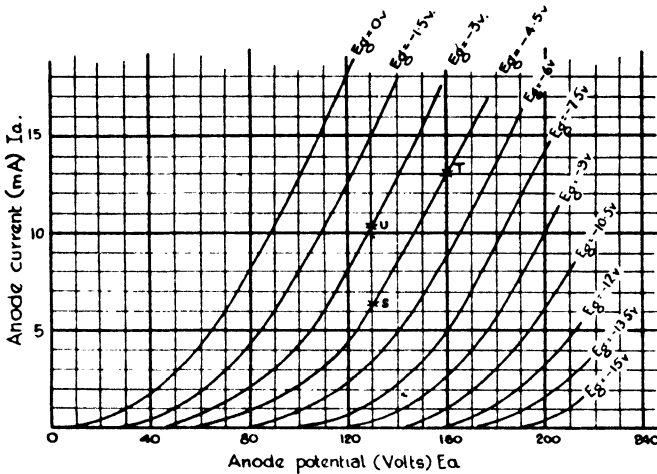


FIG. 306.—Anode characteristics of a triode (CV 1664).

Now taking the same operating point and keeping $E_a = 130$ volts, an increase in E_g from -4.5 volts to -3 volts gives an increase in I_a from 6.5 mA to 10.25 mA (point U).

i.e. $\delta E_g = 1.5$ volts $\delta I_a = 3.75$ mA

Therefore $g = \frac{3.75}{1.5} = 2.5$ mA/volt

and since $\mu = R_a \times g$

$$\mu = 4600 \times \frac{2.5}{1000}$$

i.e. $\mu = 11.5$

This example emphasises once more that the mutual characteristics and anode characteristics are merely two different ways of imparting exactly the same information. One or other of these sets of characteristics, sometimes both, is given in valve data sheets in order that suitable operating conditions may be chosen to suit the purpose for which the valve is to be used. Even if only one set of characteristics is available, it contains all the information required.

THE TRIODE VALVE AS AN AMPLIFIER

Fig. 307 shows a triode arranged as an amplifier in the simplest possible way. The signal to be amplified is applied to the grid in the form of an alternating voltage. E_g is a steady voltage applied in series with the signal, of such a magnitude as to ensure that the grid is always negative with respect to the cathode. The anode is maintained at a high positive potential relative to the cathode by a battery (the high-tension or HT battery, of voltage E_b) acting in series with the load impedance Z_L . Anode current will flow, and there will be a potential drop across the load impedance Z_L ; the potential of the anode relative to cathode will therefore be less than E_b .

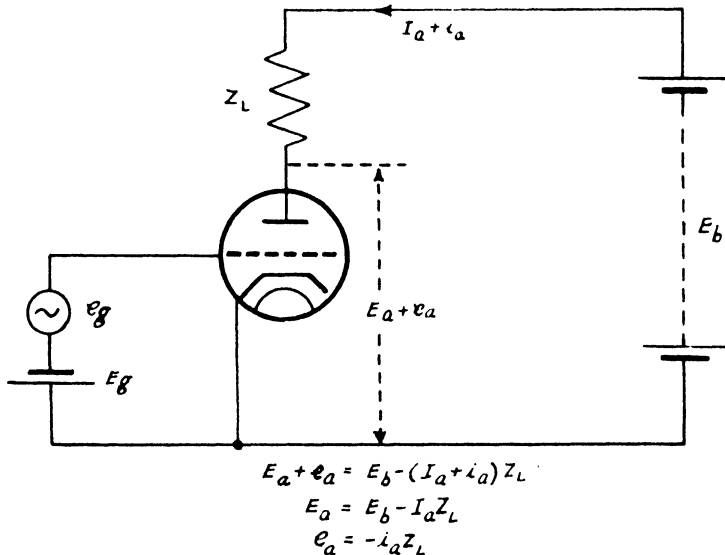


FIG. 307.—Simple circuit of a triode amplifier stage.

When no signal is being applied to the grid ($e_g = 0$), the DC bias voltage E_g will determine the value of the steady anode current I_a and the steady anode voltage E_a . If the small alternating voltage e_g is now applied in the grid circuit, an alternating component i_a is produced in the anode current; this will give an alternating voltage drop across Z_L , resulting in an alternating component e_a in the anode voltage. This alternating component may be utilised as required.

Amplifiers are subdivided into two classes according to the use made of the voltage developed across the load impedance. In the simplest case, it is required merely to develop the maximum possible voltage across the load, and to apply it to the grid of a second valve

for further amplification. Since the grid circuit of a valve is voltage-operated without consumption of power, it is immaterial what *power* is developed in Z_L . Such a stage of amplification is called a "voltage amplifier".

In certain cases, however, the main consideration is the *power* developed in the anode load. For example, in an audio amplifier the *loudness* of the audible result will depend on the *power* dissipated in the loud-speaker or telephone receiver which will be acting as the anode load of the final stage of amplification. This last stage, in which power is the primary concern, is called a "power amplifier", and amplifiers of this type require separate treatment which will be given later.

Dynamic characteristics

In the previous section (see Figs. 305 and 306) an operating point on the characteristics was chosen, determined by the values of E_a and E_g , and the alterations in anode current produced by an additional voltage e_g applied to the grid were then considered. This will now be considered in greater detail.

The mutual characteristics so far considered have shown how I_a varies with E_g provided E_a is kept *constant*. Similarly, in the case of the anode characteristics, there was the proviso that E_g be kept *constant*. These characteristics are known as the "static characteristics", and give certain information about the valve itself, making possible the choice of suitable valves and suitable working conditions for any particular purpose.

But it may now be seen that if a valve is connected up in a particular circuit, as in Fig. 307, with an anode load of impedance Z_L , then if the potential on the grid is varied the potential on the anode is also varied. This does not, however, occur under the conditions under which the static mutual characteristics are plotted, *i.e.* constant E_a . When I_a changes, so does the voltage drop across Z_L , and since the anode voltage is applied from a battery of constant voltage E_a , the anode voltage E_a will change. Thus to get a true picture in this case a set of characteristics is required giving the variation of I_a with E_g , subject to the simultaneous and consequent variations of E_a , the extent of which will vary with the load impedance. Such a set of characteristics is called a set of "dynamic" mutual characteristics, and would be characteristic not of the valve itself, but of the valve when connected to a particular value of anode load. This would appear to necessitate a set of dynamic characteristics for every value of load impedance; fortunately the dynamic characteristics corresponding to any particular value of load impedance can be deduced from the static characteristics as will be shown by an example. For this reason, the latter type only will be found on valve data sheets.

Calculation of gain from dynamic characteristics

Consider the circuit of Fig. 307. The case where the available

HT voltage (E_b) is 190 volts will now be considered, supposing that the valve is a CV 1664 whose static mutual characteristics were shown in Fig. 305 and are repeated in Fig. 308. For simplicity, consider a purely resistive load of $30,000\Omega$.

Now when $I_a = 0$, there will be no potential drop across the anode load, and $E_a = 190$ volts. From the static characteristic corresponding to 190 volts, it is seen that $I_a = 0$ corresponds to $E_g = -15$ volts. The point *A* is therefore on the dynamic characteristic.

When $I_a = 3$ mA, the potential drop across the resistive load will be 90 volts, so that $E_a = 100$ volts; the point *B*, corresponding to $E_a = 100$ volts and $I_a = 3$ mA, will therefore lie on the dynamic characteristic. In the same way by assuming other values for I_a ,

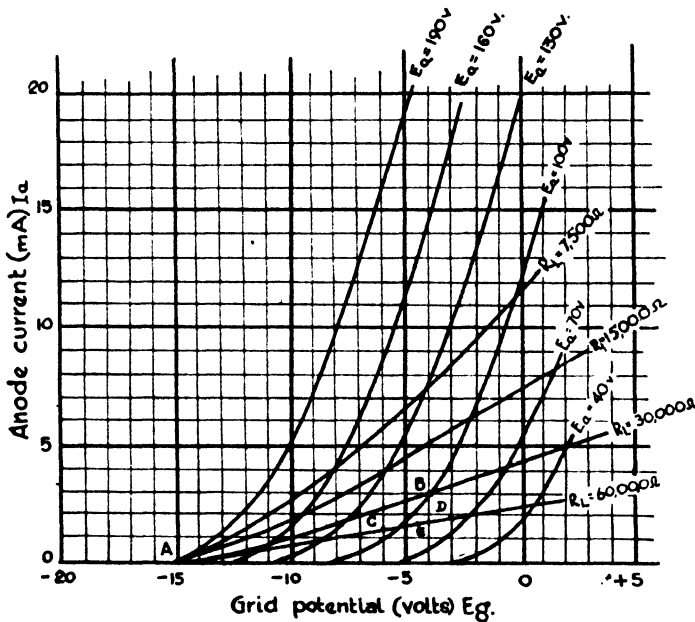


FIG. 308.—Dynamic mutual characteristics for various values of load resistance.

the dynamic characteristic corresponding to a resistive load of 30,000 ohms (or for any other value of resistance) may be plotted completely. A number of these dynamic characteristics is shown in Fig. 308.

These facts are at once apparent :—

(a) The characteristics are for the most part very straight except for slight curvature near cut-off.

(b) The higher the load resistance the smaller the slope of the dynamic characteristics, and *vice versa*.

(c) The smaller the load resistance, the more nearly does the dynamic characteristic coincide with the static characteristic

$E_g = 190$ volts, and the greater is the curvature at the lower end.

The dynamic characteristic corresponding to an available HT supply of 190 volts and a load resistance of 30,000 ohms having been deduced, the operating point on that characteristic (say, $E_g = -4.5$ volts, corresponding to an anode current of 2.8 mA) may be chosen. Now suppose an alternating voltage is applied to the grid in addition to the steady bias -4.5 volts, and let the peak value of the signal be 1.5 volts; then the grid potential will vary between -6 volts and -3 volts, and it is now apparent that for the given load, $30,000\Omega$, the variations in anode current will all lie on the dynamic mutual characteristic corresponding to that value of load. Therefore I_a will vary between 2.3 mA and 3.3 mA; that is, a total variation of 1 mA, or 0.5 mA on either side of the "no signal" anode current of 2.8 mA. The change in anode current will be proportional to the change in grid voltage, and an undistorted signal will result provided that the dynamic characteristic is straight throughout the range of the variation of grid voltage. For this reason the operating point is chosen in the centre of the straight portion of the characteristic lying in the range of negative values of grid potential. This allows the maximum voltage signal to be applied to the grid without causing distortion; for, generally speaking, the voltage on the grid, relative to the cathode, must always be sufficiently negative to prevent the flow of grid current, and yet, on the other hand, not so negative as to cause operation over the lower curved portion of the dynamic characteristic.

With a signal of peak voltage 1.5 volts on the grid, an alternating anode current of peak value 0.5 mA flows in the load resistance of $30,000\Omega$, thus developing a peak voltage of 15 volts across the load. Thus in the particular circuit considered there is a voltage amplification of 10. This is known as the "stage gain", and it depends on the value of the load resistance.

Suppose the load is now changed to $60,000\Omega$. Choosing again $E_g = -4.5$ volts, it is seen that a 1.5 volt peak signal will cause an alternating anode current of peak value 0.275 mA (points *C* and *D*, Fig. 308) about the steady value 1.6 mA (point *E*). This gives a peak alternating voltage of 16.5 volts across the $60,000\Omega$ load—that is, a stage gain of 11.

It will be verified later, that the higher the load resistance, the higher the stage gain; but the stage gain will always be less than the amplification factor (μ) of the valve as derived from its static characteristic. (For this valve, $\mu = 11.5$.)

The load line

Corresponding to the dynamic mutual characteristics, are the "load lines" on the graph of the anode characteristics. Fig. 309 shows the static anode characteristics for the CV 1664 (the triode considered in the preceding paragraphs) together with load lines

for various values of resistive anode load, assuming again an available HT supply of 190 volts.

From Fig. 307 it can be seen that (taking $Z_L = R_L$, a pure resistance) :—

$$E_a = E_b - I_a R_L \quad (8)$$

If R_L and E_b are constants, the two variables I_a and E_a may be plotted in the form of a graph. This will be a straight line (since equation 8 is linear in E_a and I_a), and it will clearly pass through the points given (i) by $E_a = E_b$, $I_a = 0$ and (ii) by $E_a = 0$, $I_a = \frac{E_b}{R_L}$. This straight line is called the "load line" for the particular load

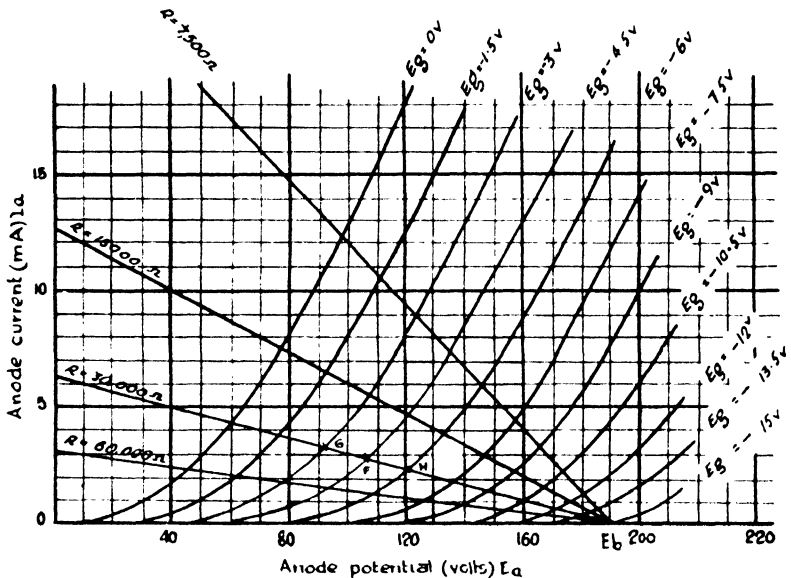


FIG. 309.—Anode characteristics showing load lines for various values of anode load.

considered and the HT supply available. Consider in particular the load line for $R_L = 30,000\Omega$ and $E_b = 190$ volts. Suppose that $E_g = -4.5$ volts. The -4.5 volts anode characteristic meets the $30,000\Omega$ load line in the point F , corresponding to $E_a = 106$ volts, $I_a = 2.8$ mA. Let this be taken as the operating point; that is, let E_g be made -4.5 volts; because the valve has a $30,000\Omega$ load and an available HT supply of 190 volts, this point F shows that the anode current will be 2.8 mA. Now suppose a signal of peak value 1.5 volts is applied to the grid, *i.e.* E_g will vary between -3 volts and -6 volts (points G and H). From the points of intersection of the corresponding characteristics with the $30,000\Omega$ load line, it can be seen that I_a varies between 3.3 mA and 2.3 mA and E_a between 91 and 121 volts. Thus for equal swings of grid

voltage about the standing bias, equal swings in the value of anode current (and of anode voltage) are obtained; this implies no distortion. In choosing a load, therefore, a value must be selected such that the corresponding load line makes equal intercepts on the anode characteristics. The selection of a load line making equal intercepts is exactly equivalent to selecting a straight dynamic characteristic.

Returning to the swings in anode current, these have a peak value of $\frac{3.3 - 2.3}{2}$, *i.e.* 0.5 mA, giving a peak value to the alternating voltage across the 30,000 Ω load of 15 volts. Since the applied signal was 1.5 volts peak, this represents a stage gain of 10—which result has already been obtained by considering the dynamic mutual characteristic corresponding to a load of 30,000 ohms.

Thus, in the same way that the static mutual and anode characteristics are exactly equivalent as far as imparting information about the valve itself is concerned, so the dynamic mutual characteristic and the load line are equivalent ways of expressing the behaviour of the valve with a given resistive anode load, and either method may be used in designing a stage. It is, however, somewhat easier to detect inequality of intercepts on the load line than to detect slight curvature of the dynamic characteristic, so that the load line method of choosing operating conditions is the one usually employed.

Equivalent circuits

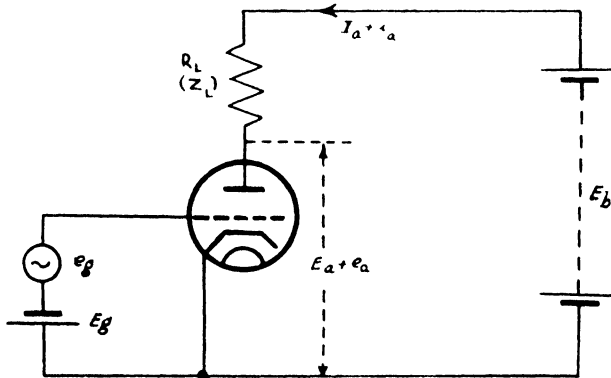


FIG. 310.—Simple circuit of a triode amplifier.

Consider the circuit of Fig. 310. It has already been demonstrated that the steady value of anode current I_a is determined by the steady values of grid voltage E_g and anode voltage E_a . Suppose now the grid voltage is changed by an amount e_g . If the anode voltage were kept constant, the corresponding change in anode current would be i_a' given by:—

$$i_a' = g e_g \quad (9)$$

It has been seen, however, that the anode voltage will not remain constant owing to the change in potential drop across R_L caused by the change in anode current.

Now suppose that the anode voltage changes by an amount e_a , due to this cause or any other; then the corresponding change i_a'' in anode current, assuming the grid voltage to be kept constant, is given by:—

$$i_a'' = \frac{e_a}{R_a} \quad (10)$$

Therefore the total variation in anode current due to simultaneous changes in anode voltage and grid voltage will, to the first order, be given by:—

$$i_a = g \cdot e + \frac{1}{R_a} e_a \quad (11)$$

But the change in anode voltage consequent upon a change e_g of grid potential will be:—

$$e_a = -i_a R_L \quad (12)$$

The negative sign occurs because a positive increment in grid voltage will cause an increase in voltage drop across R_L and therefore a *reduction* in anode voltage (see Fig. 311).

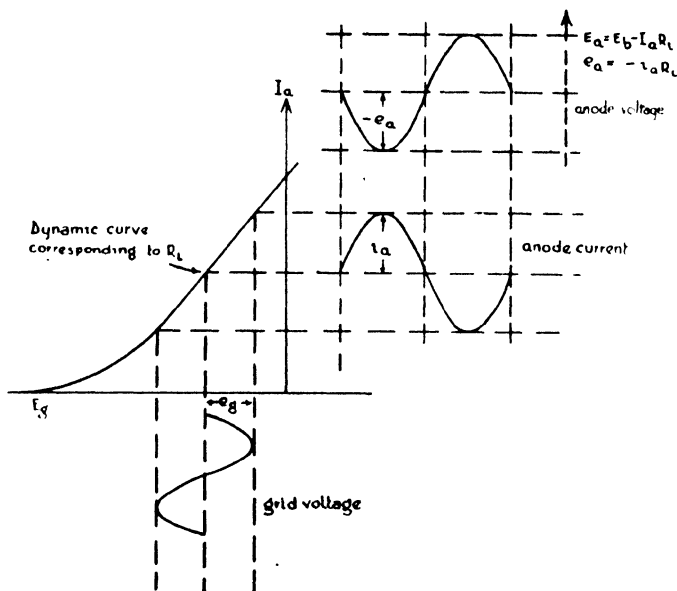


FIG. 311.—Illustrating relation between e_g , i_a and e_a for resistive load.

Eliminating e_a between equations 11 and 12:—

$$i_a = g e_g - \frac{i_a R_L}{R_a}$$

i.e.

$$i_a = \frac{R_a g}{R_a + R_L} e_g$$

$$i.e. \quad i_a = \frac{\mu}{R_a + R_L} e_g \quad (13)$$

From equation 13, it can easily be seen that Fig. 312 is the equivalent circuit of Fig. 310. This, it is to be noted, applies only to AC components of current and voltage. The separation of AC and DC components can be justified by the superposition theorem (p. 231), as long as the linear part of the valve characteristic is

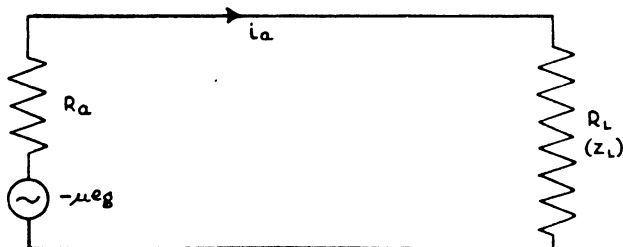


FIG. 312.—Equivalent circuit of triode amplifier (constant-voltage generator form).

used. It is usual to take i_a in a clockwise sense, and regard the generator as having a negative EMF. Equation 13, with the new interpretation on the direction of i_a , becomes:—

$$i_a = \frac{-\mu e_g}{R_a + R_L} \quad (14)$$

If R_L in Figs. 310 and 312 be replaced by a general impedance Z_L , equation 14 becomes:—

$$i_a = \frac{-\mu \cdot e_g}{R_a + Z_L} \quad (15)$$

The change in voltage produced across Z_L will then be given by:—

$$e_z = \frac{-\mu e_g Z_L}{R_a + Z_L} \quad (16)$$

The stage gain M will be the ratio of the magnitudes of e_z and e_g .

$$\therefore M = \frac{\mu |Z_L|}{|R_a + Z_L|} \quad (17)$$

From this equation it will be seen that the stage gain M is always less than the amplification factor μ of the valve, but that it may be made as near to μ as required by taking a sufficiently large value of $|Z_L|$, provided that there is no limit to the value of E_s available. The equivalent circuit of Fig. 312 is known as the "constant-voltage generator" form of the equivalent circuit of an amplifier, and is the basis of most amplifier design calculations. This form is usually the most convenient for use when triodes are involved, but the "constant-current generator" form (Fig. 313) is preferable when R_a is much greater than the anode load Z_L , as is often the case with pentodes. The equivalence of the two forms may be verified as follows:—

Dividing numerator and denominator of the right-hand side of equation 15 by R_a :—

$$i_a = \frac{\frac{-\mu}{R_a} e_g}{1 + \frac{Z_L}{R_a}}$$

$$i.e. \quad i_a = -g e_g \cdot \frac{R_a}{R_a + Z_L} \quad (18)$$

The voltage developed across the anode load is therefore

$$E_L = -g e_g \cdot \frac{R_a Z_L}{R_a + Z_L} \quad (19)$$

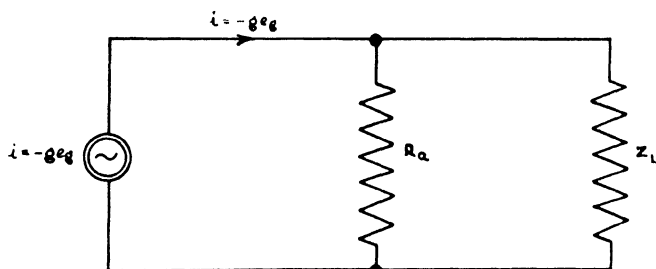


FIG. 313.—Constant-current form of the equivalent circuit of an amplifier.

This is the voltage developed by a constant current $-g e_g$ across a circuit consisting of R_a and Z_L in parallel (see Fig. 313).

$$\text{Hence} \quad M = g \frac{R_a |Z_L|}{|R_a + Z_L|} \quad (20)$$

which is clearly equivalent to equation 17.

Grid current

The question of the flow of grid current has so far been dismissed because :—

(a) The grid has in general been kept so negative with respect to the cathode, that the grid will not collect electrons emitted by the cathode ; and

(b) Even if the grid is slightly positive with respect to the cathode, the grid current will generally be very small since the grid surface is very small.

Characteristics showing the grid current plotted against grid potential are often given on the mutual characteristic,—using a magnified scale for current, since the grid current is of the order of microamps. The grid current will depend on anode potential, being small when the anode potential is high ; for very small anode voltages, the grid current may be of the order of milliamps for positive grid voltages approaching the anode potential.

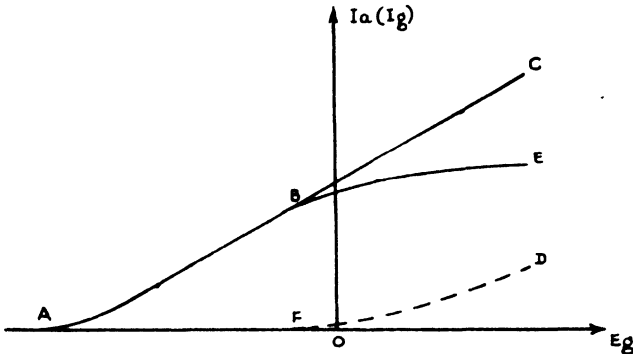


FIG. 314.—Effect of grid current on the dynamic mutual characteristic.

Although in certain instances it is desirable that grid current should flow (*e.g.*, provision of grid leak bias), it is in general undesirable in amplifiers for two reasons.

(a) Fig. 314 shows a dynamic mutual characteristic *ABC* such as would be obtained if no grid current flowed for positive grid voltages—that is to say, *ABC* is really a graph of total space current against grid voltage. If a portion of this space current is due to grid current, shown by the graph *FD*, then *ABE* will represent the graph of anode current against grid potential. Thus, due to the flow of grid current, a dynamic characteristic tends to take the form of the curve *ABE*. This curvature of the dynamic characteristic for positive grid potentials will introduce distortion, and the output will no longer correspond to the input. In the same way, flow of grid current will cause the anode characteristics to intersect the load line in unequal intercepts at positive grid voltages.

(b) A flow of grid current implies a dissipation of power in the grid circuit, and the valve is no longer strictly a voltage-operated device. Thus flow of grid current causes small power losses.

Effect of gas

If even a very small quantity of gas is present in a valve, the electrons emitted by the cathode will collide with the molecules of the gas, thereby ionising them. The positive ions thus formed are attracted towards the cathode and the negative control grid. The negative ions formed are attracted towards the anode. Those ions which bombard the cathode tend to destroy its electron-emitting properties, while those reaching the grid constitute a negative grid current, flowing from grid to cathode through the external circuit. This current will develop a voltage across the grid-cathode resistance in such a direction as to make the grid less negative, thereby increasing the space current; this increases the number of positive ions produced, causing an increase in grid

current and the application of a further positive voltage to the grid. If the grid-cathode resistance is sufficiently high, this process may become cumulative, and the space current rises rapidly to an excessive value, causing damage to the valve.

Effect of secondary emission

A further danger to valves caused by a grid-cathode circuit of high resistance lies in the possibility of "secondary emission" from the grid. If one primary electron from the cathode, impinging on the grid, causes the emission from the grid of several secondary electrons, the grid will acquire a positive charge; and if the grid-cathode resistance is high, this charge will not leak away immediately. More primary electrons will therefore be attracted to the grid, causing the emission of further secondary electrons, an increase in the positive charge on the grid, and a corresponding increase in the space current of the valve. This process is cumulative, and the space current may increase to an excessive value and cause damage to the valve.

Effects of open-circuited ("free") grid

When a valve is operated with a circuit of unduly high resistance between grid and cathode, one of three things may happen:—

(1) If any gas is present in the valve, positive ions reaching the grid may cause the space current to rise rapidly to a dangerous value.

(2) If secondary emission takes place from the grid, the space current may again rise rapidly to a dangerous value.

(3) If no gas is present, and no secondary emission takes place from the grid, electrons leaving the cathode may accumulate on the grid, thus imparting to it a negative charge. A condition of equilibrium is soon reached in which the grid has a large negative charge, and the space current is reduced almost to cut-off. Although in this case there is little possibility of damage being done, the valve will clearly cease to perform its normal function.

These three ill-effects can be avoided by keeping the resistance of the grid-cathode circuit low; and valve manufacturers, in their tables of operating data, usually state the maximum value of this resistance for each type of valve. For most small receiving valves, it is of the order of $2M\Omega$, while for power valves (in which the rise of current due to gas or positive ions is much more serious) it is much less.

Interelectrode capacity

Other characteristics of the valve that must be considered are the capacities that exist between the various pairs of electrodes.

In the case of a triode there are three such capacities; these are shown in Fig. 315:—

(a) The *grid-cathode capacity*, C_{gk} , effectively in parallel with the input circuit and sometimes called the *input capacity*.

(b) The *anode-cathode capacity*, C_{aa} , in parallel with R_L and sometimes called the *output capacity*.

(c) The *grid-anode capacity*, C_{ga} , providing a leakage path by which energy may be transferred from anode circuit to grid circuit, and therefore sometimes referred to as the *leakage capacity*.

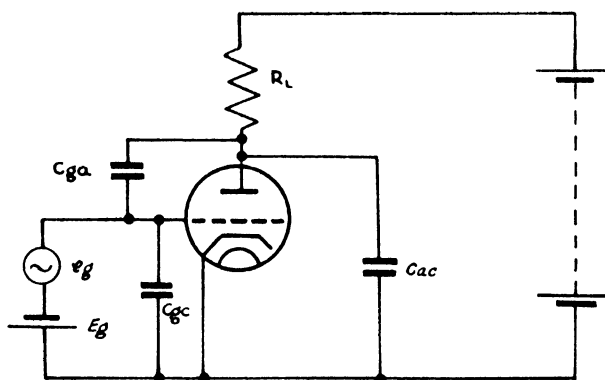


Fig. 315.—Triode amplifier showing interelectrode capacities.

Each of these capacities has in effect a high resistance shunt across it due to DC leakage resistance between electrodes, but this resistance is in general very high and will be neglected, as it introduces unnecessary complications into the equivalent circuit. The effect of these capacities is as follows :—

Grid-cathode capacity gives the valve a finite input impedance ; this causes a current to flow in the grid circuit, and so causes dissipation of power in the resistive component of the grid circuit impedance.

Anode-cathode capacity puts a shunt across the anode load and reduces the stage gain at high frequencies.

Grid-anode capacity.—This is the most important of the interelectrode capacities, and will be discussed in greater detail. Clearly it provides, particularly at high frequencies, a leakage path between anode and grid circuits by means of which voltage changes on the anode will be fed back to the grid. If this voltage fed back to the grid is of sufficient magnitude and is in the correct phase, the valve may cease to function as an amplifier and become an oscillator. This leakage capacity is the cause of instability in the triode, particularly when used as an amplifier at radio frequencies. Historically, the evolution of the screen-grid and pentode valves was a direct consequence of attempts to reduce the grid-anode capacity to such an extent that the valve would be stable as an RF amplifier ; but these pentodes have other advantages over triodes, such as very high μ , and are now almost universally employed where a voltage amplifier at audio or carrier frequencies is required.

Miller effect

The effect of grid-anode capacity on the grid-cathode impedance is known as "Miller effect". It can be shown that, with a resistive load, the input impedance is equivalent to a capacity

$$C = C_{gc} + C_{ga}(1 + M)$$

where C_{gc} and C_{ga} are the grid-cathode and grid-anode capacities respectively, and M is the gain of the stage.

If the anode load is reactive and a phase-shift θ occurs in the amplifier, the input impedance is equivalent to a condenser C in parallel with a resistance R , where:—

$$C = C_{gc} + C_{ga}(1 + M \cos \theta)$$

and

$$R = \frac{-1}{\omega C_{ga} \cdot M \sin \theta}$$

This resistive term will be negative if θ is positive, *i.e.*, for inductive loads, and may cause oscillations.

TETRODE VALVES

As was pointed out in a previous section, the screen-grid valve or tetrode was originally introduced to overcome ill-effects of grid anode capacity which become apparent when a triode is used as an RF amplifier. It has two grids between cathode and anode; the grid nearer the cathode performs exactly the same function as the grid in the triode and is usually referred to as the "control grid", while the additional grid acts as an electrostatic screen between the control grid and the anode, and is therefore called the "screen-grid" or "screen". The screen is maintained at a high positive potential approaching that of the anode, and has a considerable effect on the electron stream between control grid and anode.

Consider the electrostatic field between the electrodes in terms of "lines of force". If the screen were a solid metal plate maintained at a potential equal to that of the anode, lines of force leaving the cathode and grid would terminate on the screen, and there would be no electrostatic field in the space between screen and anode. Thus there would be no capacity between anode and screen, nor between grid and anode. Now consider the screen made up in the form of a close wire mesh and maintained at a potential not necessarily equal to, but approaching, that of the anode. This time the screening effect will be considerable but not perfect, though with a fine mesh structure it will be practically so. The result is that there will be capacity between the pairs of electrodes grid and screen, screen and anode, and anode and grid; though the grid-anode capacity will be very much reduced from that in a triode. In commercial types of screen grid valve the residual grid-anode capacity varies from 0.001 $\mu\mu\text{F}$ to 0.02 $\mu\mu\text{F}$, as compared with 2 $\mu\mu\text{F}$ to 8 $\mu\mu\text{F}$ for a triode.

Fig. 316 shows a typical anode characteristic for a tetrode, drawn under conditions of constant grid voltage (E_g) and constant screen voltage (E_s). When the anode potential is zero, all the

emitted electrons are attracted to the screen, giving a fairly high screen current (I_{sg}); the anode current (I_a) will be zero. If, now, the anode potential is increased, some of the electrons passing through the meshes of the screen are carried on by their momentum and come under the influence of the anode, to which they are attracted, giving an anode current which will increase with

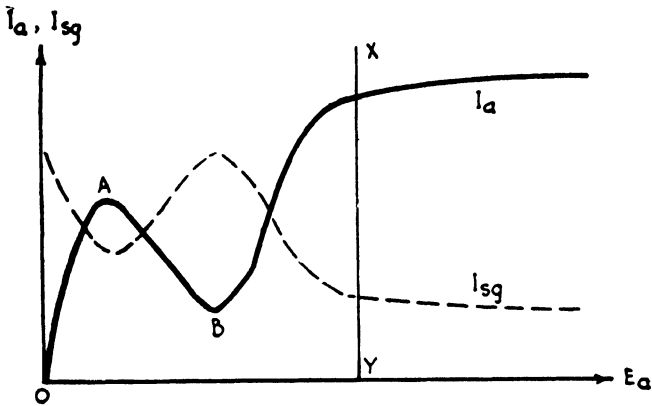


FIG. 316.—Anode characteristic of a screen grid valve or tetrode showing the effect of secondary emission.

increased anode potential. Due to the screening effect of the screen, however, the potential of the anode will have very little effect on the electrostatic field in the vicinity of the cathode, and an increase in anode potential will not appreciably increase the total space current. Any increase in anode current will therefore be at the expense of the screen current (see portion OA of curve shown in Fig. 316).

Secondary emission

As the anode potential increases, so also will the velocity of the electrons on arrival at the anode. The effect of bombarding the anode with fast moving electrons is that other electrons may be ejected by the force of impact. The quantity of electrons thus ejected (or "secondary electrons", as they are usually called) will vary with the material of the anode and the velocity of the electrons reaching the anode from the cathode ("primary electrons"). In certain circumstances as many as ten secondary electrons may be liberated by one fast-moving primary electron. This phenomenon of "secondary emission" also occurs in the diode and triode, but in these cases secondary electrons emitted from the anode are attracted back into the anode and have no effect on the behaviour of the valve. With the tetrode, however, the velocity of the primary electrons is sufficiently high to cause secondary emission while the anode is at a lower potential than the screen grid; there is therefore a tendency for the screen to collect these secondary electrons emitted

from the anode, thereby causing an increase in screen current at the expense of anode current. A further increase in anode potential will increase the velocity of the primary electrons and therefore increase the emission of secondary electrons; if the screen is still at a higher potential than the anode it will collect practically all these slow-moving secondary electrons, with the result that the anode current will actually *decrease* with increased anode potential.

This state of affairs is represented by the portion *AB* of the anode characteristic (Fig. 316). Under the operating conditions that give this portion of the characteristic, the valve behaves as a *negative resistance* device, since an increase in anode voltage causes a decrease in the anode current, and a decrease in anode voltage an increase in the anode current. This negative resistance property is used in the dynatron oscillator (see Chapter 10).

If the anode potential is still further increased, the majority of the secondary electrons will no longer be attracted to the screen, but more and more will be drawn back into the anode and the anode current will once more increase with increased anode potential, at the expense of a decreasing screen current. The portion of the tetrode characteristic that is useful for most purposes is that portion well to the right of the vertical line *XY* in Fig. 316. In this region the curve becomes practically straight, and the anode current is nearly independent of anode voltage indicating a very high value of AC resistance R_a . The effect of the grid, however, is practically the same as if the screen and anode together formed the collecting electrode—that is to say, the mutual conductance is of the same

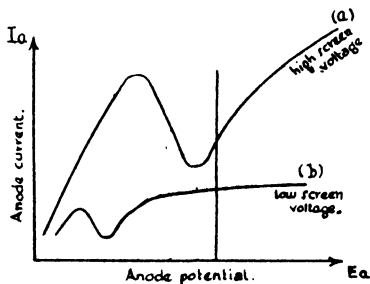


FIG. 317.—Anode characteristics for a tetrode showing effect of varying screen potential.

order as for a triode. Hence, from the relationship between the valve constants, the amplification factor μ is high. The mutual characteristics have much the same shape as those of a triode, but the curves for different values of anode voltage are closer together, indicating the high AC resistance.

The screen potential, as might be expected, has a considerable effect on the shape of the anode characteristic since it determines at what anode potential the effects of secondary emission will cease to be apparent; it also determines the total space current, and hence the maximum standing anode current.

Fig. 317 shows anode characteristics for a typical tetrode plotted for high (curve *a*) and low (curve *b*) screen voltages. The screen voltage is obtained either by a tapping on the HT battery, or more commonly by connecting the screen to HT positive by means of a dropping resistor of suitable value or a potentiometer, as shown

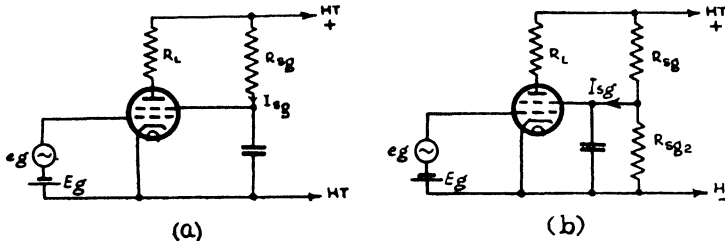


FIG. 318.—Simple circuit of a tetrode arranged as an amplifier.

in Fig. 318*a* and *b* respectively; the value of the resistance may be calculated from the fact that the screen current is normally about a quarter of the value of the anode current.

The screen-grid valve as an amplifier

Fig. 318 shows a tetrode arranged as a voltage amplifier. With an alternating voltage applied between cathode and grid, there will be fluctuations in screen current, just as there are fluctuations in anode current. The screen current will therefore cause fluctuations in the screen voltage due to the potential drop across R_{sg} . Since there is capacity between grid and screen of about the same order as between grid and anode for a triode there is still a leakage path for the transfer of energy from anode circuit to grid, thereby nullifying to a large extent the advantage of a low residual grid anode capacity. This effect is overcome by connecting the screen grid to the cathode through a condenser. This will represent a negligible impedance at high frequencies, and the screen grid and cathode will be virtually at the same (alternating) potential. There will then be no coupling between anode and grid circuits, apart from the very small residual grid-anode capacity. It should be noted that the advantages of low grid-anode capacity will be nullified unless great care is taken to screen the grid and anode circuits external to the valve. For this reason most valves are now metallised, and either the grid or the anode lead is brought out to the top cap to which a connection is made by means of a screened lead.

Due to the restriction on the working part of the characteristic imposed by secondary emission, the screen grid tetrode is of little or no use as a power amplifier, and its use as a voltage amplifier is limited, since it can handle only a very small grid swing. These valves are practically obsolete.

The critical-distance tetrode

In practice, in order to retain the essential features of the

THE CRITICAL-DISTANCE TETRODE

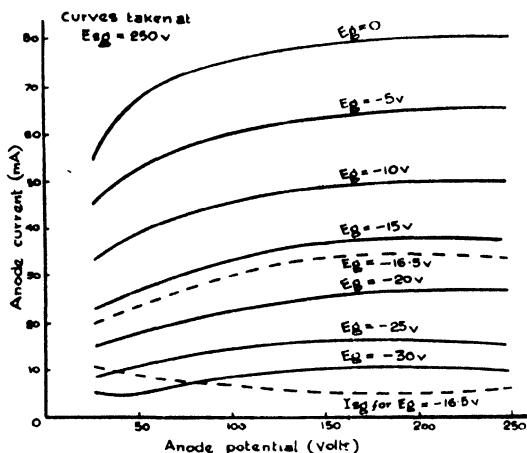


FIG. 319.—Anode characteristics of a critical-distance tetrode.

tetrode (*i.e.*, low grid-anode capacity and high amplification factor), and at the same time to increase its voltage and power handling capacity with limited anode voltages, it is necessary to suppress or reduce considerably the effects of secondary emission from the anode. There are several ways of achieving this.

One way is to design the valve with a small grid-screen and large anode-screen separation combined with the use of an open-meshed screen. The screen potential will still largely govern the space current, and the open-meshed screen will allow most of the electrons to pass through and come under the influence of the anode.

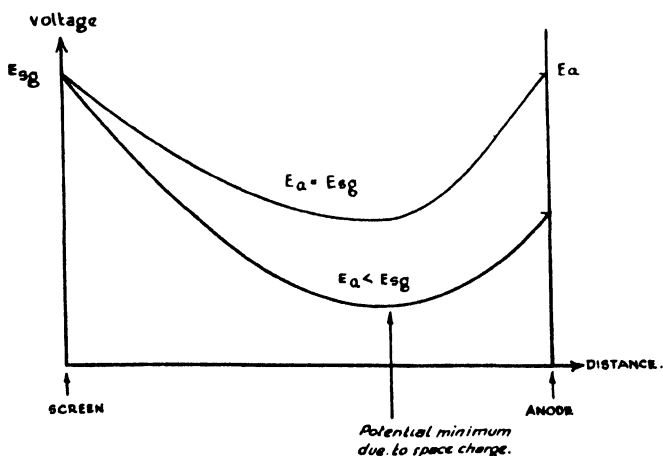


FIG. 320.—Potential distribution between screen and anode in critical-distance or beam tetrode.

Even if the anode potential is very low compared with that of the screen, secondary electrons emitted at the anode will have to travel a considerable distance before the attraction of the screen is greater than that of the anode. Thus the effect of secondary screen current is entirely eliminated, and the anode characteristics of a "critical-distance tetrode" are as shown in Fig. 319. The screen current is made small by optical alignment of the wires of the control grid and of the screen, so that the latter will intercept a minimum number of electrons.

Fig. 320 shows the potential distribution between screen and anode for a critical-distance or beam tetrode.

The beam tetrode

To reduce further the effects of secondary emission additional electrodes may be provided between screen grid and anode.

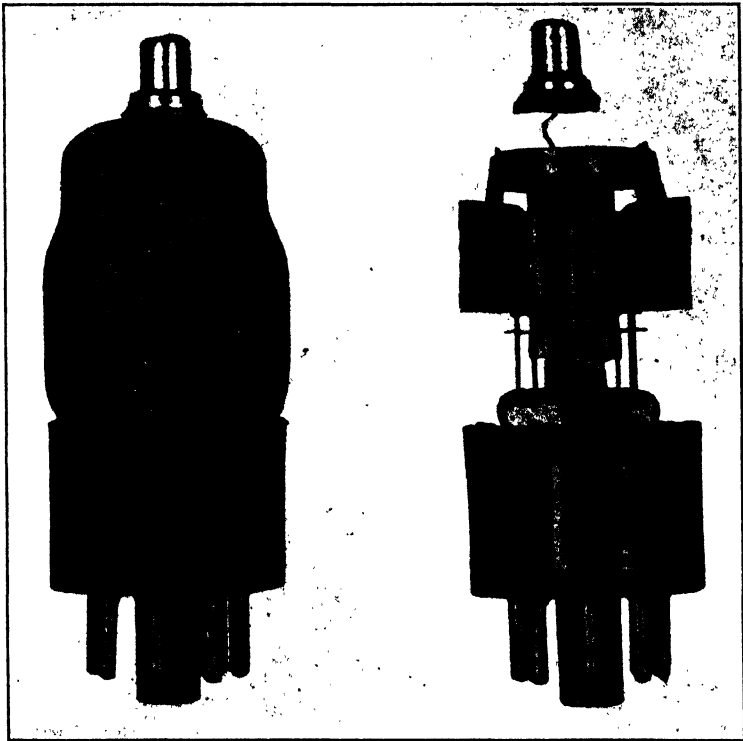


PLATE 18.—CV 1343 (ARP 38) beam tetrode valve.

These electrodes are connected to the cathode inside the valve and will repel the electron stream. The electrodes are arranged so that they concentrate the electron stream into a comparatively narrow beam (see Fig. 321), and for this reason are usually referred to as "beam-forming plates". The concentration of the electrons

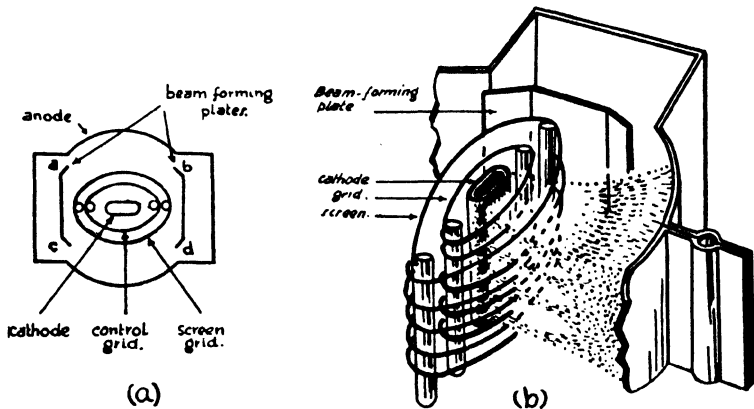


FIG. 321.—Arrangement of electrodes in the beam tetrode.

into a beam, combined with a large distance between screen and plate, gives an intensified space-charge effect in the screen-anode space which will repel the secondary electrons back into the anode. The screen current is again made small by having an open-meshed screen, and optical alignment of control grid and screen. Such a valve is called a "beam tetrode"—the 6V6 being a typical example. A set of anode characteristics for this valve is given in Fig. 322.

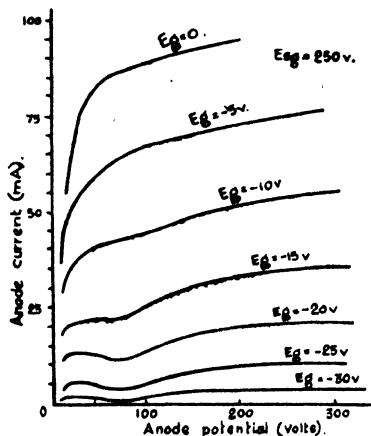


FIG. 322.—Anode characteristics of the 6V6.

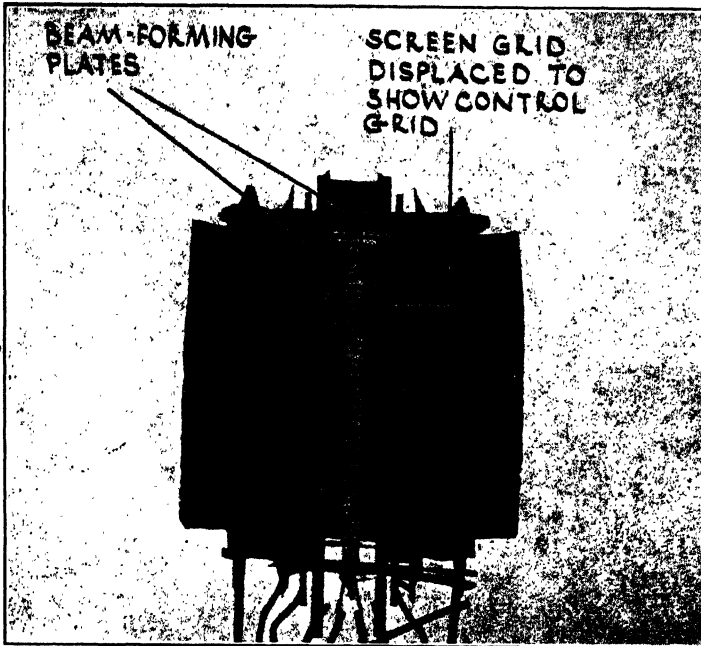


PLATE 19.—6V6 beam tetrode valve, showing electrode structure.

Valves of the critical distance and beam tetrode types are often referred to as “kinkless” tetrodes for obvious reasons; in view of their suitability as power amplifiers they are also called “output tetrodes”.

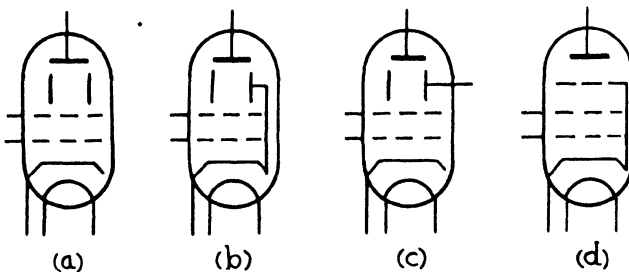


FIG. 323.—Graphical symbols for the beam tetrode.

In Fig. 323, *a*, *b* and *c* show the graphical symbols used for a beam tetrode. Fig. 323*a* is the general symbol, *b* is that used when internal connection is made between the beam-forming plates

and cathode, while c is used when the beam-forming plates are brought out to a separate terminal. The symbol of Fig. 323*d* is sometimes used, though strictly it refers only to a true pentode (see next section) that has the connection between the fourth electrode (suppressor grid) and cathode made internally.

PENTODE VALVES

An alternative method of reducing secondary emission is the introduction of an additional electrode, in the form of a third grid, between the screen and the anode. This third grid is called the "suppressor", and the resulting five-electrode or "pentode" valve is one of the most important types. The suppressor is given a negative potential relative to anode and screen, and this prevents the low-velocity secondary electrons from reaching the screen; it is usually built of very open-mesh wire so that it does not interfere appreciably with the passage of the high-velocity primary electrons towards the anode. The suppressor-grid is usually connected to cathode, but, since some other connection may require to be made (as, for example, in suppressor-grid modulation), the lead to the suppressor-grid is usually brought out of the valve to a separate pin and the connection made externally. In certain cases where a pentode is suitable only as a power amplifier the connection is made internally, and the pentode then has the same external connections as a tetrode (see Fig. 323*d*).

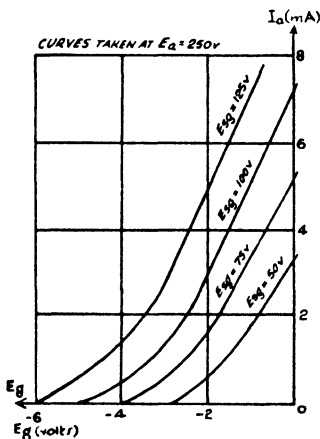


FIG. 324.—Mutual characteristics of a typical pentode (CV 1056).

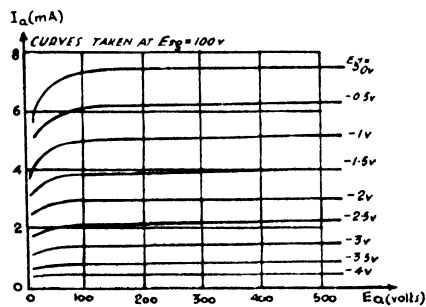


FIG. 325.—Anode characteristics of a typical pentode (CV 1056).

Fig. 324 shows the mutual characteristics, and Fig. 325 the anode characteristics, of a typical pentode, the CV 1056 (VR56) (EF36). The constants of such a valve are approximately:—

$$g = 2.4 \text{ mA/volt}; R_s = 1.5 \text{ M}\Omega, \text{ and } \mu = 3600.$$

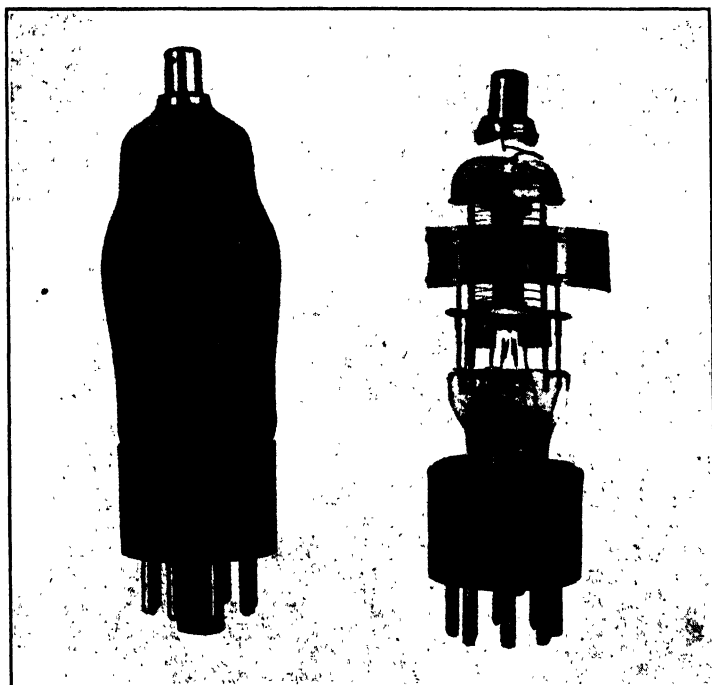


PLATE 20.—CV 1053 (ARP 34) (EF39) pentode valve.

Variable- μ pentodes

The variable- μ pentode is a pentode in which the control grid is made to have an asymmetrical structure. This is normally done by making the pitch of the grid vary along its length, the meshes of the grid being closer at one end than at the other. An alternative method is to allow the cathode to project some distance outside the control grid. In either case the result is that various parts of the valve reach cut-off with different grid bias voltages, so that the overall cut-off comes gradually rather than abruptly.

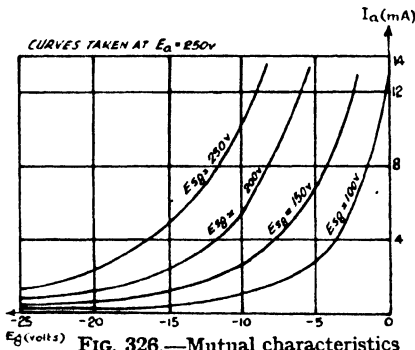


FIG. 326.—Mutual characteristics (for various E_g) of variable- μ pentode (CV 1053).

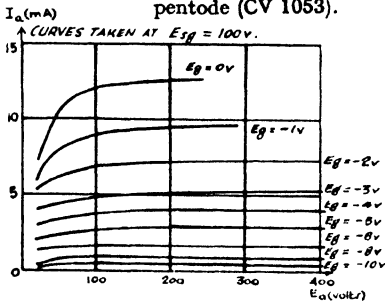


FIG. 328.—Anode characteristics (for various E_g) of variable- μ pentode (CV 1053).

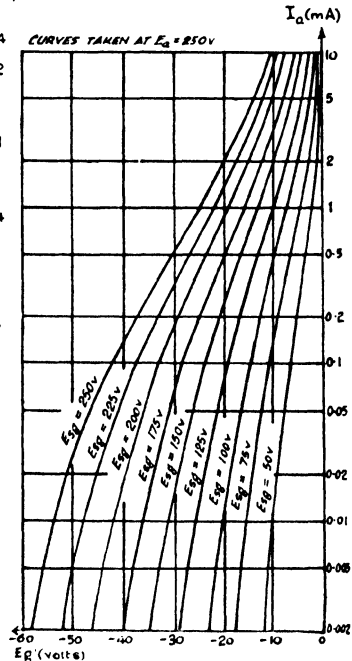


FIG. 327.—Mutual characteristics (for various E_g) to log scale.

Fig. 326 shows a set of mutual characteristics of a typical variable- μ pentode CV 1053 (ARP34) (EF39), plotted for constant anode voltage, but variable screen voltage. As given in valve data sheets, such curves are often plotted with anode current on a logarithmic scale of microamps, in order to include the whole range of anode currents, and at the same time give an accurate picture of the lower part of the characteristic. A set of curves plotted to such a scale is given in Fig. 327 and does, of course, look entirely different from Fig. 326, but is nevertheless equivalent to it. Fig. 328 shows the anode characteristic of the same valve, plotted

for constant screen voltage but variable grid voltage. Fig. 329 shows mutual characteristics, plotted for constant screen and variable anode voltage; and Fig. 330 shows anode characteristics, plotted for constant grid and variable screen voltage.

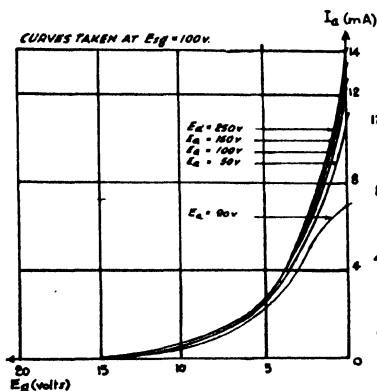


FIG. 329.—Mutual characteristics (for various E_a) of variable-mu pentode (CV 1053).

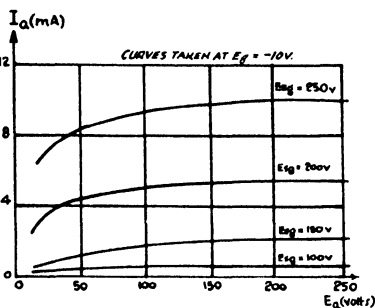


FIG. 330.—Anode characteristics (for various E_{sg}) of variable-mu pentode (CV 1053).

The object of a variable-mu valve is that it enables the stage gain of a voltage amplifier stage to be varied over a wide range by varying the bias voltage on the control grid, and therefore the "g" of the valve.

The pentode as an amplifier

The general principles of amplifier stages using either tetrodes or pentodes are the same, but they differ from those employed for

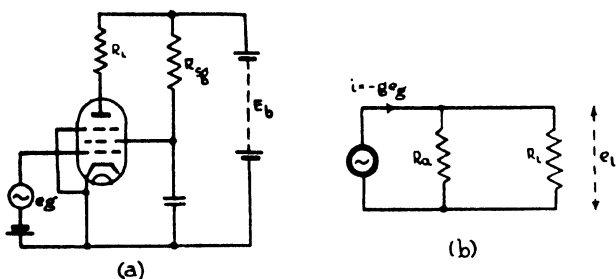


FIG. 331.—Pentode arranged as a voltage amplifier, with constant current generator form of equivalent circuit.

the triode amplifier stage. For the moment all reference to power amplifiers will be omitted, and attention concentrated on voltage amplifier stages.

Fig. 331a shows a pentode arranged as a voltage amplifier, and Fig. 331b shows the constant-current generator form of the

equivalent circuit. When using a triode as a voltage amplifier a load resistance somewhat higher than the AC resistance of the triode is chosen in order to get as high a value of stage gain as is reasonably possible consistent with the available HT supply voltage and the drop across the anode load. With the pentode, the value of R_L is limited by supply voltage considerations to a value that is normally small compared with the AC resistance of the valve. For example, a reasonable value of anode load for a pentode having an AC resistance of $1.5 \text{ M}\Omega$ may be of the order of $100 \text{ k}\Omega$.

For pentodes, the constant-current generator form of equivalent circuit (Fig. 331*b*) is therefore preferable to the constant-voltage generator form.

Clearly the stage gain is given by:—

$$M = \frac{e_L}{e_p} = g \frac{R_a R_L}{R_a + R_L} \quad (\text{see equation 20})$$

i.e.

$$M = g \frac{R_L}{1 + \frac{R_L}{R_a}} \quad (21)$$

If, as is usually the case, R_a is very much larger than R_L , the result for a pentode may be written as:—

$$M = g R_L \quad (22)$$

Now suppose that the pentode of Fig. 331*a* is a CV 1091 (ARP35) (EF50), anode characteristics of which are given in Fig. 332.

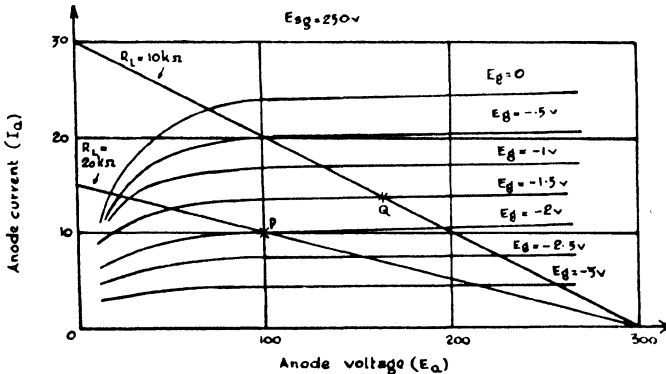


FIG. 332.—Anode characteristics of a pentode (CV 1091)

Suppose that an HT voltage supply of 300 volts is available, and that it is decided to try a load resistance of $10 \text{ k}\Omega$. Using the same method as for a triode (p. 341), one can draw the load line, and choose the operating point Q . From the equal intercepts it can be seen that grid swings up to 1.5 volts may be handled without undue distortion.

The peak value of the alternating component of the anode current corresponding to the 1.5 volt signal will be 9.5 mA, giving

a peak voltage of 95 volts across the anode load. Thus the stage gain (M) would be :—

$$M = \frac{95}{1.5} = 63$$

Using the formula of equation 22, this result can be obtained easily, for from the valve data $g = 6.5$ mA/volt.

i.e.

$$g = 6500 \text{ } \mu\text{mhos}$$

\therefore

$$M = gR_L = 6500 \times 10^{-6} \times 10^4 = 65$$

which is approximately the same result as before.

If an anode load of $20 \text{ k}\Omega$ is chosen, another load line is obtained with the operating point P . This time the intercepts indicate that

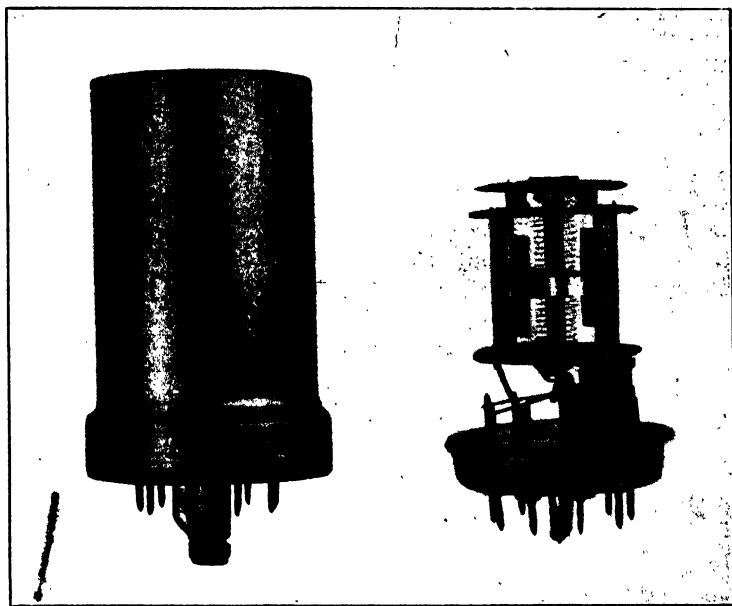


PLATE 21.—CV 1091 (ARP 35) (EF 50) pentode valve.

a peak signal of only 0.5 volts may be applied without undue distortion. The peak value of alternating anode current corresponding to the 0.5 volt peak signal is 3.25 mA, and the peak alternating voltage across the anode load is 65 volts. Thus the stage gain is given by :—

$$M = \frac{65}{0.5} = 130$$

Alternatively, using equation 22, since $g = 6500$ μmhos and $R_L = 20 \text{ k}\Omega$:—

$$M = 6500 \times 10^{-6} \times 20 \times 10^3 = 130$$

which agrees with the figure previously obtained.

The greater the anode load the greater the voltage gain, just as in a triode, but an increase in anode load may give a considerable increase in distortion, unless the signal applied to the grid is very small. This question of distortion will be considered in more detail when considering power amplifiers. For voltage amplifiers, the input signal voltages are usually very small, and the highest possible load is taken consistent with the available HT voltage and the magnitude of the signal to be amplified.

MISCELLANEOUS VALVE TYPES

Frequency-changer valves

If the potential on the suppressor grid of a pentode is varied, there will be a corresponding variation in the anode current. This

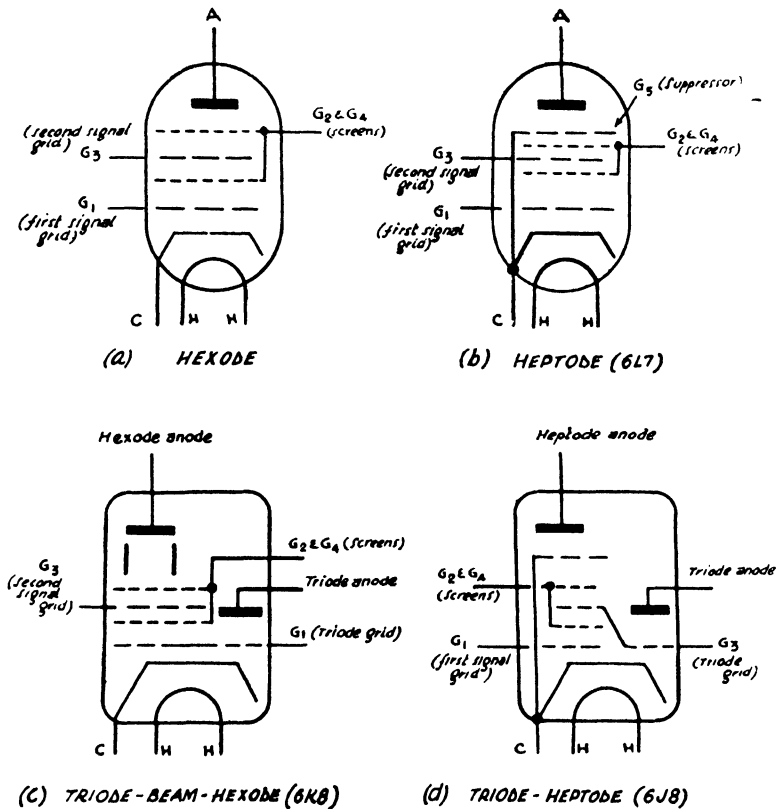


FIG. 333.—Frequency-changer valves.

fact can be used to allow two independent signal voltages simultaneously to control a single anode current, by applying one voltage to the control grid and the other to the suppressor. Owing to the

non-linearity of the valve, intermodulation between the frequencies of the two inputs will take place, as will be seen in Chapter 11. The anode-suppressor capacity of a pentode used in this way has the same ill-effects as the anode-grid capacity of a triode; special "frequency-changer" valves, as they are called, have therefore been developed with electrostatic screening between the anode and the second signal grid.

The hexode

The hexode is a modified pentode valve, having an extra electrostatic screen interposed between the third ("suppressor", or "second signal-") grid and the anode (*see* Fig. 333*a*). This additional screen (G_4) is usually connected internally to the existing screen (G_2), and is maintained at a steady positive potential, so that it functions in exactly the same manner as the screen of a tetrode, and the hexode forms a much more stable frequency-changer than the pentode.

The heptode

Since, in the hexode, a screen at positive potential is adjacent to the anode, trouble may be experienced from secondary-emission effects as in the case of the tetrode (*see* p. 351). This difficulty can be overcome either by employing the principle of the beam tetrode, or by the insertion of a suppressor grid between screen and anode. In the first case, the resulting valve is called a "beam hexode", and in the latter, a "heptode" (*see* Fig. 333*b*, which represents a type 6L7).

Triode hexodes and triode-heptodes

Frequency-changer valves are normally used to intermodulate two signals, one of which is generated by an oscillator coupled directly to one of its two control or signal grids. To reduce the number of valves needed in a piece of equipment, hexodes and heptodes are sometimes built into an envelope that also contains a triode; this triode can be used as an oscillator, and has its grid internally connected to one of the two signal grids of the hexode or heptode. Fig. 333*c* shows a representation of a triode-beam-hexode, such as the type 6K8, in which the triode grid is internally connected to the hexode grid nearest the cathode, while Fig. 333*d* shows a triode-heptode (*e.g.* the 6J8), in which the triode grid is connected to the third grid (G_3).

The co-planar-grid valve

The co-planar-grid valve, exemplified by the 4045A (*see* Fig. 334), is sometimes used in the output stage of multi-channel carrier telephone equipment.

It is virtually a tetrode in which the screen grid and the control grid are intermeshed so that they are co-planar and equidistant from the cathode. In operation, the control grid (*a*) is given a negative bias of 60 volts so that it can handle a very large grid

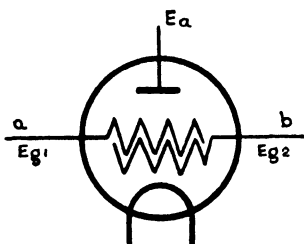


FIG. 334.—Co-planar valve (4045 A).

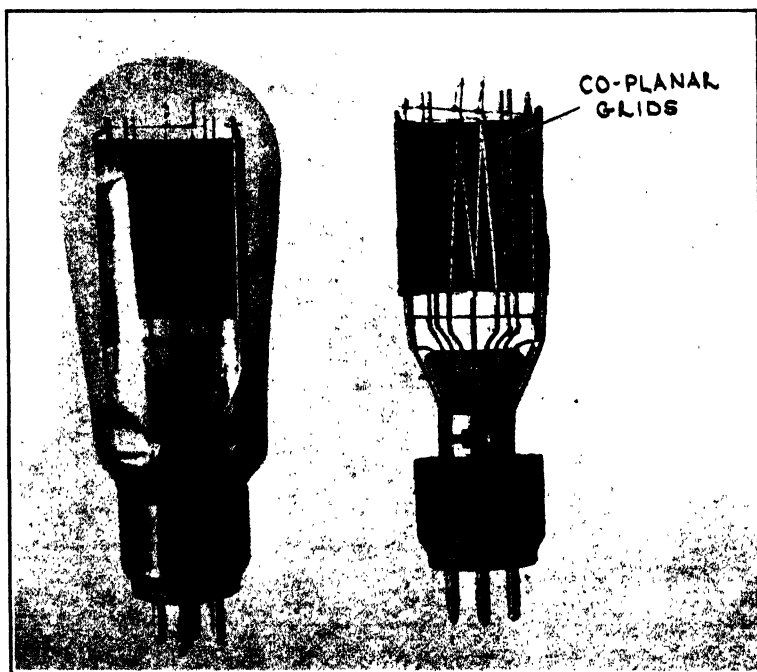


PLATE 22.—4045A Co-planar grid valve

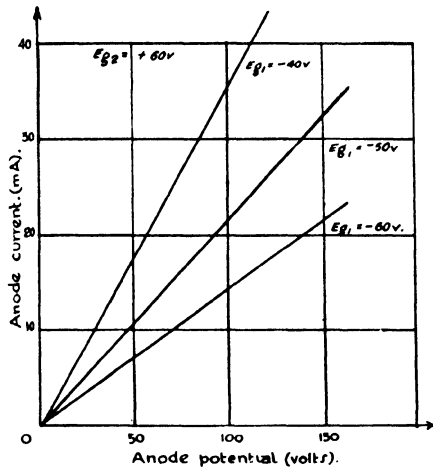


FIG. 335.—Anode characteristics of the Co-planar valve (4045 A).

swing without becoming positive; the co-planar-grid (*b*) is given a positive bias of about 60 volts. As far as anode current is concerned, the valve behaves as a triode in which the grid potential is zero—that is, the anode current is large. Fig. 335 shows anode characteristics for this valve.

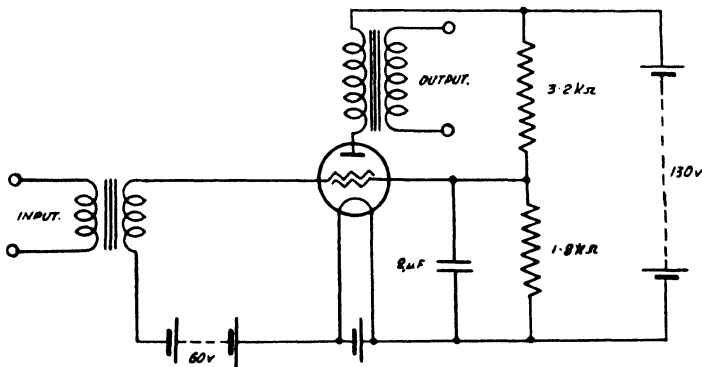


FIG. 336.—Co-planar valve employing grid bias battery

METHODS OF BIASING

Bias

It has been seen that a steady negative bias must be applied to the grid of a valve used as an amplifier, in addition to the signal voltage. The various ways in which this can be done will be considered in the ensuing paragraphs. It will be noted that, in every case, a DC path exists between grid and cathode; this is

most important, for as has been seen (page 348), if an open-circuit or even a high resistance path exists between grid and cathode, damage may result.

Battery bias

So far it has been assumed that the grid bias voltage is obtained from a battery in the grid circuit. This is known as "battery bias", and is only one of the various methods by which a steady potential difference may be maintained between cathode and grid. The method is seldom used nowadays, about the only example in line equipment being the -60 volts grid bias for the co-planar valve (see Fig. 336).

Filament current bias

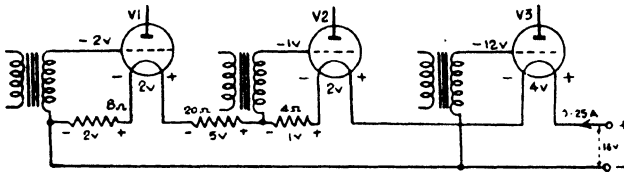


FIG. 337.—Method of obtaining filament current bias.

This is a convenient method for obtaining bias with directly-heated valves, particularly when a number of valves are operated with their filaments in series, an example being shown in Fig. 337.

The three valve filaments are in series with various resistances, and the whole filament circuit draws 0.25 amps filament current. Valves V1 and V2 take 0.25 amps at 2 volts, and V3 takes 0.25 amps at 4 volts. The voltage drops across the various filaments and resistances are shown in the diagram. It is easily seen that the potentials of the various grids relative to the negative ends of the respective filaments are as shown in the diagram, and that these are maintained by the flow of filament current.

Bias from HT supply

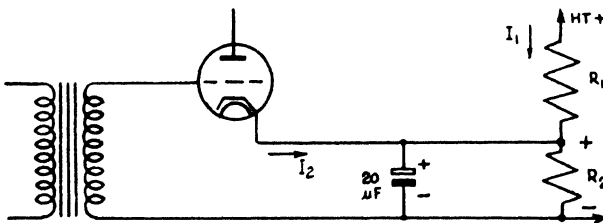


FIG. 338.—Method of obtaining bias from HT supply.

If a large grid bias voltage is required, the cathode of an indirectly-heated valve may be made positive with respect to the grid by employing a potentiometer across the HT supply, as shown in Fig. 338. When determining the values of R_1 and R_2 , it should

be remembered that R_2 carries not only the potentiometer current I_1 but also the cathode current I_2 of the valve. The bias applied is therefore $(I_1 + I_2) R_2$.

The disadvantage of this method is that the resultant HT voltage available to be applied between anode and cathode of the valve has been reduced by the amount of grid bias voltage applied.

Cathode bias

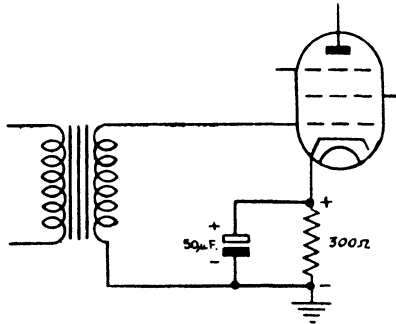


FIG. 339.—Method of obtaining cathode current bias.

Fig. 339 shows the method of producing bias that is most often used with indirectly-heated valves. A resistance—in this case 300Ω —is inserted in the cathode lead of the valve; this resistor has to carry the whole of the standing cathode current, *i.e.* the sum of the steady anode and screen currents. Across this resistor there will be developed a steady voltage in the sense shown; this will

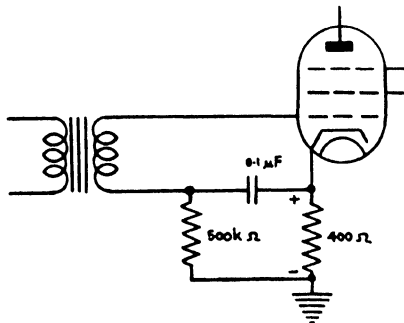


FIG. 340.—Another method of decoupling the cathode resistor.

make the grid negative with respect to cathode, the amount of bias depending on the value of cathode resistance and on the cathode current. The large capacity condenser shunting this resistor is provided for decoupling—that is, providing an alternative low impedance path for the oscillatory currents. If the condenser were

not connected, the variations in anode current would cause variations in the potential across the cathode resistor; these would be fed on to the grid and would be of such a phase as to oppose the applied signal. The omission of the cathode decoupling condenser is a convenient way of obtaining "current negative feedback", and is fully discussed in Chapter 9. If bias only is required, the cathode resistor must be decoupled, otherwise both bias and current negative feedback are obtained.

Another example of the provision of cathode bias without current negative feedback is shown in Fig. 340.

The only essential difference between this circuit and the last is in the method of decoupling. A large resistance is included in the grid circuit, and this enables the cathode resistor to be efficiently decoupled using quite a small decoupling condenser. At 1600 c/s, the reactance of the 0.1 μF condenser is in the region of 1000Ω . Thus the voltage developed across this condenser and applied between cathode and grid will be only $\frac{1000}{\sqrt{500,000^2 + 1000^2}} \approx \frac{1}{500}$ th of the alternating voltage developed across the cathode resistor.

Grid leak bias

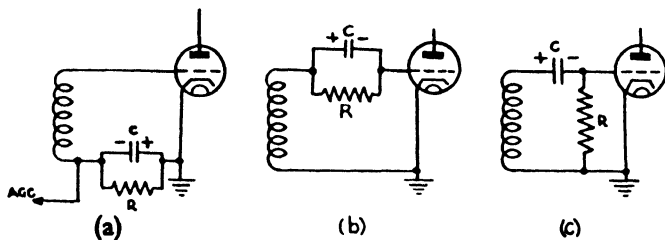


FIG. 341.—Grid leak bias.

This form of biasing, which depends on the flow of grid current for the production of the bias voltage, is frequently employed in oscillatory circuits. Fig. 341 shows three circuits for producing this type of bias; all three are in common use and the action is the same in each case. Consider Fig. 341a; when a signal is applied to the input, the grid will become positive with respect to the cathode on every positive half-cycle. Grid current will flow, developing a voltage across the resistor R and charging up the condenser C in such a direction as to bias the grid negatively. During the negative half-cycles, no grid current will flow, and the condenser C will start to discharge through the resistor R . If the time constant of C and R is large compared with the periodic time of the input signal, the condenser will retain its charge from one positive half-cycle to the next, and a steady negative bias will be produced. Equilibrium will be set up with the valve running into grid current on the peaks of the positive half-cycles (see Fig. 342), the grid current flowing being just sufficient to maintain the charge on the condenser.

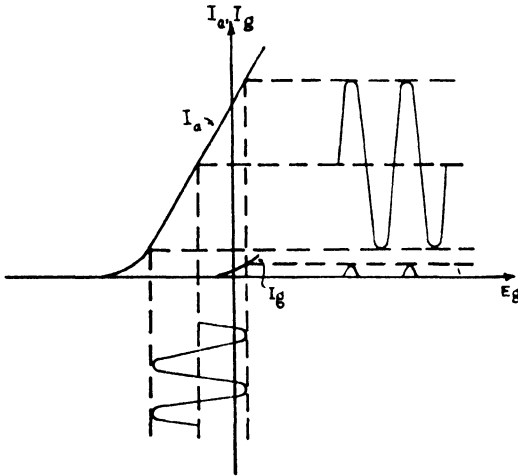


FIG. 342.—Explaining operation of grid leak bias.

This circuit is equivalent to that shown in Fig. 343a ; for the valve will pass current from grid to cathode, but not in the reverse direction, and it can thus be regarded as a rectifier. This is a half-wave rectifier circuit, and it produces a DC voltage across C as shown in Fig. 343b. If the ripple in the output is to be small, it follows that the time constant CR must be greater than the period of one cycle. If CR is large, the voltage across C is almost constant ; and as has been seen, this voltage constitutes the bias on the grid of the valve.

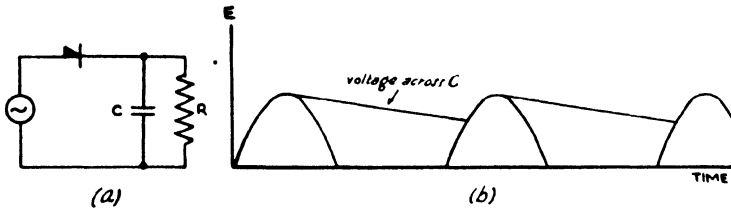


FIG. 343.—(a) Equivalent circuit for grid leak bias, and (b) Voltage across grid condenser.

If the amplitude of the signal on the grid increases, the bias will also increase to the new peak value ; and if the signal decreases, the bias will decrease, though the rate at which the bias follows the signal will depend on the time constant CR . If this method of biasing is used with a variable- μ valve, a type of Automatic Gain Control (AGC) results, for the larger the input, the larger the bias, and the smaller the amplification factor of the valve and the stage gain. In this way the amplitude of the output can be kept more

or less constant. In the arrangement of Fig. 341a the voltage developed across C and R can be applied as AGC bias to other stages.

DECOUPLING

The circuits of Fig. 344 and Fig. 345 have already been discussed, but they are now repeated for emphasis. As regards Fig. 344 it was stated (p. 353) that fluctuations in screen current would cause the potential of the screen to vary with respect to cathode, and would eventually feed back into the grid circuit unless a condenser C is

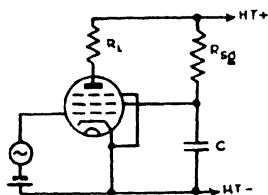


FIG. 344.—Decoupling of screen circuit in a pentode or tetrode.

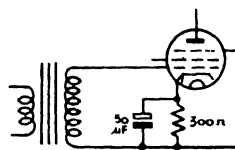


FIG. 345.—Decoupling of cathode resistor.

inserted between cathode and screen to provide a low impedance path for the alternating screen current and prevent it flowing through R_{sg} . The condenser C is said to *decouple* R_{sg} . In Fig. 345 the cathode resistor is common to both grid and anode circuits, and it was noted that if the alternating component of the anode current were allowed to flow in it, the resulting alternating voltage would be fed into the grid circuit. It was also noted that if the cathode resistor were shunted by means of a large capacity condenser, the alternating component of the anode current would have an alternative low impedance path, and very little alternating voltage would be applied to the grid circuit. The $50 \mu\text{F}$ condenser is said to *decouple* the cathode resistor.

Decoupling, then, is effected by providing an alternative low impedance path for the alternating components in order to prevent alternating voltages being developed across an impedance. An impedance that is common to two or more circuits will always introduce interaction between those circuits, unless it is decoupled.

Grid circuit of directly heated valve

Fig. 346a shows the circuit of an amplifier employing filament current bias. This filament current bias is derived from the 4-volt potential drop across the 16Ω resistor in the filament circuit. This particular filament circuit is connected across the LT supply in parallel with a vibrator, which produces disturbing voltages across the LT supply.

In a directly-heated valve the potential of the cathode varies along its length, so that if the length of the filament is divided into

a large number of short elements, each of which may be regarded as equipotential throughout its length, then the potential of the anode relative to the "cathode" will be greater for an element near the negative end of the filament than for one near the positive end. Similarly the grid will be more negative with respect to the positive end of the filament. The result of these two factors is that the various elements of the filament contribute unequally to the anode current (see Fig. 347), $E_a + \frac{E_g}{\mu}$ being greater for elements near the negative end of the filament. The total anode current may be regarded as a function of $E_g' + \frac{E_a'}{\mu}$, where E_g' and E_a' are the grid and anode potentials respectively relative to a point, called the "mean emission point", which is off-set towards the negative end of the filament. The position of the mean emission point varies for different valves, but is generally about one-third of the way along the filament from the negative end.

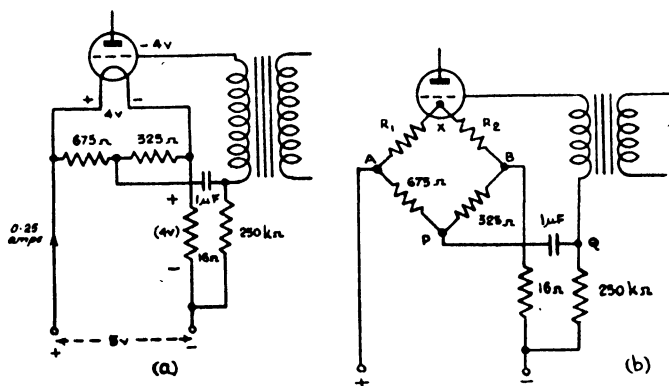


FIG. 346.—(a) Decoupling of filament circuit in the case of a directly-heated valve.
 (b) Equivalent circuit showing the mean emission point.

Returning now to Fig. 346b. The point X is the mean emission point of the filament. All emission will be assumed to take place at this point. The resistors AX and XB represent the resistance of the filament on either side of this mean emission point, and the two resistors AP and PB are chosen so that APBX is a balanced Wheatstone bridge,

$$i.e. \frac{AX}{XB} = \frac{AP}{PB}$$

$$i.e. \frac{R_1}{R_2} = \frac{675}{325}$$

Thus if the vibrator circuit applies an alternating voltage across AB, the point P will be at the same potential as the mean

emission point X . The $1\ \mu\text{F}$ condenser connecting P and Q provides a low impedance path at the vibrator frequency and ensures that there is no alternating potential difference between Q and P , and therefore none between Q and X . Thus as far as the disturbing alternating voltages set up by the vibrator are concerned, the

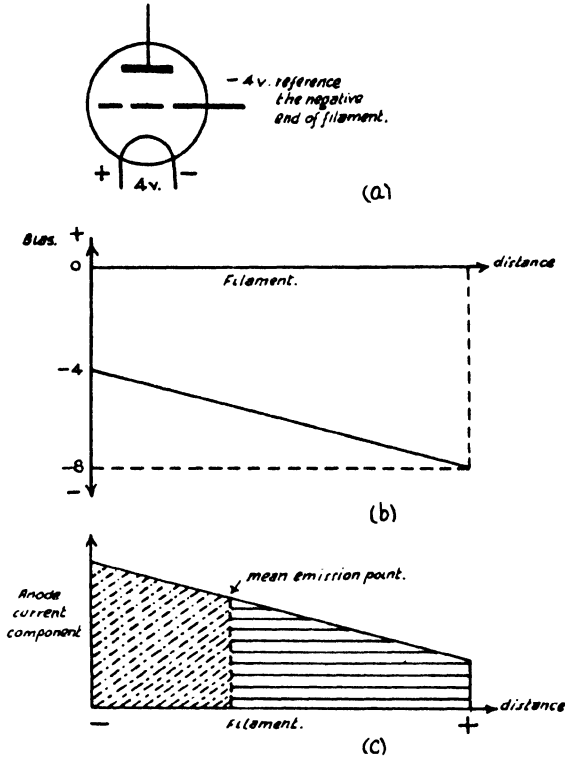


FIG. 347.—Illustrating mean emission point of directly-heated filament.

grid is at the same potential as the mean emission point of the filament; the space charge and hence the anode current will therefore be independent of these disturbing voltages. The grid circuit in this case is said to be decoupled to the mean emission point of the filament.

Anode circuit decoupling

Fig. 348 shows the arrangement of an amplifier stage that is one of several sharing the same HT supply. In this case the internal resistance of the battery (or other form of supply) is an impedance common to two or more anode circuits (and also screen circuits, if pentodes are used); to prevent coupling between stages, it is necessary that the resistance of the battery be decoupled to prevent alternating components of the various anode currents flowing through it. A resistance R is placed in each anode circuit, and the

condenser C provides an alternative path whose impedance is low compared with R . In addition, since the HT supply to this stage is fed *via* the potentiometer formed by R and C , alternating components from other circuits connected to the same power supply will be reduced to negligible amplitudes, provided that R is large compared with the reactance of C at the frequencies concerned.

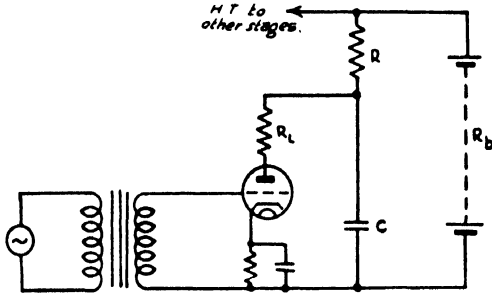


FIG. 348.—Decoupling of an HT supply common to several stages.

The values of C and R used may vary with the degree of decoupling required, which will depend on the number of stages sharing the common supply, and the relative importance of each stage as a disturbing influence on the others. Typical values are 5000Ω and $2\ \mu\text{F}$ for audio frequencies; at carrier frequencies a smaller capacity condenser may provide a sufficiently low impedance alternative path, and 5000Ω and $0.5\ \mu\text{F}$ are typical values. The degree of decoupling is increased by increasing both R and C —e.g. $20\text{k}\Omega$ and $4\ \mu\text{F}$ may be used in an audio frequency amplifier where decoupling is particularly important.

CHAPTER 8

VALVE AMPLIFIERS

Valve amplifiers may be divided into "voltage amplifiers" and "power amplifiers"—*i.e.* those which are designed to deliver a large *voltage* (but no current), as when feeding the grid of a subsequent stage; and those which are designed to deliver actual *power*, as in the case of an output stage feeding a loudspeaker. Those within either of these classes can be sub-divided into "wide-band amplifiers" and "narrow-band amplifiers".

Wide-band amplifiers are designed to give more or less uniform amplification over a wide frequency range, which may be from very low frequencies (of the order of 100 c/s), up to a maximum that may be anywhere from 3 kc/s to several Mc/s for line equipment amplifiers. For convenience in treatment, wide-band amplifiers may be further subdivided according to the type of coupling, of which resistance-capacity coupling is the most important.

Narrow-band amplifiers are designed to give amplification over a narrow band of frequencies, *e.g.* from 480 to 520 c/s, or from 460 to 470 kc/s—the word "narrow" meaning, in this connection, that the difference between the highest and lowest frequencies amplified is small compared with the mid-band frequency.

RESISTANCE-CAPACITY COUPLED VOLTAGE AMPLIFIERS

Fig. 349*a* shows a simple resistance-capacity coupled stage; when a signal is applied to the grid of V_1 , alternating voltages are

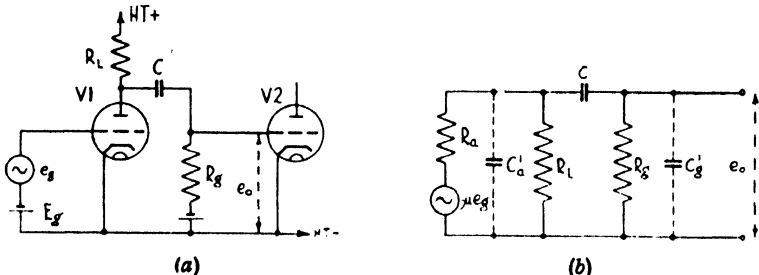


FIG. 349.—Resistance-capacity coupled stage with equivalent circuit.

developed across the load resistance R_L , which is effectively between anode and cathode of V_1 . Anode and cathode are connected by the circuit consisting of C and R_t in series, and the voltage across R_t is applied between grid and cathode of V_2 .

Equivalent circuit in constant-voltage generator form

The equivalent circuit in the constant-voltage generator form is shown in Fig. 349*b*, and it will be noted that two capacities C_a' and C_g' have been included which do not appear in the original circuit diagram. C_a' is the output capacity of V_1 , made up of anode-cathode capacity plus any stray wiring capacity to the left of the coupling condenser C , and C_g' is the input capacity of V_2 plus stray capacities to the right of the coupling condenser.

From the equivalent circuit it is clear that, since the network contains capacity, the voltage e_o applied to the second stage will vary with frequency, and therefore the stage gain $\frac{e_o}{e_g}$ will also vary with frequency. A complete analysis of the behaviour of this network is difficult, but the analysis can be simplified by dividing the range of frequencies into three parts.

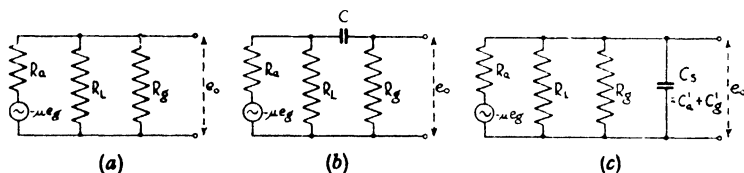


FIG. 350.—Equivalent circuits of R-C coupled stage for medium, low and high frequencies.

Over a certain intermediate range of frequencies the small capacities C_a' and C_g' will have a high reactance and will not appreciably shunt the resistors R_L and R_g respectively. Also, the series condenser C will have only a small reactance, which can be neglected in comparison with R_g . The resulting equivalent circuit of Fig. 350*a* is therefore substantially correct for medium frequencies; since this is a purely resistive circuit, the stage gain will be independent of frequency over the range where the simplification is valid, and this range clearly depends on the values of R_L , R_g , C , C_a' and C_g' .

At lower frequencies, where this simplification is not admissible, the reactance of C_a' will still be negligible as a shunt on R_L , and C_g' negligible compared with R_g , but the reactance of C may be quite large and will increase with decrease in frequency. The equivalent circuit for low frequencies is shown in Fig. 350*b*. Since the reactance of C increases with decrease in frequency, and C and R_g form a voltage divider across R_L , e_o and hence the stage gain will decrease as the frequency decreases.

At high frequencies, the reactance of C will be negligible compared with R_g , but the capacities C_a' and C_g' will together form an appreciable shunt on R_L and R_g ; this shunting capacity is denoted by C_s in Fig. 350*c*, which is the simplified equivalent circuit applicable for high frequencies. The shunting effect of C_s across the load becomes more marked, and causes a reduction in the stage gain at higher frequencies.

Variation of gain with frequency

Fig. 351 shows the way in which stage gain varies with frequency in a typical R-C coupled stage. The three ranges of frequency are clearly seen here, although the boundaries are of course not sharply

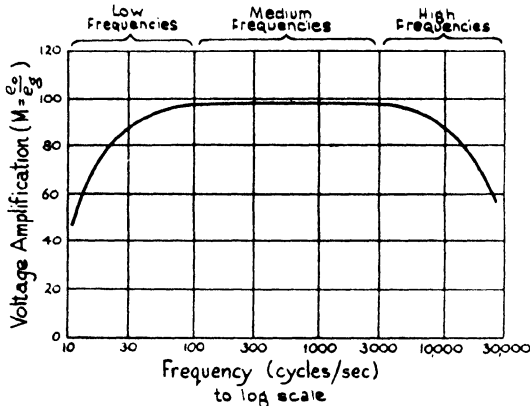


FIG. 351.—Gain/frequency response of a typical R-C coupled stage.

defined. In particular, the medium frequency range, over which the stage gain is substantially constant, is seen to be from about 100 c/s to 3000 c/s.

From Fig. 350*a*, the stage gain at medium frequencies is seen to be:—

$$M = \mu \cdot \frac{R_L'}{R_s + R_L'} \quad (1)$$

$$\text{where } R_L' = \frac{R_L R_p}{R_L + R_p} \quad (2)$$

Thus M is always less than μ , but may be increased, subject to this limitation, by an increase of R_L' , and equation 2 shows that, for a high value of R_L' , both R_L and R_p must be large.

Suppose, then, that an effort be made to secure a high stage gain by selecting very large values for R_L and R_p . At high frequencies the shunting effect of C_s (see Fig. 350*c*) will become appreciable at much lower frequencies than before; that is to say, the stage gain will begin to fall off at much lower frequencies. Thus although the stage gain at middle frequencies has been increased, this increase is obtained at the expense of a reduction in the frequency range over which the response is flat. The design of an R-C coupled amplifier is therefore a compromise between the stage gain at middle frequencies, and the frequency range over which the response is flat; one can be increased only at the expense of the other.

R-C stage using pentode valves

Fig. 352*a* shows a simple R-C coupled stage using pentodes,

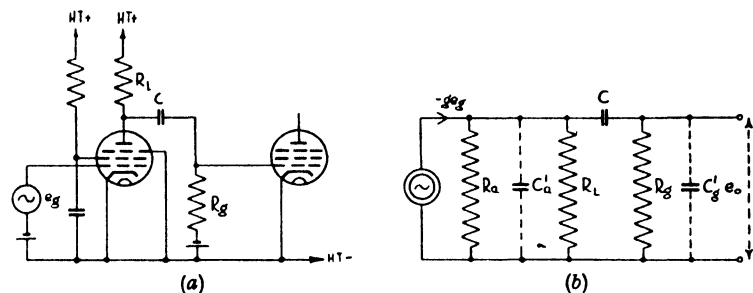


FIG. 352.—Resistance-capacity coupled amplifier employing pentode valves.

and Fig. 352*b* the corresponding equivalent circuit in the constant-current generator form. Figs. 353*a*, *b* and *c* show the simplified equivalent circuits for medium, low and high frequencies respectively.

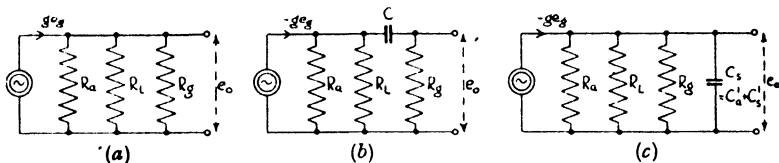


FIG. 353.—Equivalent circuits of Fig. 352*a* for medium, low and high frequencies.

In the case of medium frequencies (Fig. 353*a*) :—

$$M = g \cdot R_{eq} \tag{3}$$

where

$$R_{eq} = \frac{1}{\frac{1}{R_a} + \frac{1}{R_L} + \frac{1}{R_g}}$$

For a pentode, R_a is large compared with R_L and R_g in parallel, so that only a small error is introduced by neglecting $\frac{1}{R_a}$ compared with $\left(\frac{1}{R_L} + \frac{1}{R_g}\right)$

$$\therefore R_{eq} \approx \frac{R_L R_g}{R_L + R_g} \tag{4}$$

If, as is frequently the case, R_g is much larger than R_L (e.g., $R_L = 30 \text{ k}\Omega$, $R_g = 0.5 \text{ M}\Omega$) this can be simplified still further, giving :—

$$R_{eq} \approx R_L$$

Thus for a pentode, with the proviso that $R_L \ll R_g$:—

$$M = g \cdot R_L \tag{5}$$

It will be clear from Fig. 353 *b* and *c* that the stage gain decreases

at low and at high frequencies, and that the general shape of the gain-frequency response is the same for a pentode as for a triode (Fig. 351).

Stage gain of R-C stage at low and high frequencies

A rather more detailed examination will now be made of the stage gain of an R-C coupled stage at low and high frequencies.

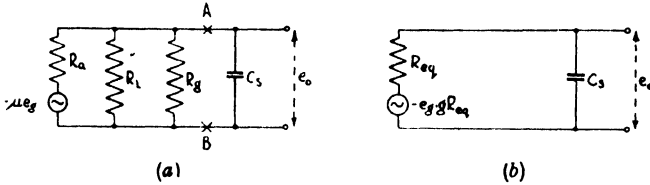


FIG. 354.—Equivalent circuits of an R-C coupled stage at high frequencies.

Fig. 354a shows the equivalent circuit for high frequencies. By Thévenin's theorem, that part of the circuit to the left of AB can be replaced by a simple generator. The impedance of this generator is the impedance looking into AB to the left, i.e., R_{π} and the EMF of the generator will be the open circuit voltage at AB, i.e., the voltage output of the stage over the medium frequency range, i.e., $-e_g \cdot g \cdot R_{\pi}$ (using equation 3). Thus Fig. 354b is another form of the equivalent circuit. From this circuit :—

$$e_o = -e_g \cdot g \cdot R_{\pi} \cdot \frac{\frac{-j}{\omega C_s}}{R_{\pi} - \frac{j}{\omega C_s}}$$

i.e.

$$\frac{e_o}{e_g} = -g \cdot R_{\pi} \cdot \frac{1}{j\omega C_s R_{\pi} + 1} \tag{6}$$

Taking the modulus of both sides :—

$$\left| \frac{e_o}{e_g} \right| = \frac{-gR_{\pi}}{\sqrt{1 + \omega^2 C_s^2 R_{\pi}^2}}$$

∴ from equation 3 :—

$$\text{Stage gain at high frequencies} = \frac{\text{Stage gain at medium frequencies}}{\sqrt{1 + \omega^2 \cdot C_s^2 \cdot R_{\pi}^2}}$$

As the denominator increases with frequency, this shows that the amplification at high frequencies decreases with increase in frequency.

Equation 6 also indicates that the amplification $\left(\frac{e_o}{e_g}\right)$ is a vector quantity ; that is, signals suffer a phase change in passing through the stage. This phase-shift ϕ is given by :—

$$\phi = 180^\circ - \tan^{-1} \omega C_s R_{\pi} \tag{7}$$

From this equation, ϕ appears to be a multi-valued function ;

the correct result to take is that for which $\tan^{-1} \omega C_s R_{eq}$ lies between 0° and 90° ; because, as ω decreases, so φ approaches 180° , which is the value of the phase-shift in the stage for medium frequencies.

It is customary to disregard this 180° , and to say that over the medium frequency range there is no phase-shift, and that for high frequencies there is an advance φ' in phase relative to medium frequencies, given by:—

$$\varphi' = -\tan^{-1} \omega C_s R_{eq} \tag{8}$$

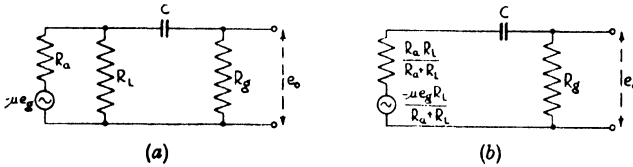


FIG. 355.—Equivalent circuits of an R-C coupled stage at low frequencies.

Similarly, Thévenin's theorem can be applied to the low-frequency equivalent circuit of Fig. 355a, the result being the circuit b.

From this it follows that:—

$$e_o = \frac{-\mu e_g R_L}{R_a + R_L} \cdot \frac{R_g}{\frac{R_a R_L}{R_a + R_L} + R_g - \frac{j}{\omega C}}$$

Hence
$$\frac{e_o}{e_g} = -\frac{\mu R_L R_g}{(R_a + R_L) \left(R - \frac{j}{\omega C} \right)}$$

where
$$R = \frac{R_a R_L}{R_a + R_L} + R_g$$

This may be re-arranged thus:—

$$\frac{e_o}{e_g} = \frac{-\mu \cdot R_L \cdot R_g}{(R_a + R_L)} \cdot \frac{1}{\left(R - \frac{j}{\omega C} \right)}$$

i.e.
$$\frac{e_o}{e_g} = \frac{-\mu \cdot R_L \cdot R_g}{R_a R_L + R_a R_g + R_L R_g} \cdot \frac{1}{\left(1 - \frac{j}{\omega C R} \right)}$$

$$= \frac{-g \cdot R_{eq}}{1 - \frac{j}{\omega C R}} \tag{9}$$

Taking the modulus of both sides:—

$$\left| \frac{e_o}{e_g} \right| = \frac{-g R_{eq}}{\sqrt{1 + \left(\frac{1}{\omega C R} \right)^2}}$$

∴ from equation 3:—

$$\text{Stage gain at low frequencies} = \frac{\text{Stage gain at medium frequencies}}{\sqrt{1 + \left(\frac{1}{\omega CR}\right)^2}} \quad (10)$$

Since $\frac{1}{\omega C}$ increases with decrease in frequency, this shows that the stage gain at low frequencies decreases with decrease in frequency.

Also, from equation 9, the phase-shift at low frequencies is $\tan^{-1}\left(\frac{1}{\omega CR}\right)$ relative to the phase-shift at medium frequencies.

With the convention of zero phase-shift at medium frequencies, the phase-shift at low frequencies is therefore:—

$$\varphi' = \tan^{-1}\left(\frac{1}{\omega CR}\right) \quad (11)$$

Thus equation 11 indicates that at low frequencies there is a positive phase-shift (relative to the phase at medium frequencies), and this phase-shift increases as the frequency decreases; and equation 8 indicates that there is a negative phase-shift at high frequencies, which increases with increased frequency.

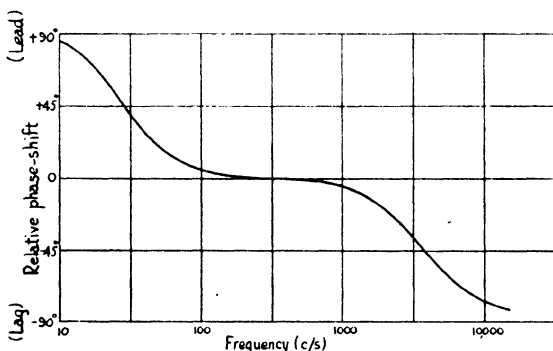


FIG. 356.—Phase/frequency characteristic of a typical R-C coupled stage.

For a single R-C coupled stage, the phase-shift will never exceed 90° either way at any frequency. A graph showing a typical phase-frequency characteristic (the phase-shift being measured relative to middle frequencies) is shown in Fig. 356.

Universal response curves for R-C coupled amplifiers

It is often convenient to have a response curve that may be applied to all R-C coupled amplifiers. Considering first the low frequencies: Let f_0 be the frequency at which the reactance

$X_c \left(= \frac{1}{\omega C} \right)$ of the coupling condenser is numerically equal to the resistance $R = \frac{R_s R_L}{R_s + R_L} + R_r$. This frequency comes within the range of low frequencies.

Then, from equation 10, the stage gain at f_c will be 0.707 times the stage gain at medium frequencies; and from equation 11, the phase shift at f_c will be $+45^\circ$ relative to the phase-shift at medium frequencies. In the same way the stage gain and phase-shift may be found for any other low frequency expressed as a multiple of f_c . Table XIV is prepared in this way.

TABLE XIV
Gain of R-C amplifier at low frequencies

Frequency	Relative amplification (voltage ratio)	Relative amplification in decibels $= 20 \cdot \log_{10}$ (voltage ratio)	Relative phase-shift
0.1 f_c	0.100	-20.0	84° 18'
0.2 f_c	0.196	-14.2	78° 42'
0.5 f_c	0.447	-7.0	63° 26'
f_c	0.707	-3.0	45°
2 f_c	0.895	-0.97	26° 34'
5 f_c	0.980	-0.17	11° 18'

Now considering the high frequencies, let f'_c be the frequency at which the reactance of the total shunting capacity C_s is numerically equal to the resistance $R_{st} = \frac{1}{\frac{1}{R_s} + \frac{1}{R_L} + \frac{1}{R_r}}$

TABLE XV
Gain of R-C amplifier at high frequencies

Frequency	Relative amplification (voltage ratio)	Relative amplification in decibels $= 20 \cdot \log_{10}$ (voltage ratio)	Relative phase-shift
0.2 f'_c	0.980	-0.17	-11° 18'
0.5 f'_c	0.895	-0.97	-26° 34'
f'_c	0.707	-3.0	-45°
2 f'_c	0.447	-7.0	-63° 26'
5 f'_c	0.196	-14.2	-78° 42'
10 f'_c	0.100	-20.0	-84° 18'

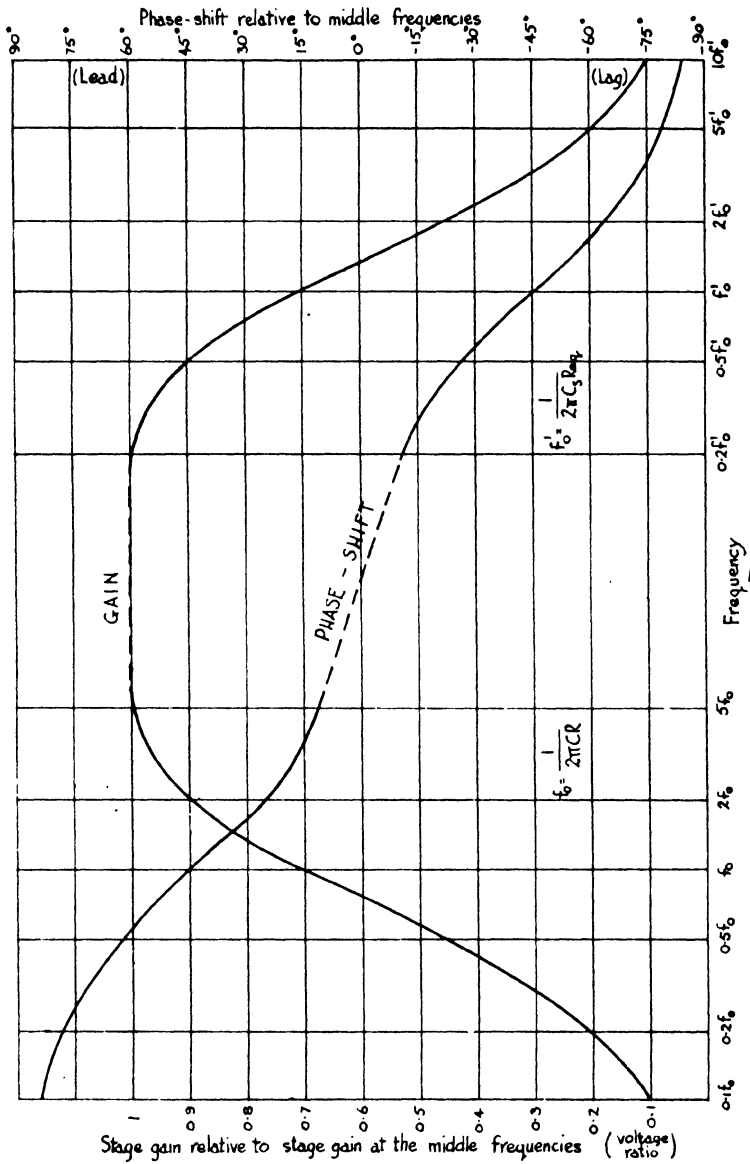


FIG. 357.—Universal response curves for a resistance-capacity coupled amplifier.

Then, from equation 7, the stage gain at f_o' is 0.707 times the stage gain at medium frequencies, and from equation 8, the phase shift at f_o' is -45° relative to that at medium frequencies. Table XV is compiled for other high frequencies expressed in terms of f_o' .

Fig. 357 shows a universal response curve for a resistance-capacity amplifier. The procedure for obtaining the response curves for a particular amplifier is as follows:—

(i) Calculate the stage gain at middle frequencies, using equations 1 or 3.

(ii) Calculate the frequency f_o from the relationship

$$f_o = \frac{1}{2\pi CR}$$

and read off the gain and phase shift at low frequencies from the curves of Fig. 357.

(iii) Estimate the total shunting capacity C_s and calculate the frequency f_o' from the relationship

$$f_o' = \frac{1}{2\pi C_s R_{eq}}$$

then read off the gain and phase-shift at high frequencies from the curves of Fig. 357.

Example.—

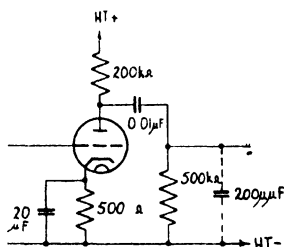


FIG. 358.—R-C coupled stage to illustrate use of universal response curve.

Consider a circuit (*see* Fig. 358) having the following constants:—

$$\begin{array}{ll} \mu = 100 & R_s = 100,000\Omega \\ R_L = 200,000\Omega & R_p = 500,000\Omega \\ C_s = 200 \mu\mu F & C = 0.01\mu F \end{array}$$

Find the mid-frequency gain, and those frequencies at the top and bottom of the range at which the gain has dropped by 6 db.

Step 1.—Mid-frequency gain

$$R_L' = \frac{R_L R_s}{R_L + R_s} = 143,000\Omega$$

$$\text{Gain} = \frac{\mu R_L'}{R_L' + R_s} = 100 \cdot \frac{143,000}{243,000} = 58.8$$

Step 2.—Low-frequency gain

$$f_o = \frac{1}{2\pi C R}, \text{ where } R = \frac{R_L \cdot R_s}{R_L + R_s} + R_s = 567,000 \Omega$$

$$\therefore f_o = \frac{10^8}{2\pi \cdot 567,000} = 27 \text{ c/s}$$

But f_o is the frequency at which the gain is 0.707 times its mid-frequency value. The frequency required is that at which the gain has dropped by 6 db; *i.e.*, the voltage gain has dropped to half its mid-frequency value. This can be found from Fig. 357, and is equal to about $0.6 f_o$, *i.e.* about 16 c/s.

Step 3.—High-frequency gain

$$f_o' = \frac{1}{2\pi C_s R_{eq}}, \text{ where } R_{eq} = (R_s, R_L, \text{ and } R_g \text{ in parallel})$$

$$R_L' = (R_L \text{ and } R_g \text{ in parallel}) = 143,000 \Omega$$

$$\therefore R_{eq} = \frac{143,000 \cdot 100,000}{243,000} = 58,800 \Omega$$

$$\therefore f_o' = \frac{10^{12}}{2\pi \cdot 200 \cdot 58,800} = 13,500 \text{ c/s}$$

From Fig. 357, the frequency at which the gain is half the mid-frequency gain is about $1.7 f_o'$, *i.e.* about 23,000 c/s.

Load line for R-C coupled amplifiers

It has been seen that the load line for a valve with a resistance R_L in the anode circuit passes through the HT supply voltage point

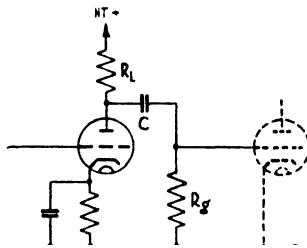


FIG. 359.—Illustrating AC shunting of load resistance R_L by R_g .

on the horizontal axis. In the circuit of Fig. 359, this is true only as far as direct currents are concerned; the DC load line will pass through E_b , and will have a slope $\frac{1}{R_L}$, and the operating point of the valve will lie on this line.

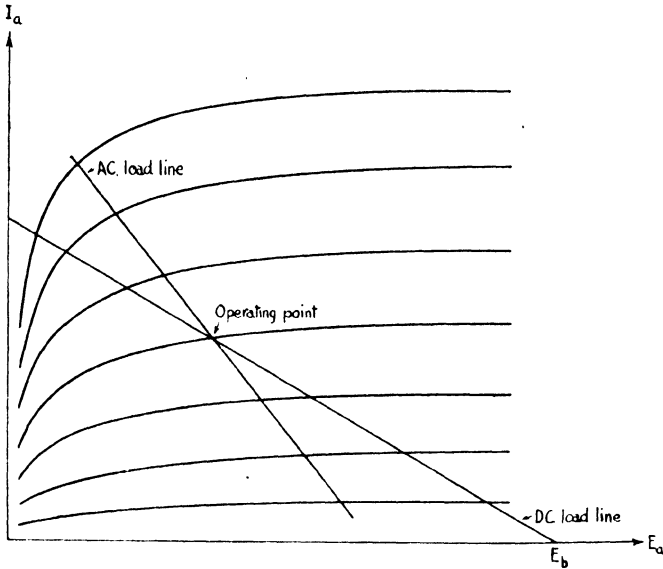


FIG. 360.—DC and AC load lines.

For rapid variations of anode voltage, however, C has a low impedance (in the working frequency range), and the equivalent load on the valve, R_L' , is equal to $(R_L$ and R_g in parallel), *i.e.* $\frac{R_L \cdot R_g}{R_L + R_g}$. So far as AC variations are concerned, therefore, the load line has a slope of $\frac{R_L + R_g}{R_L \cdot R_g}$, and passes through the operating point. This will not be identical with the DC load line (whose slope is $\frac{1}{R_L}$) unless $R_g \gg R_L$. The two load lines are shown in Fig. 360.

CHOKE AND TRANSFORMER-COUPLED VOLTAGE AMPLIFIERS

Choke-capacity coupling

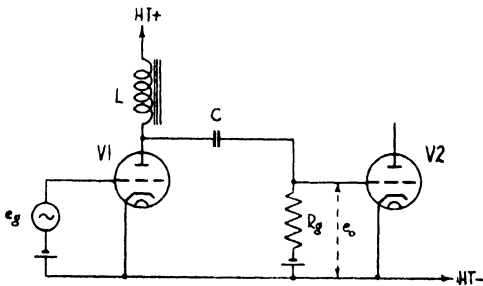


FIG. 361.—A simple choke-capacity coupled stage.

Fig. 361 shows the simple circuit of a choke-capacity coupled amplifier stage. A comparison with Fig. 349a shows that this differs from resistance-capacity coupling only in that the anode load resistor R_L is replaced by an iron-cored inductance L . This has the advantage that, although it offers a high impedance to the alternating components of the anode current, it can be made to have a low DC resistance. The DC voltage drop across it will be small, and under static conditions practically the whole available HT voltage will be applied to the anode, thus enabling lower voltage HT supplies to be used. The frequency response is reasonably flat over a central range of frequencies, but at low frequencies the gain falls off because of the decreased impedance of the choke at low frequencies. In order to extend the flat response to lower frequencies it is necessary to have as high a value of inductance

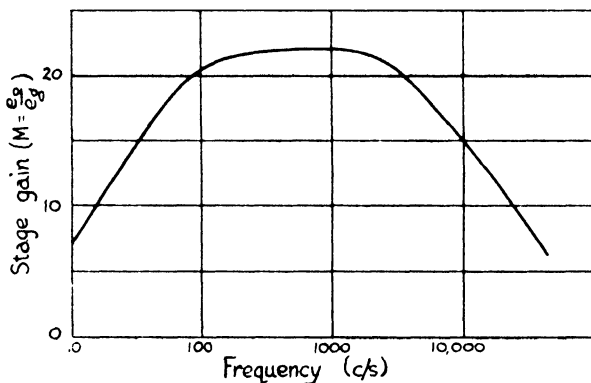


FIG. 362.—Gain/frequency response of a typical choke-capacity coupled stage.

as possible, so that the impedance of the choke is still quite large at low frequencies; thus to give an impedance of $60 \text{ k}\Omega$ at 500 c/s , the choke would require an inductance of about 20 henries. The coupling condenser also causes a falling-off of gain at low frequencies, just as in the R-C coupled amplifier; but its capacity can always be made so large that the falling-off in gain at low frequencies due to the decrease in load impedance occurs considerably before that due to excessive condenser reactance.

As the frequency is increased, the gain tends to rise due to the increase in the reactance of L and the reduction in the reactance of C with increase in frequency. The rise in gain continues until frequencies are reached at which the reactance of C may be neglected, and the reactance of L is very large compared with R_a and R_s in parallel. The value of R_s affects not only this gain, at medium frequencies, but also the range over which the gain is substantially flat. At high frequencies the gain drops off due to the shunting effect of the input capacity of V_2 . Fig. 362 shows a typical gain-frequency response curve for a choke-capacity coupled stage.

Load line for choke-capacity coupled amplifier

A reactive load on a valve is represented on the characteristics as an elliptical load line, and not a straight line. This follows from

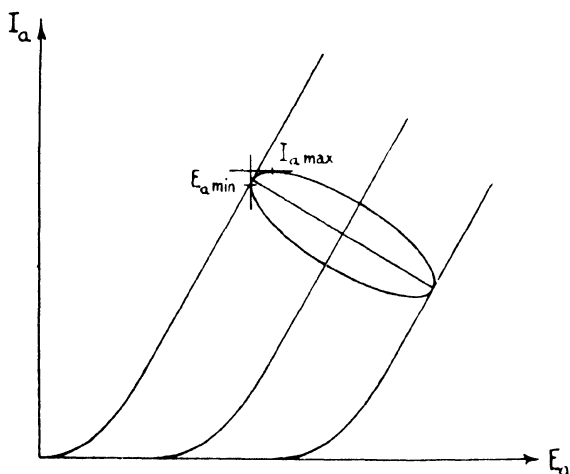


FIG. 363.—Reactive load ellipse.

the fact that, with a reactive load, the anode voltage and current are out of phase, and so peaks occur at different instants. The load line, being the locus of points representing the current and voltage at different instants, can be shown from the equations for E_a and I_a to be, in fact, an ellipse, as shown in Fig. 363.

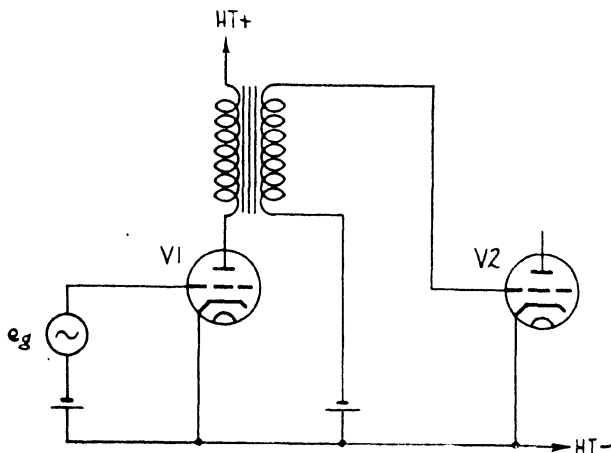
Transformer coupling

FIG. 364 (a).—Simple transformer-coupled stage.

Fig. 364*a* shows a transformer-coupled amplifier; it will be seen that the primary of the transformer forms the load impedance and the secondary is connected between grid and cathode of the following stage.

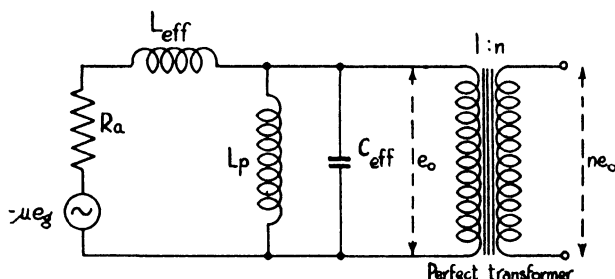


FIG. 364 (b).—Simplified equivalent circuit of transformer-coupled stage.

Fig. 364*b* shows a simplified equivalent circuit; compare this with Fig. 207 (of Chapter 5).

L_p = primary inductance of transformer.

$L_{eff} = L_1 + \frac{1}{n^2} L_2$ = total leakage inductance, referred to primary

L_1 = leakage inductance of primary winding.

L_2 = leakage inductance of secondary winding.

C_{eff} = shunt capacity, made up of the self-capacity of the primary winding; and of the self-capacity of the secondary and the input capacity of V_g , both referred to the primary.

The full equivalent circuit would also contain components to account for primary and secondary resistance, eddy current and hysteresis losses and capacity between the windings, but all these are small enough in practice to be neglected, and have been omitted for simplicity.

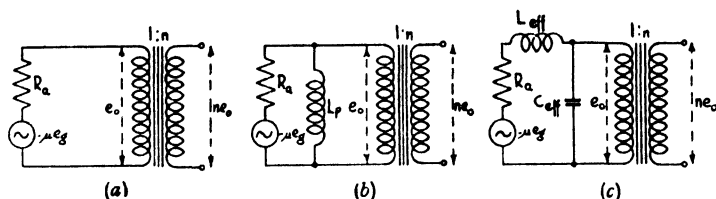


FIG. 365.—Simplified equivalent circuits of transformer-coupled stage applicable to medium, low and high frequencies.

Fig. 365 gives the simplified equivalent circuits relating respectively to the middle, low and high ranges of the frequency band. Over the middle range (see Fig. 365*a*) the impedance of the primary inductance is high (L_p may be about 20 henries), and the

reactances of L_{eff} will be small and C_{eff} will be large. They can therefore be neglected, and the stage gain will be:—

$$M = \left| \frac{ne_o}{e_p} \right| = n \left| \frac{e_o}{e_p} \right| = n\mu \tag{12}$$

One advantage of transformer coupling therefore is that by using a step-up transformer, it is possible to obtain a stage gain exceeding the amplification factor of the valve.

At low frequencies, the reactance of the transformer primary will be lower and must be considered, whilst the reactances of L_{eff} will still be small and that of C_{eff} will be large. The equivalent circuit is then that shown in Fig. 365*b*. In this case:—

$$M = \left| \frac{ne_o}{e_p} \right| = n \left| \frac{e_o}{e_p} \right| = n \frac{\omega L_p \mu}{\sqrt{R_a^2 + \omega^2 L_p^2}}$$

i.e.

$$M = \mu n \frac{1}{\sqrt{1 + \left(\frac{R_a}{\omega L_p}\right)^2}} \tag{13}$$

This shows that the stage gain falls as the frequency is decreased, the rate at which it falls being dependent on $\frac{R_a}{L_p}$. If L_p is made larger, the stage gain will remain reasonably constant down to a lower frequency. For a wide frequency range working down to low frequencies, a very high value of primary inductance is necessary.

At high frequencies the reactances of L_{eff} and C_{eff} become important, and the circuit of Fig. 365*c* applies. Then:—

$$M = \left| \frac{ne_o}{e_p} \right| = n \left| \frac{e_o}{e_p} \right| = \frac{n\mu \cdot \frac{1}{\omega C_{eff}}}{\sqrt{R_a^2 + \left(\omega L_{eff} - \frac{1}{\omega C_{eff}}\right)^2}} \tag{14}$$

Now suppose the series resonant frequency of L_{eff} and C_{eff} is ω_o ,

$$i.e. \quad \omega_o L_{eff} = \frac{1}{\omega_o C_{eff}} \tag{15}$$

and let

$$x = \frac{\omega}{\omega_o} \tag{16}$$

Substituting $\omega = x\omega_o$ in equation 14:—

$$M = \frac{\mu n \cdot \frac{1}{x\omega_o C_{eff}}}{\sqrt{R_a^2 + \left(x\omega_o L_{eff} - \frac{1}{x\omega C_{eff}}\right)^2}}$$

i.e.

$$M = \frac{\mu n}{\sqrt{x^2 R_a^2 \omega_o^2 C_{eff}^2 + (x^2 \omega_o^2 L_{eff} C_{eff} - 1)^2}}$$

$$i.e. \quad M = \frac{\mu^2}{\sqrt{\left(\frac{x}{Q_0}\right)^2 + (x^2 - 1)^2}} \quad (17)$$

$$\text{where} \quad Q_0 = \frac{1}{R_s \omega_0 C_{eff}} = \frac{\omega_0 L_{eff}}{R_s} \quad (18)$$

i.e. Q_0 is the circuit Q at the frequency for which C_{eff} and L_{eff} are in series resonance.

By differentiating equation 17 it can be shown that the stage gain is maximum with respect to x when:—

$$x^2 = 1 - \frac{1}{2Q_0^2} \quad (19)$$

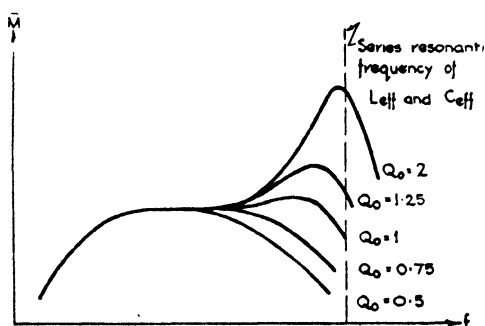


FIG. 366.—Gain-frequency response of transformer-coupled stage showing effect of Q_0 on high frequency response.

Fig. 366 shows typical response curves for a transformer coupled stage, and the effect on gain at high frequencies of a variation in Q_0 .

From the curves it is clear that the flattest response is obtained when Q_0 is slightly less than unity. This means that for a given transformer there is a proper value of R_s which must be used to give the correct value of Q_0 . Intervalve transformers are usually produced to work with valves of AC resistance of about 10,000 ohms, *i.e.* with a triode. Intervalve transformer coupling is not often used with pentodes over the audio range, but where it is used the transformer primary must be shunted by a resistance (*see* Fig. 367).

The simplified equivalent circuit is shown in Fig. 368*a*; this clearly reduces (by Thévenin's theorem) to that of Fig. 368*b*.

R_{eq} is the equivalent resistance of R_s and R in parallel; and since, for a pentode, R_s is very large, $R_{eq} \approx R$. At high frequencies, therefore, R determines the value of Q_0 and hence the high frequency response; the value of R selected is thus the value giving the optimum circuit Q at the resonant frequency of L_{eff} and C_{eff} .

One requisite of an intervalve transformer for use in the circuits

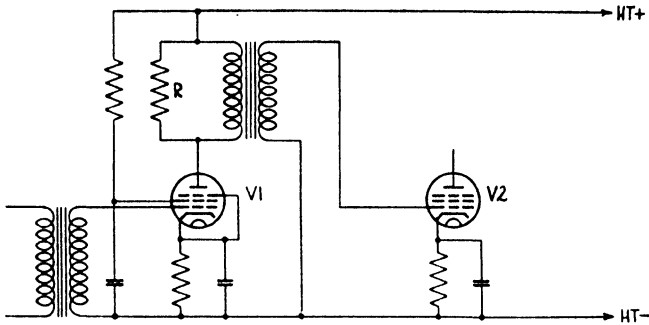


FIG. 367.—Transformer-coupled stage using pentode.

so far considered is that it shall have a large value of primary inductance and at the same time shall be capable of carrying the standing anode current in its primary without undue saturation of the iron core. If saturation occurs, distortion will be produced.

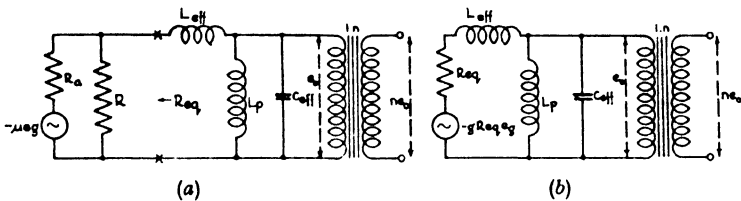


FIG. 368.—Equivalent circuits of transformer-coupled stage using pentode.

In addition, the values of the inductances of the transformer windings will drop. This places practical limitations on the transformer, making it bulky and of low step-up ratio. By using a choke parallel-feed circuit as in Fig. 369, these difficulties are largely

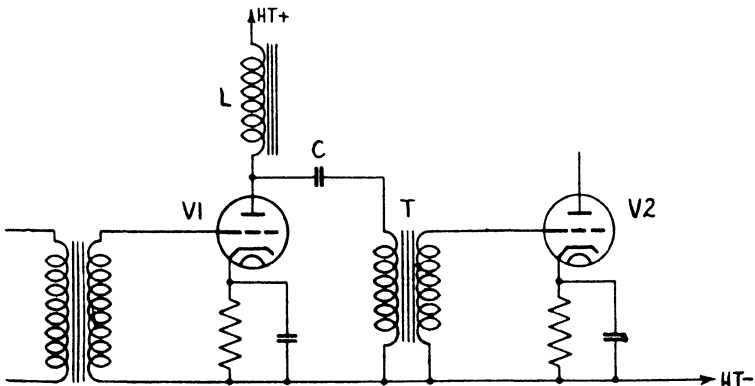


FIG. 369.—Transformer coupling using parallel feed.

overcome; the resulting transformer can be made more compact, with a core of very high permeability material. Comparing two transformers of the same size, one designed for parallel feed and the other for series feed: the parallel-feed transformer can be made to have about three times the primary inductance, and roughly the same value of leakage inductance, as the series-feed transformer. The choke can generally be made to have a larger inductance than a transformer for use in the same circuit, for it has only one winding and iron losses are less important. The overall result is a flatter gain-frequency response at low frequencies, although there will still be a falling-off at very low frequencies produced by the choke and coupling condenser.

Input transformers

Where it is necessary to couple the grid of the first stage of an amplifier to a low impedance such as a transmission line, this is usually done by means of a step-up transformer as in Fig. 370.

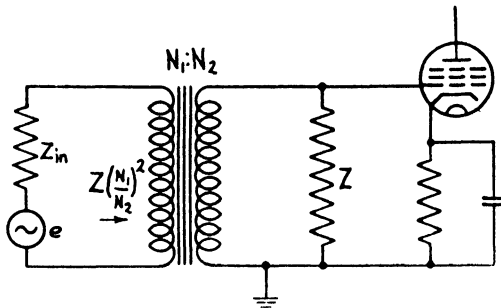


FIG. 370.—Input transformer.

It will be seen that this is, in all essential features, equivalent to the interstage coupling of Fig. 364 with the input impedance of the line replacing the AC resistance of V_1 . Thus the equivalent circuit of Fig. 364, and the analysis which follows, holds for input transformers as well as interstage transformers. The primary inductance will be in proportion to the impedance of the line and the transformer may have a high step-up ratio (*e.g.* 1 to 22). In order to obtain the correct input impedance, an impedance Z may be placed across the secondary of the transformer.

TUNED VOLTAGE AMPLIFIERS

In the commonest type of tuned amplifier the load impedance is supplied by a parallel resonant circuit, which gives the necessary high impedance load over a comparatively narrow band of frequencies. Such amplifiers can be made very selective with respect to frequency, making it possible to amplify signals of a desired frequency whilst eliminating other signals.

Amplifiers of this type are used :—

- (a) for amplification of radio-frequency signals ;
- (b) for amplification of intermediate frequencies in super-heterodyne radio-frequency receivers ;
- (c) for amplification of a narrow band of frequencies within the audio range, as in certain VF telegraph equipment.
- (d) for amplification of 500 c/s voice frequency (VF) signals in many types of VF signalling units.

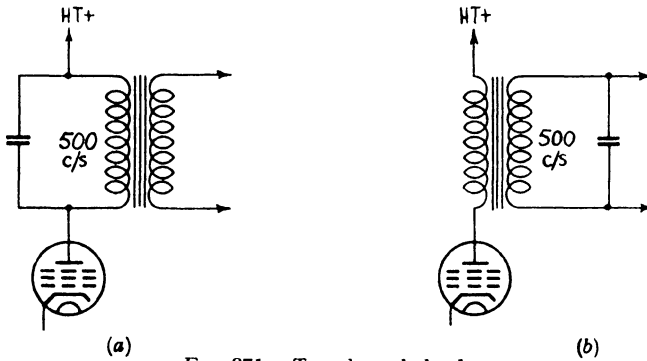


FIG. 371.—Tuned anode load.

Fig. 371 shows two arrangements of the tuned anode load which is the basis of many VF signalling units.

In both cases the response curve is of the type shown in Fig. 372.

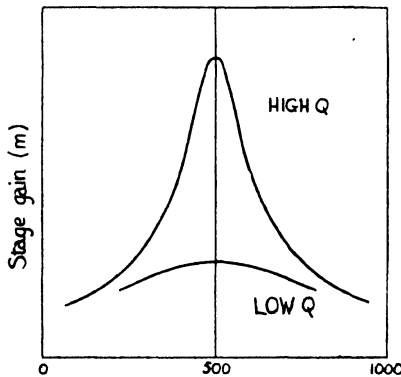


FIG. 372.—Response curve of amplifier using tuned anode load.

This shows that if the Q of the parallel resonant circuit is high, the amplification at resonance will be high and the frequency discrimination will be critical. This is the ideal response curve

for a VF signalling receiver where it is desired to select only one frequency, but if it is required to have a constant gain over a band of frequencies, say from 1800 to 1920 c/s, it is necessary to reduce the Q of the tuned circuit. This will decrease the amplification at resonance and may necessitate an additional stage of voltage

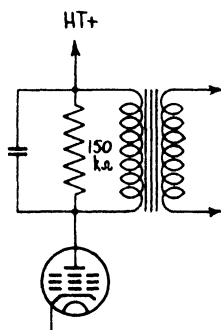


FIG. 373.—Tuned anode load with shunt resistance to broaden the frequency response.

amplification in order to obtain the required gain. The simplest method of reducing the Q is the introduction of a shunt resistance across the tuned circuit, as shown in Fig. 373.

Band-pass coupling

For intermediate frequency (IF) amplification in a superheterodyne receiver, a different form of coupling is used between stages. This is *band-pass* coupling, as shown in Fig. 374.

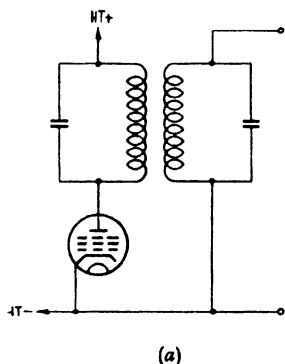


FIG. 374.—Tuned amplifier with band-pass coupling.

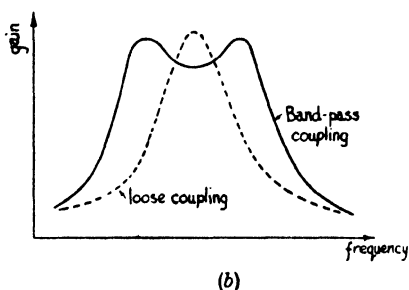


FIG. 375.—Response curve of tuned amplifier using band-pass coupling.

Here both primary and secondary of the transformer are tuned to the required intermediate frequency (say, 465 kc/s); and, with suitable values of Q and of the coupling coefficient, the response curve will be as in Fig. 375.

Clearly such an amplifier gives very good discrimination against frequencies appreciably off resonance, while at the same time it responds uniformly to a band of frequencies immediately above and below the resonant frequency. Two such IF transformers may be coupled together, as in Fig. 376, the response curve being

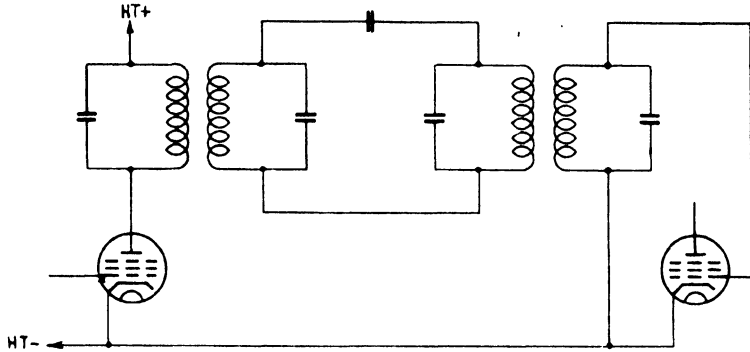


FIG. 376.—Typical coupling between stages using double band-pass coupling.

similar to Fig. 375, but giving greater discrimination against frequencies appreciably off resonance.

Shunt resistances may be inserted across primary or secondary to flatten the response, if required. At the same time this will reduce the frequency discrimination.

GAIN CONTROL IN AMPLIFIERS

A large number of amplifiers used in line terminal equipment utilise methods of gain control depending on the application of varying amounts of "negative feed back"; the principles of this method are dealt with in the next chapter. Other methods that

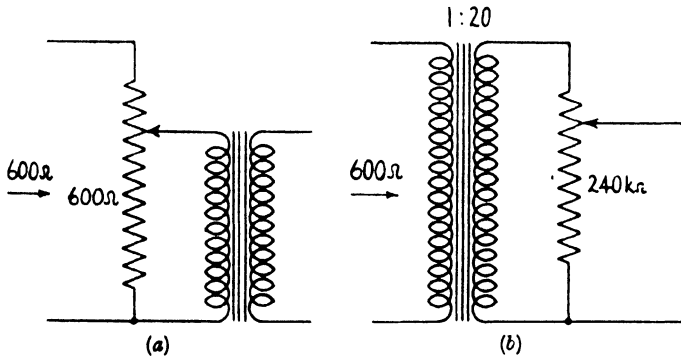


FIG. 377.—Gain control by potentiometer on input transformer.

will be encountered, either singly or in combination, for producing variation in gain, are :—

(i) A constant gain amplifier is provided with variable attenuation pads in the input circuit, the output circuit or both.

(ii) A potentiometer is provided on either the low impedance (line) side or the high impedance side of the input transformer.

Fig. 377 shows the gain potentiometer on the low and high impedance sides of the input transformer.

(iii) Variation in gain is provided by means of varying tappings on the input transformer, thereby varying the turns ratio.

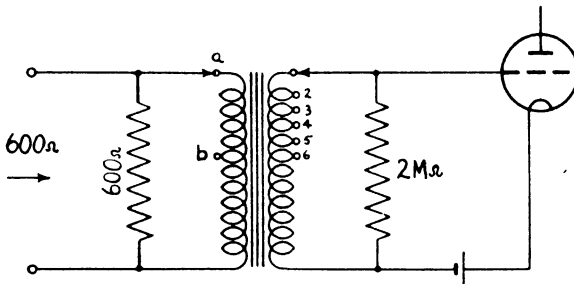


FIG. 378.—Gain control by tappings on input transformer.

Fig. 378 shows an instance where both the primary and the secondary turns are variable. For example, the taps *a* and *b* on the low impedance side may be arranged to give a variation of 3 db, and the six taps 1–6 on the high impedance side to give a variation of $\frac{1}{2}$ db each.

Automatic gain control (AGC)

Automatic gain control (sometimes referred to as automatic volume control or AVC) was originally introduced to combat fading in radio receivers. The requirement is for a device that will maintain the output approximately constant at any desired level, in spite of fairly large fluctuations in the general level of the incoming signal. Precisely the same problem arises in the case of line communication, though in this case the variations in input level are caused by variations in line attenuation and generally take place much less rapidly than does fading in a radio receiver. In many cases these variations in overall circuit attenuation can be tolerated, but in a voice-frequency telegraph system, for example, a change in the level of the input signal will affect the operation of the receive relay and introduce distortion to the incoming signal, unless AGC is applied to the receive amplifier.

The general principle of AGC is that a portion of the incoming signal, after amplification, is applied to a diode or metal rectifier, and the rectified current is used to produce voltage across a resistor; the DC component of this voltage, which will be proportional to the amplitude of the incoming signal, is utilised to provide negative

bias for the amplifying stages. These stages usually employ variable- μ valves. Thus the greater the input signal, the greater the negative bias on the variable- μ valves, and the less the overall gain of the receive amplifier. The term "simple AGC" is applied to a system of AGC such that with zero signal input, all amplification stages have maximum sensitivity; but an AGC bias is produced and fed to the controlled valves by all signals, however weak.

Delayed AGC involves the use of a special circuit in which the AGC bias does not appear until the signal input reaches a certain pre-arranged value. This results in the sensitivity of the receiver remaining at maximum for weak signals.

Examples of AGC circuits

Fig. 379 shows the AGC circuit used in a superheterodyne receiver of a high frequency carrier system. Part of the output

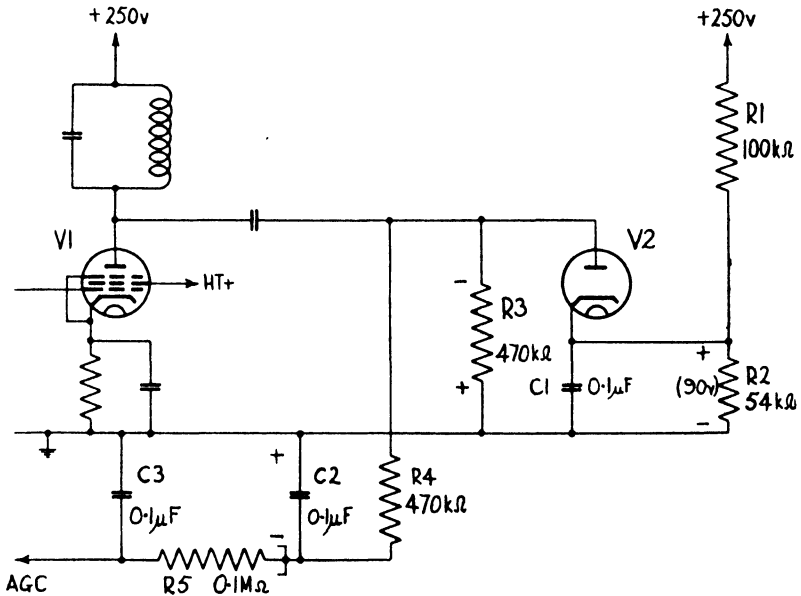


FIG. 379.—AGC circuit used in a superhet receiver.

of the 465 kc/s IF amplifier is fed to the grid of the AGC amplifier valve V_1 , which is a tuned amplifier of a type similar to those already discussed. The output is coupled to the diode V_2 . The cathode of V_2 is maintained at about 90 volts positive with respect to the earth line by means of the potentiometer R_1 , R_2 between HT positive and earth; this provides the voltage delay in the AGC, for no current can flow through the diode until the peak value of the signals applied between anode and earth exceeds 90 volts. When the signals are above this level, V_2 acts as a shunt diode

rectifier and produces a rectified component giving a potential across R_3 of polarity as shown in Fig. 379. The negative potential of the top end of K_3 relative to earth is applied, via the resistor R_4 (decoupled by C_2) and *via* individual smoothing circuits such as R_5 and C_3 , to the grids of the variable- μ pentodes of the preceding amplifier stages. Since these amplifiers have tuned anode loads, the output is practically free from any harmonic distortion that may be produced in the valve due to working on the curved portion of the mutual characteristic.

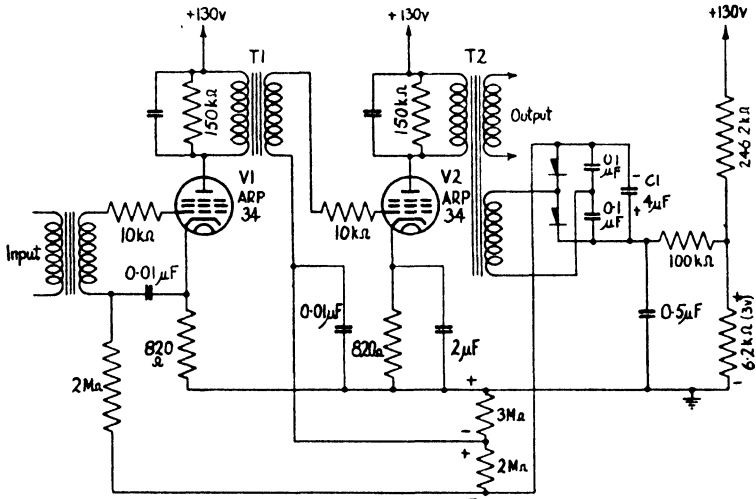


FIG. 380.—AGC circuit used in VF telegraph equipment.

Fig. 380 shows another AGC circuit, this time used in the receive side of a VF telegraph equipment. Part of the output of a tuned amplifier is applied to a voltage doubler circuit that develops a DC potential across C_1 as shown. The AGC bias is applied to V_1 and V_2 via a potential divider that gives V_1 a larger AGC bias than V_2 . Delay voltage is provided by a potentiometer ($6.2\text{ k}\Omega$ and $246.2\text{ k}\Omega$) between HT positive and earth. If the incoming signal increases in amplitude, the negative bias voltage produced by the AGC circuit and applied to V_1 and V_2 will be increased, and the gain of the amplifier reduced. If the incoming signal decreases in amplitude, the negative bias will decrease and the gain of the amplifier increase. In this way the output voltage across the secondary of the transformer T_2 is kept substantially constant, even though large changes may occur in the input level. In this case the AGC is so effective that a decrease in the input voltage by as much as 900 times (59 db) may have no appreciable effect on the output voltage. This enables the apparatus concerned to operate satisfactorily on all input voltages from 1.8 volts down to 2 millivolts without any manual gain control.

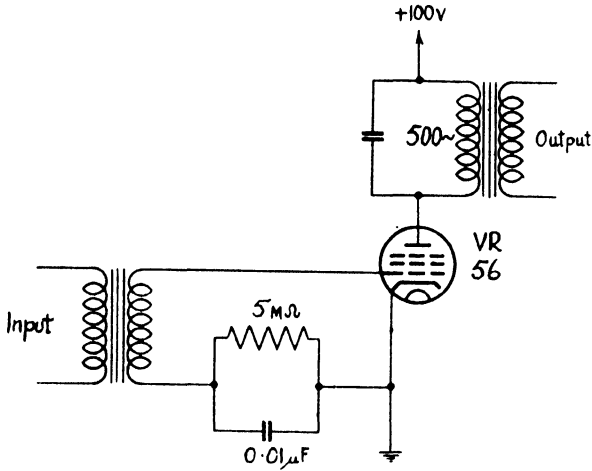


FIG. 381.—Limiter amplifier used in a VF signalling receiver.

Another circuit that may be classed as giving a type of AGC is shown in Fig. 381. This is the first stage of a VF signalling receiver, and its function is to give a constant voltage output independent of the amplitude of the 500 c/s input, provided that the input exceeds a certain minimum level. It will be seen that it consists merely of a tuned amplifier to which grid leak bias is

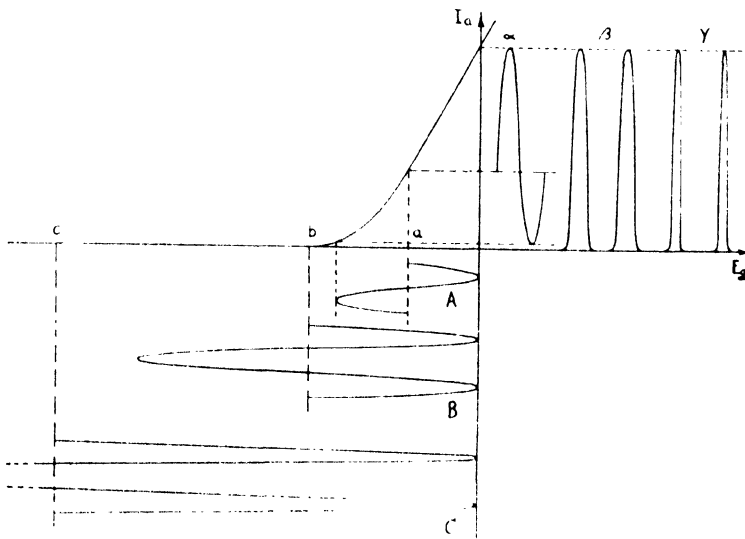


FIG. 382.—Action of limiter amplifier.

applied. It has already been seen that when grid leak bias is applied to a valve, the bias voltage on the grid is just sufficient to cause a small amount of grid current to flow on the positive peaks of applied signal (see p. 370).

In Fig. 382 there are shown three signals of varying amplitudes. For small signals such as *A*, the operating point is at *a*, and the output signal *a* applied to the tuned circuit in the anode will give a voltage output that varies with the amplitude of the input signal. If the amplitude of the input is increased to that of the signal *B* the operating point recedes to *b* and the output will be *β*. That the output now becomes independent of any further increase in the input level is seen from a consideration of the input signal *C*, which gives the output *γ*. It is thus the value of the cut-off bias that determines the value of input signal above which limiting takes place, and to make this value small it is usual to supply the limiter valve with a low anode voltage. It will be seen that the distortion produced by such a limiter with large input signals is very great.

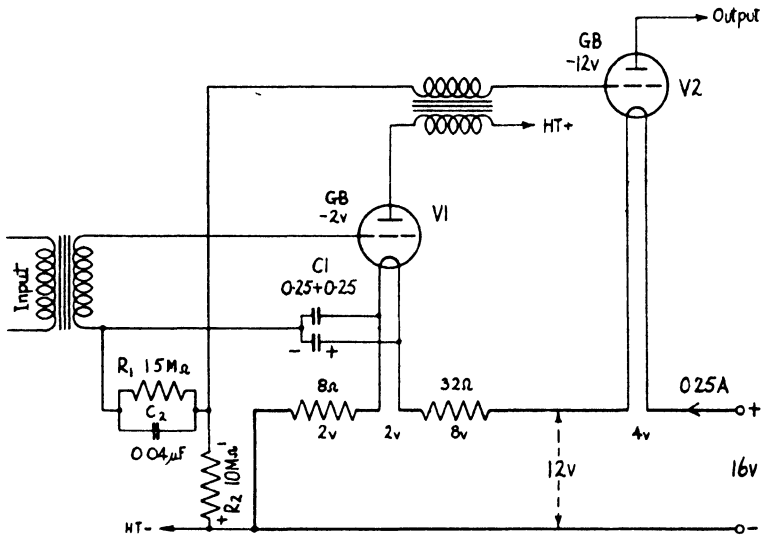


FIG. 383.—AGC circuit used in a VF telegraph detector.

As a last example of AGC, consider the amplifier-detector of a VF telegraph system (see Fig. 383). The standing bias arrangements of this circuit (filament bias) have already been considered. The first stage V_1 has a 2-volt bias, and the second V_2 , a 12-volt bias. The first stage has a high gain, and for large signals V_2 tends to run into grid current on the positive peaks. When grid current flows, a potential is developed across R_2 , and the two parts of condenser C_1 are charged with polarity as shown, and the

voltage across these condensers is applied to V_1 as AGC bias. The discharge path for C_1 is *via* R_1 and R_2 , giving a time constant of 6.5 seconds. In order to prevent the amplifier being cut-off by its AGC bias due to a sudden high level transient, C_2 and R_1 , with a time constant of 60 milliseconds, impose a time delay on the application of the AGC bias to V_1 ; thus the bias on V_1 will not increase until an increase in the level of the received signal has been maintained for a period of that order. AGC bias is also applied to V_2 , but it has practically no effect on this valve, since the AGC voltage is small compared with the large initial bias.

DISTORTION AND NOISE IN AMPLIFIERS

Distortion

Any transmission system (an amplifier being a particular example) is said to introduce distortion if the input and output signals are not *identical in waveform*. This change in waveform may occur due to one or more of a number of causes. These different types of distortion are rigidly defined below for the sake of reference, although in practice it may be difficult to separate the distortion produced by a particular system into these subdivisions.

Attenuation distortion

The name "attenuation distortion" is applied to the case of a transmission system where there is a variation of gain or loss with frequency. It is assessed with the system operated under steady-state conditions by applying a series of signals of sinusoidal waveform at different frequencies.

Phase distortion

Phase distortion occurs when the time of propagation through a transmission system varies with frequency. Owing to the different relative phase relationships then existing, the output waveform may appear to be quite different from the input waveform, even though the same frequencies are present in the same relative amplitudes.

Phase distortion will always be present unless the graph of the overall phase-shift plotted against frequency is a straight line passing through a point on the phase-shift axis corresponding to zero or some integral multiple of 2π radians.

It may be noted that the phase distortion encountered in an audio frequency amplifier is, in general, not important, since the ear is insensitive to small differences in phase.

Non-linear distortion

"Non-linear distortion" is the general name given to a certain type of distortion that occurs when the transmission properties of a system are dependent on the instantaneous magnitude of the applied signal, and it may be sub-divided into amplitude distortion, harmonic distortion, and intermodulation distortion.

Amplitude distortion is defined as the variation of gain or loss of a system with the amplitude of the input. It is measured with the system operated under steady-state conditions with an input of sinusoidal waveform.

Harmonic distortion is due to the production of harmonics in the output when a sinusoidal input of specified amplitude is applied. It is expressed as the ratio of the RMS voltage of all the harmonics in the output, to the total RMS voltage at the output.

Intermodulation distortion is due to the production of combination frequencies in the output when two or more sinusoidal voltages of specified amplitude are applied at the input. For two "parent" frequencies p and q , the output may contain frequencies such as $(p \pm q)$, $(2p \pm q)$, $(p \pm 2q)$, etc., in addition to the frequencies p and q .

Noise in amplifiers

All amplifiers give some output even when there is no input signal. Such output is commonly referred to as "noise", a general term that is further sub-divided according to the causes producing it.

Hum

The term "hum" is applied to extraneous output voltages having their origin in associated or adjacent power circuits. The chief causes of hum are the use of AC heater supply, poor smoothing in an HT supply produced by rectification from an AC supply, and pick-up due to stray electrostatic and electromagnetic fields produced by adjacent power leads. All modern indirectly heated valves are designed to reduce hum from heater supply to a workable minimum, and a further reduction may be obtained by connecting the centre tap of the heater supply to HT—. Hum due to AC ripple in the anode supply can be reduced by providing a more adequate smoothing filter, and that due to stray fields by screening of grid leads, earthing of metal chassis and the use of twisted heater leads. It should be noted that vibrator power packs deriving their power from a DC source may cause strong alternating fields in the neighbourhood of the battery leads, which should therefore be twisted.

It is particularly important to suppress as far as possible any hum picked up in the early stages of a multi-stage amplifier, since any extraneous voltages produced here will be subject to amplification in the later stages. This statement will apply equally to other types of noise.

Microphonic noise

The term "microphonic noise" is used to cover effects arising from mechanical vibration of parts of the circuit, particularly valves. It may be minimised by mounting the valves in such a way

that they are protected from mechanical vibrations transmitted through the chassis, e.g. by using sprung valve holders.

Thermal agitation noise

The random motion of the electrons in a conductor produces minute voltages across the terminals of the conductor, and these voltages are constantly changing in value. This is liable to produce noise, particularly in the earlier stages of an amplifier, where it is subject to further amplification. Since the random motion of the electrons is dependent on the temperature of the conductor, this effect is known as "thermal agitation", and it produces noise voltages that are distributed over the whole frequency spectrum.

Valve noise

Thermionic valves introduce a certain amount of noise into an amplifier, since the anode current is subject to random variations.

Contact noise

Noise may also be caused by poor or intermittent electrical contact. This may arise from dirty or damaged switch contacts, terminals, or connections, leaky condensers, faulty resistances, etc. Carbon resistors also are liable to introduce noise, due to changes in contact resistance between adjacent granules. This effect increases with increased current, and precludes the use of carbon resistors as anode loads in the early stages of a high-gain amplifier if a low noise level is essential.

POWER AMPLIFIERS

So far, only voltage amplification has been considered; that is to say, the sole aim has been the production of a large *voltage* across the anode load. The case will now be considered where the important factor is the *power* developed in the anode load. Power amplifiers are most conveniently classified according to the conditions under which they operate, as determined by the potentials applied to the grid and anode and by the amplitude of the applied signal voltage on the grid. In general, the operation is the same in the case of wide- and narrow-band amplifiers.

Class "A" power amplifiers

An amplifier is said to operate under "Class A" conditions when the waveform of its output is the same as that of its input, as is the case with the majority of voltage amplifiers. This is achieved by biasing the valve to the centre of the straight portion of the mutual (i_a/e_g) characteristic, and applying an input signal that is small enough not to entail operation off this straight portion.

Triode Valves.—Consider the triode amplifier shown in Fig. 384*a*, and its equivalent circuit given in Fig. 384*b*. As is usual with power amplifiers, the AC anode load for the valve is connected through a transformer; this has negligible DC resistance so the

steady DC anode voltage is equal to E_b for all operating conditions. The transformer turns ratio has been taken as 1:1 for convenience; any value might be found in practice.

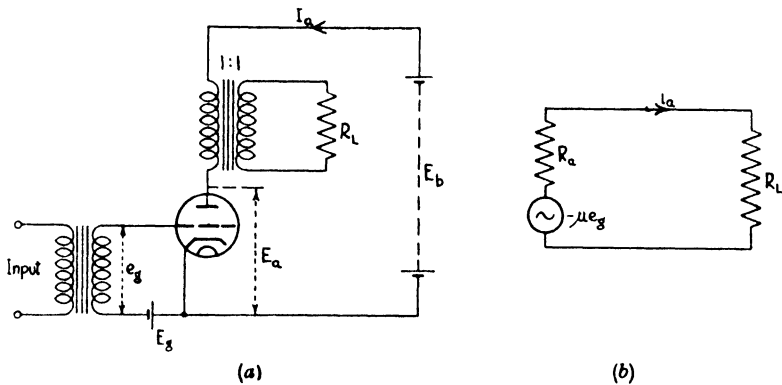


FIG. 384.—Simple triode amplifier with equivalent circuit.

The important problem in this circuit is to determine the conditions that will give maximum undistorted power in the load R_L for a given supply voltage E_b . It might at first appear, from the maximum power transfer theorem, that the value of R_L giving maximum power output is $R_L = R_a$. This is true only for a given small value of e_g , and under these conditions the power output is low, although it is a maximum with respect to R_L . The absolute maximum power output is obtained by making e_g the maximum permitted by the straight portion of the dynamic characteristic for the particular value of R_L . Under these conditions, the only quantities that can be varied are thus the anode load R_L and the grid bias E_g . This can be simplified still further; for, given any value of R_L , the optimum value of the grid bias E_g is the one that puts the operating point at the centre of the straight part of the valve characteristic. Hence variations of R_L alone will be considered, it being assumed that the bias E_g and the input e_g are adjusted in each case to the optimum values. The optimum value of R_L is most easily obtained from the anode characteristics of the valve.

Consider Fig. 385, which shows the anode characteristics of a triode. It is assumed that all the anode characteristic curves are linear above a fixed minimum anode current I_{min} . Let the anode voltage corresponding to I_{min} for $E_g = 0$ be E_s ; so E_s is also fixed. The slope of the curves is given by $\tan \theta = \frac{1}{R_a}$. The load line for R_L is drawn with the "usable" portion as a solid line; it is bounded by the curved region of the characteristics at the bottom, and by grid current at the top of the range. The operating point Q lies on the line E_b , and is adjusted so that it lies at the centre of the working part of the load line. This is done by adjusting the fixed grid bias.

Before the output power can be calculated, an expression must be found for the peak AC anode current i_a obtained with maximum permissible grid swing. Now e_a is the corresponding peak AC anode voltage, and it follows that:—

$$e_a = i_a \cdot R_L \tag{20}$$

An equation for i_a may be obtained from the fact that the distance $AC = AB + BC$;

$$\begin{aligned} \text{i.e.} \quad E_b - E_o &= AB + e_a \\ &= BD \cdot \cot \theta + e_a \\ &= 2 \cdot i_a \cdot \cot \theta + e_a \\ &= 2 \cdot i_a \cdot R_o + i_a \cdot R_L \end{aligned}$$

$$\therefore i_a = \frac{E_b - E_o}{2R_o + R_L} \tag{21}$$

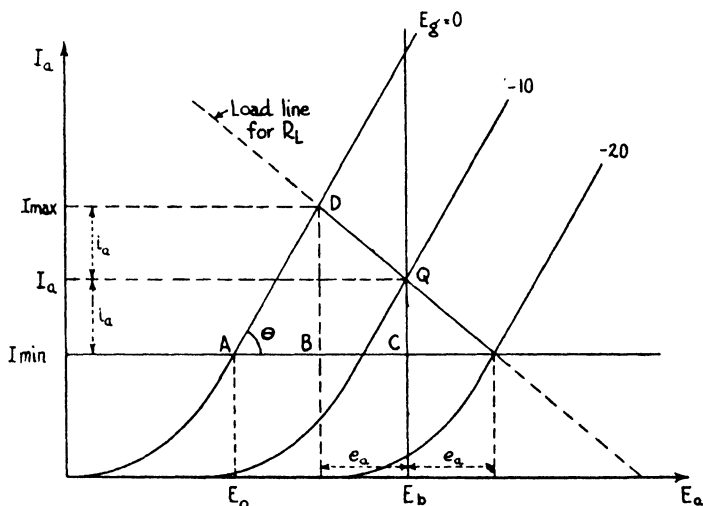


FIG. 385.—Anode characteristics of a triode, showing load line.

The output power can now be calculated:—

$P_o = \frac{1}{2} i_a^2 R_L$ (the " $\frac{1}{2}$ " is due to i_a being a peak, not RMS, value).

$$\text{i.e.} \quad P_o = \frac{(E_b - E_o)^2}{2} \cdot \frac{R_L}{(2R_o + R_L)^2} \tag{22}$$

The maximum value of P_o will occur when $\frac{dP_o}{dR_L} = 0$

$$\text{i.e., when} \quad \frac{(E_b - E_o)^2}{2} \left[\frac{1}{(2R_o + R_L)^2} - \frac{2 \cdot R_L}{(2R_o + R_L)^3} \right] = 0$$

$$\text{i.e., when} \quad 2R_o + R_L = 2R_L$$

$$\text{i.e., when} \quad R_L = 2R_o \tag{23}$$

Hence the optimum load for a triode valve is twice the AC resistance. The maximum output power is:—

$$P_{max} = \frac{(E_b - E_o)^2}{2} \cdot \frac{2R_a}{(2R_a + 2R_o)^2}$$

i.e.
$$P_{max} = \frac{(E_b - E_o)^2}{16 R_o} \quad (24)$$

It can also be shown that the grid bias is given by:—

$$E = \frac{3}{4} \frac{(E_b - E_o)}{\mu} \quad (25)$$

Pentode and Tetrode Valves.—With these valves, the characteristics are not the same shape as those of a triode, and the above results do not apply. In this case it is best to draw the anode characteristics, and fix an operating point. E_b is given,

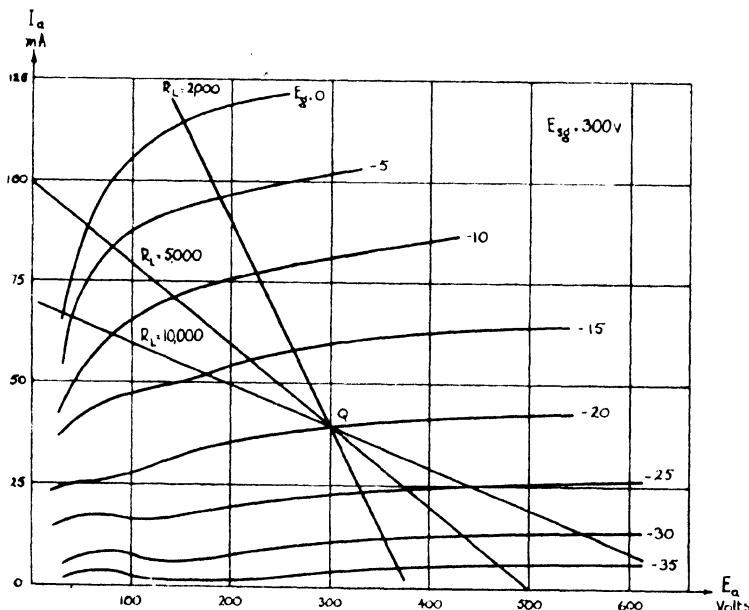


FIG. 386.—Anode characteristics of a 6V6 with three load lines.

and I_a is usually the highest steady current permissible, determined by the maximum anode dissipation. Various load lines should then be drawn, and that one selected which gives *minimum distortion*. This will usually be the line that is drawn from the operating point towards the "knee" of the characteristic.

Fig. 386 shows the characteristics of a 6V6 valve, with three load lines drawn. Methods of estimating percentage distortion will be discussed later, but it can be seen that, on the 2000-ohm line,

the grid voltage curves become widely spaced at the top and close together at the bottom of the line. In the case of the 10,000-ohm line, on the other hand, the curves are cramped at the top. It is clear that the 5000-ohm load affords the best compromise: the grid voltage swing for this load should not exceed the — 5-volt curve.

Efficiency of a Class A power amplifier

In a triode the product of the anode voltage E_a and the standing anode current I_a represent the power dissipated in the valve itself, in the form of heat. This is known as the *anode dissipation*, and must not be confused with the output power developed in the load. In tetrodes and pentodes the product of screen voltage and screen current represents an additional power dissipation, *i.e.* the *screen dissipation*; the sum of anode and screen dissipation in a pentode or tetrode is called the *total dissipation*. The amount of anode (or total) dissipation that can be tolerated is limited by the cooling arrangements within the valve. Valve data sheets give maximum permissible values for anode dissipation in the case of output triodes, and for total dissipation in the case of output tetrodes and pentodes.

The *efficiency* of a class A power amplifier is given by the ratio of the power output to the power supplied by the HT supply.

Thus :—

$$\begin{aligned} \text{Efficiency} &= \frac{\text{Power output}}{\text{Power supplied by HT supply}} \\ &= \frac{\text{Power output}}{\text{Power output} + \text{total dissipation}} \end{aligned} \quad (26)$$

Consider a class A power amplifier, and let E_{max} and E_{min} , I_{max} and I_{min} , be the maximum and minimum values of anode voltage and anode current respectively; then the RMS value of the alternating voltage is $\frac{E_{max} - E_{min}}{2\sqrt{2}}$, and that of the current is

$$\begin{aligned} &\frac{I_{max} - I_{min}}{2\sqrt{2}} \\ \therefore \text{Power output} &= \frac{(E_{max} - E_{min})(I_{max} - I_{min})}{8} \end{aligned} \quad (27)$$

For a triode, the power drawn from the HT supply is $E_a I_a$, where E_a is the voltage of the supply, and I_a is the standing anode current at the operating point.

$$\therefore \text{Efficiency} = \frac{(E_{max} - E_{min})(I_{max} - I_{min})}{8 E_a I_a} \quad (28)$$

Thus it will be seen that this efficiency can never exceed 50 per cent.; for E_{min} and I_{min} can never be less than zero, I_{max} can never be more than twice I_a , and E_{max} must always be less than twice E_a . In practice the efficiency of a triode is never greater than 25 per cent., although in the case of a pentode or beam tetrode the

efficiency may go up to about 35 per cent. From equation 26, with this limitation on efficiency, clearly the maximum undistorted power output is roughly proportional to the maximum permissible total (anode) dissipation; that is to say, if a large power output is required, a valve having a large maximum permissible total dissipation must be chosen.

Calculation of harmonic distortion

(a) *Triodes.*—Fig. 387 shows a dynamic mutual characteristic for a triode. If the operating point Q is chosen in the middle of the straight portion, this represents class A working. If the working portion of the characteristic is not absolutely straight, the output

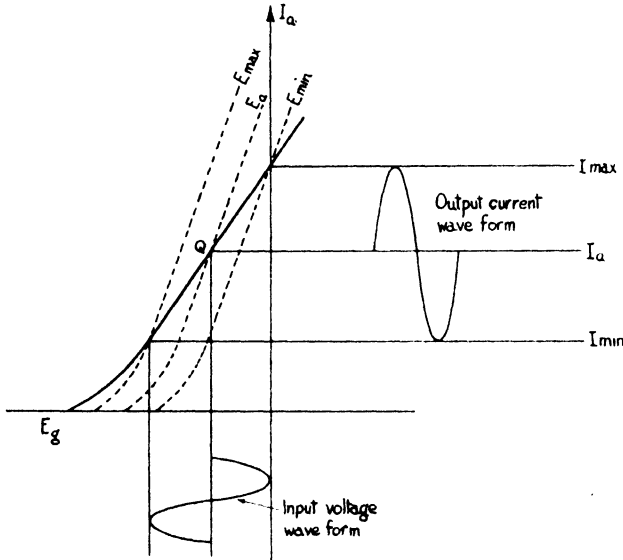


FIG. 387.—Dynamic mutual characteristic of a triode, showing notation for calculation of harmonic distortion.

waveform will not reproduce accurately a sinusoidal input voltage waveform, and the result will be harmonic distortion; in particular, the output will contain a DC and second harmonic components as well as the fundamental. In Chapter 2, it was shown how a Fourier's analysis could be made of an input-output curve; with the notation of Fig. 387, it can be shown that:—

$$\text{Direct current component} = A_0 \approx \frac{I_{max} + I_{min} + 2I_a}{4} \quad (29)$$

$$\text{Fundamental} = A_1 \approx \frac{I_{max} - I_{min}}{2} \quad (30)$$

$$\text{Second harmonic} = A_2 \approx \frac{I_{max} + I_{min} - 2I_a}{4} \quad (31)$$

$$\text{and } \therefore \frac{\text{Second harmonic}}{\text{Fundamental}} = \frac{A_2}{A_1} \approx \frac{I_{max} + I_{min} - 2I_a}{2(I_{max} - I_{min})} \quad (32)$$

In a triode amplifier, only the second harmonic distortion is important and it is this ratio $\frac{A_2}{A_1}$ which determines the percentage distortion; *i.e.* for maximum undistorted output $\frac{A_2}{A_1}$ must be less than 0.05 to give the arbitrary limit of 5 per cent. distortion which is selected as being the smallest amount of harmonic distortion that can be detected by the human ear.

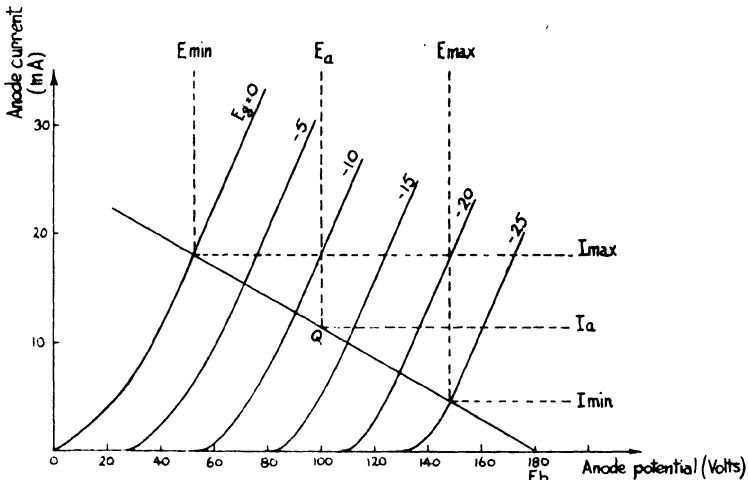


FIG. 388.—Load line for a triode, showing notation for calculating harmonic distortion.

Fig. 388 shows the same notation applied to the load line on the anode characteristics; equations 29 to 32 also apply in this case.

(b) *Pentodes and tetrodes.*—Class A power amplifiers using pentodes or tetrodes require special consideration because the anode current depends on the screen voltage and is substantially independent of the anode voltage. Consequently the mutual characteristics for a constant screen voltage are as shown in Fig. 389, *i.e.* they are practically coincident except at low anode voltages. The dynamic characteristic will therefore be as shown. As compared with the dynamic characteristic of a triode this shows much greater curvature and instead of becoming straighter as the load resistance is increased, develops a point of inflection and the curvature increases. Such a dynamic characteristic gives rise to higher harmonics than second, the main distortion being third harmonic.

From the dynamic characteristic (see Fig. 389) the anode current corresponding to certain values of applied signal can be obtained.

Let I_a = anode current for zero signal voltage.

I_{max} = anode current for maximum positive signal peaks.

I_{min} = anode current for maximum negative signal peaks.

I_2 = anode current for 0.707 of maximum positive signal peaks.

I_3 = anode current for 0.707 of maximum negative signal peaks.

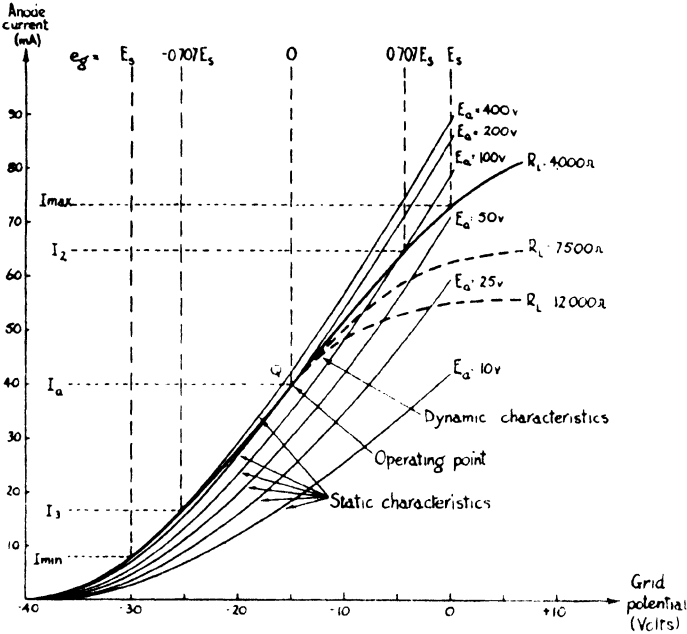


FIG. 389.—Dynamic mutual characteristics of a pentode, showing notation for calculation of harmonic distortion.

With this notation it can be shown that :—

$$\text{Direct current component} = A_0 \simeq \frac{\frac{1}{2}(I_{max} + I_{min}) + (I_2 + I_3) + I_a}{4} \quad (33)$$

$$\text{Fundamental} = A_1 \simeq \frac{(I_{max} - I_{min}) + \sqrt{2}(I_2 - I_3)}{4} \quad (34)$$

$$\text{Second harmonic} = A_2 \simeq \frac{(I_{max} + I_{min}) - 2I_a}{4} \quad (35)$$

$$\text{Third harmonic} = A_3 \simeq \frac{(I_{max} - I_{min}) - \sqrt{2}(I_2 - I_3)}{4} \quad (36)$$

$$\text{Fourth harmonic} = A_4 \simeq \frac{\frac{1}{2}(I_{max} + I_{min}) - (I_2 + I_3) + I_a}{4} \quad (37)$$

$$\text{Total harmonic distortion} = \sqrt{A_2^2 + A_3^2 + A_4^2} \quad (38)$$

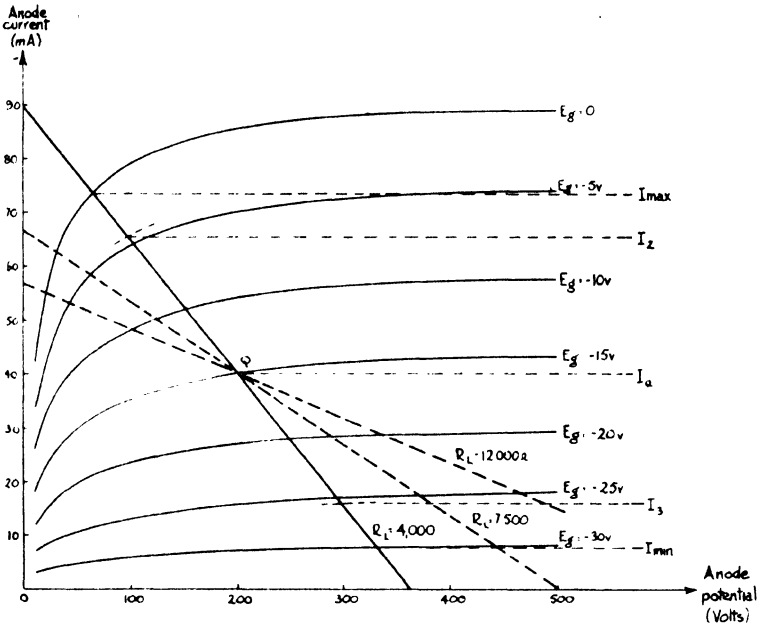


FIG. 390.—Load line for a pentode, showing notation for calculation of harmonic distortion.

Fig. 390 shows how the various anode currents necessary for calculating distortion are derived from the load line on the anode characteristics.

Push-pull Class A amplifiers

In the push-pull amplifier two valves are arranged as shown in Fig. 391.

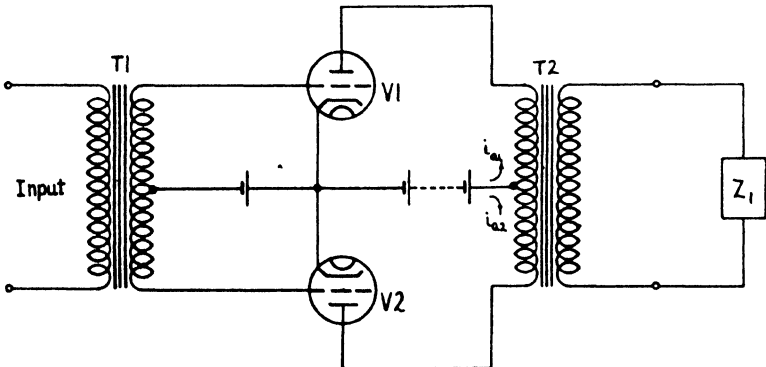


FIG. 391.—Push-pull amplifier.

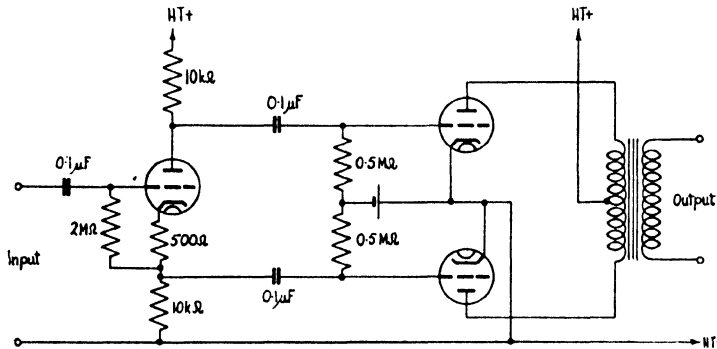


FIG. 392.—Push-pull amplifier with phase-splitter valve.

The signals applied to the two grids are 180° out of phase but equal in amplitude. These signals may be obtained by using either a centre-tapped transformer, or a phase-splitter valve (see Fig. 392), and the outputs of the two valves are combined by means of an output transformer having a centre-tapped primary.

Fig. 393a shows the output waveforms of the two valves and these are combined in the load impedance as shown in Fig. 393b.

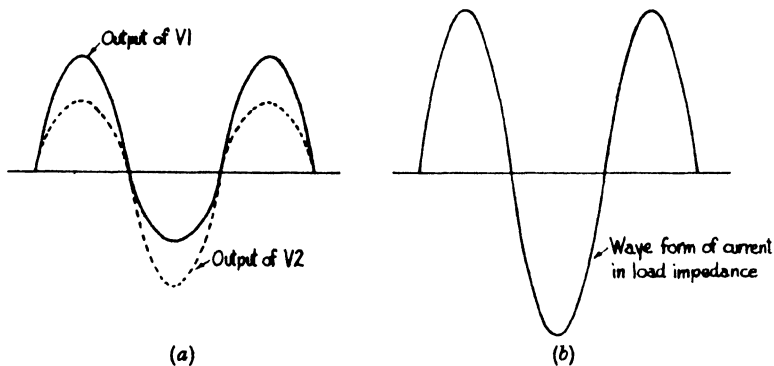


FIG. 393.—Combination of outputs of two valves in class A push-pull.

In Fig. 393a the individual outputs of the two valves have been drawn very rich in second and other even-order harmonics, but it will be seen that the combined output is entirely free from second harmonic distortion.

Let the alternating component of the anode current flowing through the valve V_1 be given by the series:—

$$i_{a1} = A \cdot e_g + B \cdot e_g^2 + C \cdot e_g^3 + D \cdot e_g^4 + \dots$$

where A , B , C , D , etc., are constants, and e is the applied grid signal.

Provided that V_1 and V_2 have similar characteristics, the alternating component of anode current flowing through valve V_2 will then be given by:—

$$i_{a2} = A(-e_g) + B(-e_g)^2 + C(-e_g)^3 + D(-e_g)^4 + \dots$$

$$= -A \cdot e_g + B \cdot e_g^2 - C \cdot e_g^3 + D \cdot e_g^4 - \dots$$

The alternating flux produced in the output transformer will be proportional to the difference between these two currents:—

$$\Phi = k \cdot (i_{a1} - i_{a2})$$

$$= 2k \cdot (A \cdot e_g + C \cdot e_g^3 + \dots)$$

Even harmonic distortion terms thus cancel out, leaving only the odd harmonic terms.

In class A push-pull, the valves are operated in substantially the same way as for a single valve in class A; that is, the operating point is at the centre of the straight portion of the dynamic characteristic, and the maximum signal that may be applied to each grid is limited to the straight portion of the characteristics. The maximum signal that may be applied to the two valves in class A push-pull, and hence the maximum power output obtainable for a given percentage distortion, is greater than twice that for a single valve, owing to this cancellation of even harmonic distortion.

The advantages of the push-pull connection, assuming identical valves, are:—

(a) The direct currents in the two halves of the output transformer produce opposing fluxes, so that there will be no direct current saturation in the output transformer.

(b) The signal-frequency components of current in the HT supply cancel out, and hence there is no common-impedance coupling with other stages using the same power supply.

(c) If the HT supply is derived from AC mains, there is no tendency for mains hum to be introduced in this stage.

(d) Due to cancellation of even harmonic distortion, a greater power output per valve can be obtained before the permissible distortion limit is reached.

Class B power amplifiers

In a class B amplifier, the grid bias is adjusted to “projected cut-off”—*i.e.* to the point P (Fig. 394), where the straight portion of the dynamic characteristic, when extended, meets the axis of zero anode current. Except for very small input voltages, the anode current on positive half-cycles is directly proportional to the input voltage, while on negative half-cycles it is virtually zero. When no signal is applied the anode current is very small, and cathode grid bias is therefore unsatisfactory for this method of working.

The output (anode) current of a single valve working under class B conditions is thus seen to be a succession of pulses that are almost identical in waveform to the positive half-cycles of the input voltage; so that if a sinusoidal voltage be applied to the grid, the anode current will consist of a series of half sine waves similar

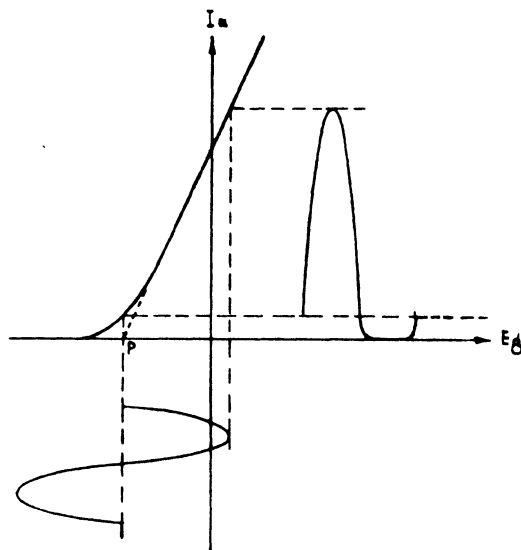


FIG. 394.—Dynamic mutual characteristic, showing class B bias conditions.

to the output from a half-wave rectifier (see Fig. 395a). Current thus flows for approximately 180° of the input cycle, and the valve may be said to operate with an "angle of flow" of 180° (as opposed to 360° for a valve in class A). The distortion produced by such an arrangement is so great as to prohibit its use in an audio-frequency amplifier. If two such valves be operated in push-pull, however,

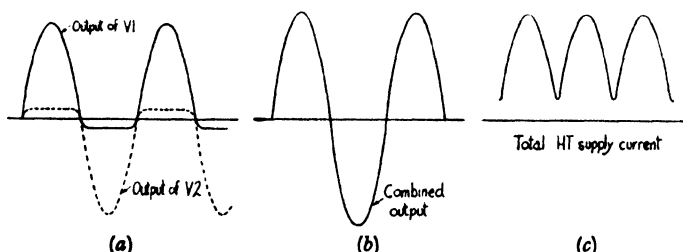


FIG. 395.—Combination of outputs of two valves in class B push-pull.

then each will contribute one half-cycle towards a combined anode current that is identical in waveform to the grid input (excitation) voltage; two valves in push-pull under class B conditions may thus be adjusted to give a distortionless output.

Provided that the impedance of the grid circuit is low, the dynamic characteristic of a valve is still substantially straight for small positive grid voltages, and it is possible to run into the positive-grid region on peaks without introducing excessive distortion. This will give an increase in the maximum permissible

input voltage and consequently in the output power, but in order to obtain the low grid-circuit impedance, it may be necessary to use a step-down (instead of a step-up) transformer to the push-pull stage. Grid current will flow on the positive peaks of the incoming signal, and this represents a loss of power. This power must be supplied by the previous stage, known as the "driver" stage, which must be designed accordingly.

Thus to obtain maximum efficiency in class B operation, the grid is allowed to become positive on the peaks of input signal. The maximum excitation amplitude is then over twice that permissible for the same valve when working under class A conditions, and the power output from the two valves in class B push-pull may be from five to six times that obtainable from a single valve working class A. Owing to the low value of anode current in the no-signal condition, the efficiency of a class B amplifier is much higher than that of a class A, the theoretical maximum being 78·5 per cent. ; in practice, efficiencies of from 50 to 65 per cent. are usual.

It will be seen from Fig. 395c that the total HT supply current to the two valves varies at twice the signal frequency ; adequate decoupling must therefore be provided, as in the case of a single valve in class A, if feedback to earlier stages is to be avoided. Furthermore, the mean value of the anode current of each individual valve—and therefore that of the total HT supply current—rises as the input signal voltage increases ; good regulation of the power supply is therefore essential. A further disadvantage of class B amplifiers is that if the bias voltage is incorrect or if the two valves are not perfectly matched, severe distortion may be introduced.

Class AB power amplifiers

Class AB amplifiers are used to obtain efficiencies greater than are obtainable from class A amplifiers, while at the same time avoiding the critical adjustments necessary for distortion-free operation of class B amplifiers. Two valves are used in push-pull, and the bias is greater than that for class A operation, but not as great as for class B ; the operating point *P* is thus anywhere between the centre *Q* of the "straight" portion of the characteristic (see Fig. 396) and the point *B* corresponding to projected cut-off bias.

Where an alternating voltage is applied to the grid of a single valve operating under these conditions, the output is badly distorted, as shown in Fig. 396 ; when two valves are used in push-pull, however, the distortion is very small. This may be verified, by drawing the individual dynamic characteristics of the two valves, as in Fig. 397, with the two operating points *P*₁ and *P*₂ in line. From these may be drawn the combined dynamic characteristic, which can be seen to approximate to a straight line over most of its length. With careful design the distortion can be kept within reasonable limits.

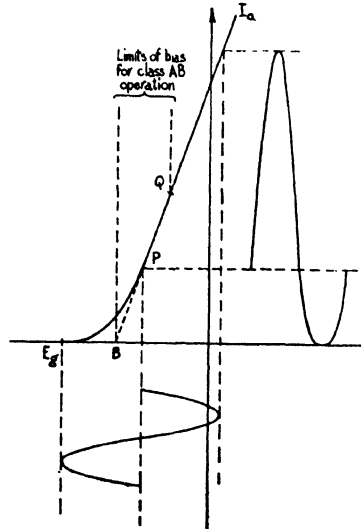


FIG. 396.—Dynamic mutual characteristic, showing class AB bias conditions.

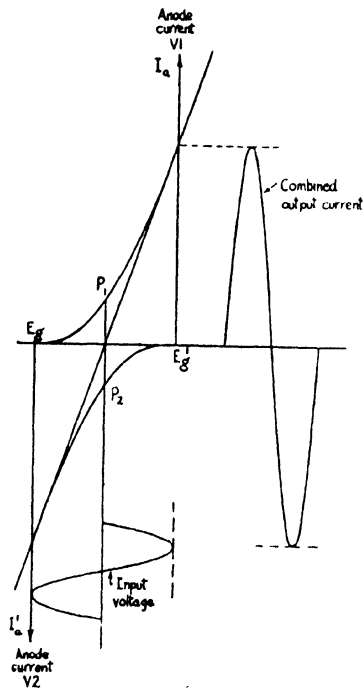


FIG. 397.—Combination of outputs of two valves in class AB push-pull.

When no grid current flows, the suffix 1 may be added to the name (class AB₁). When the grid is allowed to run positive on the peaks of the incoming signal, the suffix 2 may be added (class AB₂).

As in the case of the class B amplifier, the mean value of the anode current of each valve rises as the input voltage increases, so that good regulation of the power supply is necessary. The alternating component of the total HT supply current, however, is smaller than in the case of a class B amplifier, particularly at low input signal levels, since the current taken by one valve does, to a certain extent, decrease as that taken by the other increases. Class AB amplifiers do not require quite such elaborate and carefully designed decoupling, nor do they require such careful supervision as do class B. Quite appreciable unbalance between the two valves, and deviation from the intended bias conditions, may be tolerated.

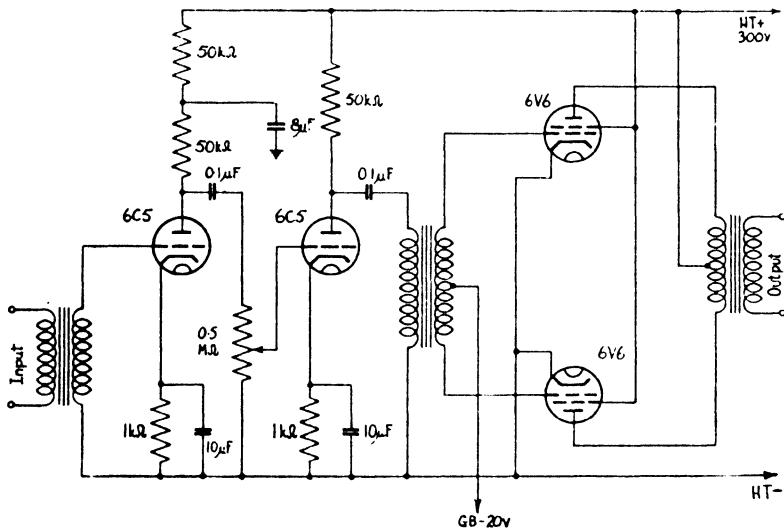


FIG. 398.—Amplifier employing two 6V6's in push-pull in output stage, working under class AB conditions and giving 13 watts output.

The efficiency of 40 to 50 per cent. obtainable in practice, together with these considerations, makes the class AB amplifier very suitable for use in public address systems where medium power output and efficiency are required and moderate distortion can be tolerated.

Class C tuned amplifiers

The class C tuned amplifier differs from an ordinary tuned amplifier in that the valve is given a bias several times greater than the cut-off value. When a signal is applied, anode current flows

in pulses that last for only a fraction of a cycle (*see* Fig. 399). Owing to the distortion produced, such an amplifier is not used for audio-frequency amplification. For radio-frequency amplification, the pulses of anode current are passed through a parallel resonant circuit sharply tuned to the frequency of the input; the output across the tuned circuit is therefore sinusoidal. Since anode current

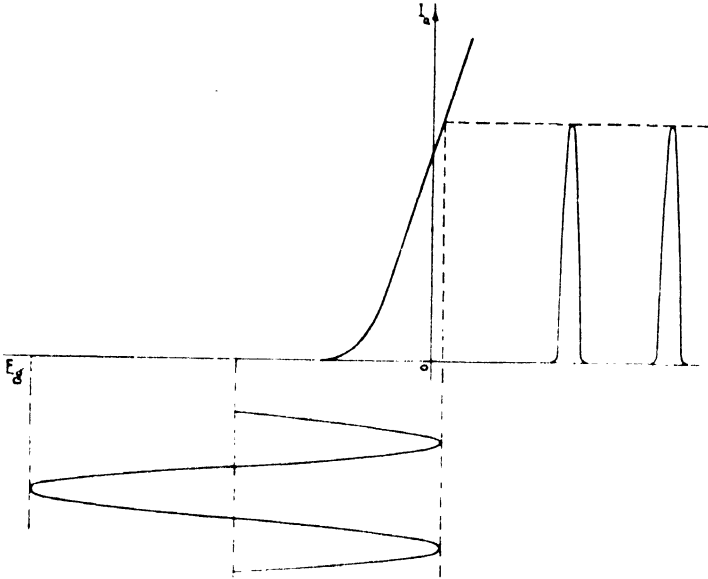


FIG. 399.—Mutual characteristic, showing class C bias conditions.

flows for only a fraction of a half-cycle, the efficiency of a class C amplifier is very high and may approach 100 per cent. Its application, however, is limited, because the output voltage is not directly proportional to the input voltage. In class C operation it is usual to allow the grid to become positive on the peaks of the input signal. The efficiency will be greater if the duration of the pulses of anode current is reduced; this also reduces the power output, although this output is developed at higher efficiency. In practice, the anode current is made to flow for about one-third of a cycle, giving efficiencies of the order of 80 per cent.; this is the best compromise between high output and high efficiency.

CHAPTER 9

FEEDBACK

Soon after the discovery of the amplifying property of the triode valve, it was found that the gain of an amplifier could be increased by feeding back a portion of the output signal into the input, in such a way as to aid the incoming signal. This form of in-phase feedback was originally known as "regeneration" or "reaction", and is now known under the general title of "positive feedback". In addition to increasing the gain, it was noted that this form of feedback led to a decrease in the gain stability of the amplifier, and for this reason this method of increasing the gain of an amplifier is seldom used to-day.

On the other hand, the advantages to be obtained by sacrificing gain by the application of anti-phase or "negative" feedback have been realised only in recent years. In this form of feedback, a portion of the output signal is fed back into the input in opposition to the incoming signal. This results in a decrease in the gain of the amplifier, but, provided sufficient feedback is applied, a great improvement in the gain stability and general performance of the amplifier is obtained. In fact, it converts a valve amplifier from a device whose gain depends on numerous factors such as supply voltage and age of valves, into a precision device whose gain may be made independent of these external factors.

EFFECT OF FEEDBACK ON GAIN

Positive feedback

The application of positive feedback to an amplifier having an initial gain M will now be considered. Assume that positive

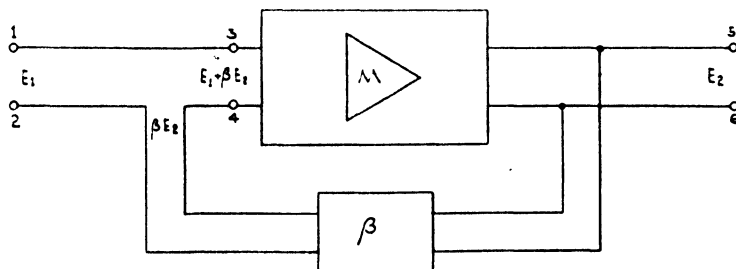


FIG. 400.—Application of positive feedback to an amplifier.

feedback is applied in such a manner, that a fraction β of the output voltage is fed back into the input circuit in phase with the incoming signal (see Fig. 400). In such a case, β is known as the "feedback factor".

Since a valve is a voltage-operated device as far as the grid circuit is concerned, no *power* need be fed back, and the presence of the β -network need not affect the output voltage.

Let the input voltage at terminals 1-2 be E_1 , and let the output voltage at terminals 5-6 be E_2 .

Since a fraction β of the output voltage E_2 is fed back into the input, the voltage fed back is $\beta \cdot E_2$.

This fed-back voltage is in phase with the incoming signal E_1 , and hence the total input at terminals 3-4 will now be $E_1 + \beta \cdot E_2$.

The gain of the amplifier from terminals 3-4 to 5-6 is M ; therefore the output voltage $E_2 = M (E_1 + \beta \cdot E_2)$.

From this, it follows that:—

$$E_2 (1 - \beta \cdot M) = M \cdot E_1.$$

The overall gain (M_o) of the amplifier with positive feedback is therefore:—

$$M_o = \frac{E_2}{E_1} = \frac{M}{1 - \beta \cdot M} \quad (1)$$

The application of positive feedback to the amplifier is thus seen to increase the gain of the amplifier from M to $\frac{M}{1 - \beta \cdot M}$.

Example of positive feedback.—An amplifier has a voltage gain of 200. If $\frac{1}{50}$ th of the output voltage is fed back into the input in phase with the incoming signal, find the new gain.

In this case, $M = 200$. The gain M_o with feedback is therefore:—

$$\begin{aligned} M_o &= \frac{M}{1 - \beta \cdot M} \\ &= \frac{200}{1 - \frac{200}{50}} = 400 \end{aligned}$$

Thus the gain has been doubled by the application of positive feedback.

Find the new gain, if the positive feedback is so increased that $\frac{1}{25}$ th of the output voltage is fed back.

The new gain M_o with feedback is:—

$$\begin{aligned} M_o &= \frac{M}{1 - \beta \cdot M} \\ &= \frac{200}{1 - \frac{200}{25}} = 1000 \end{aligned}$$

Instability and oscillation

If too much feedback is applied, the amplifier may become unstable and oscillations may occur. This may be considered simply as follows:—

Consider the positive feedback amplifier shown in Fig. 400, and assume that there is no input signal. Owing to a transient effect, let a voltage e_2 appear at the output terminals 5-6. A fraction β of this voltage will be fed back *via* the feedback path into the input of the amplifier. Here it will enter the amplifier as a voltage $\beta \cdot e_2$, and, after amplification, will appear in the output as $\beta \cdot M \cdot e_2$. If the gain of the amplifier is such that $\beta \cdot M \cdot e_2$ equals the initial transient voltage e_2 , then the voltage will have "regenerated" itself, and the cycle will be repeated. There will thus be a continuous output voltage, and the amplifier is then said to be in a state of oscillation.

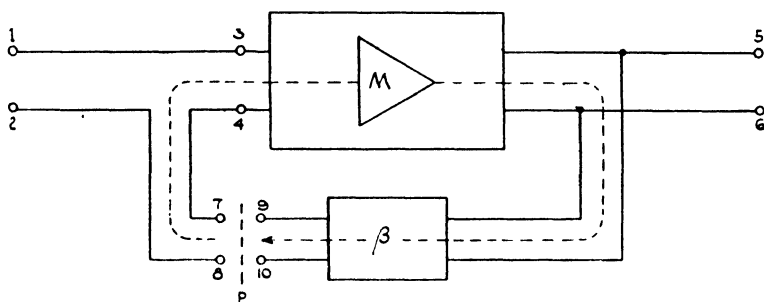


FIG. 401.—Feedback loop path.

It is evident that oscillations occur when $\beta \cdot M \cdot e_2 = e_2$, or in other words, when:—

$$\beta \cdot M = 1 \quad (2)$$

" βM " is known as the "loop gain", since it represents the gain that may be measured by breaking the feedback loop at any point. Considering the point P in Fig. 401, it will represent the gain measured from terminals 7-8 to 9-10.

It follows from the above, that an amplifier with positive feedback will be stable provided that the loop gain βM is less than one. Since the gain M_0 with positive feedback is:—

$$M_0 = \frac{M}{1 - \beta M}$$

it will be seen that when $\beta M = 1$, the gain of the amplifier is infinite. It is under these conditions that an output voltage may be obtained even with no input signal.

To be more accurate, oscillations occur when $\beta M = 1, \angle 0^\circ$. The angle 0° is introduced here to ensure that the feedback is truly positive. M , which denotes the gain of the amplifier without

feedback, will, in general, be a vector quantity having both modulus and angle, since the output voltage will, in all probability, not only exceed the input voltage, but will also be out of phase with it. This may be represented mathematically by writing:—

$$M = |M|, \angle \theta \quad (3)$$

where $|M|$ gives the absolute ratio of the output voltage to input voltage, and θ is the phase angle between them.

The condition for oscillation is therefore that:—

$$\beta \cdot |M| = 1$$

and $\angle \theta = 0^\circ$.

It is only at the frequency for which *both* these conditions are fulfilled that the system will oscillate.

It should be noted that, in most practical cases, oscillation will occur if βM appears to exceed 1, provided that the angle of βM is exactly 0° . This is because in a valve amplifier $|M|$ will automatically adjust itself to give the correct oscillatory condition. There is generally no such self-adjustment as far as θ is concerned (see "Resistance-capacity oscillators", in Chapter 10).

Measurement of amplifier gain

This principle provides an easy method of carrying out a rough check on the gain of an audio-frequency amplifier without the use

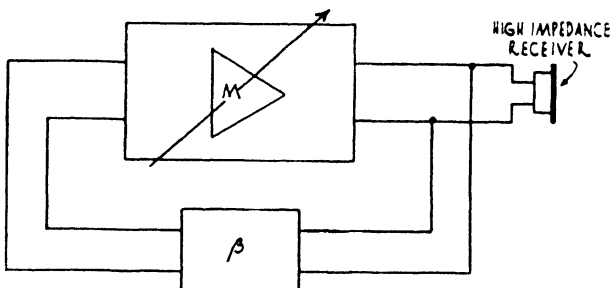


FIG. 402.—Method of checking gain of amplifier.

of elaborate test equipment. The output terminals are connected back to the input terminals *via* a network of known attenuation, in such a manner as to apply positive feedback. A high impedance telephone receiver is placed across the output terminals, so that any oscillation may immediately be detected (see Fig. 402). Then either the gain of the amplifier, or the attenuation of the network, is adjusted until oscillations just start. At this setting, the gain of the amplifier and the attenuation of the network must be such that $\beta \cdot |M| = 1$. From the known loss of the network, the voltage gain of the amplifier can be calculated. Using the decibel notation, if β is, say, a 27 db loss, then $|M|$ must be a 27 db gain.

The frequency of oscillation is that frequency for which the phase shift through the amplifier and network is zero, *i.e.* the frequency for which $\beta \cdot M$ has an angle of 0° .

Negative feedback

The case of an amplifier employing negative feedback will now be considered. In this case, the voltage fed back *opposes* the applied signal, and the voltage at terminals 3-4 (*see* Fig. 403) will therefore be $(E_1 - \beta \cdot E_2)$, instead of $(E_1 + \beta \cdot E_2)$ as in the positive feedback case.

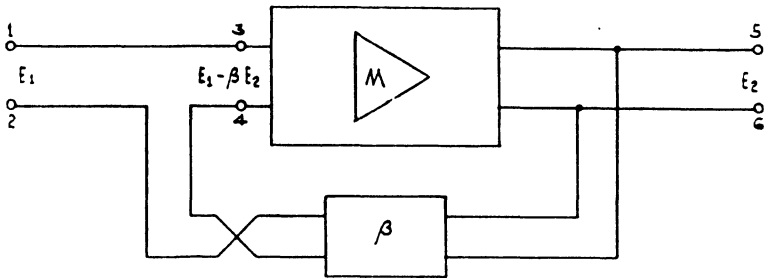


FIG. 403.—Application of negative feedback to an amplifier.

The gain of the amplifier from terminals 3-4 to 5-6 is still M ; hence the output voltage $E_2 = M (E_1 - \beta \cdot E_2)$

$$\therefore E_2 (1 + \beta M) = M \cdot E_1$$

The overall gain M_o of the amplifier from terminals 1-2 to 5-6 with negative feedback is therefore :—

$$M_o = \frac{E_2}{E_1} = \frac{M}{1 + \beta M} \tag{4}$$

The application of negative feedback thus reduces the gain of the amplifier from M to $\frac{M}{1 + \beta M}$.

Example.—

Consider an amplifier having a voltage gain of 240. Let $\frac{1}{5}$ th of the output voltage be fed back into the input in opposition to the incoming signal; that is, $\beta = \frac{1}{5}$. The new gain, with feedback, is :—

$$M_o = \frac{M}{1 + \beta \cdot M} = \frac{240}{1 + \frac{240}{5}} = 48$$

The voltage gain is seen to be reduced from 240 to 48 by the application of this amount of negative feedback.

Application of a large amount of negative feedback

Considering the result that the gain with negative feedback is $\frac{M}{1 + \beta M}$, it will be seen that, if βM is large compared with 1,

then the denominator may be considered to be approximately equal to βM , and the gain M_o becomes :—

$$M_o = \frac{M}{1 + \beta M} \approx \frac{M}{\beta M} = \frac{1}{\beta} \quad \text{provided } \beta M \gg 1 \quad (5)$$

This approximates to the practical case of applying a large amount of feedback to an amplifier having a very high inherent gain. The fact that the effective gain (M_o) of such an amplifier approximates to $\frac{1}{\beta}$ is very important, since it means that the gain is now independent of M . Any factor that may cause a change in M will not alter the effective gain of the negative feedback amplifier. Thus while changes in valves, variations in the amplification factor of a valve with age, and variations in supply voltage may have a large effect on the gain (M) of the amplifier before feedback is applied, they will nevertheless have little effect on the gain after negative feedback has been applied, since these factors do not affect β . The gain of such an amplifier is said to have been "stabilised" by the application of negative feedback.

Example.—

Consider an amplifier having a voltage gain of 20,000, and let $\frac{1}{50}$ th of the output voltage be fed back into the input in opposition to the incoming signal.

This reduces the gain of the amplifier down to :—

$$M_o = \frac{20,000}{1 + \frac{1}{50} \cdot 20,000} = 49.9$$

Suppose that, for any reason, the inherent gain of the amplifier drops to 10,000. This drastic reduction in gain reduces the gain of the amplifier with negative feedback to :—

$$M_o' = \frac{10,000}{1 + \frac{1}{50} \cdot 10,000} = 49.75$$

Any other method of reducing the overall gain of the amplifier (*e.g.*, by an attenuator in the input) would still give a reduction by one-half when the inherent gain M dropped from 20,000 to 10,000, whereas after the application of negative feedback the overall gain drops only from 49.9 to 49.75.

Adjustment of gain of a negative feedback amplifier

From the foregoing, it follows that once a large amount of negative feedback has been applied, any normal gain control that may be applied to the amplifier itself within the feedback loop will be ineffective. Alterations in the overall gain can, however, be made by making β variable. In practical cases, two methods of gain control are adopted :—

(a) β is fixed; the amplifier has a constant gain, and alterations in "apparent gain" are obtained by attenuating the input signals by means of a network or potentiometer *outside* the feedback loop.

(b) β is variable; the gain control then takes the form of a "variable- β " control. In such a case, the gain can be varied only over a small range, otherwise too great a change in performance and in the input and output impedances of the amplifier would result.

EFFECT OF NEGATIVE FEEDBACK ON DISTORTION

In addition to the effect it has on the stability of gain, negative feedback can be used to reduce all forms of distortion produced in an amplifier.

Attenuation distortion

Attenuation distortion, which is distortion due to a variation in the gain of an amplifier with frequency, is greatly reduced by the application of negative feedback over the range of frequencies for which $\beta \cdot M$ is large, provided that β is made independent of frequency (say, by using a simple resistive network). This follows directly from the fact that the gain in such a case approximates to $\frac{1}{\beta}$, and if β is independent of frequency, so also will be the gain.

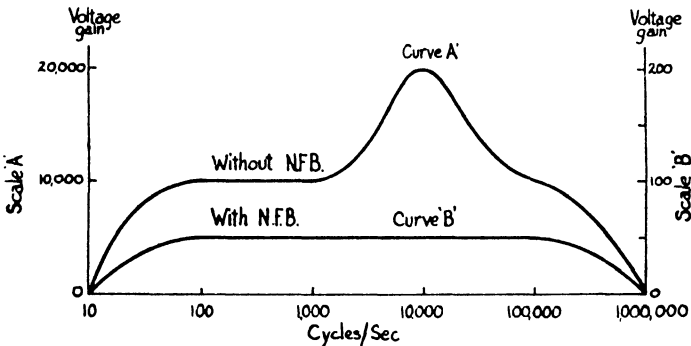


FIG. 404.—Gain-frequency response curve of an amplifier with and without negative feedback.

Consider an amplifier not employing negative feedback, and having a frequency response characteristic as shown by curve "A" in Fig. 404. It will be noted that such an amplifier exhibits attenuation distortion. The voltage gain rises from zero at 10 c/s to 10,000 at 100 c/s and at 1000 c/s, reaching a maximum of 20,000 at 10 kc/s, and falling to 10,000 again at 100 kc/s, dropping to zero at 1 Mc/s. From 1 kc/s to 10 kc/s, the gain rises from 10,000 to 20,000—an increase of 100 per cent.

If negative feedback is applied so that $\frac{1}{50}$ th of the output voltage is fed back into the input, the gain will vary only from 49.75 at 1 kc/s to 49.9 at 10 kc/s—a variation of only 0.3 per cent. The response curve for the amplifier after feedback has been applied is shown in Fig. 404 by curve "B".

Fig. 405 shows the gain-frequency response curves of an actual three-stage amplifier taken before and after the application of negative feedback for which $\beta = \frac{1}{100}$. It will be noted that the effects of negative feedback do not become really pronounced until the inherent gain M has become large enough to make βM very much greater than 1. This only occurs above 1000 c/s.

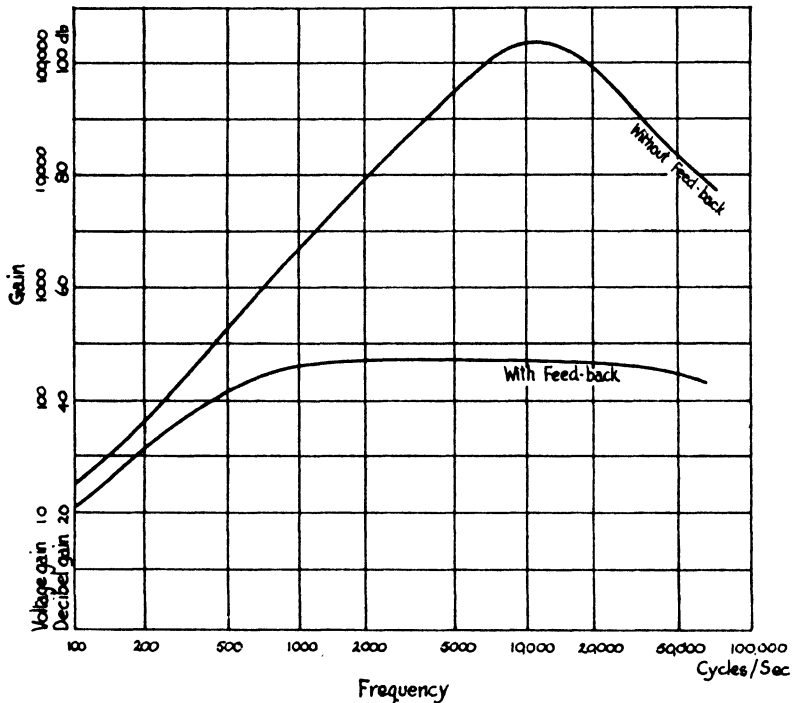


FIG. 405.—Effect of negative feedback on the gain-frequency response of an actual three-stage amplifier.

So far it has been assumed that a flat frequency response curve has been desired, and this has been achieved by making β independent of frequency. It should, however, be noted that the independence of β on frequency is not an essential condition for the application of negative feedback. In fact, in certain circumstances attenuation distortion is desired, and β is then made so to vary with frequency as to give the negative feedback amplifier the required gain-frequency response curve (see Chapter 23, "Equalisers").

Non-linear distortion

In general, the percentage of non-linear distortion in the output of an amplifier will be reduced by the application of negative feedback. This follows from the fact that, when negative feedback

is applied, any harmonics in the output will be fed back into the input, will be amplified by the amplifier, and will appear in the output 180° out of phase with those appearing in the output due to distortion of the original input signal.

However, it should be remembered that the application of negative feedback will reduce the gain of the amplifier, and hence a larger input will be required to obtain the same output with feedback than without. If this increased input has to be obtained from a pre-amplifier, care must be taken to see that this pre-amplifier is not now overloaded, otherwise the increase in distortion produced by the pre-amplifier may exceed the reduction in distortion achieved by the application of negative feedback. In the case of a multi-stage amplifier, the term "pre-amplifier" refers to all the previous stages outside the feedback loop. Thus, in a two-stage amplifier, negative feedback should never be applied to the second stage alone, unless it is certain that the first stage can supply the required increased output without overloading. It is generally better, in such a case, to apply overall feedback from the output of the second stage to the input of the first.

It can be stated that, in a multi-stage amplifier, most of the non-linear distortion will be produced by the last (output) stage, since this stage is handling the signal of largest amplitude, and that the distortion will, in general, be a function of the amplitude of the output of the stage, being very small for small outputs, but increasing as the output increases. It follows, therefore, that when considering an expression for the reduction of distortion due to the application of negative feedback, the input signal must be so adjusted that the same output is obtained in all cases, otherwise an incorrect comparison will be obtained. An approximate formula will now be deduced for the effect of negative feedback on the percentage distortion in the output of an amplifier having a non-linear gain characteristic.

Without negative feedback.—

Consider an amplifier such that, without negative feedback (Fig. 406a), the relationship between the input voltage E and the output voltage E_2 is given by:—

$$E_2 = M \cdot E + N \cdot E^2$$

$M \cdot E$ represents the amplitude of fundamental frequencies in the output, and $N \cdot E^2$ represents the amplitude of distortion frequencies in the output.

Then the percentage distortion in the output is:—

$$\begin{aligned} \text{Percentage distortion} &= \frac{\text{amplitude of distortion frequencies}}{\text{amplitude of fundamental frequencies}} \cdot 100\% \\ &= 100 \cdot \frac{N \cdot E^2}{M \cdot E} \% \\ &= \frac{100 \cdot N \cdot E}{M} \% \end{aligned}$$

NEGATIVE FEEDBACK

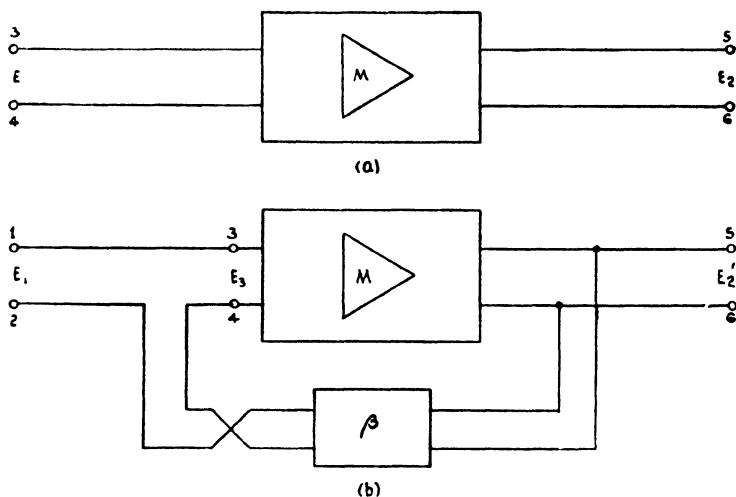


FIG. 406.—Effect of negative feedback on the non-linear distortion produced by an amplifier.

With negative feedback.—

Let a fraction β of the output voltage be fed back into the input in opposition to the incoming signal (Fig. 406b). Let the input voltage at terminals 1,2 be adjusted to some value E_1 that will give the same fundamental output as before the application of NFB; let the resulting voltage at terminals 3,4 be E_3 , and let the corresponding output voltage (with feedback) at terminals 5,6 be E_2' . Then the relation between the input and output of the amplifier itself will be :—

$$E_2' = M \cdot E_3 + N \cdot E_3^2$$

The voltage E_3 at terminals 3, 4 is given by :—

$$\begin{aligned} E_3 &= E_1 - \beta \cdot E_2' \\ &= E_1 - \beta \cdot M \cdot E_3 - \beta \cdot N \cdot E_3^2 \end{aligned}$$

$$\therefore E_3 (1 + \beta \cdot M) = E_1 - \beta \cdot N \cdot E_3^2$$

whence

$$E_3 = \frac{E_1}{1 + \beta M} - \frac{\beta N E_3^2}{1 + \beta M}$$

Substituting in the original equation for E_2' :—

$$\begin{aligned} E_2' &= M \cdot \left(\frac{E_1}{1 + \beta M} - \frac{\beta N E_3^2}{1 + \beta M} \right) + N \cdot E_3^2 \\ &= \frac{M \cdot E_1}{1 + \beta M} + \frac{N}{1 + \beta M} \cdot E_3^2 \end{aligned}$$

The value of the input voltage E_1 must, as stated above, be such that the fundamental component of the output is the same ($M \cdot E$) as before the application of feedback.

Hence
$$\frac{M \cdot E_1}{1 + \beta M} = M \cdot E$$

i.e.
$$E_1 = (1 + \beta M) \cdot E$$

whence
$$E_3 = E - \frac{\beta \cdot N \cdot E_3^2}{1 + \beta M}$$

$$\begin{aligned} \text{Then } E_2' &= M \cdot E + \frac{N}{1 + \beta M} \cdot \left(E - \frac{\beta N E_2^2}{1 + \beta M} \right)^2 \\ &= M \cdot E + \frac{N \cdot E^2}{1 + \beta M} \text{ if the distortion is small.} \end{aligned}$$

Hence the percentage distortion with NFB, for the same fundamental output ($M \cdot E$) as before the application of NFB, is:—

$$\text{percentage distortion} = \frac{100 \cdot N \cdot E}{M} \cdot \frac{1}{1 + \beta M} \%$$

The percentage distortion is therefore reduced according to the relation:—

$$\frac{\text{Percentage distortion with feedback}}{\text{Percentage distortion without feedback}} = \frac{1}{1 + \beta M}$$

Thus if the gain of an amplifier is reduced by 30 db due to the application of negative feedback, the harmonic distortion present in the output will also be reduced by 30 db for the same output voltage.

It should be noted that, although the gain is reduced, the design procedure for an amplifier is unaffected by the application of negative feedback. The correct operating point and anode load for, say, the output stage of an amplifier remain for all practical purposes unchanged, but by reducing the harmonic content for a given output power, negative feedback will allow a still greater output power to be obtained before the permissible distortion limit is exceeded.

Phase distortion

The application of negative feedback reduces the phase-shift through an amplifier. As has been stated, there will, in general, be a phase-shift through an amplifier, so that the output voltage will be out of phase with the input voltage, and the amplification M will be a vector quantity, having both a modulus and an angle.

$$\text{Let } M = |M| \angle \theta$$

Then the gain M_0 with feedback is:—

$$\begin{aligned} M_0 &= |M_0| \angle \theta_0 = \frac{M}{1 + \beta \cdot M} \\ &= \frac{|M| \angle \theta}{1 + \beta \cdot |M| \angle \theta} = \frac{|M| \angle \theta}{1 + \beta \cdot |M| \cdot \cos \theta + j \cdot \beta \cdot |M| \cdot \sin \theta} \end{aligned}$$

$$\text{Hence } \theta_0 = \theta - \tan^{-1} \frac{\beta |M| \cdot \sin \theta}{1 + \beta \cdot |M| \cdot \cos \theta}$$

Thus, by the application of negative feedback, the phase-shift is reduced by an angle $\tan^{-1} \frac{\beta |M| \cdot \sin \theta}{1 + \beta \cdot |M| \cdot \cos \theta}$ (7)

Noise

The application of negative feedback reduces noise in the output of an amplifier. This noise may be due to the valves, crosstalk from neighbouring amplifiers, or power supply hum such as that produced by a poorly-smoothed HT supply. The only limitation is that the noise must have been generated or picked up by the amplifier within the feedback loop. Noise picked up by, say, an input transformer, which is outside the feedback loop, behaves as part of the incoming signal; the signal-to-noise ratio in such a case will therefore be unaffected by the application of negative feedback.

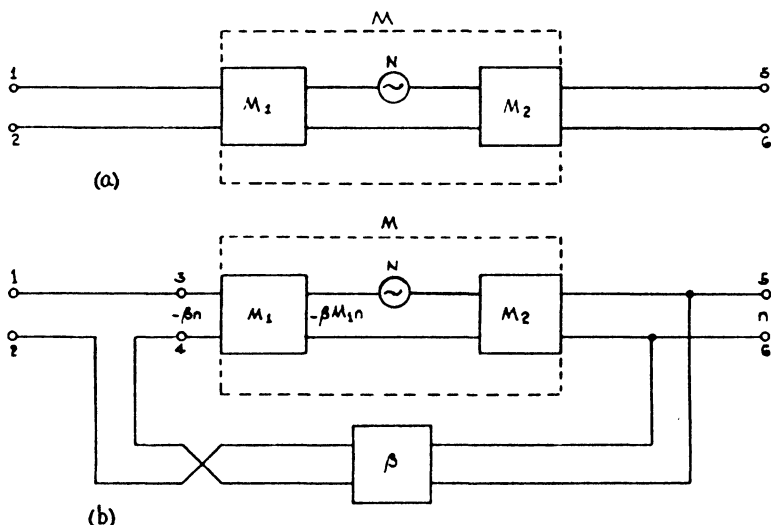


FIG. 407.—Effect of negative feedback on the noise produced by an amplifier.

Consider an amplifier with no feedback applied to it. It is assumed that noise present in the output is produced by a generator of EMF N situated within the amplifier (see Fig. 407a).

Let the gain of the amplifier preceding the generator be M_1 , and let the gain after the generator be M_2 . Then if M be the total gain of the amplifier without feedback,

$$M = M_1 \cdot M_2$$

The noise N is amplified by succeeding stages of the amplifier, and will appear in the output as a voltage $M_2 \cdot N$.

Apply negative feedback so that a fraction β of the output voltage is fed back into the input in opposition to the incoming signal, as shown in Fig. 407b. Let the noise voltage in the output in this case be n . A fraction β of this output is fed back, and will be applied to the input as a voltage $-\beta n$ at terminals 3-4. Thus N will be opposed by $-\beta \cdot M_1 \cdot n$. In the equilibrium condition, the noise output voltage n is therefore given by:—

$$n = (N - \beta \cdot M_1 n) \cdot M_2$$

$$\therefore n(1 + \beta \cdot M_1 M_2) = M_2 \cdot N$$

$$\therefore n = M_2 \cdot N \cdot \frac{1}{1 + \beta \cdot M_1 M_2}$$

$$\therefore n = M_2 \cdot N \cdot \frac{1}{1 + \beta \cdot M} \quad (8)$$

Thus the noise with negative feedback

$$= \text{Noise without feedback} \times \frac{1}{1 + \beta \cdot M}$$

It follows that negative feedback reduces noise in the output of an amplifier by the same factor as that by which the gain is reduced.

Example.—

$M = 240$; noise level in output without feedback = 100 mV.

What is the noise level when $\beta = \frac{1}{25}$?

The noise level in the output after negative feedback has been applied is:—

$$n = 100 \cdot \frac{1}{1 + \frac{1}{25} \cdot 240} = 20 \text{ mV.}$$

This reduction in noise level from 100 mV down to 20 mV may be compared with the reduction in gain from 240 to 48 (*see p. 425*).

Summary of effects of negative feedback on amplifier performance

Before proceeding further, the following is a summary of the effects of the application of negative feedback on the performance of an amplifier:—

- (1) The gain of the amplifier is reduced.
- (2) The attenuation distortion due to the variation in gain of the amplifier with frequency is reduced.
- (3) The phase shift through the amplifier is reduced.
- (4) Distortion due to non-linearity of the amplifier is reduced.
- (5) Noise in the output of the amplifier is reduced.
- (6) Change in overall amplification due to change in inherent gain (M) is reduced.
- (7) Frequency response may be adjusted to any desired value by choice of a suitable feedback network.

All the above have already been mentioned; in addition:—

- (8) Both input and output impedances of the amplifier are modified. For example, the output impedance may be so modified that the voltage gain becomes independent of the output load.

The effect of negative feedback on output impedance depends on the method of applying the feedback. Typical methods will now be discussed.

VOLTAGE NEGATIVE FEEDBACK

In this type of feedback, the voltage fed back is proportional to the voltage across the anode load.

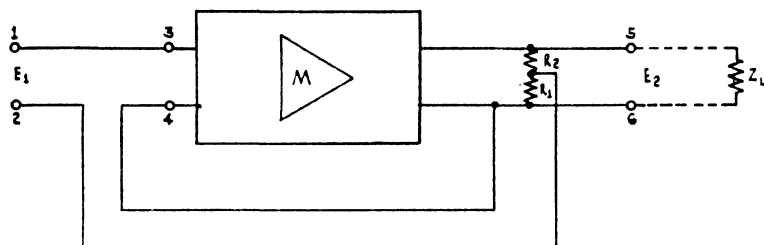


FIG. 408.—Fundamental circuit for voltage negative feedback.

The voltage fed back is usually obtained by placing a potentiometer across the anode load. Consider Fig. 408, where R_1 and R_2 constitute the potentiometer. R_1 and R_2 are large compared with Z_L ; it is assumed that the input impedance to the amplifier is so large as to be considered infinite. It follows that, since $\beta = \frac{R_1}{R_1 + R_2}$, the gain M_o of the amplifier with this form of feedback will be:—

$$M_o = \frac{M}{1 + \frac{R_1}{R_1 + R_2} \cdot M} = \frac{M \cdot (R_1 + R_2)}{R_1 \cdot (1 + M) + R_2} \quad (9)$$

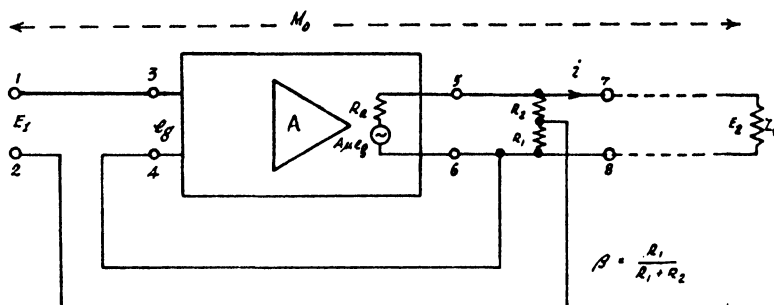


FIG. 409.—Equivalent circuit for voltage negative feedback amplifier.

An alternative approach is to consider the equivalent circuit (Fig. 409). Let the output stage of the amplifier before negative feedback is applied behave as a generator producing an EMF $A\mu e_o$, and having an internal resistance R_a . For a multi-stage amplifier employing a 1:1 output transformer, μ and R_a will be the amplification factor and AC resistance respectively of the last

stage, and A will be the voltage gain of all the preceding stages. In a simple single-stage amplifier not using input and output transformers, A will be unity, and μ and R_a will refer to the valve employed.

Let the current flowing in the anode load be i . Considering the circuit 6, 5, 7, 8 :—

$$\begin{aligned} A\mu e_p &= i(R_a + Z_L) \\ \therefore A\mu Z_L e_p &= iZ_L(R_a + Z_L) \\ \therefore A\mu Z_L e_p &= E_2(R_a + Z_L) \end{aligned} \tag{10}$$

But $e = E_1 -$ voltage fed back

$$\therefore e_p = E_1 - \beta E_2 \tag{11}$$

Substituting in (10) :—

$$\begin{aligned} A\mu Z_L (E_1 - \beta E_2) &= E_2(R_a + Z_L) \\ \therefore E_2(R_a + Z_L + A\mu\beta Z_L) &= E_1 A\mu Z_L \end{aligned}$$

$$\text{Thus } M_o = \frac{E_2}{E_1} = \frac{A\mu Z_L}{R_a + Z_L(1 + A\mu\beta)} \tag{12}$$

Effect on output impedance

When negative feedback is applied to an amplifier an apparent change occurs in the AC resistance of the valve employed in the output stage. Since the output impedance of the amplifier depends on this AC resistance, a change in output impedance will take place when feedback is applied. The effect of voltage negative feedback on the output impedance of an amplifier will now be considered.

Without feedback.—

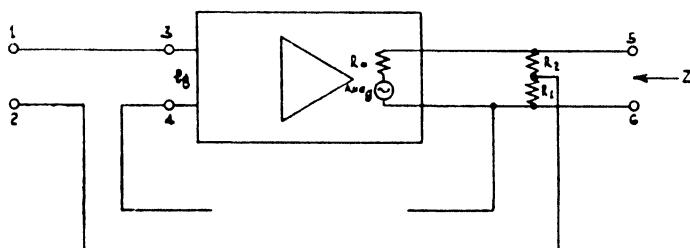


FIG. 410a.—Output impedance of amplifier without negative feedback.

The impedance Z looking back into the amplifier is :—

$$Z = R_a \tag{13}$$

assuming that R_1 and R_2 are large compared with R_a . If R_1 and R_2 are not large compared with R_a then the output impedance will be reduced by the presence of this shunt resistance in both this and the feedback case.

With feedback.—

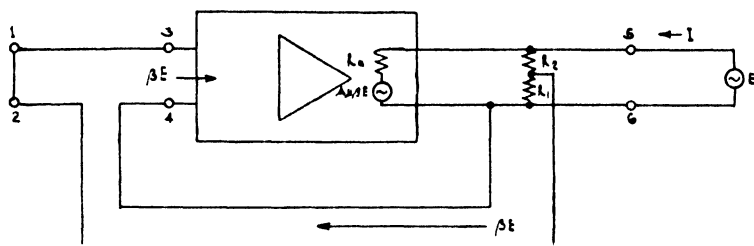


FIG. 410b.—Output impedance of amplifier with negative feedback.

Let a generator of EMF E be applied, and let a current I flow. Then, by Ohm's Law, the new impedance looking back into the amplifier, Z_f , is:—

$$Z_f = \frac{E}{I}$$

Consider the current I flowing.

$$I = \frac{E + A \mu \beta E}{R_o}$$

$$\therefore Z = \frac{E}{I} = \frac{R_o}{1 + \beta A \mu}$$

$$\therefore Z_f = \frac{Z}{1 + \beta A \mu} \quad (14)$$

Voltage negative feedback thus decreases the output impedance of the amplifier in accordance with the relation:—

$$\text{Output impedance with feedback} = \frac{\text{Output impedance without feedback}}{1 + \beta A \mu}$$

Note that while the gain is reduced by the factor $(1 + \beta \cdot M)$, the output impedance is reduced by the factor $(1 + \beta \cdot A \mu)$ —NOT $(1 + \beta \cdot M)$.

Single-stage voltage negative feedback amplifier

Fig. 411 represents a single-stage negative feedback amplifier employing voltage negative feedback. $R_1 + R_2$ will be large compared with Z_L ; C is inserted to prevent HT from reaching the grid, and will have a reactance small compared with $(R_1 + R_2)$ over the working range.

If the valve has an amplification factor μ , and an AC resistance R_o , then the voltage gain M without negative feedback is:—

$$M = \frac{\mu \cdot Z_L}{R_o + Z_L} \quad (15)$$

The voltage gain M_o after feedback has been applied is:—

$$M_o = \frac{M}{1 + \beta M}$$

$$i.e. \quad M_o = \frac{\mu \cdot Z_L}{R_s + Z_L + \mu \cdot \beta \cdot Z_L} \quad (16)$$

It will be noted that this result can be obtained from equation 12 by putting $A = 1$.

Equation 16 may be rewritten as :—

$$M_o = \frac{\mu' \cdot Z_L}{R_s' + Z_L} \quad (17)$$

where
$$\mu' = \frac{\mu}{(1 + \beta \cdot \mu)}$$

and
$$R_s' = \frac{R_s}{(1 + \beta \cdot \mu)}$$

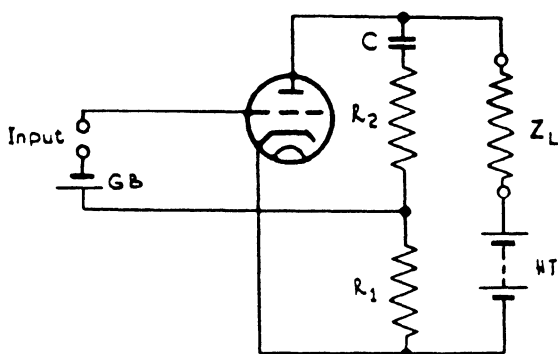


FIG. 411.—Single-stage amplifier with voltage negative feedback.

Thus, after feedback has been applied, the valve behaves as if both its amplification factor and its AC resistance had been reduced in the same ratio—*i.e.*, multiplied by $\frac{1}{(1 + \beta \cdot \mu)}$. This reduction in impedance is of great importance in the output stage of an amplifier, since it facilitates the matching of a high-impedance valve, such as a pentode, to a low-impedance load.*

In the limiting case, when a large amount of feedback has been applied ($\beta \cdot \mu \gg 1$), the valve impedance becomes so low that the valve behaves as a constant-voltage generator; that is, the output voltage is independent of the anode load Z_L .

* It will be realised from this that although triode valves are used as examples throughout this chapter, the arguments apply equally well to tetrode and pentode valves.

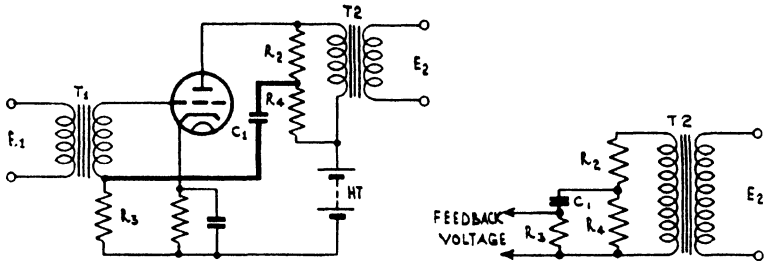


FIG. 412.—Example of single-stage amplifier with voltage negative feedback.

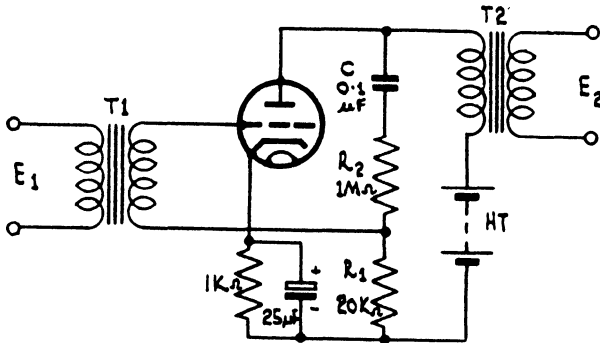


FIG. 413.—Example of single-stage amplifier with voltage negative feedback.

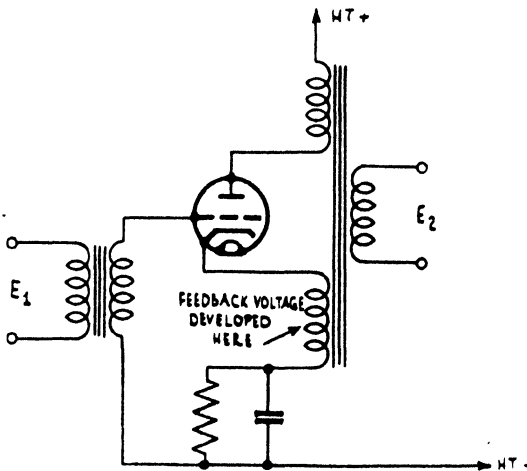


FIG. 414.—Example of single-stage amplifier with voltage negative feedback.

Example.—

Consider a 6V6 valve, having $R_a = 50,000$ ohms, and $\mu = 200$. Applying voltage negative feedback so that $\beta = \frac{1}{50}$, then the new anode impedance Z is :—

$$\begin{aligned} Z &= \frac{Z}{1 + \beta \cdot \mu} \\ &= \frac{50,000}{1 + \frac{1}{50} \cdot 200} \\ &= 10,000 \text{ ohms.} \end{aligned}$$

Practical methods of applying voltage negative feedback

Single-stage feedback

Three methods of applying voltage negative feedback to a single-stage amplifier are shown in Figs. 412, 413 and 414.

In Fig. 412, at frequencies for which the reactance of C_1 is negligible,

$$\beta = \frac{R_1}{R_1 + R_2}$$

where

$$R_1 = \frac{R_3 \cdot R_4}{R_3 + R_4}$$

In Fig. 413, at frequencies for which the reactance of C is negligible,

$$\beta = \frac{R_1}{R_1 + R_2} = \frac{1}{51}$$

Multi-stage feedback

Fig. 415 shows a three-stage amplifier with voltage feedback applied over all three stages.

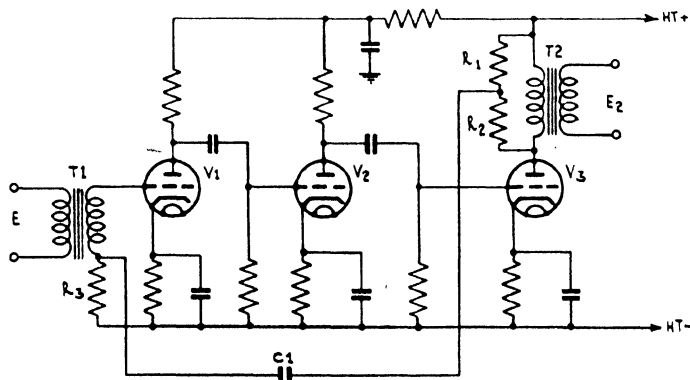


FIG. 415.—Multi-stage voltage negative feedback amplifier.

CURRENT NEGATIVE FEEDBACK

When the voltage fed back is proportional to the current flowing in the anode load, current feedback is said to have been applied.

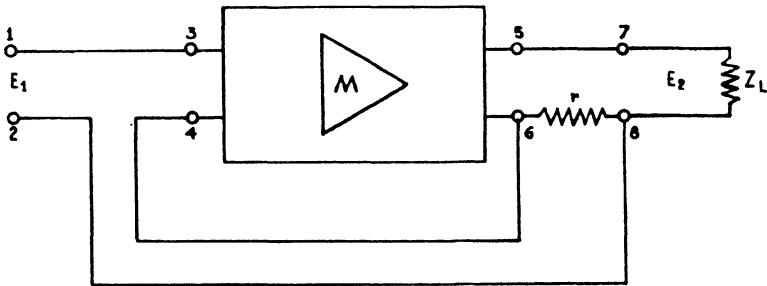


FIG. 416.—Fundamental circuit for current negative feedback

This form of feedback is usually obtained by placing a small resistance r in series with the anode load, and feeding back the voltage developed across it in opposition to the incoming signal.

Considering $(r + Z_L)$ to be the load on the amplifier (Fig. 416), then $\beta = \frac{r}{r + Z_L}$, but it must be remembered that it is only the voltage across Z_L that must be considered when calculating the overall voltage gain of the amplifier.

The voltage gain M' of the amplifier without feedback is

$$M' = \frac{Z_L}{r + Z_L} \cdot M \tag{18}$$

and the voltage gain M_o of the amplifier with negative feedback is

$$M_o = \frac{M'}{1 + \beta M'} \tag{19}$$

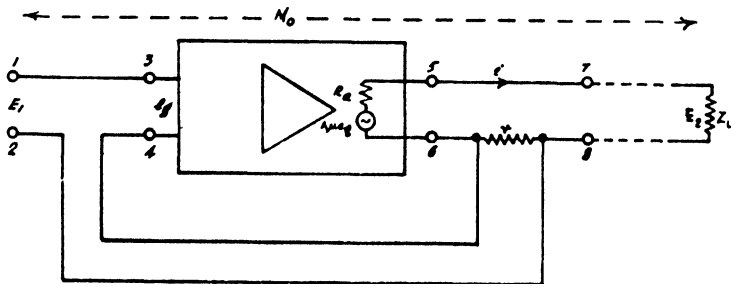


FIG. 417.—Equivalent circuit for current negative feedback amplifier.

As before, an alternative approach, leading to the same result, is to consider the equivalent circuit of the amplifier, Fig. 417. Let the output stage of the amplifier behave as a generator of EMF

$A\mu e_o$, with an AC resistance R_o .

Let the current flowing in the anode load be i . Considering the circuit 6, 5, 7, 8.

$$\begin{aligned} A\mu e_o &= i(R_o + r + Z_L) \\ \therefore A\mu Z_L e_o &= iZ_L(R_o + r + Z_L) \\ \therefore A\mu Z_L e_o &= E_2(R_o + r + Z_L) \end{aligned} \tag{20}$$

But $e_o = E_1 - \text{voltage fed back}$

$$\therefore e_o = E_1 - ir \tag{21}$$

Substituting in (20) :—

$$\begin{aligned} A\mu Z_L (E_1 - ir) &= E_2 (R_o + r + Z_L) \\ A\mu Z_L E_1 - A\mu r E_2 &= E_2 (R_o + r + Z_L) \\ \therefore M_o &= \frac{E_2}{E_1} = \frac{A\mu Z_L}{R_o + Z_L + r(1 + A\mu)} \end{aligned} \tag{22}$$

Effect on output impedance

Consider the effect of current negative feedback on the output impedance of the amplifier.

Without feedback (Fig. 418).—

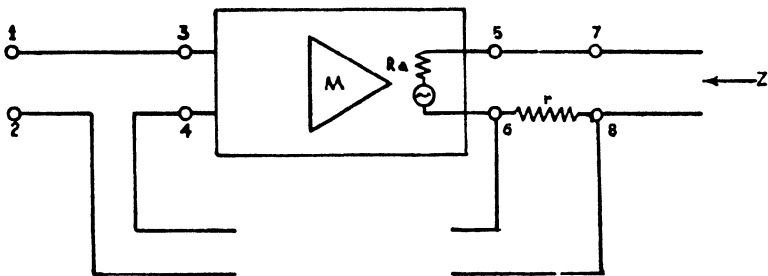


FIG. 418.—Output impedance of an amplifier without feedback.

The impedance Z looking back into the amplifier is :—

$$Z = R_o + r \tag{23}$$

With feedback (Fig. 419).—

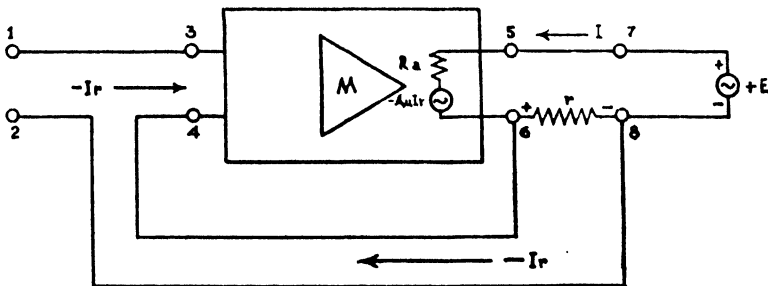


FIG. 419.—Output impedance of an amplifier with current negative feedback.

Applying a generator of EMF E , let a current I flow. Hence, the new impedance Z_j looking back into the amplifier is:—

$$Z_j = \frac{E}{I}$$

Consider the current flowing:—

$$I = \frac{E - A\mu I r}{R_o + r}$$

∴

$$I R_o + I r = E - I A \mu r$$

∴

$$E = I R_o + I A \mu r + I r$$

Hence

$$Z_j = \frac{E}{I} = R_o + r (A \cdot \mu + 1) \tag{24}$$

Thus

$$\frac{Z_j}{Z} = \frac{R_o + r + A \cdot \mu \cdot r}{R_o + r}$$

$$= 1 + \frac{A \cdot \mu \cdot r}{R_o + r}$$

∴

$$Z_j = Z (1 + \beta' \cdot A \cdot \mu) \tag{25}$$

where

$$\beta' = \frac{r}{R_o + r}$$

Thus current negative feedback increases the output impedance in accordance with the relation:—

Output impedance with feedback =

$$\text{Output impedance without feedback} \times (1 + \beta' A \mu).$$

Note that the multiplying factor is $(1 + \beta' A \mu)$ —not $(1 + \beta M)$.

Single-stage current negative feedback amplifier

The simplest method of applying single-stage current negative feedback to a valve employing cathode bias, is to remove the condenser from across the cathode resistor. Fig. 420 represents such an amplifier.

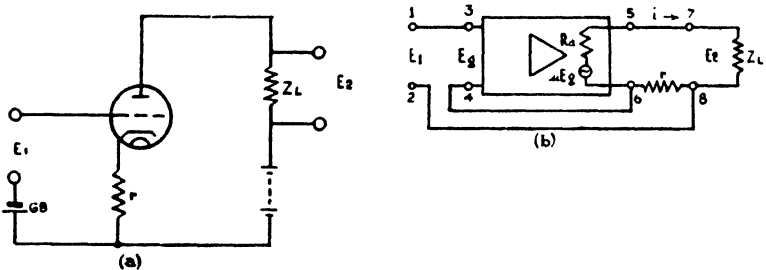


FIG. 420.—Single-stage current negative feedback amplifier.

Let the valve have an amplification factor μ and an anode impedance R_o .

Gain with feedback, from either equation 19 or 22, is given by:—

$$M_o = \frac{E_2}{E_1} = \frac{\mu Z_L}{R_o + Z_L + r(1 + \mu)} \tag{26}$$

Let this equal
$$\frac{\mu Z_L}{R_a' + Z_L} \quad (27)$$

where
$$R_a' = R_a + r(1 + \mu) \quad (28)$$

Thus after current negative feedback has been applied, the valve behaves as if its amplification factor is unchanged, but its internal impedance has been increased by $r(1 + \mu)$.

If $\mu r \gg (R_a + Z_L)$ the gain approximates to $\frac{Z_L}{r}$. The output voltage, E_2 , (which is equal to $\frac{Z_L \cdot E_1}{r}$), is proportional to Z_L . The output current, i , (which is equal to $\frac{E_2}{Z_L}$, i.e. to $\frac{E_1}{r}$), is independent of Z_L . The valve impedance thus becomes so high that the valve acts as a constant-current generator, providing an output-current independent of the value of the load impedance.

Example.—

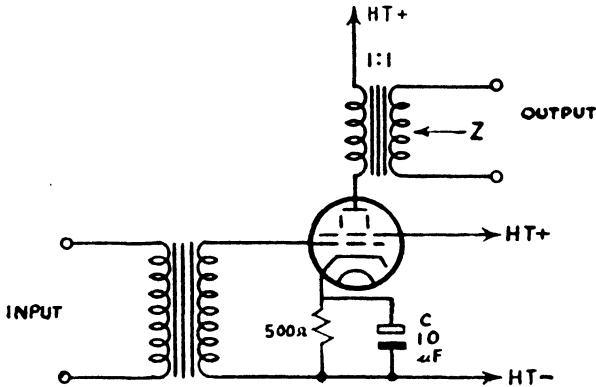


FIG. 421.

A 6V6 valve has the following constants:—

$$R_a = 50,000 \text{ ohms.} \quad \mu = 200.$$

It is used in a voltage amplifier (see Fig. 421).

Determine the effect on the output impedance Z of removing condenser C .

Without feedback:—

$$Z = R_a = 50,000 \text{ ohms.}$$

With feedback:—

$$\begin{aligned} Z &= R_a + r(\mu + 1) \\ &= 50,000 + 500 \times 201 \\ &= 150,500 \text{ ohms.} \end{aligned}$$

Removal of C thus increases the output impedance by 100,000 ohms.

Practical methods of applying current negative feedback

Single-stage current feedback

Fig. 422 shows current negative feedback applied to a single amplifier stage, where the feedback resistance is (a) equal to, (b) smaller than, and (c) larger than, the cathode bias resistance.

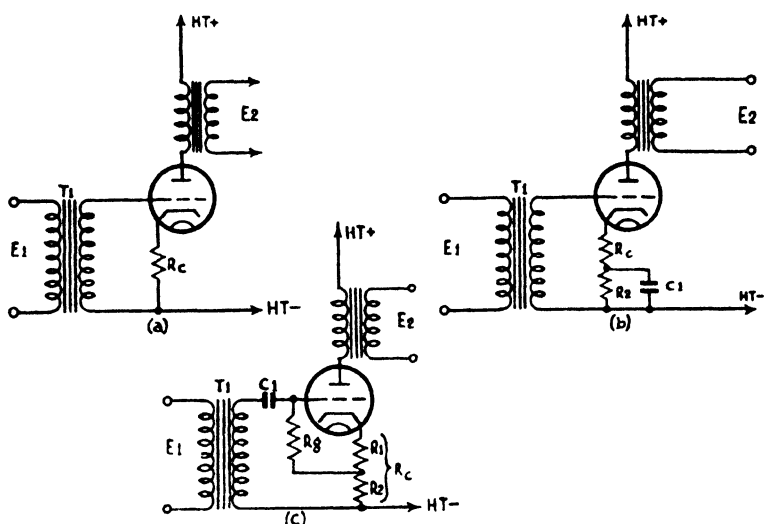


FIG. 422.—Practical methods of applying current negative feedback to a single-stage amplifier.

- (a) R_c provides both bias and negative feedback.
 (b) R_c provides negative feedback, $R_c + R_a$ provide bias.
 (c) $R_1 + R_2 = R_c$ provides negative feedback, R_1 provides bias
 ($R_g \approx 2$ megohms).

Single-stage current feedback varying with frequency

Figs. 423 and 424 show how current negative feedback can be applied to make the gain increase or decrease with frequency.

In Fig. 423, X is comparable with R over the working range. Negative feedback applied depends on frequency, being greatest at the lowest frequency. The greater the negative feedback, the lower the gain.

In Fig. 424, X_L increases with increase in frequency, and therefore the negative feedback increases. Thus the gain decreases with increase in frequency.

Multi-stage current feedback

In Fig. 425, single-stage current negative feedback has been applied by not decoupling the cathode resistors r_1 and r_2 . Feedback over two stages has been applied, since all current through the load (T_2) flows through part (R) of r_1 , developing a voltage that is in opposition to the incoming signal.

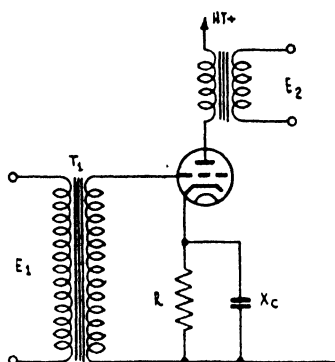


FIG. 423.—Single-stage current feedback varying with frequency—gain increases with increase in frequency.

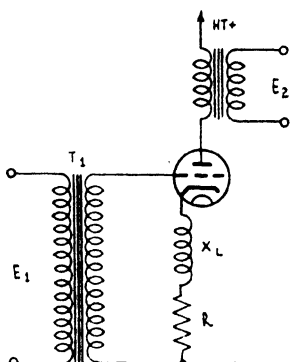


FIG. 424.—Single-stage current feedback varying with frequency—gain decreases with increase in frequency.

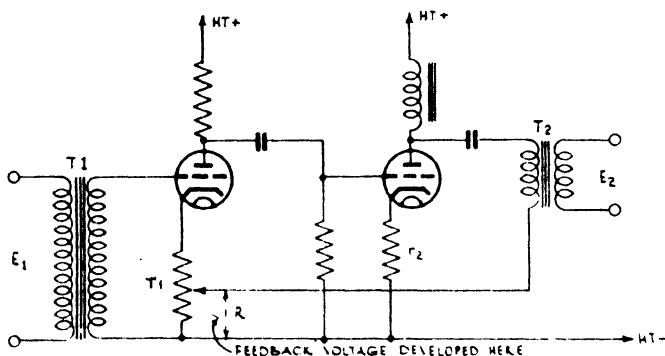


FIG. 425.—Two-stage current negative feedback amplifier.

COMPOSITE NEGATIVE FEEDBACK

Simultaneous application of both current and voltage negative feedback is called "composite feedback" (see Fig. 426).

In this form of feedback, the voltage fed back in opposition to the incoming signal depends on both the voltage and the current in the anode load. The value of the total feedback factor (β) in such a case is

$$\beta = \beta_1 + \frac{r}{Z_L} \tag{29}$$

$$\text{where } \beta_1 = \frac{R_1}{R_1 + R_2} \tag{30}$$

When calculating the gain of a composite negative feedback amplifier ($r + Z_L$) is considered to be the load, but as in the current

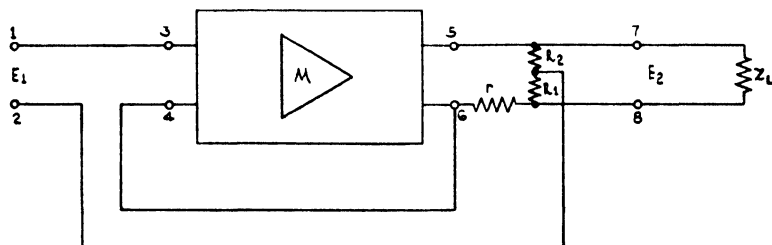


FIG. 426.—Basic composite feedback circuit.

feedback case only the voltage across Z_L must be considered when calculating the overall voltage gain.

Alternatively, it may be assumed as before, that the output stage of the amplifier behaves as a generator of EMF $A\mu e_g$, and having AC resistance R_o .

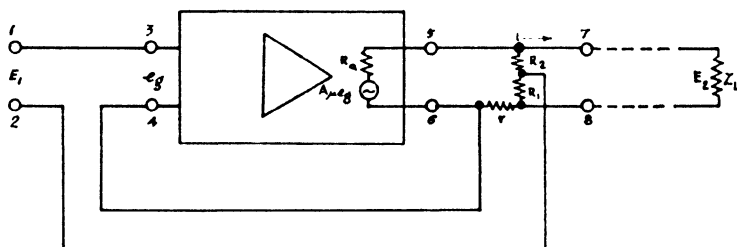


FIG. 427.—Equivalent circuit for composite feedback amplifier.

Considering Fig. 427, let the current flowing in the output circuit 6, 5, 7, 8, be i .

$$\text{Then } e_o = E_1 - ir - \frac{R_1}{R_1 + R_2} \cdot E_2$$

$$\therefore e_o = E_1 - ir - \frac{R_1}{R_1 + R_2} \cdot i Z_L$$

$$\text{Let } \frac{R_1}{R_1 + R_2} = \beta_1$$

$$\therefore e_o = E_1 - ir - \beta_1 i Z_L$$

$$\text{But } i = \frac{A\mu e_o}{R_o + r + Z_L}$$

$$\text{Hence } i = \frac{A\mu(E_1 - ir - \beta_1 i Z_L)}{R_o + r + Z_L}$$

$$\therefore i R_o + ir + i Z_L = A\mu E_1 - A\mu ir - A\beta_1 \mu i Z_L$$

$$i = \frac{A\mu E_1}{R_o + r(1 + A\mu) + Z_L(1 + \beta_1 A\mu)}$$

The gain M_o with feedback is :—

$$M_o = \frac{E_2}{E_1} = \frac{iZ_L}{E_1} = \frac{A\mu Z_L}{R_o + r(1 + A\mu) + Z_L(1 + \beta_1 A\mu)} \quad (31)$$

Effect on output impedance

Consider the effect of composite negative feedback on the output impedance of an amplifier. Assume, as before, that the output stage of the amplifier behaves as a generator of EMF $A\mu e$, and internal impedance R_o .

Without feedback (Fig. 428).—

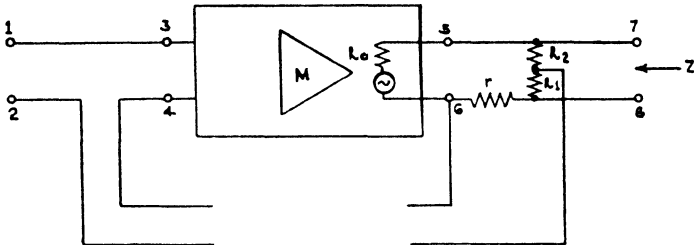


FIG. 428.—Output impedance of an amplifier without negative feedback.

The impedance Z looking back into the amplifier is :—

$$Z = R_o + r \quad (32)$$

assuming that

$$R_1 + R_2 \gg R_o + r$$

With feedback (Fig. 429).—

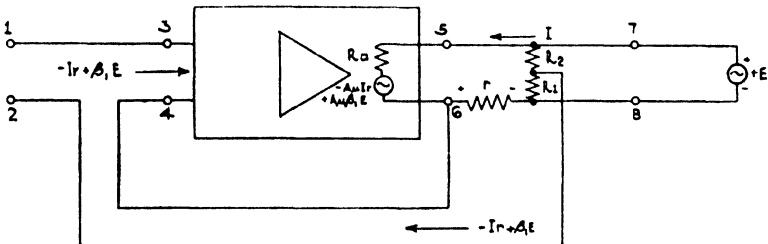


FIG. 429.—Output impedance of an amplifier with composite feedback.

Applying a generator of EMF E , let a current I flow. Hence, the new impedance Z looking back into the amplifier is :—

$$Z_f = \frac{E}{I}$$

The current I is given by :—

$$I = \frac{E - A\mu I r + \beta_1 A\mu E}{R_o + r}$$

$$\therefore I(R_o + r + A\mu r) = E(1 + \beta_1 A\mu)$$

$$\therefore Z_f = \frac{E}{I} = \frac{R_o + r(1 + A\mu)}{1 + \beta_1 A\mu} \quad (33)$$

and
$$\frac{Z_f}{Z} = \frac{R_o + r(1 + A\mu)}{(R_o + r)(1 + \beta_1 A\mu)} \quad (34)$$

By a careful choice of β_1 and r , Z_f can be made to have any value, *i.e.* less than, equal to, or greater than Z .

If A is large and $\beta_1 A\mu \gg 1$, Z_f approximates to $\frac{r}{\beta_1}$, which is independent of any of the valve characteristics.

Single-stage composite negative feedback amplifier

Fig. 430 represents a composite negative feedback amplifier.

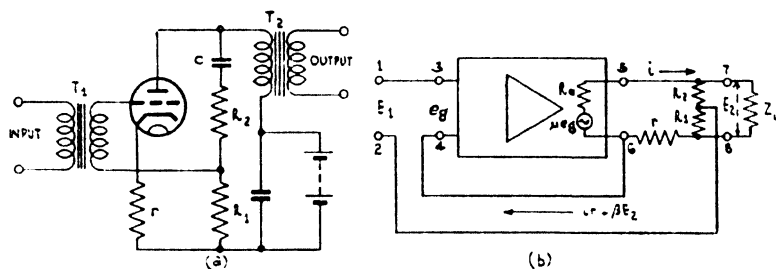


FIG. 430.—Single-stage composite negative feedback amplifier.

Let the valve have an amplification factor μ and an AC resistance R_o .

Putting $A = 1$ in equation 31, the gain M_o with feedback is:—

$$M_o = \frac{E_o}{E_1} = \frac{\mu Z_L}{R_o + r(1 + \mu) + Z_L(1 + \beta_1\mu)}$$

$$\text{Let } M_o = \frac{\mu^* Z_L}{R_o^* + Z_L} \quad (35)$$

$$\text{where } \mu^* = \frac{\mu}{1 + \beta_1\mu} \quad (36)$$

$$\text{and } R_o^* = \frac{R_o + (\mu + 1)r}{1 + \beta_1\mu} \quad (37)$$

Thus after composite negative feedback has been applied the valve behaves as if its amplification factor had been reduced to $\frac{\mu}{1 + \beta_1\mu}$ and its AC resistance changed to $\frac{R_o + (\mu + 1)r}{1 + \beta_1\mu}$.

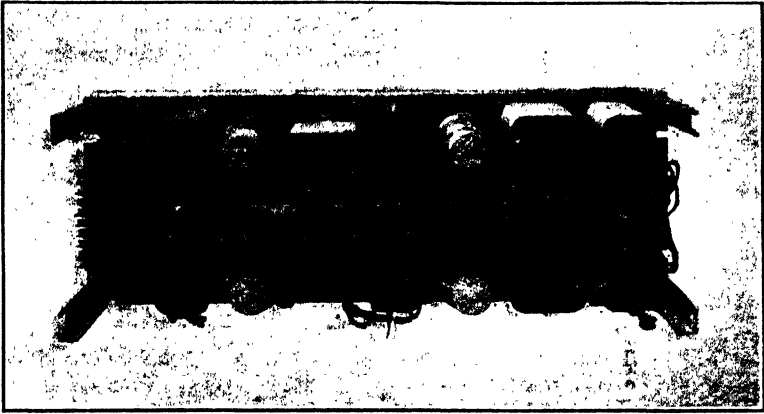


PLATE 23.—Two-stage amplifiers employing current negative feedback.

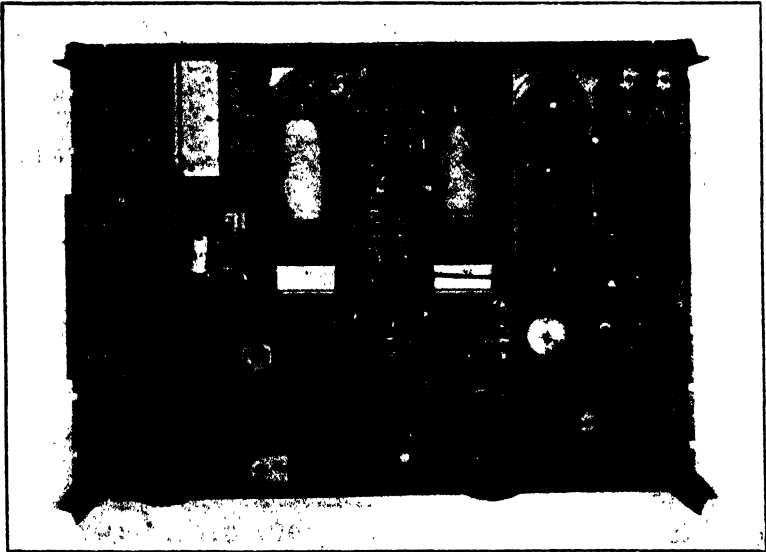


PLATE 24.—Three-stage amplifier employing composite negative feedback.

Example.—

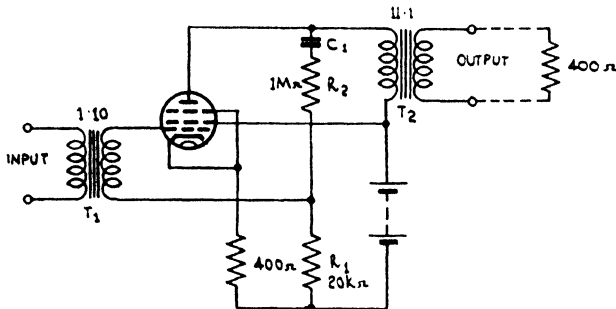


FIG. 431.

Fig. 431 shows a single-stage negative feedback amplifier employing composite feedback and designed to work into a 400-ohm load. The pentode valve used has the following constants:—

$$R_o = 10^6 \text{ ohms}$$

$$G_m = 2.2 \text{ mA/V}$$

$$\mu = 2200$$

What is the gain and output impedance?

$$\beta_1 = \frac{R_1}{R_1 + R_2} = \frac{20,000}{20,000 + 1,000,000} = \frac{1}{51}$$

$$\text{Hence } \beta_1 \mu = \frac{1}{51} \cdot 2200 = 43.2$$

The anode load Z_L on the valve is the reflected impedance of 400 ohms through transformer T_2 .

$$\therefore Z_L = 400 \times 11^2 \\ = 48,400 \Omega$$

The gain of the stage M_o with negative feedback is:—

$$M_o = \frac{\mu Z_L}{R_o + r(1 + \mu) + Z_L(1 + \beta_1 \mu)} \\ = \frac{2200 \cdot 48,400}{1,000,000 + 400(1 + 2200) + 48,400(1 + 43.2)} \\ = 26.5$$

Since the input transformer T_1 is 1 : 10 step up and the output transformer T_2 11 : 1 step down the overall voltage gain from input to output terminals = $\frac{10}{11} \times 26.5 = 24.1$.

The impedance Z_f looking back into the anode of the valve is:—

$$Z_f = \frac{R_o + r(1 + \mu)}{1 + \beta_1 \mu}$$

$$= \frac{10^6 + 400 (1 + 2200)}{1 + 43 \cdot 2}$$

$$= 42,500 \text{ ohms.}$$

The ratio of transformer T_2 is 11 : 1 step down,

$$\text{Hence output impedance} = \frac{42,500}{121} = 352 \text{ ohms.}$$

If feedback were not applied the output impedance would depend entirely on the R_a of the valve and on the turns ratio of T_2 . It would be :—

$$\frac{10^6}{121} = 8270 \text{ ohms.}$$

SERIES AND PARALLEL FEEDBACK

Series negative feedback

In all cases of feedback so far discussed, the signal fed back has been applied in series with the incoming signal. This type of feedback is known as "series" feedback. The distinguishing

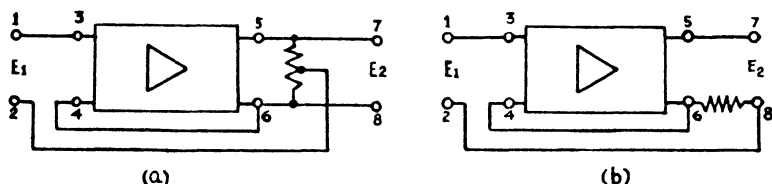


FIG. 432.—(a) Series voltage feedback ; input impedance increased ; output impedance reduced.
 (b) Series current feedback ; input impedance increased ; output impedance increased.

property of series feedback is that the input impedance is increased, no matter whether the feedback depends on the voltage or current in the anode load or both. This latter consideration affects only the output impedance (see Fig. 432a and b).

There are two standard methods of applying the feedback in series with the incoming signal. These are shown in Fig. 433a and b.

In general, method (a) can be adopted only when a transformer input circuit is employed. Method (b) is used only in conjunction with an indirectly heated valve ; single-stage current negative feedback also will automatically be applied to V_1 , since no decoupling condenser can be connected across R_a .

It should be noted that a voltage applied to a resistance R in the grid circuit Fig. 433a will apply, between the grid and cathode of the valve, a signal that is 180° out of phase with that obtained when the voltage is applied to a resistance R_a in the cathode circuit Fig. 433b. Hence if the feedback obtained in (a) is negative, that obtained in (b) will be positive, and *vice versa*.

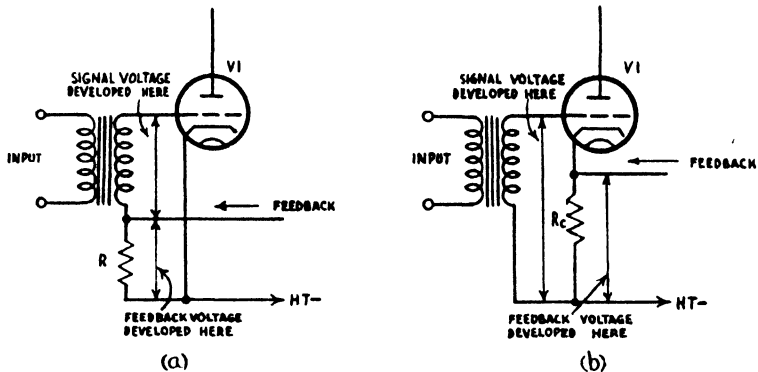


FIG. 433.—Methods of applying series voltage feedback.
 (a) Voltage developed across resistor in grid circuit.
 (b) Voltage developed across cathode resistor.

If method (b) is to be applied to a pentode valve, the screen grid should be decoupled to the cathode, as in Fig. 434, and not to HT —, as is the usual practice. This is to prevent alternating components of the screen current from flowing through R_c .

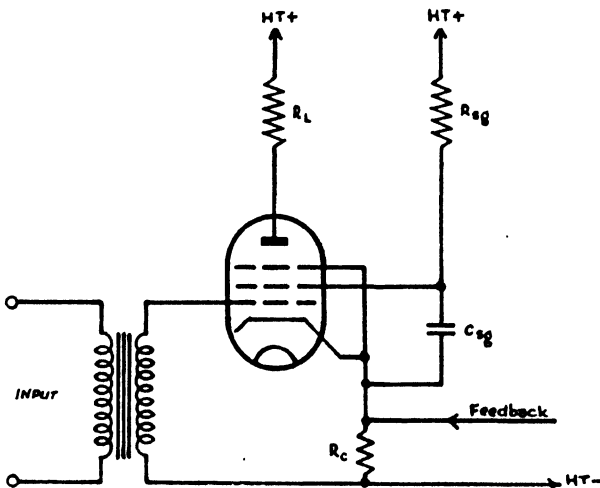


FIG. 434.—Voltage developed across cathode resistor. Note screen decoupled to cathode.

Input impedance with series feedback

To prevent either the accumulation of electrons (grid —) or the loss of electrons due to secondary emission (grid +), there must always be a conducting path between grid and cathode of resistance less than a certain value. This value depends on the particular valve (e.g. about $2M\Omega$ for a high slope pentode, or $250k\Omega$ for an

output pentode or beam tetrode). If this resistance lowers the input impedance Z to a value too low for the particular application, Z may be increased by the application of a series negative feedback circuit. Fig. 435 shows an amplifier having an input impedance of $10M\Omega$ although the value of the grid leak resistor is only $2M\Omega$.

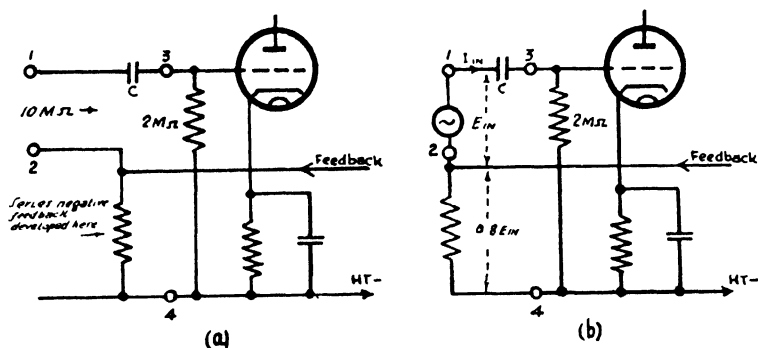


FIG. 435.—Example of the effect of series negative feedback on the input impedance of an amplifier.

This may be seen very simply by applying a voltage E_{IN} to the input terminals 1, 2. Let the input current be I_{IN} , so that the input impedance $Z_{IN} = \frac{E_{IN}}{I_{IN}}$. Owing to the application of E_{IN} , let the negative feedback produce a voltage $0.8 E_{IN}$ in opposition to E_{IN} (see Fig. 435b). Consider circuit 1, 2, 4, 3.

$$I_{IN} = \frac{E_{IN} - 0.8 E_{IN}}{2.10^6} = \frac{0.2 E_{IN}}{2.10^6}$$

(assuming the input impedance of the valve itself to be infinite and the reactance of C to be very small at the frequency considered).

Hence
$$Z_{IN} = \frac{E_{IN}}{I_{IN}} = \frac{2.10^6}{0.2} = 10 M\Omega.$$

Parallel negative feedback

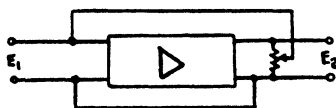


FIG. 436.—Parallel voltage feedback ; input impedance reduced ; output impedance reduced.

An alternative method of applying feedback is in parallel with the incoming signal. This has the effect of decreasing the input impedance. Once again the signal fed back may depend on either the voltage or the current in the anode load, or on both, and this

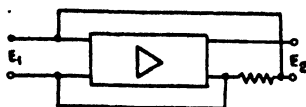


FIG. 437.—Parallel current feedback ; input impedance reduced ; output impedance increased.

will determine the output impedance. The input impedance is decreased in all cases of parallel feedback.

The general properties of negative feedback, such as the reduction in gain for a given value of β , the reduction in distortion, *etc.*, are independent of whether the feedback is series, parallel, current or voltage.

Input impedance with parallel negative feedback

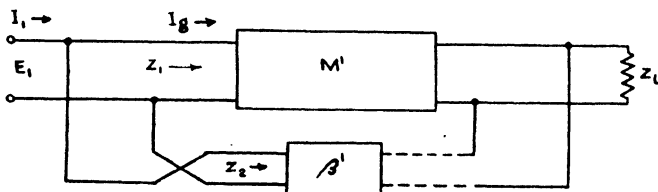


FIG. 438.—Effect of parallel negative feedback on the input impedance of an amplifier.

Let M' be the current gain of the amplifier ; let the input impedance of the amplifier without feedback be Z_1 ; let a fraction β' of the output current be fed back, and let the impedance of the β' network be Z_2 .

Hence total input impedance Z without feedback is $Z = \frac{Z_1 Z_2}{Z_1 + Z_2}$.

With feedback, a fraction β' of the output current is fed back into the input in opposition to the incoming signal.

If current I_o flows into the amplifier, output current $= M' I_o$,
 \therefore the current fed back $= \beta' M' I_o$.

Since negative feedback is applied,

$$\frac{Z_2}{Z_1 + Z_2} I_1 - \beta' M' I_o = I_o$$

$$\therefore I_1 = \frac{Z_1 + Z_2}{Z_2} \cdot I_o (1 + \beta' M')$$

Voltage across input terminals $E_1 = I_o \cdot Z_1$

$$\text{Input impedance} = \frac{E_1}{I_1} = \frac{Z_1 I_o}{I_1} = \frac{Z_1 Z_2}{Z_1 + Z_2} \cdot \frac{1}{1 + \beta' M'}$$

where $\beta'M'$ is the current gain round the loop path.

By breaking the loop path at a resistive point, it will be seen that the current loop gain is equal to the voltage loop gain βM .

$$\text{Hence the input impedance} = \frac{Z_1 Z_2}{Z_1 + Z_2} \cdot \frac{1}{1 + \beta M}$$

Thus parallel feedback reduces the input impedance in accordance with the relation :—

$$\text{Input impedance with parallel feedback} = \frac{\text{Input impedance without feedback}}{1 + \beta M}$$

where βM is the voltage loop gain.

Combined series and parallel feedback

If series and parallel feedback are applied simultaneously, the amplifier can be given any desired input impedance, and this impedance can be made independent of the input impedance of

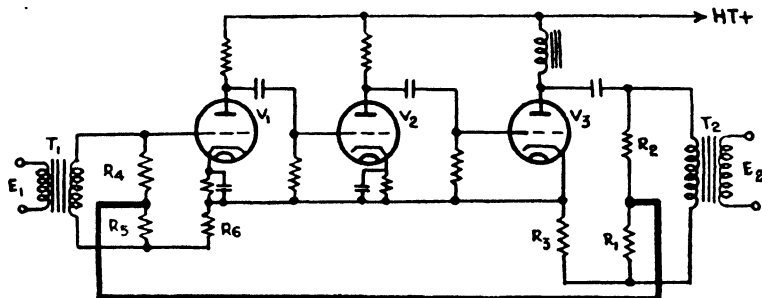


FIG. 439.—Multi-stage amplifier with combined series and parallel negative feedback.

the first valve. If this feature is combined with current and voltage feedback (composite feedback) in the output circuit, the amplifier can be given not only the desired input impedance, but also the desired output impedance. Fig. 439 shows a typical three-stage amplifier embodying both series and parallel, and current and voltage, negative feedback, applied over all three stages.

THE CATHODE FOLLOWER

In certain cases where an amplifier is required having a very high input impedance and a very low output impedance, a cathode follower circuit is employed. This is really a special case of the application of series voltage negative feedback to a single-stage amplifier. The circuit is shown in Fig. 440, and it will be noted that the load is in the cathode circuit so that the entire voltage developed across the load is fed back to the input in opposition to the incoming signal. β is therefore equal to unity, and there is always an overall loss instead of a gain. This may be verified as follows :—

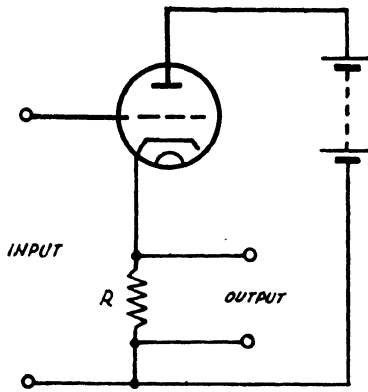


FIG. 440.—The cathode follower.

Let R_s = AC resistance of the valve.

μ = amplification factor of the valve.

The gain M without feedback is:—

$$M = \frac{\mu R}{R_s + R}$$

The gain M_o with feedback is:—

$$M_o = \frac{M}{1 + \beta M} = \frac{M}{1 + M}, \text{ since } \beta = 1.$$

Hence

$$M_o = \frac{\frac{\mu R}{R_s + R}}{1 + \frac{\mu R}{R_s + R}}$$

$$\therefore M_o = \frac{\mu R}{R_s + (1 + \mu) R} \quad (38)$$

Since $R_s + (1 + \mu)R$ must always be greater than μR , it follows from equation 38 that M_o is always less than 1.

Output impedance.—Owing to the application of voltage negative feedback, the valve behaves as if its AC resistance has been reduced

to $R_s' = \frac{R_s}{1 + \beta \mu} = \frac{R_s}{1 + \mu}$, since $\beta = 1$. The output impedance will be equal to R in parallel with R_s' , i.e. :—

$$\text{Output impedance} = \frac{R \cdot R_s}{R_s + (1 + \mu) R} = \frac{M_o}{g}$$

where g is the mutual conductance of the valve in question.

Example.—

A valve having the following constants is used in a cathode follower circuit working into a 5000-ohm load. Find the gain and output impedance.

$$R_s = 15,000 \Omega$$

$$\mu = 29$$

$$\text{Gain} = \frac{\mu R}{R_s + (1 + \mu)R} = \frac{29 \times 5000}{15,000 + 30 \times 5000} = 0.88$$

$$\text{Output impedance} = \frac{R \cdot R_s}{R_s + (1 + \mu)R} = \frac{5000 \times 15,000}{15,000 + 30 \cdot 5000} = 455 \Omega.$$

INSTABILITY IN NEGATIVE FEEDBACK AMPLIFIERS

Consider a feedback amplifier having a gain without feedback of $M = |M| \angle \theta$. Let the feedback factor be β . So far, it has been seen that oscillations may occur if *positive* feedback is applied with $\beta|M| > 1$ and $\theta = 0^\circ$. A negative feedback amplifier appears, at first sight, to be stable for all values of βM . However, when θ reaches $\pm \pi$ the feedback will no longer be negative but positive, since

$$\beta|M|, \angle \pm \pi = -\beta|M|, \angle 0^\circ.$$

The change in sign of β indicates a change from negative to positive feedback. Thus if the loop gain $\beta|M|$ at the frequency or frequencies at which the loop phase-shift reaches $\pm \pi$ is equal to or exceeds 1, oscillations will, in all probability, occur. The frequency at which oscillation occurs will be that for which the absolute phase-shift round the loop is zero, the circuit adjusting itself to make βM exactly equal to 1, $\angle 0^\circ$.

Consider a negative feedback amplifier having gain-frequency and phase-shift-frequency characteristics as in Figs. 441 and 442.

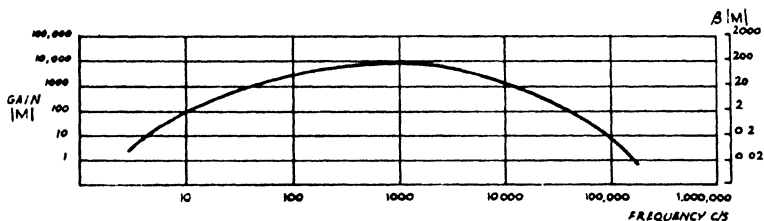


FIG. 441.—Variation of gain with frequency.

Assume that the feedback path introduces no phase-shift, and that β is independent of frequency and equal to $\frac{1}{50}$.

Let the gain of amplifier without feedback be $|M|, \angle \theta$.

At 1000 c/s the phase-shift = 0, and pure negative feedback is applied.

At 10 c/s and at 100,000 c/s, θ has reached $+\pi$ and $-\pi$ respectively. These are known as the " π " frequencies of the amplifier. At these frequencies the feedback has become purely positive feedback; but even though positive feedback is now being applied, oscillations will occur only if βM is greater than or equal to 1.

At 10 c/s, $\beta = \frac{1}{50}$; $M = 100$; $\beta M = 2$ — unstable.

At 100,000 c/s, $\beta = \frac{1}{50}$; $M = 10$; $\beta M = \frac{1}{5}$ — stable.

Hence the amplifier will tend to oscillate at the lower π frequency, *i.e.* 10 c/s.

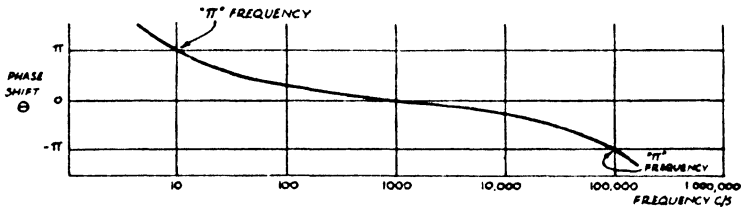


FIG. 442.—Variation of phase-shift with frequency.

To obtain full benefit from negative feedback a large amount must be applied. The chief problem in applying a large amount of feedback to a multi-stage amplifier is thus one of stability. Provided that the loop phase-shift at the frequencies zero and infinity does not reach $\pm\pi$, the system can never be unstable, no matter how much negative feedback is applied; little difficulty is thus experienced over one- or two-stage amplifiers unless transformers are present in the feedback loop. With a multi-stage amplifier the loop phase-shift will probably reach $+\pi$ at some low frequency, and $-\pi$ at some high frequency. These " π " frequencies may be far outside the working range of the amplifier, but to make certain that instability does not occur it is essential to ensure that the gain $|M|$ at these frequencies is low enough to make $\beta|M|$ less than 1.

At first it seems that the simplest method of avoiding oscillation is to make certain that the amplifier gain falls off as rapidly as possible outside the working range, so that the value of M will be such as to make $\beta|M|$ less than 1 when the π frequencies are reached. Unfortunately such a drop-off in gain can be produced only by the inclusion of reactive components in the amplifier, and these components will increase the phase-shift. In fact, it can be shown that if this "cut-off" proceeds over an extended range at a rate greater than 12 db per octave (*i.e.* 4 to 1 drop in voltage gain as the frequency is doubled or halved) a phase-shift of π will be produced, and a " π " frequency reached. The design of modern feedback amplifiers is therefore concentrated on producing as rapid

as possible a fall-off in gain outside the working range, bearing this fact in mind. A decrease in gain of 10 db per octave is considered to allow ample margin for stability. Since resistance-capacity coupling in an amplifier introduces a change in gain that approaches asymptotically to 6 db/octave or a multiple of 6 db/octave, corrective networks must be used to give the required overall

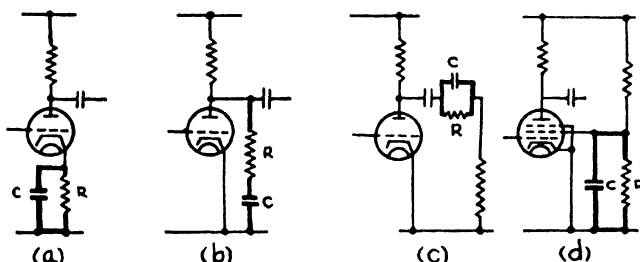


FIG. 443.—Corrective networks for stabilising NFB amplifiers.

response. Typical networks of this type are shown in Fig. 443, where the reactance of the condenser C is comparable with the resistance R at the frequencies considered.

Conditionally stable amplifiers

It may have been noted that, when referring to positive feedback, it was stated that when $\beta|M| > 1$, oscillations *may* occur, and not that they *will*. This is because it is possible to construct an amplifier for which the feedback is apparently positive and $\beta|M| > 1$, yet the amplifier is stable; although it becomes unstable if the value of $|M|$ drops. Such an amplifier is said to be "conditionally stable".

That such an amplifier is theoretically possible may be shown from the fact that the gain M_o of any feedback amplifier is:—

$$M_o = \frac{M}{1 - \beta M}$$

where β is positive in sign for positive feedback and negative in sign for negative feedback.

To be strictly accurate, both M and β should be considered as vector quantities, since not only M , but also β may introduce phase-shift.

$$\text{Let } M = |M| \angle \theta$$

$$\text{and } \beta = |\beta| \angle \psi$$

$$\text{Then } M_o = \frac{|M| \angle \theta}{1 - |\beta M| \angle \theta + \psi}$$

$$\text{and } |M_o| = \frac{|M|}{|1 - \beta M|}$$

Consider the cases where the loop phase-shift is zero.

$|1 - \beta M| < 1$ —Increased gain

$|1 - \beta M|$ being less than 1 means that β must be positive and βM must lie between 0 and 2 if the loop phase-shift is zero.

$|1 - \beta M| > 1$ —Decreased gain

$|1 - \beta M|$ being greater than 1 means that either β can be negative and $|\beta M|$ can have any value, or β can be positive and $|\beta M|$ can be greater than 2.

In the general case where the loop gain βM will introduce a phase-shift $\angle \theta + \psi$, the gain will be decreased if $+\beta M$ plotted in a complex plane lies outside the circle of unit radius and centre $+1 + j0$, and will be increased if βM lies inside the circle.

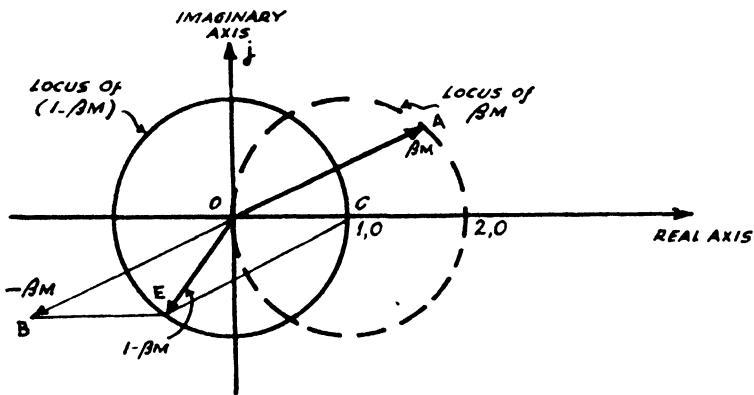


FIG. 444.—Feedback circle diagram.

This is shown in Fig. 444, where OA represents the vector βM , and OB represents $-\beta M$. OB is then added to the vector OC which represents $+1$ to give the resultant vector OE , so that:—

$$\begin{aligned}\vec{OE} &= \vec{OC} + \vec{OB} \\ &= +1 + (-\beta M) \\ &= 1 - \beta M\end{aligned}$$

If $|1 - \beta M|$ is equal to 1, the point E must lie on the circle of centre O and radius 1; it can easily be shown that the point A must therefore lie on a circle of centre C and radius 1.

For $OCEB$ is a parallelogram,

$$\therefore EC = BO \text{ and } EC \text{ is parallel to } BO.$$

But BOA is a straight line, and $OA = OB$,

$$\therefore EC = OA \text{ and } EC \text{ is parallel to } OA.$$

$$\therefore OECA \text{ is a parallelogram.}$$

$$\therefore CA = OE = 1.$$

Although from this graph the effect of feedback on gain can be determined, no indication is given as to whether instability will occur.

Nyquist's condition for oscillation

Nyquist's condition for oscillation due to the application of positive feedback states:—

Let the locus of βM be plotted in a complex plane for frequencies from 0 to ∞ : then if the locus encloses the point $[1, 0]$, oscillations will occur. If not, no matter what may be the absolute value of $|\beta M|$, oscillations will not occur.

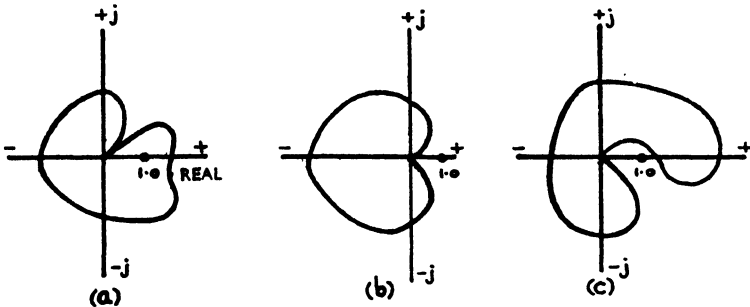


FIG. 445.—Locus of βM for (a) unstable, (b) stable, and (c) conditionally stable amplifiers.

Hence in Fig. 445 the amplifier (a) is unstable, (b) is stable, (c) is conditionally stable.

Thus the only certain method of determining whether oscillations will occur, particularly in a doubtful case, is to plot the locus of $|\beta M| \angle \theta + \psi$, and to see whether the point $[1, 0]$ is included. Alternatively, oscillations may be prevented by ensuring that $|\beta M|$ is less than 1 when $\angle \theta + \psi$ reaches $+\pi$ or $-\pi$.

APPLICATION OF NEGATIVE FEEDBACK TO LINE COMMUNICATION EQUIPMENT

Negative feedback is applied to the amplifiers employed in line communication equipment to stabilise the gain, to give the correct output impedance, to reduce distortion, and to give the required gain-frequency response.

It is essential in line equipment to prevent changes in gain due to power supply voltage variations, changes of valves, etc. This is very important in, for example, the case of the repeaters employed on long circuits, where a change in gain of a few db at each repeater station might result in such a large overall change in gain that the circuit would become unworkable.

With regard to obtaining the correct output impedance, two methods are adopted. The first method is to apply composite negative feedback, and this is adjusted to give not only the correct reduction in gain, but also the required output impedance. The

second method is to apply current negative feedback only. This, in itself, will give a very high output impedance, and, in order to obtain the correct impedance a shunting resistance is placed across the output. A loss of power will result, but an output impedance substantially independent of the AC resistance of the last stage will be obtained.

A particular case is that of an amplifier being used to drive a loudspeaker. Only voltage feedback is generally applied so as to provide a low output impedance to damp the resonance of the speaker.

Series (and not parallel) feedback is the form of feedback most frequently used. This tends to give the amplifiers a high input impedance and necessitates the use of an input transformer and shunting resistance to obtain the required input impedance.

In the case of carrier telephone and VF telegraph repeaters, where several bands of frequencies are amplified simultaneously by one amplifier, it is essential to reduce distortion to an absolute minimum to prevent intermodulation between the channels. Negative feedback enables this low overall distortion to be obtained in an amplifier having a high gain and high output power. It is no exaggeration to say that negative feedback has made possible the wide-band carrier systems in which several hundred channels, covering a frequency band extending up to several megacycles/sec, are all amplified simultaneously by a single amplifier without undue intermodulation.

With regard to response curves, feedback is used either with β independent of frequency to give the amplifier a flat frequency response curve over a large frequency range, or with β a function of frequency, so as to provide the required gain-frequency curve to match, say, the attenuation of the line (see Chapter 23, "Equalisers").

CHAPTER 10

OSCILLATORS

Under the general heading of oscillators may be grouped all devices that provide an alternating output, whilst deriving their input from a direct current source, without changing their circuit configuration by means of switching ; this proviso excludes rotating machinery (whose commutators act as switches), and buzzers, vibrators, etc. The frequency at the output may be fixed, adjustable in steps, or continuously variable.

Oscillators fall into two main classes ; those of the first and most common class have an output waveform that is sinusoidal ; those of the second class, called "relaxation" oscillators, are designed to give an output with a large harmonic content. Oscillators of the first type, which produce a sinusoidal output, can be further subdivided according to their principles of operation ; for although the majority of oscillators employ thermionic valves, they do not all use them in the same way. The only oscillator of the second class that will be considered in this chapter is the "multivibrator". Oscillators producing saw-tooth waveforms suitable for the time-bases of cathode ray oscilloscopes will be found in Chapter 12.

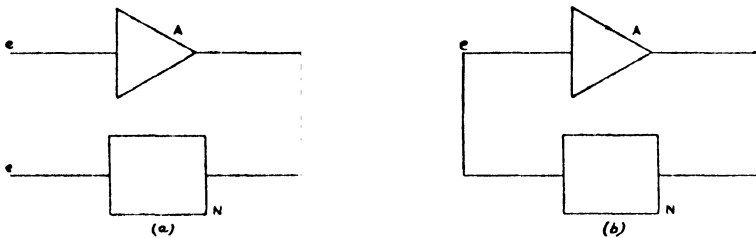


FIG. 446.—Illustrating the basic principle of a feedback oscillator.

The basic principle of most valve oscillators is as follows. Fig. 446a shows an alternating voltage of instantaneous value e , and of some definite fixed frequency, applied to the input of an amplifier A . The amplifier output is applied to a network N . Now suppose that the loss of the network N and the gain of the amplifier A can be so adjusted, that the output voltage of the network is equal in *magnitude and phase* to the amplifier input voltage. If the output of the network is now connected directly to the input of the amplifier, as in Fig. 446b, the amplifier will continue to supply its own input, maintaining the original input voltage e at the original frequency.

Thus if an amplifier output, or part of the output, is fed back to the input, the system will oscillate at the frequency at which the feedback voltage is equal in magnitude and phase to the input voltage. It is evident that if an oscillator is required to oscillate at one particular frequency, it must incorporate some frequency-discriminating circuit either in the amplifier itself or in the feedback network.

Suppose that the stage gain of the amplifier is M ; that is, if the input voltage to the amplifier is e , the output voltage will be Me . Now suppose that the feedback network is such that the voltage fed back is a fraction β of the amplifier output voltage; that is, in the case considered, the voltage fed back to the amplifier input is βMe . The condition for maintenance of oscillation is therefore $\beta Me = e$, i.e. $\beta M = 1 \angle 0^\circ$; the angle $\angle 0^\circ$ is inserted as a reminder that the phase as well as the magnitude must be correct (see previous chapter). In a normal oscillator circuit this quantity βM is made slightly greater than unity; this, in theory, would give an oscillation of constantly increasing amplitude. In practice, however, due to the curvature of the dynamic characteristic of the valve employed the stage gain M drops slightly as the input voltage increases, and the circuit settles down to produce oscillations of magnitude such that $\beta M = 1 \angle 0^\circ$.

If initially βM is made much greater than unity, considerable overloading will have to occur before the stage gain drops to the value making $\beta M = 1 \angle 0^\circ$, and in this case the output waveform will be distorted. If a good sine-wave output is required, it is therefore important so to adjust the feedback that the circuit is only *just* oscillating.

L-C CIRCUIT OSCILLATORS

The simplest valve oscillators are those in which the output from a single-stage amplifier is fed back to its input, and in which the maintenance condition ($\beta M = 1$), and therefore the frequency of the resulting oscillations, is controlled by a resonant L-C circuit. It is important to bear in mind, that in a single-stage amplifier, a phase shift of 180° exists between grid and anode voltages. Hence if a single-stage oscillator is to be constructed, a further 180° phase-shift must be introduced into the feedback path. There are several ways of accomplishing this, the most common being the use of a transformer; other methods will be mentioned as they occur in the individual oscillator circuits.

Tuned-anode oscillator

In the tuned-anode oscillators shown in Fig. 447, a transformer is used to give the 180° phase-shift in the feedback. It is connected between anode and grid circuits, and to fix the frequency of oscillation the anode winding is tuned with a parallel condenser. The series- and parallel-fed circuits are equivalent, the advantage

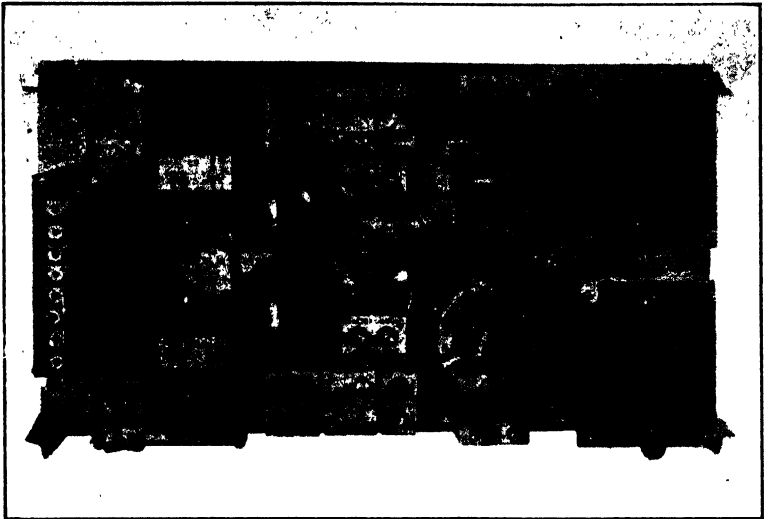


PLATE 25.—Single-stage parallel-fed tuned-anode L-C oscillators.

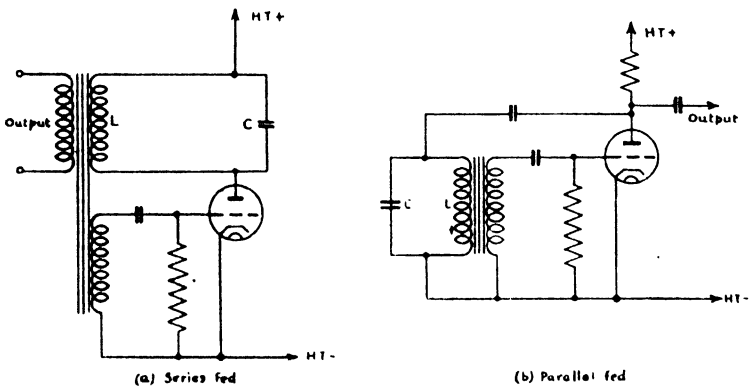


FIG. 447.—Tuned-anode oscillators.

of the parallel-fed circuit being that the anode winding of the transformer does not carry the standing anode current (see transformer-coupled amplifiers, p. 393).

The frequency of oscillation is approximately the resonant frequency of L and C , i.e. $f \approx \frac{1}{2\pi\sqrt{LC}}$. The condenser and resistance in the grid circuit constitute a grid leak bias circuit. The output of this, as of any other oscillator, may be taken off in a variety of ways—e.g. from a third winding on the transformer, *via* a condenser from the grid or anode, or from across a resistance between cathode and HT—.

Tuned-grid oscillator

Fig. 448 shows typical series- and parallel-fed tuned-grid oscillators. These are very similar to the tuned-anode oscillators already discussed, the only point of difference being that this time

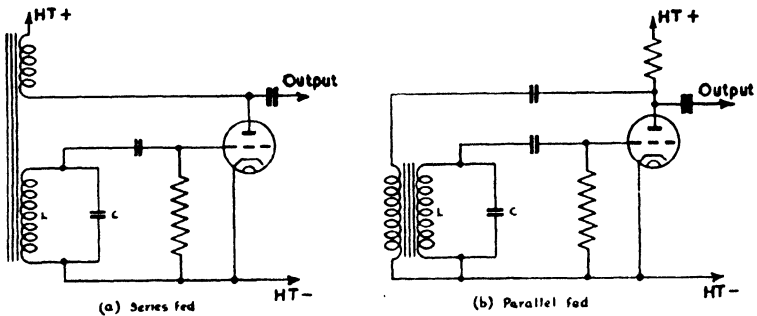


FIG. 448.—Tuned-grid oscillators.

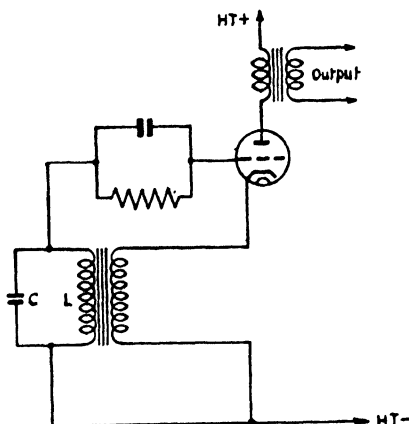


FIG. 449.—Tuned-grid oscillator employing feedback from cathode circuit.

the grid winding of the coupling transformer is tuned, instead of the anode winding. The frequency of the oscillator is again approximately the resonant frequency of L and C , i.e. $f \approx \frac{1}{2\pi\sqrt{LC}}$.

A modified tuned-grid oscillator is shown in Fig. 449. In this circuit, the feedback is from the cathode to the grid, instead of from the anode to the grid.

Hartley oscillator

In the Hartley oscillator, the tuned circuit is connected between grid and anode, and the cathode is connected to a tapping on the inductance; in this way a 180° phase change is introduced into

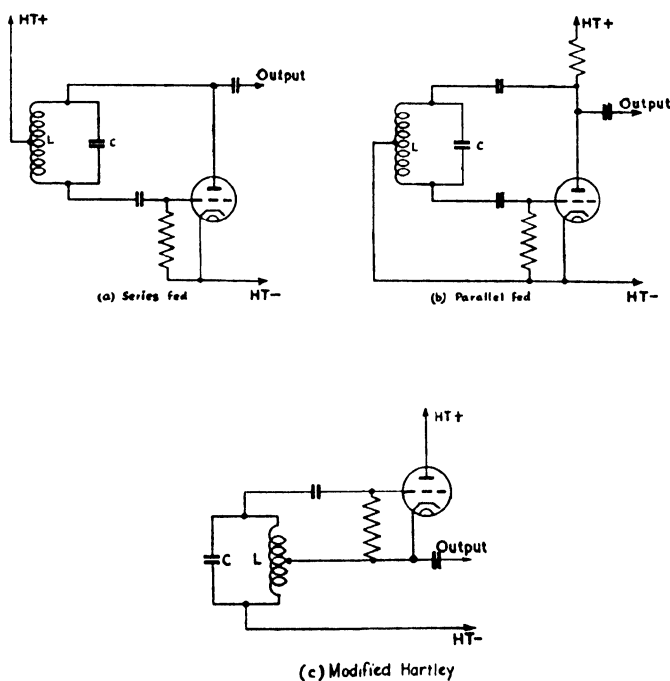


FIG. 450.—Hartley oscillators.

the feedback. In the normal Hartley oscillator, either series or parallel fed, the cathode is earthed (HT —). In the modified or "inverted" Hartley oscillator, the "anode end" of the inductance is earthed. The frequency is given by the relation $f \approx \frac{1}{2\pi\sqrt{LC}}$.

Colpitts oscillator

The Colpitts oscillator shown in Fig. 451 is similar to the shunt fed Hartley oscillator, except that the cathode is connected to an intermediate tapping on the *condenser* instead of on the *inductance*.

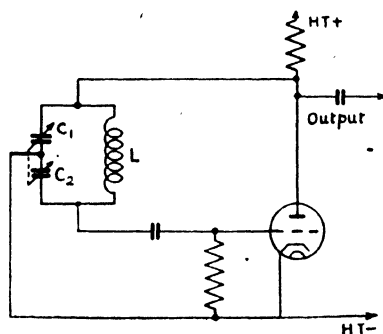


FIG. 451.—Colpitts oscillator.

The frequency is given by $f \approx \frac{1}{2\pi\sqrt{LC}}$, where C is the capacity of C_1 and C_2 in series.

Push-pull oscillator

Fig. 452 shows a simple push-pull oscillator. The operation of the circuit is as follows. Suppose the voltage across the tuned

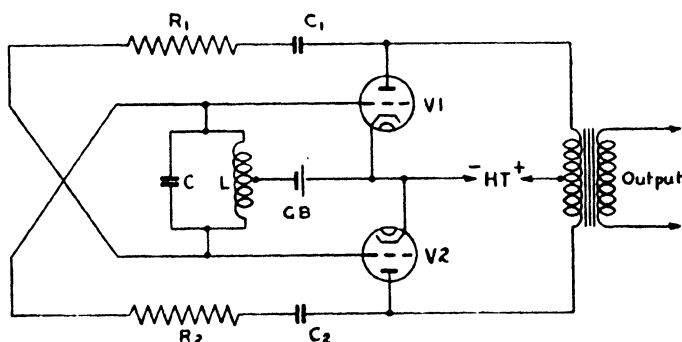


FIG. 452.—Simple push-pull oscillator.

circuit LC makes the grid of V_1 momentarily positive and therefore the grid of V_2 momentarily negative. This causes an increase in the anode current of V_1 and a decrease in that of V_2 , producing a finite resultant current in the primary of the output transformer. The anode potential of V_1 will decrease, and that of V_2 will rise, these changes being applied to the grids of V_2 and V_1 respectively *via* the feedback circuits R_1, C_1 and R_2, C_2 . Thus the feedback is

in the correct phase for the maintenance of oscillations, and the changes in the resultant current through the primary of the output transformer induce an alternating voltage in the output winding. The frequency of oscillation is approximately the resonant frequency of L and C , *i.e.* $f \approx \frac{1}{2\pi\sqrt{LC}}$.

This push-pull connection has the same advantages as the push-pull amplifier, namely a higher output can be obtained with practically no second harmonic distortion. For this reason triode valves are used, since the distortion produced in a triode is largely second harmonic, and thus in a push-pull connection the output is practically distortionless.

Grid bias

Grid leak bias is the method normally used in oscillators, and has been employed in the circuits so far considered. It has the advantage that before oscillations begin the valve is operating at the steepest part of its characteristic, giving the best starting conditions, *i.e.* maximum stage gain. When the oscillations have reached a steady value the bias will be just sufficient to prevent the grid running too far into the region of positive grid voltage.

The time constant of the bias circuit should be greater than the periodic time at the frequency of oscillation. If the time constant is too small, excessive grid current will flow on the positive half-cycle and will cause distortion; if on the other hand it is too large, "squegging" may occur as described below. Typical values are 0.5 M Ω and 0.01 μ F for a 500 c/s oscillator; *i.e.*, a time constant of 5 milli-seconds where the periodic time is 2 milli-seconds.

An oscillator employing this means of bias is, in general, self-starting and is capable of working satisfactorily over a wide range of values of the feedback voltage; it is therefore the easiest type of oscillator to construct, but has two main disadvantages. The first is that if for any reason the oscillator does not oscillate, the grid is not biased back, and the anode current may rise to a sufficiently high value to cause damage to the valve; to avoid this, an additional external bias is sometimes employed, usually in the form of cathode bias or battery bias. The second disadvantage is that the voltage output of such an oscillator is generally not constant. For this reason, where a constant output is essential, the bias is often provided externally, cathode bias or filament current bias being the usual methods employed.

It is worth noting that in the case of an oscillator employing grid leak bias, the anode current drops considerably when oscillation takes place; this property is sometimes used to discover whether a high frequency oscillator is operating or not.

Squegging

If the time constant of the grid bias circuit is too large, regular or irregular interruptions of the oscillations may occur. This is

most likely to happen if the feedback is greater than required, for in this case, initially $|\beta M| > 1$, and the oscillations increase rapidly in magnitude, each positive half-cycle increasing the grid bias voltage and reducing the effective stage gain. Eventually one positive half-cycle increases the bias to such a degree that $|\beta M| < 1$; if the time constant of the bias circuit is small, the bias voltage will drop during the next half-cycle to the point where $|\beta M| \geq 1$ and oscillations will be maintained. If, on the other hand, the time constant is large, the condition $|\beta M| < 1$ will persist, and the oscillations will rapidly die out. The valve will now be biased beyond cut-off, and oscillations will not recommence



FIG. 453.—Waveform of output from squegging oscillator.

until the bias condenser has discharged to the point at which anode current flows once more and $|\beta M| > 1$. The waveform of the output is as shown in Fig. 453.

Mathematical treatment

The frequency of the output and the maintenance condition for any oscillator may be calculated mathematically from the equivalent circuit. This method will be demonstrated by considering a special case—that of the tuned anode oscillator shown in Fig. 454.

In the equivalent circuit, the resistance R is the resultant resistive load on the circuit, and will be made up partly by the resistance of the windings and partly by the output load, all being referred to the anode winding. Let the alternating currents through L and C be x and y respectively, so that the total alternating anode current is $x + y$. If the flow of grid current is neglected:—

$$e_g = j\omega Mx \quad (1)$$

where M is the mutual inductance between the grid and anode windings. Now applying Kirchhoff's Law round the tuned circuit:—

$$x(R + j\omega L) + \frac{jy}{\omega C} = 0$$

$$\text{i.e.} \quad y = j\omega C(R + j\omega L) \cdot x \quad (2)$$

Also, applying Kirchhoff's Law round the complete circuit:—

$$\begin{aligned} x(R + j\omega L) + R_a(x + y) &= -\mu e_g \\ &= -j\mu\omega Mx \quad (\text{from equation 1}) \end{aligned}$$

Eliminate y using equation 2:—

$$x(R + R_a + j\omega L) + j\omega CR_a(R + j\omega L)x + j\mu\omega Mx = 0$$

$$\text{i.e.} \quad x[R + R_a - \omega^2 LCR_a + j\omega(L + CRR_a + \mu M)] = 0$$

If the circuit is oscillating, $x \neq 0$, and therefore the condition for oscillation is:—

$$R + R_a - \omega^2 LCR_a + j\omega(L + CRR_a + \mu M) = 0$$

i.e. $R + R_o - \omega^2 LCR_o = 0$ (3)

and $L + CRR_o + \mu M = 0$ (4)

The first of these conditions gives the frequency of oscillation, namely:—

$$\omega^2 = \frac{1 + \frac{R}{R_o}}{LC}$$

i.e. $f = \frac{1}{2\pi\sqrt{LC}} \cdot \sqrt{1 + \frac{R}{R_o}}$ (5)

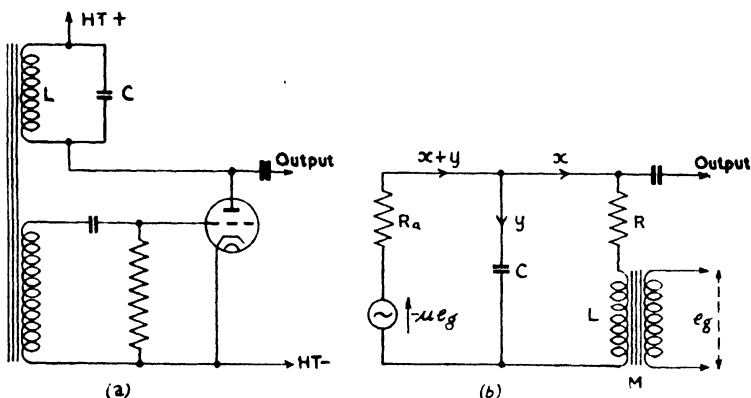


FIG. 454.—Tuned-anode oscillator with equivalent circuit.

Note that the frequency of oscillation depends on R_o and R , *i.e.* on the output load. If, however, $R \ll R_o$ (as is usual in practice, if the oscillator is not on load)

$$f = \frac{1}{2\pi\sqrt{LC}} \text{ c/s}$$

The second condition (equation 4) may be written:—

$$M = - \frac{L + CRR_o}{\mu} \text{ henries} \quad (6)$$

and gives what is called the "maintenance condition". The fact that M takes a negative value merely shows that the transformer must be so connected as to give 180° phase-shift between anode and grid.

OSCILLATOR STABILITY

For most purposes, it is of great importance that the frequency and the output voltage of an oscillator shall be stable—that is, that they should remain constant at the values to which they are adjusted. The factors on which stability depends, and means of ensuring it, will now be considered.

Frequency stability

Taking the example of the tuned-anode oscillator investigated above, the frequency is given by :—

$$f = \frac{1}{2\pi\sqrt{LC}} \cdot \sqrt{1 + \frac{R}{R_0}}$$

and it has been seen that, if $R \ll R_0$, this reduces to

$$f = \frac{1}{2\pi\sqrt{LC}}$$

In this case the frequency depends only upon the constants of the tuned circuit. Valve capacities must be included in the value of C , but these are normally constant.

Effect of temperature

It was shown in the last paragraph that the oscillator frequency was determined almost entirely by the components forming the tuned circuit. If the oscillator frequency is to remain constant for variations in temperature, it is important to ensure that the values of L and C do not vary.

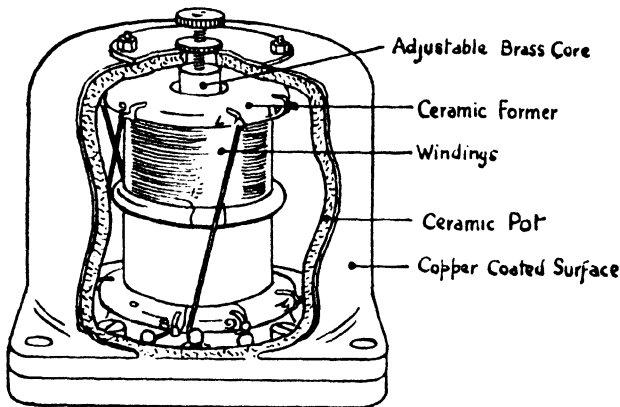


FIG. 455.—Typical inductance having high temperature-stability.

With good condensers, the effect of temperature on C is very small. Condensers can be designed to have almost any desired capacity-temperature characteristic; they can be so made that the capacity will increase, decrease, or remain constant with changes in temperature. Inductances, on the other hand, are more susceptible to temperature changes, as expansion will alter the inductance. Compensation is therefore required to ensure that the inductance has a small temperature coefficient. In addition, to prevent permanent changes in inductance, the former on which the coil is wound should have the same coefficient of expansion as the wire of the coil. If screening is employed, it must be so arranged that the change in its effect on the inductance of the coil

with temperature is negligible. Fig. 455 shows an inductance wound on a ceramic former, having a low coefficient of expansion, and screened by means of a copper-sprayed ceramic pot. Such an inductance has good frequency stability.

Resistance stabilisation

Now consider the oscillator working into a load. In this case, the condition $R \ll R_s$ no longer holds, and the frequency depends on R and on R_s , that is, on the load and on the valve constants; the frequency thus varies with a change of supply voltage. This state of affairs is undesirable, and can be minimised by using parallel feed through a large resistance, which has the effect of increasing artificially the value of R_s .

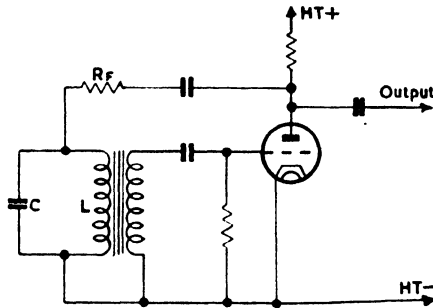


FIG. 456.—Tuned anode oscillator, parallel fed, with feedback resistance to improve frequency stability.

Fig. 456 shows a typical parallel fed tuned anode circuit utilising a feedback resistance R_f . This resistance has also the advantage of giving a fine control over the amount of feedback. The feedback resistance R_f must be large compared with R_s and R_L in parallel, where R_L is the load impedance in the anode circuit. Note that although variations of output load may now have little effect on frequency, they may still have a considerable effect on the maintenance condition for oscillation.

Buffer amplifier

The most satisfactory way of ensuring a high degree of frequency stability in an oscillator is, however, to use another valve as an amplifier stage following the oscillator. Such an amplifier is known as a "buffer" amplifier; and, since the oscillator works straight into the grid circuit of the buffer amplifier, the load on the oscillator is negligible and the frequency stability is high.

A typical circuit is shown in Fig. 457.

Note that in this case the tuned circuit, parallel-fed from the anode of the first valve, forms the grid circuit of the second valve.

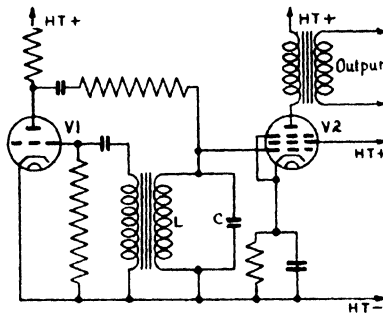


FIG. 457.—Oscillator with buffer amplifier, giving high frequency stability.

Electron-coupled oscillators

An electron-coupled oscillator, an example of which is shown in Fig. 458, although employing only one valve, is equivalent to an oscillator followed by a buffer amplifier, and has the same high frequency stability.

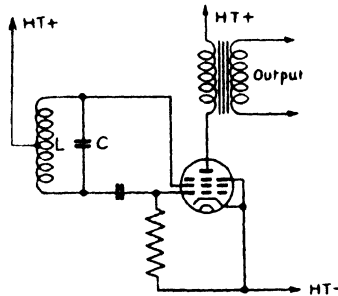


FIG. 458.—Electron-coupled Hartley oscillator.

The valve used is either a tetrode or a pentode, and the screen is used as the "anode" of the oscillator; thus in Fig. 458 the screen, the grid and the cathode are connected up in the form of a series-fed Hartley oscillator. Changes in anode load (within certain limits) have no effect on screen current and hence the load does not affect the oscillator circuit. On the other hand the oscillating voltage between cathode and grid affects the anode current; since the output is taken from the anode circuit, the valve behaves as its own buffer amplifier.

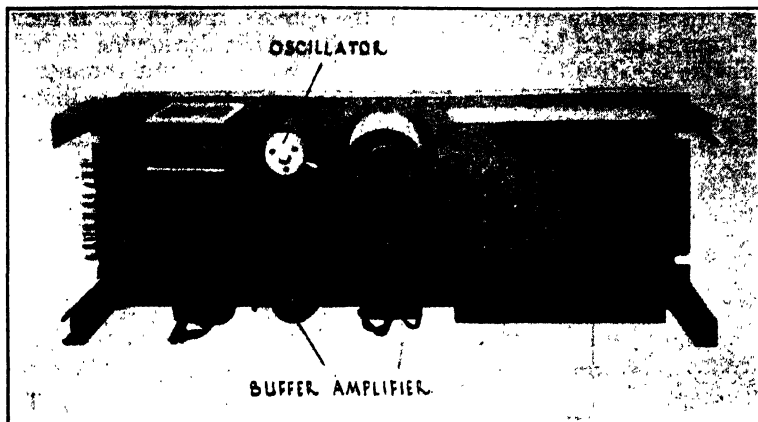


PLATE 26.—Electron-coupled tuned-grid oscillator employing an additional buffer amplifier.

Output voltage

There are two main factors that affect the output voltage of a valve oscillator—namely, the HT supply voltage and the amount of feedback. Variations of the former produce approximately proportional variations in output voltage. The output is also increased if the amount of feedback is increased, though this will also result in increased distortion. It is never possible to forecast accurately the output voltage of an oscillator. If, however, the feedback is so adjusted that oscillation only just takes place, the output voltage will rise to the point where the valve characteristics cease to be linear, due either to cut-off at the bottom end or to saturation or grid current at the top. If *fixed* bias is used, and is so adjusted that grid current flows on a smaller grid swing than that required to cut the valve off, the peak value of alternating voltage on the grid will normally just equal the fixed bias voltage; for if the grid swing increases beyond this point, grid current will flow and the circuit will be heavily damped, thereby reducing the grid swing. It is important to remember that, although an oscillator valve may be operating under conditions that would normally produce enormous distortion, the voltage across the tuned circuit may be almost sinusoidal, due to its impedance being small at all other frequencies.

Stabilisation of output voltage

The variations of output voltage with supply voltage may be minimised by the insertion in the circuit of some form of non-linear

resistance. A tungsten filament lamp, for instance, has a resistance that rises rapidly with increase in the current through it. If such a lamp is placed in the cathode circuit without decoupling, it will provide negative feedback that increases as the current through it increases (see Fig. 459, which shows the carrier-frequency oscillator of a single-channel carrier telephone system).

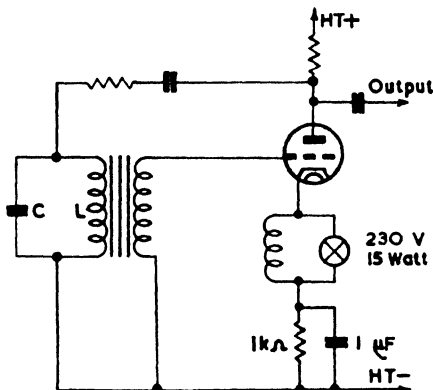


Fig. 459.—Carrier-frequency oscillator, showing tungsten-filament lamp for stabilising output voltage.

The inductance in parallel with the lamp carries most of the DC cathode current, whilst forming a negligible shunt on the lamp at the oscillator frequency. An increase in output, consequent upon an increase in HT supply voltage, therefore increases the alternating current in the lamp. This results in an increase in the lamp resistance, an increase in the amount of current negative feedback, and a reduction in the stage gain, thus stabilising the output voltage.

Neon stabiliser

Another method of stabilising the voltage output is shown in Fig. 460. This method gives better stabilisation than the last

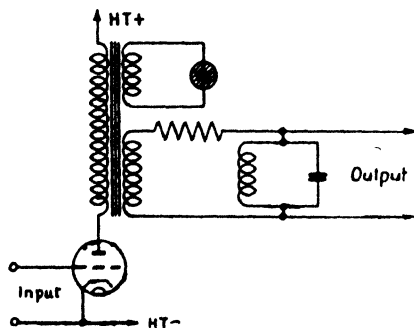


Fig. 460.—Neon stabiliser.

and is used when a stable output voltage is essential, *e.g.* the pilot oscillator on certain carrier telephone systems. The oscillator output, obtained *via* a buffer amplifier, has a neon stabiliser connected across it. This consists of a neon tube connected across a third winding of the output transformer. The neon lamp "flashes over" and offers a low impedance when the voltage across it exceeds a certain value. This value is exceeded by the peaks of the output waveform, which are therefore cut off. The distortion introduced by this method is eliminated by a tuned circuit following the stabiliser, as shown in Fig. 460.

Lamp bridge stabilisation

Another type of oscillator makes use of the properties of a lamp bridge to obtain constant output. As explained in Chapter 5, the lamp bridge consists of a Wheatstone bridge made up with a tungsten filament lamp in one arm and fixed resistances in the

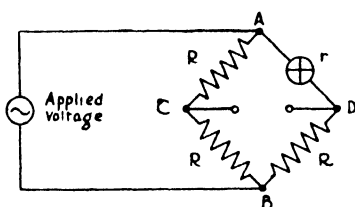


FIG. 461.—Basic circuit of lamp bridge stabiliser.

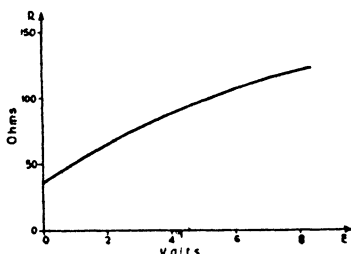


FIG. 462.—Variation of resistance with applied voltage for a 6-volt tungsten-filament switch-board indicator lamp.


other three (*see* Fig. 461). The resistance of the lamp varies with the voltage across it (*see* Fig. 462), and hence with the voltage across the bridge.

By a suitable choice of components, the bridge can be made to balance at one particular value of applied voltage, the balance being independent of frequency. Consider the positive half-cycle of an applied voltage, such as to make point *A* positive with respect to point *B*. If the applied voltage is less than that required for balance, the resistance of the lamp will be smaller than the value required for balance. Since the resistance of the lamp is now less than *R*, point *D* will be at a higher potential than point *C*, and current will flow in the output in the direction as shown in Fig. 463*a*.

If, on the other hand, the applied voltage is greater than the value required for balance, the resistance of the lamp will be greater than *R*, point *C* will be at a higher potential than point *D*, and current will flow in the output in the reverse direction, as shown in Fig. 463*b*.

It will be seen that the bridge introduces a phase-shift of 180° in

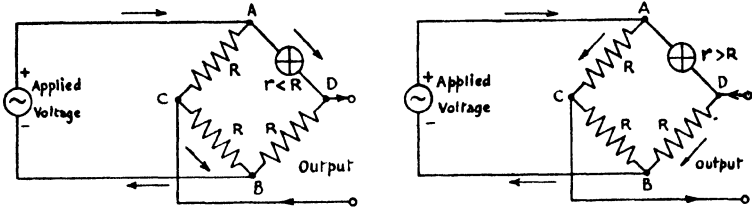the output as the applied voltage increases through the value required for balance. This effect takes place for both DC and audio-frequency voltages. The bridge is inserted in the feedback path of an oscillator in such a way as to make the feedback positive if the output voltage is below the critical value, and negative if



(a) Applied voltage less than that required for balance. (b) Applied voltage greater than that required for balance.

FIG. 463.—Lamp bridge, showing phase relationship between input and output on either side of balance condition.

above. On switching on, the lamp is cold, and oscillations are built up since positive feedback is being applied. The oscillations will increase in amplitude until the output voltage is just below the value required to balance the bridge, and the output will be stabilised at this value. Fig. 464 gives an example of this type of oscillator.

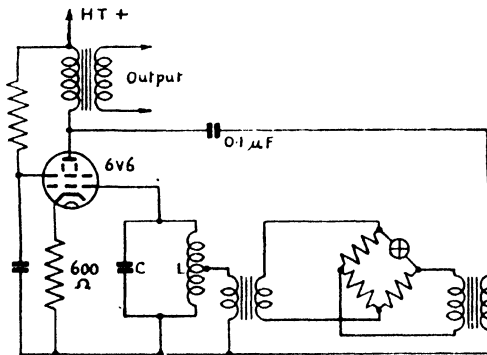


FIG. 464.—Oscillator with lamp bridge stabilisation.

NEGATIVE-RESISTANCE OSCILLATORS

Consider the circuit of Fig. 465 ; a resistance r is connected across a parallel tuned circuit. Let the currents in the various parts of the network be as shown ; then considering the steady state only and applying Kirchoff's Laws :—

$$r(x + y) - y \cdot \frac{j}{\omega C} = 0$$

$$\therefore \quad rx = -y \left(r - \frac{j}{\omega C} \right) \tag{7}$$

and $r(x + y) + x(R + j\omega L) = 0$
i.e. $ry = -x(r + R + j\omega L)$ (8)

Multiplying equation 7 by equation 8 :—

$$r^2xy = xy \left(r - \frac{j}{\omega C} \right) (r + R + j\omega L)$$

i.e. $xy \left[rR + j\omega Lr - j \frac{r}{\omega C} - j \frac{R}{\omega C} + \frac{L}{C} \right] = 0$

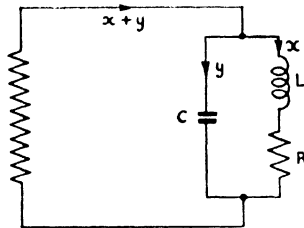


FIG. 465.—Illustrating the principle of the negative resistance oscillator.

If the circuit is oscillating, $xy \neq 0$, and the condition for oscillation is therefore :—

$$rR + \frac{L}{C} + j \left(\omega Lr - \frac{r+R}{\omega C} \right) = 0 \tag{9}$$

This gives the *maintenance condition* :—

$$rR + \frac{L}{C} = 0$$

i.e. $r = -\frac{L}{CR}$ (10)

and the frequency is given by :—

$$\omega Lr - \frac{r+R}{\omega C} = 0$$

i.e. $\omega^2 = \frac{1 + \frac{R}{r}}{LC}$

Hence, using equation 10 :—

$$\omega^2 = \frac{1 - \frac{R^2C}{L}}{LC}$$

i.e. $\omega^2 = \frac{1}{LC} - \frac{R^2}{L^2}$

$$\text{or} \quad = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} \quad (11)$$

Therefore, if a negative resistance equal to $-\frac{L}{CR}$ is connected across a parallel tuned circuit, oscillations will be maintained at the resonant frequency of the tuned circuit.

Negative resistances may be obtained in a number of ways, and three methods using a thermionic valve will be discussed in some detail. It is worth mentioning that a carbon arc has a negative resistance, and this was the basis of the earliest radio-frequency oscillators used in the "spark" transmitters.

The dynatron oscillator

The dynatron oscillator uses a tetrode valve to provide negative resistance. As has been explained in Chapter 7, the anode characteristic of a screen-grid valve has a region of negative slope

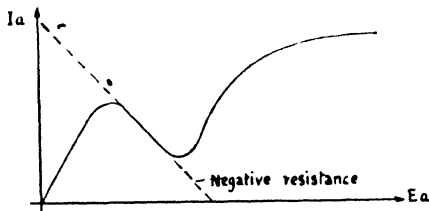


FIG. 466.—Anode characteristic of a tetrode, showing negative resistance.

(see Fig. 466). This means that an increase in anode voltage in this region produces a decrease in anode current; in other words the AC resistance R_a is negative in this region. This region occurs when the anode potential is slightly less than the screen potential.

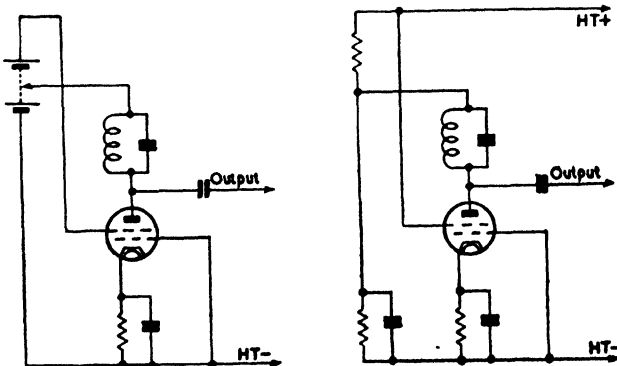


FIG. 467.—Dynatron oscillator
(a) with tap on battery
(b) with potential divider.

Fig. 467 shows a simple dynatron oscillator. The main advantage of this type of oscillator is that, provided the negative resistance is of such a value that oscillations only just take place, the frequency stability is very high. The value of negative resistance can be adjusted by varying the bias on the grid. The reason for the good frequency stability is that the only valve characteristic likely to affect the frequency of oscillation is the anode-cathode capacity. This capacity is initially very small, and the effect of any change in it due to electrode expansion will be negligible. There is, in addition, no variable coupling factor between the anode and grid circuits, as exists in the oscillators so far discussed.

The transitron oscillator

A pentode valve may be used as a negative-resistance device. If the suppressor grid of a pentode is driven positive, there is little change in the electrostatic field near the cathode, and so no appreciable change in the total space current; the anode current, however, increases, and the screen current drops. If the suppressor grid is connected to the screen *via* a condenser C' , as shown in Fig. 468, there will be a negative AC resistance between the screen and earth.

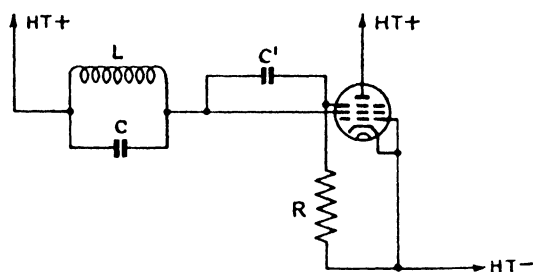


FIG. 468.—Illustrating the principle of the transitron oscillator.

This may be seen from the fact that, if an alternating voltage is applied to the screen, on the positive half-cycle the screen potential will rise; so also will that of the suppressor, since they are coupled by condenser C' , and this will cause the screen current to drop, since the suppressor potential has a greater effect than the screen potential on the screen current. A rise in screen potential thus corresponds to a drop in screen current. On the negative half-cycle, the potential of the screen will drop, and the screen current will rise.

A parallel tuned circuit in the screen lead will therefore oscillate, being in series with a negative resistance. This is known as a transitron oscillator, and it has the same high degree of frequency stability as the dynatron type. Fig. 469 shows a typical transitron oscillator circuit. The negative resistance is controlled by means of the resistance R_1 in the suppressor circuit. A typical value for R_1 would be of the order of 25 k Ω , and this resistor is adjusted until the circuit just oscillates.

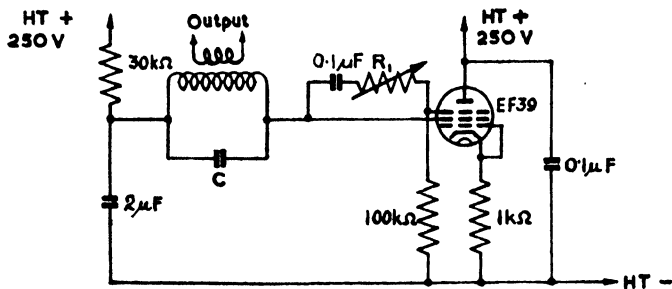


FIG. 469.—Typical transistron oscillator circuit.

Tuned-anode tuned-grid oscillator

It can be shown that, due to what is known as the "Miller effect", the anode load affects the grid-cathode impedance of a valve; moreover, the input impedance of a valve may have a negative resistance component if the anode load is inductive (*see* p. 350). This fact can be utilised to give a negative-resistance oscillator, as shown in Fig. 470.


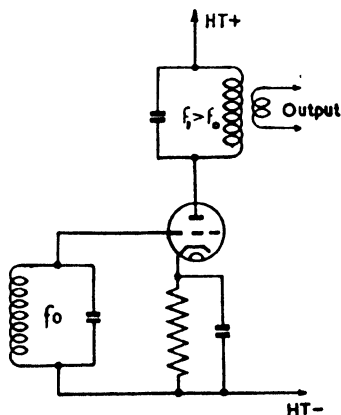


FIG. 470.—Tuned-anode tuned-grid oscillator.


In the tuned-anode tuned-grid oscillator, the tuned circuit proper is in the grid circuit, and is tuned to a frequency f_0 . The parallel circuit in the anode circuit is tuned to a frequency f_1 slightly greater than f_0 , and consequently at the frequency f_0 it represents a large inductive anode load. Thus, by the effect discussed above, the tuned grid circuit will have a negative resistance across it, and oscillations at the frequency f_0 will take place. Note that there is no direct coupling between the tuned circuits. The oscillator is little used at audio-frequencies, and its most frequent application is as a high-frequency crystal-controlled oscillator, when the grid tuned circuit is replaced by a quartz crystal, the result being a very stable oscillator whose frequency corresponds to the parallel resonant frequency of the crystal.

Parasitic oscillations

High frequency oscillations sometimes occur in amplifier circuits, due to stray capacity and inductance; these are known as "parasitic" oscillations. They are usually the result of a tuned-anode tuned-grid circuit being set up, particularly if transformers are used for input and output. The tuning capacities are the valve inter-electrode capacities, and these resonate with the stray inductance of the wiring. A simple amplifier circuit using transformer input and output is shown in Fig. 471*a*, and Fig. 471*b* shows the equivalent circuit at high frequencies.

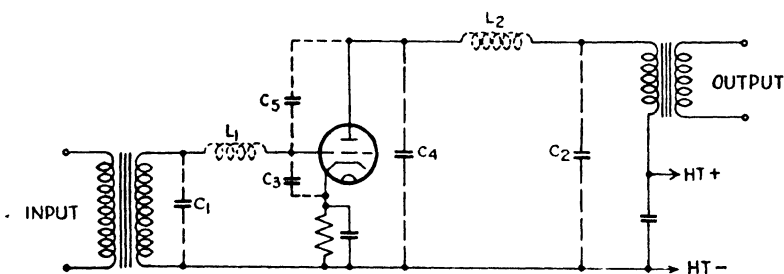

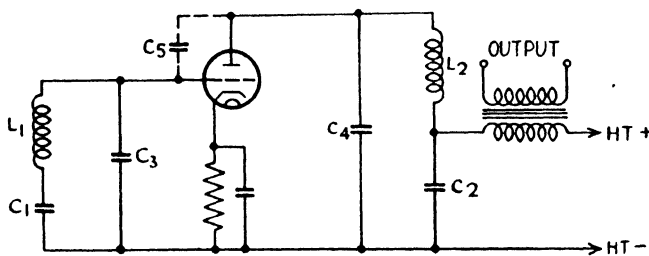(a) Simple amplifier circuit, showing stray capacities and inductances.



(b) Equivalent circuit at high frequencies, acting as a tuned-anode tuned-grid oscillator.

FIG. 471.—Parasitic oscillations in an amplifier.

The capacities C_1 and C_2 are the stray capacities to earth in the transformers and associated wiring; L_1 and L_2 are stray wiring inductances, and C_3 , C_4 and C_5 are valve inter-electrode capacities. C_1 and C_2 will generally be large compared with C_3 and C_4 . Both grid circuit and anode circuit will have a parallel resonant frequency which will be high, in view of the small capacities and inductances involved. If the parallel resonant frequency of the anode circuit is slightly higher than that of the grid circuit, the circuit will behave as a tuned-anode tuned-grid oscillator, producing high frequency parasitic oscillations.

There are two main methods of combating this effect. The first is the insertion in the grid lead of a resistance sufficiently high to neutralise the negative-resistance component of the valve's input

impedance. Alternatively, a small air-core inductance may be put in series with the anode ; this has the effect of increasing the stray anode inductance, and thus lowering the parallel resonant frequency of the anode circuit. If this frequency can be brought down below the parallel resonant frequency of the grid circuit, the system will not oscillate. Whether the grid resistance or the anode inductance is used, it is important to make sure that it is connected as close to the electrode as possible.

VARIABLE FREQUENCY OSCILLATORS

Coarse adjustment of frequency can be made in any tuned circuit oscillator by varying either L or C in steps. Fine adjustment is normally carried out by small continuously variable trimmer condensers across the main tuning condenser, though continuously variable inductances are sometimes used. Note that in the two cases treated mathematically on pages 471 and 479, the maintenance condition involves both L and C , and a change in frequency produced by varying L and C will also change the maintenance condition and consequently the output voltage.

Frequency coverage

An "L-C" or tuned circuit oscillator with an adjustable frequency can be made using a variable condenser for the tuning capacity C . This is quite satisfactory at radio frequencies, for although changing C will change the maintenance condition, it is possible to arrange a fairly constant output voltage over a certain working frequency range. Using normal components, this frequency range gives a ratio of approximately three to one ; thus an oscillator could be made to give a frequency continuously variable from 1 Mc/s to 3 Mc/s or from 100 kc/s to 300 kc/s. Such ranges as these represent a wide variation in frequency, and such an oscillator could be useful as a test oscillator at these frequencies.

Coming down the frequency scale to the audio range, however, an audio oscillator could only be made continuously variable from, say, 300 c/s to 900 c/s or from 1000 c/s to 3000 c/s, so that a single continuously variable frequency oscillator cannot cover the whole audio range and would be of little practical use. One of the easiest solutions to this problem is the beat-frequency oscillator (BFO), which can easily be made to cover the whole audio frequency range.

The beat-frequency oscillator

Fig. 472 shows, in a block schematic form, the essential components of a beat-frequency oscillator. It consists of two high frequency oscillators, one fixed and one variable, the difference of the two frequencies being in the audio range. The two outputs are mixed together in a square-law detector or balanced modulator, and the products passed *via* one or more stages of amplification to a low-pass filter that passes only the audio component. By this

means the complete audio range can be obtained from one fixed oscillator, and one oscillator with quite a small percentage variation. For example, suppose the range required is 0 to 20 kc/s and the fixed oscillator has a frequency of 100 kc/s; then the other oscillator need only be variable between 100 kc/s and 120 kc/s. The main advantages of this type of oscillator are its simplicity and the fact that a well-designed BFO has a fairly constant output voltage over

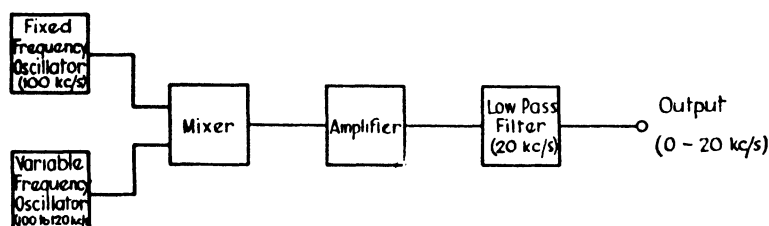


FIG. 472.—Essential components of a beat-frequency oscillator.

the whole frequency range. One disadvantage is the fact that the production of harmonics is inevitable in the mixer, and the output of a BFO is consequently never a perfect sine wave. Harmonic distortion is also produced in a different way. Suppose that the two high-frequency oscillators are tuned to 100,000 c/s and 100,200 c/s respectively, the fundamental in the output being 200 c/s. Since any oscillator produces harmonics, frequencies of 200,000 and 200,400 c/s are applied to the mixer, producing a certain amount of 400 c/s output; this is additional to the second harmonic distortion produced by the mixer. Thus the harmonic distortion can be reduced by inserting a low-pass filter, with a cut-off frequency of, say, 150 kc/s, between the fixed-frequency oscillator and the mixer. This ensures that the fixed oscillator applies pure 100 kc/s to the mixer, and even though the variable oscillator may be rich in harmonics, there will be no harmonics in the audio output other than those produced in the mixer.

A second disadvantage is that the oscillators must be extremely stable, for a variation of 1 per cent. in either of the oscillators in Fig. 472 would produce an error of 1000 c/s in the audio output. This error is largely minimised by making the two oscillators as similar as possible, so that an external influence that causes the frequency of one oscillator to vary may be assumed to cause a similar variation in the frequency of the other.

Thirdly, if a very low frequency output is attempted there is a tendency for the two oscillators to "lock" at exactly the same frequency. By using buffer amplifiers between the oscillators and the mixer, or alternatively by interposing a suitable bridge circuit, this can be largely prevented, and frequencies down to 10 c/s may be produced. Notwithstanding these facts, the BFO is excellent as a general purpose audio test oscillator.

RESISTANCE-CAPACITY OSCILLATORS

Fig. 473 shows an amplifier with a flat gain-frequency response, and zero phase-shift over a very wide frequency range. The output of this amplifier is coupled back to the input through a network whose phase-shift varies with frequency. If it can be arranged that the phase-shift of the network is zero, then the circuit will oscillate at that frequency, provided that the gain of the amplifier is equal to the loss in the network. For if this is the case, the feedback voltage is equal to the input voltage in magnitude and phase at this frequency, and this is the condition for the maintenance of oscillations.

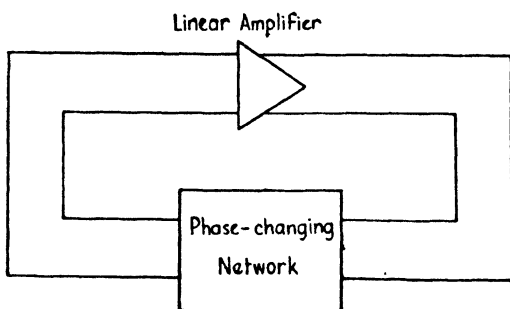


FIG. 473.—Illustrating the principle of the resistance-capacity oscillator.

Almost any combination of reactances and resistances can be used for the network. It would be an advantage, however, if the circuit could be arranged so that the required amplifier gain is independent of frequency and a network used that has a minimum attenuation at the zero phase-shift frequency. Consider the resistance-capacity network of Fig. 474.

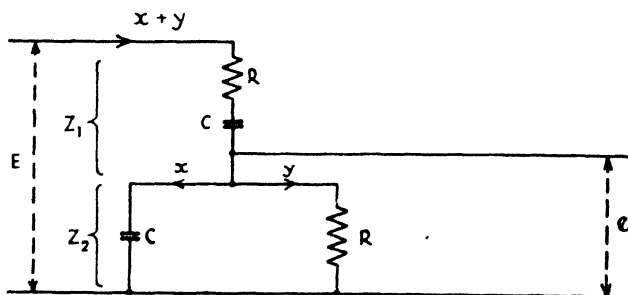


FIG. 474.—Phase-changing network suitable for use in R-C oscillators.

Let Z_1 be the impedance of R and C in series.

Let Z_2 be the impedance of R and C in parallel.

Then
$$\frac{e}{E} = \frac{Z_2}{Z_1 + Z_2}$$

But $Z_1 = R - \frac{j}{\omega C}$ and $Z_2 = \frac{-\frac{jR}{\omega C}}{R - \frac{j}{\omega C}}$

Hence
$$\begin{aligned} \frac{e}{E} &= \frac{\frac{-\frac{jR}{\omega C}}{R - \frac{j}{\omega C}}}{R - \frac{j}{\omega C} - \frac{jR}{R - \frac{j}{\omega C}}} \\ &= \frac{-\frac{jR}{\omega C}}{\left(R - \frac{j}{\omega C}\right)^2 - \frac{jR}{\omega C}} \\ &= \frac{1}{R^2 - \frac{1}{\omega^2 C^2} - \frac{3jR}{\omega C}} \end{aligned} \quad (12)$$

Thus e and E are in phase when :—

$$R^2 - \frac{1}{\omega^2 C^2} = 0$$

i.e. $\omega^2 = \frac{1}{R^2 C^2}$ (13)

or $f = \frac{1}{2\pi RC}$ (14)

Now, from equation 12 :—

$$\begin{aligned} \left|\frac{e}{E}\right|^2 &= \frac{\frac{R^2}{\omega^2 C^2}}{\left(R^2 - \frac{1}{\omega^2 C^2}\right)^2 + \frac{9R^2}{\omega^2 C^2}} = \frac{1}{\frac{\omega^2 C^2}{R^2} \left(R^2 - \frac{1}{\omega^2 C^2}\right)^2 + 9} \\ \therefore \left|\frac{e}{E}\right|^2 &= \frac{\omega^2 C^2}{R^2} \left(R^2 - \frac{1}{\omega^2 C^2}\right)^2 + 9 \end{aligned}$$

This is a minimum when $\omega^2 = \frac{1}{R^2 C^2}$, and its value at this frequency is 9. Thus at a single frequency given by $f = \frac{1}{2\pi RC}$ the phase-shift through the network is zero and the attenuation (voltage ratio) is a minimum and equal to 3 (see Fig. 475). Hence for oscillations to be maintained the amplifier must have a voltage

gain of 3. The frequency is controlled by varying the two equal resistors R simultaneously by means of a single control.

Notice that from equation 14 the frequency is inversely proportional to R ; it follows therefore that if resistances R_1 and R_2 give frequencies f_1 and f_2 respectively, then R_1 and R_2 in parallel will give a frequency of $f_1 + f_2$.

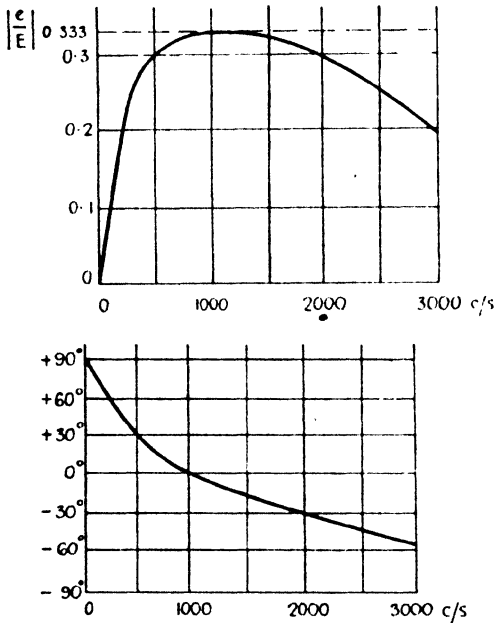


FIG. 475.—Attenuation and phase shift of network giving zero phase shift at 1000 c/s.

This simplifies the calibration of the oscillator, for it is possible to use several variable resistances in parallel for the variable resistance R , one being calibrated in tens of cycles, another in hundreds, another in thousands, and so on. The frequency of the oscillator will then be the sum of the frequencies indicated on the decade controls. A further simplification is possible if C is given a value of $0.00795 \mu\text{F}$. Equation 14 then reduces to $f = \frac{20 \times 10^6}{R}$, and this simplifies the construction of the resistance controls. It is also possible to increase the range of the oscillator by providing a "multiply by ten" key; this will merely substitute for C a capacity equal to $\frac{C}{10}$.

The most important part of this type of oscillator is the amplifier; for although the gain is only 3 (voltage ratio) the phase-shift must be zero at all frequencies in the working range; thus the linearity

of the amplifier is the limiting factor in the frequency range. Another point about the amplifier is that the output impedance must be low; for if this condition is not satisfied, it will be equivalent to an increase in the resistance of the series arm of the network, and consequently the calibration of the oscillator will be upset. Voltage negative feedback may be applied to obtain this low output impedance.

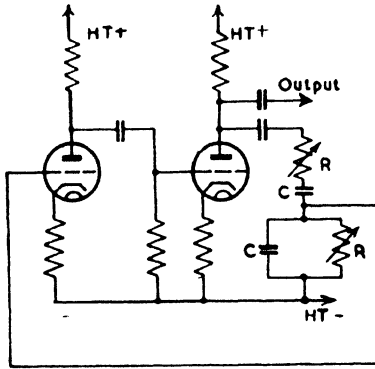


FIG. 476.—Skeleton circuit of two-valve R-C oscillator.

A skeleton diagram of an R-C oscillator is shown in Fig. 476, which is intended merely to show how the phase-changing network is fitted into the amplifier circuit; no details of the amplifier are shown, as this follows standard practice.

Single-stage R-C oscillator

It is possible to make a single-stage R-C oscillator, provided some network is connected between anode and grid that introduces 180° phase-shift to give positive feedback. Several networks of the type shown in Fig. 477 can be used for this purpose.

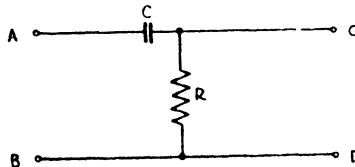


FIG. 477.—Phase-changing network.

The voltage across CD in this network will be ahead of the voltage across AB by some angle between 0° and 90° , depending on the relative impedances of R and C at the frequency considered. To obtain 180° phase-shift, three of these networks have to be used, as it is not possible to get quite 90° phase-shift from one.

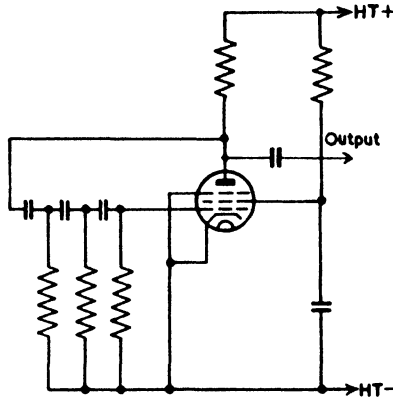


FIG. 478.—Single-stage R-C oscillator.

The three networks are connected between anode and grid, giving a circuit of the type shown in Fig. 478. This type of oscillator is most suitable for use at fixed frequencies.

THE MULTIVIBRATOR

The most common relaxation oscillator circuit, and the only one to be considered here, is the multivibrator, shown in Fig. 479 ;

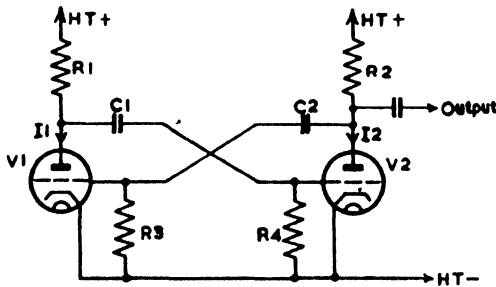


FIG. 479.—Multivibrator circuit.

it is assumed for simplicity that $R_1 = R_2$, $R_3 = R_4$ and $C_1 = C_2$, and this is usually the case in practice. It will be seen that the multivibrator consists of a two-stage resistance-capacity coupled amplifier, with the output fed directly back to the input. As the total phase-shift through such an amplifier is 360° , clearly the circuit will oscillate, the frequency depending on the component values.

To follow the operation of the circuit, suppose that, on switching on, a small positive voltage appears on the grid of V_1 . This causes an increase in the anode current I_1 of the valve V_1 , and a decrease in the anode potential of V_1 which is passed to the grid of V_2 . This decrease in the grid potential of V_2 causes a decrease in I_2 ,

and an increase in the anode potential of V_2 ; this drives the grid of V_1 more positive. This process is continued and the effect is cumulative, the grid of V_1 growing more positive and the grid of V_2 more negative until V_2 is biased back to cut-off; the whole process is, of course, practically instantaneous. The circuit remains in this condition while the negative potential on the grid of V_2 leaks away, the time for this depending on the time constant of C_1 and R_4 . The positive potential on the grid of V_1 disappears much more quickly due to the flow of grid current. As soon as the grid potential of V_2 reaches the point where anode current can flow once more, the anode potential of V_2 will begin to fall due to the fact that I_a is increasing; this drives the grid of V_1 negative and the whole action is repeated in the opposite direction until V_1 is cut off. The grid potential and anode current waveforms for each valve are shown in Fig. 480.

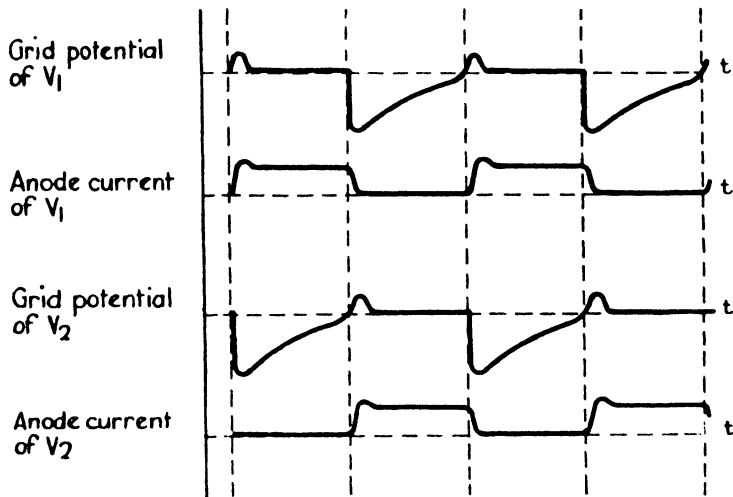


FIG. 480.—Variation of grid potential and anode current in multivibrator.

These waveforms are particularly rich in harmonics, the anode currents being approximately square wave, and this is one of the important properties of the multivibrator. The second important property is the fact that the frequency can easily be locked in synchronism with another frequency. The best method if pentodes are used is to inject the synchronising voltage on to the suppressor grid of either valve. The multivibrator will lock even if the injected frequency is several times its own frequency. Suppose, for example, a multivibrator is working at a frequency of the order of 100 cycles per second. If a 1000 c/s voltage is injected, the multivibrator can be made to lock at 100 c/s. In this way a frequency dividing system is obtained.

The frequency can be varied by altering R_3 and R_4 , and may be as low as desired by making these resistances large enough (e.g., one

cycle per minute is quite possible with this circuit using very high values for R_3 and R_4). At the other end of the scale, the limit on high frequencies is about 100 kc/s, which is about the limit for satisfactory resistance-capacity coupling.

It was assumed for simplicity that $R_1 = R_2$, $R_3 = R_4$, and $C_1 = C_2$; this simplification gives a symmetrical output, the valves being cut off for equal periods of time. In the more general case when these equalities do not hold, the operation of the circuit is just the same, but the valves are cut off for unequal periods, and the output is asymmetrical.

CHAPTER 11

MODULATION

ADDITION OF TWO SINE WAVES

If two pure sine waves are applied simultaneously to a communication system, their instantaneous amplitudes may be added. Fig. 481 shows the equivalent circuit of a network in which the sum of the two voltages e_1 and e_2 appears across the impedance Z_1 ; Fig. 482 shows the equivalent circuit of a network in which the sum of the currents i_1 and i_2 flows through the impedance Z_2 .

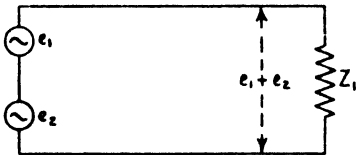


FIG. 481.—Addition of two sinusoidal voltages.

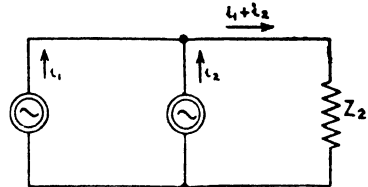


FIG. 482.—Addition of two sinusoidal currents.

Consider the two sine waves shown in Fig. 483*a* and *b*. These waveforms have equal amplitudes, and their frequencies f_1 and f_2 differ only slightly. The addition of these two waveforms is given by Fig. 483*c*. This resultant waveform *c* consists only of frequencies f_1 and f_2 ; filters, tuned circuits, or any similar simple device will be sufficient to re-separate the independent frequencies. Applying Fourier's analysis to the waveform verifies the fact that no other frequencies are present.

Curve *c* may, however, be considered as a waveform having a frequency $\frac{f_1 + f_2}{2}$ and varying in amplitude in such a way as to have a cosine-wave envelope of frequency $\frac{f_1 - f_2}{2}$. This may be seen from Fig. 483, and verified mathematically.

$$\begin{aligned} \text{Let } y_1 &= A \cdot \sin 2\pi f_1 t \\ \text{and } y_2 &= A \cdot \sin 2\pi f_2 t \\ \text{Then } y_1 + y_2 &= A (\sin 2\pi f_1 t + \sin 2\pi f_2 t) \\ &= 2A \sin 2\pi \frac{f_1 + f_2}{2} t \cdot \cos 2\pi \frac{f_1 - f_2}{2} t \end{aligned}$$

This is equivalent to a sine wave of frequency $\frac{f_1 + f_2}{2}$ varying sinusoidally in amplitude from $+2A$ through 0 to $-2A$, and back through 0 to $+2A$ again, with a frequency of $\frac{f_1 - f_2}{2}$. If the *absolute* amplitude of the waveform is considered, the increase and decrease occurs at a frequency of $(f_1 - f_2)$; the latter is called the "beat frequency".

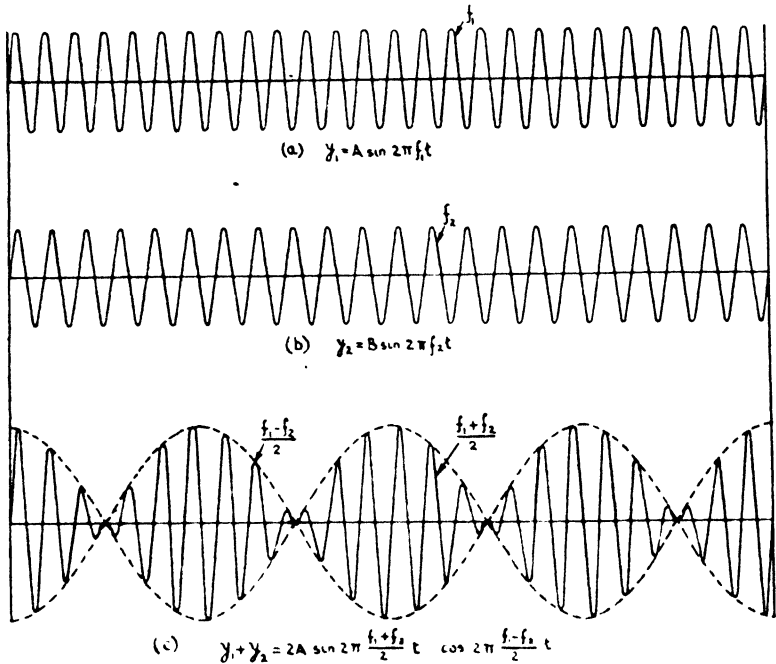


FIG. 483.—Addition of two sine waves of equal amplitudes (i.e. $A = B$).

Beat notes

The above discussion applies to all sinusoidal waveforms, and hence it applies equally well to sound waves. This is important, because it gives rise to *audible* beat notes. Suppose that the frequencies under consideration are $f_1 = 255$ c/s and $f_2 = 257$ c/s. These two, when present simultaneously, will produce exactly the same sound as a 256 c/s frequency varying in amplitude in a sinusoidal manner with a frequency of 2 c/s; the two resultant waveforms are, in fact, exactly equivalent.

When frequencies of this nature are close together and in the audio range, the human ear cannot distinguish the individual frequencies, and the tones of 255 c/s and 257 c/s, when present simultaneously, give the impression that a note of 256 c/s is present, varying in amplitude at a frequency of 2 c/s. This is called a 2 c/s

beat note. If the frequencies were 254 c/s and 258 c/s the ear would give the impression that only a 256 c/s note were present, varying in amplitude at a frequency of 4 c/s, and so on.

However, this state of affairs applies only when the frequencies are close together, within, say, 30 c/s. Listening simultaneously to notes of 286 c/s and 226 c/s, one hears the two pure sine waves, not a note of 256 c/s "beating" at 60 c/s.

Waves of different amplitudes

So far it has been assumed that the amplitude of the sine wave of frequency f_1 is the same as that of f_2 . If the amplitudes are

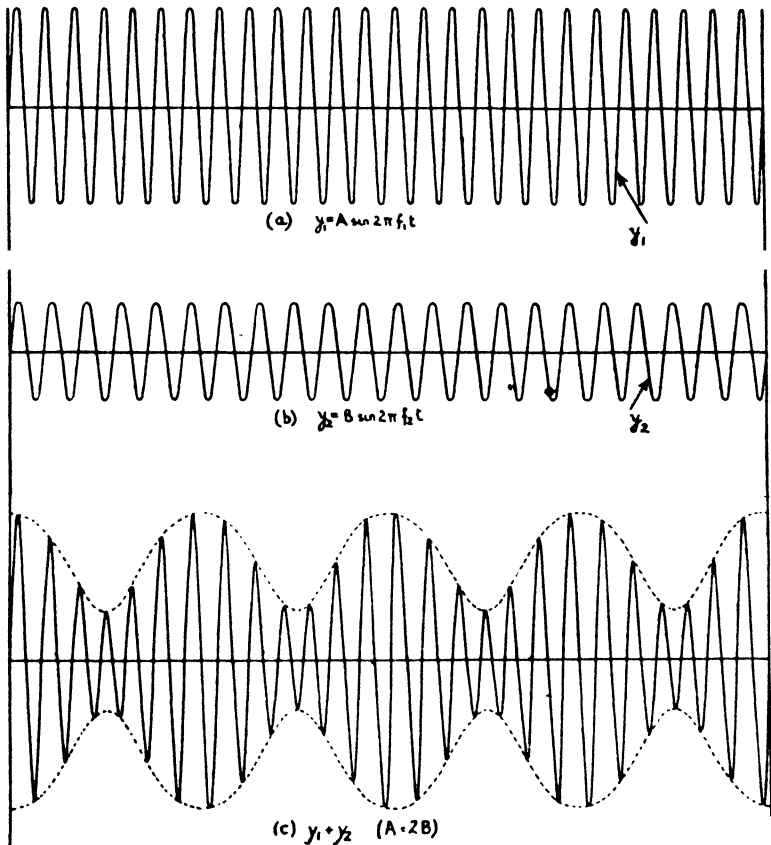


FIG. 484.—Addition of two sine waves of unequal amplitudes ($A = 2B$).

different, the general shape of the resultant will alter slightly, but the beat note may still be detected.

Fig. 484 shows the addition of two sine waves when the amplitude of y_1 is twice the amplitude of y_2 .

Synchronising two audio frequencies

This "beat note" phenomenon gives a very simple method of synchronising two frequencies within the audio range, but it should be remembered that no beat note will be heard if the parent frequencies are outside the audio limits. In such a case an AC meter would give a convenient method of detecting the variation in amplitude due to the presence of beat notes, since the deflection obtained is a function of the envelope amplitude of the waveform.

Waves of widely different frequencies

This general shape of waveform is maintained until the frequency of y_1 becomes exactly twice that of y_2 . When this occurs,


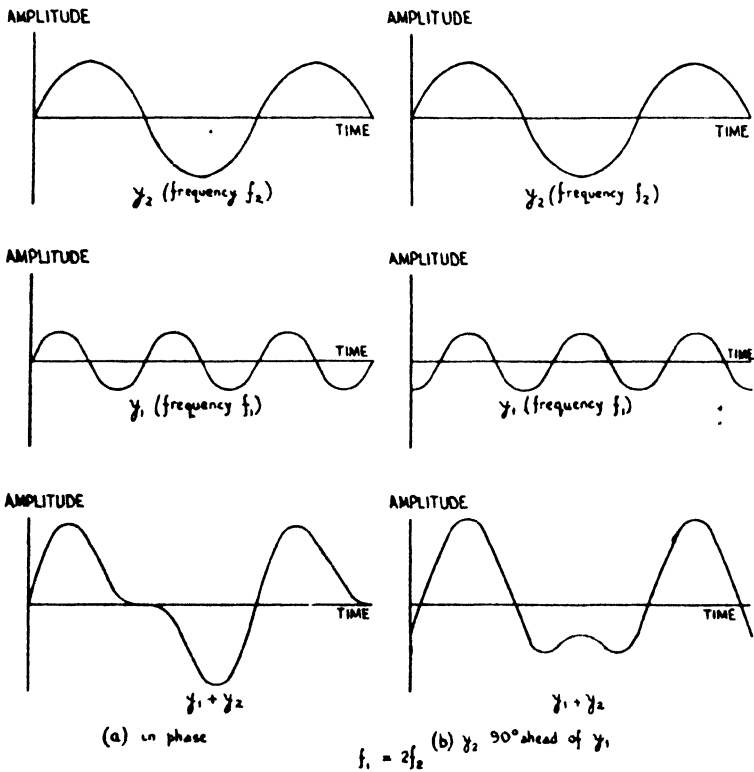



FIG. 485.—Addition of two sine waves of different amplitudes, the frequency of one being twice that of the other.

the waveform is simply that of a sine wave (of frequency f_2) with second harmonic distortion, the exact shape of the resultant depending on the relative phases of y_1 and y_2 (see Fig. 485).

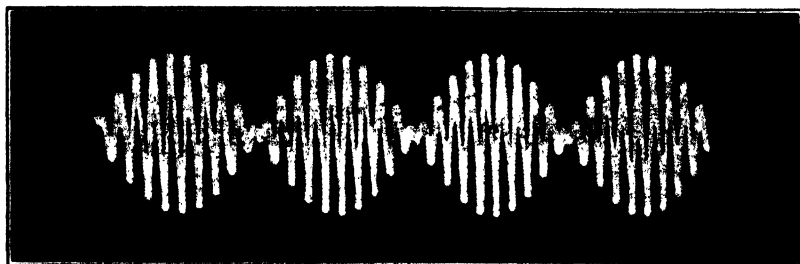
When the frequency of y_1 is greater than twice that of y_2 , the resultant waveform shows clearly the superposition of y_1 on y_2 .



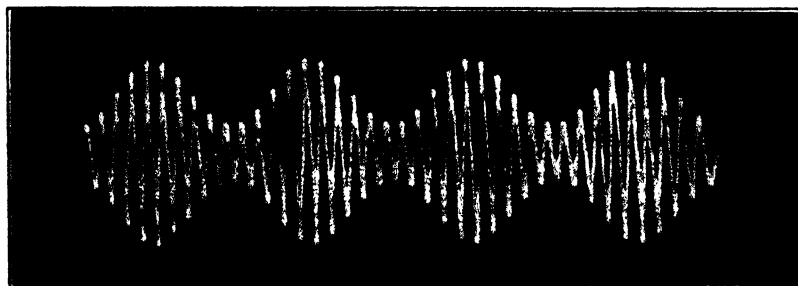(a) Addition of two sine waves of equal amplitude.



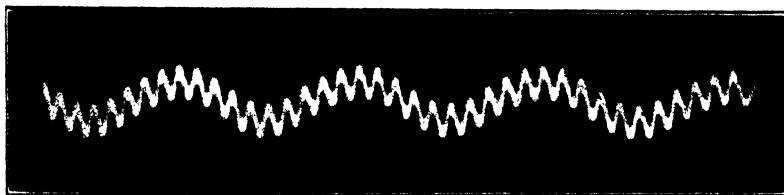(b) Addition of two sine waves of unequal amplitude.



(c) Addition of two sine waves, the frequency of one being ten times the frequency of the other.

Fig. 486*a* shows the addition waveform of the sine waves y_1 and y_2 with the amplitude of y_1 equal to one-tenth of the amplitude of y_2 . Fig. 486*b* shows the resultant of the two curves when the amplitudes are equal. In both cases the frequency of y_1 is twenty times the frequency of y_2 . The two resultants should be contrasted with those of Figs. 483 and 484.

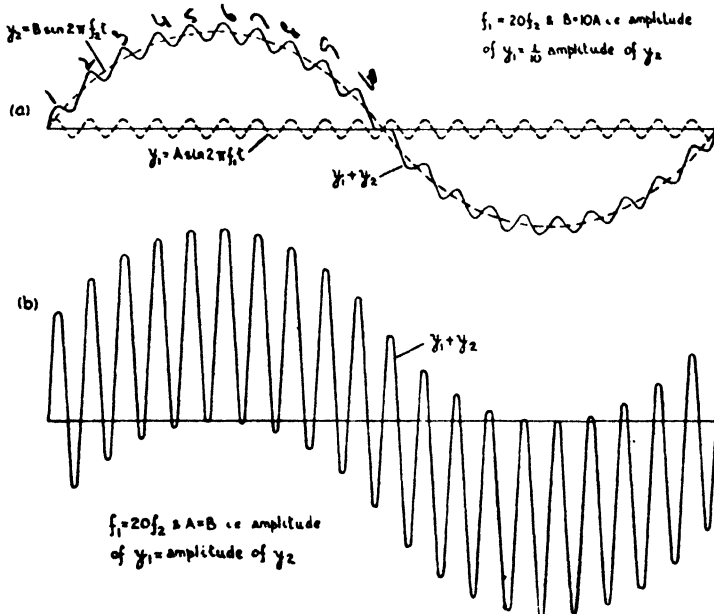


FIG. 486.—Addition of two sine waves, the frequency of one being twenty times the frequency of the other.

AMPLITUDE MODULATION

If the amplitude of a sine wave of frequency f_0 is varied sinusoidally between the limits $A + a$ and $A - a$ with a frequency f —i.e., the amplitude at any instant is $(A + a \cdot \sin 2\pi ft)$ —then the equation of the resultant waveform will be:—

$$y = (A + a \cdot \sin 2\pi ft) \cdot \sin 2\pi f_0 t$$

$$\text{i.e.} \quad y = A \left(1 + \frac{a}{A} \sin 2\pi ft\right) \cdot \sin 2\pi f_0 t \quad (1)$$

Such a waveform is known as an "amplitude modulated" waveform; the frequency f_0 is known as the "carrier" frequency, and the frequency f is known as the "modulating" frequency;

$\frac{a}{A}$ is known as the "modulation factor", and $\frac{100a}{A}$ per cent. as the "percentage modulation" (see Fig. 487).

Equation 1 for the waveform may be simplified by letting

$$\begin{aligned} 2\pi f &= \omega \\ \text{and } 2\pi f_c &= p \end{aligned}$$

In this case, equation (1) becomes:—

$$y = A \left(1 + \frac{a}{A} \sin \omega t \right) \sin pt \tag{2}$$

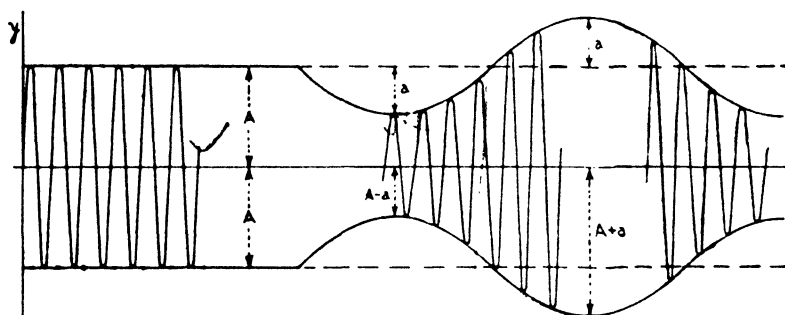


FIG. 487.—Amplitude modulation.

Sidebands

This resultant waveform does not consist simply of frequencies f_c and f as would be the case had the two frequencies been "added", in fact, there is no longer any component of frequency f present in the resultant, although two new frequencies $f_c + f$ and $f_c - f$ have been produced.

This may be verified mathematically:—

$$\begin{aligned} A \left(1 + \frac{a}{A} \sin \omega t \right) \sin pt &= A \sin pt + a \sin pt \cdot \sin \omega t \\ &= A \sin pt + \frac{a}{2} \cos (p - \omega)t - \frac{a}{2} \cos (p + \omega)t \end{aligned} \tag{3}$$

(from equation 40, p. 43).

It will be noted that the amplitude a and the frequency $f (= \frac{\omega}{2\pi})$ of the modulating waveform appear only in the second and third terms.

Considering the terms separately:—

(a) $A \sin pt$ corresponds to a sine wave of the carrier frequency (f_c) and of maximum amplitude A .

(b) $\frac{a}{2} \cos (p - \omega)t$ corresponds to a sine (or cosine) wave of frequency $(f_c - f)$ and of maximum amplitude $\frac{a}{2}$. This frequency is known as the "lower sideband" (LSB) frequency.

(c) $-\frac{a}{2} \cos (p + \omega)t$ corresponds to a sine (or cosine) wave

of frequency $(f_c + f)$ and of maximum amplitude $\frac{a}{2}$. This frequency is known as the "upper sideband" (USB) frequency.

It follows, therefore, that an amplitude modulated waveform is equivalent to three sine waves, namely the carrier, the upper sideband, and the lower sideband.

Thus the waveform, shown in Fig. 487, may be separated by filters or tuned circuits into its three constituent sine waves having frequencies f_c , $(f_c + f)$, $(f_c - f)$.

Conversely, three sine waves having the correct amplitudes, frequency and phase will, when present simultaneously, be equivalent to an amplitude modulated waveform.

Example.—

If a carrier frequency of 6 kc/s is amplitude modulated by an audio frequency of 1600 c/s, what frequencies will be present in the output ?

Carrier	= 6 kc/s
Upper sideband	= 6 + 1.6 = 7.6 kc/s
Lower sideband	= 6 - 1.6 = 4.4 kc/s

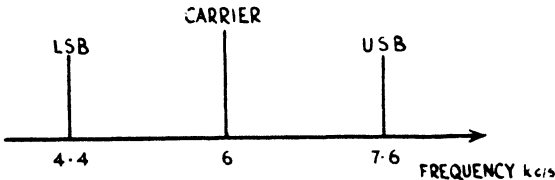


FIG. 488.—Sidebands produced when a carrier frequency of 6 kc/s is amplitude modulated by an audio frequency of 1600 c/s.

If the carrier frequency is modulated simultaneously by a number of frequencies a number of sideband frequencies will be produced.

Example.—


If a carrier frequency of 300 c/s is modulated by a square-waveform of 25 c/s, what frequencies will be produced ?

A square waveform of 25 c/s may be considered as the sum of an infinite number of sine waves (p. 106), all of which are odd harmonics of a 25 c/s sine wave, the amplitude decreasing as the number of the harmonic increases. The modulating frequencies present are therefore 25 c/s, 75 c/s, 125 c/s, 175 c/s, etc., with decreasing amplitudes, up to infinity.


These will give rise to a series of upper and lower sidebands,

thus:—


<i>Lower Sidebands.</i>	<i>Carrier.</i>	<i>Upper Sidebands.</i>
	300 c/s	
275 c/s		325 c/s
225 c/s		375 c/s
175 c/s		425 c/s
125 c/s		475 c/s
...		...

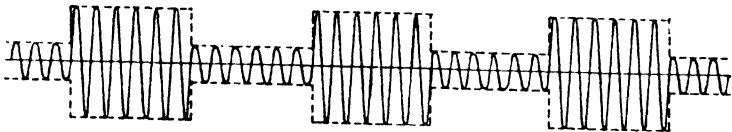

(a) 50% MODULATION

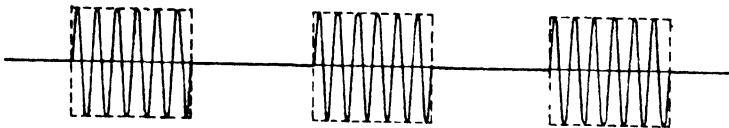

(b) 100% MODULATION

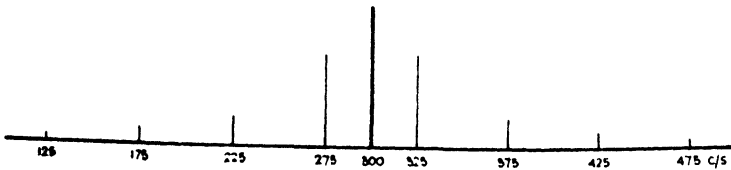

(c) SIDEBANDS PRODUCED

FIG. 489.—Modulation of 300 c/s with a square-waveform, frequency 25 c/s.

It should be noted that 100 per cent. modulation with such a square-waveform is equivalent to switching the carrier on and off at a rate of 25 times a second.

If the carrier frequency is modulated by a band of frequencies, only the highest and lowest frequencies in the band are usually considered, and the sideband frequencies produced by these are calculated. All other sideband frequencies will be within these limits.

Example.—

A carrier frequency of 16 kc/s is modulated by audio frequencies ranging from 300 to 2700 c/s. What will be the range of the upper and lower sidebands?

300 c/s will produce an upper sideband frequency of 16.3 kc/s and a lower sideband frequency of 15.7 kc/s.

2700 c/s will produce an upper sideband frequency of 18.7 kc/s and a lower sideband frequency of 13.3 kc/s.

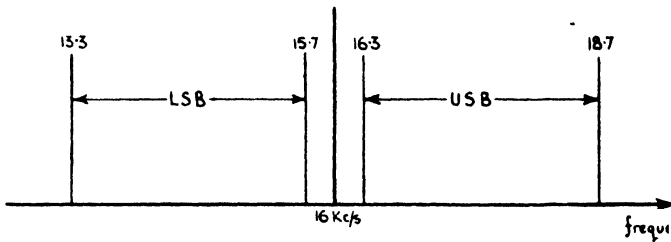


FIG. 490.—Sidebands produced when a carrier frequency of 16 kc/s is amplitude modulated by audio frequencies of 300 c/s and 2700 c/s.

Thus the upper sideband will range from 16.3 to 18.7 kc/s, and the lower sideband will range from 15.7 down to 13.3 kc/s, as shown in Fig. 490.

Application of modulated waveforms

The chief function of a modulated waveform is to transmit the intelligibility originally contained in the modulating signal, but in a different frequency band. The transmission of intelligibility entails the transmission of signals corresponding to both the amplitude and the frequency of the modulating waveform. It may be conveyed in the following ways:—

- (1) By transmitting the complete amplitude-modulated signal, consisting of carrier, upper sideband, and lower sideband,
- (2) by transmitting the carrier and the upper sideband only,
- (3) by transmitting the carrier and the lower sideband only,
- (4) by transmitting the upper sideband alone, and replacing the carrier at the receiving station,
- (5) by transmitting the lower sideband alone and replacing the carrier at the receiving station.

In all cases the original modulating signal is regained at the receiving station by a process known as “demodulation”. All the above methods are employed in line communication systems, and will be discussed more fully in Chapter 22.

Since the intelligibility is contained in the sidebands, it is useless to transmit the carrier alone. The only remaining method would be to suppress the carrier and to transmit both the upper and lower sidebands together. This method has not been included in the above list, since it is seldom used owing to the practical difficulties of demodulating the signal at the receiving end. In such a case,

the carrier must be replaced at the receiving station with not only exactly correct frequency, but also the correct phase.

MODULATORS

The function of a modulator is to produce sidebands. As has been seen, the exact composition of the signal transmitted, and hence the modulator used, will depend on the method of working adopted. The modulators now to be described all deliver, in their output, the carrier frequency as well as both upper and lower sidebands, and they illustrate the fundamental principles of amplitude modulation. After these, will be described the modulators used when it is desired not to transmit the carrier.

Non-linear impedance modulator

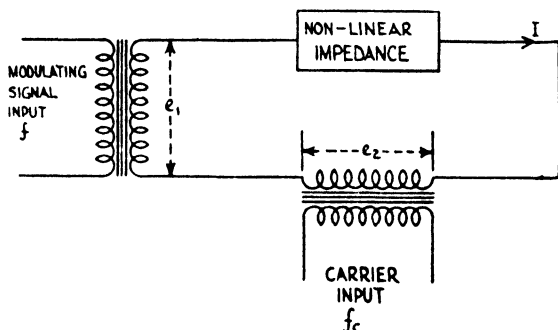


FIG. 491.—Simple non-linear impedance modulator.

Fig. 491 shows the circuit of a simple non-linear impedance (NLI) modulator. Assume that the non-linear impedance has a characteristic such that :—

$$i = a + b \cdot e + c \cdot e^2$$

where e is the voltage applied. i is the current flowing, and a , b and c are constants.

Let the current flowing be I ,

$$\begin{aligned} \text{and the voltage applied} &= e_1 + e_2 \\ &= E_1 \sin \omega t + E_2 \sin pt \end{aligned}$$

$$\begin{aligned} \text{Hence } I &= a + b(E_1 \sin \omega t + E_2 \sin pt) + c(E_1 \sin \omega t + E_2 \sin pt)^2 \\ &= a + bE_1 \sin \omega t + bE_2 \sin pt + cE_1E_2 \cos(p - \omega)t \\ &\quad - cE_1E_2 \cos(p + \omega)t + \text{harmonics.} \\ &= \text{DC} + \text{modulating signal} + \text{carrier} + \text{LSB} + \text{USB} \\ &\quad + \text{harmonics.} \end{aligned}$$

If it is desired to obtain an output voltage containing the modulation products, a linear impedance Z must be included in the circuit, and the voltage taken off from across Z .

Thermionic valves and metal rectifiers as modulators

Although *any* non-linear impedance may be employed as a modulator, there are two main classes of modulators in general use:—

- (1) *Thermionic valve modulators*, normally employed when the complete modulated waveform is to be transmitted.
- (2) *Metal rectifier modulators*, normally used when a "suppressed carrier" output waveform is required.

Valve modulators

The circuits employing valve modulators may be divided into two classes. In the first, the modulating frequency and the carrier frequencies are both applied between the same grid and the cathode (*see*

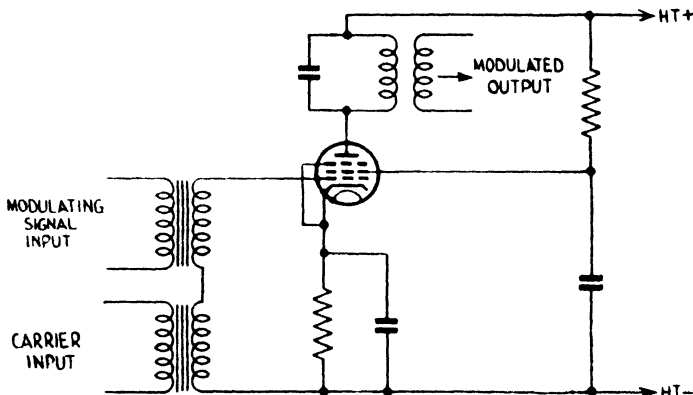


FIG. 492.—Thermionic valve modulator using grid modulation.

Fig. 492), and the non-linear part of the mutual characteristic of the valve is utilised to produce the required modulation products. In this respect the valve behaves in a similar manner to the non-linear impedance just discussed, except that the amplification property of the valve is utilised in addition to its non-linear property. This method is known as "grid modulation".

The disadvantage of this method of modulation is the interaction that tends to occur between the carrier and signal input circuits.

In the second class, separate electrodes are used for the injection of the two frequencies, and reliance is placed upon the fact that the voltage applied to one grid produces a variation in the slope of the mutual characteristic of the other. Since the only coupling between the two signals is *via* the electron stream, interaction is reduced to a minimum. However, this method entails the use of a multi-grid valve, of which the pentode is a simple type. Fig. 493 shows the use of a pentode valve as a modulator, the modulating signal being applied to the control grid, and the carrier frequency applied to the suppressor. This method is known as suppressor grid modulation; the circuit is taken from a high frequency carrier telephone

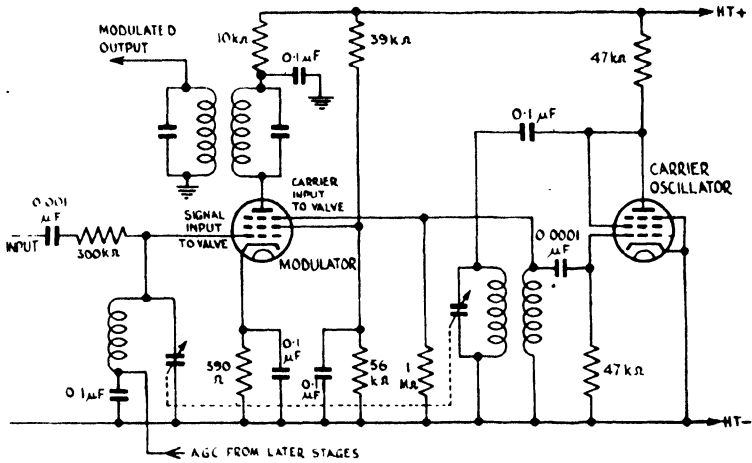


FIG. 493.—Suppressor grid modulation.

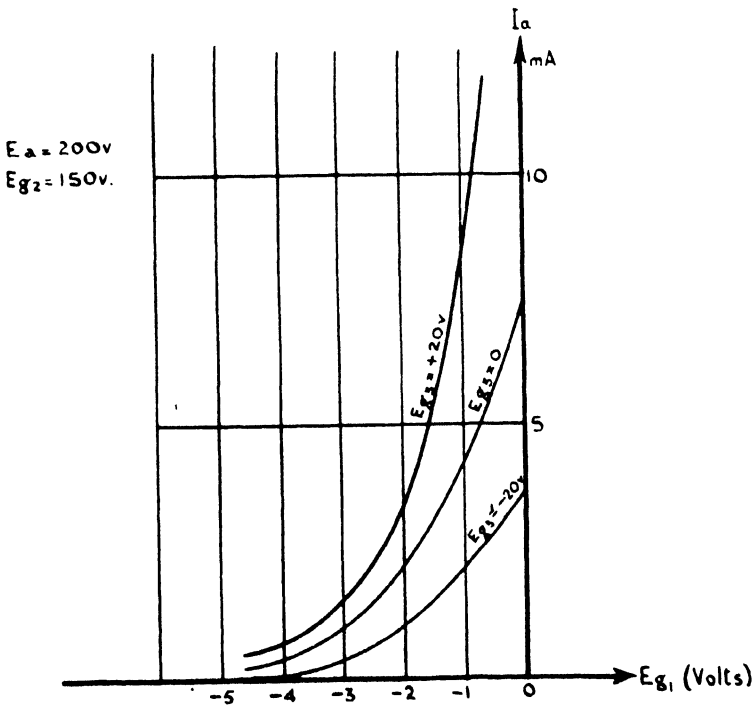


FIG. 494.—The effect of variations in suppressor voltage on the control grid mutual characteristic for a typical pentode valve.

system. Fig. 494 shows the effect of variations in suppressor voltage on the control grid mutual characteristic for a typical pentode valve.

As has been seen in Chapter 7, a number of different types of valve have been designed specially for use as modulators. In

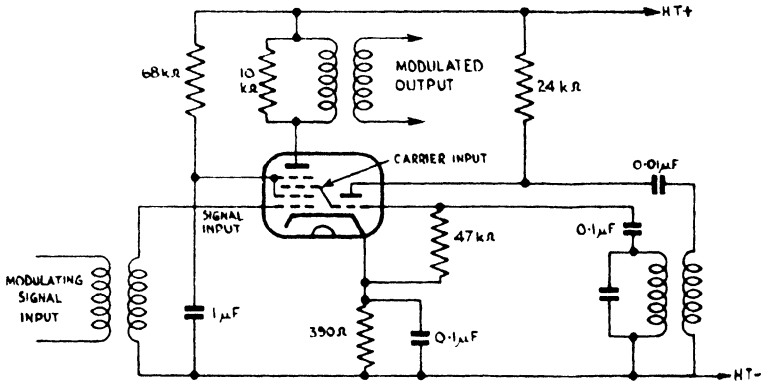


FIG. 495.—Modulation using a triode-hexode frequency changer

certain cases the triode oscillator producing the carrier frequency may be included in the same envelope. Fig. 495 shows a modulator circuit employing a valve of this type—a triode-hexode.

Metal rectifier modulators

In carrier telephone circuits, where the carrier frequency is low (below 40 kc/s in a three-channel carrier telephone system), metal rectifier modulators may be used successfully. At higher frequencies the inherent capacity of the rectifiers introduces a shunt loss, and unless care is taken to reduce this loss to a minimum, satisfactory working will be impossible. Metal rectifier modulators employing low-capacity rectifier elements have nevertheless been devised for operation at carrier frequencies up to 2 Mc/s. Above this frequency, thermionic valve modulators are used.

Metal rectifier modulators are low-level devices, and will operate only at a part of a circuit where the power level is low. This means that, in general, such a metal rectifier modulator will be followed by a power amplifier.

MODULATION IN SUPPRESSED CARRIER SYSTEMS

The output of all the modulators so far described consists of both upper and lower sidebands and the carrier. The "balanced" modulators now to be considered "suppress" the carrier, so that

their output contains no component of carrier frequency, but only the two wanted sidebands, plus some unwanted products of modulation, which can be removed by filters.

Balanced modulators

A balanced modulator is one that gives an output containing the upper and lower sidebands, but with the carrier suppressed. The presence of these two sidebands simultaneously will give rise to an output corresponding to a beat note waveform.

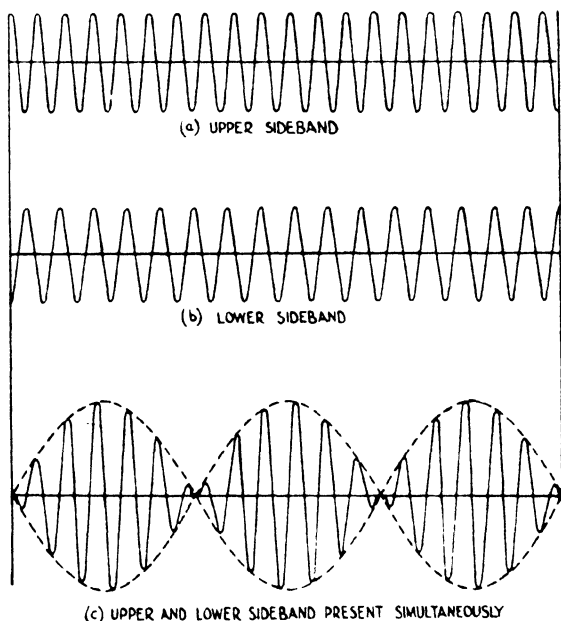


FIG. 496.—Addition of two sidebands without carrier.

Fig. 497a shows a typical balanced modulator circuit. The carrier is applied to the centre-taps of transformers $T1$ and $T2$, and provided that rectifiers $W1$ and $W2$ are exactly matched, no carrier frequency component will be present in the output of $T2$. A "carrier leak" control may be provided by the insertion of a potentiometer at B , as shown in Fig. 497b. This potentiometer enables the relative magnitudes of the carrier currents flowing through the two halves of the primary of $T2$ to be adjusted until the minimum carrier output is obtained.

The operation of this balanced modulator will now be explained. It has been seen that the impedance of a metal rectifier to small AC signals varies considerably with the DC bias voltage applied (*see* p. 293), being very small when the rectifier is forward-biased, and very large when the rectifier is back-biased (*see* Fig. 497c).

AMPLITUDE MODULATION

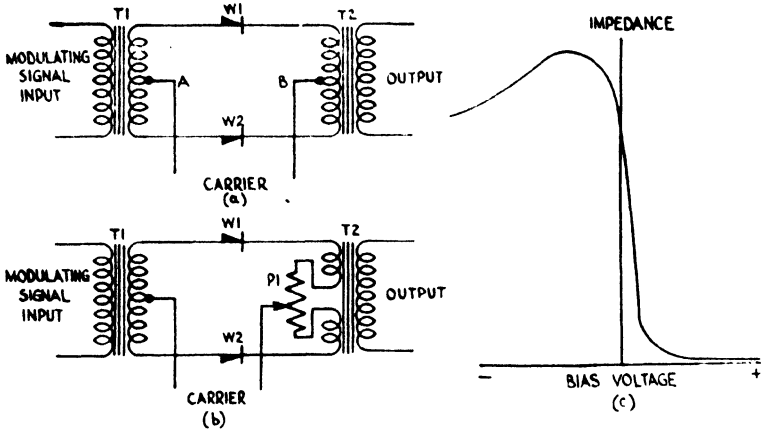


FIG. 497.—Balanced modulator.

Assuming that the amplitude of the carrier input is large compared with the modulating signal input, only the biasing of the rectifiers by the carrier need be considered. Consider the half-cycles of the carrier when *A* is at a higher potential than *B* (Fig. 497*a*): the rectifiers will be forward-biased (see Fig. 498), the path between the two transformers *T1* and *T2* will have a low impedance, and the signal tone will pass to the output. During the other half-cycle when *B* is at a higher potential than *A*, the rectifiers are back-biased (see Fig. 499), and the impedance between *T1* and *T2* will be high, preventing signal tone from passing to the output.

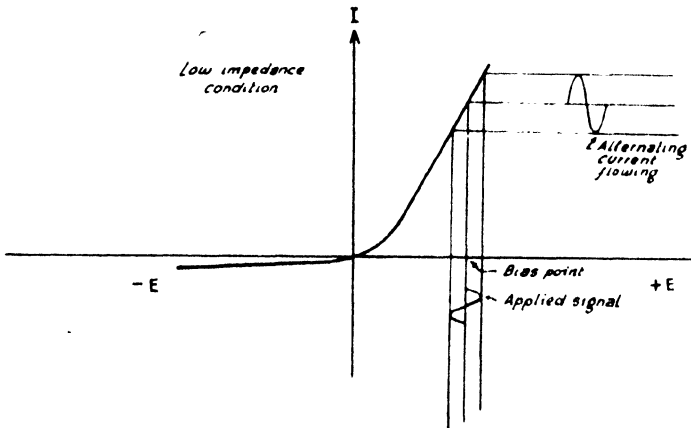


FIG. 498.—Application of small alternating voltage to a forward-biased metal rectifier.

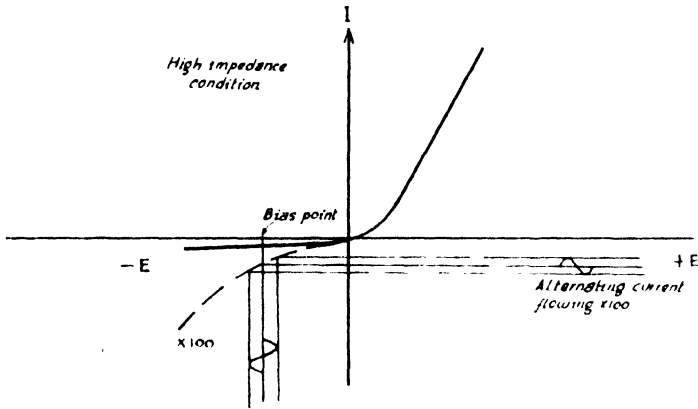


FIG. 499.—Application of small alternating voltage to a back-biased metal rectifier.

The input and output waveforms are shown in Fig. 500. The output waveform appears to show no resemblance to the anticipated waveform of Fig. 496c. This is due, however, to the presence of a large number of frequencies, including a modulating signal component in addition to the upper and lower sidebands. The output waveform follows the modulating signal input during the positive half-cycles of the carrier, but is zero during the negative half-cycles. This is exactly the waveform produced when the signal input waveform of Fig. 500a is multiplied by the square waveform of Fig. 500d.

$$\begin{aligned}
 \text{Output} &= E_1 \sin \omega t \times \left[\frac{1}{2} + \frac{2}{\pi} \left\{ \sin pt + \frac{1}{3} \sin 3pt + \dots \right\} \right] \\
 &= \frac{E_1}{2} \sin \omega t + \frac{2E_1}{\pi} \sin pt \cdot \sin \omega t + \frac{2E_1}{3\pi} \sin 3pt \sin \omega t + \dots \\
 &= \frac{E_1}{2} \sin \omega t + \frac{E_1}{\pi} \left[\cos (p - \omega)t - \cos (p + \omega)t \right] \\
 &\quad + \frac{E_1}{3\pi} \left[\cos (3p - \omega)t - \cos (3p + \omega)t \right] + \dots \\
 &= \text{modulating signal} + \text{upper and lower sidebands of} \\
 &\quad \text{carrier frequency} + \text{upper sideband and lower side-} \\
 &\quad \text{band of 3 times carrier frequency} + \dots
 \end{aligned}$$

The output thus consists of a modulating signal component and the wanted upper and lower sidebands, plus an infinite number of sidebands corresponding to the odd harmonics of the carrier, the amplitude decreasing as the number of the harmonic increases. Note that there are no sidebands present corresponding to any harmonics of the modulating signal.

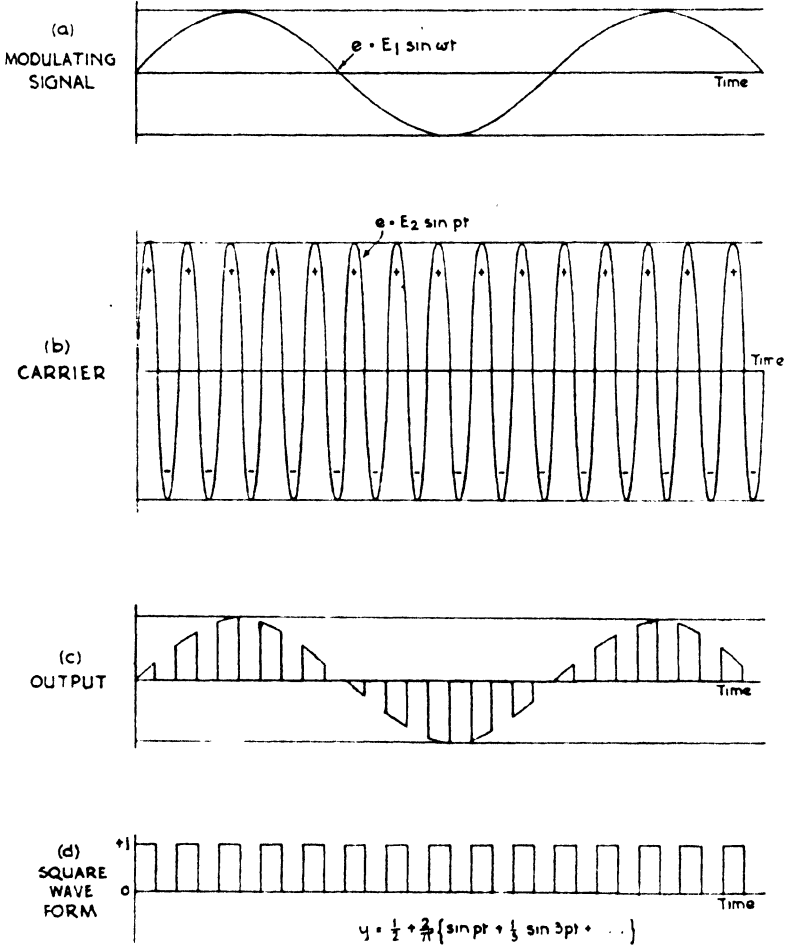


FIG. 500.—Waveform produced by balanced modulator

The Cowan modulator

An alternative form of balanced modulator frequently used in America is the Cowan modulator shown in Fig. 501.

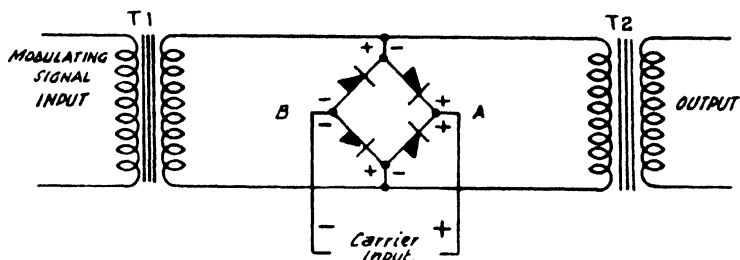


FIG. 501.—The Cowan modulator.

Its operation may be explained as follows. During those half-cycles of the carrier when *A* is at a higher potential than *B*, as indicated in Fig. 501, all the rectifiers are back-biased, and the rectifier network presents only a negligibly small shunt loss in the signal path from *T1* to *T2* (see Fig. 502*a*).

During those half-cycles of carrier when *B* is at a higher potential than *A*, all the rectifiers are forward-biased, and the rectifier network presents a virtual short-circuit across the signal path,

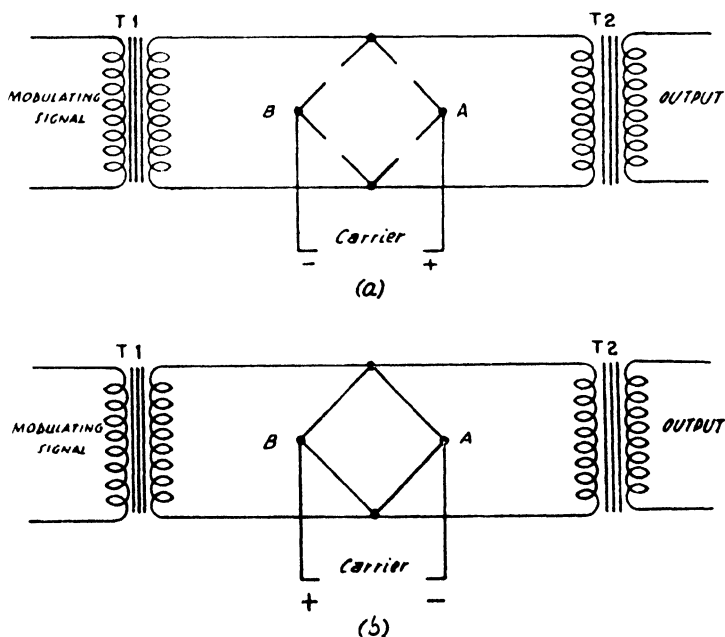


FIG. 502.—Equivalent circuits for the Cowan modulator.

preventing tone from reaching the output. This will give rise to exactly the same output waveform as that shown in Fig. 500c, and the output will contain the modulating signal, upper and lower sidebands, and additional modulation products, but no carrier.

Double-balanced bridge-ring modulators

It is possible to design modulators in which not only the carrier but also the modulating signal frequencies are suppressed. The suppression of the carrier is achieved in a manner similar to that employed in the balanced modulator, namely, by applying the

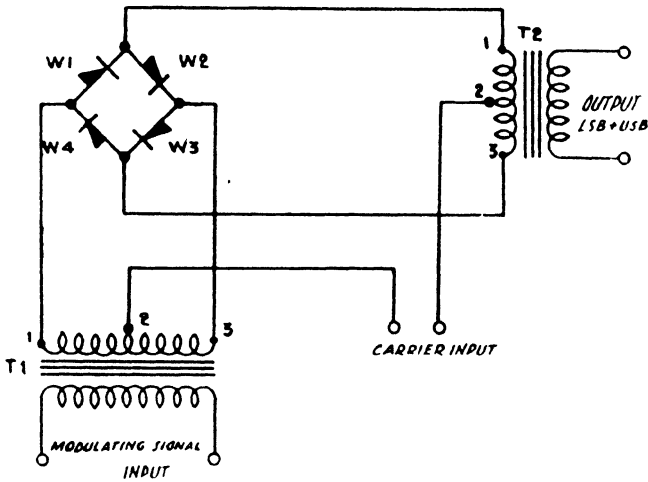


FIG. 503.—Double-balanced bridge-ring modulator.

carrier to the centre-taps of the input and output transformers, a carrier leak potentiometer being incorporated if required. In addition, the modulating signal is suppressed by arranging the four modulating rectifiers in the form of a bridge. The modulating

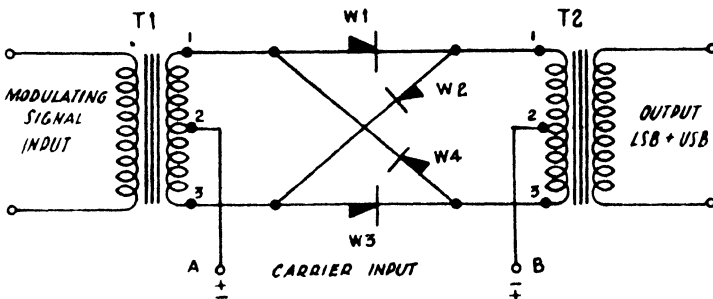


FIG. 504.—Fig. 503 redrawn in the lattice form.

signal input is applied across one diagonal of this bridge, the output being taken from the other diagonal, as shown in Fig. 503. In this manner, sidebands will be obtained in the output free from modulating signal or carrier frequencies.

This bridge network shown in Fig. 503 may be redrawn in the lattice form, as in Fig. 504.

To deduce the output waveform from such a modulator when the amplitude of the carrier input is large compared with that of the modulating signal, consider the biasing effect of the positive and negative half-cycles of the carrier input on the rectifiers.

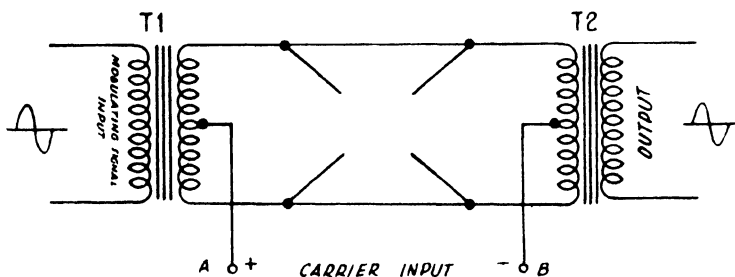


FIG. 505.—Double-balanced bridge-ring modulator with series rectifier elements forward-biased and parallel rectifier elements back-biased.

When *A* is at a higher potential than *B*, rectifiers *W1* and *W3*, being forward-biased, will offer a low impedance path, whereas rectifiers *W2* and *W4*, being back-biased, will offer only a high impedance path to the signal passing from transformer *T1* to transformer *T2*. The majority of the modulating signal current will therefore flow through the low impedance offered by *W1* and *W3* (see Fig. 505).

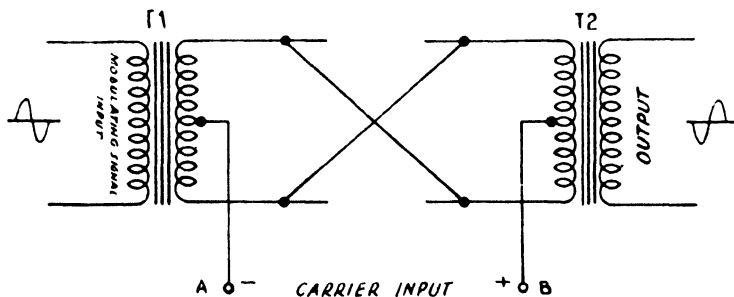


FIG. 506.—Double-balanced bridge-ring modulator with series rectifier elements back-biased and parallel rectifier elements forward-biased.

On the next half-cycle of carrier, *B* will be at a higher potential than *A*; rectifiers *W1* and *W3*, now being back-biased, offer a high-impedance path, but rectifiers *W2* and *W4* provide a low impedance

AMPLITUDE MODULATION

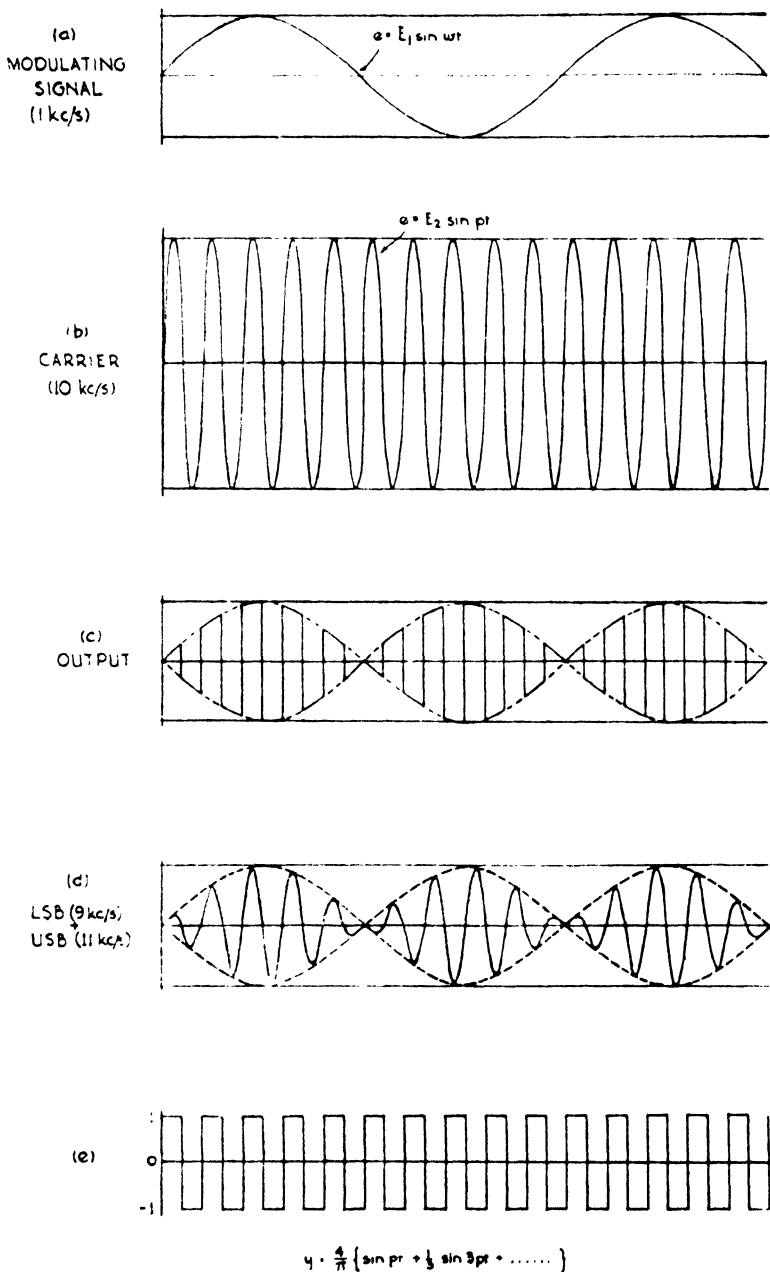


FIG. 507.—Waveform produced by double-balanced modulator when the carrier frequency is ten times the modulating frequency.

path. The majority of the signal will therefore pass from transformer $T1$ to $T2$ via the low impedance offered by $W2$ and $W4$ (see Fig. 506).

It will be noted that after each half-cycle of the carrier the signal in the output undergoes a phase-shift of 180° . Since the carrier frequency will, in general, be greater than that of the modulating signal, this change in phase will occur several times during each cycle of the input signal; the output waveform when the carrier frequency is ten times the modulating signal frequency is shown in Fig. 507c.

It will be noted that the output waveform c differs slightly from the beat note waveform d of the two sidebands. This is due to the presence of harmonics.

Inspection of the output waveform shows it to be equivalent to the modulating signal waveform multiplied by the square waveform e . Since the square waveform has unit amplitude, and the same frequency as the carrier, it may be represented by the equation:—

$$y = \frac{4}{\pi} \left[\sin pt + \frac{1}{3} \sin 3pt + \frac{1}{5} \sin 5pt + \dots \right]$$

Thus the output waveform may be represented by:—

$$\begin{aligned} E_1 \sin \omega t \times \frac{4}{\pi} \left[\sin pt + \frac{1}{3} \sin 3pt + \frac{1}{5} \sin 5pt + \dots \right] \\ = \frac{4E_1}{\pi} \left[\sin \omega t \sin pt + \frac{1}{3} \sin \omega t \sin 3pt + \frac{1}{5} \sin \omega t \sin 5pt + \dots \right] \\ = \frac{2E_1}{\pi} \left[\cos (p - \omega)t - \cos (p + \omega)t \right] \\ + \frac{2E_1}{3\pi} \left[\cos (3p - \omega)t - \cos (3p + \omega)t \right] \\ + \frac{2E_1}{5\pi} \left[\cos (5p - \omega)t - \cos (5p + \omega)t \right] + \dots \end{aligned}$$

It will be seen that this result is similar to that obtained for the balanced modulator. However, the modulating signal component is no longer present, and by comparing the equations it will be seen that the sidebands have twice the amplitude, indicating that an improvement in the output is obtained by the use of the double-balanced bridge-ring modulator.

Other forms of double-balanced bridge-ring modulators

Several arrangements of the double-balanced principle are now used. Fig. 508 shows a double-balanced modulator having an improved rectifier biasing system.

This circuit may be redrawn to emphasise the double-balanced structure by considering $T2$ as two transformers in series (Fig. 509).

To explain its operation, Fig. 508 is redrawn once again as in Fig. 510.

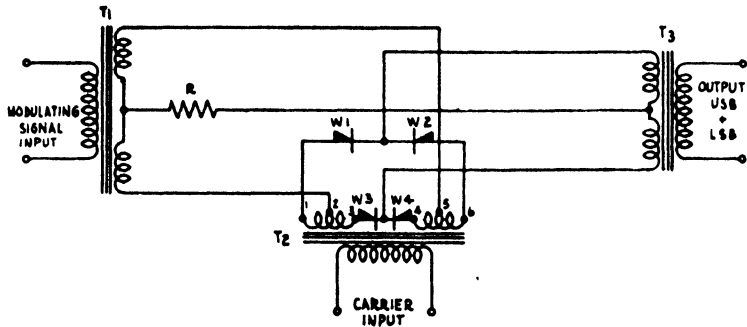


FIG. 508.—Double-balanced modulator—alternative form.

Considering the positive half-cycle of the carrier, rectifiers $W1$ and $W4$ are forward-biased, rectifiers $W2$ and $W3$ are back-biased (Fig. 511a). Considering the negative half-cycle of the carrier, rectifiers $W2$ and $W3$ are forward-biased, rectifiers $W1$ and $W4$ are back-biased (Fig. 511b).

It follows that the input signal undergoes a phase reversal on every half-cycle of the carrier, and the output waveform must therefore be the same as that produced by the first bridge-ring modulator discussed (see Fig. 507c). The output thus contains the two sidebands, but no carrier frequency and no modulating signal frequency components.

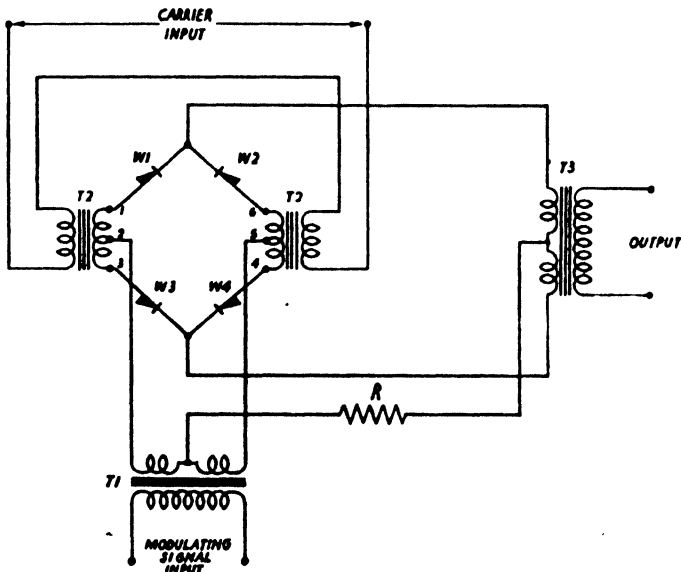


FIG. 509.—Double-balanced modulator (redrawn to explain operation).

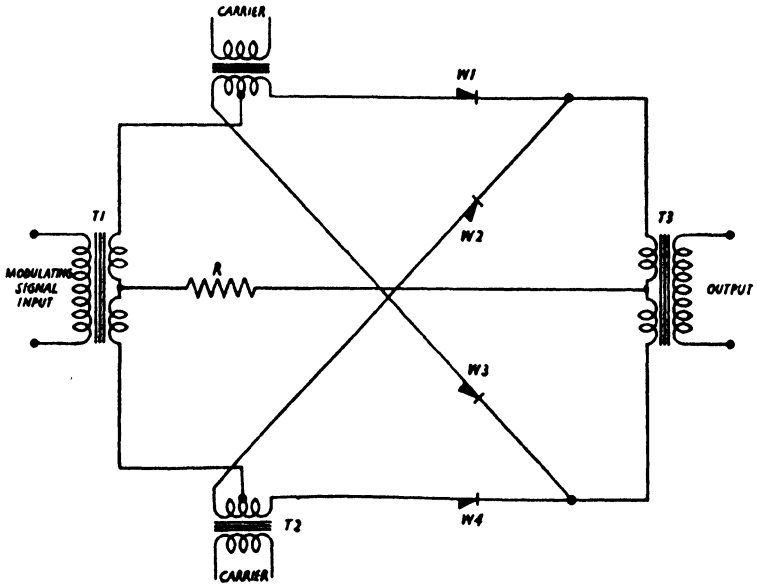


FIG. 510.—Double-balanced modulator (redrawn to explain operation).

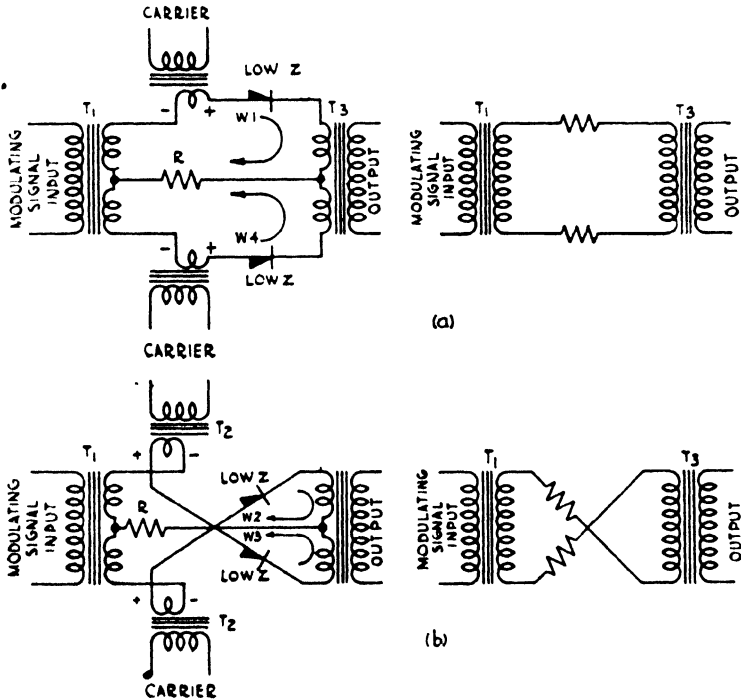


FIG. 511.—Operation of double-balanced modulator.

It will be noted that R limits the carrier current flowing, and that the potential drop across R tends to back-bias all the rectifiers. However, when in operation, one pair of rectifiers is forward-biased by half the windings of T_2 whilst the other pair are back-biased by the remaining windings.

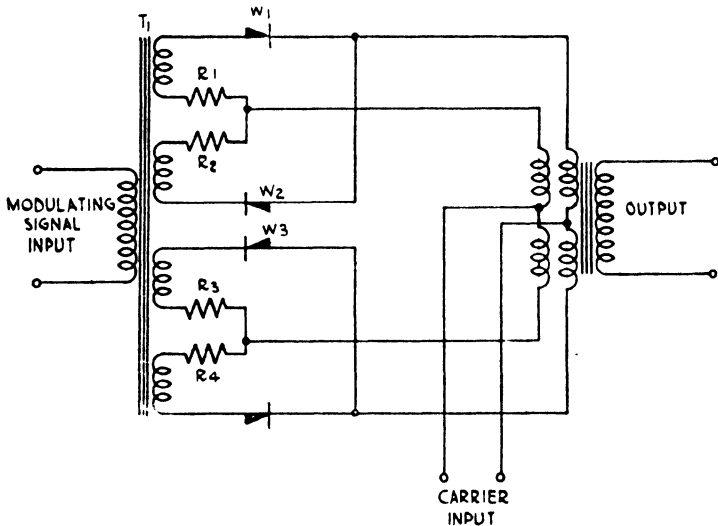


Fig. 512.—Alternative type of double-balanced modulator.

Fig. 512 shows an alternative type of modulator in use, the principle of operation is very similar and it gives the same output waveform (Fig. 507c).

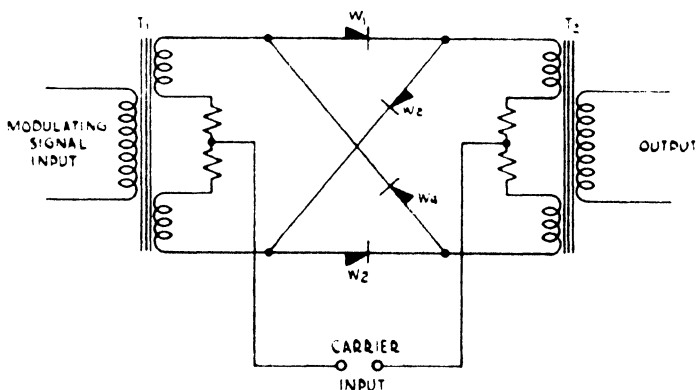


Fig. 513.—Simple double-balanced modulator.

Its derivation from the simple double-balanced modulator may be seen from Figs. 513, 514 and 515. Fig. 515 will be seen to be identical with Fig. 512.

Replacing T_1 by a transformer having one primary and four secondary windings, Fig. 514 is obtained.

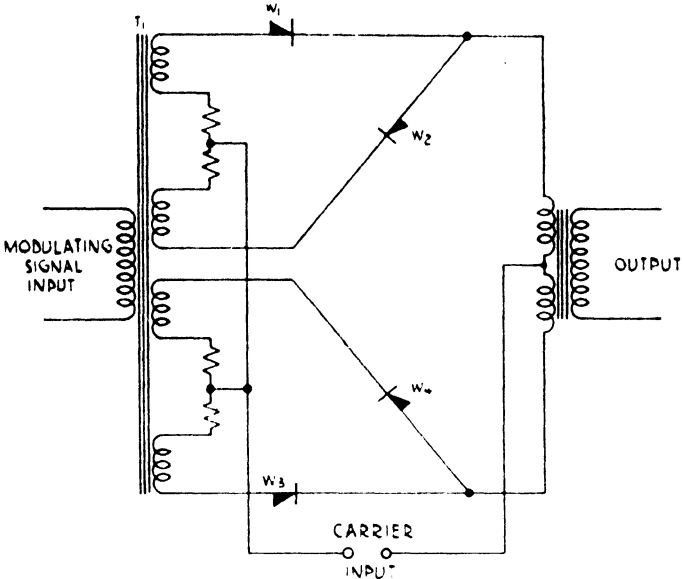


FIG. 514.—Derivation of alternative type of double-balanced modulator.

Replacing T_2 by a five-winding transformer gives Fig. 515.

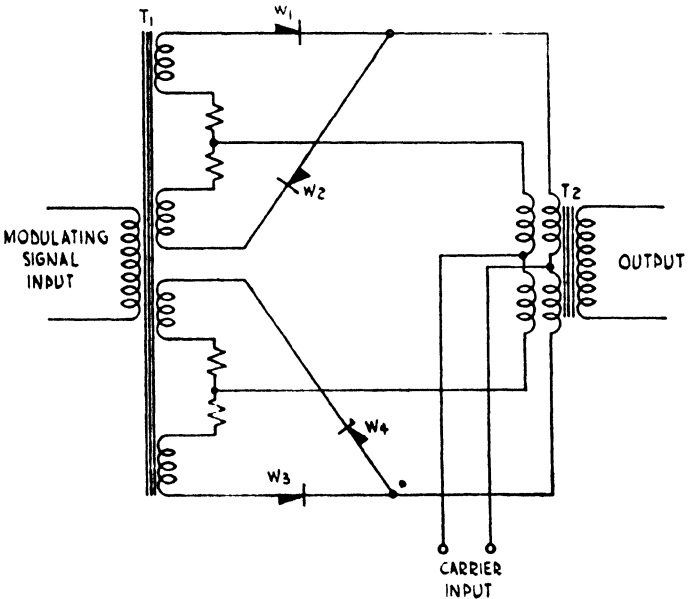


FIG. 515.—Alternative type of double-balanced modulator.

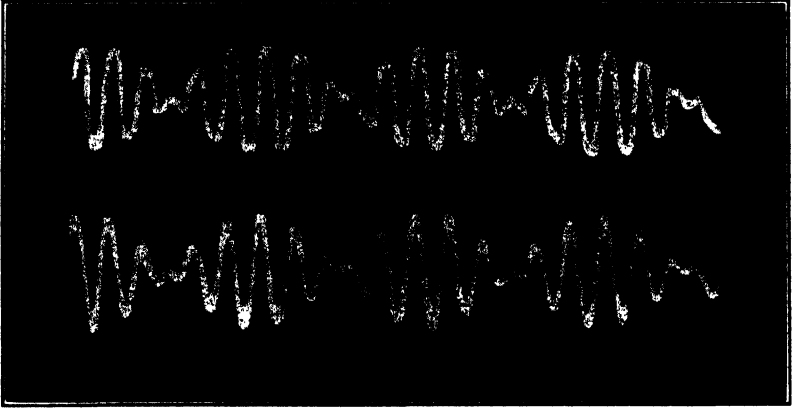


PLATE 28.—CRO traces using a double-beam tube.

- (a) Output of bridge-ring modulator (above).
 (b) Addition waveform of two sine waves having the same frequencies as upper and lower sidebands (below).

DEMODULATORS

The function of a demodulator is to reproduce the modulating frequency. The method adopted in the process of demodulation depends on whether or not the carrier frequency is present in the received waveform. If present, demodulation may be carried out simply by using a non-linear impedance, this process being known as detection.

Linear detection

When the non-linear impedance adopted is the metal rectifier or the diode valve, the process of detection resolves itself into one of rectification (*see* Fig. 516).

Assuming the non-linear impedance employed has a characteristic as shown in Fig. 517, the waveform after rectification can be considered to be the product of the input waveform and a square waveform of carrier frequency (Fig. 518).

The output waveform

$$\begin{aligned}
 &= A \sin pt \left(1 + \frac{a}{A} \sin \omega t \right) \left[\frac{1}{2} + \frac{2}{\pi} \left(\sin pt + \frac{1}{3} \sin 3pt + \dots \right) \right] \\
 &= \dots + \frac{2}{\pi} \cdot \sin pt \cdot A \sin pt \left(1 + \frac{a}{A} \sin \omega t \right) \cdot \dots
 \end{aligned}$$

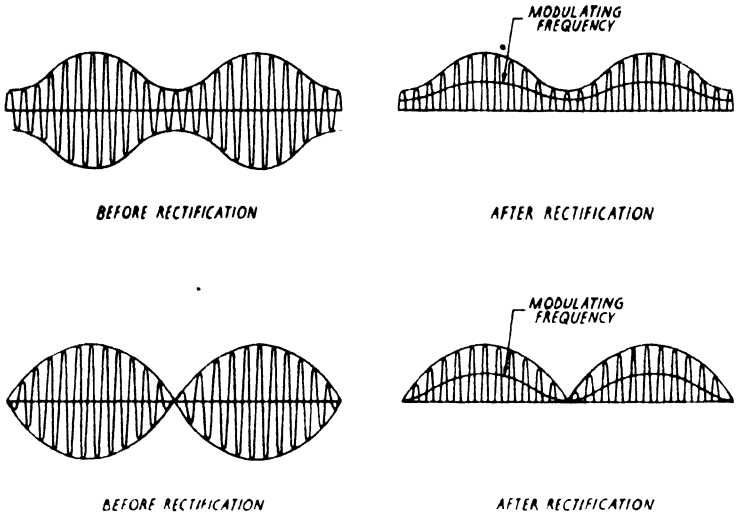


FIG. 516.—*Above* : Carrier plus both sidebands.
Below : Carrier plus one sideband (either USB or LSB)

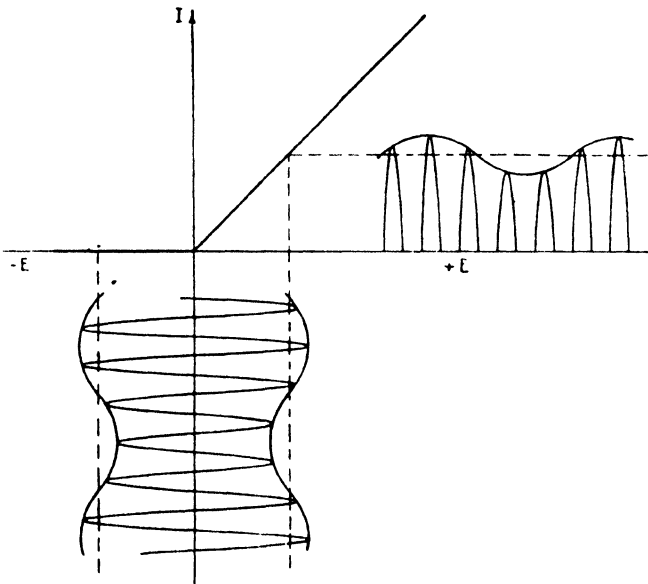


FIG. 517.—Rectification of amplitude-modulated waveform.

AMPLITUDE MODULATION

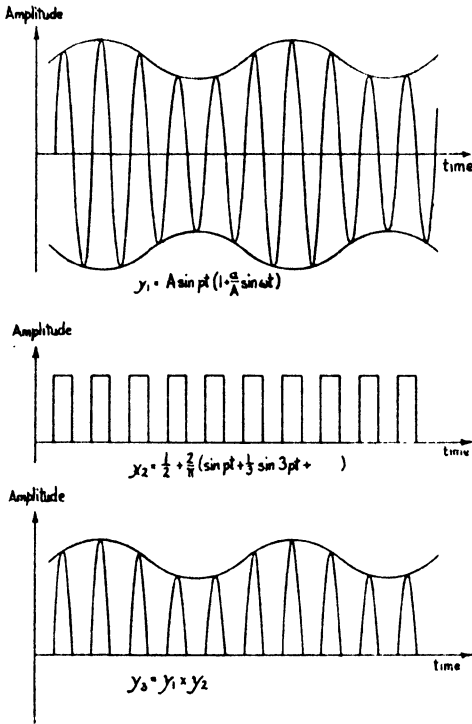


FIG. 518.—Rectifier output considered as the product of the modulated carrier input, and a square wave of carrier frequency.

$$\begin{aligned}
 &= \dots + \frac{A}{\pi} \left(1 - \cos 2pt\right) \left(1 + \frac{a}{A} \sin wt\right) \dots \\
 &= \dots + \frac{A}{\pi} - \frac{A}{\pi} \cos 2pt + \frac{a}{\pi} \cdot \sin wt - \frac{a}{\pi} \cdot \sin wt \cdot \cos 2pt
 \end{aligned}$$

↑
↑

 DC
 Modulating frequency

The term $\frac{a}{\pi} \sin wt$ corresponds to the original modulating frequency which is the lowest alternating frequency in the output. It may be separated from all the other components of detection by means of either a low-pass filter or a resistance-capacity network.

The diode as a detector

A diode valve may be used as a detector (or demodulator) for an amplitude modulated signal. When the carrier frequency is high compared with the modulating frequency, a resistance-capacity network may be used to separate out the required modulating frequency from the products of detection. Such circuits will now be considered.

When used as a detector, the diode may be arranged in the form of either a series circuit (Fig. 519a) or a shunt circuit (Fig. 519b). In each case, R is the load resistor across which potentials at the modulating frequency are required. Consider first the series diode of Fig. 519a. If an unmodulated carrier signal were applied to the input of the circuit and the load resistance R were disconnected from the circuit, electrons would flow in the direction shown, whenever the anode were made positive with respect to the cathode—that is, on every “positive” half-cycle—until the potential across C were equal to the peak voltage of the incoming carrier signal. The presence of the load resistor R causes C to discharge slightly during the half-cycle that makes the anode negative with respect to the cathode. Thus for an unmodulated input a voltage

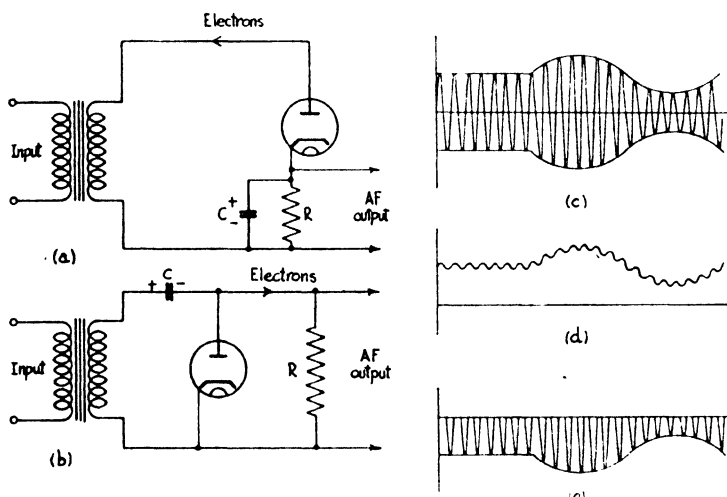


FIG. 519.—The diode as a detector, showing (a) series, and (b) shunt connections.

is developed across R which is composed of a DC voltage slightly smaller than the peak voltage of the carrier, and a carrier frequency ripple whose magnitude will depend on the time constant of R and C . If the time constant is large, the voltage across C will drop very little during one half-cycle of the carrier, and the ripple will be small. If the applied signal is a modulated carrier signal, as in Fig. 519c, and the time constant of C and R , although large compared with the periodic time of the carrier, is small compared with the periodic time of the highest modulating frequency likely to be encountered, then the voltage developed across R will have the form of Fig. 519d. That is to say, the voltage across R will still be slightly less than the peak voltage of the applied carrier (together with a carrier ripple), but in view of the low value of time constant of C and R (compared with the periodic time of the audio

modulating frequency), this voltage across R will be able to follow the audio-frequency variations in the applied HF peak voltage. The alternating component of the voltage across R is then fed *via* a DC blocking condenser to the grid of the next stage, which will be an audio amplifier.

The shunt diode (Fig. 519*b*) will give similar results. On the half-cycle of carrier that makes the anode positive with respect to cathode, electrons will flow from cathode to anode, charging the condenser C with polarity as shown. On the other half-cycle, electrons will flow downwards through the load resistance R . Across C is developed a DC voltage, plus a carrier ripple, and also an audio-frequency variation if the input is modulated and the time constant of C and R is of suitable value. The voltage across R will be as shown in Fig. 519*e*.

Metal rectifier as detector

In the above example of diode detection the diode valve may be replaced by a metal rectifier. In fact any method of rectification employing metal rectifiers may be used as a form of detector.

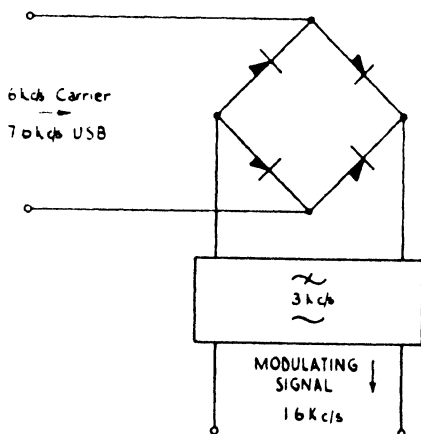


FIG. 520.—Metal rectifier detector.

Fig. 520 shows the use of a full-wave bridge rectifier as a demodulator, a low-pass filter being employed, in this case, to eliminate the unwanted products of demodulation. To ensure efficient operation, a path must be provided, usually within the LP filter, for the DC component of demodulation.

Square-law detection

Square-law detection is the name given to detection by means of a device such that the application of a sinusoidal input gives rise to components in the output proportional to the square of the input. Anode bend detection employing a valve biased to

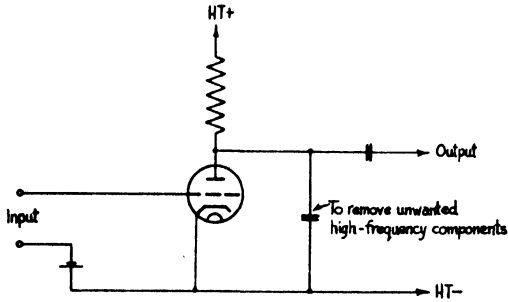


FIG. 521.—Anode bend detector.

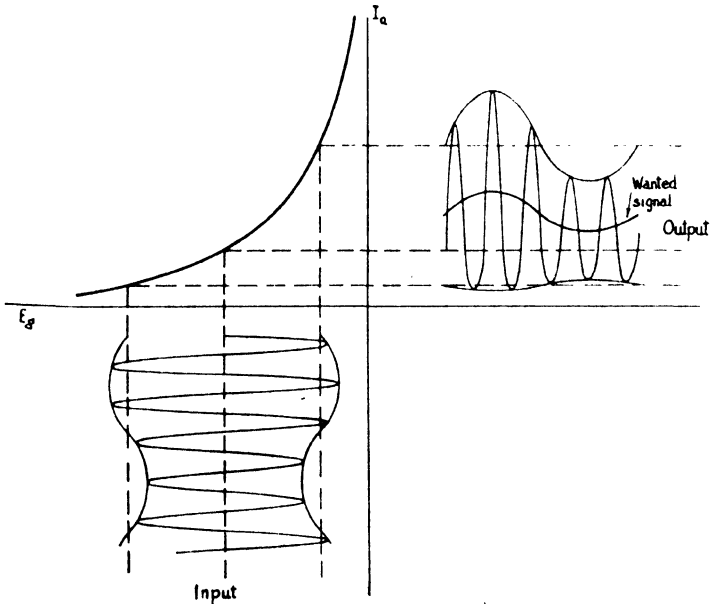


FIG. 522.—Principle of square-law (anode bend) detection.]

operate on the curved portion of its characteristic is an example of square-law detection (see Fig. 521 and Fig. 522).

A summary of the principal frequencies produced by both square-law modulation and square-law detection are given in Fig. 523.

f = frequency of modulating signal.

f_c = frequency of carrier.

AMPLITUDE MODULATION

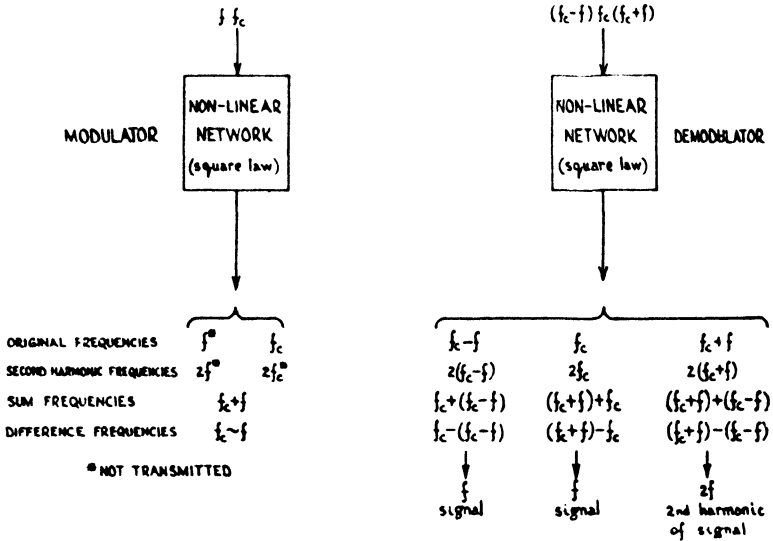


FIG. 523.—Frequencies produced by square-law modulation and demodulation.

DEMULATION IN SUPPRESSED CARRIER SYSTEMS

As has already been stated, when only a single sideband and no carrier is transmitted, the modulating frequency may be reproduced by *modulating* the received waveform, using a local oscillator to

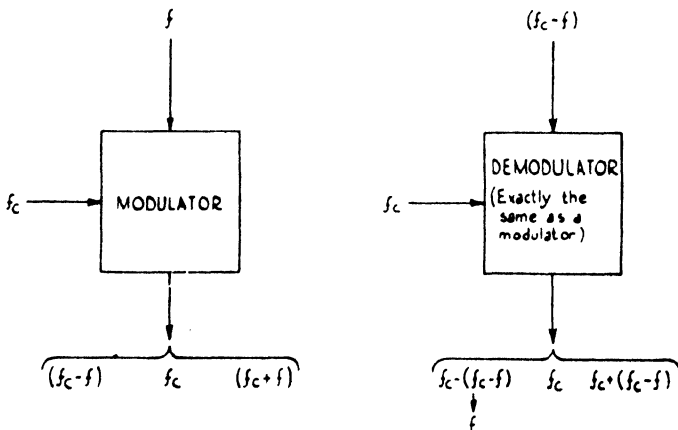


FIG. 524.—Frequencies produced by modulation and demodulation.

generate the carrier frequency. Any of the forms of modulator described above may be employed. Suppose that the lower sideband ($f_c - f$) is received: modulating it with the carrier f_c will produce an upper sideband ($2f_c - f$) and a lower sideband f (see Fig. 524). Since only the lower sideband is required, the upper sideband must be removed by means of a filter.

Demodulation using simple balanced modulator

The circuit used for modulation (see Fig. 497) may also be used for demodulation. The carrier frequency generated by the local oscillator is fed into the centre-taps of the transformers, as before, the incoming sideband being applied to transformer T_1 . The output

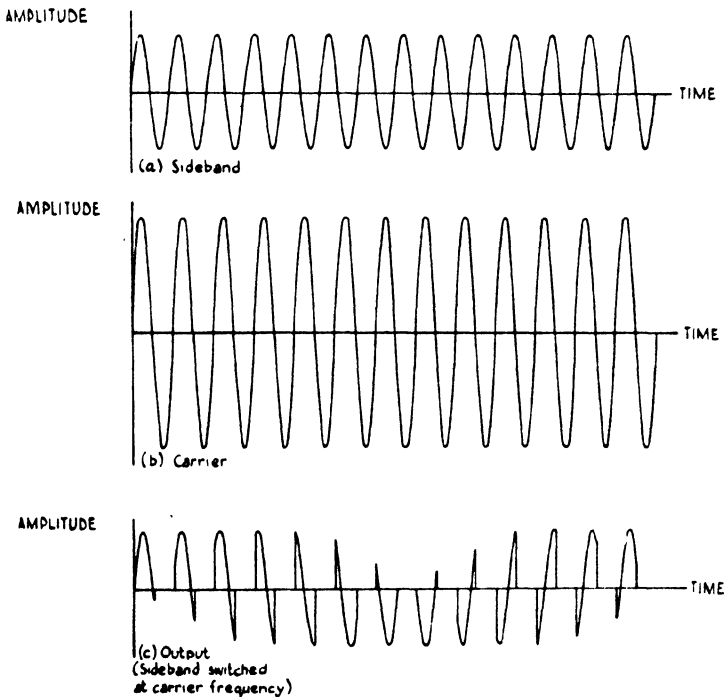


FIG. 525.—Simple balanced demodulator waveforms.

waveform (see Fig. 525c) is produced by the sideband being switched on and off at the carrier frequency. This output waveform contains a component corresponding to the original modulating signal. This may be shown mathematically:—

Let the received sideband be:—

$$e_1 = E_1 \sin (p + \omega)t$$

and let the local oscillator generate a signal:—

$$e_2 = E_2 \sin (p + \delta)t,$$

which represents a signal having a slightly different frequency from that originally fed to the modulator at the sending end.

If E_2 is large compared with E_1 , then the output waveform corresponds to a square waveform of unit amplitude and frequency $\frac{p + \delta}{2\pi}$, multiplied by the received sideband (see pages 508-9).

The output waveform y_3 is therefore :—

$$\begin{aligned} y_3 &= \frac{E_1}{2} \sin(p + \omega)t + \frac{2E_1}{\pi} \sin(p + \omega)t \cdot \left\{ \sin(p + \delta)t \right. \\ &\quad \left. + \frac{1}{3} \sin 3(p + \delta)t + \dots \right\} \\ &= \frac{E_1}{2} \sin(p + \omega)t + \frac{2E_1}{\pi} \left\{ \sin(p + \omega)t \cdot \sin(p + \delta)t \right. \\ &\quad \left. + \frac{1}{3} \sin(p + \omega)t \cdot \sin 3(p + \delta)t + \dots \right\} \\ &= \frac{E_1}{2} \sin(p + \omega)t + \frac{E_1}{\pi} \left\{ \cos(\omega - \delta)t - \cos(2p + \omega + \delta)t \right\} \\ &\quad + \frac{E_1}{3\pi} \left\{ \cos(2p - \omega + 3\delta)t - \cos(4p + \omega + 3\delta)t \right\} + \dots \end{aligned}$$

The required signal is represented by the term $\frac{E_1}{\pi} \cos(\omega - \delta)t$,

and it will be seen that its frequency has been changed by $\frac{\delta}{2\pi}$.

This shows that the signal obtained will have the same frequency as the modulating signal only when the two carrier oscillators are exactly synchronised, otherwise the received frequency will have been changed by the amount of the discrepancy between the two oscillators.

Provided only one sideband has been transmitted, the phase with which the carrier frequency is replaced is of no consequence.

Demodulation using double-balanced modulator

In a similar manner, the double-balanced modulators shown in Figs. 503, 508 and 512 may be used for demodulation. Once again, the carrier frequency must be generated by a local oscillator.

The output waveform (see Fig. 526c) is produced by introducing 180° phase-shifts in the sideband at the carrier frequency. Owing to the double-balanced nature of the modulator, there will be neither sideband nor carrier components in the output. The output will, however, contain a component corresponding to the original modulating signal.

This may be shown mathematically; assume that the received sideband is :—

$$y_1 = E_1 \cdot \sin(p + \omega) \cdot t$$

and that the local oscillator generates a signal

$$y_2 = E_2 \cdot \sin(p + \delta) \cdot t$$

then the output waveform will be :—

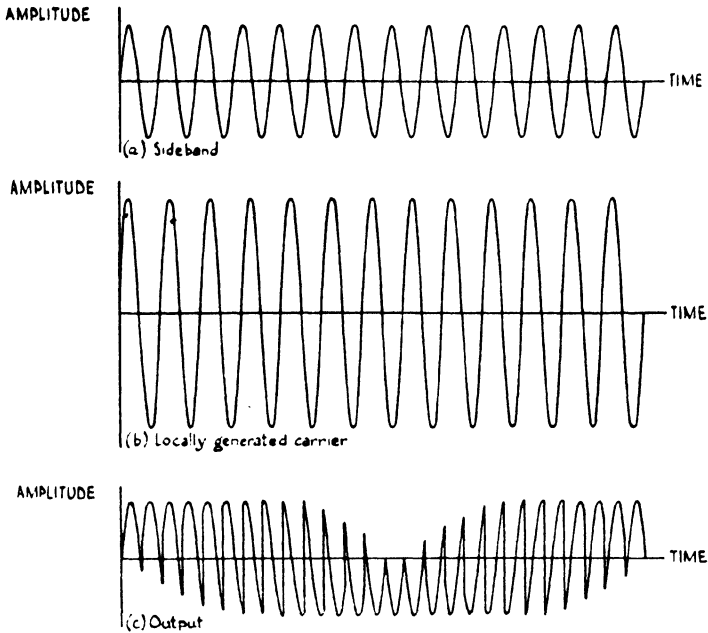


FIG. 526.—Double-balanced bridge-ring demodulator waveforms.

$$\begin{aligned}
 y_s &= \frac{4E_1}{\pi} \cdot \sin(p + \omega)t \cdot \left\{ \sin(p + \delta)t + \frac{1}{3} \sin 3(p + \delta)t + \dots \right\} \\
 &= \frac{2E_1}{\pi} \left\{ \cos(\omega - \delta)t - \cos(2p + \omega + \delta)t \right. \\
 &\quad \left. + \frac{1}{3} \cos(2p - \omega + 3\delta)t - \frac{1}{3} \cos(4p + \omega + 3\delta)t + \dots \right\}
 \end{aligned}$$

The required signal component is $\frac{2E_1}{\pi} \cos(\omega - \delta)t$, *i.e.*, it has twice the amplitude of that obtained in the case of the simple balanced modulator. The same need for synchronism between the two carrier oscillators is still applicable.

AMPLITUDE, PHASE, AND FREQUENCY MODULATION

So far mention has only been made of amplitude modulation. There are two other modulation systems occasionally used in line communication, namely, "phase modulation" and "frequency modulation". Briefly, the characteristic features of the three systems are as follows:—

(1) *Amplitude modulation (AM)*.—The intelligence is contained in the amplitude term; the carrier amplitude is usually a linear function of the instantaneous amplitude of the modulating waveform.

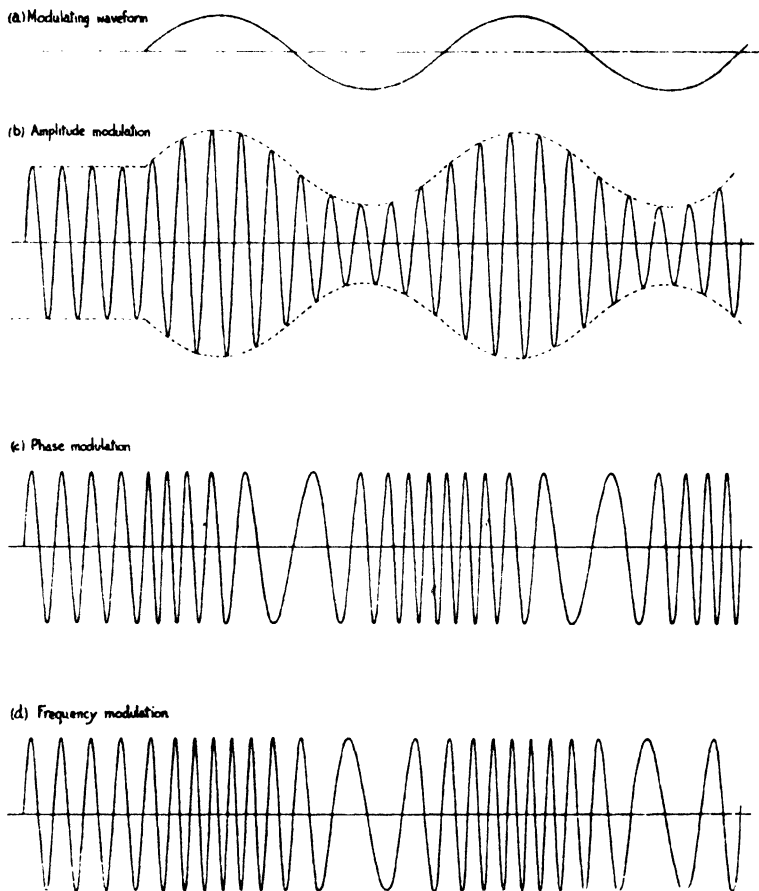


FIG. 527.—Waveforms using a sine wave as the modulating signal.

(2) *Phase modulation (PM)*.—The amplitude of the carrier is constant; the intelligence is imposed by causing the instantaneous phase term to be a linear function of the instantaneous amplitude of the modulating waveform.

(3) *Frequency modulation (FM)*.—The instantaneous frequency is a linear function of the instantaneous amplitude of the modulating waveform.

Fig. 527 shows a carrier (b) amplitude-, (c) phase-, and (d) frequency-modulated by a given sinusoidal modulating signal.

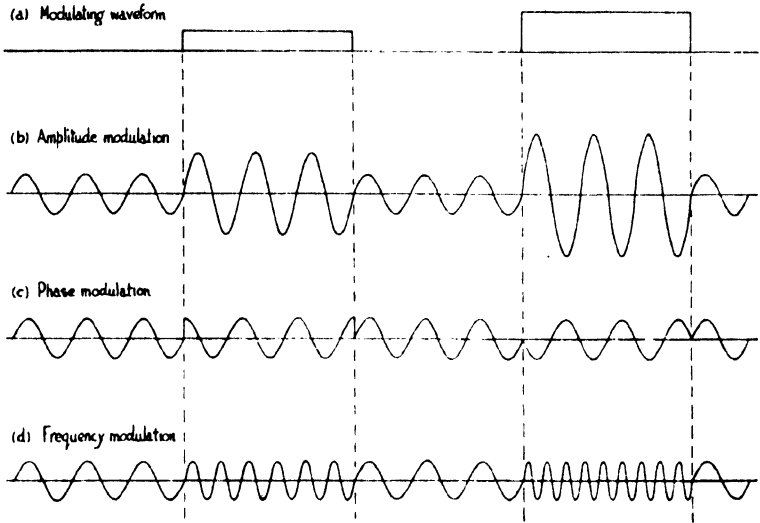


FIG. 528.—Waveforms using a square-wave as the modulating signal.

Fig. 528 shows a carrier (*b*) amplitude-, (*c*) phase-, and (*d*) frequency-modulated by a square-wave modulating signal.

CHAPTER 12

THE CATHODE RAY OSCILLOSCOPE

The study and measurement of alternating currents and voltages is a most important one from the communications point of view. It has been shown that meters may be constructed which give certain restricted information about, say, an alternating voltage. Such a voltmeter records either the RMS, the mean, or the peak value of the voltage, depending on the calibration, but it gives no indication of the purity of the waveform; that is to say, a meter cannot differentiate between a voltage having components at different frequencies and a pure sinusoidal voltage of the same RMS (or mean or peak) value. Nor, if used to measure voltages at different parts of a circuit, can a meter give information regarding phase relationship.

A meter suffers also from other disadvantages due to the inertia of its moving parts. For instance, the pointer does not deflect instantaneously; and having been deflected, does not immediately come to rest, however "dead beat" the action may be. All voltmeters have a finite impedance and represent a load on any circuit to which they are applied, taking power from it and thereby disturbing the circuit conditions and giving rise to a false reading. In addition, no meter is completely satisfactory over a large range of frequencies such as is encountered in communication engineering.

The cathode ray oscilloscope (or "CRO", as it is usually called) overcomes all these disadvantages, and gives a complete graphical representation of an alternating quantity. It is thus a valuable instrument for use in communication engineering.

The principle is that a stream of electrons is focused into a narrow beam and made to impinge on a fluorescent screen; this glows visibly where hit by the electron beam, which thus produces a spot of light. The electron beam, and the spot it produces on the screen, can be deflected horizontally and vertically by two independent deflector systems, the deflection produced being proportional to the voltage (or current) applied to the system.

If, for example, it is desired to examine the waveform of a 50 c/s voltage, the spot is made to move at a uniform speed across the screen from left to right, and at the same time the alternating voltage is applied to give a vertical deflection. Since the horizontal deflection at any instant is proportional to time, and the vertical deflection is proportional to the instantaneous value of the voltage,

the spot will trace out a graph showing the instantaneous voltage as a function of time. When the spot reaches the right-hand side of the screen it can be brought back very rapidly, and in such a way that when the process is repeated the spot traces out the same path as on the previous occasion. In this way a stationary picture of the waveform is obtained.

The construction of the tube and the principles underlying its operation will now be discussed in greater detail.

THE CATHODE RAY TUBE

A simple cathode ray tube is shown in Fig. 529. It consists of an evacuated glass bulb containing a heated cathode, which may be directly or indirectly heated, and an anode which is maintained at a positive potential relative to the cathode. The anode is made

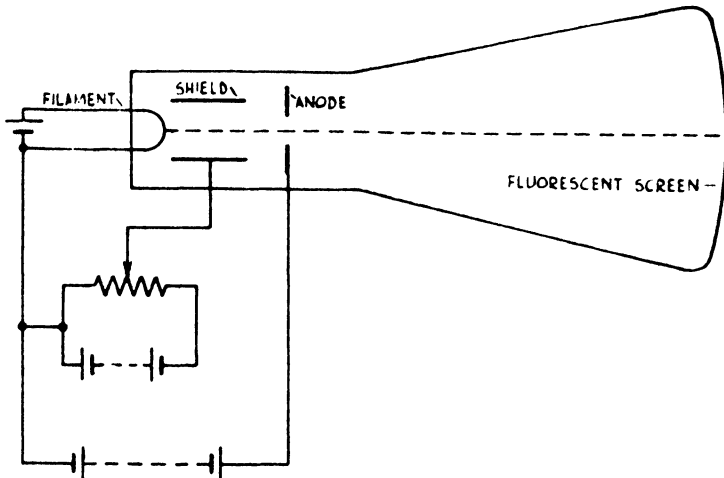


FIG. 529.—Simple cathode ray tube.

in the form of a disc having a hole in the centre, and is situated close to the cathode. Electrons emitted by the cathode are attracted towards the anode. Most of the electrons will be attracted to the anode, but some will pass through the central hole and continue to travel in a straight line until impinging on the fluorescent screen at the end of the tube. This screen is formed by coating the inside of the glass with a fluorescent substance which glows under the impact of electrons. Where the electrons strike this fluorescent screen, therefore, a patch of light appears.

In order to increase the number of electrons passing through the central anode aperture, a cylindrical shield is fitted so as to concentrate the electrons in transit from cathode to anode into a narrow beam. This effect is obtained by maintaining the shield at a negative potential relative to the cathode. The electrons are repelled by this shield, and the electron stream is therefore concentrated along its axis, thereby increasing the proportion of electrons that pass through the anode.

Brilliance

The brilliancy of the light spot on the fluorescent screen will depend on the energy contained in the electron stream—that is, on the number and velocity of the electrons bombarding the screen at any instant. In order to obtain a sufficiently powerful electron stream, an anode potential of the order of 1000 volts is required in the normal hot-cathode or low voltage tube. The potential of the shield will to a certain extent affect the electron stream in the same way that the grid potential affects the anode current in a thermionic valve.

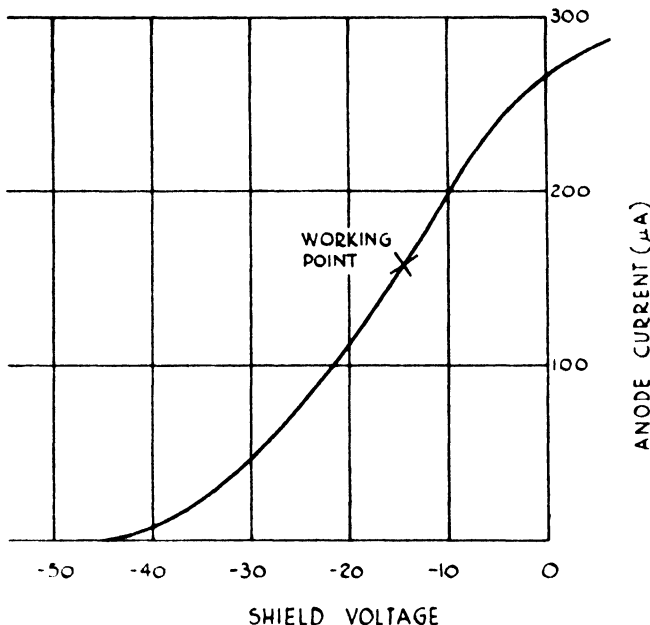


FIG. 530.—Characteristic of cathode ray tube.

Fig. 530 shows how the shield potential affects the anode current; it will be seen that the more negative the shield becomes, the smaller the number of electrons drawn towards the anode; but, due to the concentrating effect of the shield, the greater the percentage of these electrons arriving on the fluorescent screen. These two factors have a conflicting effect on the number of electrons actually arriving at the screen, and at some point on the curve the screen will receive the maximum number of electrons and the light spot will have maximum brilliance.

The fluorescent screen

Many substances are fluorescent; that is, they have the property that they emit light when subjected to electron bombardment. This property is, however, possessed by different substances

to different degrees ; for instance, one substance may emit a greater intensity of light than another for a given rate of bombardment ; again, the frequency—that is, the colour of the light emitted—varies from substance to substance. All fluorescent materials continue to emit light for some time after the electron bombardment has ceased ; this is known as “after-glow”, and its duration varies with different substances from a few microseconds to many seconds. In some applications, it is an advantage for a tube to have a long after-glow.

The phenomenon of fluorescence has not yet been satisfactorily explained, but certain general observations may be made. In general, fluorescent materials consist of a crystalline metallic salt containing a minute trace of impurity. This impurity, known as the activator, is essential, since the base substance in its pure state frequently has no fluorescent properties. The base and the activator together determine the fluorescent properties described above. A short representative list of fluorescent materials used for the screens of cathode ray tubes is given below.

TABLE XVI
Fluorescent screen materials

<i>Base</i>	<i>Activator</i>	<i>Colour of trace</i>
*Zinc silicate	manganese	blue-green
Zinc sulphide	manganese	orange
Zinc sulphide	silver	blue
Zinc sulphide	copper	green

* Occurs in nature as “willemite”, and is the material most commonly used for CRO screens.

In selecting a material for the screen of a cathode ray tube, these various properties must be considered in relation to the use to which the tube is to be applied. A screen that emits a high intensity of light for a given rate of electron bombardment is desirable in practically all cases, since otherwise high anode voltages would be required to produce the required brilliancy of the image. It is also essential that the substance can be applied to the end of the tube in such a way that it produces a uniform screen.

If the tube is to be used for visual examination of waveforms, as is usually the case, the trace must be of a colour that produces minimum fatigue and eye strain whether viewed in daylight or in artificial lighting. The best colour for this purpose is found to be green, though blue may be slightly better in artificial light. If the waveform under examination is recurrent, and the spot of light may be made to trace the same path again and again, an after-glow of 10 or 20 microseconds will be sufficient, with the natural persistence of vision, to give the impression of a stationary trace

at all but the lowest frequencies. For visual examination of very low-frequency waveforms, and in particular for transients, *i.e.*, non-recurrent waveforms, a longer after-glow is desirable and may be of the order of several seconds.

If the tube is intended only for photographic work a blue trace is desirable, the blue light being more "actinic" than the green; that is, it has a greater effect on the light-sensitive material of the photographic film for a given exposure. In a general purpose tube, intended for both photographic and visual examination, a screen is used that gives a blue-green trace. Tubes for television purposes are required to give a white trace, which is obtained by using a mixture of two or more fluorescent materials each giving a different portion of the spectrum.

FOCUSING

For oscillograph work, a very small sharply defined light spot is required; and although a certain amount of focusing can be obtained by adjustment of the shield potential, this in itself is not sufficient, and it is necessary to adopt some additional focusing device. There are three principal methods by which this may be done. The first is by using a "soft" or gas-focused tube, which has an inherent focusing effect on the electron stream; the second method is electrostatic focusing, in which the electron stream is passed through an electrostatic field that is so shaped as to cause the electrons to converge on the screen. This type of focusing has the advantage that it can be controlled easily. The third method, electromagnetic focusing, is rarely used, except in tubes intended for television work.

Gas-focusing

In the gas-focused or soft tube, a high vacuum is first formed in the normal way, and then a small quantity of inert gas such as argon or helium is introduced. The passage of the electron beam through the rarified gas has the effect of ionising the gas—that is, splitting the atoms into free electrons and positive ions. The free electrons add themselves to the electron beam, and the relatively heavy positive ions drift slowly towards the cathode. Due to their mutual attraction the electrons and ions form a narrow beam, that is, the presence of the positive ions exerts an automatic and very effective focusing effect on the electron beam. This type of tube has two main disadvantages:—

(a) *Loss of focus at high frequencies.*—At high deflecting speeds, the relatively heavy positive ions tend to lag behind the electron beam, due to their greater inertia, resulting in loss of focus at high frequencies.

(b) *Limited life.*—The positive ions moving towards the cathode ultimately strike it, doing appreciable damage to the sensitive emitting surface. This limits the life of the tube to a few hundred hours.

Electrostatic focusing

The electrostatic method of focusing employs a complex anode system. Fig. 531 shows an arrangement using three anodes. This is the configuration of electrodes used nowadays in the majority of cathode ray tubes, though the potentials applied to the various

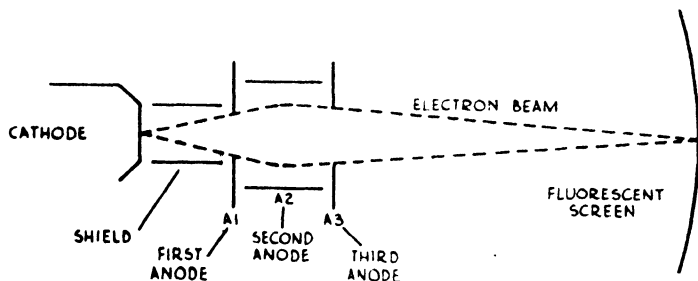


FIG. 531.—Electrostatic focusing in a three-anode tube.

anodes differ. The whole electrode system forms an electronic "lens" which acts on the electron beam in much the same way as does a converging optical lens on a beam of light. The theory of electron optics, which explains the action of an electric lens, will not be discussed; in any case the practical electric lens is usually designed empirically. In general, the first and third anodes are kept at fixed potentials and the shape of the electric field is controlled by varying the potential on the second anode; in this way the focal length of the electric lens may be adjusted to give optimum focusing of the electron beam, producing a very small spot of light on the fluorescent screen. Brilliancy is still controlled by the shield potential.

The potential of the shield, however, has a distinct effect on the focus, as has also the potential of the focusing anode on brilliancy. The result is that to a certain extent the two controls must be adjusted together to give optimum focus at the required brilliancy. It may be stated here that the trace should never be brighter than is absolutely necessary; the brighter the trace, the greater the impact of the electron beam on the fluorescent screen, and the shorter the life of the fluorescent material.

Electromagnetic focusing

This type of focusing was used in the earliest tubes and may still be found in the case of tubes used for particular purposes. It is not generally so convenient as electrostatic focusing for a general purpose tube.

In an electromagnetically focused tube, a simple electrode structure is required consisting simply of cathode, negative potential shield and high potential perforated anode; focusing is then carried out by means of a coil surrounding the neck of the tube, as

shown in Fig. 532*a*. The focusing action of this coil, which carries a direct current, is as follows. The axis of the electromagnetic field due to the coil will lie along the axis of the tube, and consequently electrons moving along this axis will experience no force due to the (parallel) magnetic field. Suppose, however, that an electron leaves the axis and acquires a velocity v making an angle α with the axis of the tube, and therefore with the magnetic field (Fig. 532*b*). This electron will have a velocity component $v \cos \alpha$ parallel to the field and $v \sin \alpha$ at right angles. The component parallel to the field can be neglected for the moment, since this gives rise to no force on the electron; but the velocity at right angles to the field will result in a deflecting force. The direction of this force may be seen from Fig. 532*c*. For suppose the direction of the field is down into the paper, the axis of the field passing through the point O , then, by Fleming's left-hand rule, and remembering that a moving electron is equivalent to a current in

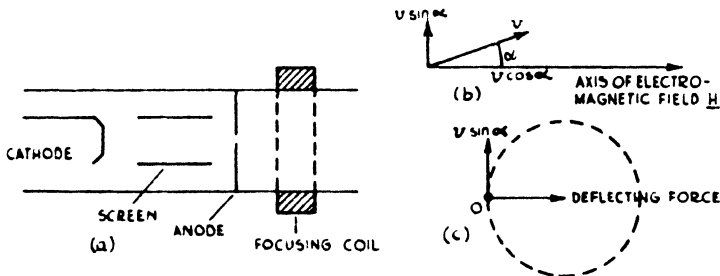


FIG. 532.—Position of focusing coil and principles of electromagnetic focusing.

the reverse direction, it is seen that a force acts on the electron at right angles to its transverse velocity. This force will be constant and equal to $Hev \sin \alpha$ dynes, where e is the charge on the electron in electrostatic units. Under these circumstances, the electron will move in a circle, so far as its transverse motion is concerned. If the radius of its transverse orbit is r cm, and the mass of the electron is m grams, then the centrifugal force will be given by $\frac{m (v \sin \alpha)^2}{r}$ dynes, and this force must be balanced by the deflecting force due to the magnetic field. Thus:—

$$Hev \sin \alpha = \frac{m (v \sin \alpha)^2}{r}$$

i.e.
$$r = \frac{mv \sin \alpha}{He} \text{ centimetres.}$$

The electron is constrained to move in a circle of this radius; its tangential velocity will remain at $v \sin \alpha$ since no force acts on the electron in the direction of this velocity at any time, and consequently there can be no acceleration or deceleration in this

direction. The electron describes one complete revolution of its circular orbit in a time :—

$$t = \frac{2\pi r}{v \sin \alpha} = \frac{2\pi m}{He} \text{ secs.}$$

The time taken for the electron to describe a complete revolution and arrive back on the axis of the magnetic field is independent of both the velocity of the electron and on its departure angle α . During this interval of time, however, the electron will have travelled a distance $\frac{2\pi m}{He} \cdot V$ cm, where V is the axial velocity of the electrons in the beam, and will be considered to have the same value for all the electrons. The motion of the electrons therefore is a spiral one, and if the cathode is considered as a point source of electron emission, the electron stream will be focused to a point at positions distributed at distances $\frac{2\pi mV}{He}$ cm along the axis of the tube. If the distance between cathode and screen is l cm, then a field of strength

$$H = N \cdot \frac{2\pi mV}{el} \text{ gauss}$$

will focus the electron beam accurately on to the screen, where N is a whole number. In practice the smallest field capable of giving a focusing action is employed, so that $N = 1$, and the electrons are brought together on the screen after performing only one revolution in the spiral path.

DEFLECTION

So far, only the general construction of the cathode ray tube has been considered, together with the arrangements for producing on the fluorescent screen a small sharply defined spot of light. It is now necessary to investigate the means by which this spot may be moved across the screen under the influence of externally applied forces. There are two methods, known respectively as electromagnetic and electrostatic deflection. These will now be considered separately.

Electromagnetic deflection

Fig. 533 shows how a pair of deflecting coils may be arranged at the neck of the tube to produce a magnetic field at right angles to the electron beam. The direction of the deflection is given by Fleming's left-hand rule, the electron beam being subject to a deflecting force in just the same way as a current-carrying conductor. It is important that the magnetic field produced by the coils be uniform and symmetrical. The deflection is proportional to the magnetic field; that is, proportional to the current passing through the deflecting coil. Such a coil has an inductive impedance and may therefore disturb the circuit under test.

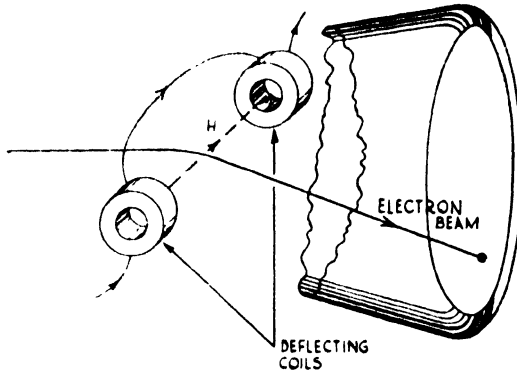


FIG. 533.—Electromagnetic deflection.

Electrostatic deflection

In the electrostatic method of deflection, two plates are arranged one on each side of the beam, as shown in Fig. 534. If a voltage is applied across these deflector plates, the beam will be attracted towards the positive plate and repelled from the negative one, so that the spot of light on the screen will change its position.

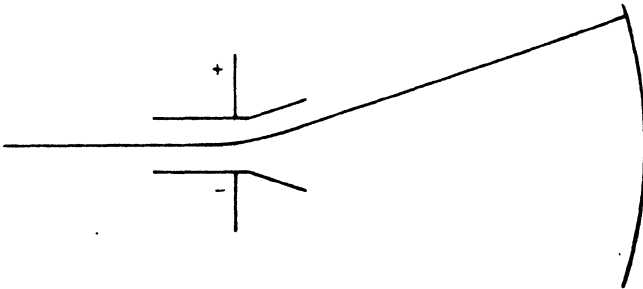


FIG. 534.—Electrostatic deflection.

The deflection corresponding to a particular value of deflecting voltage (or current) will be directly proportional to the strength of the deflecting electrostatic (or magnetic) field, to the length of the electron path lying in the field, and to the distance of the fluorescent screen from the deflecting system. For high sensitivity all these constant factors are made as large as possible subject to limitations of space. The deflection also depends on the anode voltage, to which it is inversely proportional, since a higher anode voltage gives an increased electron velocity and hence a smaller deflection. Thus "hard" tubes, which have a higher anode potential than "soft" tubes, are less sensitive. Again, a cold-cathode or high-voltage tube is less sensitive than a hot-cathode or low-voltage tube. In Fig. 534 the deflector plates are very close together at

the end nearer the cathode to give maximum sensitivity, but diverge towards the fluorescent screen in order that a wide angular deflection of the beam may be possible.

If the voltage across the deflector plates (or the current through the deflecting coils) is alternating, the spot will follow the variations in voltage (or current) exactly and without appreciable time lag. As the spot of light is moved back and forth under the influence of an alternating potential applied to the deflector plates, it will trace out a straight line; this, due partly to the normal persistence of vision and partly to the "after-glow" properties of the fluorescent material, will appear as a continuous line, unless the frequency is very low, in which case the actual motion of the spot may be followed by the eye.

TIME BASES

If a second pair of deflector plates are so fitted as to produce an independent deflection at right angles to the first, then the spot of light may be moved to any position on the screen instead of merely in a straight line. The plates that cause a horizontal deflection are called the "X" plates, and those causing a vertical deflection are called the "Y" plates. If the voltage under examination is applied across the Y plates, and at the same time a voltage is applied to the X plates that will cause the spot to travel at a uniform rate across the screen, then clearly the trace on the screen will be an accurate graph showing the instantaneous voltage plotted against time.

If the voltage applied to the Y plates is a transient—that is, if it occurs once only—it may be impossible to examine the trace by eye, and one must therefore photograph the trace as it is produced, or else use a fluorescent screen that will retain the trace for a reasonable period after its formation. If, however, the voltage under examination is recurrent, the voltage on the X plates may be so controlled that it moves the light spot uniformly across the screen from left to right, and having reached the limit of its sweep to the right it then returns the spot very rapidly to the left where it begins its sweep again. If it can be arranged that the second and subsequent traces lie exactly on top of the first, then the eye will obtain the impression of a stationary trace on the screen; Fig. 535 shows such a trace. It will be seen from this example that, during the time that the voltage on the Y plates passes through two complete cycles, the deflecting voltage on the X plates moves the spot once across the screen from left to right, giving the trace *ABCDEF*. Then the spot is moved very rapidly from right to left giving the trace *FA*, which is called the fly-back. This fly-back appears inevitably since the return of the spot, in practice, occupies a finite time; it is, however, much fainter than the main trace, because the fly-back time is small.

The means whereby the deflecting voltage on the X plates is controlled is called a "time base", and in order to ensure that

a stationary trace appears on the screen it is necessary to "synchronise" the time base with the voltage under examination ; that is to say, the time occupied by the sweep and the fly-back must be equal to the time occupied by a whole number of cycles of the recurrent voltage on the Y plates. Methods of producing a time base of the required shape, and then synchronising it as required, will be considered separately.

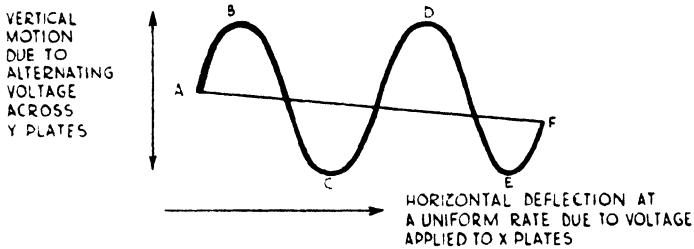


FIG. 535.—Formation of an oscilloscope trace.

The time base that would be required to produce the trace of Fig. 535 is what is known as a "linear" time base ; that is, the voltage applied to the X plates takes the form shown in Fig. 536.

Fig. 537 shows a simple time base using a gas relay. This consists of a triode that has been made "soft" by the inclusion, after evacuation of the air has been completed, of a small quantity of an inert gas such as neon, argon or helium ; certain devices of this type have been given the trade name of "thyatron". For a given anode voltage and a sufficient negative bias on the grid, this valve will behave as an ordinary triode biased beyond cut-off ;

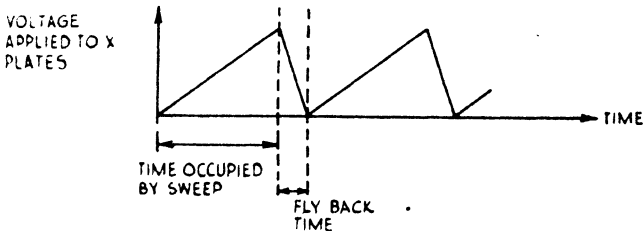


FIG. 536.—Linear time base.

that is, no anode current will flow. Now suppose that the grid bias remains constant whilst the anode voltage is increased ; a value of anode voltage will be reached, where anode current begins to flow, and it is here that the similarity to the ordinary "hard" triode ends. For the inert gas, being at low pressure, is readily ionised by the impact of the electron stream on its molecules. At each collision more electrons are released to join the electron stream, and these in turn collide with other molecules and cause further ionisation. In this way a very rapid cumulative current is obtained, giving

a very low resistance between anode and cathode. Once ionisation has taken place and current has started to flow, this condition will persist until the anode voltage is removed—or at any rate reduced to a very low value, much lower than the value of anode voltage at which anode current would cease in a similarly biased “hard” triode.

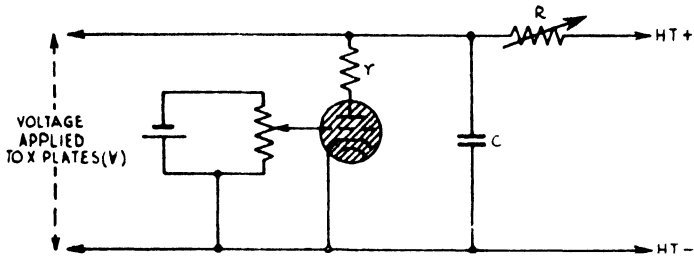


FIG. 537.—Simple time base using a gas relay.

In the circuit of Fig. 537, suppose that the HT voltage is 200 volts and that it has just been switched on. The condenser C will begin to charge up through the resistance R and the voltage V across the condenser will rise exponentially at a rate controlled by the time constant CR . When V reaches a certain value, say 150 volts, the gas relay will “trigger”, this triggering point being determined by the negative potential on the grid. Once the relay has triggered, its resistance becomes negligible; and the condenser C discharges through the resistance r , which is a small resistance (about 500 ohms) to limit the anode current in the relay. The value of r is a compromise, since it must be large enough to limit the anode current to a safe value, and at the same time it must be small enough to ensure a rapid fly-back. The voltage V therefore decreases exponentially at a rate determined by the much smaller time constant Cr until it reaches a value of about 10 volts, when the ions in the tube re-associate, and the anode current is once more



FIG. 538.—Output waveform from circuit of Fig. 537.

cut off by the grid bias. This process repeats itself, the voltage V varying with time, as shown in Fig. 538. It will be noticed that such a time base does not give a strictly linear deflection, but the discrepancy can be minimised by ensuring that the condenser only charges up to about 20 per cent. of the available HT voltage, since the growth of charge on the condenser over this interval is approximately linear. This method of securing a linear time base has the disadvantage of requiring a high value of HT supply voltage. For

suppose that the X plates require a deflecting voltage of 100 volts to give a full-screen deflection, the HT supply required must be, at a minimum, 500 volts.

An alternative method of obtaining a linear scan is shown in Fig. 539. Here the condenser is charged through a saturated diode, which acts as a constant-current device, and therefore the condenser C will charge linearly. If the diode, which must be

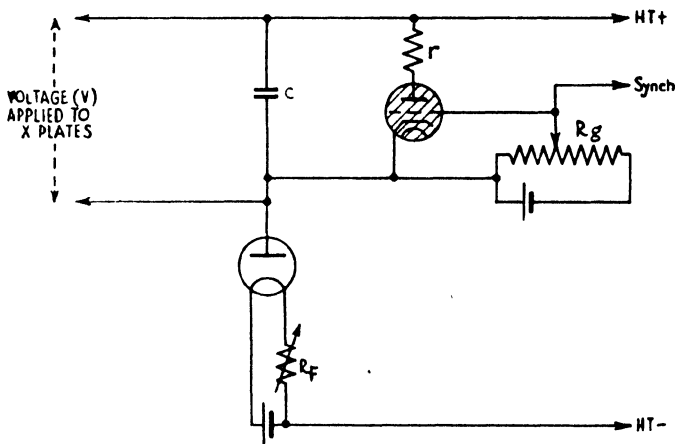


FIG. 539.—Time base circuit using a saturated diode.

directly heated, is given a reduced filament current (controlled by R_f), it is possible to arrange that the emission is so much reduced that the valve saturates for an anode voltage of, say, 20 volts. If, therefore, the anode voltage is raised above 20 volts, however much it may be increased, the anode current will remain constant; and the condenser, charging through the diode, will therefore charge linearly until it attains a voltage within 20 volts of the available HT supply voltage. Thus a linear sweep is obtained provided only that the available HT voltage is about 20 volts in excess of the deflecting voltage required to give a full-scale deflection. The fly-back is obtained by using a gas relay across the condenser as in the previous circuit. The charging rate is controlled by the resistance R_f and the amplitude of the sweep by R_g .

Fig. 540 shows a circuit that operates in much the same way, but here a pentode is used as a constant-current charging device. This method has the advantage that a directly heated valve is not essential, and consequently a separate source of DC LT voltage is not required. The principle of this circuit is that a pentode, having suitable constant voltages applied to screen and grid, has an anode current that is virtually independent of anode voltage provided the latter exceeds, say, 60 V. Thus the voltage on the condenser C increases linearly until it attains a value about 60 V below the available HT supply. The charging rate is controlled by the

potentiometer P , which varies the value of anode current taken by the pentode; and the amplitude of the sweep is controlled by Q , which varies the triggering point of the gas relay.

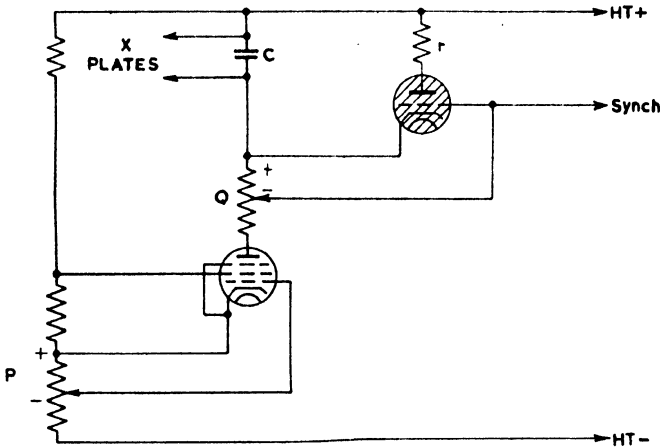


FIG. 540.—Time base circuit using a pentode charging arrangement.

Time base circuits employing gas relays have one common disadvantage, namely, that they cannot be used to produce very high velocity sweeps and so cannot be used with CROs intended for examining high-frequency waves. This is due to the comparative slowness with which the ionised gas re-associates after the relay has triggered, since the condenser cannot begin to charge again until re-association is complete. It must be remembered that a saw-tooth waveform contains not only the fundamental, but also an infinite series of harmonics, of which at least the first ten are of sufficient amplitude to be important and require production by the saw-tooth generator. For these reasons, time base circuits of the type described will not operate satisfactorily at frequencies greatly in excess of 10 kc/s.

Time base using a transitron saw-tooth oscillator

Another time base suitable for low and medium frequency work is shown in Fig. 541. This transitron saw-tooth oscillator has the advantage that it uses only one valve.

Consider that at a given instant the valve is drawing a high anode current that is greater than the charging current of C_1 through R_2 . The condenser C_1 will discharge, causing a decrease in anode voltage. As the anode voltage falls, the anode current will at first remain practically constant, and then commence to fall as the "knee" of the anode characteristic is passed; this results in a rising screen current which causes a falling screen voltage due to the drop across R_3 , and therefore a falling suppressor voltage due to the coupling condenser C_2 . These factors cause a further decrease in anode current and the whole process continues

cumulatively until the anode current is completely cut off, the suppressor by this time being at a negative potential.

This condition persists for a short time while C_1 begins to charge up exponentially *via* R_1 and R_2 . This means that the potential of the anode rises, and a point is eventually reached where the valve takes anode current again at the expense of the screen, causing a rise in screen volts and therefore in suppressor volts. This process also is cumulative, giving a rapid increase in anode current, which

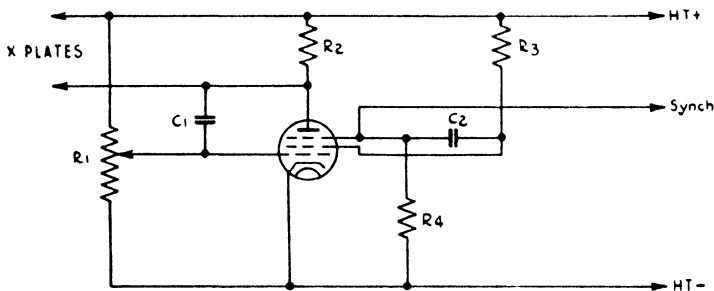


FIG. 541.—Transatron saw-tooth oscillator.

discharges C_1 and leaves the suppressor positive. If the suppressor grid takes a large current when it is driven positive, and if C_2 is sufficiently small compared with C_1 , the suppressor grid will be driven negative by the voltage drop across R_4 due to suppressor current flowing before the discharge of C_1 is complete. This cuts off the anode current, and C_1 begins to recharge.

With suitable choice of components, the voltage across C_1 has a saw-toothed waveform and may be used to provide a linear time base (*see* Fig. 542).

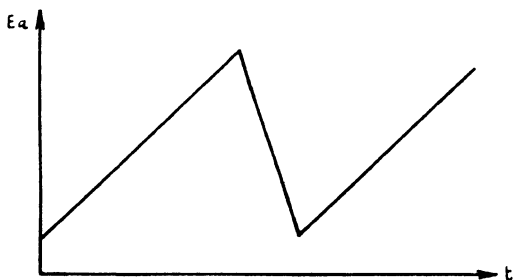


FIG. 542.—Saw-toothed output of transatron oscillator.

The potentiometer R_1 controls the total space current and therefore the duration of the periods of charge and discharge; it thus determines the sweep frequency of the time base.

Synchronisation of time bases

It has been mentioned that, in order to obtain a stationary trace, the time taken by the time base sweep plus the fly-back time must be equal to the time occupied by a complete number of cycles of the voltage under examination. The frequency of the time base is controllable over wide limits by a coarse control that switches in suitable values of capacity, and by a fine control in the form of the potentiometer that controls the charging current. *e.g.*, *P* in Fig. 540. The mere adjustment of time base frequency is not, however, sufficient to ensure a stationary picture, for this would demand that the frequency of the time base and of the voltage under examination both remain absolutely constant. It is therefore necessary to employ some device to synchronise the time base with the voltage under examination.

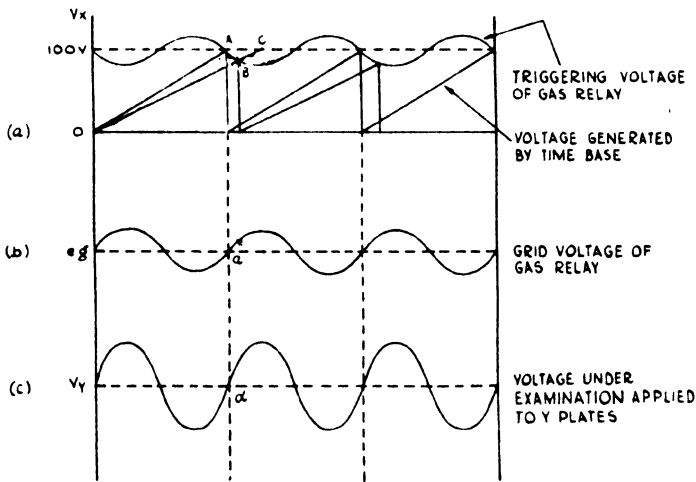


FIG. 543.—Illustrating principle of synchronisation.

If a small portion of the voltage applied to the Y plates is also fed to the grid of the gas relay, it will cause the grid voltage to vary a little about its normal value at the frequency of the voltage under examination. Now suppose that the gas relay is adjusted to trigger at, say, 100 volts, and that the time base frequency has been adjusted as nearly as possible so that the relay triggers at the end of each complete cycle of the voltage on the Y plates (*see* Fig. 543); this should lead to a stationary trace showing one complete cycle (assuming, for simplicity, that the fly-back time is zero).

When the time base is correctly adjusted, the gas relay is triggering at *A* corresponding to the point α on the Y plate voltage, and to point *a* on the grid voltage of the gas relay; *i.e.*, the gas relay is triggering at the correct value of 100 V, the grid voltage having been adjusted to give this condition. Now suppose that the

time base frequency falls below its correct value. This means that at the point α on the Y plate voltage curve, the gas relay has not yet triggered because the triggering voltage of the relay (100 V, say) has not yet been attained. Since the grid voltage of the gas relay is varying, however, so also will the triggering voltage of the relay, with the result that the relay will trigger at the point B ; that is, at a lower voltage, and consequently earlier, than would have been the case (point C) without the application of a synchronising voltage. A similar argument holds if the time base frequency rises above its correct value, the synchronising voltage this time delaying the triggering of the relay. Provided, therefore, that the time base frequency is reasonably close to the value required, it is possible to arrange that for a very small value of synchronising voltage the relay always triggers within a very small fraction of a cycle of its correct value. Theoretically, however large the discrepancy, a sufficiently large synchronising voltage will synchronise the time base perfectly; but large synchronising voltages, though producing a stationary trace, may give rise to a distorted picture. It is therefore important that the synchronising voltage be as small as possible and the time base frequency adjusted with reasonable accuracy, in which case a perfectly stable trace will result.

High-frequency time bases

It has been mentioned that the gas relay or soft valve type of time base does not give satisfactory operation at high frequencies, and so for a time base frequency in excess of 10 kc/s it is necessary

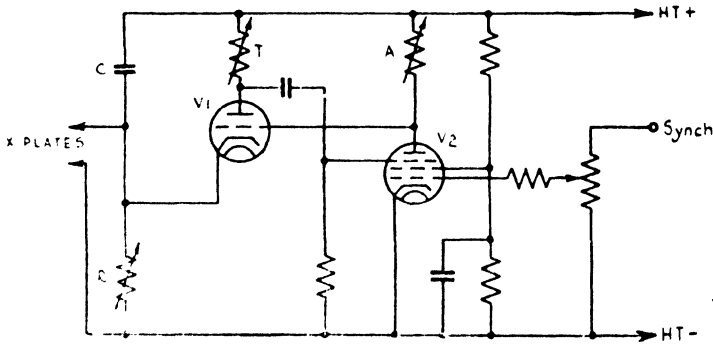


FIG. 544.—Puckle's hard valve time base.

to use a form of time base employing hard valves only. One such circuit, due to Puckle, is shown in Fig. 544, and its operation is somewhat similar to that of the multivibrator relaxation oscillator (see p. 490).

To explain the action of this circuit, consider the condenser C uncharged; V_1 will then take no anode current, the anode and cathode both being at the same potential, namely, that of $HT+$.

The grid of V_1 , moreover, will be at a lower potential than the cathode, due to the voltage drop across A caused by the anode current of V_2 . In this condition the condenser C will begin to charge exponentially through R ; and as the voltage across C increases, the voltage of the cathode of V_1 will fall relative to HT+. Initially the grid of V_1 is at a lower potential than the cathode; and if this bias is made fairly large, by adjustment of A , then the valve V_1 will be cut off until the voltage across C has reached a predetermined value. When V_1 starts to draw anode current, its anode potential drops, and this drop is applied to the suppressor grid of V_2 ; this causes a rise in anode potential of V_2 which is applied to the grid of V_1 , causing a further increase in anode current. Thus the condenser begins to discharge, and the discharge current increases very rapidly, so giving the fly-back. As soon as the condenser has discharged the anode current ceases, and the consequent rise in V_1 anode potential drives the suppressor grid of V_2 positive, and hence the grid of V_1 negative, thus giving a rapid restoration to the original conditions.

This circuit will produce time base frequencies up to about 100 kc/s. The resistance R determines the charging rate of C , and is designated the "velocity" control; it is the fine adjustment on the sweep frequency. Resistance T limits the discharge current and is a control on the fly-back time; it is usually called the "trigger" control. Resistance A determines the negative bias on the grid of V_1 when the sweep is about to start, and so therefore controls the voltage that is being applied to the X plates when V_1 begins to draw anode current. It therefore determines the length of the sweep, and is called the "amplitude" control.

Finally, the synchronising voltage is applied to the grid of V_2 ; suppose that, at a given instant, this is negative. The resultant reduction in anode current of V_2 causes the anode potential of V_2 to rise; this drives the grid of V_1 more positive, thereby reducing the anode potential at which V_1 commences to draw anode current. The explanation of synchronisation as applied to soft valve time bases will therefore apply equally in this case; since, if the time base is running slow, a negative synchronising voltage is being applied to the grid of V_2 , and therefore a much larger positive voltage to the grid of V_1 , at the instant when V_1 should have triggered. The result is a lowering of the triggering voltage of V_1 , so that the triggering takes place almost instantaneously.

ADDITIONAL FEATURES

Deflection amplifiers

If the voltage under examination is applied direct to the Y plates, the voltage range is limited by the sensitivity of the tube. For instance, if the voltage is small, say of value 2 volts RMS, the trace may have an amplitude of only 2 mm. In order to make possible

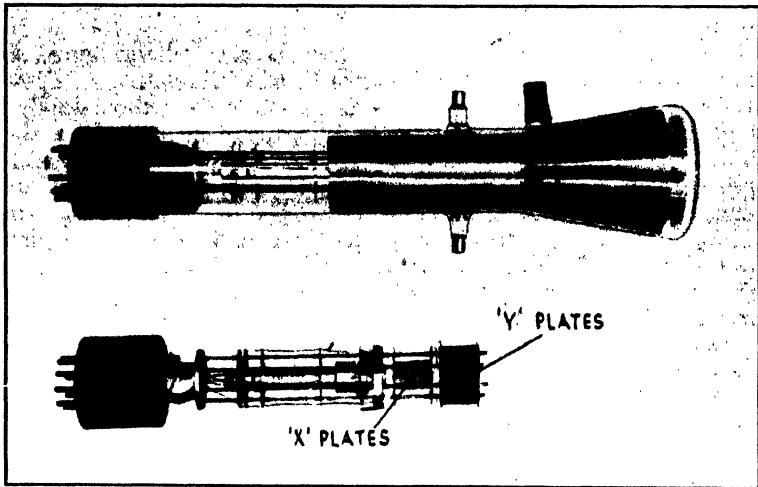


PLATE 29.—Single-beam cathode ray tube.

the examination of small voltages, deflection amplifiers are usually built into the CRO. These are usually straightforward single-stage amplifiers of variable gain, and they enable voltages of very small amplitude to be examined. It is important that a deflection amplifier should introduce as little distortion as possible, since otherwise the CRO becomes valueless as a means of estimating the amount of distortion in a given waveform. It should also be realised that however good a deflecting amplifier may be, it will inevitably introduce distortion at very low and at very high frequencies, so that in general the use of deflection amplifiers limits the frequency range of the instrument.

Attenuators may also be provided for the examination of high voltages in excess of the voltage required for full-screen deflection.

Double-beam tube

A cathode ray tube of the type so far discussed is able to produce only a single trace, showing how a single voltage varies with time ; whereas it is often required to compare two such traces. This may easily be done by the use of the double-beam tube due to Fleming-Williams.

Fig. 545 shows how the two beams are obtained. The electrode system is exactly the same as that in a single-beam tube, as are the methods of focusing and brilliancy control. The only difference is that the single beam, after formation, is split by the presence of an earthed

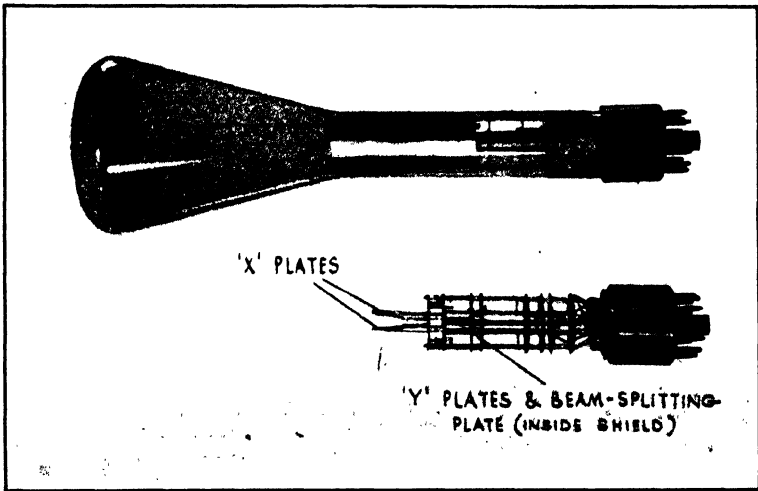


PLATE 30.—Double-beam cathode ray tube.

“ beam-splitting plate ” E mounted between the Y deflector plates. Besides splitting the single beam into two separate beams, this plate acts as a deflecting plate common to the two beams. Thus the first beam may be deflected by applying a voltage between E

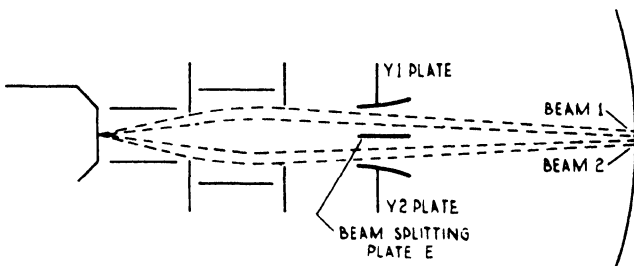


FIG. 545.—Fleming-Williams' double-beam tube, showing beam-splitting plate.

and Y_1 , and the second beam may be deflected independently by a voltage between E and Y_2 . The two beams, after formation, pass between normal X plates, which control the sweep of both beams simultaneously by means of a common time base.

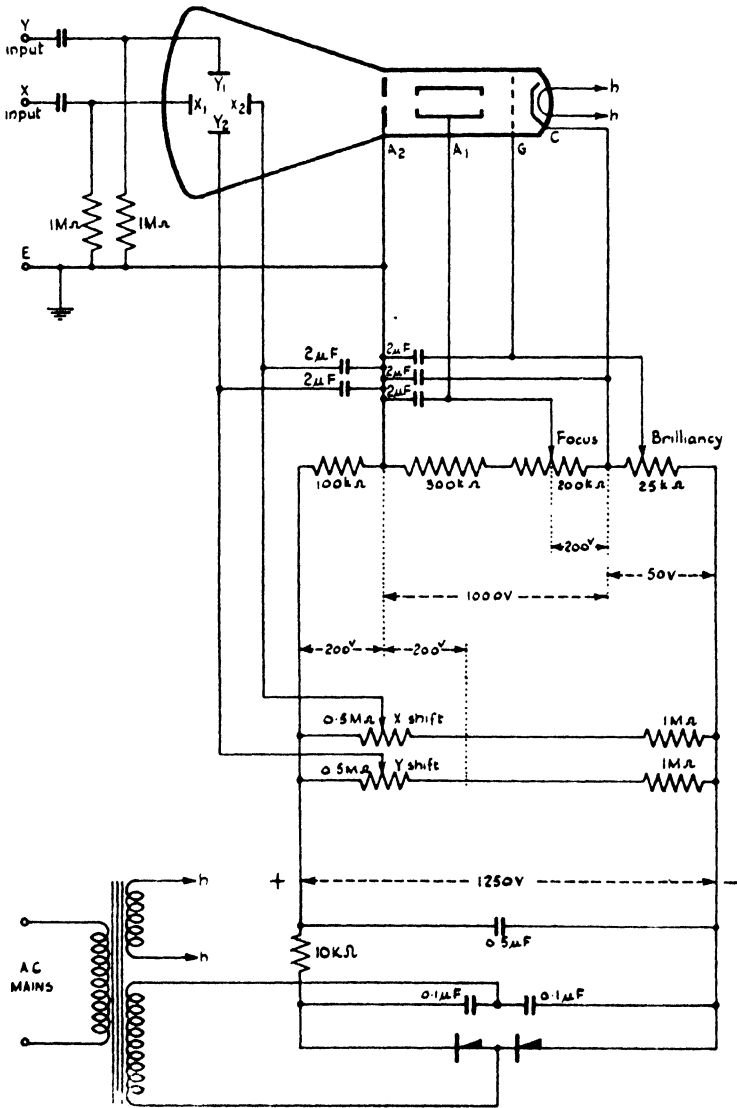


FIG. 546.—Typical power supply for single-beam electrostatically-focused tube.

Shifts

In the double-beam tube it is essential to provide some means of separating the two traces produced on the screen ; for, as shown in Fig. 545, the beams when not deflected will be very close together and will give a single spot, or two spots very close together. This separation of the traces is easily accomplished by applying a steady positive potential to Y_1 and Y_2 relative to E . If these potentials are made independently variable, it is possible to move the two traces vertically to any part of the screen. This vertical or Y-shift facility is usually provided also on single-beam tubes. An X-shift is also provided on tubes of both types in the form of a variable steady potential applied to the X plates in addition to the time base voltage. By the use of these two shifts, the trace may be moved to any part of the screen.

Distortion

If the screen is flat, equal increments in deflecting voltage will produce equal deflections. As, in practice, the screen is curved, a small amount of distortion is introduced. With normal tubes, however, this is of the order of 2 per cent., and can be neglected.

Power supply

Fig. 546 shows a typical power supply arrangement for a single-beam electrostatically-focused tube.

APPLICATIONS OF THE CRO

Voltage measurements

The examination of voltage waveforms applied to the Y plates has already been considered in order to describe the working of the CRO. In addition to the examination of the waveform, it is possible to use the CRO to measure the amplitude of the voltage. In order to do this the tube must be calibrated ; that is to say, if it is known that a certain voltage produces a definite amplitude of trace, then twice that voltage will produce a trace having twice that amplitude. A CRO may be thus calibrated either for peak values or for RMS values ; and if, in addition, the deflection amplifiers and/or attenuators are calibrated, a wide range of fairly accurate measurement can be obtained.

Current measurements

Current waveforms may be examined by passing the current through a non-inductive resistor and examining the voltage drop across this in the normal way. If it is required to *measure* current, the resistance must be small in order to minimise its effect on the circuit under test ; it will therefore usually be necessary to use a calibrated amplifier for such a measurement. One particularly useful application of the double-beam tube is that it enables current and voltage tests to be made simultaneously on a circuit, so that

the phase relationship between current and voltage may be seen clearly by comparing the two traces.

Some CROs have electromagnetic deflector coils fitted as an alternative to electrostatic deflector plates; in such a case current measurements can be made directly; but in general the impedance of the deflector coils is such that this method introduces greater errors than does the presence of a small resistance.

Frequency comparison

Frequencies may readily be measured if the frequency of the time base is known. Thus if the time base is sweeping 1000 times per second, and a stationary trace of one cycle appears on the screen, the voltage on the Y plates must have a frequency of 1000 c/s. Similarly, if two full cycles appear on the screen, the frequency must be 2000 c/s. This method will be only an approximate one if the applied signal is allowed to synchronise the time base. Suppose that the frequency were not 2000 c/s, but, say, 2100 c/s; then, if the time base were set to 1000 c/s, it would be synchronised by the work voltage and would actually run at 1050 c/s, giving two complete cycles on a stationary trace.

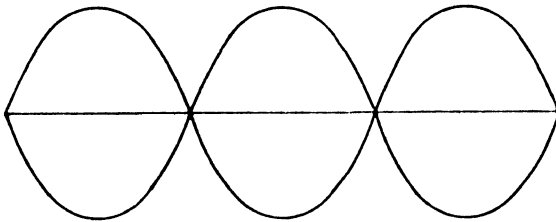


FIG. 547.—Trace when frequency applied to Y plates is $1\frac{1}{2}$ times the sweep frequency.

It is however not essential to use the applied voltage for synchronising the time base. Suppose a 50 c/s mains supply, at a suitably reduced voltage, is applied to the grid of the gas relay, and the time base is set to give a 50 c/s sweep. Then, supposing the mains to give an accurate 50 c/s frequency, the time base will be synchronised to sweep at 50 c/s. If, then, the 2100 c/s input voltage is applied to the Y plates, a stationary trace showing 42 complete cycles will result. Similarly, if the time base were set for 100 c/s and synchronised by the 50 c/s supply, the trace would again be stationary and would contain 21 complete cycles. This can be made the basis of an accurate method of frequency comparison. It is, of course, not necessary that the synchronising voltage should be the 50 c/s mains frequency; it might equally well be obtained from a standard oscillator of, say, 1 kc/s. In order that voltages other than the work voltage may be used for synchronising the time base, it is usual to have a "Synch" terminal which may either be strapped to the Y plates or connected to an external synchronising voltage as required.

In order to obtain a stationary trace it is not necessary that the frequency applied to the Y plates should be an exact multiple of the sweep frequency, although this is the only case where an integral number of cycles is obtained. Suppose that the sweep frequency were 1000 c/s and that a frequency of 1500 c/s were applied to the Y plates. In this case the Y plate voltage would complete 3 cycles while the time base swept twice. The resultant trace would be as shown in Fig. 547.

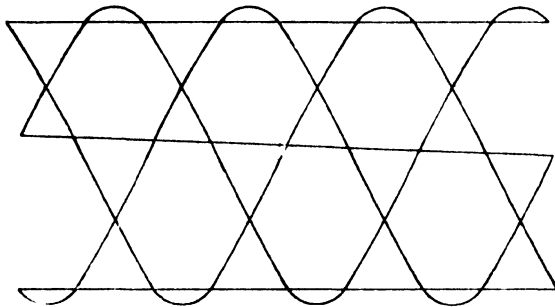


FIG. 548.—Trace when frequency applied to Y plates is $1\frac{1}{2}$ times the sweep frequency.

Similarly, if the ratio of the work frequency to the sweep frequency were 4 : 3, a stationary trace would result ; but this time the trace would repeat itself every third sweep of the time base and would be correspondingly fainter and more involved (see Fig. 548).

Phase-shift measurements

If the time base circuit is disconnected from the X plates and a sinusoidal voltage $E \sin \omega t$ is applied, the beam will execute

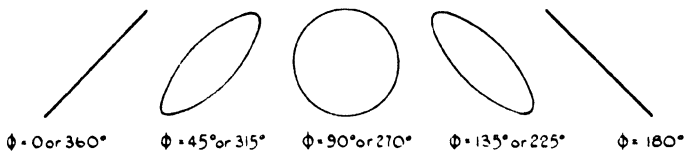


FIG. 549.—Traces illustrating phase measurements.

a horizontal sweep, travelling backwards and forwards in simple harmonic motion. If, simultaneously, a voltage of equal amplitude and frequency but in a different phase, e.g. $E \sin (\omega t + \varphi)$, is applied to the Y plates, a stationary trace will result, but the shape of the trace will depend on the phase angle φ between the two voltages.

Fig. 549 shows the shape of this trace for different values of the phase angle φ . Some of these are easily verified ; for suppose

$\varphi = 180^\circ$, then the horizontal deflection at a time t is given by :—

$$x = kE \sin \omega t$$

and the vertical deflection (assuming equal sensitivity) by :—

$$y = kE \sin (\omega t + 180^\circ) = -kE \sin \omega t$$

whence the equation of the trace is seen to be the line :—

$$y = -x$$

Again suppose $\varphi = 90^\circ$, in this case :—

$$x = kE \sin \omega t$$

$$y = kE \sin (\omega t + 90^\circ) = kE \cos \omega t$$

whence, eliminating t , the equation is that of the circle :—

$$x^2 + y^2 = k^2 E^2$$

For values of phase angle other than 0 , $\frac{\pi}{2}$, π , and $\frac{3\pi}{2}$, the equations are again simple to find, but rather more difficult to identify. The resultant trace, however, can in all cases be shown to be an ellipse.

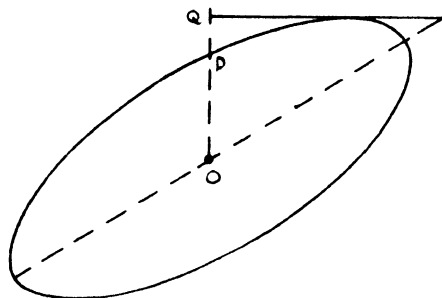


FIG. 550.—Phase ellipse.

From this phase ellipse, the phase angle may be found with fair accuracy. Consider the ellipse of Fig. 550. Let the horizontal and vertical deflections be given by :—

$$x = kE \sin \omega t$$

$$\text{and } y = kE \sin (\omega t + \varphi) \text{ respectively.}$$

Then at the point P the horizontal deflection is zero, and therefore $\sin \omega t = 0$.

Hence OP , which represents the vertical deflection at this instant, is given by :—

$$OP = kE \sin \varphi$$

Also OQ is equal to the amplitude of the vertical sweep ;

$$\therefore OQ = kE$$

$$\therefore \sin \varphi = \frac{OP}{OQ}$$

From which φ can at once be determined.

Lissajous figures

Now suppose that the two sinusoidal voltages applied to the X and Y plates are not exactly of the same frequency, but differ by a fraction of a cycle. For instance, suppose that the frequency on the X plate is 1000 c/s, and that on the Y plate is 1000.1 c/s. These frequencies produce a pattern on the screen that approximates to the phase ellipse, but instead of the two voltages having a constant phase difference, this difference is constantly changing, and so therefore will the orientation and eccentricity of the phase ellipse.

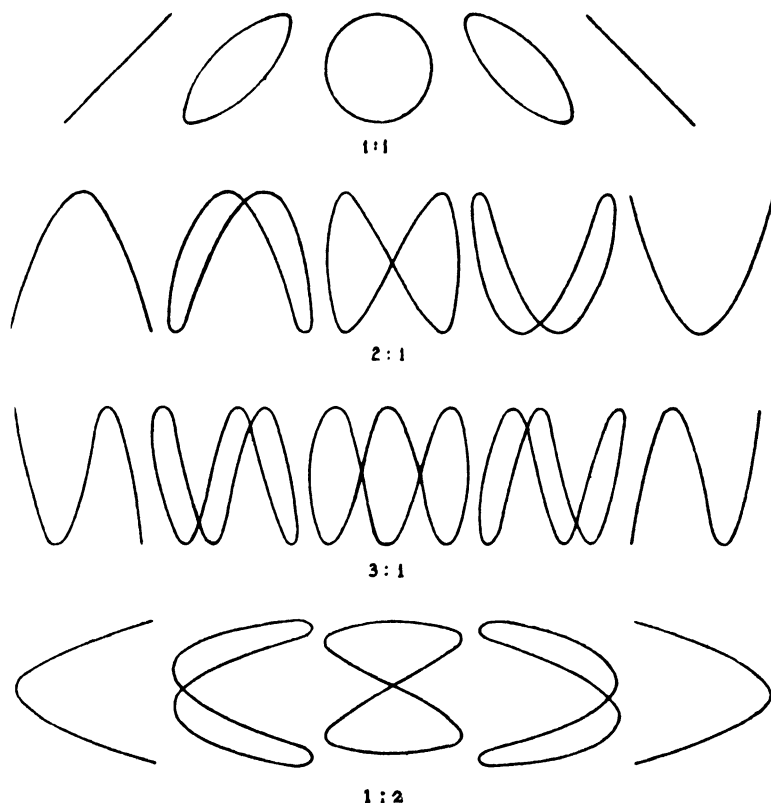


FIG. 551.—Some simple Lissajous figures.

In fact, the trace will pass successively through all the stages shown in Fig. 551 (top line), and in this particular example it will complete the cycle in 10 seconds. In the second line are seen the various possible shapes of the trace for a frequency ratio $f_y : f_x = 2 : 1$. The other traces in this figure should now be self-explanatory. It should be noted that this method for comparing frequencies is impracticable unless the frequencies are an exact multiple to within a few cycles per minute.

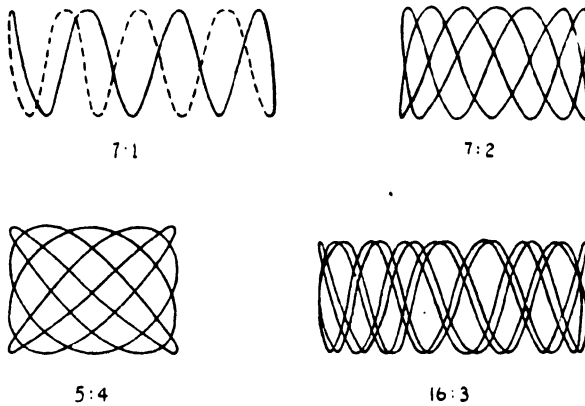


FIG. 552.—Some more complex Lissajous figures.

In order to interpret Lissajous figures it is not necessary to remember pattern shapes, but merely a simple rule connecting the frequency ratio with the number of loops, *viz.* :—

$$\frac{f_v}{f_h} = \frac{\text{Number of loops horizontally}}{\text{Number of loops vertically}}$$

In applying this rule it is simplest to count the loops when the trace is open; by studying the traces of Figs. 551 and 552. the student should quickly grasp the use of this rule.

Characteristic curves

Another important application of the CRO is in observing characteristic curves. A characteristic curve is a graphical representation of the way in which a given physical quantity y varies with another quantity x . If, therefore a voltage proportional to x be fed to the X plates of a CRO, and at the same time a voltage

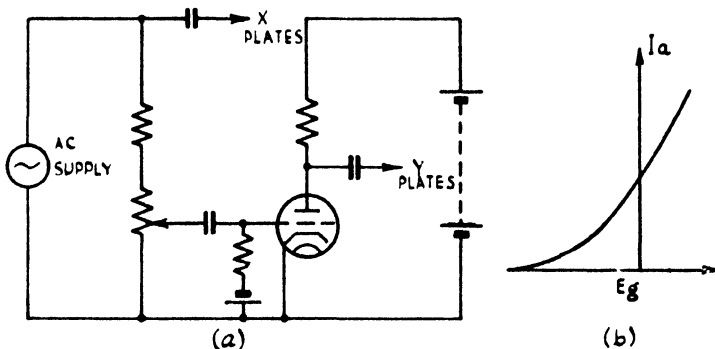


FIG. 553.—Use of CRO to observe mutual characteristics of a valve.

proportional to y is fed to the Y plates, then the spot will trace out the required characteristic.

A particularly easy example of this is a method of obtaining valve characteristics.

Fig. 553 shows a simple circuit enabling the CRO to be used to observe the mutual characteristic of a triode. The valve is set up in the normal way, with suitable DC voltages on the anode and grid, and then an AC voltage of suitable amplitude is applied to the grid; the same voltage is also applied to the X plates of the tube. The anode current will vary with the sinusoidal voltage applied to the grid, and the anode voltage will vary as the anode current. The anode voltage therefore is applied to the Y plates. Provided there is exactly 180° phase-shift in the valve, the trace will show an exact replica of the mutual characteristic of the valve. If the phase-shift has a value differing from 180° , then the spot will travel different paths on its go and return sweeps, and a narrow closed loop will result.

Another characteristic that can be plotted quite simply using a slightly more complex technique is the hysteresis curve of a magnetic material.

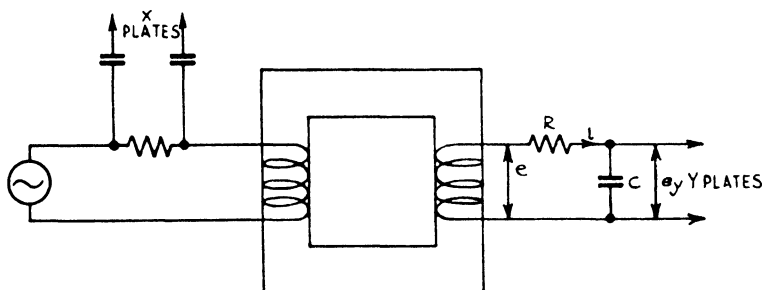


FIG. 554.—Circuit for examining hysteresis curves.

Fig. 554 shows a typical circuit. The specimen of material under examination must effectively form the core of a transformer. The magnetic field H , which is normally plotted on the horizontal axis, is proportional to the magnetising current; an AC supply is accordingly fed to the magnetising windings *via* a small resistance, and the voltage across this is applied to the X plates. The voltage induced across a small secondary winding is proportional to the rate of change of the flux in the magnetic material, that is:—

$$e \propto \frac{dB}{dt}$$

In order to apply a voltage to the Y plates that is proportional to the flux B , it is necessary to use a phase-shifting circuit consisting of capacity C and resistance R arranged as shown.

From the figure, $e_v = \frac{q}{C}$

where q is the charge on the condenser

$$\text{i.e.} \quad e_v = \frac{1}{C} \int i dt$$

But if the values of capacity and resistance are so chosen that

$$\frac{1}{\omega C} \ll R,$$

$$\text{then} \quad i \simeq \frac{e}{R}$$

$$\therefore \quad e_v \simeq \frac{1}{CR} \int e dt$$

$$\text{i.e.} \quad e_v \propto B$$

It should be noted that, in order to produce a hysteresis curve, the amplitude of the magnetising current should be sufficiently large to cause saturation on the peaks, otherwise the trace will merely take the form of a distorted phase ellipse.

CHAPTER 13

FOUR-TERMINAL NETWORKS

A four-terminal network is a network having only one pair of input and one pair of output terminals. When its electrical properties are unaffected by interchanging the input and output terminals, the network is said to be "symmetrical"; if this is not the case, it is said to be "asymmetrical" or "dissymmetrical".

SYMMETRICAL NETWORKS

Symmetrical networks have two important electrical characteristics, namely, characteristic impedance (Z_0) and propagation constant (γ). Two networks having the same characteristic impedance and the same propagation constant are said to be equivalent.

Characteristic impedance

If an infinite number of identical symmetrical networks are connected in tandem as in Fig. 555a, the impedance measured at

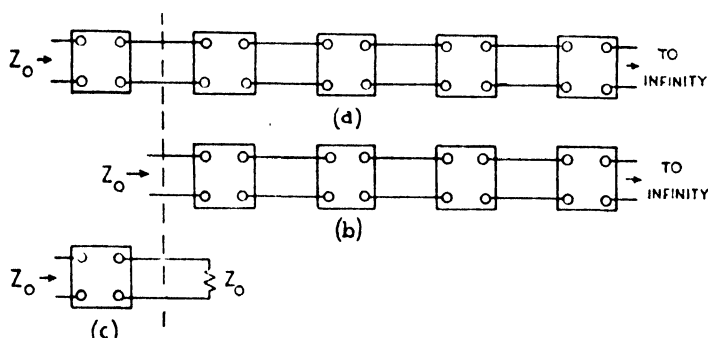


Fig. 555.—Illustrating characteristic impedance of four-terminal network.

the input terminals of the first network will have some definite value depending only on the composition of the networks. This impedance is an important property of the network, and is called its "characteristic impedance", represented by Z_0 . It will be seen later that this characteristic impedance may be calculated from a knowledge of the component values of the network.

If the first network of the infinite chain shown in Fig. 555a be disconnected, the number of networks remaining will still be

infinite, and therefore the input impedance looking into the second network will be Z_0 (Fig. 555*b*). It follows that, if the first section be connected to an impedance equal to Z_0 , as in Fig. 555*c* (instead of to the infinite chain of networks of Fig. 555*b* whose input impedance is Z_0), its input impedance will still be Z_0 .

Thus it can be seen that if any symmetrical network is terminated with its characteristic impedance Z_0 , the input impedance will also be Z_0 . Similarly, if its input terminals are connected to a generator of impedance Z_0 , then its output impedance will be equal to Z_0 . When both these conditions are satisfied and both the input and output terminals of the network are terminated in Z_0 , the network is said to be *correctly terminated*.

Propagation constant

In addition to the characteristic impedance just considered, symmetrical networks have another important property, the propagation constant, which represents the relationship between the input and output currents.

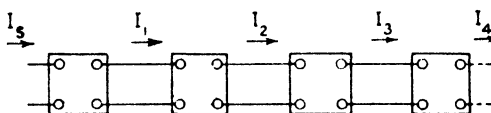


FIG. 556.—Illustrating propagation constant of four-terminal network.

Consider a recurrent network consisting of a series of identical symmetrical sections, as shown in Fig. 556. The current leaving any section will be a definite proportion of that entering the section and will, in general, be out of phase with it. This means that the ratio of the current entering any section to that leaving it is a vector quantity having both modulus and angle. Since all sections are identical, this vector will be the same for all sections. It is convenient to write this vector in the form e^γ , where γ is a complex number. Hence let :—

$$\frac{I_s}{I_1} = e^\gamma \quad (1)$$

Since each section is identical, it follows that :—

$$e^\gamma = \frac{I_s}{I_1} = \frac{I_1}{I_2} = \frac{I_2}{I_3}, \text{ etc.}$$

Thus
$$\frac{I_s}{I_2} = \frac{I_1}{I_2} \times \frac{I_s}{I_1} = e^{2\gamma}$$

and
$$\frac{I_s}{I_3} = \frac{I_2}{I_3} \times \frac{I_1}{I_2} \times \frac{I_s}{I_1} = e^{3\gamma}$$

Considering the case of a finite number of sections n , correctly terminated, if the current at the sending end is I_s and that at the

receiving end I_R , then :—

$$\frac{I_S}{I_R} = e^{n\gamma} \quad (2)$$

Since γ is a complex number, let $\gamma = \alpha + j\beta$

$$\begin{aligned} \text{Then } e^\gamma &= e^{\alpha+j\beta} = e^\alpha \cdot e^{j\beta} \\ &= e^\alpha (\cos \beta + j \sin \beta) \\ &= e^\alpha \sqrt{\cos^2 \beta + \sin^2 \beta} \left/ \tan^{-1} \frac{\sin \beta}{\cos \beta} \right. \\ &= e^\alpha \angle \beta \end{aligned} \quad (3)$$

e^γ is seen to be a vector of modulus e^α and angle β . e^α gives the ratio of the absolute magnitudes of currents entering and leaving a section; β gives the phase angle between these two currents.

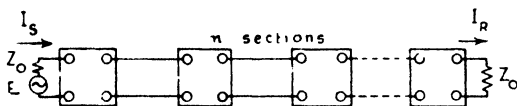


FIG. 557.— n four-terminal networks, correctly terminated.

For n sections correctly terminated :—

$$\frac{I_S}{I_R} = e^{n\gamma} = e^{n\alpha} \angle n\beta \quad (4)$$

In this case the ratio of absolute magnitudes of current sent and current received will be $e^{n\alpha}$, and the phase angle will be $n\beta$. Since the sections are symmetrical, both the input and output circuits will be terminated in the same impedance Z_0 . The input voltage E_S will be equal to $I_S Z_0$, and the output voltage E_R will be equal to $I_R Z_0$.

$$\text{Hence } \frac{I_S}{I_R} = \frac{I_S Z_0}{I_R Z_0} = \frac{E_S}{E_R}$$

$$\text{and } \frac{E_S}{E_R} = e^{n\gamma} = e^{n\alpha} \angle n\beta \quad (5)$$

Attenuation constant and the neper

The real part α of the propagation constant γ is called the "attenuation constant" of the section, and is measured in "nepers".* It is equal to the logarithm, to the base e , of the

* It must be noted that, throughout this and subsequent chapters, the values obtained for attenuation and phase-shift, unless otherwise stated, are in nepers and radians. These results can be converted into the more convenient units for practical work, the decibel and the degree, by multiplying by 8.686 and 57.3 respectively. (See also Conversion Tables, pages 839 and 804.)

ratio of the modulus of the current entering the section, to that leaving it.

$$\text{For } e^{\alpha} = \left| \frac{I_s}{I_1} \right|$$

$$\therefore \alpha = \log_e \left| \frac{I_s}{I_1} \right| \text{ nepers}$$

For n sections, from equation 4 :—

$$\left| \frac{I_s}{I_R} \right| = e^{n\alpha}$$

so that the attenuation introduced by n sections is :—

$$\log_e \left| \frac{I_s}{I_R} \right| = n\alpha \text{ nepers.}$$

Phase constant

The imaginary part β of the propagation constant γ is called the "phase constant" of the section, and is equal to the angle in radians by which the current leaving the section lags behind that entering it. From equation 4 the phase-shift introduced by n sections is $n\beta$ radians.

ASYMMETRICAL NETWORKS

Asymmetrical networks generally have different characteristic impedances on the two sides; and to be strictly accurate, when dealing with such networks, the terms "iterative impedance" and "image impedance" should be used in place of "characteristic impedance".

Iterative impedance

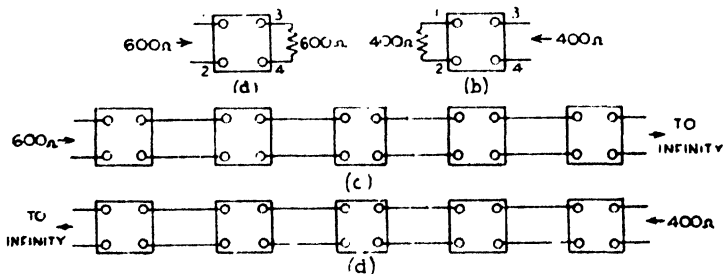


FIG. 558.—Illustrating iterative impedances of asymmetrical network.

The iterative impedance of a four-terminal network is defined as the input impedance measured at one pair of terminals when an infinite number of such networks are connected in tandem. This is the value of the impedance measured at one pair of terminals

of the network when the other pair of terminals is terminated with an impedance of the same value. Iterative impedances will be different for the two pairs of terminals of an asymmetrical network (see Fig. 558). Thus the impedance looking into terminals 1 and 2 is 600Ω when terminals 3 and 4 are terminated in 600Ω , and the impedance looking into terminals 3 and 4 is 400Ω when terminals 1 and 2 are terminated in 400Ω .

When the two iterative impedances are equal (as they are in the case of symmetrical networks), the common value is the characteristic impedance of the network.

Image impedance

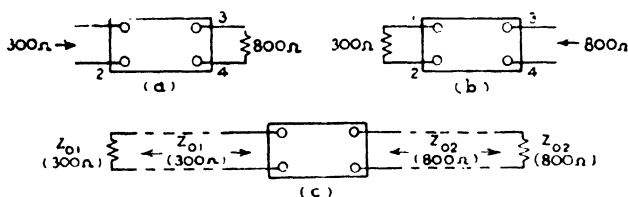


FIG. 559.—Illustrating image impedances of asymmetrical network.

The image impedances of a network are those impedances such that when one of them is connected across the appropriate pair of terminals of the network, the other is presented by the other pair of terminals (see Fig. 559a and b). In the case of an asymmetrical network, the two image impedances are different. Thus the input impedance at terminals 1 and 2 of the network shown in Fig. 559 is 300Ω when terminals 3 and 4 are terminated in 800Ω , and the input impedance at terminals 3 and 4 is 800Ω when terminals 1 and 2 are terminated in 300Ω . When the two image impedances are equal (as they are in the case of symmetrical networks), their common value is equal to the characteristic impedance of the network.

An asymmetrical network is said to be correctly terminated when it is terminated in its image impedances. (Fig. 559c.)

Image-transfer constant

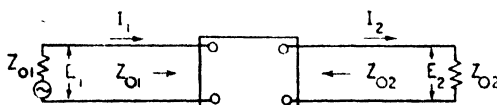


FIG. 560.—Illustrating image-transfer constant of asymmetrical network.

When an asymmetrical section, terminated in its image impedances, is considered (Fig. 560), the ratio $\frac{I_1}{I_2}$ will be different

from the ratio $\frac{E_1}{E_2}$. In such a case, the term "propagation constant" is not employed, and instead the "image-transfer constant" θ is considered.

θ is defined as one-half the logarithm to the base e of the vector ratio of the volt-amperes entering the network, to the volt-amperes leaving it, the network being terminated by its image impedances.

$$\text{Thus} \quad \theta = \sqrt{\frac{E_1 I_1}{E_2 I_2}} \quad (6)$$

The real part of the image-transfer constant is known as the "image-attenuation constant", and the imaginary part is known as the "image-phase constant".

INSERTION LOSS OF A FOUR-TERMINAL NETWORK

When a network is introduced between a generator and a load, the resultant reduction in power in the load is known as the "insertion loss" of the network. It is usual to express this loss of power in either the decibel or the neper notation.

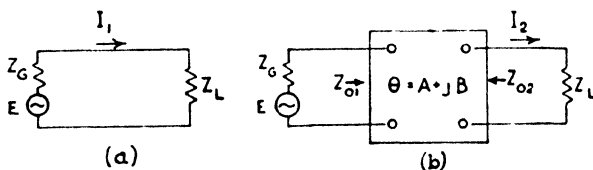


FIG. 561.—Insertion loss of four-terminal network.

Consider the case of a generator of internal impedance Z_G working into a load Z_L (see Fig. 561a). Let the current flowing be I_1 . If a four-terminal network having image impedances Z_{01} and Z_{02} and image-transfer constant θ be inserted between the generator and the load, as in Fig. 561b, then the current will be altered to some value I_2 , say. The insertion loss is given by:—

$$\text{Insertion loss} = \log \left| \frac{I_1}{I_2} \right| \text{ nepers}$$

or:—

$$\text{Insertion loss} = 20 \log_{10} \left| \frac{I_1}{I_2} \right| \text{ decibels.}$$

It can be shown that, if $\theta = A + jB$, the insertion loss is given by:—

$$A + \log_e \left| \frac{Z_G + Z_{01}}{2\sqrt{Z_G Z_{01}}} \right| + \log_e \left| \frac{Z_L + Z_{02}}{2\sqrt{Z_L Z_{02}}} \right| - \log_e \left| \frac{Z_G + Z_L}{2\sqrt{Z_G Z_L}} \right| \\ + \log_e \left| 1 - \frac{Z_{01} - Z_G}{Z_{01} + Z_G} \cdot \frac{Z_{02} - Z_L}{Z_{02} + Z_L} \cdot e^{-2\theta} \right| \text{ nepers} \quad (7)$$

and the insertion phase-shift is given by :—

$$\left\{ B + \text{angle of } \frac{Z_g + Z_{01}}{2\sqrt{Z_g Z_{01}}} + \text{angle of } \frac{Z_L + Z_{02}}{2\sqrt{Z_L Z_{02}}} - \text{angle of } \frac{Z_g + Z_L}{2\sqrt{Z_g Z_L}} \right. \\ \left. + \text{angle of } \left(1 - \frac{Z_{01} - Z_g}{Z_{01} + Z_g} \cdot \frac{Z_{02} - Z_L}{Z_{02} + Z_L} \cdot e^{-2\theta} \right) \right\} \text{ radians} \quad (8)$$

RECURRENT NETWORKS

Ladder networks

The type of recurrent network most commonly encountered in line transmission is the ladder network. It exists in two forms—the “unbalanced” ladder network (see Fig. 562a), and the “balanced” ladder network (Fig. 562b).

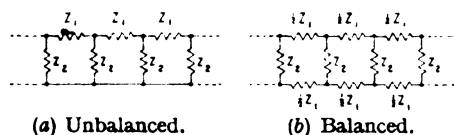


FIG. 562.—Ladder networks.

Both the balanced and the unbalanced ladder networks may be considered as being built up of a number of “sections” (as shown in Figs. 563 and 564), which are known, by reason of their shape, as “T”, “π” and “L” sections in the unbalanced form, and as “H”, “O” and “C” sections in the balanced form. These sections are all arranged to have a total series impedance Z_1 and a total shunt impedance Z_2 .

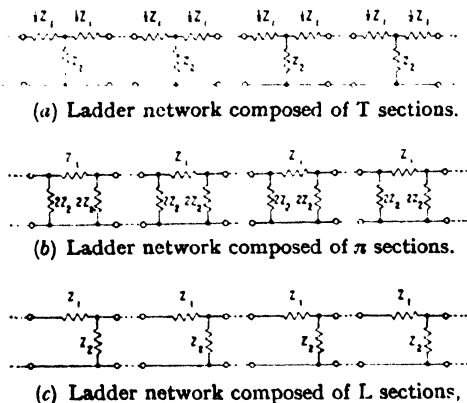


FIG. 563.—Unbalanced ladder networks of Fig. 562a represented as a series of sections.

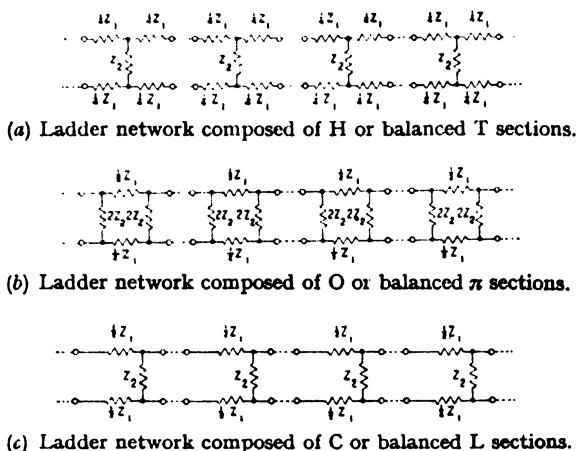


FIG. 564.—Balanced ladder network of Fig. 562b represented as a series of sections.

In these figures the T and π sections, of which the ladder network is considered to consist, are shown as being symmetrical; the ladder network could, however, equally well be represented by a series of asymmetrical sections, such as those shown in Fig. 565.

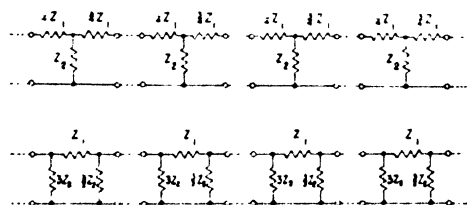


FIG. 565.—Unbalanced ladder network represented as a series of asymmetrical sections.

In fact, the L section (which is asymmetrical) is merely a particular case of the asymmetrical T section (with one series arm equal to zero), or of the asymmetrical π section (with one shunt arm equal to infinity).

Other recurrent networks

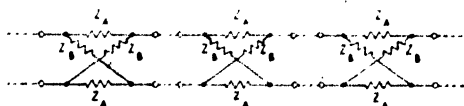


FIG. 566.—Lattice network.

In addition to the ladder structure, two other forms of recurrent networks are encountered, namely the "lattice" and the "bridged-T" networks, shown in Figs. 566 and 567 respectively.

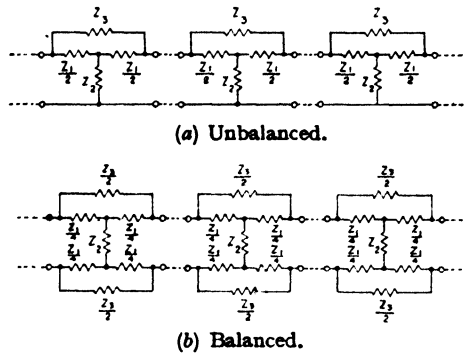


Fig. 567.—Unbalanced and balanced forms of bridged-T section.

The lattice section is usually a balanced symmetrical structure. The bridged-T section may be balanced or unbalanced, symmetrical or asymmetrical, though the unbalanced symmetrical form shown is the most usual.

Equivalence of balanced and unbalanced sections

Both the balanced and unbalanced sections have identical transmission properties, as long as no connections are made between the input and output terminals external to the network. Thus in Fig. 568, *a* and *b* are equivalent, provided that no connection is made as in *c*.

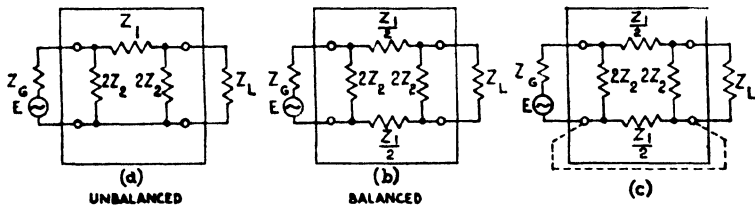


Fig. 568.—Illustrating equivalence of balanced and unbalanced sections.

THE T SECTION

The symmetrical T section shown in Fig. 569 is one of the most

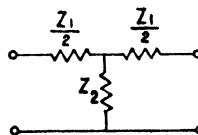


Fig. 569.—Symmetrical T section.

important networks encountered in line transmission theory. It was shown in Fig. 563a that a ladder network could be regarded as being made up of these sections. To give a total series-arm impedance of Z_1 in the ladder network, the two series-arm impedances in the T section must each be $\frac{Z_1}{2}$.

Characteristic impedance

To find the characteristic impedance (Z_0) of such a section, terminate the section on one side with Z_0 , and determine the input impedance. Equating this input impedance to Z_0 gives an equation from which Z_0 may be determined.

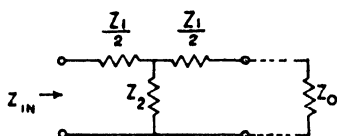


FIG. 570.—Symmetrical T section terminated in Z_0 .

Considering Fig. 570 :—

$$Z_{IN} = \frac{Z_1}{2} + \frac{Z_2 \left(\frac{Z_1}{2} + Z_0 \right)}{Z_2 + \frac{Z_1}{2} + Z_0}$$

But $Z_{IN} = Z_0$

$$\therefore Z_0 = \frac{Z_1}{2} + \frac{Z_2 \left(\frac{Z_1}{2} + Z_0 \right)}{Z_2 + \frac{Z_1}{2} + Z_0}$$

$$\therefore Z_0 Z_2 + \frac{Z_0 Z_1}{2} + Z_0^2 = \frac{Z_1 Z_2}{2} + \frac{Z_1^2}{4} + \frac{Z_0 Z_1}{2} + \frac{Z_1 Z_2}{2} + Z_0 Z_2$$

$$\therefore Z_0^2 = \frac{Z_1^2}{4} + Z_1 Z_2 \quad (9)$$

Thus giving $Z_0 = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2} \quad (10)$

Open- and short-circuit impedances

The values of Z_1 and Z_2 may be determined by measuring the input impedance for two given terminations. For convenience, these two terminations are taken as an open-circuit and a short-circuit.

Let the input impedance on open-circuit (Fig. 571a) be Z_{oo} .

Then $Z_{oo} = \frac{Z_1}{2} + Z_2 \quad (11)$

Let the input impedance on short-circuit (Fig. 571*b*) be Z_{so} .

Then
$$Z_{so} = \frac{Z_1}{2} + \frac{\frac{Z_1 Z_2}{2}}{\frac{Z_1}{2} + Z_2}$$

$$\therefore Z_{so} = \frac{Z_1 Z_2 + \frac{Z_1^2}{4}}{\frac{Z_1}{2} + Z_2} \tag{12}$$

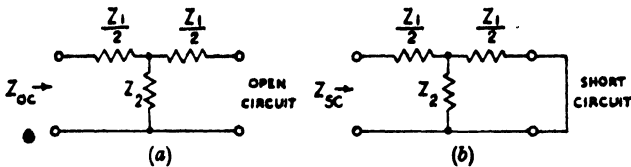


FIG. 571.—Symmetrical T section on open- and short-circuit.

It will be noted that multiplying (11) and (12) gives:—

$$Z_{oo} \cdot Z_{so} = \left(\frac{Z_1}{2} + Z_2 \right) \times \frac{\frac{Z_1^2}{4} + Z_1 Z_2}{\frac{Z_1}{2} + Z_2}$$

$$= \frac{Z_1^2}{4} + Z_1 Z_2$$

$$= Z_0^2 \text{ (from equation 10)}$$

that is $Z_0 = \sqrt{Z_{oo} Z_{so}}$ (13)

This formula is most useful, and should be memorised.

From these equations, Z_1 and Z_2 may be determined in terms of Z_{oo} and Z_{so} :—

Squaring (11):—

$$Z_{oo}^2 = \frac{Z_1^2}{4} + Z_1 Z_2 + Z_2^2$$

$$= Z_0^2 + Z_2^2 \quad \text{(from equation 10)}$$

$$= Z_{oo} Z_{so} + Z_2^2 \quad \text{(from equation 13)}$$

$$\therefore Z_2^2 = Z_{oo}^2 - Z_{oo} Z_{so}$$

$$\therefore Z_2 = \sqrt{Z_{oo} (Z_{oo} - Z_{so})} \tag{14}$$

$$\therefore \text{from (11), } Z_1 = 2 [Z_{oo} - \sqrt{Z_{oo} (Z_{oo} - Z_{so})}] \tag{15}$$

Example 1.—

Find the characteristic impedance of the T section shown in Fig. 572.

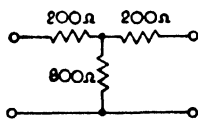


FIG. 572.

This is most easily done by using the formula $Z_0^2 = Z_{oo} Z_{so}$.

$$Z_{oo} = 200 + 800 = 1000 \Omega$$

$$\begin{aligned} Z_{so} &= 200 + (200 \text{ and } 800 \text{ in parallel}) \\ &= 200 + 160 = 360 \Omega \end{aligned}$$

Hence $Z_{oo} Z_{so} = 1000 \cdot 360 = 36 \cdot 10^4$

$$\begin{aligned} Z_0 &= \sqrt{Z_{oo} Z_{so}} \\ &= 600 \Omega \quad \text{Ans.} \end{aligned}$$

Example 2.—

A symmetrical T section composed of pure resistances has the following values for open- and short-circuit impedances:—

$$Z_{oo} = 800 \text{ ohms } \angle 0^\circ, \quad Z_{so} = 600 \text{ ohms } \angle 0^\circ.$$

Determine Z_1 and Z_2 for this T section.

$$\begin{aligned} Z_1 &= 2 [800 - \sqrt{800(800 - 600)}] \\ &= 2 [800 - \sqrt{800 \cdot 200}] \\ &= 2 [800 - 400] = 800 \text{ ohms} \end{aligned}$$

$$Z_2 = \sqrt{800 \cdot 200} = 400 \text{ ohms.} \quad \text{Ans.}$$

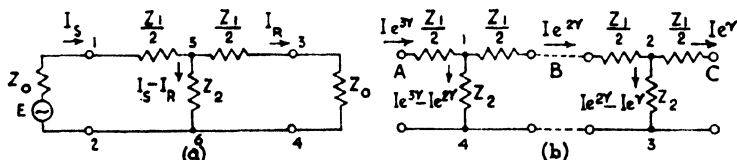
Propagation constant

FIG. 573.—Propagation constant of T section.

Consider a T section correctly terminated, as shown in Fig. 573a. Let the input current be I_s and the output current be I_R .

By definition,

$$\frac{I_s}{I_R} = e^{\gamma}$$

Applying Kirchhoff's Law to mesh 5, 3, 4, 6:—

$$-(I_s - I_R) Z_1 + \frac{I_R Z_1}{2} + I_R Z_0 = 0$$

$$\therefore I_2 Z_2 = I_2 \left(Z_2 + \frac{Z_1}{2} + Z_0 \right)$$

$$\text{Hence } e^\gamma = \frac{I_2}{I_1} = \frac{Z_2 + \frac{Z_1}{2} + Z_0}{Z_2}$$

$$\therefore e^\gamma = 1 + \frac{Z_1}{2Z_2} + \frac{Z_0}{Z_2} \quad (16)$$

$$\text{Since } Z_0 = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}$$

$$\therefore e^\gamma = 1 + \frac{Z_1}{2Z_2} + \frac{1}{Z_2} \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}$$

$$\text{i.e. } e^\gamma = 1 + \frac{Z_1}{2Z_2} + \sqrt{\left(\frac{Z_1}{2Z_2}\right)^2 + \frac{Z_1}{Z_2}} \quad (17)$$

The propagation constant of a T section is therefore given by:—

$$\gamma = \log. \left\{ 1 + \frac{Z_1}{2Z_2} + \sqrt{\left(\frac{Z_1}{2Z_2}\right)^2 + \frac{Z_1}{Z_2}} \right\} \quad (18)$$

From equation 17:—

$$e^\gamma = 1 + \frac{Z_1}{2Z_2} + \sqrt{\left(\frac{Z_1}{2Z_2}\right)^2 + \frac{Z_1}{Z_2}}$$

$$\text{whence } e^{-\gamma} = \frac{1}{1 + \frac{Z_1}{2Z_2} + \sqrt{\left(\frac{Z_1}{2Z_2}\right)^2 + \frac{Z_1}{Z_2}}}$$

which simplifies to:—

$$e^{-\gamma} = 1 + \frac{Z_1}{2Z_2} - \sqrt{\left(\frac{Z_1}{2Z_2}\right)^2 + \frac{Z_1}{Z_2}} \quad (19)$$

Adding:—

$$e^\gamma + e^{-\gamma} = 2 + \frac{Z_1}{Z_2}$$

$$\therefore \frac{e^\gamma + e^{-\gamma}}{2} = 1 + \frac{Z_1}{2Z_2}$$

$$\text{or } \cosh \gamma = 1 + \frac{Z_1}{2Z_2} \quad (20)$$

Equation 20 may be derived more simply by considering two successive T sections in a recurrent network (see Fig. 573b).

Let the currents at the points A, B and C be:—

$$Ie^{z\gamma}, Ie^{2z\gamma} \text{ and } Ie^\gamma.$$

Applying Kirchhoff's Law to mesh 1, 2, 3, 4 gives:—

$$(Ie^{2\gamma}) \cdot Z_1 + (Ie^{2\gamma} - Ie^\gamma)Z_2 - (Ie^{2\gamma} - Ie^{2\gamma})Z_3 = 0$$

Dividing by $Ie^{2\gamma}$:—

$$Z_1 + Z_2 - e^{-\gamma}Z_2 - e^\gamma Z_2 + Z_2 = 0$$

$$\therefore Z_2(e^\gamma + e^{-\gamma}) = Z_1 + 2Z_2$$

$$\therefore \frac{e^\gamma + e^{-\gamma}}{2} = 1 + \frac{Z_1}{2Z_2}$$

$$\text{Thus, as before,} \quad \cosh \gamma = 1 + \frac{Z_1}{2Z_2}$$

Other useful expressions involving γ may be obtained.

$$\text{Equation 16 gives :—} \quad e^\gamma = 1 + \frac{Z_1}{2Z_2} + \frac{Z_0}{Z_2}$$

Equation 20 gives :—

$$\cosh \gamma = 1 + \frac{Z_1}{2Z_2}$$

But $e^\gamma = \cosh \gamma + \sinh \gamma$.

Therefore, by subtraction :—

$$\sinh \gamma = \frac{Z_0}{Z_2} \quad \text{or} \quad Z_2 = \frac{Z_0}{\sinh \gamma} \quad (21)$$

$$\text{Hence} \quad \tanh \gamma = \frac{\sinh \gamma}{\cosh \gamma} = \frac{Z_0}{Z_2 \left(1 + \frac{Z_1}{2Z_2}\right)} = \frac{Z_0}{Z_2 + \frac{Z_1}{2}}$$

$$\text{Now} \quad Z_0 = \sqrt{Z_{00}Z_{20}}$$

$$\text{and} \quad Z_2 + \frac{Z_1}{2} = Z_{00}$$

$$\therefore \tanh \gamma = \frac{\sqrt{Z_{00}Z_{20}}}{Z_{00}} = \sqrt{\frac{Z_{20}}{Z_{00}}} \quad (22)$$

Equation 22 is useful, as it enables γ to be calculated from the open- and short-circuit impedances. It can thus be seen that both the characteristic impedance and the propagation constant of a network can be determined from Z_{00} and Z_{20} . From this, it follows that two networks will behave similarly if they have the same Z_{00} and Z_{20} .

$$\text{Since} \quad \cosh \gamma = 1 + \frac{Z_1}{2Z_2}$$

$$\frac{Z_1}{Z_2} = 2(\cosh \gamma - 1) = 2 \times 2 \sinh^2 \frac{\gamma}{2}$$

$$\therefore \sinh \frac{\gamma}{2} = \frac{1}{2} \sqrt{\frac{Z_1}{Z_2}} \quad (23)$$

Now $\sinh \frac{\gamma}{2} \cdot \cosh \frac{\gamma}{2} = \frac{\sinh \gamma}{2} = \frac{Z_0}{2Z_2}$ (from equation 21)

$$\therefore \cosh \frac{\gamma}{2} = \frac{Z_0}{2Z_2} \times \frac{1}{\sinh \frac{\gamma}{2}} = \frac{Z_0}{2Z_2} \times 2\sqrt{\frac{Z_2}{Z_1}} = \frac{Z_0}{\sqrt{Z_1 Z_2}}$$

$$\therefore \tanh \frac{\gamma}{2} = \frac{\sinh \frac{\gamma}{2}}{\cosh \frac{\gamma}{2}} = \frac{1}{2} \sqrt{\frac{Z_1}{Z_2}} \times \frac{\sqrt{Z_1 Z_2}}{Z_0} = \frac{Z_1}{2Z_0}$$

$$\therefore Z_1 = 2Z_0 \tanh \frac{\gamma}{2} \tag{24}$$

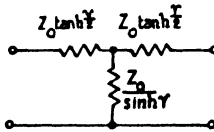


FIG. 574.—T section, showing values of components in terms of characteristic impedance and propagation constant.

Equations 21 and 24 enable the components of a T section to be calculated if Z_0 and γ are known. The section is shown in Fig. 574.

Input impedance of a T section terminated in Z_R

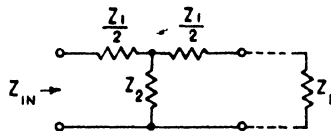


FIG. 575.—T section terminated in an impedance Z_R .

Consider a T section terminated in Z_R (see Fig. 575). The input impedance is given by:—

$$\begin{aligned} Z_{IN} &= \frac{Z_1}{2} + \frac{Z_2 \left(\frac{Z_1}{2} + Z_R \right)}{Z_2 + \frac{Z_1}{2} + Z_R} \\ &= \frac{Z_2 \left(\frac{Z_1}{2} + Z_R \right) + \frac{Z_1^2}{4} + Z_1 Z_R}{Z_2 + \frac{Z_1}{2} + Z_R} \end{aligned}$$

$$\text{But } \frac{Z_1^2}{4} + Z_1 Z_2 = Z_0^2$$

$$\begin{aligned} \therefore Z_{IN} &= \frac{Z_R \left(\frac{Z_1}{2} + Z_2 \right) + Z_0^2}{Z_2 + \frac{Z_1}{2} + Z_R} \\ &= Z_0 \frac{Z_R \left(1 + \frac{Z_1}{2Z_2} \right) + Z_0 \frac{Z_0}{Z_2}}{Z_0 \left(1 + \frac{Z_1}{2Z_2} \right) + Z_R \frac{Z_0}{Z_2}} \end{aligned}$$

$$\text{But } \frac{Z_0}{Z_2} = \sinh \gamma \text{ (equation 21)}$$

$$\text{and } 1 + \frac{Z_1}{2Z_2} = \cosh \gamma \text{ (equation 20).}$$

$$\text{Thus } Z_{IN} = Z_0 \frac{Z_R \cosh \gamma + Z_0 \sinh \gamma}{Z_0 \cosh \gamma + Z_R \sinh \gamma} \quad (25)$$

Input impedance of a T section having a high attenuation

Considering equation 25, and replacing γ by $\alpha + j\beta$, gives:—

$$\begin{aligned} Z_{IN} &= Z_0 \frac{Z_R \cosh(\alpha + j\beta) + Z_0 \sinh(\alpha + j\beta)}{Z_0 \cosh(\alpha + j\beta) + Z_R \sinh(\alpha + j\beta)} \\ &= Z_0 \frac{Z_R \cosh \alpha \cos \beta + jZ_R \sinh \alpha \sin \beta + Z_0 \sinh \alpha \cos \beta + jZ_0 \cosh \alpha \sin \beta}{Z_0 \cosh \alpha \cos \beta + jZ_0 \sinh \alpha \sin \beta + Z_R \sinh \alpha \cos \beta + jZ_R \cosh \alpha \sin \beta} \end{aligned}$$

If α is large:—

$$\cosh \alpha = \sinh \alpha$$

In this case:—

$$\begin{aligned} Z_{IN} &= Z_0 \frac{Z_R \cos \beta + jZ_R \sin \beta + Z_0 \cos \beta + jZ_0 \sin \beta}{Z_0 \cos \beta + jZ_0 \sin \beta + Z_R \cos \beta + jZ_R \sin \beta} \\ &= Z_0 \quad (26) \end{aligned}$$

Hence if the attenuation (α) is large, the input impedance is equal to Z_0 for all values of phase-shift (β) and for all values of terminating impedance (Z_R).

This result is of fundamental importance, and is applicable to all line transmission networks.

Example.—

A T section (Fig. 576) has an attenuation of 3.45 nepers (30 db) and a purely resistive characteristic impedance of 600Ω . What is the input impedance (a) on open-circuit, (b) on short-circuit, and (c) when terminated in a $2 \mu\text{F}$ condenser ($\omega = 5000$ radians/sec.)?

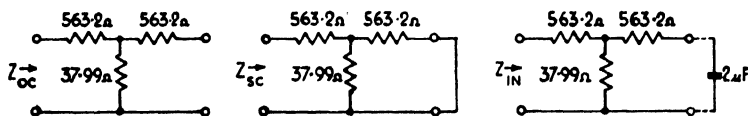


FIG. 576.

- (a) $Z_{OC} = 563.2 + 37.99 = 601 \text{ ohms } \angle 0^\circ \text{ Ans.}$
- (b) $Z_{SC} = 563.2 + \frac{37.99 \cdot 563.2}{601.2} = 599 \text{ ohms } \angle 0^\circ \text{ Ans.}$
- (c) $Z_{IN} = 563.2 + \frac{37.99 (563.2 - j.100)}{37.99 + 563.2 - j.100} = 599 \text{ ohms } \angle -0^\circ 2' \text{ Ans.}$

THE π SECTION

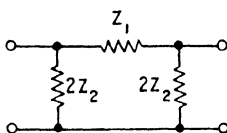


FIG. 577.—Symmetrical π section.

The symmetrical π section, Fig. 577, is another very important network encountered in line transmission.

Characteristic impedance

The characteristic impedance of the π section may be found in an identical method to that employed for the T section, namely, by terminating the section in Z_0 and equating the input impedance to Z_0 .

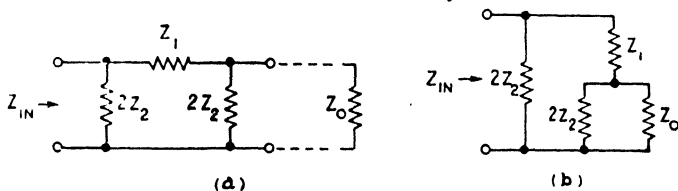


FIG. 578.—Symmetrical π section terminated in Z_0 .

The input impedance Z_{IN} will be $2Z_2$ in parallel with the series combination of Z_1 and ($2Z_2$ and Z_0 in parallel). Fig. 578b.

$$\therefore \frac{1}{Z_{IN}} = \frac{1}{2Z_2} + \frac{1}{Z_1 + \frac{1}{\frac{1}{Z_0} + \frac{1}{2Z_2}}}$$

or writing $Y = \frac{1}{Z}$ (i.e., using admittances) :—

$$Y_{IN} = \frac{Y_2}{2} + \frac{Y_1 \left(Y_0 + \frac{Y_2}{2} \right)}{Y_1 + Y_0 + \frac{Y_2}{2}}$$

But $Y_{IN} = Y_0$

$$\therefore Y_0 = \frac{Y_2}{2} + \frac{Y_1 Y_0 + \frac{Y_1 Y_2}{2}}{Y_0 + Y_1 + \frac{Y_2}{2}}$$

$$\therefore Y_0^2 + Y_0 Y_1 + \frac{Y_0 Y_2}{2} = \frac{Y_0 Y_2}{2} + \frac{Y_1 Y_2}{2} + \frac{Y_2^2}{4} + Y_1 Y_0 + \frac{Y_1 Y_2}{2}$$

$$\therefore Y_0^2 = \frac{Y_2^2}{4} + Y_1 Y_2$$

$$\therefore Y_0 = \sqrt{\frac{Y_2^2}{4} + Y_1 Y_2} \quad (\text{compare this with equation 10}) \quad (27)$$

$$\text{This gives } Z_0 = \frac{1}{\sqrt{\frac{1}{4Z_2^2} + \frac{1}{Z_1 Z_2}}} = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2} \quad (28)$$

Writing $Z_{0\pi}$ for the characteristic impedance of a T section, and $Z_{0\pi}$ for the characteristic impedance of a π section having the same total series and shunt impedances, this gives :—

$$Z_{0\pi} = \frac{Z_1 Z_2}{Z_{0\pi}} \quad (29)$$

Open- and short-circuit impedances

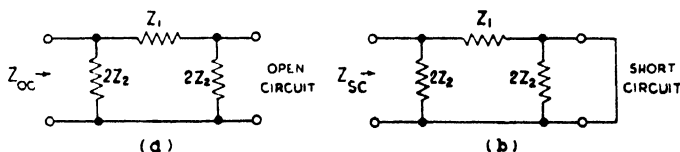


FIG. 579.—Symmetrical π section on open- and short-circuit.

If one side of the π section is open-circuited (see Fig. 579a), then the input impedance measured at the other side will be :—

$$Z_{oo} = \frac{2Z_2 (Z_1 + 2Z_2)}{2Z_2 + Z_1 + 2Z_2} = \frac{2Z_2 (Z_1 + 2Z_2)}{Z_1 + 4Z_2} \quad (30)$$

If one side is short-circuited (see Fig. 579b), then the input impedance measured at the other side will be :—

$$Z_{so} = \frac{2Z_1 Z_2}{Z_1 + 2Z_2} \quad (31)$$

The product of these two impedances is:—

$$\begin{aligned} Z_{00} \cdot Z_{80} &= \left\{ \frac{2Z_2(Z_1 + 2Z_2)}{Z_1 + 4Z_2} \right\} \times \left\{ \frac{2Z_1Z_2}{(Z_1 + 2Z_2)} \right\} \\ &= \frac{4Z_1Z_2^2}{Z_1 + 4Z_2} \\ &= \frac{Z_1^2Z_2^2}{\frac{Z_1^2}{4} + Z_1Z_2} \\ &= Z_0^2 \end{aligned}$$

Thus $Z_0 = \sqrt{Z_{00} \cdot Z_{80}}$ (32)

It will be noticed that this result is the same as that obtained for the T section (p. 571); in fact, it is of universal application for any symmetrical section.

Propagation constant

Consider a π section connected between a generator of internal impedance Z_0 and a load Z_0 . Let the input and output currents be I_s and I_R respectively (see Fig. 580).

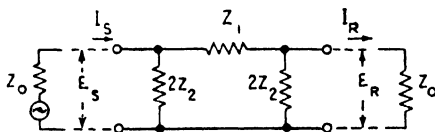


FIG. 580.—Propagation constant of π section.

Since the network is symmetrical, by definition:—

$$\frac{I_s}{I_R} = \frac{E_s}{E_R} = e^\gamma$$

From Fig. 580 it will be seen that:—

$$E_R = \frac{\frac{Z_0 \cdot 2Z_2}{Z_0 + 2Z_2}}{Z_1 + \frac{Z_0 \cdot 2Z_2}{Z_0 + 2Z_2}} \cdot E_s$$

$$\therefore \frac{E_s}{E_R} = e^\gamma = 1 + \frac{Z_1(Z_0 + 2Z_2)}{Z_0 \cdot 2Z_2}$$

Let $Y_0 = \frac{1}{Z_0}$, $Y_1 = \frac{1}{Z_1}$ and $Y_2 = \frac{1}{Z_2}$

$$\therefore e^\gamma = 1 + \frac{1}{Y_1} \left(Y_0 + \frac{Y_2}{2} \right)$$

$$e^\gamma = 1 + \frac{Y_2}{2Y_1} + \frac{Y_0}{Y_1} \tag{33}$$

$$\text{Hence } \gamma = \log_e \left\{ 1 + \frac{Y_2}{2Y_1} + \frac{Y_0}{Y_1} \right\} \quad (34)$$

This may be compared with the value of propagation constant obtained for a T section on page 573; it is important to note that it gives the same value.

$$\begin{aligned} \text{For } \gamma_\pi &= \log_e \left\{ 1 + \frac{Y_2}{2Y_1} + \frac{Y_{0\pi}}{Y_1} \right\} \\ &= \log_e \left\{ 1 + \frac{Z_1}{2Z_2} + \frac{Z_1}{Z_{0\pi}} \right\} \\ &= \log_e \left\{ 1 + \frac{Z_1}{2Z_2} + \frac{Z_1 Z_{0T}}{Z_1 Z_2} \right\} \\ \text{i.e. } \gamma_\pi &= \log_e \left\{ 1 + \frac{Z_1}{2Z_2} + \frac{Z_{0T}}{Z_2} \right\} \\ &= \gamma_T \end{aligned} \quad (35)$$

Hence all other expressions for γ derived for the T section apply also to the π section—e.g., $\cosh \gamma = 1 + \frac{Z_1}{2Z_2}$.

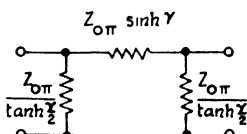


FIG. 581.— π section, showing values of components in terms of characteristic impedance and propagation constant.

The π section having characteristic impedance $Z_{0\pi}$ and propagation constant γ is shown in Fig. 581.

THE HALF-SECTION

Both the symmetrical T section of Fig. 582a and the symmetrical π section of Fig. 582b may be split into two half-sections. It will be seen that the resultant half-sections are identical, as shown in Fig. 582c; thus either a T section or a π section may be constructed from two such half-sections.

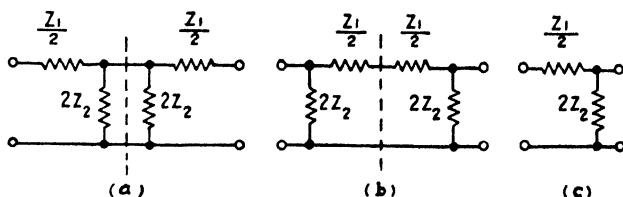


FIG. 582.—Showing how (a) a T section, and (b) a π section, is composed of two half-sections as in (c).

A half-section is an example of an asymmetrical network; the expression "characteristic impedance" does not therefore apply, and the network must be considered from the point of view of either iterative impedances or image impedances.

Iterative impedances

The two iterative impedances of a half-section may be found by calculating the input impedance Z'_0 when the section is terminated at the other pair of terminals in Z'_0 .

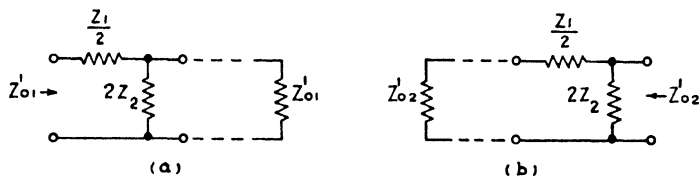


FIG. 583.—Iterative impedances of half-section.

Considering the half-section shown in Fig. 583a:—

$$Z'_{01} = \frac{Z_1}{2} + \frac{2Z_2 Z'_{01}}{2Z_2 + Z'_{01}}$$

$$\therefore 2Z_2 Z'_{01} + Z'_{01}{}^2 = Z_1 Z_2 + \frac{1}{2} Z_1 Z'_{01} + 2Z_2 Z'_{01}$$

$$\therefore Z'_{01}{}^2 - \frac{1}{2} Z_1 Z'_{01} - Z_1 Z_2 = 0$$

$$\therefore Z'_{01} = \sqrt{\frac{Z_1^2}{16} + Z_1 Z_2} + \frac{Z_1}{4} \tag{36}$$

Again, considering the half-section shown in Fig. 583b:—

$$Z'_{02} = \frac{2Z_2(\frac{1}{2}Z_1 + Z'_{02})}{2Z_2 + \frac{1}{2}Z_1 + Z'_{02}}$$

$$\therefore Z'_{02} = \sqrt{\frac{Z_1^2}{16} + Z_1 Z_2} - \frac{Z_1}{4} \tag{37}$$

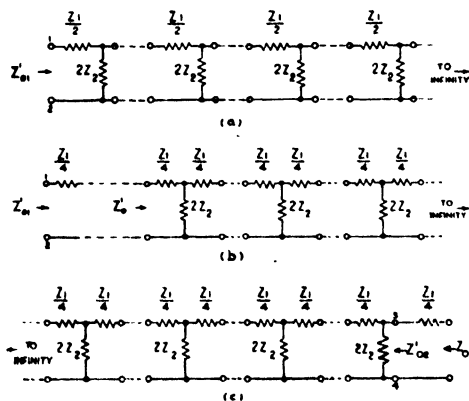


FIG. 584.—Ladder structure formed by an infinite number of half-sections.

The ladder structure formed by an infinite number of half-sections is shown in Fig. 584*a*; it can be seen to be identical with the series of T sections shown in Fig. 584*b* and *c* having series-arms $\frac{Z_1}{4}$ and shunt-arms $2Z_2$, with a series element $\frac{Z_1}{4}$ added at the input at 1, 2, and subtracted from the input at 3, 4. The characteristic impedance of the T section shown is $\sqrt{\frac{Z_1^2}{16} + Z_1 Z_2}$. The two iterative impedances of the half-sections are thus greater and less than this by $\frac{Z_1}{4}$.

Image impedances

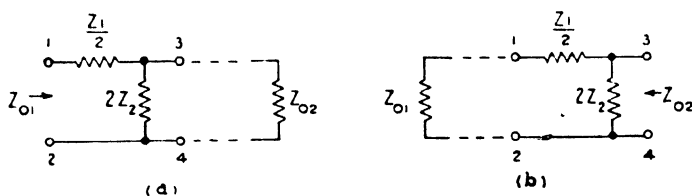


FIG. 585.—Image impedances of half-section.

Let the image impedances of the section be Z_{01} at terminals 1, 2, and Z_{02} at terminals 3, 4 (see Fig. 585).

By definition, if an impedance Z_{02} is connected to terminals 3, 4, the input impedance at 1, 2 will be Z_{01} .

$$Z_{01} = \frac{1}{2}Z_1 + \frac{2Z_2 Z_{02}}{2Z_2 + Z_{02}} = \frac{Z_1 Z_2 + \frac{1}{2}Z_1 Z_{02} + 2Z_2 Z_{02}}{2Z_2 + Z_{02}}$$

$$\therefore Z_{01} Z_{02} + 2Z_2 Z_{01} - \left(\frac{1}{2}Z_1 + 2Z_2\right) Z_{02} = Z_1 Z_2 \quad (38)$$

Similarly, if an impedance Z_{01} is connected to terminals 1, 2, the input impedance at 3, 4 will be Z_{02} .

From Fig. 585*b* :—

$$Z_{02} = \frac{2Z_2 \left(\frac{Z_1}{2} + Z_{01}\right)}{2Z_2 + \frac{Z_1}{2} + Z_{01}}$$

$$\therefore Z_{01} Z_{02} - 2Z_2 Z_{01} + \left(\frac{Z_1}{2} + 2Z_2\right) Z_{02} = Z_1 Z_2 \quad (39)$$

Subtracting equation 39 from 38 :—

$$4Z_2 Z_{01} - (Z_1 + 4Z_2) Z_{02} = 0$$

$$\text{Whence } \frac{Z_{01}}{Z_{02}} = \frac{\frac{Z_1}{4} + Z_2}{Z_2} \quad (40)$$

Adding equations 38 and 39:—

$$Z_{01}Z_{02} = Z_1Z_2$$

$$\therefore Z_{01}^2 = \left(\frac{Z_1 + Z_2}{\frac{Z_1}{2}} \right) Z_1Z_2$$

$$\therefore Z_{01} = \sqrt{\frac{Z_1^2}{4} + Z_1Z_2} = Z_{0T} \tag{41}$$

and
$$Z_{02} = \sqrt{\frac{Z_1^2}{4} + Z_1Z_2} = Z_{0\pi} \tag{42}$$

The image impedances on the two sides of a half-section having a series impedance $\frac{Z_1}{2}$ and a shunt impedance $2Z_2$ are thus seen

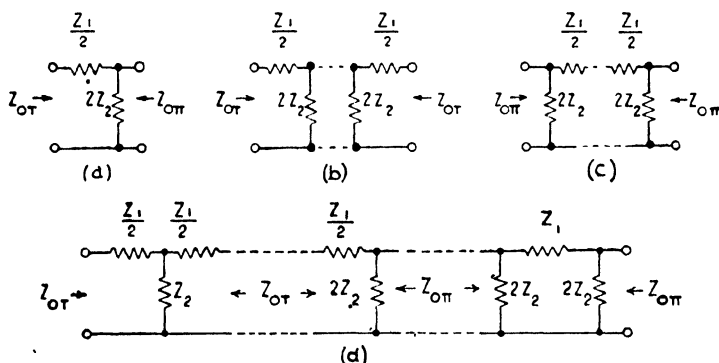


FIG. 586.—Matching a T and a π section, using a half-section.

to be Z_{0T} and $Z_{0\pi}$ (Fig. 586a). These impedances are equal respectively to the characteristic impedance of a T section and of a π section having a total series impedance Z_1 and a total shunt impedance Z_2 , that is, to the characteristic impedance of that T and of that π section which are produced by combining two such half-sections (Fig. 586b and c). A half-section can therefore be used for matching between a T section and a π section if both these have the same total series and shunt impedances (see Fig. 586d).

Open- and short-circuit impedances

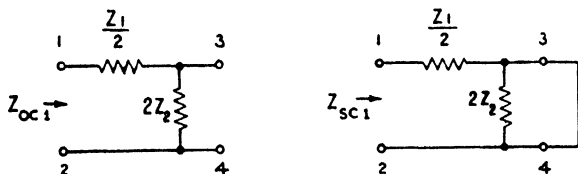


FIG. 587.—Impedances of half-section on open- and short-circuit, looking in at terminals 1 and 2.

The impedances presented at terminals 1, 2 of the half-section (Fig. 587) when the terminals 3, 4 are open- and short-circuited are :—

$$Z_{oo1} = \frac{Z_1}{2} + 2Z_2 \quad (43)$$

$$Z_{so1} = \frac{Z_1}{2} \quad (44)$$

$$\begin{aligned} \text{Hence } \sqrt{Z_{oo1}Z_{so1}} &= \sqrt{\left(\frac{Z_1}{2} + 2Z_2\right)\frac{Z_1}{2}} \\ &= \sqrt{\frac{Z_1^2}{4} + Z_1Z_2} \quad (45) \\ &= \text{image impedance looking in at 1, 2} \end{aligned}$$

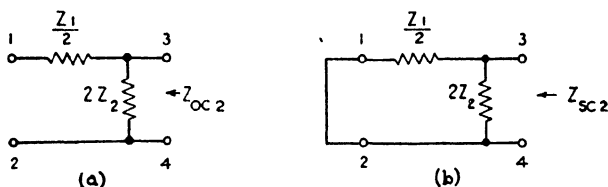


FIG. 588.—Impedances of half-section on open- and short-circuit, looking in at terminals 3 and 4.

Similarly, the impedances presented at terminals 3, 4 when 1, 2 are open- and short-circuited (Fig. 588) are :—

$$Z_{oo2} = 2Z_2$$

$$Z_{so2} = \frac{Z_1Z_2}{\frac{Z_1}{2} + 2Z_2}$$

$$\begin{aligned} \text{Hence } \sqrt{Z_{oo2}Z_{so2}} &= \sqrt{\frac{2Z_1Z_2^2}{\frac{Z_1}{2} + 2Z_2}} \\ &= \frac{Z_1Z_2}{\sqrt{\frac{Z_1^2}{4} + Z_1Z_2}} \quad (46) \\ &= \text{image impedance looking in at 3, 4.} \end{aligned}$$

Thus the impedances obtained by taking the geometric mean of the open- and short-circuit impedances at the two sides of the half-section are seen to be equal to the image impedance. *This is true for any asymmetrical network and provides a convenient method for the determination of the image impedances.*

THE L SECTION

The ladder network of Fig. 562*a* and *b* can be analysed into a series of "L" or "C" sections (Fig. 589) instead of T or π sections.

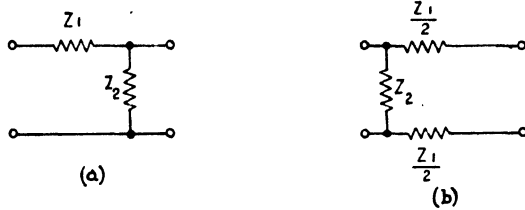


FIG. 589.—Unbalanced and balanced forms of L section.

Such sections are frequently used for matching purposes.

Iterative impedances

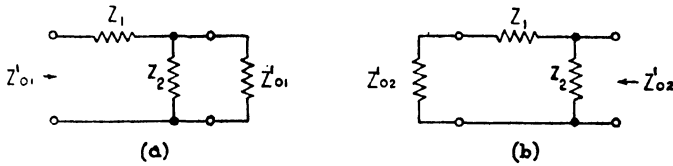


FIG. 590.—Iterative impedances of L section.

The iterative impedances of the L section (*see* Fig. 590) may be found by the same method as adopted for the half-section:—

$$Z'_{01} = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2 + \frac{Z_1}{2}} \quad (47)$$

$$Z'_{02} = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2 - \frac{Z_1}{2}} \quad (48)$$

Image impedances

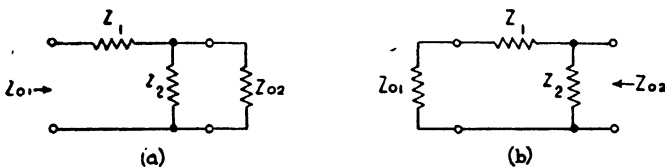


FIG. 591.—Image impedances of L section.

The image impedances of the L section (*see* Fig. 591) may be found by the method previously adopted; they are of course also equal to the geometric means of the corresponding open- and short-circuit impedances.

$$Z_{01} = \sqrt{Z_{001} \cdot Z_{sc1}} = \sqrt{Z_1 Z_2 + Z_1^2} \quad (49)$$

$$Z_{02} = \sqrt{Z_{002} \cdot Z_{sc2}} = \frac{Z_1 Z_2}{\sqrt{Z_1 Z_2 + Z_1^2}} \quad (50)$$

Z_1 and Z_2 may be obtained in terms of Z_{01} and Z_{02} , giving :—

$$Z_1 = \sqrt{Z_{01}(Z_{01} - Z_{02})} \quad (51)$$

$$Z_2 = Z_{02} \sqrt{\frac{Z_{01}}{Z_{01} - Z_{02}}} \quad (52)$$

THE LATTICE SECTION

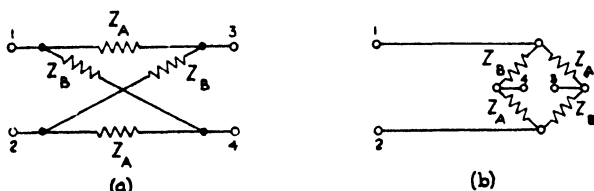


FIG. 592.—Lattice section, with representation as a bridge.

Lattice sections are symmetrical and balanced, and will therefore have characteristic impedances and propagation constants. The lattice structure, Fig. 592*a*, may be redrawn as a bridge structure, Fig. 592*b*.

Characteristic impedance

Let the lattice section of Fig. 593*a* be terminated at terminals 3, 4 in an impedance Z_0 . Then if Z_0 is the characteristic impedance of the section, the impedance looking into terminals 1, 2 will also be Z_0 .

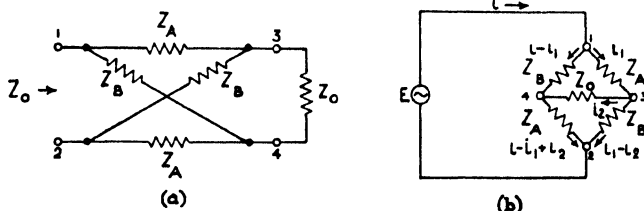


FIG. 593.—Characteristic impedance of lattice section.

The value of impedance looking into terminals 1, 2 can be found by the application of Kirchhoff's Laws. The meshes may be seen more clearly by redrawing Fig. 593*a* in the bridge form, as in Fig. 593*b*.

Let the voltage applied to terminals 1, 2, be E , and let currents i_1 and i_2 flow as indicated.

From the mesh 1, 4, 3, 2 :—

$$\begin{aligned} E &= (i - i_1)Z_B - i_2Z_0 + (i_1 - i_2)Z_B \\ \text{i.e.} \quad E &= iZ_B - i_2(Z_0 + Z_B) \end{aligned} \quad (53)$$

From the mesh 1, 3, 4, 2:—

$$\begin{aligned} E &= i_1 Z_A + i_2 Z_0 + (i - i_1 + i_2) Z_A \\ \text{i.e.} \quad E &= i Z_A + i_2 (Z_0 + Z_A) \end{aligned} \quad (54)$$

From these two equations:—

$$\begin{aligned} i_2 &= \frac{E - i Z_A}{Z_0 + Z_A} = \frac{i Z_B - E}{Z_0 + Z_B} \\ \therefore \frac{E}{i} (2Z_0 + Z_A + Z_B) &= Z_A (Z_0 + Z_B) + Z_B (Z_0 + Z_A) \end{aligned} \quad (55)$$

But $\frac{E}{i}$ = input impedance at 1, 2, = Z_0

$$\begin{aligned} \therefore Z_0 (2Z_0 + Z_A + Z_B) &= Z_A (Z_0 + Z_B) + Z_B (Z_0 + Z_A) \\ \therefore 2Z_0^2 &= 2Z_A Z_B \\ Z_0 &= \sqrt{Z_A Z_B} \end{aligned} \quad (56)$$

Open- and short-circuit impedances

The impedances presented at one pair of terminals of a lattice section, when the other pair is open- and short-circuited, are respectively:—

$$Z_{oo} = \frac{1}{2}(Z_A + Z_B) \quad (57)$$

$$Z_{so} = \frac{2Z_A Z_B}{Z_A + Z_B} \quad (58)$$

$$\therefore \sqrt{Z_{oo} \cdot Z_{so}} = \sqrt{\frac{1}{2}(Z_A + Z_B) \cdot \frac{2Z_A Z_B}{Z_A + Z_B}} = \sqrt{Z_A Z_B} = Z_0 \quad (59)$$

This verifies once again that the geometric mean of the open- and short-circuit impedances equals the characteristic impedance Z_0 (image impedance in the case of asymmetrical sections).

Propagation constant

Let γ be the propagation constant. By definition:—

$$\frac{i}{i_2} = e^\gamma$$

From equation 55 above:—

$$i_2 = \frac{E - i Z_A}{Z_0 + Z_A} = \frac{i Z_B - E}{Z_0 + Z_B}$$

But $E = i Z_0$

$$\therefore i_2 = \frac{Z_0 - Z_A}{Z_0 + Z_A} = \frac{Z_B - Z_0}{Z_0 + Z_B}$$

$$\text{Hence } e^\gamma = \frac{Z_0 + Z_A}{Z_0 - Z_A} = \frac{Z_B + Z_0}{Z_B - Z_0} \quad (60)$$

$$\text{or } \gamma = \log. \frac{Z_0 + Z_A}{Z_0 - Z_A} = \log. \frac{Z_B + Z_0}{Z_B - Z_0} \quad (61)$$

In addition, since $e^\gamma = \frac{Z_0 + Z_A}{Z_0 - Z_A}$,

$$Z_A (e^\gamma + 1) = Z_0 (e^\gamma - 1)$$

$$\therefore \frac{Z_A}{Z_0} = \frac{e^\gamma - 1}{e^\gamma + 1} = \frac{e^{\frac{\gamma}{2}} - e^{-\frac{\gamma}{2}}}{e^{\frac{\gamma}{2}} + e^{-\frac{\gamma}{2}}} = \tanh \frac{\gamma}{2} \tag{62}$$

$$\therefore \tanh \frac{\gamma}{2} = \frac{Z_A}{Z_0} = \frac{Z_A}{\sqrt{Z_A Z_B}} = \sqrt{\frac{Z_A}{Z_B}} \tag{63}$$

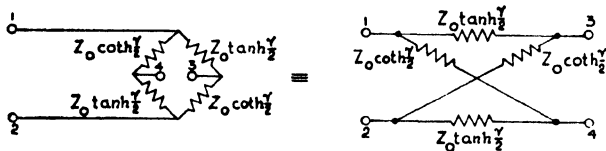


FIG. 594.—Lattice section, showing values of components in terms of characteristic impedance and propagation constant.

The lattice section having characteristic impedance Z_0 and propagation constant γ , deduced from equations 56 and 63, is shown in Fig. 594.

THE BRIDGED-T SECTION

Characteristic impedance

The characteristic impedance of the bridged-T section may be found, as in the case of the lattice section, by assuming one pair of terminals to be terminated in Z_0 , and an EMF E to be applied

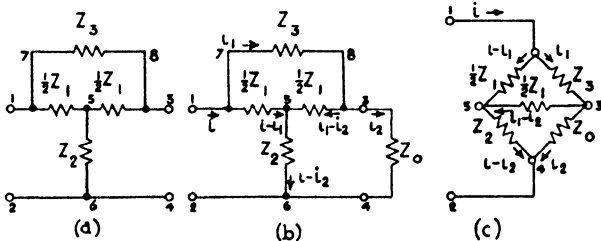


FIG. 595.—Bridged-T section.

to the other pair of terminals. Then, if currents flow as indicated in Fig. 595b, the following equations are obtained:—

From the mesh 178342:— $i_1 Z_3 + i_2 Z_0 = E$ (64)

whence $i_1 = \frac{E}{Z_3} - \frac{i_2 Z_0}{Z_3}$

From the mesh 15342:— $i \cdot \frac{Z_1}{2} - i_1 Z_1 + i_2 \left(\frac{Z_1}{2} + Z_0 \right) = E$ (65)

$$\text{From the mesh 1562 :— } i\left(\frac{Z_1}{2} + Z_3\right) - i_1\frac{Z_1}{2} - i_2Z_3 = E \quad (66)$$

Solving these equations gives :—

$$Z_0 = \sqrt{\left(\frac{Z_1^2}{4} + Z_1Z_3\right) \frac{Z_3}{Z_1 + Z_3}} \quad (67)$$

In practice, the two series links $\frac{Z_1}{2}$ are frequently made equal to Z_0 . Equation 67 then reduces to :—

$$Z_0 = \sqrt{Z_2Z_3} \quad (68)$$

Open- and short-circuit impedances of bridged-T section

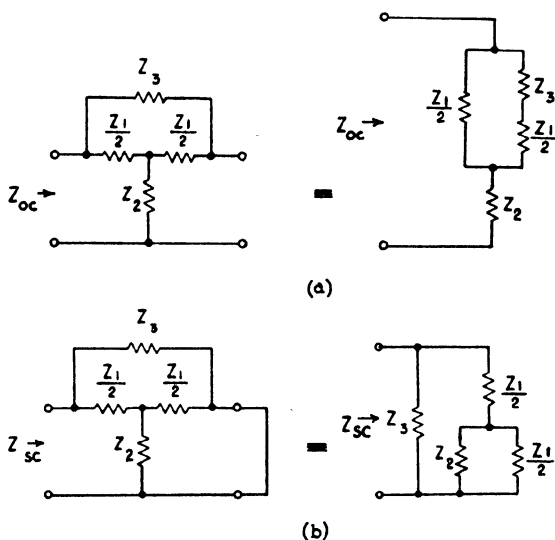


FIG. 596.—Bridged-T section on open- and short-circuit.

The impedances presented at one pair of terminals of the bridged-T section, while the other pair of terminals is open-circuited and short-circuited, are respectively :—

$$\begin{aligned} Z_{00} &= Z_2 + \frac{\frac{1}{2}Z_1(\frac{1}{2}Z_1 + Z_3)}{Z_1 + Z_3} \\ &= \frac{Z_3(Z_1 + Z_3) + \frac{1}{2}Z_1(\frac{1}{2}Z_1 + Z_3)}{Z_1 + Z_3} \\ Z_{s0} &= \frac{Z_3 \left\{ \frac{1}{2}Z_1 + \frac{\frac{1}{2}Z_1Z_3}{\frac{1}{2}Z_1 + Z_3} \right\}}{Z_3 + \frac{1}{2}Z_1 + \frac{\frac{1}{2}Z_1Z_3}{\frac{1}{2}Z_1 + Z_3}} \end{aligned} \quad (69)$$

$$\begin{aligned}
 &= \frac{Z_1 Z_3 (\frac{1}{2} Z_1 + Z_3)}{\frac{1}{2} Z_1 (\frac{1}{2} Z_1 + Z_3) + Z_3 (Z_1 + Z_3)} \quad (70) \\
 \therefore \sqrt{Z_{00} Z_{30}} &= \sqrt{\frac{Z_1 Z_3 (\frac{1}{2} Z_1 + Z_3)}{Z_1 + Z_3}} \\
 &= \sqrt{\left(\frac{Z_1^2}{4} + Z_1 Z_3\right) \cdot \frac{Z_3}{Z_1 + Z_3}}
 \end{aligned}$$

Hence $Z_0 = \sqrt{Z_{00} Z_{30}}$

Propagation constant

From equations 64 and 65 :—

$$\begin{aligned}
 i_s &= \frac{iZ_0(Z_1 + Z_3) - i\frac{1}{2}Z_1 Z_3}{Z_0 Z_1 + \frac{1}{2}Z_1 Z_3 + Z_3 Z_0} \\
 &= \frac{i\{Z_0(Z_1 + Z_3) - \frac{1}{2}Z_1 Z_3\}}{Z_0(Z_1 + Z_3) + \frac{1}{2}Z_1 Z_3} \\
 \therefore \frac{i}{i_s} &= \frac{Z_0(Z_1 + Z_3) + \frac{1}{2}Z_1 Z_3}{Z_0(Z_1 + Z_3) - \frac{1}{2}Z_1 Z_3} \\
 \therefore \gamma &= \log_e \frac{Z_0(Z_1 + Z_3) + \frac{1}{2}Z_1 Z_3}{Z_0(Z_1 + Z_3) - \frac{1}{2}Z_1 Z_3} \quad (71)
 \end{aligned}$$

When $\frac{Z_1}{2} = Z_0$, this reduces to :—

$$\gamma = \log_e \left(1 + \frac{Z_3}{Z_0}\right) \quad (72)$$

or, on substituting for Z_3 from equation 68, to :—

$$\gamma = \log_e \left(1 + \frac{Z_0}{Z_3}\right) \quad (73)$$

NETWORK EQUIVALENCE THEOREMS**Equivalence of T and π sections***

Theorem.—At any one frequency a T section can be interchanged, in any network, with a π section, and *vice versa*, provided that certain relations are maintained between the elements of the two sections.

Since the T section, Fig. 597a, may be redrawn as a *star* (Fig. 597b), and the π section, Fig. 597c, may be redrawn as a *mesh* (Fig. 597d), this is sometimes known as a "star-mesh conversion".

If the impedance looking into the terminals 1 and 3 are equated for the two sections, the following relationship is obtained :—

$$Z_1 + Z_3 = \frac{Z_0(Z_A + Z_B)}{Z_A + Z_B + Z_0} \quad (74)$$

* The T and π sections so far discussed have *not* been equivalent, but have been related to the same ladder network. In this section, electrically equivalent T and π networks are considered.

Similarly, equating impedances looking into terminals 3 and 4,

$$Z_3 + Z_3 = \frac{Z_A(Z_B + Z_0)}{Z_A + Z_B + Z_0} \tag{75}$$

and equating impedances looking into terminals 1 and 2:—

$$Z_3 + Z_1 = \frac{Z_B(Z_0 + Z_A)}{Z_A + Z_B + Z_0} \tag{76}$$

Now add equations 74 and 76 and subtract 75,

$$Z_1 = \frac{Z_B Z_0}{Z_A + Z_B + Z_0} = \frac{Z_B Z_0}{\Delta} \tag{77}$$

where $\Delta = Z_A + Z_B + Z_0$

Similarly, adding 74 and 75 and subtracting 76,

$$Z_2 = \frac{Z_0 Z_A}{Z_A + Z_B + Z_0} = \frac{Z_0 Z_A}{\Delta} \tag{78}$$

Finally adding 75 and 76 and subtracting 74,

$$Z_3 = \frac{Z_A Z_B}{Z_A + Z_B + Z_0} = \frac{Z_A Z_B}{\Delta} \tag{79}$$

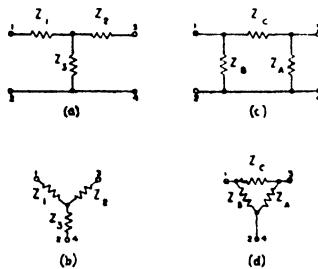


FIG. 597.—T section represented as a star, and π section represented as a mesh.

These equations, 77, 78 and 79, give the relations between the impedance elements for a certain impedance equivalence between the two sections under rather special conditions. It will now be shown that these equations give the equivalence of the two sections under the more stringent conditions depicted in Fig. 598a and b. In Fig. 598a the T section is used to connect a

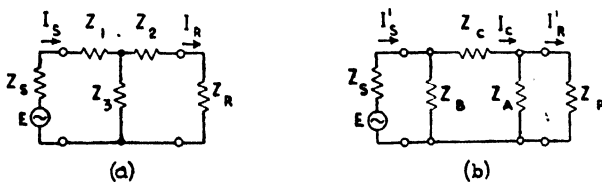


FIG. 598.—(a) T section, and (b) π section, connecting a generator to a load.

generator of internal impedance Z_s and voltage E to a load impedance Z_B . In Fig. 598*b* the π section is used to connect the same generator to the same load. The equivalence of the two sections will be proved by showing that the currents I_s and I_B are the same for the two networks.

From Fig. 598*a* the current I_s is seen to be :—

$$I_s = \frac{E}{Z_s + Z_1 + \frac{Z_2(Z_3 + Z_B)}{Z_2 + Z_3 + Z_B}} \quad (80)$$

Now suppose that Z_1 , Z_2 and Z_3 have the values given by equations 77, 78 and 79 respectively. Substituting these values in equation 80 gives :—

$$I_s = \frac{E}{Z_s + \frac{Z_B(Z_B Z_0 + Z_B Z_A + Z_0 Z_A)}{Z_0 Z_A + Z_A Z_B + \Delta Z_B}} \quad (81)$$

From Fig. 598*b*, the current I'_s is seen to be :—

$$I'_s = \frac{E}{Z_s + \frac{Z_B \left(Z_0 + \frac{Z_A Z_B}{Z_A + Z_B} \right)}{Z_B + Z_0 + \frac{Z_A Z_B}{Z_A + Z_B}}}$$

$$\text{i.e.} \quad I'_s = \frac{E}{Z_s + \frac{Z_B(Z_0 Z_A + Z_B Z_0 + Z_B Z_A)}{Z_A Z_B + Z_0 Z_A + Z_B \Delta}} \quad (82)$$

Hence $I_s = I'_s$

From Fig. 598*a* :—

$$I_B = \frac{Z_3}{Z_2 + Z_3 + Z_B} I_s$$

or, if Z_1 , Z_2 and Z_3 have the values assigned to them by equations 77, 78 and 79 respectively :—

$$I_B = \frac{Z_A Z_B}{Z_0 Z_A + Z_A Z_B + \Delta Z_B} I_s \quad (83)$$

From Fig. 598*b* :—

$$I'_B = \frac{Z_A}{Z_A + Z_B} I_0, \text{ where } I_0 \text{ is the current in the}$$

impedance Z_0 .

Similarly,

$$I_0 = \frac{Z_B}{Z_B + Z_0 + \frac{Z_A Z_B}{Z_A + Z_B}} I'_s$$

$$\therefore I'_B = \frac{Z_A Z_B}{Z_A Z_B + Z_0 Z_A + \Delta Z_B} I'_s \quad (84)$$

But $I'_s = I_s$; hence, comparing equations 83 and 84, it will be seen that $I'_B = I_B$.

The two sections are therefore equivalent when a generator of

impedance Z_B is connected to terminals 1 and 3, and a load impedance Z_C to terminals 2 and 3. Since the equations 81, 82, 83 and 84 are all symmetrical with respect to Z_A , Z_B and Z_C (that is, they are unchanged if Z_A , Z_B and Z_C are interchanged in cyclic order), it follows that the sections are equivalent if the load and generator are each connected to any two of the three terminals. Finally, since E , Z_B and Z_C are quite general values, the equivalence in all respects of the two sections is established.

Given a π section, therefore, it is possible to replace it in any network by the equivalent T section whose elements are given by equations 77, 78 and 79.

$$\text{Let } \Delta' = Z_2 Z_3 + Z_3 Z_1 + Z_1 Z_2$$

Then, from equations 77, 78 and 79 :—

$$\Delta' = \frac{Z_A^2 Z_B Z_C + Z_B^2 Z_C Z_A + Z_C^2 Z_A Z_B}{\Delta^2}$$

$$\text{i.e. } \Delta' = \frac{Z_A Z_B Z_C}{\Delta}$$

$$\text{i.e. } \frac{\Delta'}{Z_1} = Z_A, \text{ using equation 77}$$

$$\text{i.e. } Z_A = \frac{Z_2 Z_3 + Z_3 Z_1 + Z_1 Z_2}{Z_1} \quad (85)$$

$$\text{Similarly, } Z_B = \frac{Z_2 Z_3 + Z_3 Z_1 + Z_1 Z_2}{Z_2} \quad (86)$$

$$\text{and } Z_C = \frac{Z_2 Z_3 + Z_3 Z_1 + Z_1 Z_2}{Z_3} \quad (87)$$

Therefore, given a T section, it is possible to replace it in any network by the equivalent π section whose elements are given by equations 85, 86 and 87.

It is possible to simplify these results by considering admittances instead of impedances. Thus :—

$$\frac{\Delta'}{Z_1 Z_2 Z_3} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}$$

$$\text{i.e. } \Delta' = \frac{Y_1 + Y_2 + Y_3}{Y_1 Y_2 Y_3}$$

Now, from (85) :—

$$Y_A = \frac{1}{Y_1 \Delta'} = \frac{Y_1 Y_2 Y_3}{Y_1 (Y_1 + Y_2 + Y_3)}$$

$$\text{i.e. } Y_A = \frac{Y_2 Y_3}{Y_1 + Y_2 + Y_3} = \frac{Y_2 Y_3}{\Delta''} \quad (88)$$

$$\text{where } \Delta'' = Y_1 + Y_2 + Y_3$$

$$\text{Similarly, } Y_B = \frac{Y_3 Y_1}{Y_1 + Y_2 + Y_3} = \frac{Y_3 Y_1}{\Delta''} \quad (89)$$

$$\text{and } Y_C = \frac{Y_1 Y_2}{Y_1 + Y_2 + Y_3} = \frac{Y_1 Y_2}{\Delta''} \quad (90)$$

The significance of the statement that this theorem is true only at a single frequency will be made clear by an example.

Example.—

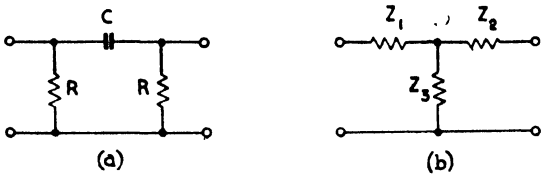


FIG. 599.

Suppose the simple π structure of Fig. 599a is part of a more complex network, and consider a particular frequency having a corresponding angular velocity ω_0 . Using the notation of Fig. 598b:—

$$Z_A = Z_B = R \text{ and } Z_C = \frac{-j}{\omega_0 C}$$

Now apply the theorem and replace the π section by the equivalent T section of Fig. 599b. Using equations 77, 78 and 79:—

$$Z_1 = Z_2 = \frac{\frac{-jR}{\omega_0 C}}{2R - \frac{j}{\omega_0 C}} = \frac{-jR(2\omega_0 CR + j)}{4\omega_0^2 C^2 R^2 + 1}$$

$$\text{i.e. } Z_1 = Z_2 = \frac{R - j2\omega_0 CR^2}{4\omega_0^2 C^2 R^2 + 1}$$

$$\text{and } Z_3 = \frac{R^2}{2R - \frac{j}{\omega_0 C}} = \frac{(2\omega_0 CR^2 + jR^2)\omega_0 C}{4\omega_0^2 C^2 R^2 + 1}$$

Z_1 and Z_2 are equivalent to resistances in series with condensers, but the values of resistance and capacity both depend on ω_0 . Similarly, Z_3 is equivalent to a resistance in series with an inductance, the values of both components depending on ω_0 . If therefore some other frequency ω'_0 is chosen, an entirely different T section will result. It is also important to notice that in some cases a resistive or reactive element in the equivalent circuit may turn out to be negative; that is to say, the equivalent circuit may not be physically realizable using passive components.

Equivalence of a complex network to a simple three-element configuration

Theorem.—Any four-terminal network made up of linear impedances, no matter how complex it may be, can be represented, at a single frequency, by a simple T or π section.

This theorem follows at once from the equivalence of the T and π section. A complicated network can be reduced to a single section by successive transformations from T to π and the reverse, as will be seen from the following example.

Example.—

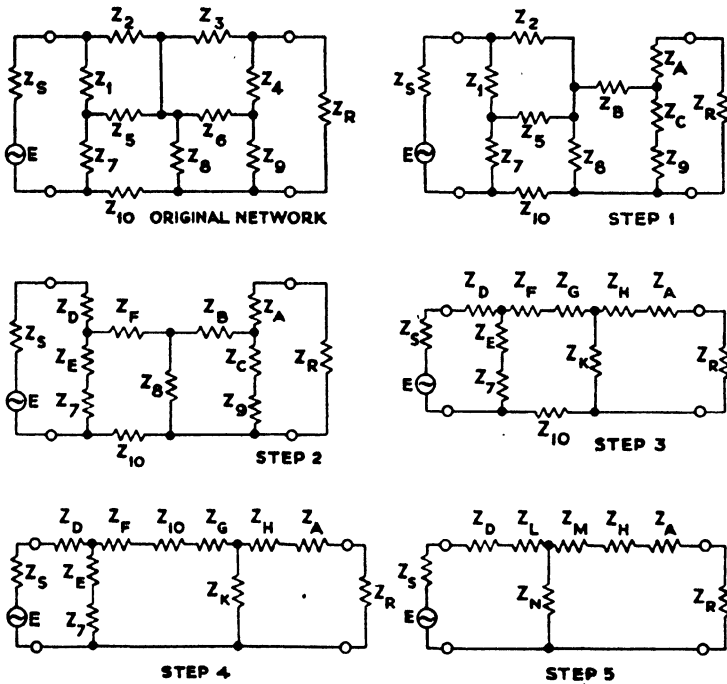


Fig. 600.—Reduction of a complex network to a simple T section.

Fig. 600 shows the reduction of a fairly complex network to a simple T section in 5 steps; the number of steps required in a particular case will, of course, increase with the complexity of the network.

- Step 1. Reduce the π network consisting of Z_3 , Z_4 and Z_6 to a T network Z_A , Z_B , Z_C .
- Step 2. Reduce the π network Z_2 , Z_1 , Z_5 to a T network Z_D , Z_B , Z_F .
- Step 3. Reduce the π network Z_8 , Z_B , $Z_0 + Z_9$ to a T network Z_G , Z_B , Z_K .
- Step 4. Transfer the impedance Z_{10} from the lower to the upper arm of the network. This is permissible because the same current flows through Z_{10} and through Z_F and Z_9 in series. Z_{10} can therefore be placed in series with Z_F and Z_9 in the same arm without affecting the voltage developed across the load impedance Z_R .
- Step 5. Reduce the π network $Z_7 + Z_B$, $Z_F + Z_{10} + Z_G$, Z_K to a T network Z_L , Z_M , Z_N .

A simple T section now connects the generator and load, the T section being the equivalent of the original transmission network.

Though it is sometimes useful to perform the actual reduction of a complex network to a simple equivalent T or π section, the most important aspect of this theorem is the fact that it demonstrates the existence of such simple equivalent circuits.

T and π sections equivalent to a perfect transformer

For some purposes, it is convenient to replace the separate primary and secondary circuits of a perfect transformer by one circuit linked by a network of impedances. "T" and " π " sections can be used to represent a perfect transformer that has an impedance in series or in shunt with either winding.

The values of the components of these equivalent networks are derived by considering the impedances at the input and at the output terminals with the other terminals open- and short-circuited.

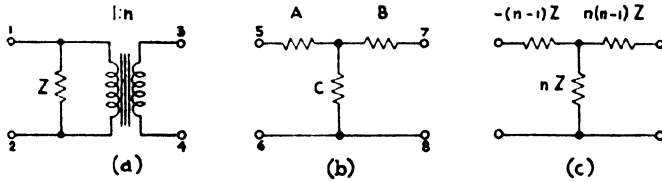


FIG. 601.—Transformer with an impedance Z across primary, and equivalent T section.

For example, suppose that the transformer in Fig. 601a can be replaced by the T network of Fig. 601b. If this supposition is justified, then the impedance between terminals 1 and 2, with terminals 3 and 4 open-circuited (which will be denoted by Z_{1200}), must be the same as that (Z_{5600}) between terminals 5 and 6, with 7 and 8 open-circuited.

$$\text{Hence:—} \quad Z_{1200} = Z_{5600}, \quad \text{or} \quad Z = A + C \quad (91)$$

$$\text{Similarly,} \quad Z_{3400} = Z_{7800}, \quad \text{or} \quad n^2 Z = B + C \quad (92)$$

$$\text{and} \quad Z_{1280} = Z_{5680}, \quad \text{or} \quad 0 = A + \frac{BC}{B+C} \quad (93)$$

$$\text{and} \quad Z_{3480} = Z_{7880}, \quad \text{or} \quad 0 = B + \frac{AC}{A+C} \quad (94)$$

$$\text{From (91) and (92),} \quad A = (Z - C) \quad \text{and} \quad B = (n^2 Z - C)$$

$$\text{From (93),} \quad AB + BC + CA = 0$$

$$\therefore (Z - C)(n^2 Z - C) + (n^2 Z - C)C + C(Z - C) = 0$$

$$\therefore n^2 Z^2 - CZ - n^2 CZ + C^2 + n^2 CZ - C^2 + CZ - C^2 = 0$$

$$\therefore n^2 Z^2 - C^2 = 0$$

$$\therefore C = nZ$$

$$A = Z - nZ = -(n-1)Z \quad (95)$$

$$B = n^2 Z - nZ = n(n-1)Z \quad (96)$$

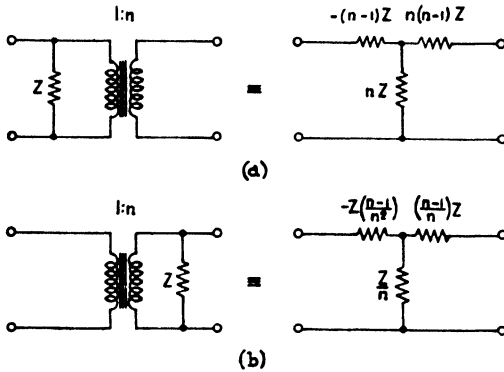


FIG. 602.—Transformers with impedances in shunt with primary and secondary windings, together with equivalent T sections.

The components of the equivalent T network therefore have the values shown in Fig. 601c. Some of the more useful equivalent T and π networks are shown in Figs. 602 and 603. It must be noted that, in each case, one component is a negative impedance, and the equivalent circuit of the transformer alone can never be physically realised using passive components (unless Z is a pure reactance, in which case the equivalent circuit can be physically realised at any one frequency). However, when the transformer is connected into a circuit, the negative impedance may come in series or parallel with a large positive impedance, so that the two can be replaced by a single (smaller) positive impedance. The circuit as a whole can then be represented by a physically realizable equivalent circuit.

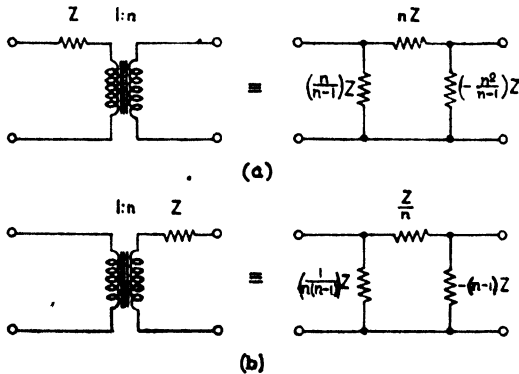


FIG. 603.—Transformers with impedances in series with primary and secondary windings, together with equivalent π sections.

Development of lattice sections with series impedances

Theorem.—If any impedance Z be subtracted simultaneously from all four arms of a lattice section, and placed in series with the input and output terminals of the section, then the resulting section is electrically identical to the original lattice section.

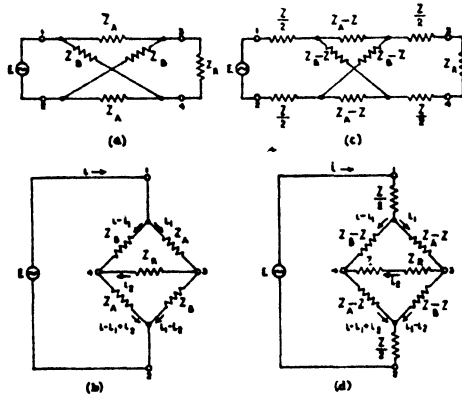


FIG. 604.—Development of lattice section with series impedances.

Consider the lattice section shown in Fig. 604*a*, and the resulting section (Fig. 604*c*) when it is modified in this way. Let these two sections be terminated on one side with any impedance Z_B , and let a voltage E be applied to the other pair of terminals. Then if currents flow as indicated in the figures, the application of Kirchhoff's second law to the two sections yields the following equations:—

Original lattice section (Fig. 604*b*):—

$$\text{Mesh 1432.} \quad E = (i - i_1)Z_B - i_2Z_B + (i_1 - i_2)Z_B$$

$$\text{i.e.} \quad E = iZ_B - i_2(Z_B + Z_B) \quad (97)$$

$$\text{Mesh 1342.} \quad E = i_1Z_A + i_2Z_B + (i - i_1 + i_2)Z_A$$

$$\text{i.e.} \quad E = iZ_A + i_2(Z_A + Z_B) \quad (98)$$

Putting Z_B equal to the characteristic impedance Z_0 , these equations can be solved, as on page 587, to give the characteristic impedance Z_0 and the propagation constant γ , namely:—

$$Z_0 = \sqrt{Z_A Z_B}$$

$$\text{and} \quad \gamma = \log_e \frac{Z_0 + Z_A}{Z_0 - Z_A} = \log_e \frac{Z_B + Z_0}{Z_B - Z_0}$$

Modified lattice section (Fig. 604*d*):—

$$\text{Mesh 1432.} \quad E = \frac{1}{2}Zi + (i - i_1)(Z_B - Z) - i_2(Z + Z_B)$$

$$\quad \quad \quad + (i_1 - i_2)(Z_B - Z) + \frac{1}{2}Zi$$

$$\text{i.e.} \quad E = iZ_B - i_2(Z_B + Z_B) \quad (99)$$

$$\begin{aligned} \text{Mesh 1342.} \quad E &= \frac{1}{2}Zi + i_1(Z_A - Z) + i_2(Z + Z_B) \\ &\quad + (i - i_1 + i_2)(Z_A - Z) + \frac{1}{2}Zi \\ \text{i.e.} \quad E &= iZ_A + i_2(Z_B + Z_A) \end{aligned} \tag{100}$$

Equations 99 and 100 are seen to be identical with equations 97 and 98 respectively, and they will therefore yield the same results for Z_θ and for γ . The modified lattice section of Fig. 604c is therefore electrically equivalent to the original lattice section of Fig. 604a.

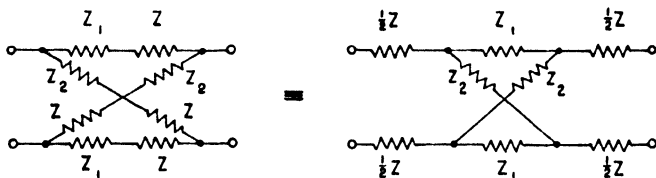


FIG. 605.—Lattice section, and equivalent developed section with series impedances.

In practice, this theorem is most useful when all four arms of the lattice section have a common series impedance. This is illustrated in Fig. 605, where $Z_A = Z_1 + Z$ and $Z_B = Z_2 + Z$.

Equivalence of a lattice to a T section

Theorem.—A lattice section can be interchanged, in any network, with a T section, and *vice versa*, provided that certain relations are maintained between the elements of the two sections.

This theorem follows from the last theorem. No restriction was imposed on the value of the impedance Z that was subtracted

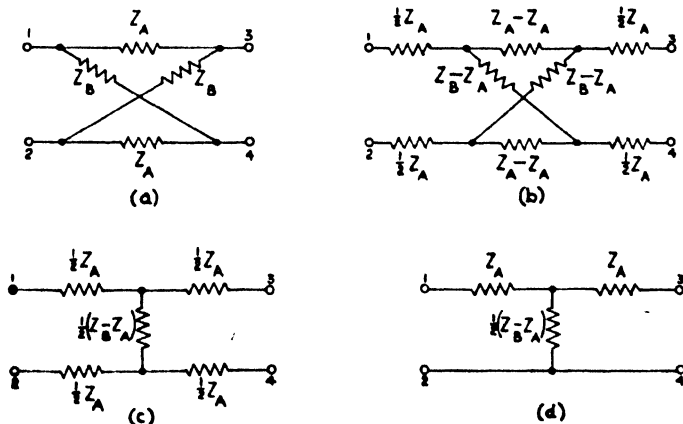


FIG. 606.—Equivalence of lattice and T sections.

from all four arms of the lattice section, and placed in series with the terminals; Z can therefore be made equal to Z_A .

When Z_A is subtracted from all four arms of the section shown in Fig. 606*a*, and placed in series with the terminals, the "lattice" arms are seen (Fig. 606*b*) to be in parallel, and the resulting section can be redrawn as in Fig. 606*c*. This is a balanced T section, the unbalanced form of which is shown in Fig. 606*d*.

The characteristic impedance and propagation constant of the T section shown in Fig. 606*d* are given by:—

$$\begin{aligned} Z_{0T} &= \sqrt{\frac{1}{4}(2Z_A)^2 + 2Z_A \frac{1}{2}(Z_B - Z_A)} \\ &= \sqrt{Z_A Z_B} \end{aligned} \quad (101)$$

$$\begin{aligned} \text{and } \gamma_T &= \log^* \left\{ 1 + \frac{2Z_A}{(Z_B - Z_A)} + \frac{2Z_0}{(Z_B - Z_A)} \right\} \\ &= \log^* \left(\frac{Z_A + 2Z_0 + Z_B}{Z_B - Z_A} \right) \\ &= \log^* \frac{\sqrt{Z_B} + \sqrt{Z_A}}{\sqrt{Z_B} - \sqrt{Z_A}} = \log^* \frac{Z_0 + Z_A}{Z_0 - Z_A} \end{aligned} \quad (102)$$

These results are identical with those obtained on page 587 for the original lattice section of Fig. 606*a*, and therefore the two sections are electrically equivalent.

Development of lattice sections with shunt impedances

Theorem.—If any admittance Y be subtracted simultaneously from all four arms of a lattice section, and placed across the input and output terminals, then the resulting section is electrically identical to the original lattice section.

Consider the lattice section shown in Fig. 607*a*, and the resulting section (Fig. 607*d*) when it is modified in this way. Let these two sections be terminated on one side with any admittance Y_B , and let a voltage E , applied to the other pair of terminals, cause an input current i . Let the voltages appearing across the various components of the two networks be as shown in Figs. 607*b* and *e* respectively; then the currents flowing will be as indicated in Figs. 607*c* and *f* and the application of Kirchhoff's first law to each terminal in turn yields the following equations:—

Original lattice section (Fig. 607*c*):—

$$\begin{aligned} \text{Terminal 1.} \quad & i = Y_B(E_1 + E_2) + Y_A E_1 \\ \text{i.e.} \quad & i = E_1(Y_A + Y_B) + E_2 Y_B \end{aligned} \quad (103)$$

$$\begin{aligned} \text{Terminal 2.} \quad & i = Y_A(E - E_1 - E_2) + Y_B(E - E_1) \\ \text{i.e.} \quad & i = E(Y_A + Y_B) - E_1(Y_A + Y_B) - E_2 Y_A \end{aligned} \quad (104)$$

$$\begin{aligned} \text{Terminal 3.} \quad & 0 = Y_B(E - E_1) + Y_B E_2 - Y_A E_1 \\ \text{i.e.} \quad & 0 = E Y_B - E_1(Y_A + Y_B) + E_2 Y_B \end{aligned} \quad (105)$$

From (103) and (105) :—

$$i = EY_B + E_2(Y_B + Y_R) \tag{106}$$

From (104) and (105) :—

$$i = EY_A - E_2(Y_A + Y_B) \tag{107}$$

Putting Y_R equal to Y_0 , and eliminating E_2 from equations 106 and 107, one obtains :—

$$Y_0 = \frac{i}{E} = \frac{Y_A(Y_B + Y_0) + Y_B(Y_A + Y_0)}{Y_A + Y_B + 2Y_0}$$

Whence

$$Y_0 = \sqrt{Y_A Y_B}$$

And therefore

$$Z_0 = Y_0^{-1} = \frac{1}{\sqrt{Y_A Y_B}} = \sqrt{Z_A Z_B} \quad (\text{as seen on p. 587}) \tag{108}$$

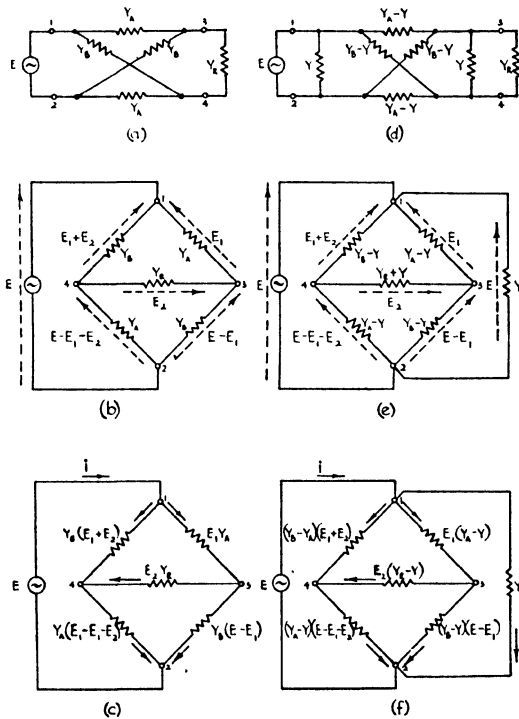


FIG. 607.—Development of lattice section with shunt impedances.

Also, from equation 107, putting $EY_0 = i$, one obtains :—

$$E(Y_A - Y_0) = E_2(Y_A + Y_0)$$

$$\gamma = \log_e \frac{E}{E_2}$$

$$= \log_e \frac{Y_A + Y_0}{Y_A - Y_0}$$

$$\begin{aligned} \gamma &= \log_e \frac{Z_A^{-1} + Z_0^{-1}}{Z_A^{-1} - Z_0^{-1}} \\ &= \log_e \frac{Z_0 + Z_A}{Z_0 - Z_A} \quad (\text{as seen on p. 587}) \quad (109) \end{aligned}$$

Modified lattice section (Fig. 607f) :—

Terminal 1.— $i = YE + (Y_B - Y)(E_1 + E_2) + (Y_A - Y)E_1$
i.e. $i = EY + E_1(Y_A + Y_B - 2Y) + E_2(Y_B - Y)$ (110)

Terminal 2.— $i = YE + (Y_A - Y)(E - E_1 - E_2)$
 $\quad \quad \quad + (Y_B - Y)(E - E_1)$
i.e. $i = E(Y_A + Y_B - Y) - E_1(Y_A + Y_B - 2Y)$
 $\quad \quad \quad - E_2(Y_A - Y)$ (111)

Terminal 3.— $0 = (Y_A - Y)E_1 - (Y_B + Y)E_2$
 $\quad \quad \quad - (Y_B - Y)(E - E_1)$
i.e. $0 = -E(Y_B - Y) + E_1(Y_A + Y_B - 2Y)$
 $\quad \quad \quad - E_2(Y_B + Y)$ (112)

From (110) and (112) :—

$$i = EY_B + E_2(Y_B + Y_B) \quad (113)$$

From (111) and (112) :—

$$i = EY_A - E_2(Y_A + Y_B) \quad (114)$$

Equations 113 and 114 are seen to be identical with equations 106 and 107 respectively, and they will therefore yield the same results for Z_0 and γ . The modified lattice section of Fig. 607d is therefore electrically equivalent to the original lattice section of Fig. 607a.

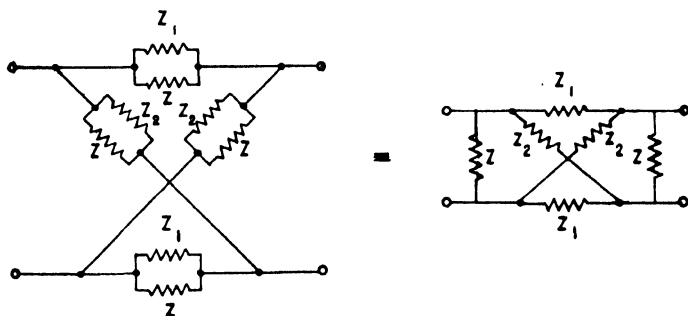


FIG. 608.—Lattice section, and equivalent developed section with shunt impedances.

In practice, this theorem is most useful when all four arms of a lattice section have a common shunt impedance. This is illustrated in Fig. 608, where $Z_A = Y_A^{-1}$ consists of Z_1 and Z in parallel, and $Z_B = Y_B^{-1}$ consists of Z_2 and Z in parallel.

Equivalence of a lattice to a π section

Theorem.—A lattice section can be interchanged, in any network, with a π section, and *vice versa*, provided that certain relations are maintained between the elements of the two sections.

This theorem follows from the previous theorem. No restriction was imposed on the value of the admittance Y that was subtracted from the series and lattice arms and placed across the input and output terminals; Y can therefore be made equal to Y_B .

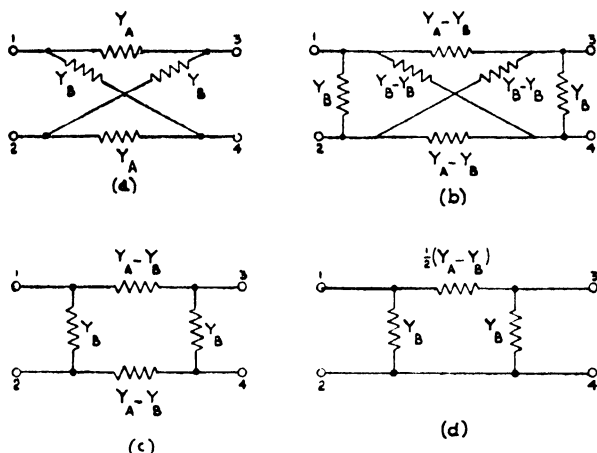


FIG. 609.—Equivalence of lattice and π sections.

When Y_B is subtracted from both series and lattice arms of the section shown in Fig. 609a, and placed in shunt with both the input and the output terminals, the admittance of each of the lattice arms is seen to be zero (Fig. 609b), and the resulting section can be redrawn as in Fig. 609c. This is a balanced π section, the unbalanced form of which is shown in Fig. 609d.

The characteristic impedance and propagation constant of the π section shown in Fig. 609d are given by:—

$$Y_{0\pi} = Z_{0\pi}^{-1} = \sqrt{\frac{1}{2}(Y_A - Y_B)2Y_B + \frac{1}{4}(2Y_B)^2}} = \sqrt{Y_A Y_B} \tag{115}$$

$$\therefore Z_{0\pi} = \frac{1}{\sqrt{Y_A Y_B}} = \sqrt{Z_A Z_B} \tag{116}$$

and
$$\gamma = \log_e \left\{ 1 + \frac{2Y_B}{Y_A - Y_B} + \frac{2Y_0}{Y_A - Y_B} \right\} = \log_e \frac{Y_A + 2Y_0 + Y_B}{Y_A - Y_B}$$

$$\gamma = \log_e \frac{\sqrt{Y_A} + \sqrt{Y_B}}{\sqrt{Y_A} - \sqrt{Y_B}} = \log_e \frac{Y_A + Y_0}{Y_A - Y_0} \quad (117)$$

$$= \log_e \frac{Z_A^{-1} + Z_0^{-1}}{Z_A^{-1} - Z_0^{-1}} = \log_e \frac{Z_0 + Z_A}{Z_0 - Z_A} \quad (118)$$

These results are identical with those obtained on page 587 for the original lattice section of Fig. 609a, and therefore the two sections are electrically equivalent.


CHAPTER 14

ATTENUATION AND ATTENUATORS

EXPRESSION OF ATTENUATION IN DECIBELS AND IN NEPERS

The *decibel* is fundamentally a unit of power ratio, but, as has been shown in Chapter 5, it can be used to express current ratios when the resistive components of the impedances through which the current flows are equal, and voltage ratios when the conductive components of these impedances are equal. The *neper* is fundamentally a unit of current ratio, but it can be used to express power ratios when the resistive components of the impedances are equal.

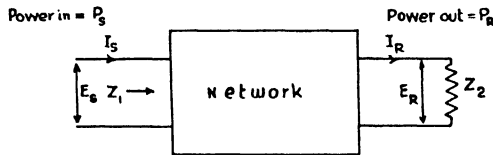The loss of power in a transmission line or electrical network is known as "attenuation". Attenuation may be measured using either the decibel or the neper notation.



$$Z_1 = R_1 + jX_1 = \frac{1}{G_1 + jB_1} \qquad Z_2 = R_2 + jX_2 = \frac{1}{G_2 + jB_2}$$

FIG. 610.—Attenuation measured using decibel and neper notations.

If the power entering a network is P_s and the power leaving it is P_R (see Fig. 610), then the attenuation in decibels is defined as:—

$$\text{Attenuation in decibels} = 10 \cdot \log_{10} \left| \frac{P_s}{P_R} \right| \qquad (1)$$

If the current entering a network is I_s and the current leaving it is I_R , then the attenuation in nepers is defined as:—

$$\text{Attenuation in nepers} = \log_e \left| \frac{I_s}{I_R} \right| \qquad (2)$$

Because of its derivation from the exponential e , the neper is the most convenient unit for expressing attenuation in theoretical work. The decibel, on the other hand, being defined in terms of logarithms to base 10, is a more convenient unit in practical calculations using the decimal system of reckoning. The conditions under which the two units may be used can be summarised in the

following equations, the notation of which is indicated in Fig. 610 :—

$$\text{Attenuation in db} = 10 \cdot \log_{10} \left| \frac{P_s}{P_r} \right| \quad (3)$$

$$= 20 \cdot \log_{10} \left| \frac{I_s}{I_r} \right| \quad (\text{provided that } R_1 = R_2) \quad (4)$$

$$= 20 \cdot \log_{10} \left| \frac{E_s}{E_r} \right| \quad (\text{provided that } G_1 = G_2) \quad (5)$$

$$\text{Attenuation in nepers} = \log_e \left| \frac{I_s}{I_r} \right| \quad (6)$$

$$= \log_e \left| \frac{E_s}{E_r} \right| \quad (\text{provided that } |Z_1| = |Z_2|) \quad (7)$$

$$= \frac{1}{2} \log_e \left| \frac{P_s}{P_r} \right| \quad (\text{provided that } R_1 = R_2) \quad (8)$$

If the resistive components of the impedances at the input and output of the network are equal, then the attenuation may be readily converted from one notation to the other, for :—

$$\begin{aligned} (\text{Attenuation in db}) &= 20 \cdot \log_{10} \left| \frac{I_s}{I_r} \right| \\ &= 20 \cdot \log_e \left| \frac{I_s}{I_r} \right| \times \log_{10} e \\ &= 8 \cdot 686 \cdot \log_e \left| \frac{I_s}{I_r} \right| \\ &= 8 \cdot 686 \times (\text{attenuation in nepers}) \end{aligned}$$

Thus :—

$$\text{Attenuation in db} = 8 \cdot 686 \times \text{attenuation in nepers} \quad (\text{provided that } R_1 = R_2) \quad (9)$$

$$\text{Attenuation in nepers} = 0 \cdot 1151 \times \text{attenuation in db} \quad (\text{provided that } R_1 = R_2) \quad (10)$$

ATTENUATING NETWORKS

In transmission equipment, it is frequently desired to attenuate the currents and voltages at certain stages. Attenuators and pads are networks designed to meet this requirement, and since, to prevent attenuation distortion, all frequencies must be attenuated to the same degree, the networks must consist of purely resistive components. No phase-shift will be introduced by such networks; thus, for each network, the phase constant (β) will be zero, and the propagation constant (γ) will simply be equal to the attenuation constant (α)*. A fixed attenuator is sometimes known as a "pad".

* Bearing these facts in mind, the designs and properties of attenuating networks may be deduced from the equations of Chapter 13. In this chapter, however, the results will, in many cases, be obtained in a simple manner from first principles for the benefit of the readers less familiar with the subject.

These networks, by choice of suitable resistances, may have any required value of attenuation. They may be designed to have any resistive value of characteristic impedance, if symmetrical, or of image impedances if asymmetrical. One of these networks may therefore be used in place of a transformer for matching between circuits of different resistive impedance, thus avoiding, particularly in carrier-frequency circuits, the attenuation distortion introduced by a transformer. The attenuation introduced will be of little consequence if valve amplification is included in the circuit.

There are three conditions that the attenuating network must fulfil. It must give :—

- (1) the correct input impedance ;
- (2) the correct output impedance ;
- (3) the specified attenuation.

This attenuation is usually quoted in decibels :—

$$\text{Attenuation in decibels} \quad D = 10 \log_{10} \frac{P_s}{P_r}$$

where P_s is power input and P_r power output.

In the following considerations the symbol N will be used for $\sqrt{\frac{P_s}{P_r}}$, *i.e.* :—

$$\text{Attenuation } D = 20 \log_{10} \sqrt{\frac{P_s}{P_r}} = 20 \log_{10} N \quad (11)$$

If both pairs of terminals of the network are matched to the same impedance, then :—

$$\frac{P_s}{P_r} = \frac{I_s^2}{I_r^2}$$

Therefore for a pad in a symmetrical circuit, $N = \frac{I_s}{I_r}$, but in an

asymmetrical circuit the value $N = \sqrt{\frac{P_s}{P_r}}$ must always be used.

Symmetrical T type

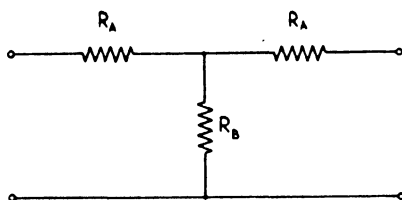


FIG. 611.—Symmetrical T network.

This is one of the most common types of pad, and consists of a divided series arm and one central shunt arm. The pad used between equal impedances will be symmetrical, *i.e.*, the series arm is divided into two equal parts (*see* Fig. 611). The values of the

series and shunt arms for a given value of impedance and attenuation will now be determined.

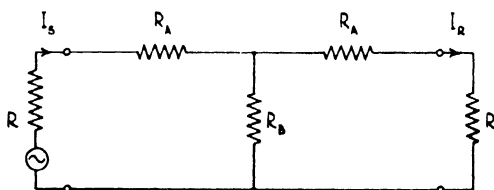


FIG. 612.—Symmetrical T network.

Consider the input current I_s (Fig. 612). At the shunt arm it divides in proportion to the conductances.

$$\text{Hence} \quad I_B = \frac{R_B}{R_B + R_A + R} \cdot I_s \quad (12)$$

$$\therefore N \equiv \frac{I_s}{I_B} = \frac{R_B + R_A + R}{R_B} \quad (13)$$

But the impedance looking into the attenuator is required to be R .

$$\begin{aligned} \text{Hence} \quad R &= R_A + \frac{R_B(R_A + R)}{R_B + R_A + R} \\ &= R_A + \frac{R_A + R}{N} \end{aligned}$$

$$\therefore R(N - 1) = R_A(N + 1)$$

$$\therefore R_A = R \left(\frac{N - 1}{N + 1} \right) \quad (14)$$

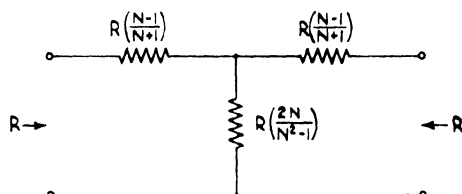


FIG. 613.—T network having input and output impedance equal to R .

$$\text{But} \quad N = \frac{R_B + R_A + R}{R_B}$$

$$\begin{aligned} \therefore R_B(N - 1) &= R_A + R \\ &= R \left(\frac{2N}{N + 1} \right) \end{aligned}$$

$$\therefore R_B = R \left(\frac{2N}{N^2 - 1} \right) \quad (15)$$

Using these formulae, therefore, an attenuator can be designed to give the specified attenuation, and to be properly matched to the circuit.

The resultant T section is shown in Fig. 613.

It may be noted that the results obtained also follow directly from Fig. 574 (Chapter 13, page 575), bearing in mind that in this case the characteristic impedance of the required T section is R and the propagation constant is α .

$$\text{i.e. } R_A = R \tanh \frac{\alpha}{2} = R \frac{e^{\frac{\alpha}{2}} - e^{-\frac{\alpha}{2}}}{e^{\frac{\alpha}{2}} + e^{-\frac{\alpha}{2}}} = R \frac{e^\alpha - 1}{e^\alpha + 1} = R \left(\frac{N - 1}{N + 1} \right)$$

$$\text{and } R_B = \frac{R}{\sinh \alpha} = \frac{2R}{e^\alpha - e^{-\alpha}} = \frac{2Re^\alpha}{e^{2\alpha} - 1} = R \left(\frac{2N}{N^2 - 1} \right)$$

$$\text{where } e^\alpha = \frac{I_s}{I_R} = N$$

Example.—Design a T type pad to give 25 db attenuation and to have a characteristic impedance of 600 ohms.

$$N = \text{antilog}_{10} \frac{D}{20} = \text{antilog}_{10} \frac{25}{20}$$

$$= 17.8$$

$$R_A = R \left(\frac{N - 1}{N + 1} \right)$$

$$= 600 \times \frac{16.8}{18.8}$$

$$= 536 \text{ ohms.}$$

$$R_B = 2R \left(\frac{N}{N^2 - 1} \right)$$

$$= 1200 \times \frac{17.8}{316}$$

$$= 67.6 \text{ ohms. } \textit{Ans.}$$

Asymmetrical T type

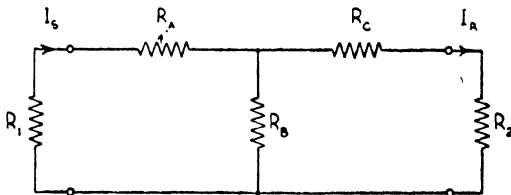


FIG. 614.—Asymmetrical T section.

Fig. 614 shows a pad that is not symmetrical.

Here
$$N = \sqrt{\frac{P_s}{P_r}} = \sqrt{\frac{I_s^2 R_1}{I_r^2 R_2}} \quad (16)$$

Using this and formulae for the input and output impedances, it can be shown that :—

$$R_A = R_1 \left(\frac{N^2 + 1}{N^2 - 1} \right) - 2\sqrt{R_1 R_2} \left(\frac{N}{N^2 - 1} \right) \quad (17)$$

$$R_B = 2\sqrt{R_1 R_2} \left(\frac{N}{N^2 - 1} \right) \quad (18)$$

$$R_C = R_2 \left(\frac{N^2 + 1}{N^2 - 1} \right) - 2\sqrt{R_1 R_2} \left(\frac{N}{N^2 - 1} \right) \quad (19)$$

A network consisting of these components will have image impedances R_1 and R_2 . If $R_1 > R_2$ then it will be found that $R_A > R_C$.

L type

If a pad is required for matching purposes only, then the design will be such as to give minimum attenuation. Examining the T section it will be seen that this condition will be reached when R_C has been reduced to zero.

This then forms the L type pad (see Fig. 615).

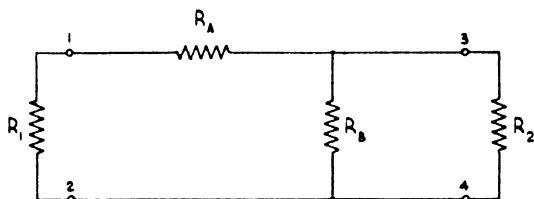


FIG. 615.—L type network.

To obtain values for R_A and R_B , consider input impedances. Looking in at terminals 1 and 2 :—

$$R_1 = R_A + \frac{R_2 R_B}{R_2 + R_B}$$

$$\therefore R_1 R_B + R_1 R_2 = R_A R_B + R_2 R_A + R_2 R_B \quad (20)$$

and looking in at terminals 3 and 4 :—

$$R_2 = \frac{R_B (R_1 + R_A)}{R_B + R_1 + R_A}$$

$$R_2 R_B + R_2 R_A + R_1 R_2 = R_B R_A + R_1 R_B \quad (21)$$

Adding equations 20 and 21 :—

$$2R_1 R_2 = 2R_A R_B$$

$$\text{or } R_A = \frac{R_1 R_2}{R_B}$$

Substituting in (20) :—

$$R_B = \sqrt{\frac{R_1 R_2^2}{R_1 - R_2}} \quad (22)$$

Hence $R_A = \sqrt{R_1(R_1 - R_2)}$ (23)

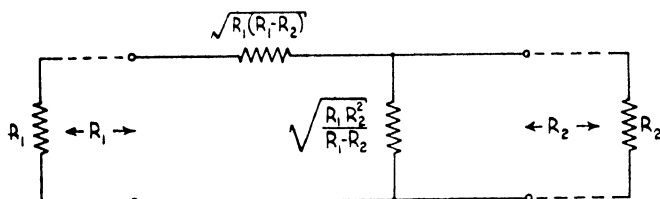


FIG. 616.—L network having image impedances R_1 and R_2 .

Fig. 616 shows the resultant L type network. It is a network having image impedances R_1 and R_2 .

π type

This attenuator is another common type, consisting of one series arm and two shunt arms. When used purely as an attenuator between equal impedances, symmetry demands that these two shunt arms shall be equal.

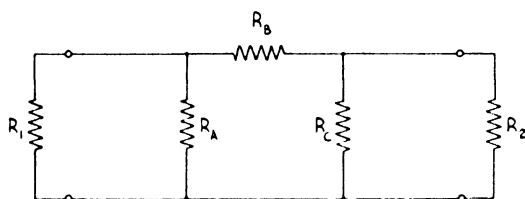


FIG. 617.— π network.

By calculation similar to that used for the T section it may be shown that :—

$$R_A = R_C = R \left(\frac{N+1}{N-1} \right) \quad (24)$$

$$R_B = R \left(\frac{N^2 - 1}{2N} \right) \quad (25)$$

In a pad used for matching, $R_A \neq R_C$, and the following formulae apply :—

$$R_A = R_1 \left(\frac{N^2 - 1}{N^2 - 2NS + 1} \right) \quad (26)$$

$$R_B = \frac{\sqrt{R_1 R_2} (N^2 - 1)}{2N} \quad (27)$$

$$R_o = R_2 \left(\frac{N^2 - 1}{N^2 - 2\frac{N}{S} + 1} \right) \quad (28)$$

where $S^2 = \frac{R_1}{R_2}$.

There is no difference in the performance of the T and π type pads and each one will suit any requirement, but one will probably be found to have more suitable or standard components than the other. It may be noted that a deviation of 5 per cent. from the calculated values of the resistances will mismatch the impedances by no more than the same amount, and vary the attenuation by as little as 0.5 db.

Balanced T, L and π types

When it is required to balance the two legs of the circuit, as is frequently the case in transmission equipment, then the preceding pads must be modified by dividing the series arm into two equal halves and inserting one half in each leg (see Fig. 618).

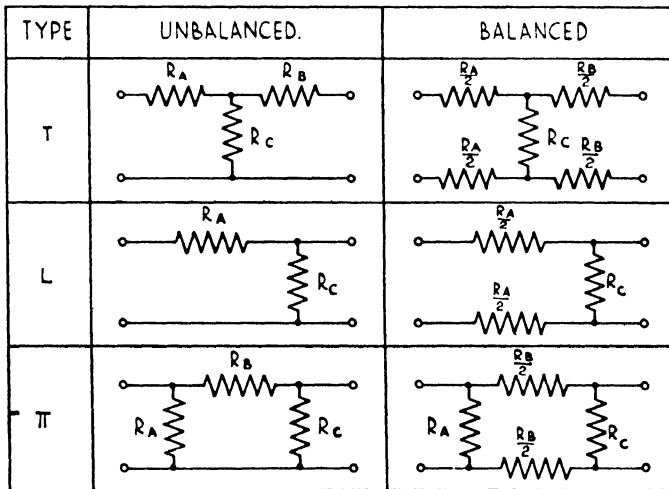


FIG. 618.—Balanced and unbalanced T, L and π networks.

When designing these balanced pads the components of the unbalanced type should be calculated using the formulae already quoted, and the series arm divided between the two legs. The characteristics of this derived pad—that is, the impedance and the attenuation—will be identical to those of the unbalanced pad.

Bridged-T type

Fig. 619 shows a symmetrical bridged-T type section used between equal impedances.

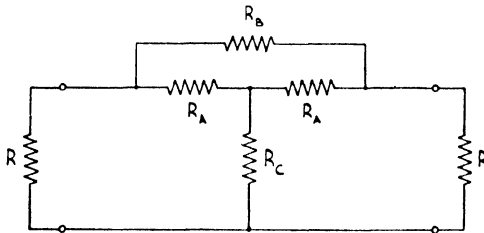


FIG. 619.—Symmetrical bridged-T network.

The network may be designed to have a constant impedance R , but any desired attenuation, by making:—

$$R_B R_C = R_A^2 = R^2$$

Thus, to vary the attenuation, without changing the design impedance, only two resistances have to be varied, *viz.*, R_B and R_C . It should be noted that, in the case of a symmetrical T or π section attenuator, three resistances have to be varied to change the attenuation without altering the impedance.

The design formulae for the bridged-T section are:—

$$R_A = R \quad (29)$$

$$R_B = R(N - 1) \quad (30)$$

$$R_C = \frac{R_A^2}{R_B} = \frac{R}{N - 1} \quad (31)$$

Example.—

Design a bridged-T attenuator having an attenuation of 40 db when working between two 600 ohms impedances.

To give 40 db attenuation, $N = 100$.

$$R_A = 600 \text{ ohms. } Ans.$$

$$R_B = 600(100 - 1) \\ = 59,400 \text{ ohms. } Ans.$$

$$R_C = \frac{600}{(100 - 1)} \\ = 6.06 \text{ ohms. } Ans.$$

The network is shown in Fig. 620.

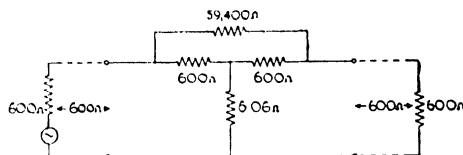


FIG. 620.—Bridged-T network having an attenuation of 40 db.

Lattice type

This type, shown in Fig. 621, is occasionally used.

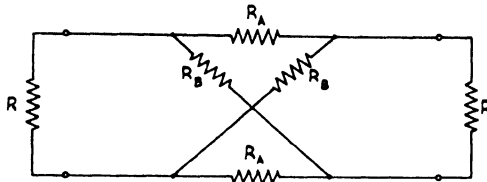


FIG. 621.—Lattice network.

The characteristic impedance R of the network can best be determined by consideration of its open-circuit and short-circuit impedances.

$$R_{oo} = \frac{R_A + R_B}{2} \quad (32)$$

$$R_{so} = 2 \frac{R_A R_B}{R_A + R_B} \quad (33)$$

$$\therefore R = \sqrt{R_{oo} R_{so}} = \sqrt{R_A R_B} \quad (34)$$

This gives the condition for matching the network to its adjacent circuit. It can, of course, be used only in a symmetrical case.

It may be shown that:—

$$N = \frac{I_o}{I_i} = \frac{R_A + R_B + 2R}{R_B - R_A}$$

But, from equation 34, $R_B = \frac{R^2}{R_A}$

$$\therefore N = \frac{R_A^2 + R^2 + 2R R_A}{R^2 - R_A^2} = \frac{R + R_A}{R - R_A} \quad (35)$$

Hence

$$R_A = R \left(\frac{N - 1}{N + 1} \right) \quad (36)$$

$$R_B = R \left(\frac{N + 1}{N - 1} \right) \quad (37)$$

DESIGN OF ATTENUATORS AND PADS

The steps in the design of any pad may be summarised as follows:—

- (1) Determine the type of pad to be used. In some cases alternative networks will be possible, and that one should be chosen which gives the most convenient component values.

- (2) Change the required decibel attenuation D to ratio N by use of Table XVII or the graph in Fig. 622.
- (3) If a T or π network is to be used for matching between unequal impedances R_1 and R_2 , verify that the value of attenuation chosen is greater than the minimum permissible attenuation given by Fig. 623, otherwise one arm of the network will work out to be negative. With the L type pad this is unnecessary.
- (4) With the information so obtained and a knowledge of the design impedance, evaluate the component values by use of the equations already stated above, noting that when it is necessary to insert a loss of more than 40 db, it is usually more convenient to use two smaller pads in series.

TABLE XVII

$$N \text{ Values } \left(N = \sqrt{\frac{P_S}{P_R}} \right)$$

D (db)	N	D (db)	N	D (db)	N	D (db)	N
1.0	1.122	18.0	7.943	35.0	56.234	52.0	398.11
2.0	1.259	19.0	8.912	36.0	63.096	53.0	446.68
3.0	1.412	20.0	10.000	37.0	70.795	54.0	501.19
4.0	1.585	21.0	11.220	38.0	79.433	55.0	562.34
5.0	1.778	22.0	12.590	39.0	89.125	56.0	630.96
6.0	1.995	23.0	14.125	40.0	100.000	57.0	707.95
7.0	2.239	24.0	15.849	41.0	112.20	58.0	794.33
8.0	2.512	25.0	17.783	42.0	125.89	59.0	891.25
9.0	2.818	26.0	19.953	43.0	141.25	60.0	1000.0
10.0	3.162	27.0	22.387	44.0	158.49	65.0	1778.3
11.0	3.548	28.0	25.119	45.0	177.83	70.0	3162.3
12.0	3.981	29.0	28.184	46.0	199.53	75.0	5623.4
13.0	4.467	30.0	31.623	47.0	223.87	80.0	10000.0
14.0	5.012	31.0	35.481	48.0	251.19	85.0	17783
15.0	5.623	32.0	39.811	49.0	281.84	90.0	31623
16.0	6.310	33.0	44.668	50.0	316.23	95.0	56234
17.0	7.079	34.0	50.119	51.0	354.81	100.0	10 ⁵

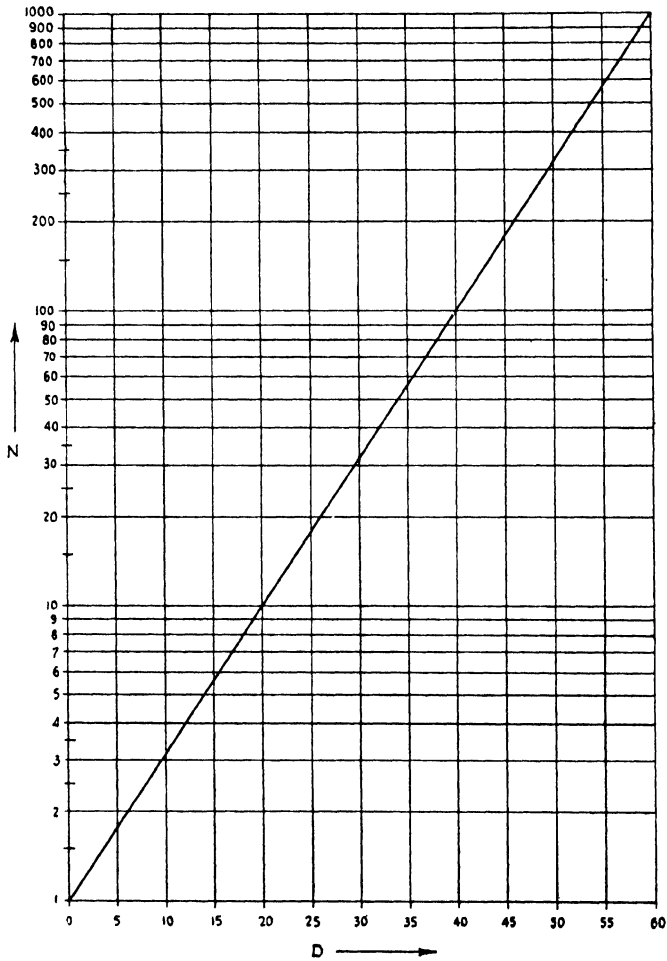


FIG. 622.—Graph for converting given decibel loss D to ratio N .

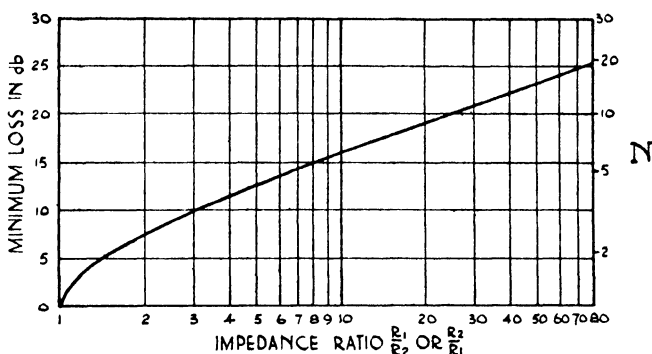


FIG. 623.—Minimum loss in T or π networks for given ratios of input and output impedances.

Example.—

Design an attenuating network to match between 400 and 800 ohms, and to give an attenuation of 15 db.

Following the steps indicated, the pad used would be either a T or π type. From Fig. 623, $\frac{R_2}{R_1} = 2$ allows a minimum of 7 db attenuation. From the table on p. 615, for 15 db attenuation $N = 5.623$.

(a) T type (see page 609) :—

$$R_A = R_1 \left(\frac{N^2 + 1}{N^2 - 1} \right) - 2\sqrt{R_1 R_2} \left(\frac{N}{N^2 - 1} \right)$$

$$= 218 \text{ ohms. Ans.}$$

$$R_B = 2\sqrt{R_1 R_2} \left(\frac{N}{N^2 - 1} \right)$$

$$= 208 \text{ ohms. Ans.}$$

$$R_C = R_2 \left(\frac{N^2 + 1}{N^2 - 1} \right) - 2\sqrt{R_1 R_2} \left(\frac{N}{N^2 - 1} \right)$$

$$= 644 \text{ ohms. Ans.}$$

The complete T section is illustrated in Fig. 624b.

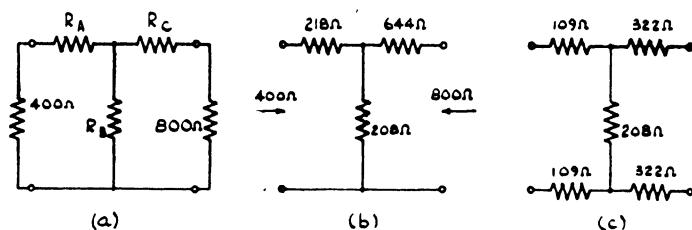


FIG. 624.—T network having input impedance of 400 Ω and output impedance of 800 Ω .

The values are quite suitable from a practical viewpoint, and the pad could now be constructed, dividing R_A and R_C between the two arms, as in Fig. 624c, if a balanced pad is required.

(b) π type (see page 611) :—

$$R_A = R_1 \left(\frac{N^2 - 1}{N^2 - 2NS + 1} \right) \\ = 497 \text{ ohms. } \textit{Ans.}$$

$$R_B = \frac{\sqrt{R_1 R_2} (N^2 - 1)}{2} \left(\frac{N^2 - 1}{N} \right) \\ = 1540 \text{ ohms. } \textit{Ans.}$$

$$R_C = R_2 \left(\frac{N^2 - 1}{N^2 - 2\frac{N}{S} + 1} \right) \\ = 1463 \text{ ohms. } \textit{Ans.}$$

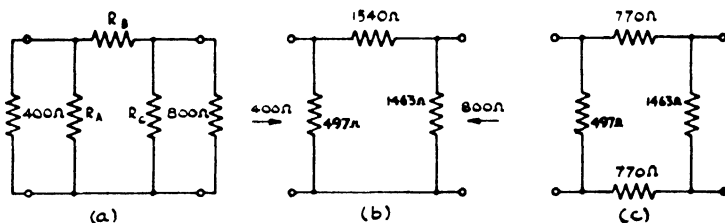


FIG. 625.— π network having input impedance of 400Ω and output impedance of 800Ω .

The complete π section is shown in Fig. 625b. Fig. 625c shows the corresponding balanced form. It will be noted that there is a considerable difference in the resistance values for the T and π types, and the more convenient may be used.




Components for attenuators in 600 ohm circuits

As 600 ohms is the characteristic impedance of most line communication circuits, the majority of attenuators and pads will come under this heading. Figs. 626 and 627 give graphs showing component values for T and π networks respectively for use in such circuits. Table XVIII gives the component values for T, π and bridged-T networks.

If the characteristic impedance is not 600 ohms, but R , the values for the components must all be multiplied by $\frac{R}{600}$.

TABLE XVIII

Pads designed for 600 ohms characteristic impedance.

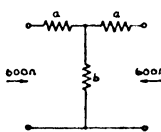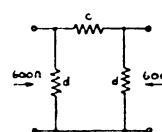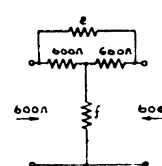Loss D in db	T pad		π pad		Bridged-T pad	
						
	a	b	c	d	e	f
1	34.50	5201	69.2	10,436	73.2	4918
2	68.79	2583	139.4	5233	155	2317
3	102.5	1703	211.1	3512	247	1456
4	135.8	1258	286.2	2651	351	1025
5	168.0	987.1	365.0	2142	467	771
6	199.4	803.4	448.1	1806	597	603
7	229.4	670.0	537.3	1569	743	485
8	258.3	567.5	634.1	1394	907	397
9	285.7	487.1	738.9	1260	1091	330
10	311.7	421.9	853.1	1155	1297	278
11	336.3	367.2	980.3	1071	1530	235
12	359.1	321.7	1119	1003	1789	201
13	380.5	282.7	1273	946.1	2080	173
14	400.4	249.3	1444	899.1	2407	149
15	418.8	220.1	1633	859.5	2773	130
20	490.9	121.2	2970	733.3	5400	66.7
25	536.1	67.61	5324	671.4	10,070	35.8
30	563.2	37.99	9486	639.0	18,370	19.6
35	579.0	21.35	16,864	621.6	33,140	10.9
40	589.1	12.00	30,000	612.1	59,400	6.06
45	593.3	6.748	53,350	606.8	106,100	3.40
50	596.2	3.795	94,860	603.8	189,100	1.90

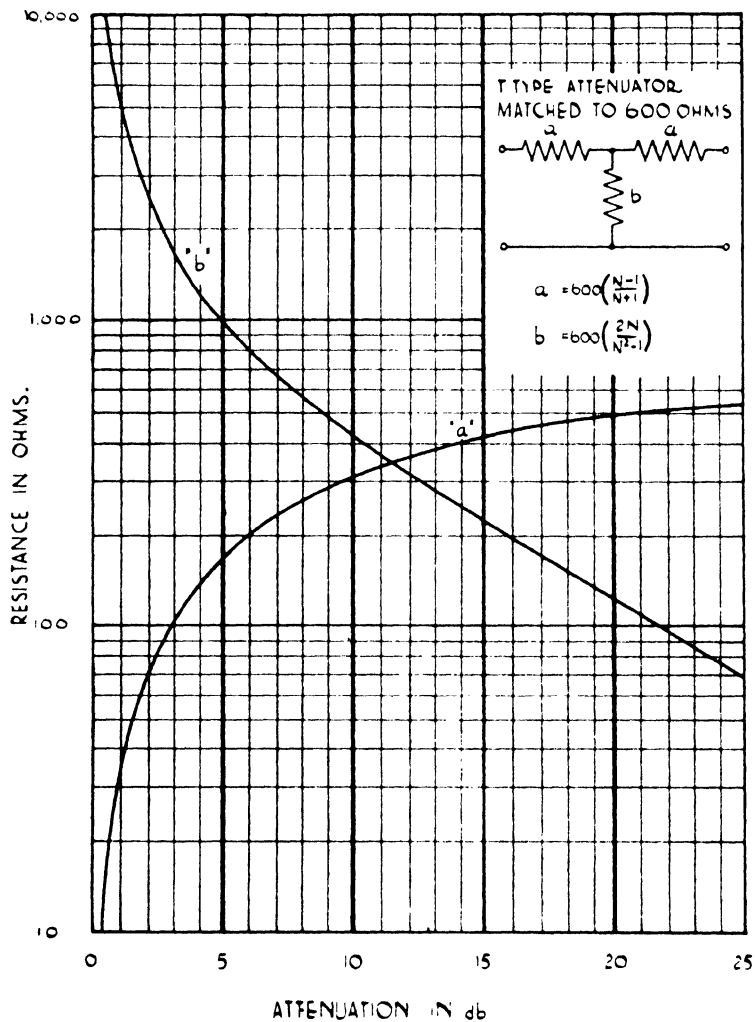


FIG. 626.—Graph giving component values for T network (characteristic impedance 600Ω).

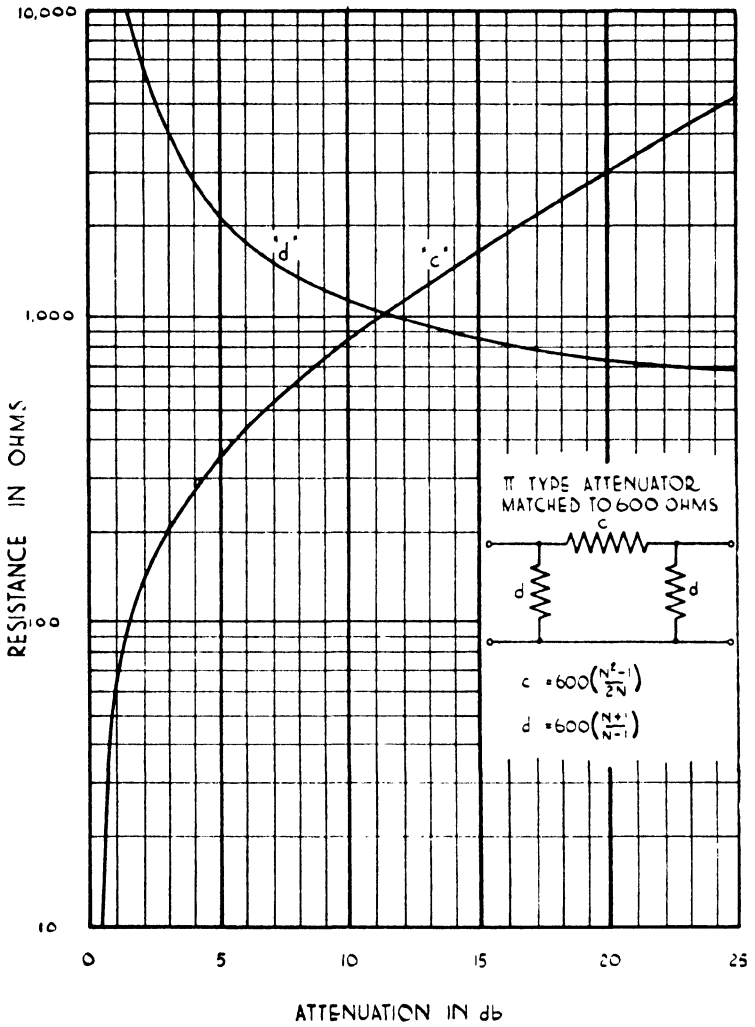


FIG. 627.—Graph giving component values for π network (characteristic impedance 600 Ω).

VARIABLE ATTENUATORS

Variable attenuators are so designed as to have a constant input and output impedance, but a variable attenuation. They may be divided into several classes depending on the method of achieving the result.

The elementary type has the simple construction of a T or π section and the resistors are variable. All are ganged together so that at different positions the pad impedance is unaltered although the attenuation is varied (see Fig. 628a and b).

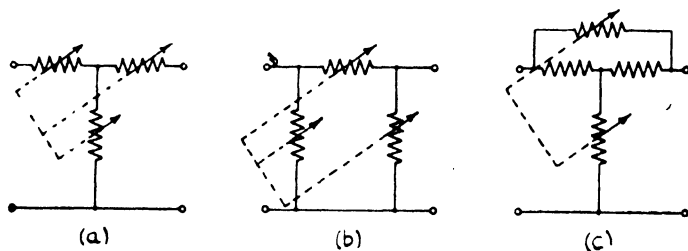


FIG. 628.—Variable attenuator.

The bridged-T type (see Fig. 628c) has already been discussed. This has the advantage compared with those mentioned above that only two resistors have to be varied, as compared with three when T or π sections are used.

A further type, simple in construction and design, consists of a number of pads, of equal impedance but different attenuation, connected in series. Each pad may be switched in or out as required.

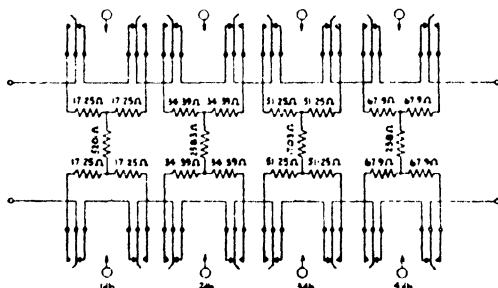


FIG. 629.—Non-reactive adjustable attenuator (characteristic impedance 600Ω).

Fig. 629 shows such an attenuator.

Each pad is of the balanced T type and may be brought into circuit by operation of the appropriate key. The resistances are

shown in ohms, and the characteristic impedance of each pad is 600 ohms.

Fig. 630 shows how the principle may be extended so that, with appropriate switching, only three pads, namely 5, 10 and 20 db, need be employed to form a variable attenuator covering the range from 0 to 30 db in 5 db steps.

S1 Posn.	Att. db.
1	0
2	5
3	10
4	15
5	20
6	25
7	30

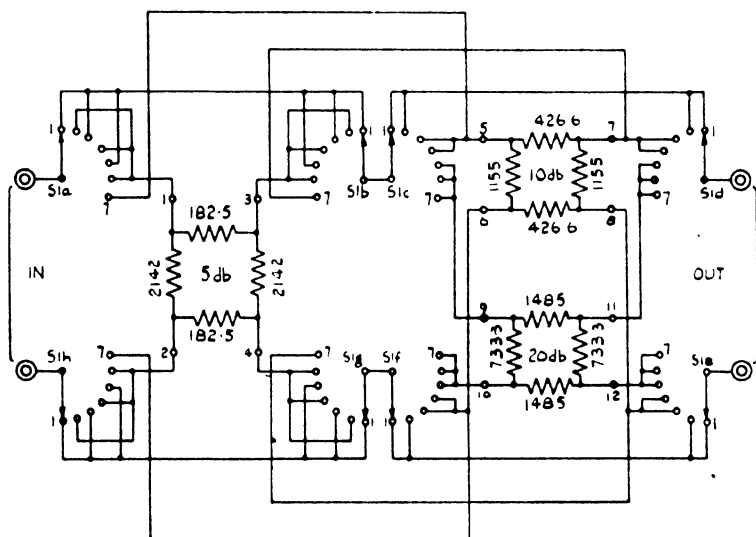


FIG. 630.—Non-reactive adjustable attenuator : Range 0-30 db.

TRANSMISSION MEASUREMENTS

It has been seen (Chap. 5) that the power level in a circuit may be expressed using the decibel notation provided that a reference power is stated; in line communication this reference power is taken as 1mW. A decibel-meter, which is the name given to an instrument measuring power levels when the decibel notation is used, should be a specially calibrated wattmeter. However, it is found impossible in practice to design a wattmeter that is sufficiently accurate at all frequencies over the required range. On the other hand if all measurements are taken at points having the same standard impedance, the voltage will give a direct

indication of the power and a suitable voltmeter may be recalibrated to read the power level directly in decibels. This is the basis of all transmission measurements.

The standard impedance usually chosen is a pure resistance of 600 ohms. All testing apparatus is therefore designed to work into this 600 ohms impedance. All points at which tests have to be made must be designed to have this impedance or else a correction factor will have to be applied.

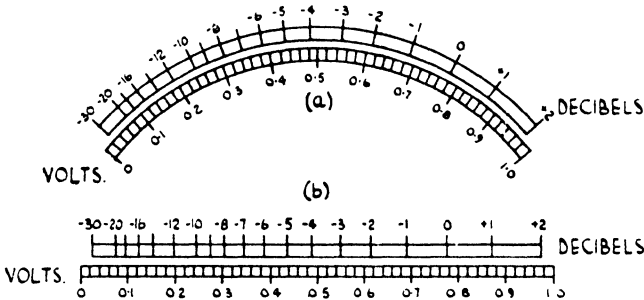


Fig. 631.—Calibration of voltmeter to read power levels above and below 1mW in 600Ω.

Since the reference power is 1mW, and this is applied to a 600 ohms resistance, the reference voltage level will be :—

$$\sqrt{0.001 \times 600} = 0.775 \text{ volts.}$$

This corresponds to a current in 600 ohms of 1.29mA.

If E is a voltage reading, the corresponding power level in decibels, reference 1mW and 600Ω, will be given by :—

$$\text{Power level} = 20 \log_{10} \frac{E}{0.775}$$

Fig. 631 shows the corresponding voltage and dbm readings.

Measurement of power levels

The reading of power level at a point in a circuit may be obtained in two ways :—

(a) "Level" or "Through" measurement.

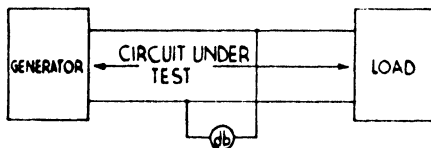


Fig. 632.—Decibelmeter giving "Level" or "Through" measurements.

A "level" measurement is obtained by tapping a high-impedance voltmeter across the circuit, as in Fig. 632. The high impedance of the meter is essential to ensure that its presence will not disturb the circuit under test (e.g., a 5000 ohm meter will introduce a shunt loss of about 0.5 db). If the impedance of the circuit under test is 600 ohms, the voltmeter, calibrated to read power level directly in decibels, will give a true reading. Any variation in circuit impedance from 600 ohms will, of course, destroy the accuracy of the measurement, but, provided that the impedance is known, a correction factor may be applied.

Let the voltage be E and let the circuit impedance be 400 ohms instead of 600 ohms.

$$\begin{aligned} \text{Power indicated on scale} &= \frac{E^2}{600} \\ \text{Actual power} &= \frac{E^2}{400} \\ \text{Error} &= 10 \log_{10} \frac{400}{600} \\ &= -1.76 \text{ db} \end{aligned}$$

i.e., the meter will read 1.76 db low.

(b) "Transmission", "Terminating" or "Loss" measurement.

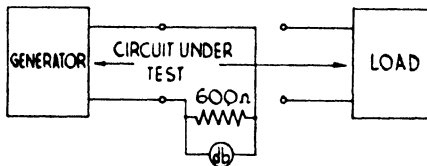


FIG. 633.—Decibelmeter giving "Transmission" measurement.

A "transmission" (TRANS) measurement is made by terminating the circuit in a 600 ohm resistance, and measuring the voltage across it using the meter, Fig. 633.

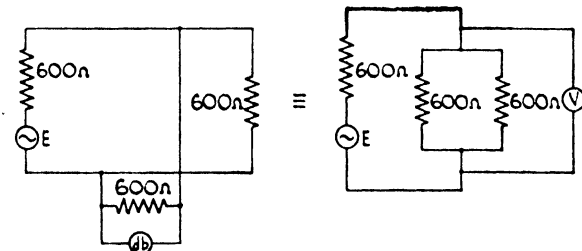


FIG. 634.—"Level" measurement with meter set at "TRANS".

Many decibel-meters give both facilities, a high impedance meter being used, the 600 ohms resistance for TRANS measurements being brought into circuit by operation of a switch. Failure to cut-out the 600 ohms when making a LEVEL measurement will give a reading that is 3.52 db too low. (See Fig. 634.)

Whereas voltage reading should be $\frac{E}{2}$, it will be $\frac{E}{3}$;

$$\begin{aligned}\therefore \text{discrepancy of reading} &= 20 \log_{10} \frac{2}{3} \\ &= -3.52 \text{ db.}\end{aligned}$$

Decibel-meters

Especially when making LEVEL measurements it is essential that the decibel-meter used shall take only the minimum possible power from the circuit under test. Since such a meter is expected to give a reading when the power in the circuit under test is of the order of, say, 0.1mW, it follows that an extremely sensitive meter movement must be used, unless some form of valve amplification is to be employed. Such a sensitive meter has the disadvantage that its movement may be easily damaged by accidental overloading. Decibel-meters may be divided into two classes according to whether or not they utilise valve amplification.

Metal rectifier type decibel-meter.—This type of decibel-meter is frequently used owing to its simplicity. In most cases a moving coil meter movement is used. The incoming signal is rectified by metal rectifiers in the form of a full-wave rectifier bridge circuit, and the rectified current is passed through the meter.


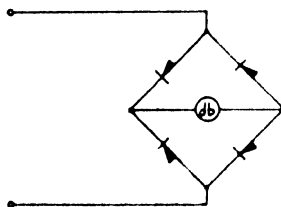


FIG. 635.—Arrangement of rectifiers in db meter.

In order to spread out the scale at the lower part of the range, specially shaped pole-pieces may be employed in the meter, as shown in Fig. 636.

Fig. 637 shows a decibel-meter suitable for use over the audio range (say up to about 5000 c/s). The frequency range is limited in this case by the input transformer. The meter will give TRANS or LEVEL readings, and the scale is calibrated reference 1mW in 600Ω to read from -15 to 0 dbm. To enable higher power

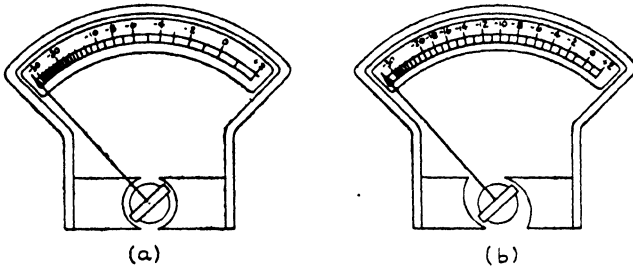

(a) Uncorrected.

(b) Corrected.

FIG. 636.—Illustrating the effect of shaped pole-pieces in db meter.

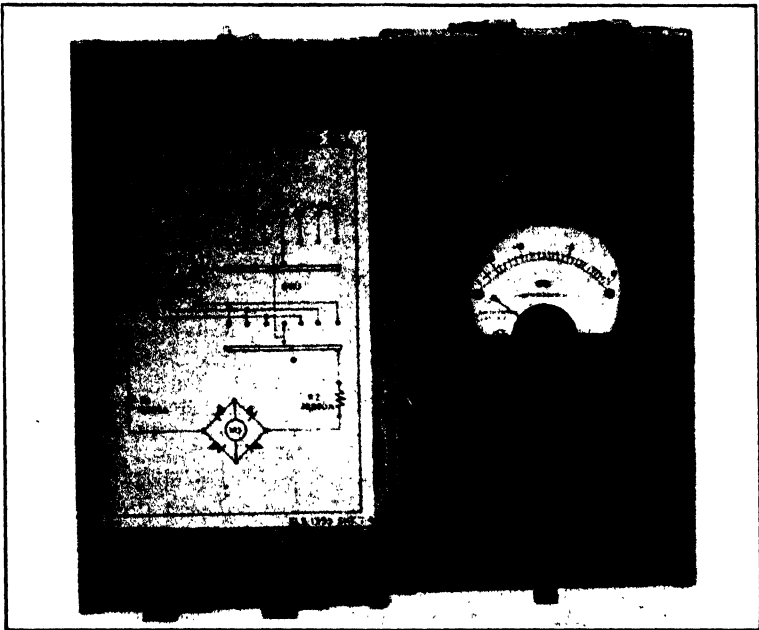


PLATE 31.—Metal-rectifier type decibel-meter (TMS No. 2).

levels to be measured, tappings are provided on the input transformer introducing attenuations of 10 or 20 db into the input circuit to the meter, thus providing two new ranges — 5 to + 10 dbm and + 5 to + 20 dbm.

The accuracy of such a meter depends on the frequency error of the rectifiers used, but by using rectifiers having an extremely small self-capacity, and omitting the input transformer it is possible to construct instruments having negligible frequency errors up to 50 kc/s.

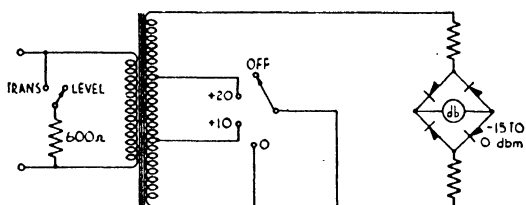


FIG. 637.— Decibel-meter for use over audio range.

The meter movement, rectifier network, and associated shunt and series resistors, may be arranged so as to present a 600 ohm impedance at the terminals, in which case the meter may be used only for TRANS measurements. Alternatively, the circuit may be arranged so as to offer a very high shunt impedance across the circuit under test, allowing LEVEL measurement to be made.

Valve type decibel-meters.—The valve type decibel-meter has two advantages over the type just discussed. Firstly, it enables much lower powers to be measured (down to — 40 dbm or lower); and secondly, the circuit may be designed so that the meter movement is not damaged by applying too large a signal at the input.

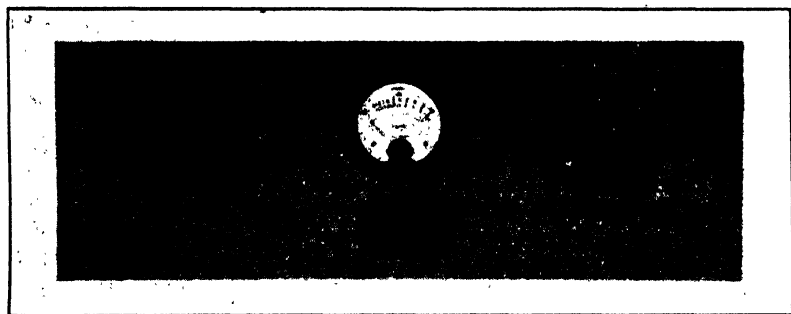


PLATE 32.—Valve type decibel-meter.

DECIBELMETERS

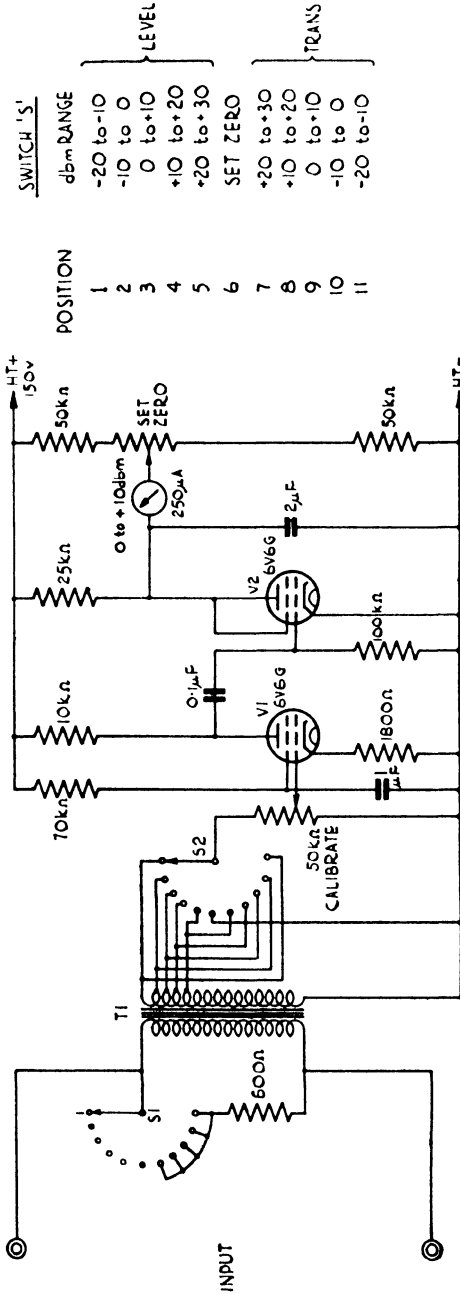


Fig. 638.—Valve type decibel-meter.

SWITCH 'S1'	db-m RANGE	LEVEL	TRANS
1	-20 to +10		
2	-10 to 0		
3	0 to +10		
4	+10 to +20		
5	+20 to +30		
6	SET ZERO		
7	+20 to +30		
8	+10 to +20		
9	0 to +10		
10	-10 to 0		
11	-20 to -10		

This type of decibel-meter usually consists of an amplifier followed by a detector stage that rectifies the amplified signal. The DC component of this rectified waveform is applied to a meter giving a deflection that may be made independent of the frequency of the incoming signal. The meter is calibrated directly in dbm. Damage to the meter from overloading is prevented by arranging that at least one stage of the amplifier acts as a limiter if too large an input signal is applied.

The input circuit may be arranged so that either LEVEL or TRANS measurements may be made. The range of the meter may be varied by adjusting the gain of the amplifier in fixed steps. Fig. 638 shows a decibel-meter of this type reading power levels from -20 to $+30$ dbm in 5 ranges.

Measurement of losses and gains

There are two main methods of measuring the loss or gain of a network. The first is to apply a tone at the required frequency, and to determine the ratio of "power in" to "power out", which,

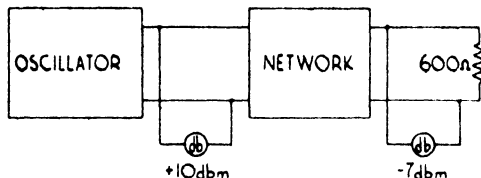


FIG. 639.—Measurement of the loss of a network by direct readings.

using the decibel notation, will be the difference in the dbm readings at the input and the output. Thus in Fig. 639, if the input power is $+10$ dbm and the output power -7 dbm, the loss, or attenuation of the network, will be 17 db.

The second method is the method of substitution. This requires a calibrated variable attenuator. To measure a network having a loss, the tone is applied first through the network, and then

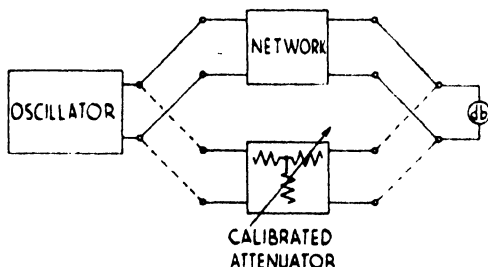


FIG. 640.—Measurement of the loss of a network by the method of substitution.

through the variable attenuator (Fig. 640). The attenuator is adjusted until the same power output level is obtained in the two cases, for constant input power. The known loss of the calibrated attenuator is then equal to the loss of the network.

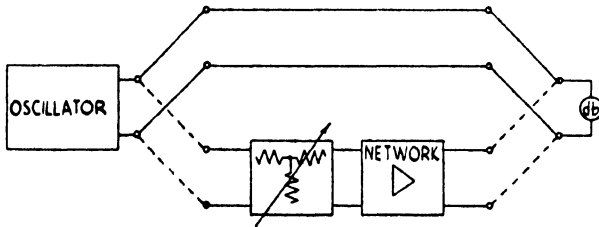


FIG. 641.—Measurement of the gain of a network.

To measure a gain, such as may occur if the network contains an amplifier, the method must be modified, since it is unlikely that a calibrated amplifier will be available. The calibrated variable attenuator may be utilised to determine the gain as follows :—

The oscillator is first applied directly to the meter and the reading noted. The calibrated attenuator and the network are then inserted between the oscillator and the meter. The attenuator is adjusted until the same meter reading is obtained. When this is the case, the loss of the attenuator must equal the gain of the amplifier, which is therefore determined. The attenuator should be placed in the input to the amplifier, or the amplifier may be overloaded.

The advantage of this latter method over the former is that the results obtained are independent of the accuracy of the decibelmeter—in fact, an uncalibrated meter can be used, provided some method is employed to ensure that the same deflection is obtained in the two cases.

Transmission measuring sets

A transmission measuring set (TMS) is the name given to the apparatus used for measuring gains and losses. Provided that some source of test tone may be found, a simple decibel-meter may be used as a TMS by applying the first of the above methods.

In general, a TMS includes :—

- (i) an oscillator ;
- (ii) a means of calibrating the output of this oscillator ;
- (iii) a means of measuring the incoming signal

Practical transmission measuring sets are usually designed on a 600 ohm basis, and this fact must be remembered when making measurements in circuits with an impedance different from this value.

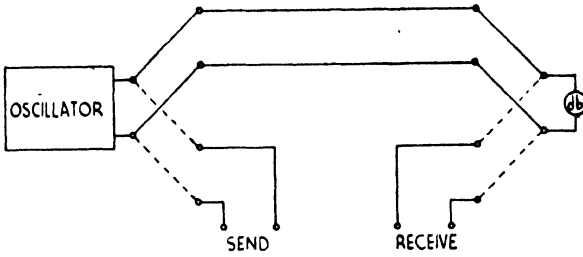


FIG. 642.—Schematic arrangement of a TMS.

Fig. 642 shows the schematic arrangement of such a TMS. To calibrate the oscillator output, the output is fed directly into the decibelmeter, and is adjusted to the required level. The output from the TMS is then applied to the circuit under test via the SEND terminal. The output from the circuit is re-applied to the TMS via the RECEIVE terminals, and the power level indicated on the meter. The difference between this latter reading and the oscillator output gives the loss or gain of the circuit under test. If the receive circuit has an input impedance of 600 ohms, only TRANS measurements may be made. Most TMSs, however, employ the principle previously discussed, *i.e.*, a high impedance voltmeter with a 600 ohms resistance in shunt if desired, thus enabling either TRANS or LEVEL measurements to be made.

The output of the oscillator may be varied over a wide range by incorporating an attenuator before the send terminals. A range of output from + 20 dbm down to - 50 dbm will enable most gains and losses to be measured.

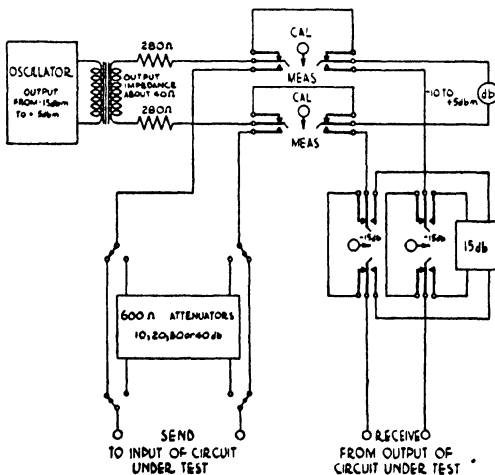


FIG. 643.—Transmission measuring set (" TRANS " measurements only).

Similar modification may be made to the receive circuit. A rectifier type meter may read directly from -10 to $+5$ dbm, but by incorporating a 15 db pad which may be inserted in the input before the meter, the upper limit of the readable level will be increased to $+20$ dbm.

Fig. 643 shows a transmission measuring set having the oscillator output at the send terminals variable from $+5$ dbm down to -55 dbm, and capable of making TRANS measurements from $+20$ dbm down to -10 dbm.

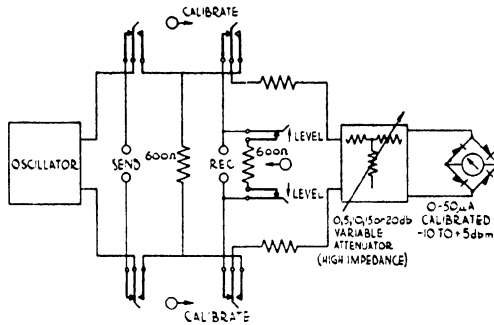


FIG. 644.—Transmission measuring set ("TRANS" and "LEVEL" measurements).

Fig. 644 shows a transmission measuring set capable of making TRANS and LEVEL measurements on the receive side.

To measure the attenuation of a long transmission line, two TMSs are required, one to supply the standard level at the sending end, and the other to measure the power received at the distant end.

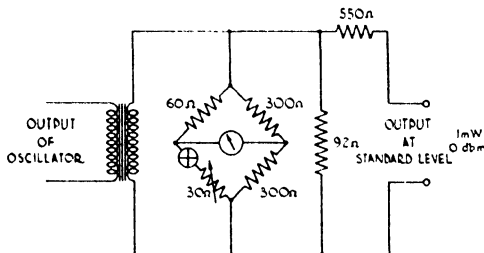


FIG. 645.—Lamp bridge used for calibrating a TMS.

A "lamp bridge" provides a convenient method of calibrating a TMS, since it has a negligible frequency error. For example, it may be used as in Fig. 645 to ensure that the output from the

oscillator is exactly 1mW, even though the only meter available has a large frequency error. The only disadvantage of the lamp bridge circuit is that it is difficult to make its impedance 600 ohms, and a matching pad must be inserted between the bridge and the output terminals.

The resistance of the lamp increases with the current through it. The 30 ohm variable resistance is adjusted so that the bridge is balanced when the voltage applied across the bridge from the transformer has an RMS value of 1.49 volts. This voltage applied to the subsequent network and 600 ohms load ensures an output of 1mW. Therefore once the correct bridge setting has been obtained, the only requirement to ensure the output of 1mW is that the bridge shall be balanced, *i.e.* nul deflection of the meter. Since any frequency error of the meter will not affect the balance point of the bridge, exactly 1mW output will be obtained irrespective of the frequency.

CHAPTER 15

FILTERS

A network that is designed to attenuate certain frequencies but pass others without loss is called a "filter". A filter therefore possesses at least one "pass band" (a band of frequencies in which the attenuation is zero) and at least one "attenuation band" (a band of frequencies in which the attenuation is finite). The frequencies that separate the various pass and attenuation bands are called "cut-off" frequencies, and are usually denoted by f_1 , f_2 , etc., or by f_0 if there is only a single cut-off frequency.

An important characteristic of all filters is that they are constructed from purely *reactive* elements, for otherwise the attenuation could never become zero. It is interesting to compare a filter, in which the attenuation changes *suddenly* from zero to some other value, with an attenuator pad (pure resistances only) of *constant* attenuation (independent of frequency), and with an equaliser (resistances and reactances) whose attenuation undergoes a *gradual* variation with frequency.

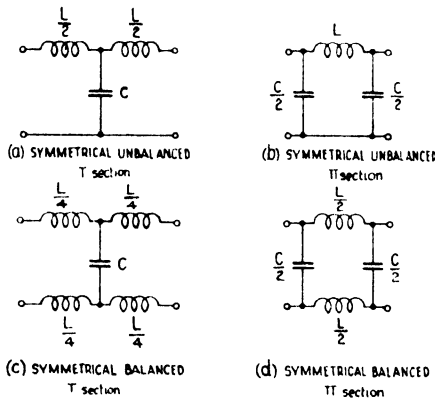


FIG. 646.—Symmetrical low-pass T and π sections in unbalanced and balanced forms.

The filters considered in this chapter will in general be symmetrical unbalanced T or π sections, as shown in Fig. 646*a* and *b* respectively, for the case of a low-pass filter.

Symmetrical balanced sections, as shown in Fig. 646*c* and *d*, will not be considered separately, since they may be deduced from the unbalanced sections, just as was done in the case of balanced attenuators.

Elementary filter sections

The simplest type of filter has only one pass band, one attenuation band, and a single cut-off frequency. If it passes all frequencies up to the cut-off frequency and attenuates all frequencies above, it is called a "low-pass" filter. If, on the other hand, it attenuates all frequencies below the cut-off frequency and passes all frequencies above, it is called a "high-pass" filter.

An "ideal" filter would have zero attenuation in the pass band and infinite attenuation in the attenuation band: an ideal low-pass filter, for example, might have an attenuation-frequency curve as shown in Fig. 647.

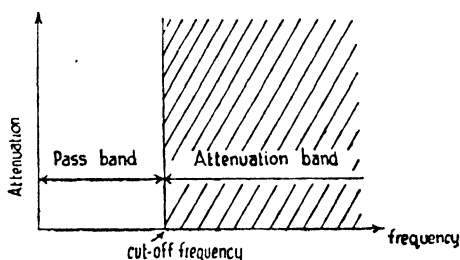


FIG. 647.—Attenuation-frequency curve of an ideal low-pass filter.

This cannot be achieved in practice. In the first place, in a practical filter it is found that the attenuation outside the pass band is finite; it can, however, be made as large as required by using a sufficient number of sections in series. Secondly, if any resistance is present (and it is impossible to construct an inductance that does not possess a certain amount of resistance), the attenuation in the pass band will not be zero; usually, however, it is only one or two decibels. Finally, mismatch losses must be considered; for although the characteristic impedance of the section may vary with frequency, it will probably be terminated in a fixed resistance, or in an impedance that does not vary with frequency in the same way as the characteristic impedance of the section.

The complete study of the behaviour of any filter requires the calculation of its propagation constant (γ), attenuation (α), phase-shift (β) and characteristic impedance (Z_0) at any frequency; this involves a somewhat advanced mathematical treatment. It is possible, however, to find the pass and attenuation bands from an elementary consideration of the variation of Z_0 with frequency, and this method will be considered first.

Theorem connecting α and Z_0

It will be assumed that the filter is correctly terminated in its characteristic impedance; the following theorem then applies:—

Over the range of frequencies for which the characteristic impedance Z_0 of a filter is purely resistive (real), the attenuation α is zero. Over the range of frequencies for which Z_0 is purely

reactive, the attenuation is greater than zero. The case where Z_0 is partly resistive and partly reactive cannot arise in purely reactive networks.

The validity of this theorem can be demonstrated from elementary considerations. If Z_0 is real, the filter and its termination will absorb power from any generator connected to it; as the filter is composed entirely of reactances it cannot itself absorb power, since in a reactance the current and voltage are always 90° out of phase. Hence all the power delivered by the generator must be passed through to the load and therefore there is no attenuation, i.e. $\alpha = 0$.

If, on the other hand, Z_0 is purely reactive, the filter and its termination cannot absorb any power, and no power is therefore passed to the load.

The last part of the above proof is rather unsatisfactory, and a more rigorous proof is therefore given below, using the normal formulae for a T or π section.

As any section may be represented by a simple T section, it is sufficient to consider just the T section shown in Fig. 648.

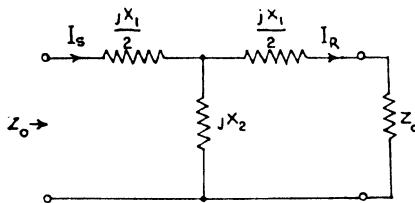


FIG. 648.—T section composed of pure reactive elements.

As the elements are all reactive, they may be written in the form jX , where X is real, but may be positive or negative.

The formulae for the characteristic impedance and propagation constant of a T section are :—

$$Z_0 = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2} \quad \text{(Equation 10 of Chap. 13)} \quad (1)$$

$$\text{and } e^\gamma = \frac{I_s}{I_R} = 1 + \frac{Z_1}{2Z_2} + \frac{Z_0}{Z_2} \quad \text{(Equation 16 of Chap. 13)} \quad (2)$$

and α can be calculated from the relationship :—

$$\alpha = 20 \log_{10} \left| \frac{I_s}{I_R} \right| \text{ db} \quad (3)$$

In this case $Z_1 = jX_1$ and $Z_2 = jX_2$, and equations 1 and 2 become :—

$$Z_0 = j \sqrt{\frac{X_1^2}{4} + X_1 X_2} \quad (4)$$

$$\text{and } \frac{I_s}{I_R} = 1 + \frac{X_1}{2X_2} - j \frac{Z_0}{X_2} \quad (5)$$

There are two cases to consider, depending on the value and sign of X_1 and X_2 . The two cases are:—

$$(a) \quad \frac{X_1^2}{4} + X_1X_2 \text{ is negative, } = -A, \text{ say,}$$

$$\text{and } (b) \quad \frac{X_1^2}{4} + X_1X_2 \text{ is positive, } = +B, \text{ say,}$$

where A and B are real and positive.

Consider first case (a). In this case, from equation 4, Z_0 is real (that is, purely resistive), and its value is:—

$$Z_0 = j \sqrt{\frac{X_1^2}{4} + X_1X_2} = j\sqrt{-A} = +\sqrt{A}$$

From equation 5:—

$$\frac{I_s}{I_R} = \left[1 + \frac{X_1}{2X_2} \right] - j \left[\frac{Z_0}{X_2} \right] = \left[1 + \frac{X_1}{2X_2} \right] - j \left[\frac{\sqrt{A}}{X_2} \right]$$

$$\begin{aligned} \therefore \left| \frac{I_s}{I_R} \right| &= \sqrt{\left(1 + \frac{X_1}{2X_2} \right)^2 + \frac{A}{X_2^2}} \\ &= \sqrt{1 + \frac{X_1}{X_2} + \frac{X_1^2}{4X_2^2} - \frac{X_1^2}{4X_2^2} - \frac{X_1}{X_2}} \\ &= 1 \end{aligned}$$

$$\text{But } \alpha = 20 \log_{10} \left| \frac{I_s}{I_R} \right|$$

Hence $\alpha = 0$ if Z_0 is real.

In case (b), Z_0 is imaginary (that is, purely reactive), and its value, from equation 4, is:—

$$Z_0 = j \sqrt{\frac{X_1^2}{4} + X_1X_2} = j \sqrt{+B}$$

In this case, from equation 5:—

$$\frac{I_s}{I_R} = \left[1 + \frac{X_1}{2X_2} \right] - j \left[\frac{Z_0}{X_2} \right] = \left[1 + \frac{X_1}{2X_2} \right] - j \left[\frac{j\sqrt{B}}{X_2} \right]$$

$$\therefore \left| \frac{I_s}{I_R} \right| = 1 + \frac{X_1}{2X_2} + \frac{\sqrt{\frac{X_1^2}{4} + X_1X_2}}{X_2}$$

which is real and cannot be unity.

Therefore $\alpha \neq 0$ if Z_0 is imaginary.

Determination of cut-off frequency

The theorem just given is of fundamental importance, since it can be applied to determine the cut-off frequency f_0 of any filter, from a consideration of Z_0 . For Z_0 is real in a pass band and imaginary in an attenuation band; hence f_0 is the frequency at which Z_0 changes from being real to being imaginary.

This point can easily be found, for a T section, by using the formula :—

$$Z_0 = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}$$

If all the elements are pure reactances, let $Z_1 = jX_1$ and $Z_2 = jX_2$, so that :—

$$Z_0 = \sqrt{\frac{-X_1^2}{4} - X_1 X_2} = \sqrt{-X_1 \left(\frac{X_1}{4} + X_2 \right)} \quad (6)$$

Hence if X_1 and $\frac{X_1}{4} + X_2$ have the same sign, Z_0 will be the square root of a negative quantity, *i.e.*, purely imaginary, and the filter will attenuate. If, however, X_1 and $\frac{X_1}{4} + X_2$ have opposite signs, Z_0 will be real and the attenuation zero.

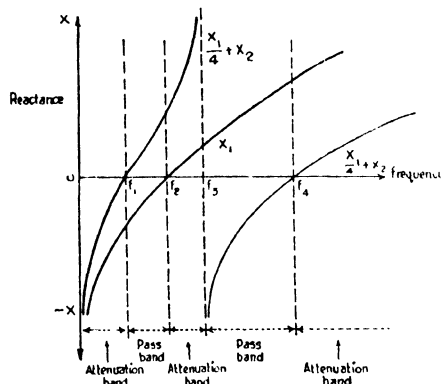


FIG. 649.—Reactance-frequency sketch for a double band-pass filter.

The easiest method is to draw *reactance sketches* for X_1 and $\frac{X_1}{4} + X_2$ against frequency. The rule is :—*Frequencies for which the curves are on opposite sides of the frequency axis are in the pass band; frequencies for which the curves are on the same side of the frequency axis are in the attenuation band; the change-over points give the cut-off frequencies.* For example, the filter whose reactance sketches are shown in Fig. 649 has two pass bands and three attenuation bands. An alternative method is to write down Z_0 in terms of frequency and calculate algebraically where it is resistive and where it is reactive.

Constant- k sections

Before applying these methods, the following definition is required :—

A "constant- k " section is a T or π section in which the

series and shunt impedances, Z_1 and Z_2 , are connected by the relationship $Z_1 Z_2 = R_0^2$, where R_0 is a real constant—that is, a resistance that is independent of frequency. R_0 is known as the “design impedance” of the section.

Consider the equation :—

$$Z_{0T} = \frac{Z_1 Z_2}{Z_{0\pi}} \quad (7)$$

which connects the characteristic impedances of T and π sections composed of the same series and shunt impedances (see Fig. 650). This formula is proved in Chapter 13, on page 578.

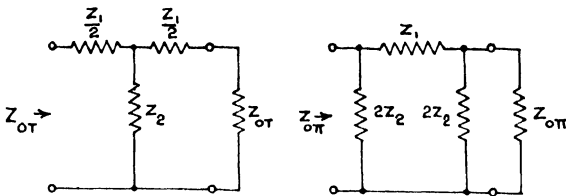


FIG. 650.—T and π sections composed of the same series and shunt impedances.

If the section is a constant- k section :—

$$Z_{0\pi} = \frac{R_0^2}{Z_{0T}} \quad (8)$$

and clearly $Z_{0\pi}$ and Z_{0T} will be real or imaginary together; and when Z_{0T} changes from real to imaginary, so also will $Z_{0\pi}$. Hence the two sections will have the same pass bands and the same cut-off frequencies.

The constant- k T or π sections of any type of filter are known as the *prototypes*; other more complex sections may be derived from the prototype, and these will be dealt with later. At the moment, the low-pass and high-pass prototype sections will be considered.

PROTOTYPE FILTER SECTIONS

Low-pass filters

The prototype T and π low-pass filter sections are shown in Fig. 651.

Here $Z_1 = j\omega L$

and $Z_2 = \frac{-j}{\omega C}$

Hence $Z_1 Z_2 = \frac{L}{C}$, and the sections are therefore constant- k sections with :—

$$R_0 = \sqrt{\frac{L}{C}} \quad (9)$$

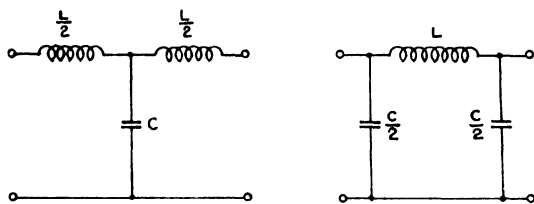


FIG. 651.—Prototype T and π low-pass filter sections.

As both sections have the same cut-off frequency, it is sufficient to calculate this for the T section only. The reactance sketches must first be drawn :—

$$Z_1 = j\omega L \quad \therefore X_1 = \omega L$$

$$Z_2 = \frac{-j}{\omega C} \quad \therefore X_2 = \frac{-1}{\omega C}$$

$$\therefore \frac{X_1}{4} + X_2 = \frac{\omega L}{4} - \frac{1}{\omega C} \tag{10}$$

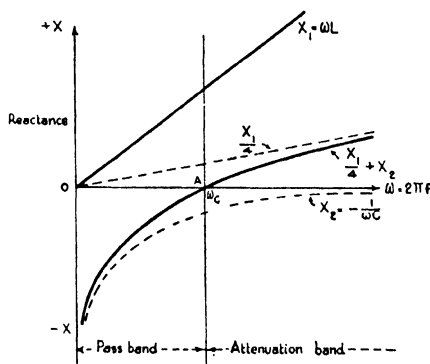


FIG. 652.—Reactance-frequency sketch for a prototype low-pass filter.

The curves are as shown in Fig. 652. It is worth noting here that all reactance-frequency curves slope upwards and to the right; that is, they have positive slope.

It will be seen that the curves are on opposite sides of the frequency axis as far as the point *A*, and on the same side from *A* onwards. Hence the pass band includes all frequencies up to the point *A*, and the attenuation band all frequencies above the point *A*. The point *A* itself marks the cut-off frequency given by $\omega = \omega_c$. The section is therefore a low-pass filter with a cut-off frequency

$$f_c = \frac{\omega_c}{2\pi}$$

ω_o is the point where the curve $\frac{X_1}{4} + X_2$ crosses the frequency axis; that is, where $\frac{\omega L}{4} - \frac{1}{\omega C} = 0$ or $\omega^2 = \frac{4}{LC}$.

$$\text{Hence } \omega_o = \frac{2}{\sqrt{LC}} \text{ or } f_o = \frac{1}{\pi\sqrt{LC}} \quad (11)$$

which gives the cut-off frequency of a low-pass T or π section.

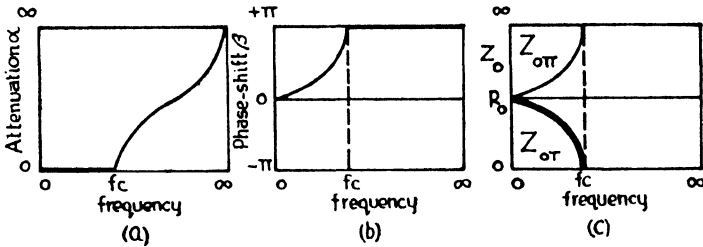


FIG. 653.—Prototype low-pass filter sections—Variation with frequency of

(a) Attenuation. (b) Phase-shift. (c) Characteristic impedance.

Fig. 653 shows the way in which α , β and Z_0 vary with frequency for a prototype low-pass section; Z_0 is not shown above the cut-off frequency as it becomes reactive in the attenuation band. It should be noted that Z_0 varies considerably from the design impedance R_0 over the pass band.

The algebraic approach to the same problem is as follows:—

$$\begin{aligned} Z_{or} &= \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2} \\ &= \sqrt{\frac{-\omega^2 L^2}{4} + \frac{L}{C}} \\ &= \sqrt{\frac{L}{C}} \times \sqrt{1 - \frac{\omega^2 LC}{4}} \\ \text{i.e. } Z_{or} &= R_0 \sqrt{1 - \frac{\omega^2 LC}{4}} \quad (12) \end{aligned}$$

Clearly Z_{or} is real if $\frac{\omega^2 LC}{4} < 1$ and imaginary if $\frac{\omega^2 LC}{4} > 1$; hence the section passes frequencies below $\omega = \frac{2}{\sqrt{LC}}$ and attenuates frequencies above this value. It is therefore a low-pass filter with a cut-off frequency given by $\omega_o = \frac{2}{\sqrt{LC}}$ or $f_o = \frac{1}{\pi\sqrt{LC}}$; this agrees with equation 11, found by the reactance sketch method.

Note that equation 12 may be written as :—

$$Z_{0T} = R_0 \sqrt{1 - \frac{\omega^2}{\omega_0^2}} \quad (13)$$

Since $Z_{0\pi} = \frac{R_0^2}{Z_{0T}}$ (from equation 8), it follows that :

$$Z_{0\pi} = \frac{R_0}{\sqrt{1 - \frac{\omega^2}{\omega_0^2}}} \quad (14)$$

From these two expressions the curves of Fig. 653c are derived.

Example.—

Consider a simple T section low-pass filter having a design impedance R_0 . Find $Z_{0\pi}$ at $f = 0.9f_0$.

$$\frac{\omega}{\omega_0} = \frac{f}{f_0} = 0.9$$

$$\therefore Z_{0\pi} = \frac{R_0}{\sqrt{1 - (0.9)^2}} = 2.3 R_0$$

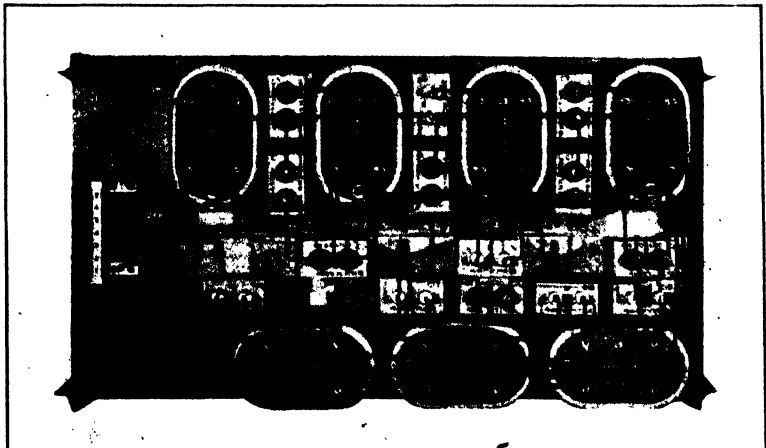


PLATE 33.—Low-pass filter on a multi-channel carrier telephone system.

More advanced mathematical treatment of the low-pass filter

In order to determine the phase-shift inside the pass band and the attenuation outside the pass band, it is convenient to introduce hyperbolic functions. It has been seen (equation 20, p. 573) that for a T section :—

$$\cosh \gamma = 1 + \frac{Z_1}{2Z_2}$$

where γ is the propagation constant of the section. Applying this to the case of the low-pass filter gives :—

$$\cosh \gamma = 1 - \frac{\omega^2 LC}{2} \quad (15)$$

Since $\gamma = \alpha + j\beta$, it follows that :—

$$\cosh \alpha \cos \beta + i \sinh \alpha \sin \beta = 1 - \frac{\omega^2 LC}{2}$$

Equating real and imaginary parts :—

$$\cosh \alpha \cos \beta = 1 - \frac{\omega^2 LC}{2} \quad (16)$$

$$\text{and} \quad \sinh \alpha \sin \beta = 0 \quad (17)$$

Equation 17 is satisfied by :—

$$\text{either } \alpha = 0 \quad \text{or} \quad \beta = n\pi$$

Pass band

If $\alpha = 0$, equation 16 gives :—

$$\cos \beta = 1 - \frac{\omega^2 LC}{2} \quad (18)$$

This corresponds to the pass band of the filter. The attenuation is zero and the phase-shift is given by equation 18. Since $\cos \beta$ must lie between +1 and -1, equation 18 can be satisfied for all frequencies from zero up to the cut-off frequency f_o , where :—

$$1 - \frac{\omega_o^2 LC}{2} = -1$$

$$\text{i.e.} \quad \frac{\omega_o^2 LC}{2} = 2$$

$$\text{i.e.} \quad \omega_o = \frac{2}{\sqrt{LC}} \quad (19)$$

$$\text{i.e.} \quad f_o = \frac{1}{\pi\sqrt{LC}} \quad (20)$$

which verifies the result already obtained.

From equation 19, equation 18 becomes :—

$$\cos \beta = 1 - 2 \frac{\omega^2}{\omega_o^2} \quad (21)$$

$$\text{Hence} \quad \beta = \cos^{-1} \left(1 - 2 \frac{\omega^2}{\omega_o^2} \right) \text{ radians.} \quad (22)$$

Alternatively to equation 21 :—

$$1 - 2 \sin^2 \frac{\beta}{2} = 1 - 2 \frac{\omega^2}{\omega_o^2}$$

Whence $\beta = 2 \sin^{-1} \frac{\omega}{\omega_o}$ radians. (23)

Attenuation Band

If $\beta = n\pi$, then $\cos \beta = \pm 1$, and equation 16 gives :—

$$\pm \cosh \alpha = 1 - \frac{\omega^2 LC}{2}$$

From equation 19 this becomes :—

$$\pm \cosh \alpha = 1 - 2 \frac{\omega^2}{\omega_o^2} \quad (24)$$

The attenuation band of the low-pass filter is given by :—

$$\beta = \pi$$

and $\cosh \alpha = 2 \frac{\omega^2}{\omega_o^2} - 1$

In the attenuation band :—

$$\alpha = \cosh^{-1} \left(\frac{2\omega^2}{\omega_o^2} - 1 \right) \text{ nepers} \quad (25)$$

or $\alpha = 2 \cosh^{-1} \frac{\omega}{\omega_o}$ nepers (26)

These results give the curves of Fig. 653a and b.

Example.—

At what frequency will a T section low-pass filter, having a cut-off frequency f_o , have an attenuation of 10 db ?

$$10 \text{ db} \equiv 1.15 \text{ neper}$$

Let $\omega = 2\pi f$, where f is the required frequency.

Then $2 \cosh^{-1} \frac{\omega}{\omega_o} = 1.15$

$$\therefore \frac{f}{f_o} = \frac{\omega}{\omega_o} = \cosh 0.575 = 1.17 \text{ (see p. 796)}$$

$$\therefore f = 1.17 f_o$$

Design of a prototype low-pass filter section

Let the design impedance R_o and the cut-off frequency f_o be given. There are two equations giving these in terms of L and C , namely :—

$$R_o = \sqrt{\frac{L}{C}} \quad (\text{from equation 9})$$

and $f_o = \frac{1}{\pi\sqrt{LC}}$ (from equation 11)

$$\text{Whence } L = \frac{R_0}{\pi f_c} \quad (27)$$

$$\text{and } C = \frac{1}{\pi R_0 f_c} \quad (28)$$

From these equations, the components of the required section can be determined.

Example.—

Suppose a prototype low-pass filter section is required, having $R_0 = 600 \Omega$ and $f_c = 1000$ c/s. Substituting the known values of R_0 and f_c in equations 27 and 28,

$$L = \frac{R_0}{\pi f_c} = \frac{600}{1000\pi} = 191.0 \text{ mH},$$

$$\text{and } C = \frac{10^6}{\pi \cdot 1000 \cdot 600} \mu\text{F} = 0.5304 \mu\text{F}$$

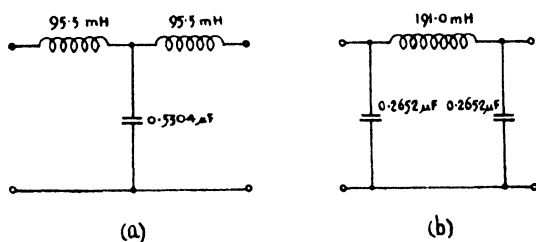


FIG. 654.

Hence the prototype T section is as shown in Fig. 654a and the π section as shown in Fig. 654b. Each has a cut-off frequency of 1000 c/s and a design impedance 600Ω ; the difference between the two is in the way in which the characteristic impedance varies with frequency.

High-pass filters

Fig. 655 shows the prototype high-pass T and π sections.

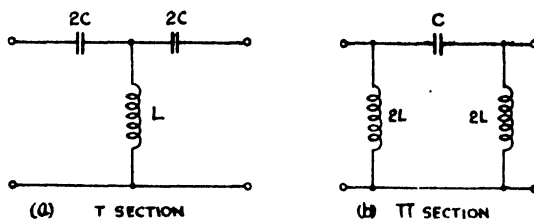


FIG. 655.—Prototype high-pass filter sections.

$Z_1 = \frac{-j}{\omega C}$, and $Z_2 = j\omega L$. Thus $Z_1 Z_2 = \frac{L}{C}$, and the sections are constant- k sections with :—

$$R_0 = \sqrt{\frac{L}{C}} \quad (29)$$

The cut-off frequency may be determined by the reactance sketch method. In this case :—

$$X_1 = -\frac{1}{\omega C} \text{ and } X_2 = \omega L$$

$$\therefore \frac{X_1}{4} + X_2 = \omega L - \frac{1}{4\omega C} \quad (30)$$

The curves are as shown in Fig. 656.

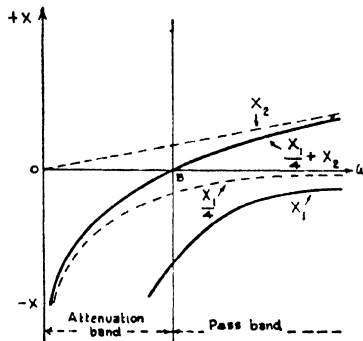


Fig. 656.—Reactance-frequency curves for a prototype high-pass filter.

Here the curves are on the same side of the horizontal axis up to the point B , giving an attenuation band. For frequencies above B , the curves are on opposite sides of the axis, giving a pass band. The point B therefore gives the cut-off frequency. This frequency is given by :—

$$\frac{X_1}{4} + X_2 = 0$$

$$\text{i.e. } \omega L - \frac{1}{4\omega C} = 0$$

$$\text{Hence } \omega_0 = \frac{1}{2\sqrt{LC}} \text{ or } f_0 = \frac{1}{4\pi\sqrt{LC}} \quad (31)$$

which gives the cut-off frequency of a high-pass T or π section.

Fig. 657 shows the way in which α , β and Z_0 vary with frequency for a prototype high-pass section. Z_0 is not shown below the cut-off frequency, as it becomes reactive in the attenuation band.

The algebraic approach is as follows :—

$$Z_{or} = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2} = \sqrt{\frac{-1}{4\omega^2 C^2} + \frac{L}{C}} = \sqrt{\frac{L}{C}} \times \sqrt{1 - \frac{1}{4\omega^2 LC}}$$

$$Z_{or} = R_0 \sqrt{1 - \frac{1}{4\omega^2 LC}} \quad (32)$$

It follows that if $4\omega^2 LC > 1$, Z_{or} is real and the filter passes. If $4\omega^2 LC < 1$, Z_{or} is imaginary and the filter attenuates.

Hence the cut-off frequency is given by :—

$$4\omega^2 LC = 1$$

i.e.
$$\omega_c = \frac{1}{2\sqrt{LC}}$$

i.e.
$$f_c = \frac{1}{4\pi\sqrt{LC}} \quad (\text{which agrees with equation 31})$$

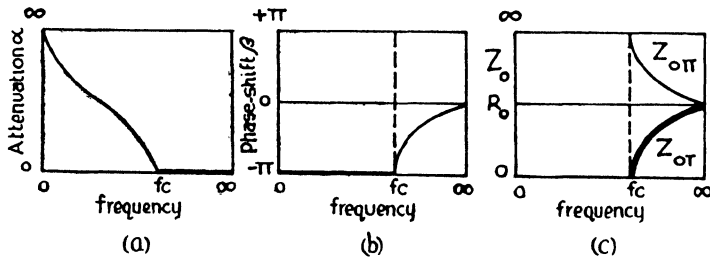


FIG. 657.—Prototype high-pass filter—Variation with frequency of

(a) Attenuation. (b) Phase-shift. (c) Characteristic impedance.

Note that Z_{or} may be written as :—

$$Z_{or} = R_0 \sqrt{1 - \frac{\omega_c^2}{\omega^2}} \quad (33)$$

and
$$Z_{o\pi} = \frac{R_0^2}{Z_{or}} = \frac{R_0}{\sqrt{1 - \frac{\omega_c^2}{\omega^2}}} \quad (34)$$

from which results the curves of Fig. 657c are obtained.

It can also be shown that, outside the pass band :—

$$\alpha = \cosh^{-1} \left(\frac{2\omega_c^2}{\omega^2} - 1 \right) = 2 \cosh^{-1} \frac{\omega_c}{\omega} \text{ nepers} \quad (35)$$

and within the pass band :—

$$\beta = \cos^{-1} \left(1 - \frac{2\omega_c^2}{\omega^2} \right) = -2 \sin^{-1} \frac{\omega_c}{\omega} \text{ radians} \quad (36)$$

These results give the curves of Fig. 657a and b.

It will be noted that the formulae 13, 14, 26 and 23 for a low-pass filter correspond exactly with the formulae 33, 34, 35 and 36 for a high-pass filter if $\frac{\omega_g}{\omega}$ is written for $\frac{\omega}{\omega_g}$.

Design of a prototype high-pass filter section

Let the design impedance R_0 and the cut-off frequency f_0 be given. There are two equations giving these in terms of L and C , namely :—

$$R_0 = \sqrt{\frac{L}{C}} \quad (\text{from equation 29})$$

and
$$f_0 = \frac{1}{4\pi\sqrt{LC}} \quad (\text{from equation 31})$$

Whence
$$L = \frac{R_0}{4\pi f_0} \quad (37)$$

and
$$C = \frac{1}{4\pi R_0 f_0} \quad (38)$$

From these equations, the component values of the required section can be determined.

Example.—

Calculate the components of a prototype high-pass filter section having a design impedance $R_0 = 600\Omega$ and a cut-off frequency $f_0 = 10$ kc/s.

Substituting the known values of R_0 and f_0 in equations 37 and 38 :—

$$L = \frac{600}{4\pi \times 10^4} = 4.774 \text{ mH}$$

and
$$C = \frac{10^6}{4\pi \cdot 600 \times 10^4} = 0.01326 \mu\text{F}$$

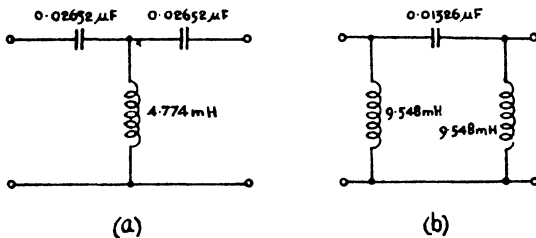


FIG. 658.

Hence the prototype T section is as shown in Fig. 658a and the π section as shown in Fig. 658b.

M-DERIVED FILTER SECTIONS

Behaviour of prototype sections

There are two obvious disadvantages of the prototype sections just discussed. In the first place, considering a low-pass section, the attenuation does not rise very rapidly after the cut-off frequency, being only 10 db at a frequency $f = 1.2f_0$; secondly, Z_0 is by no means constant over the pass band (e.g. $Z_{0\pi} = 2.3 R_0$ at $f = 0.9f_0$).

Consider first the attenuation band; the most obvious way to increase the attenuation beyond cut-off is by connecting two or more sections together. This can be done provided the impedances match correctly—e.g. a T and a π section cannot be connected together since $Z_{0T} \neq Z_{0\pi}$, but two or more T sections may be connected in series, as also may two or more π sections. Thus with two sections in series, although the attenuation over the pass band is, in theory, still zero, the attenuation over the attenuation band is doubled; so that, for example, with two low-pass filter sections, the attenuation at $f = 1.2f_0$ is 20 db, showing a much sharper cut-off than that obtained with a single section.

Unfortunately, due to resistance in the components, the attenuation in the pass band of a practical filter is not zero, but becomes quite appreciable towards cut-off. The result is that the

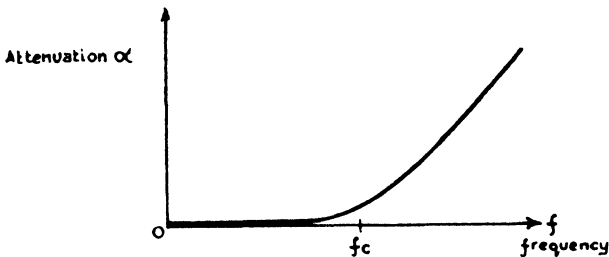


FIG. 659.—Attenuation-frequency characteristic of a typical prototype low-pass filter.

curve becomes rounded off at the cut-off frequency (see Fig. 659, which shows the attenuation-frequency characteristic of a typical low-pass filter).

What is really required is a section having the same cut-off frequency as the prototype section, but a different attenuation-frequency characteristic in the attenuation band; that is, a characteristic that rises more rapidly than that of the prototype. It will also be necessary for the new section to have the same Z_0 as the prototype at all frequencies, since otherwise the two sections cannot be connected together without mismatch. It might be thought impossible to satisfy both these requirements, but it will now be shown that it can be accomplished quite simply. Note that if the two sections have the same Z_0 , they must also have the same pass bands.

Derivation of *m*-derived sections

Consider first any T section, and construct a new section from it, having a series arm of the same type but of different value ; *i.e.* for convenience make the new Z_1 equal to mZ_1 , where m is some constant.

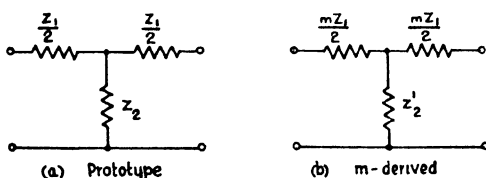


FIG. 660.—Derivation of *m*-derived T section.

The new shunt arm will be not Z_2 but Z'_2 , say, and it is necessary to find that value of Z'_2 (if any) which will make the two sections have the same value for Z_0 .

For the prototype section :—

$$Z_{0p} = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2} \tag{39}$$

For the new section :—

$$Z_{0n} = \sqrt{\frac{m^2 Z_1^2}{4} + m Z_1 Z'_2} \tag{40}$$

These two impedances will be the same if :—

$$\frac{Z_1^2}{4} + Z_1 Z_2 = \frac{m^2 Z_1^2}{4} + m Z_1 Z'_2$$

i.e. if
$$Z'_2 = \frac{Z_2}{m} + \frac{1 - m^2}{4m} Z_1 \tag{41}$$

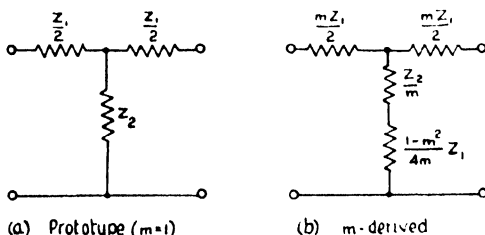


FIG. 661.—Comparison of prototype and *m*-derived T sections.

This means that Z'_2 must be an impedance $\frac{Z_2}{m}$ in series with an impedance $Z_1 \frac{(1 - m^2)}{4m}$, and both these impedances can be constructed if $0 < m < 1$. The complete “*m*-derived T section” is shown in Fig. 661*b*.

In a similar manner, a new section may be derived from a π section, having the same Z_0 at all frequencies. The complete m -derived π section is shown in Fig. 662b.

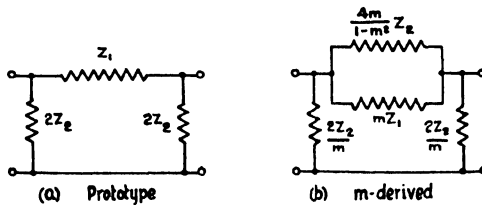


FIG. 662.—Comparison of prototype and m -derived π sections.

Note that if $m = 1$, both T and π m -derived sections reduce to the corresponding prototype sections. Note also that the characteristic impedance of the m -derived section is the same as that of the prototype, *i.e.* Z_{0T} or $Z_{0\pi}$.

The m -derived sections considered so far are perfectly general; to study further their behaviour, particular cases must be taken individually.

Low-pass m -derived sections

Fig. 663 shows both the m -derived T and π low-pass filter sections. In deducing these from the general case, note that to divide the impedance of a condenser by m , its capacity must be multiplied by m .

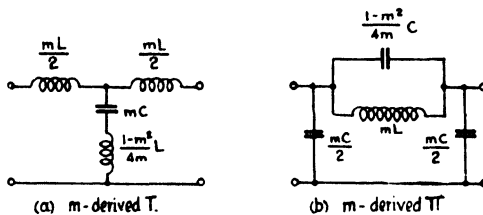


FIG. 663.— m -derived low-pass filter sections.

One important deduction can at once be made, namely, considering first the m -derived T section, that at some frequency the shunt arm will have a series resonance, giving a short-circuit across the transmission path and hence infinite attenuation. In the prototype sections, on the other hand, the attenuation becomes infinite only at infinite frequency. The frequency of infinite attenuation is denoted by f_∞ , and is given for an m -derived T section by the series resonance of the shunt arm.

This frequency is given by:—

$$\omega^2 = \frac{1}{\frac{1-m^2}{4m}L \times mC} = \frac{4}{LC(1-m^2)} = \frac{\omega_c^2}{1-m^2}$$

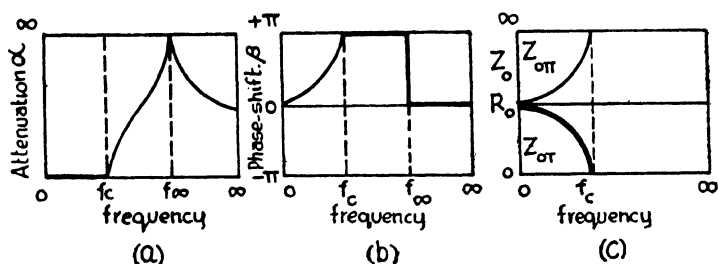


FIG. 664.—*m*-derived T and π low-pass filter sections—Variation with frequency of
 (a) Attenuation. (b) Phase-shift. (c) Characteristic impedance.

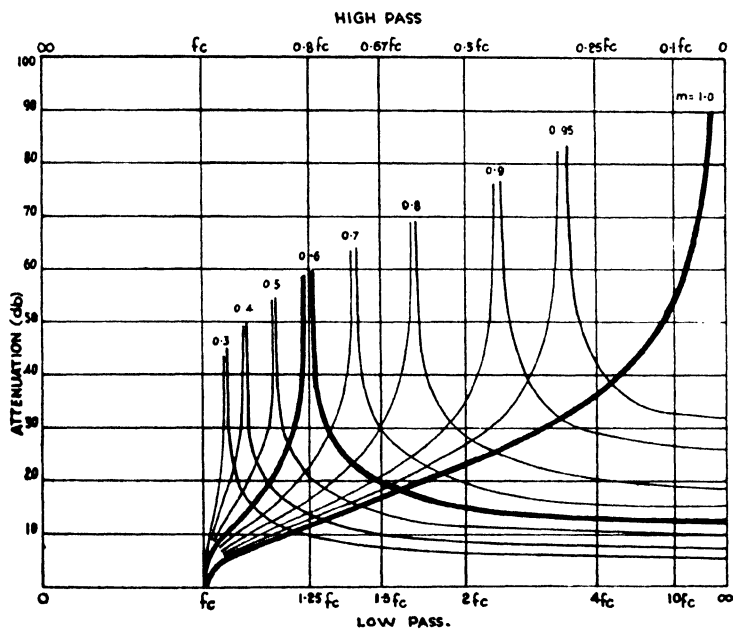


FIG. 665.—Attenuation-frequency curves for *m*-derived T and π low-pass filter sections, showing the effect of the value of *m*.

$$\text{Thus } \omega_{\infty} = \frac{\omega_0}{\sqrt{1-m^2}} \quad \text{or} \quad f_{\infty} = \frac{f_0}{\sqrt{1-m^2}} \quad (42)$$

Similarly an m -derived π section gives a frequency of infinite attenuation at the anti-resonance of the series arm; clearly this frequency has the same value as that for the T section. Fig. 664 shows the way in which α , β and Z_0 vary with frequency for an m -derived low-pass section.

Fig. 665 shows the attenuation-frequency characteristics for m -derived sections for various values of m . It will be seen that, particularly for small values of m , the attenuation rises much more rapidly than in the prototype, but falls off again after the frequency of infinite attenuation has been passed.

If f_{∞} and f_0 are known, the required value of m may be calculated from equation 42:—

$$\begin{aligned} \frac{f_{\infty}}{f_0} &= \frac{1}{\sqrt{1-m^2}} \\ \therefore 1 - m^2 &= \frac{f_0^2}{f_{\infty}^2} \\ \therefore m &= \sqrt{1 - \frac{f_0^2}{f_{\infty}^2}} \quad (43) \end{aligned}$$

This result is used when designing a low-pass filter section to have an infinite attenuation at a given frequency f_{∞} .

Example.—

Find m -derived T and π low-pass filter sections having a cut-off frequency $f_0 = 1000$ c/s, a design impedance $R_0 = 600 \Omega$, and a frequency of infinite attenuation $f_{\infty} = 1050$ c/s.

The value of m is given by:—

$$m = \sqrt{1 - \frac{f_0^2}{f_{\infty}^2}} = \sqrt{1 - \left(\frac{1000}{1050}\right)^2} = 0.305$$

It has already been shown that $L = 191.0 \text{ mH}$ and $C = 0.5304 \mu\text{F}$ for the prototype of this filter (see example on page 646). The required m -derived sections are therefore as shown in Fig. 666.

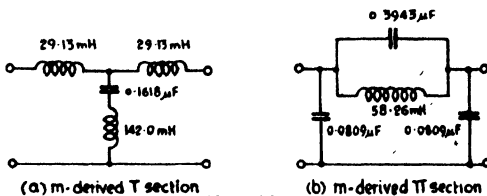


FIG. 666.

High-pass *m*-derived sections

Fig. 667 shows the T and π *m*-derived high-pass filter sections.

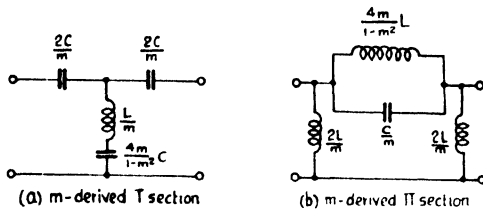


FIG. 667.—*m*-derived high-pass filter sections.

These have a frequency of infinite attenuation given by the resonance of the shunt arm in the T section, and by the anti-resonance of the series arm in the π section. This frequency is the same for the two sections, and is given by:—

$$\omega_{\infty}^2 = \frac{1 - m^2}{4LC} = (1 - m^2)\omega_0^2$$

$$\therefore \omega_{\infty} = \omega_0 \sqrt{1 - m^2} \quad \text{or} \quad f_{\infty} = f_0 \sqrt{1 - m^2} \quad (44)$$

Fig. 668 shows the way in which α , β and Z_0 vary with frequency for an *m*-derived high-pass section.

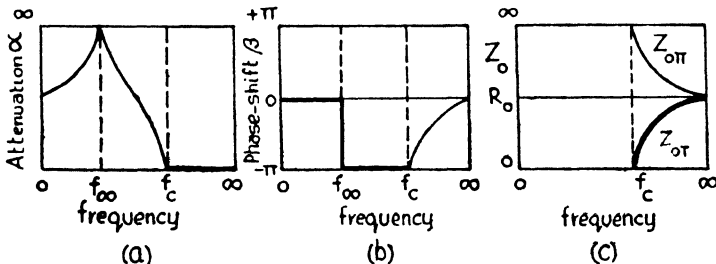


FIG. 668.—*m*-derived T and π high-pass filter sections—Variation with frequency of

- (a) Attenuation. (b) Phase-shift. (c) Characteristic impedance.

The effect of different values of *m* on the attenuation-frequency characteristics corresponds exactly to that for the low-pass filter if $\frac{f_0}{f}$ is written in place of $\frac{f}{f_0}$. Fig. 665 is therefore applicable to a high-pass filter provided that the top frequency scale is used. It follows that, as with the *m*-derived low-pass filter, a small value of *m* gives a very sharp cut-off.

If f_{∞} and f_0 are known, the value of *m* can be calculated from equation 44:—

$$f_{\infty} = f_0 \sqrt{1 - m^2}$$

$$\therefore m = \sqrt{1 - \left(\frac{f_\infty}{f_o}\right)^2} \quad (45)$$

This result is used when designing a high-pass filter to have an infinite attenuation at a given frequency f_∞ .

Example.—

Design m -derived T and π high-pass filter sections having a cut-off frequency $f_o = 10$ kc/s, design impedance $R_o = 600 \Omega$, and $m = 0.35$, and find the frequency of infinite attenuation.

This gives:— $f_\infty = f_o \sqrt{1 - m^2} = 10^4 \sqrt{1 - 0.35^2} = 9367$ c/s.

It has already been shown that $L = 4.774$ mH and $C = 0.01326 \mu\text{F}$ for the prototype of this filter (see example on page 649).

From Fig. 667 the m -derived sections having $m = 0.35$ may be determined.

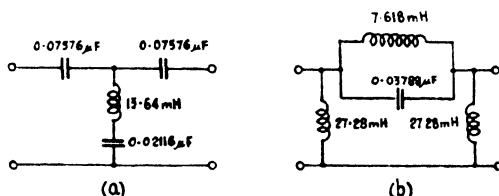


FIG. 669.

The required m -derived sections are as shown in Fig. 669.

IMPEDANCE MATCHING OF FILTERS

Impedance-matching half-sections

When a filter is composed of a number of sections, it is essential that the impedances at each junction shall be correctly matched.

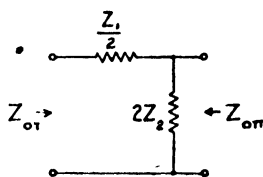


FIG. 670.—Prototype half section, showing image impedances.

Thus a T section having an impedance Z_{0T} should not be joined to a π section having an impedance $Z_{0\pi}$. If it is desirable to construct a filter containing both T and π sections, matching half-sections should be used.

The half-section shown in Fig. 670 has image impedances Z_{or} and $Z_{o\pi}$, and may therefore be employed to match a T section to a π section as in Fig. 671.

If a filter is correctly matched throughout on such an image impedance basis, the overall attenuation of the filter will be simply

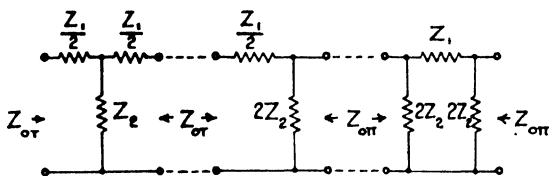


FIG. 671.—Use of prototype half-section for matching T and π sections.

the sum of the attenuations of the individual sections or half-sections, there being no internal reflection or mismatch losses.

It will be remembered that the half-section is the basic element of the symmetrical ladder networks, and that both T and π sections when divided down the centre give rise to two of these half-sections (see Fig. 672).

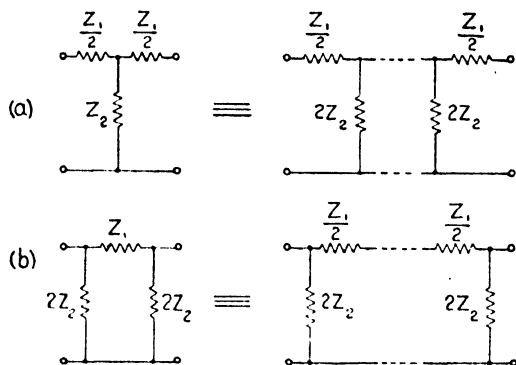


FIG. 672.—Prototype half-section as basic element of both T and π prototype sections.

Terminating half-sections

If an m -derived T section is split down the centre the result is an m -derived half-section as shown in Fig. 673a. Clearly one of the image impedances will be Z_{or} , but the other one is *not* $Z_{o\pi}$; it may be shown to depend on the value of m . Let it be called $Z_{o\pi m}$. If an m -derived π section is divided down the centre, the result is a different kind of m -derived half-section, as in Fig. 673b. In this case, the image impedances are Z_{or} and $Z_{or m}$, where this latter impedance depends on the value of m .

These two types of m -derived half-sections, which are shown in

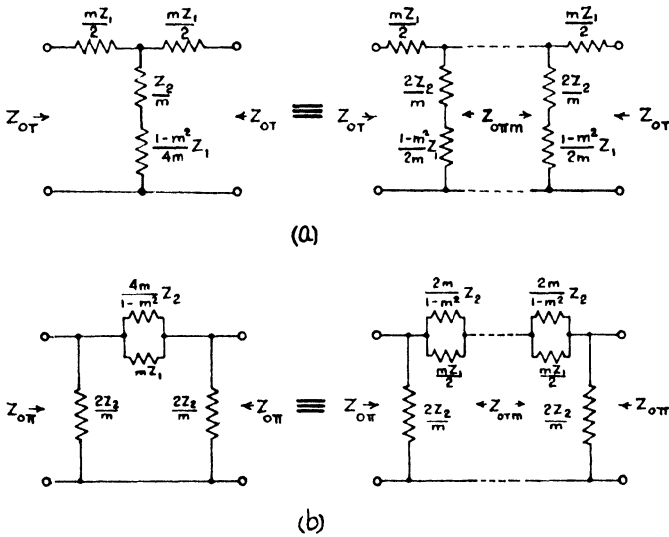


FIG. 673.—Derivation of m -derived half-sections.

Fig. 674, and the image impedances $Z_{0\pi m}$ and Z_{0Tm} are of great importance in filter theory; the reason will be apparent from Fig. 675, which shows how the values of the image impedances vary with frequency in the case of low-pass and high-pass m -derived half-sections.

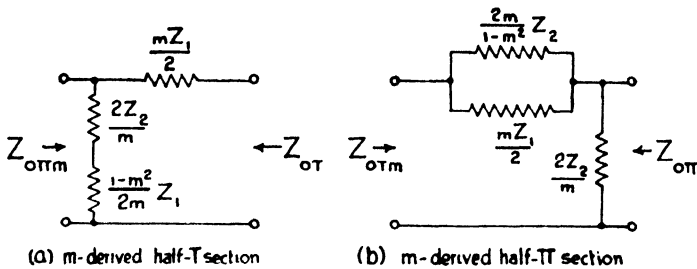


FIG. 674.— m -derived half sections showing image impedance.

The importance of “ $m = 0.6$ m -derived half-sections”, or “terminating half-sections” as they are often called, lies in the fact that, when $m = 0.6$, $Z_{0\pi m}$ and Z_{0Tm} lie between $0.9 R_0$ and $1.1 R_0$ over most of the pass-band. It will be seen that this enables a filter to be terminated accurately in a pure resistance (equal to the design impedance R_0) over practically the whole pass band.

Note that $Z_{0\pi m}$ and Z_{0Tm} are only the impedances obtained by splitting a T or π section in half. The impedance of a complete m -derived T or π section is the same as that of the prototype, i.e., Z_{0T} or $Z_{0\pi}$.

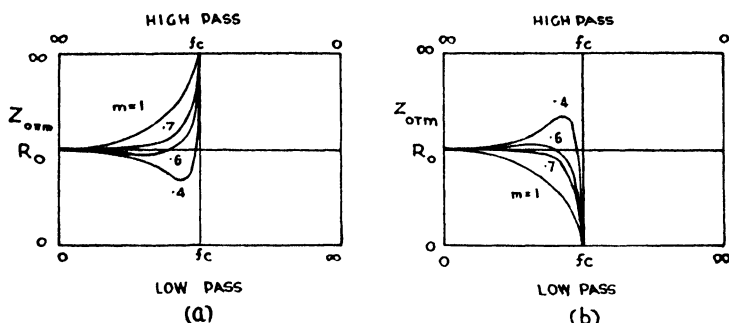


FIG. 675.—Variation of Z_{0Tm} and Z_{0Tm} with frequency for different values of m .

Example.—

Find the $m = 0.6$ terminating half-sections required for a high-pass filter with $f_0 = 10$ kc/s and $R_0 = 600\Omega$.

The prototype section has already been found to have $L = 4.774$ mH and $C = 0.01326\mu$ F (see example on page 649). By employing the method indicated by Figs. 661 and 662, the complete m -derived sections having $m = 0.6$ may be determined, and are as shown in Fig. 676a and b. The m -derived T section divides symmetrically to give m -derived half-T sections as in Fig. 676c, and the corresponding m -derived half- π section is shown in Fig. 676d.

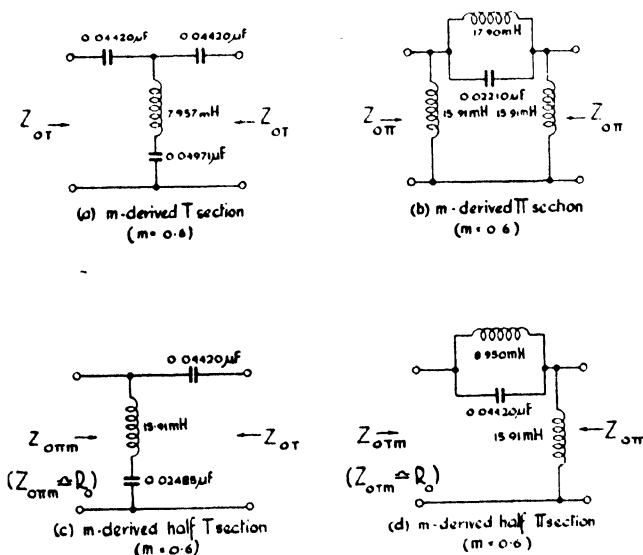


FIG. 676 a-d.

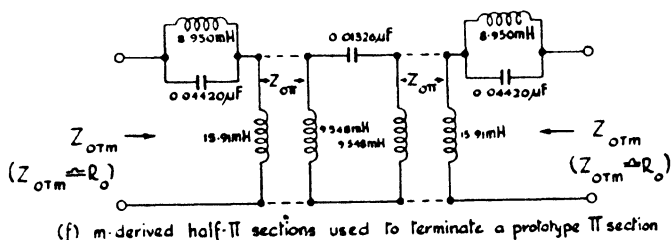
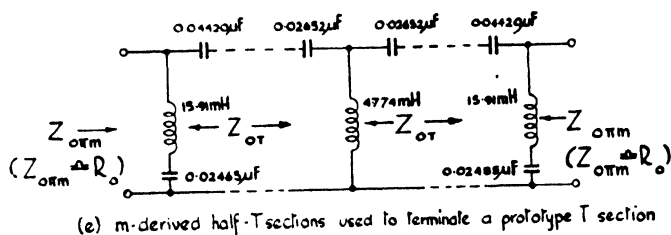


FIG. 676 e and f.—Illustrating use of m -derived half sections ($m = 0.6$) for terminating filters.

Consider further how these sections may be utilised. Fig 676e shows how m -derived half-T sections are used to terminate a filter that is made up of T sections. In this particular case a single prototype T section has been terminated in this way. The impedance relationships shown in the diagram indicate how the terminating sections fit on to the prototype sections without mismatch, whilst presenting input and output impedances practically equal to the design impedance R_0 over the whole of the pass band. Fig. 676f shows, in a similar way, how m -derived half- π sections are used to terminate a filter that is made up of π sections.

Mismatch loss in the attenuation band

It has been seen that, by using suitable m -derived half-sections with $m = 0.6$, it is possible to match the filter to purely resistive circuits, and this matching is practically perfect over about nine-tenths of the pass band. In the attenuation band, however, the characteristic impedance of the filter is a pure reactance, and the filter is terminated in a pure resistance (the design impedance R_0). The whole basis of argument so far has been the supposition made on page 636 that the filter is *always* correctly terminated in its characteristic impedance, that means, in a pure reactance, in the attenuation band.

The effect of this mis-termination may be deduced by treating the filter as a four-terminal network interposed between a generator and a load; the loss produced by the filter is then given by

equation 7 of Chapter 13 (see page 566). This method is somewhat tedious; however, it has been shown in Chapter 13 that when a network has a high attenuation, the input impedance is practically equal to Z_0 , regardless of the termination.

This applies to all transmission networks, and, in particular, to filters. Since a filter has a high value of attenuation in the attenuation band, the fact that the termination is not equal to the characteristic impedance has little effect on the input impedance of the filter. This input impedance changes from resistance to reactance at the cut-off frequencies, and gives the pass and attenuation bands just as if the original supposition actually held good.

This mismatch in the attenuation band does, however, affect the overall attenuation of the section in that it gives rise to an additional "mismatch loss" over and above the calculated

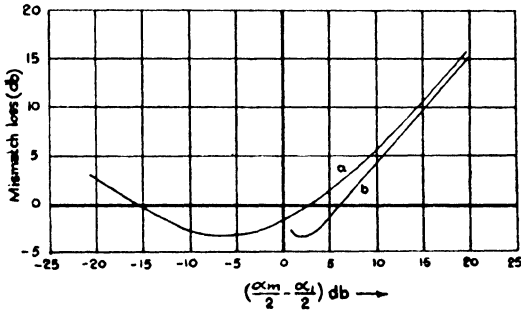


FIG. 677.—Mismatch loss per termination for an m -derived half section terminated in its design impedance (valid in the attenuation band provided $0.3 < m < 0.8$).

attenuation of the filter. The important case is that in which an m -derived half-section, used as a terminating section, is terminated in its design impedance. In this case it has been found that the mismatch loss is a function of the difference between the attenuation $\frac{\alpha_1}{2}$ of the prototype half-section and $\frac{\alpha_m}{2}$ that of the m -derived half-section. This applies for any frequency in the attenuation band, but only for sections with values of m between 0.3 and 0.8. The loss for one termination is given by the graphs in Fig. 677, curve b being used for frequencies on the pass band side of f_ω , and curve a for frequencies on the other side of f_ω .

Example.—

What is the mismatch loss at one termination of a low-pass filter at $1.2f_0$ if an $m = 0.6$ half-section is used for terminating?

The attenuation of an $m = 0.6$ section at $1.2f_0$ is (from

Fig. 665) $\alpha_m = 25$ db. The loss of the prototype at the same frequency is $\alpha_1 = 10$ db.

$$\therefore \frac{\alpha_m}{2} - \frac{\alpha_1}{2} = 7.5 \text{ db.}$$

This frequency is on the pass band side of f_∞ (for $f_\infty = 1.25 f_0$) so curve *b* is used. This gives the mismatch loss as about 1 db.

Effect of resistance on filter characteristics

Reactances used in practical filters are not pure but contain resistance. In the case of a condenser this appears as a high shunt resistance and is usually negligible. In the case of inductances, it appears as series resistance and is often comparable in magnitude with the reactance. Its effect is to round off the attenuation characteristic near f_0 and f_∞ so that there will be attenuation in the pass band. Fig. 659 shows the characteristic of a typical

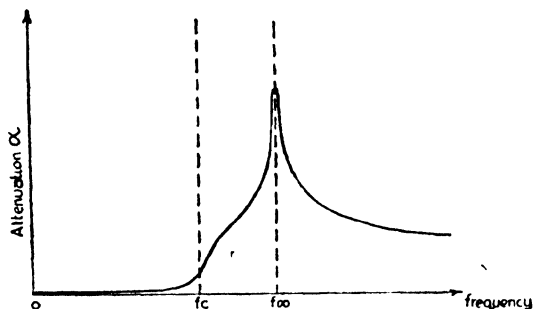


FIG. 678.—Attenuation-frequency characteristic of a typical *m*-derived low-pass filter section.

low-pass prototype section; Fig. 678 gives the curve for a practical *m*-derived low-pass section.

The attenuations of a filter section at the cut-off frequency f_0 and at the "frequency of infinite attenuation" f_∞ are not, in practice, zero and infinite, but are given approximately by the relations:—

$$\alpha_0 = \frac{12}{m\sqrt{Q}} \quad \text{db} \quad (46a)$$

$$\alpha_\infty = 20 \cdot \log_{10} \frac{4m^2Q}{1-m^2} \quad \text{db} \quad (46b)$$

where $Q = \frac{\omega L}{R}$ for the inductance.

Complete filters

Complete filters are made up of a number of sections and half-sections connected together. The design of a complete filter is dependent upon two things:—(i) the required attenuation characteristic, and (ii) the impedance. The first determines the cut-off frequency f_0 ; if this and the impedance are known, the elements of the prototype section can be calculated. The number of sections depends upon the attenuation required; if the attenuation

characteristic is to rise rapidly, at least one m -derived section with a small value of m will be required. $m = 0.3$ to 0.35 is the value usually selected; a smaller value of m causes too large an attenuation at cut-off. If, in addition, the attenuation is to remain high at frequencies well beyond the cut-off frequency, either a prototype section or an m -derived section with a larger value of m (or both) will be required. Finally, if the impedance termination is important, two terminating half-sections with $m = 0.6$ will be needed; it must be remembered that these two terminating half-sections will contribute to the total attenuation to the same extent as a complete section with $m = 0.6$.

Example.—

Design a high-pass filter to satisfy the following conditions:—

- (i) Attenuation above 10.5 kc/s to be less than 6 db.
- (ii) Attenuation below 9.5 kc/s to be greater than 30 db.
- (iii) Input and output impedances to be 600 ± 50 ohms above 12 kc/s.

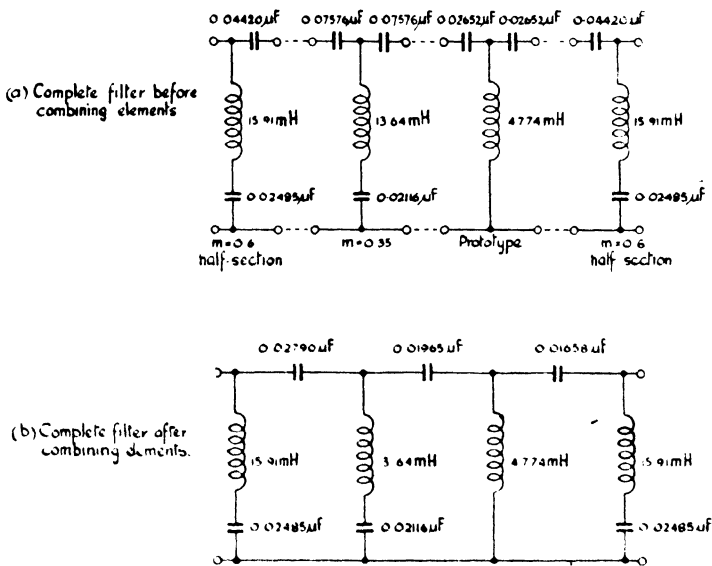


FIG. 679.

Suppose it is decided to work in terms of T sections throughout. This is in general an arbitrary decision, and in practice both types of filter would probably be worked out, the final selection being based on values and numbers of the components required in each case.

The cut-off frequency is selected as 10 kc/s, which fits in with conditions (i) and (ii). To satisfy condition (iii), two $m = 0.6$

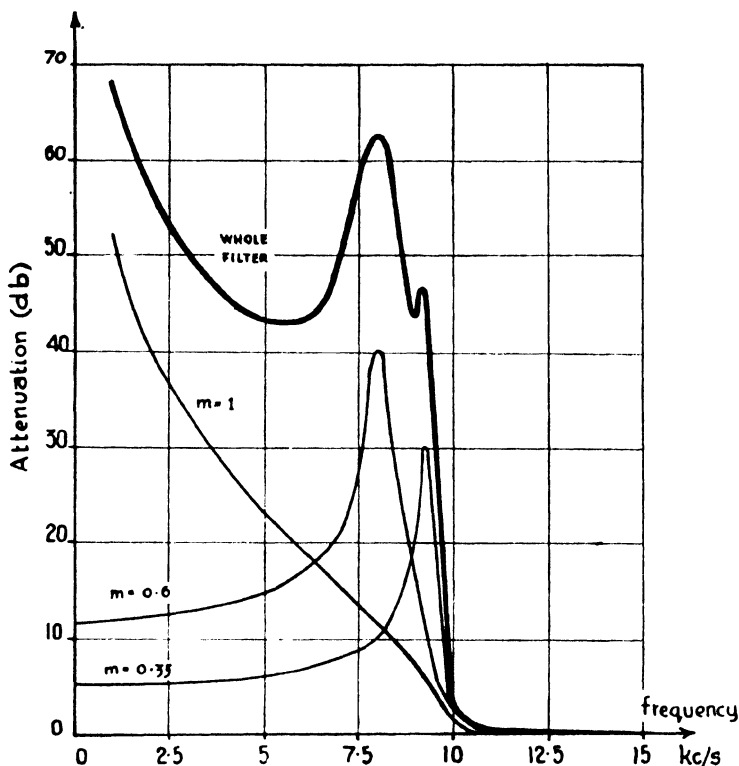


FIG. 680.—Attenuation-frequency characteristics for complete high-pass filter and for component sections.

terminating half-sections are required. To satisfy condition (ii) at low frequencies, a prototype section is needed, and since a sharp cut-off is required an m -derived section with $m = 0.35$ is included.

All three of these sections have been determined in previous examples. The prototype section is shown in Fig. 658, the $m = 0.35$ derived section in Fig. 669*a*, and the terminating half-section in Fig. 676*c*. The complete filter is therefore as shown in Fig. 679*a*, or, combining the series condensers, the final form is given in Fig. 679*b*. The attenuation-frequency curves for each section and for the whole filter are shown in Fig. 680.

BAND-PASS AND BAND-STOP FILTERS

Band-pass filters

There are several types of band-pass filter, of which one only will be discussed here. This is the constant- k type, and a prototype T section is shown in Fig. 681. It will be noted that the series

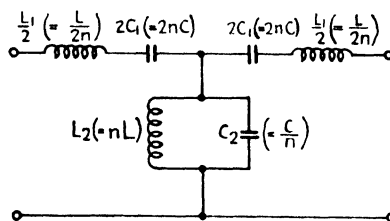


FIG. 681.—Prototype band-pass filter section.

and shunt arms are arranged to have the same resonant frequency; let this be called f_0 . It will be seen that:—

$$f_0 = \frac{1}{2\pi \sqrt{LC}} \quad \text{i.e. } \omega_0 = \frac{1}{\sqrt{LC}} \quad (47)$$

To show that the filter is constant- k , i.e. that the product of the series and shunt arm impedances is equal to a real constant, put:—

$$\sqrt{\frac{L}{C}} = R_0 \quad (48)$$

and let
$$x = \frac{f}{f_0} = \frac{\omega}{\omega_0} = \omega \sqrt{LC} \quad (49)$$

so that
$$\omega L = R_0 x \quad (50)$$

and
$$\frac{1}{\omega C} = \frac{R_0}{x} \quad (51)$$

Now the series arm $Z_1 = j\frac{\omega L}{n} - \frac{j}{n\omega C} = j\frac{R_0 x}{n} - \frac{jR_0}{nx}$

i.e.
$$Z_1 = j\frac{R_0(x^2 - 1)}{nx} \quad (52)$$

and the shunt arm $Z_2 = \frac{j\omega nL - \frac{jn}{\omega C}}{j\omega nL - \frac{jn}{\omega C}} = \frac{-jn\frac{L}{C}}{\omega L - \frac{1}{\omega C}} = \frac{jnR_0^2}{\frac{R_0}{x} - R_0 x}$

i.e.
$$Z_2 = j\frac{nR_0 x}{1 - x^2} \quad (53)$$

Multiplying equations 52 and 53, it is seen that:—

$$Z_1 Z_2 = R_0^2$$

and the section is constant- k ; equation 48 therefore gives the design impedance.

To verify that such a section has a band-pass characteristic, let $Z_1 = jX_1$ and $Z_2 = jX_2$, and draw the reactance-frequency sketches for X_1 and $\left(\frac{X_1}{4} + X_2\right)$, as in Fig. 682.

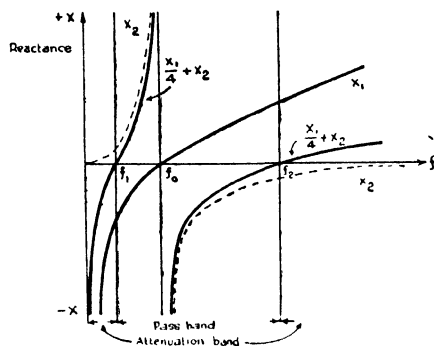


FIG. 682.—Reactance-frequency sketch for prototype band-pass filter section.

It is apparent that between f_1 and f_2 (the two series resonant frequencies of $\frac{Z_1}{4} + Z_2$) the reactance curves are on opposite sides of the frequency axis, and the filter has a pass band; outside these limits of frequency, the curves are on the same side of the frequency axis and the filter attenuates. The network is therefore a band-pass filter with cut-off frequencies f_1 and f_2 . It would be possible to find f_1 and f_2 by evaluating the series resonant frequencies of $\frac{Z_1}{4} + Z_2$, but a simpler method will be employed.

Consider the characteristic impedance of the section:—

$$Z_0 = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}$$

Then, from equations 52 and 53:—

$$Z_0 = \sqrt{R_0^2 - \frac{R_0^2(x^2 - 1)^2}{4n^2x^2}} = R_0 \sqrt{1 - \frac{(x^2 - 1)^2}{4n^2x^2}}$$

Thus Z_0 is real, giving a *pass band* if:—

$$\frac{(x^2 - 1)^2}{4n^2x^2} < 1$$

$$\text{i.e.} \quad -1 < \frac{x^2 - 1}{2nx} < 1$$

• The cut-off frequencies are given by the positive roots of the equations:—

$$\frac{x^2 - 1}{2nx} = -1 \quad \text{and} \quad \frac{x^2 - 1}{2nx} = +1$$

Hence :—

$$\begin{array}{l}
 x^2 + 2nx - 1 = 0 \\
 \therefore x^2 + 2nx + n^2 = 1 + n^2 \\
 \therefore x_1 + n = +\sqrt{1 + n^2} \\
 \therefore x_1 = -n + \sqrt{1 + n^2} \quad (54)
 \end{array}
 \left|
 \begin{array}{l}
 x^2 - 2nx - 1 = 0 \\
 \therefore x^2 - 2nx + n^2 = 1 + n^2 \\
 \therefore x_2 - n = +\sqrt{1 + n^2} \\
 \therefore x_2 = +n + \sqrt{1 + n^2} \quad (55)
 \end{array}
 \right.$$

These results give the cut-off frequencies, since $x_1 = \frac{f_1}{f_0}$ and $x_2 = \frac{f_2}{f_0}$.

Note that $x_2 - x_1 = 2n$
i.e. $f_2 - f_1 = 2nf_0$ (56)

an expression giving the *band-width* in terms of n and f_0 .

Also, from equations 54 and 55 :—

$$\begin{array}{l}
 x_1 x_2 = 1 \\
 f_1 f_2 = f_0^2
 \end{array}
 \quad (57)$$

i.e. f_0 is the mid-band frequency, where mid-band frequency is taken to be the geometric mean of the two cut-off frequencies.

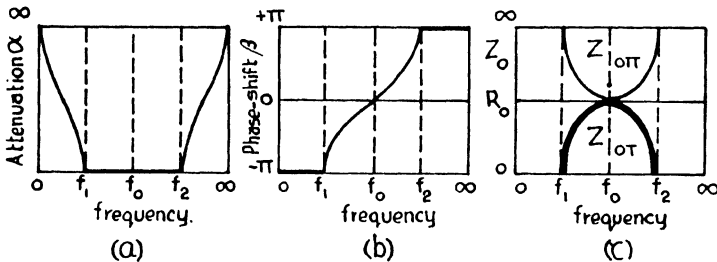


FIG. 683.—Prototype band-pass filter section—Variation with frequency of

(a) Attenuation. (b) Phase-shift. (c) Characteristic impedance.

It can be shown that the attenuation outside the pass band is given by :—

$$\alpha = \cosh^{-1} \left\{ \frac{(1 - x^2)^2}{2n^2 x^2} - 1 \right\} \quad \text{nepers} \quad (58)$$

This gives the characteristic of Fig. 683a. The phase-shift is given by :—

$$\beta = \cos^{-1} \left\{ 1 - \frac{(1 - x^2)^2}{2n^2 x^2} \right\} \quad \text{radians} \quad (59)$$

giving the curve of Fig. 683b.

$$Z_{0r} = R_0 \sqrt{1 - \frac{(x^2 - 1)^2}{4n^2 x^2}} \quad (60)$$

and :—

$$Z_{0\pi} = \frac{R_0}{\sqrt{1 - \frac{(x^2 - 1)^2}{4n^2 x^2}}} \quad (61)$$

plotted in Fig. 683c.

Design of a prototype band-pass filter

Suppose that the required cut-off frequencies f_1 and f_2 and the design impedance R_0 are given ; equation 57 then gives :—

$$f_0 = \sqrt{f_1 f_2}$$

and 56 gives :—

$$n = \frac{f_2 - f_1}{2f_0}$$

Thus f_0 and n may be found.

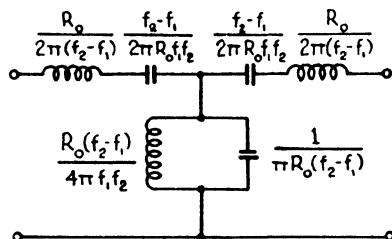


FIG. 684.—Prototype band-pass filter section with component values in terms of cut-off frequencies and design impedance.

Then, from equations 47 and 48 :—

$$L = \frac{R_0}{2\pi f_0} \quad (62)$$

$$C = \frac{1}{2\pi f_0 R_0} \quad (63)$$

Hence
$$L_1 = \frac{L}{n} = \frac{R_0}{\pi(f_2 - f_1)} \quad (64)$$

$$L_2 = nL = \frac{R_0(f_2 - f_1)}{4\pi f_1 f_2} \quad (65)$$

$$C_1 = nC = \frac{f_2 - f_1}{4\pi R_0 f_1 f_2} \quad (66)$$

$$C_2 = \frac{C}{n} = \frac{1}{\pi R_0(f_2 - f_1)} \quad (67)$$

The required section is therefore as shown in Fig. 684.

Note that the inductance in the series arm and the capacity in the shunt arm depend only on the band-width and the design

impedance, and not on the position of the band. This is worth noting in connection with multi-channel VF telegraph systems, where all the filters have the same band-width.

Example.—

Design a prototype T section for a band-pass filter having cut-off frequencies of 1000 c/s and 4000 c/s, and a design impedance of 600Ω. In this case $R_0 = 600$, $f_1 = 1000$, and $f_2 = 4000$. Putting these values into Fig. 684 :—

$$\text{Inductance in series arm is } \frac{600}{2\pi(4000-1000)} = 31.83\text{mH}$$

$$\text{Capacity in series arm is } \frac{4000-1000}{2\pi \cdot 600 \cdot 1000 \cdot 4000} = 0.1989\mu\text{F}$$

$$\text{Inductance in shunt arm is } \frac{600(4000-1000)}{4\pi \cdot 1000 \cdot 4000} = 35.80\text{mH}$$

$$\text{Capacity in shunt arm is } \frac{1}{\pi \cdot 600(4000-1000)} = 0.1768\mu\text{F}$$

The required section is therefore as shown in Fig. 685.

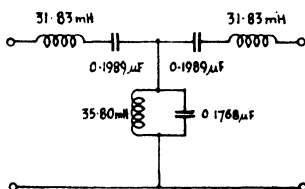


FIG. 685.—Illustrating design procedure for band-pass prototype T section.

***m*-derived band-pass sections**

Prototype band-pass filters may be derived in a similar manner to low- and high-pass filters. From Figs. 660 and 681 the *m*-derived

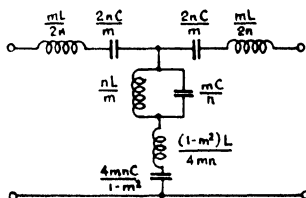


FIG. 686.—*m*-derived T section for a band-pass filter.

section of the band-pass filter is seen to be as shown in Fig. 686. The frequency or frequencies of infinite attenuation can be calculated from the series resonance of the shunt arm.

The impedance of the shunt arm is given by:—

$$Z'_2 = \frac{Z_2}{m} + \frac{Z_1(1-m^2)}{4m}$$

where Z_1 and Z_2 are the series and shunt impedances respectively of the prototype.

From equations 52 and 53:—

$$Z_1 = j \frac{R_0(x^2 - 1)}{nx} \quad \text{and} \quad Z_2 = -j \frac{R_0 nx}{(x^2 - 1)}$$

$$\begin{aligned} \therefore Z'_2 &= \frac{-jR_0 nx}{m(x^2 - 1)} + \frac{jR_0(x^2 - 1)(1 - m^2)}{4mnx} \\ &= \frac{jR_0[(1 - m^2)(x^2 - 1)^2 - 4n^2x^2]}{4mnx(x^2 - 1)} \end{aligned}$$

Therefore the series resonant condition is:—

$$(x^2 - 1)^2 = \frac{4n^2x^2}{1 - m^2}$$

$$\therefore x^2 - 1 = \pm \frac{2nx}{\sqrt{1 - m^2}}$$

$$\therefore x^2 - \frac{2nx}{\sqrt{1 - m^2}} - 1 = 0 \quad \text{or} \quad x^2 + \frac{2nx}{\sqrt{1 - m^2}} - 1 = 0$$

$$\therefore x = \frac{n}{\sqrt{1 - m^2}} \pm \sqrt{\frac{n^2}{1 - m^2} + 1} \quad \text{or}$$

$$x = \frac{-n}{\sqrt{1 - m^2}} \pm \sqrt{\frac{n^2}{1 - m^2} + 1}$$

This gives four values of x , but only two of them are positive; calling these $x_{1\infty}$ and $x_{2\infty}$, then:—

$$x_{1\infty} = \sqrt{1 + \frac{n^2}{1 - m^2}} - \frac{n}{\sqrt{1 - m^2}} \quad (68)$$

$$x_{2\infty} = \sqrt{1 + \frac{n^2}{1 - m^2}} + \frac{n}{\sqrt{1 - m^2}} \quad (69)$$

Note that $x_{1\infty} \cdot x_{2\infty} = 1$ (70)

and that $x_{2\infty} - x_{1\infty} = \frac{2n}{\sqrt{1 - m^2}}$ (71)

But $x = \frac{f}{f_0}$, so that $x_{1\infty}$ (a value of x giving infinite attenuation), is $\frac{f_{1\infty}}{f_0}$, where $f_{1\infty}$ is a frequency of infinite attenuation. Similarly $x_{2\infty} = \frac{f_{2\infty}}{f_0}$, where $f_{2\infty}$ is the other frequency of infinite attenuation.

From equation 70 :—

$$f_{1\infty} \cdot f_{2\infty} = f_0^2 \tag{72}$$

so that f_0 is the geometric mean of the frequencies of infinite attenuation, as well as being the geometric mean of the cut-off frequencies.

From equations 71 and 56 :—

$$f_{2\infty} - f_{1\infty} = \frac{2nf_0}{\sqrt{1-m^2}} = \frac{\text{Bandwidth}}{\sqrt{1-m^2}} \tag{73}$$

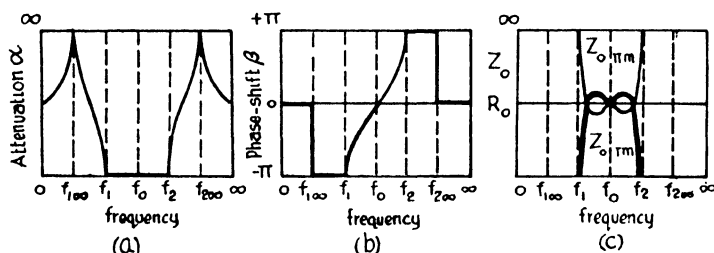


FIG. 687.— m -derived band-pass filter sections.—Variation with frequency of

- (a) Attenuation. (b) Phase-shift. (c) Z_{0pm} and Z_{0Tm}

Fig. 687a and b shows the attenuation-frequency and phase-shift frequency characteristics for m -derived band-pass sections. Fig. 687c shows Z_{0pm} and Z_{0Tm} plotted against frequency. Z_{0m} and Z_{0T} are the same as for the prototype section.

It has been shown that the shunt arm of the m -derived band-pass filter has two series resonant frequencies, being the frequencies of infinite attenuation. It can be proved that this shunt arm may be replaced by two series resonant circuits in parallel (see Fig. 688).

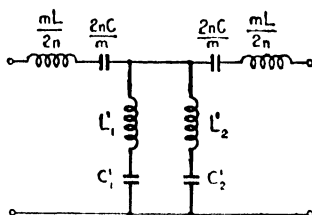


FIG. 688.—Alternative form of m -derived band-pass section.

The corresponding values of L'_1 , C'_1 , and L'_2 , C'_2 are :—

$$L'_1 = \frac{L}{n} \cdot \frac{(1-m^2)}{4m} \cdot \frac{x_{1\infty} + x_{2\infty}}{x_{1\infty}} = \frac{n}{m} \cdot \frac{1 + x_{1\infty}^2}{(1 - x_{1\infty}^2)^2} L \tag{74}$$

$$C_1' = Cn \frac{4m}{1-m^2} \cdot \frac{1}{x_{1\infty}(x_{1\infty} + x_{2\infty})} = \frac{m}{n} \frac{(1-x_{1\infty}^2)^2}{x_{1\infty}^2(1+x_{1\infty}^2)} C \quad (75)$$

$$L_2' = \frac{L}{n} \cdot \frac{1-m^2}{4m} \cdot \frac{x_{1\infty} + x_{2\infty}}{x_{2\infty}} = \frac{n}{m} \frac{1+x_{2\infty}^2}{(1-x_{2\infty}^2)^2} L \quad (76)$$

$$C_2' = Cn \frac{4m}{1-m^2} \cdot \frac{1}{x_{2\infty}(x_{1\infty} + x_{2\infty})} = \frac{m}{n} \frac{(1-x_{2\infty}^2)^2}{x_{2\infty}^2(1+x_{2\infty}^2)} C \quad (77)$$

It will be noticed that the resonant frequencies of the two series resonant circuits are $f_{1\infty}$ and $f_{2\infty}$ respectively. This form of the m -derived section is the one that is almost invariably encountered in practice (see Fig. 689).

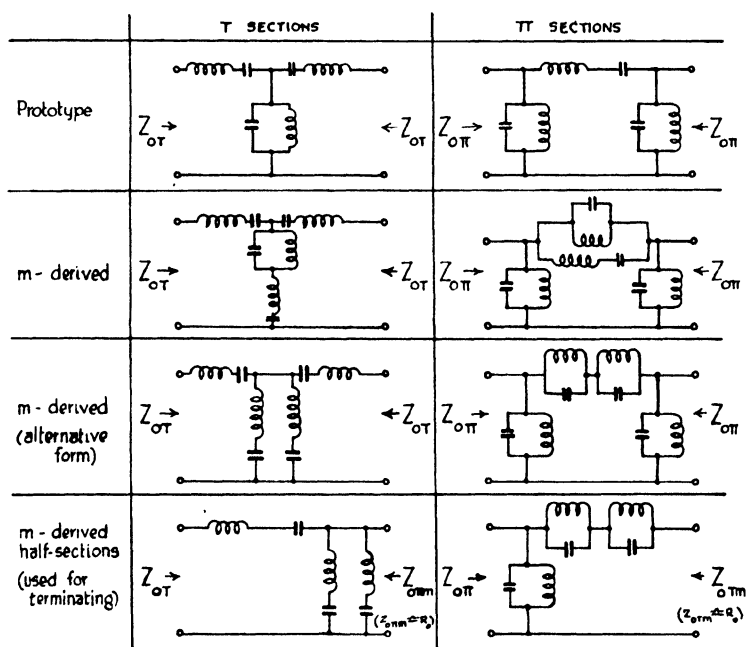


FIG. 689.—Summary of band-pass filter sections.

Band-stop filters

Fig. 690 shows the prototype T section of a band-stop filter. As in the case of the band-pass filter, the series and shunt arms are arranged to have the same resonant frequency.

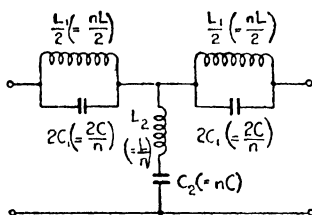


FIG. 690.—Prototype T section band-stop filter.

Let this frequency be f_0 . It will be seen that:—

$$f_0 = \frac{1}{2\pi\sqrt{LC}}, \text{ or } \omega_0 = \frac{1}{\sqrt{LC}} \tag{78}$$

To show that the filter is constant- k ,

put
$$\sqrt{\frac{L}{C}} = R_0 \tag{79}$$

and let
$$x = \frac{f}{f_0} = \frac{\omega}{\omega_0} = \omega\sqrt{LC} \tag{80}$$

so that
$$\omega L = R_0 x \tag{81}$$

and
$$\frac{1}{\omega C} = \frac{R_0}{x} \tag{82}$$

Now in this case,

the series arm $Z_1 = \frac{j\omega nL \times \frac{-jn}{\omega C}}{j\omega nL - \frac{jn}{\omega C}}$

$$= \frac{-jn \frac{L}{C}}{\omega L - \frac{1}{\omega C}}$$

$$= \frac{jnR_0^2}{\frac{R_0}{x} - R_0 x}$$

$$= j \frac{nR_0 x}{1 - x^2} \tag{83}$$

and the shunt arm $Z_2 = \frac{j\omega L}{n} - \frac{j}{n\omega C}$

$$= j \frac{R_0 x}{n} - \frac{jR_0}{nx}$$

$$= j \frac{R_0(x^2 - 1)}{nx} \tag{84}$$

Multiplying equations 83 and 84, it is seen that :—

$$Z_1 Z_2 = R_0^2$$

and the section is a constant- k section; equation 79 therefore gives the design impedance.

Fig. 691 gives the reactance-frequency sketch for X_1 and $\frac{X_1}{4} + X_2$, and shows that the section is a band-stop filter with cut-off frequencies f_1 and f_2 , which are the series resonant frequencies of $(\frac{Z_1}{4} + Z_2)$.

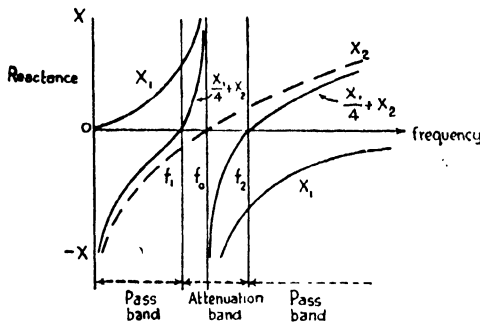


FIG. 691.—Reactance-frequency sketch for prototype band-stop filter.

Consider Z_0 for the section.

$$Z_0 = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}$$

Then, from equations 83 and 84 :—

$$Z_0 = \sqrt{R_0^2 - \frac{n^2 R_0^2 x^2}{4(1-x^2)^2}} = R_0 \sqrt{1 - \frac{n^2 x^2}{4(1-x^2)^2}}$$

It can be shown that the cut-off frequencies are given by :—

$$x_1 = \frac{-n + \sqrt{n^2 + 16}}{4} \quad \text{and} \quad x_2 = \frac{n + \sqrt{n^2 + 16}}{4} \quad (85)$$

$$\text{or } f_1 = f_0 \cdot \frac{-n + \sqrt{n^2 + 16}}{4} \quad \text{and} \quad f_2 = f_0 \cdot \frac{n + \sqrt{n^2 + 16}}{4} \quad (86)$$

Note that

$$x_2 - x_1 = \frac{n}{2}$$

$$\text{i.e.} \quad f_2 - f_1 = \frac{n f_0}{2} \quad (87)$$

giving the *bandwidth* in terms of n and f_0 .

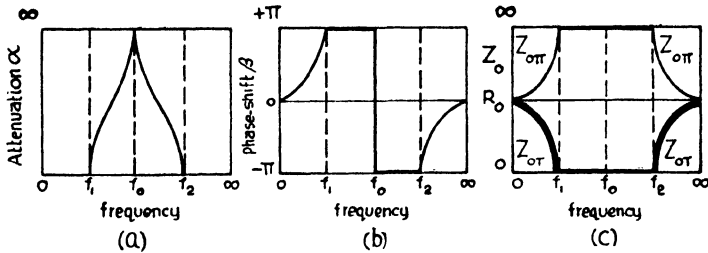


FIG. 692.—Prototype band-stop filter sections—Variation with frequency of

(a) Attenuation. (b) Phase-shift. (c) Characteristic impedance.

Also, that $x_1 x_2 = 1$
i.e. $f_1 f_2 = f_0^2$ (88)
i.e., f_0 , the *mid-band frequency*, is the geometric mean of the two cut-off frequencies. Fig. 692 shows the variation with frequency of attenuation, phase-shift and characteristic impedance.

Design of a prototype band-stop filter

Let the required cut-off frequencies be f_1 and f_2 and the design impedance R_0 .

Equation 88 then gives :—

$$f_0 = \sqrt{f_1 f_2}$$

and equation 87 gives :—

$$n = \frac{2(f_2 - f_1)}{f_0}$$

Thus f_0 and n may be found.

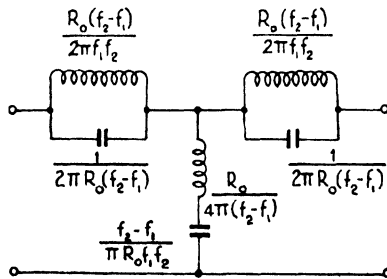


FIG. 693.—Prototype band-stop filter section with component values in terms of cut-off frequencies and design impedance.

From equations 78 and 79

$$L = \frac{R_0}{2\pi f_0} \quad \text{and} \quad C = \frac{1}{2\pi f_0 R_0}$$

Hence
$$L_1 = nL = \frac{R_0 (f_2 - f_1)}{\pi f_1 f_2} \quad (89)$$

$$L_2 = \frac{L}{n} = \frac{R_0}{4\pi (f_2 - f_1)} \quad (90)$$

$$C_1 = \frac{C}{n} = \frac{1}{4\pi R_0 (f_2 - f_1)} \quad (91)$$

$$C_2 = nC = \frac{f_2 - f_1}{\pi R_0 f_1 f_2} \quad (92)$$

The required section is therefore as shown in Fig. 693.

It is interesting to note that if a prototype band-pass half-section is taken and the series and shunt arms are interchanged, a band-stop half-section is formed that has the same cut-off frequencies as the original band-pass half-section.

m-derived band-stop section

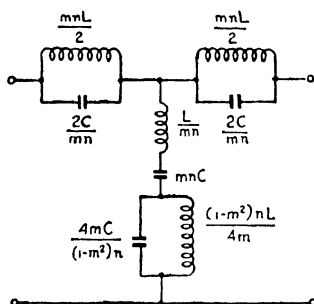


FIG. 694.—*m*-derived band-stop filter section.

m-derived band-stop sections can be obtained in the same way as for band-pass sections; Fig. 694 shows an *m*-derived band-stop T section. As with *m*-derived band-pass sections, the alternative

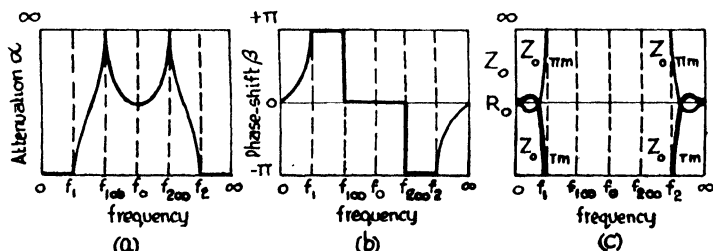


FIG. 695.—*m*-derived band-stop filter sections—Variation with frequency of

(a) Attenuation

(b) Phase-shift.

(c) Z_{0Tm} and Z_{0Tm} .

form of the shunt arm is almost invariably used (see Fig. 696). Fig. 695*a* and *b* shows the attenuation-frequency and phase-shift frequency characteristics for an m -derived band-stop filter. Fig. 695*c* shows Z_{0Tm} and $Z_{0\pi m}$ plotted against frequency. Z_{0T} and $Z_{0\pi}$ are the same as for the prototype section.

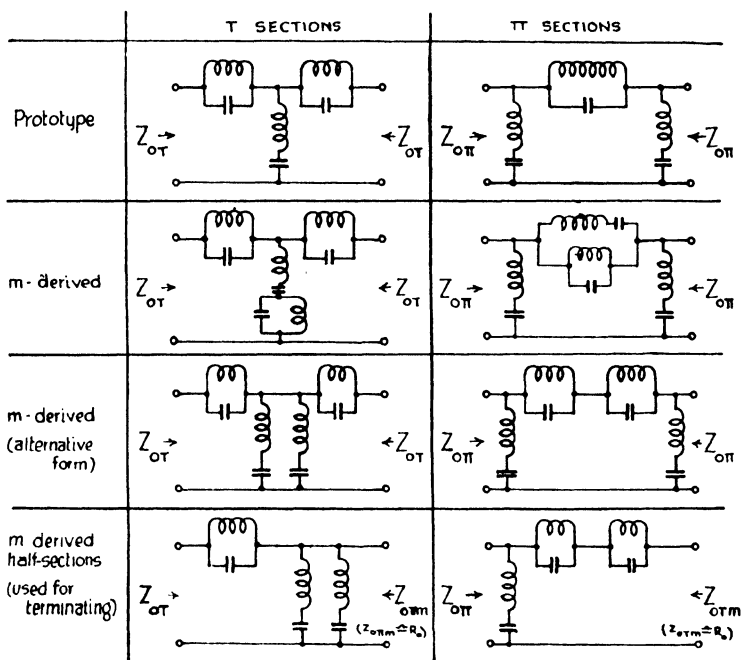


FIG. 696.—Summary of band-stop filter sections.

FURTHER FILTER DESIGN CONSIDERATIONS

Connection of filters in parallel

Consider the case of a high-pass and a low-pass filter connected in parallel at one end, the cut-off frequencies being almost equal (see Fig. 697*a*).

In the pass band of the low-pass filter, the high-pass filter adds a reactance in parallel with the resistive termination of the low-pass filter. This reactance can be represented approximately by a condenser and inductance in series, as in Fig. 697*b*. The low-pass filter is thus incorrectly terminated in its pass band.

If, however, a series inductance be added to the low-pass filter, as in Fig. 697c (*i.e.* the final series inductance of the low-pass filter be increased), the added series inductance, together with the shunting reactance of the high-pass filter, will form an approximate m -derived terminating half-section for the low-pass filter.

For an $m = 0.6$ termination, the added inductance will be 0.6 of the series inductance of a prototype half-section. Similarly the

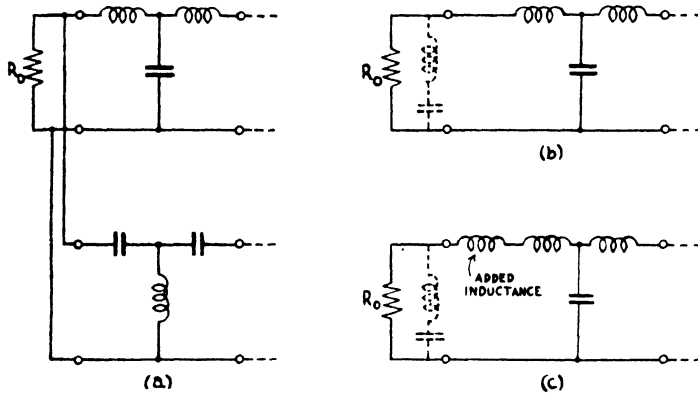


FIG. 697.—High-pass and low-pass filters in parallel.
 (a) High-pass and low-pass filters in parallel.
 (b) Equivalent circuit in the low-pass range.
 (c) Added inductance giving half-section termination.

final condenser of the high-pass filter may be modified so that in the high-pass range the high-pass filter is terminated in an equivalent m -derived half-section ($m = 0.6$). If both these modifications are carried out, both filters will be correctly terminated over their pass ranges.

Band-pass filters

The same principle applies when a number of band-pass filters with adjacent pass bands are connected in parallel. For, considering any one filter, the shunt reactance due to all the other filters in

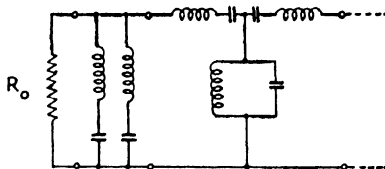


FIG. 698.—Equivalent circuit in the pass band of one of several band-pass filters in parallel.

parallel can be represented (at frequencies just outside the pass band) by two series resonant circuits in parallel (see Fig. 698).

The resonant frequencies of these circuits will be respectively just above and just below the cut-off frequencies of the filter under consideration. These resonant frequencies may be regarded as $f_{1\infty}$ and $f_{2\infty}$ for the filter considered; for these circuits are, in fact, the shunt arm of an m -derived band-pass filter (see Fig. 688). Thus to give an $m = 0.6$ half-section termination, it is necessary to increase the last series impedance of each band-pass filter by 0.6 of the series impedance of the prototype half-section.

Compensating networks

The above argument applies only to a band-pass filter that has at least one other filter above and below it; it does not hold for the first and last of a number of adjacent filters. To provide correct terminations for these filters, some additional shunt network must be provided. Such a network is called a "compensating network", and consists of two series resonant circuits in parallel (or any circuit with two series resonances); these resonant frequencies are arranged just below the lower cut-off frequency of the first filter and just above the higher cut-off frequency of the last filter. These resonant circuits take the place of the two "missing" band-pass filters, and thus complete the correct m -derived terminating half-sections for the first and last filters.

Impedance transformation in band-pass filters

It is often useful to be able to transform the impedance inside a band-pass filter—particularly when component values would otherwise be inconveniently large or small. The use of ordinary transformers for this purpose would involve taking into account such considerations as the leakage inductance, the primary inductance,

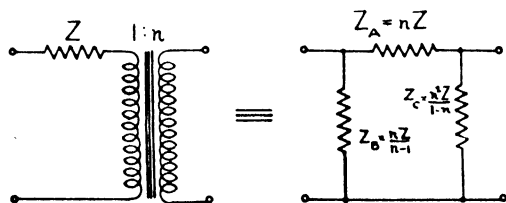


FIG. 699.— π section equivalent of an ideal transformer and series impedance.

and the capacity of the transformer windings, all of which would affect the performance of the filter. Fortunately if Z represents a capacity (see Fig. 699), it is possible to find an equivalent circuit for the transformer in terms of capacities only.

Fig. 699 shows an ideal transformer of turns ratio $1:n$ with a series impedance Z in the primary, together with its equivalent π section which was given in Chapter 13. This equivalence may be

verified by equating open- and short-circuit input impedances, as follows:—

Let Z_1 be the impedance looking into the primary with the secondary short-circuited.

$$\text{Then } Z_1 = Z = \frac{Z_A Z_B}{Z_A + Z_B} \quad (93)$$

Let Z_2 be the impedance looking into the secondary with the primary short-circuited.

$$\text{Then } Z_2 = n^2 Z = \frac{Z_A Z_O}{Z_A + Z_O} \quad (94)$$

The impedance looking into either winding with the other open-circuited is infinite (since it is an ideal transformer).

$$\therefore \frac{Z_B (Z_A + Z_O)}{Z_A + Z_B + Z_O} = \frac{Z_O (Z_A + Z_B)}{Z_A + Z_B + Z_O} = \infty$$

$$\text{Hence } Z_A + Z_B + Z_O = 0 \quad (95)$$

From (93) and (95):—

$$Z = -\frac{Z_A Z_B}{Z_O} \quad (96)$$

From (94) and (95):—

$$n^2 Z = -\frac{Z_A Z_O}{Z_B} \quad (97)$$

Multiplying (96) and (97):—

$$n^2 Z^2 = Z_A^2$$

$$\therefore Z_A = nZ \quad (98)$$

(The other root, $Z_A = -nZ$, actually gives rise to a second equivalent circuit.)

From (95) and (98):—

$$Z_B + Z_O = -nZ \quad (99)$$

From (96) and (98):—

$$\frac{Z_B}{Z_O} = -\frac{1}{n} \quad (100)$$

Eliminating Z_B from (99) and (100):—

$$Z_O - \frac{Z_O}{n} = -nZ$$

$$\therefore Z_O = \frac{n^2 Z}{1 - n} \quad (101)$$

From (100) and (101):—

$$Z_B = \frac{nZ}{n - 1} \quad (102)$$

Thus an equivalent π network is as shown in Fig. 699.

The use of this transformation will be illustrated by an example of band-pass filter design taken from a multi-channel VF telegraph system.

Design of band-pass filters for a multi-channel VF telegraph system

All the band-pass channel filters have a design impedance $R_0 = 600\Omega$, a bandwidth $f_2 - f_1 = 120$ c/s, and mid-band frequencies 420, 540, 660 and so on up to 1980 c/s. From equations

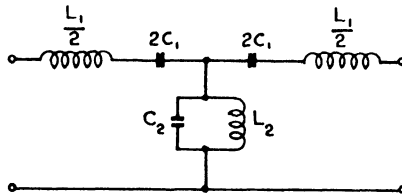


FIG. 700.—Prototype band-pass T section.

64 to 67, the values for a prototype, as shown in Fig. 700, are :—

$$L_1 = \frac{R_0}{\pi(f_2 - f_1)}, C_1 = \frac{f_2 - f_1}{4\pi R_0 f_1 f_2}, L_2 = \frac{R_0(f_2 - f_1)}{4\pi f_1 f_2}, C_2 = \frac{1}{\pi R_0(f_2 - f_1)}$$

Hence all the channel filters have :—

$$\frac{L_1}{2} = \frac{600}{2\pi \cdot 120} = 0.797\text{H} \text{ and } C_2 = \frac{1}{\pi \cdot 600 \cdot 120} = 4.421\mu\text{F}$$

Taking as an example the filter with a mid-band frequency of 1500 c/s :—

$$2C_1 = \frac{2 \cdot 120 \cdot 10^6}{4\pi \cdot 600 \cdot 1500^2} = 0.01415\mu\text{F}$$

and
$$L_2 = \frac{600 \cdot 120}{4\pi \cdot 1500^2} = 2.55\text{mH}$$

Note that the value of C_2 ($4.421\mu\text{F}$) is large and the inductance L_2 is small. C_2 would have to be a paper dielectric condenser, owing to the large cost and bulk of a mica condenser of this capacity ; but paper condensers are not stable enough for filter construction, and tend to have a high loss. L_2 would have a very small number of turns (say about 100) and an inaccuracy of ± 1 turn might affect the inductance by as much as ± 2 per cent., which is not sufficiently accurate for this filter. If the impedance at the middle of the section could be increased, a larger inductance and a smaller capacity could be used, having of course the same resonant frequency as the original shunt circuit. This can be done in theory by the use of two ideal transformers, as shown in Fig. 701a.

Alternatively it can be done by replacing the ideal transformer and the series condenser $2C_1$ by its equivalent π section as in Fig. 701b. The final form of the filter is as shown in Fig. 701c, the various shunt capacities having been combined where possible.

n can have any value that makes the components of the final section physically realisable. For example, n must be greater than one, or the capacities $\frac{2(n-1)}{n} C_1$ will not be realisable. A



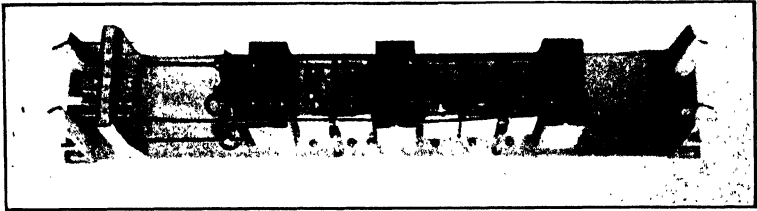



PLATE 34.—Multi-channel VF telegraph band-pass filter, mid-band frequency 1500 c/s.

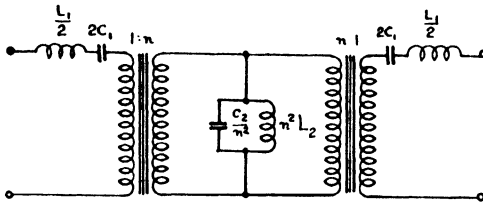

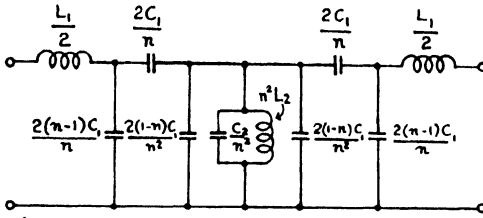(a) Impedance transformation using ideal transformers



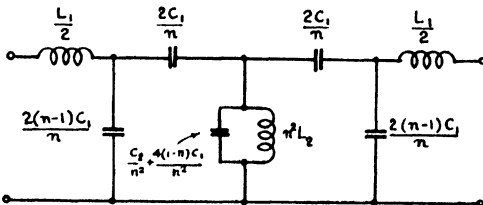(b) Impedance transformation using equivalent T sections



(c) Band-pass section with internal impedance transformation

FIG. 701.—Prototype band-pass T section with internal impedance transformation.

convenient value of n is that value which makes all the shunt capacities equal. This gives an equation :—

$$\frac{2(n-1)C_1}{n} = \frac{C_2}{n^2} + \frac{4(1-n)}{n^2}C_1$$

$$2n(n-1)C_1 = C_2 + 4(1-n)C_1$$

$$2n^2 + 2n = \frac{C_2}{C_1} + 4$$

$$4n^2 + 4n + 1 = \frac{2C_2}{C_1} + 9$$

$$n = \frac{1}{2} \left[\sqrt{\frac{2C_2}{C_1} + 9} - 1 \right] \quad (103)$$

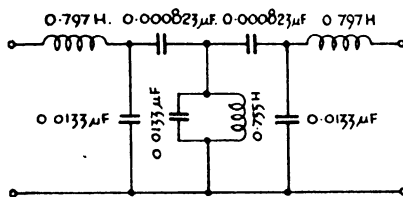


FIG. 702.—Illustrating design of prototype band-pass filter with internal impedance transformation.

In the case under consideration :—

$$C_2 = 4.421 \mu\text{F} \quad \text{and} \quad C_1 = 0.007075 \mu\text{F}$$

$$\therefore n = \frac{1}{2} \left[\sqrt{\frac{8.842}{0.007075} + 9} - 1 \right] = \frac{1}{2} [35.4 - 1]$$

$$\therefore n = 17.2 \quad \text{and} \quad n^2 = 296$$

The shunt condensers now become :—

$$\frac{2(n-1)}{n} C_1 = 0.0133 \mu\text{F}$$

The series condensers are then :—

$$\frac{2C_1}{n} = 0.000823 \mu\text{F}$$

and the shunt inductance is :—

$$n^2 L_2 = 0.755 \text{ H}$$

Hence the complete section is as shown in Fig. 702.

If, as is the case in a multi-channel VF telegraph system, the filters are all connected in parallel at one end, the series impedances

at one end will have to be increased by 0.6 of their value (to give an $m = 0.6$ termination). This must be done before the transformation of the central section is carried out; that is, the prototype is first modified, and then the transformation is carried out using the same value of n as before.

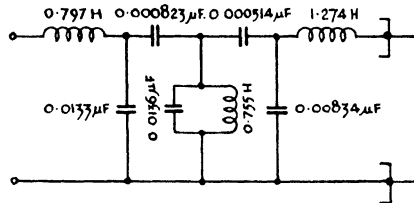


FIG. 703.—Prototype band-pass filter with internal impedance transformation, modified for parallel connection with other filters.

Fig. 703 shows the complete filter after modification in this way. The other channel filters are connected in parallel with the right-hand end.

LATTICE FILTER SECTIONS

The majority of filters in common use are of the ladder type, but "lattice" filters are occasionally encountered.

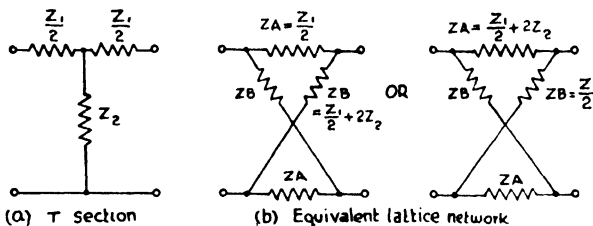


FIG. 704.—Equivalence of T section and lattice section.

In Fig. 704 is shown the equivalent lattice section for a normal T section of the ladder type. Clearly this equivalence is not complete, for the lattice section is inherently a balanced section, whereas the T section is not. They are, however, equivalent from the point of view that they have the same characteristic impedance and the same propagation constant. A mathematical proof of this will be found in Chapter 13, but the equivalence may be verified quite simply as follows:—

Since $Z_0 = \sqrt{Z_{s0} \cdot Z_{o0}}$ and $\tanh \gamma = \sqrt{\frac{Z_{s0}}{Z_{o0}}}$ for any network,

it follows that if two networks have the same open-circuit and

short-circuit impedances, they must therefore have the same values of characteristic impedance and propagation constant.

Considering the open-circuit impedance :—

$$\text{For the T section.} \quad Z_{oo} = \frac{Z_1}{2} + Z_2 \quad (104)$$

$$\text{For the lattice section } Z_{oo} = \frac{1}{2}(Z_A + Z_B) \quad (105)$$

If these are the same.—

$$Z_A + Z_B = Z_1 + 2Z_2 \quad (106)$$

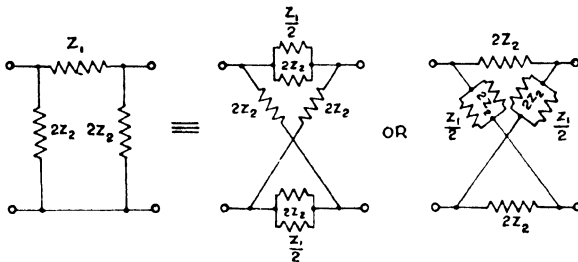


FIG. 705.—Equivalence of π section and lattice section.

Considering the short-circuit impedance :—

$$\text{For the T section.} \quad Z_{so} = \frac{Z_1}{2} + \frac{Z_1 Z_2}{2\left(\frac{Z_1}{2} + Z_2\right)}$$

$$\text{i.e.} \quad Z_{so} = \frac{\frac{Z_1^2}{4} + Z_1 Z_2}{\frac{Z_1}{2} + Z_2} \quad (107)$$

$$\text{and for the lattice section.} \quad Z_{so} = \frac{2Z_A Z_B}{Z_A + Z_B} \quad (108)$$

If these are the same :—

$$\frac{2Z_A Z_B}{Z_A + Z_B} = \frac{\frac{Z_1^2}{4} + Z_1 Z_2}{\frac{Z_1}{2} + Z_2}$$

or using equation (106) :—

$$Z_A Z_B = \frac{Z_1^2}{4} + Z_1 Z_2 \quad (109)$$

Clearly the solution of equations 106 and 109 is:—

$$Z_A = \frac{Z_1}{2} \quad \text{or} \quad \frac{Z_1}{2} + 2Z_2 \quad (110)$$

and

$$Z_B = \frac{Z_1}{2} + 2Z_2 \quad \text{or} \quad \frac{Z_1}{2} \quad (111)$$

In the same way the equivalence between a π section and a lattice section may be established, as in Fig. 705.

This equivalence may be used to derive the lattice equivalents of the ladder prototype low-pass filter; other ladder filters may be treated in the same way if their lattice equivalents are required.

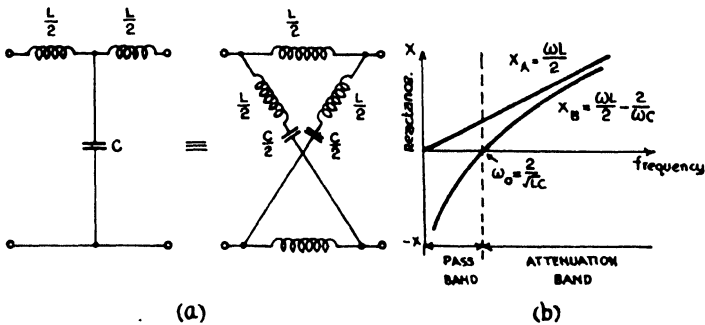


FIG. 706.—Lattice equivalent of prototype T section low-pass filter.

Fig. 706a shows a prototype T low-pass filter section having a cut-off frequency $\frac{1}{\pi\sqrt{LC}}$, and its lattice equivalent. Fig. 707a shows the corresponding π low-pass filter section, and its lattice equivalent.

If a lattice filter section of unknown type is encountered it may

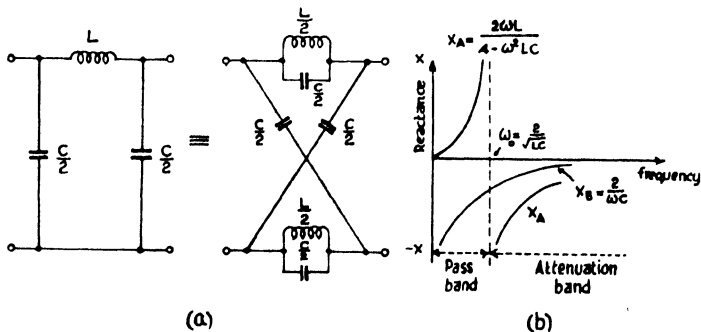


FIG. 707.—Lattice equivalent of prototype π section low-pass filter.

be explored by the reactance sketch method. For in the general lattice network of Fig. 704 :—

$$Z_0 = \sqrt{Z_A Z_B} \tag{112}$$

Thus if Z_A and Z_B are reactances of opposite sign, Z_0 is a pure resistance and the filter has zero attenuation. If, on the other hand, Z_A and Z_B are reactances of the same sign, then Z_0 is a pure reactance and the filter attenuates.

Considering the lattice filter sections of Figs. 706a and 707a, the corresponding reactance sketches are shown in Figs. 706b and 707b. In both cases it will be seen from the reactance sketches that the filters are low-pass, having a cut-off frequency $f_0 = \frac{1}{\pi\sqrt{LC}}$.

Insertion loss of a lattice section filter

Like any other 4-terminal network, the insertion loss and insertion phase-shift of a lattice filter may be determined, using equations 7 and 8 of Chapter 13 (page 566).

When, however, such a network is inserted between purely resistive impedances (such as, say, the filter's design impedances), the problem is best approached from first principles.

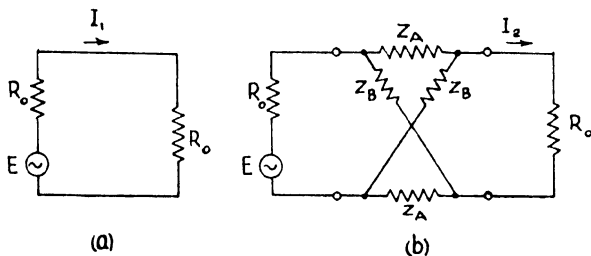


FIG. 708.—Calculation of the insertion loss of a lattice section.

Consider a generator of EMF E and internal impedance R_0 working into load R_0 (Fig. 708a). Let the current flowing be I_1 .

If a lattice network now be inserted between the generator and the load (Fig. 708b), let the new current flowing be I_2 .

Applying Kirchoff's laws to Fig. 708b, it may be shown that :—

$$I_2 = -\frac{E}{2} \cdot \frac{Z_A - Z_B}{(R_0 + Z_A)(R_0 + Z_B)}$$

Considering Fig. 708a :—

$$I_1 = \frac{E}{2R_0}$$

Hence
$$\frac{I_1}{I_2} = -\frac{(R_0 + Z_A)(R_0 + Z_B)}{R_0(Z_A - Z_B)}$$

Let $Z_A = jX_A$ and $Z_B = jX_B$

Then
$$\frac{I_1}{I_2} = - \frac{(R_0 + jX_A)(R_0 + jX_B)}{jR_0(X_A - X_B)}$$

$$\frac{I_1}{I_2} = - \frac{R_0(X_A + X_B) - j(R_0^2 - X_A X_B)}{R_0(X_A - X_B)} \quad (113)$$

Consider first the modulus of this expression, which determines the insertion loss :—

$$\begin{aligned} \left| \frac{I_1}{I_2} \right| &= \frac{\sqrt{R_0^2(X_A + X_B)^2 + (R_0^2 - X_A X_B)^2}}{R_0(X_A - X_B)} \\ &= \frac{\sqrt{(R_0^2 + X_A^2)(R_0^2 + X_B^2)}}{R_0(X_A - X_B)} \\ &= \frac{1}{\frac{X_A}{\sqrt{R_0^2 + X_A^2}} \cdot \frac{R_0}{\sqrt{R_0^2 + X_B^2}} - \frac{R_0}{\sqrt{R_0^2 + X_A^2}} \cdot \frac{X_B}{\sqrt{R_0^2 + X_B^2}}} \\ &= \frac{1}{\sin \theta_1 \cos \theta_2 - \cos \theta_1 \sin \theta_2} \\ &= \frac{1}{\sin(\theta_1 - \theta_2)} \end{aligned}$$

where $\theta_1 = \tan^{-1} \frac{X_A}{R_0}$ and $\theta_2 = \tan^{-1} \frac{X_B}{R_0}$

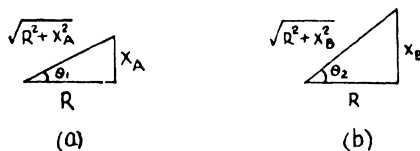


FIG. 709

The insertion loss is given by :—

$$20 \log_{10} \left| \frac{I_1}{I_2} \right| = 20 \log_{10} \frac{1}{\sin(\theta_1 - \theta_2)} \text{ db} \quad (114)$$

or
$$\log_e \left| \frac{I_1}{I_2} \right| = \log_e \frac{1}{\sin(\theta_1 - \theta_2)} \text{ nepers} \quad (115)$$

Considering the phase angle of expression 113, it is seen that :—

$$\begin{aligned} \beta &= \tan^{-1} - \frac{R_0^2 - X_A X_B}{R_0(X_A + X_B)} \\ &= \tan^{-1} - \frac{1 - \frac{X_A}{R_0} \cdot \frac{X_B}{R_0}}{\frac{X_A}{R_0} + \frac{X_B}{R_0}} \end{aligned}$$

$$= \tan^{-1} \frac{1 - \tan \theta_1 \tan \theta_2}{\tan \theta_1 + \tan \theta_2}$$

$$\therefore \beta = \tan^{-1} \frac{-1}{\tan (\theta_1 + \theta_2)}$$

Hence the insertion phase-shift β is given by:—

$$\beta = \theta_1 + \theta_2 \pm (2n + 1) \frac{\pi}{2} \tag{116}$$

Both equations 114 and 115, and equation 116, are great simplifications on equations 7 and 8 of Chapter 13 (page 566), which are the equations employed for the determination of insertion losses and insertion phase angles of ladder filters. It will be noted, therefore, that in many cases it is convenient to convert a ladder filter into its corresponding lattice, so that the above insertion loss equations may be employed.

Equivalent bridged-T sections

As may be seen by studying the low-pass filter sections of Figs. 706*a* and 707*a*, the main disadvantage of lattice sections is in

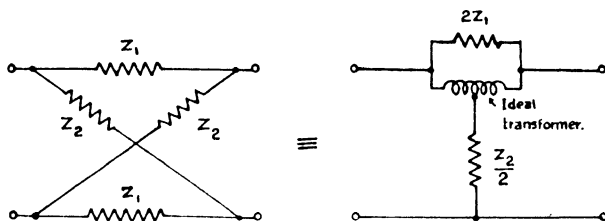


FIG. 710.—Bridged T equivalent of a lattice section (using transformer).

the greater number of components employed ; this may be obviated to a certain extent by converting from a lattice section to a bridged-T section as shown below.

From Figs. 711*a* and *b*, it will be seen that, for the bridged-T section:—

$$Z_{oo} = \frac{Z_2}{2} + \frac{1}{4} \cdot 2Z_1 = \frac{Z_1 + Z_2}{2} \tag{117}$$

and

$$Z_{so} = \frac{2Z_1 \times 4 \cdot \frac{Z_2}{2}}{2Z_1 + 4 \cdot \frac{Z_2}{2}} = \frac{2Z_1 Z_2}{Z_1 + Z_2} \tag{118}$$

By comparison with equations 105 and 108 the equivalence of Fig. 710 is established. Using this equivalence, lattice low-pass sections may be replaced by bridged-T low-pass sections as in Fig. 712.

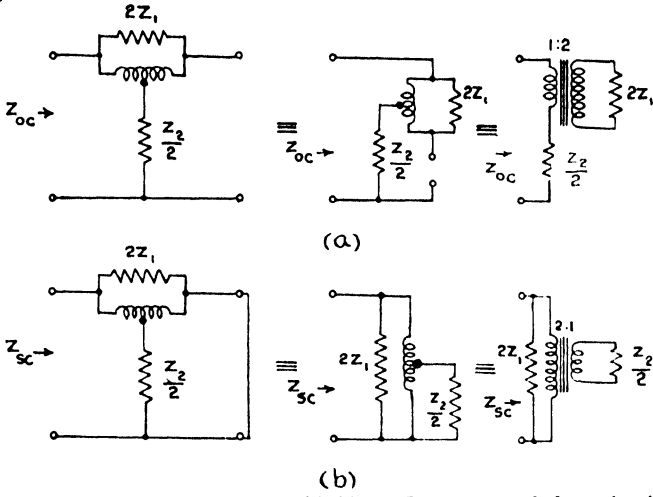


FIG. 711.—Equivalent circuit of bridged-T on open and short circuit.

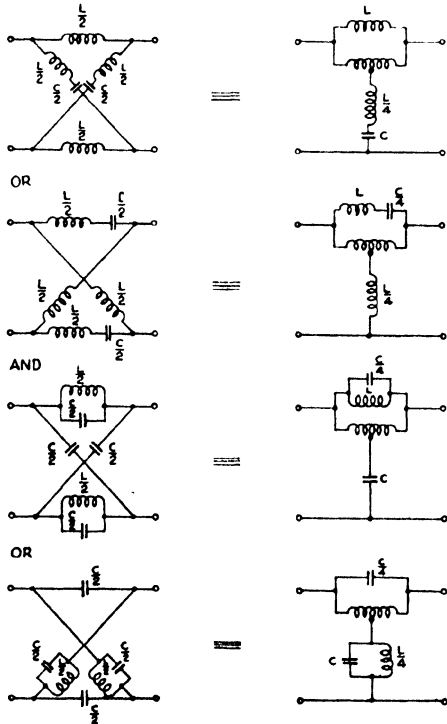


FIG. 712.—Bridged-T equivalents of lattice low-pass filter sections.

The limitations on such filter sections are imposed by the discrepancies introduced by substituting a practical transformer for the ideal transformer.

CRYSTAL FILTERS

Certain substances, notably quartz, exhibit what is known as the "piezo-electric" effect; that is to say, a mechanical strain applied to a suitably cut piece of the substance causes an EMF to be developed between two surfaces of that piece; and conversely, an EMF applied between two faces of the piece cause a mechanical deformation. These effects are used in piezo-electric microphones and similar devices.

Slices cut from a quartz crystal also have another important property: they behave electrically as a resonant circuit, of extremely high Q , resonant at the natural frequency of mechanical vibration of the slice.

The complete quartz crystal in natural state is of the general shape shown in Fig. 713*a*, and for convenience of reference, three

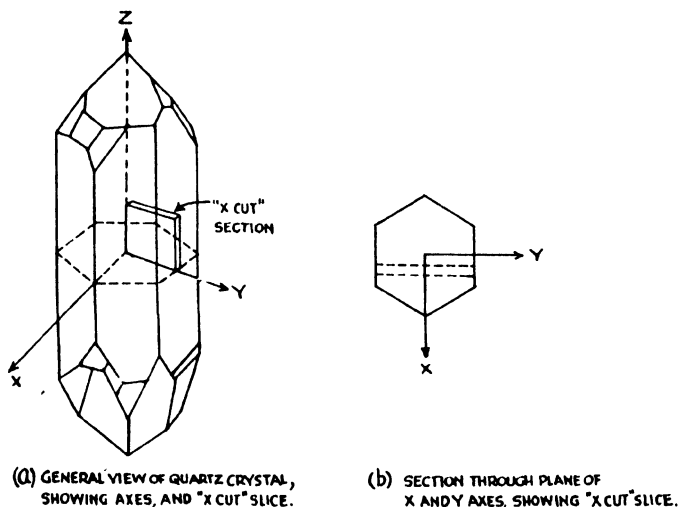


FIG. 713.—Quartz crystal showing "X cut" slice.

axes through the crystal are defined as follows: the vertical axis passing through both "points" of the crystal is called the optical or Z-axis; the line at right angles to the Z-axis parallel to any major face of the crystal is called the electrical or X-axis; and the line at right angles to both these axes, and perpendicular to any face of the crystal, is called the mechanical or Y-axis. Slices cut from the crystal for various purposes may then be described in terms of the angles between them and the three axes of the crystal; thus a slice cut with its faces perpendicular to the X-axis is called

an "X cut" crystal, as shown in Fig. 713, and this "cut" is frequently used in filters.

If such a slice be mounted between two flat metal plates to which electrical connection can be made (see Fig. 714a), it is found to behave like the equivalent circuit given in Fig. 714b. C , L , and R are merely the electrical equivalents of corresponding mechanical properties of the crystal, and their values are determined by the dimensions and physical constants of the crystal material. C' is the electrical capacity between the faces of the crystal, and in practice its effective value may be increased by the capacity of the wiring.

The series circuit composed of C , L , and R resonates at the natural (mechanical) resonant frequency of the crystal; let this frequency be f_R . In addition to this series resonant frequency, the circuit of Fig. 714b also has an anti-resonant frequency; let this be f_A . The reactance sketch for the crystal is therefore of the

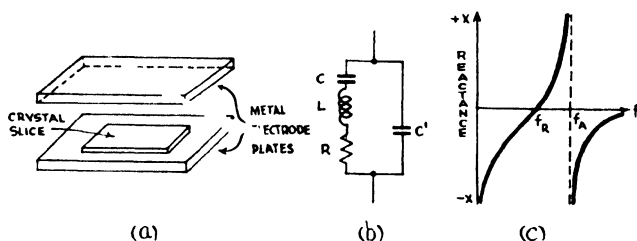


FIG. 714.—Equivalent circuit of quartz crystal.

(a) Crystal in "solid" type of mounting. (b) Equivalent circuit of quartz crystal. (c) Reactance sketch for quartz crystal.

form shown in Fig. 714c. Neglecting the equivalent resistance R (which, owing to the high Q , is relatively small), the impedance of the circuit of Fig. 714b is:—

$$\begin{aligned}
 Z &= \frac{-j \left(j\omega L - \frac{j}{\omega C} \right)}{j\omega L - \frac{j}{\omega C} - \frac{j}{\omega C'}} \\
 &= \frac{-j (\omega^2 LC - 1)}{\omega CC' \left(\omega^2 L - \frac{C + C'}{CC'} \right)}
 \end{aligned}$$

Thus the series resonant frequency is given by:—

$$\omega_R^2 = \frac{1}{LC}, \quad \text{or} \quad f_R = \frac{1}{2\pi\sqrt{LC}} \quad (119)$$

and the anti-resonant frequency by :—

$$\omega_A^2 = \frac{1}{L \cdot \frac{CC'}{C + C'}}$$

$$\begin{aligned} \therefore f_A &= \frac{1}{2\pi \sqrt{L \cdot \frac{CC'}{C + C'}}} \\ &= \frac{\sqrt{1 + \frac{C}{C'}}}{2\pi \sqrt{LC}} \\ &= f_R \cdot \sqrt{1 + \frac{C}{C'}} \end{aligned} \tag{120}$$

This can be expanded by the Binomial Theorem as :—

$$\begin{aligned} f_A &= f_R \left(1 + \frac{C}{C'} \right)^{\frac{1}{2}} \\ &= f_R \left\{ 1 + \frac{1}{2} \cdot \frac{C}{C'} + \frac{(\frac{1}{2}) \cdot (-\frac{1}{2})}{1 \cdot 2} \cdot \left(\frac{C}{C'} \right)^2 + \dots \right\} \end{aligned}$$

For the crystal itself, with no stray capacities, C' is normally 125 times C , so that the ratio $\frac{C}{C'}$ is $\frac{1}{125}$. Terms containing second and higher powers of $\frac{C}{C'}$ can therefore be neglected, so that :—

$$f_A = f_R \left(1 + \frac{C}{2C'} \right) \cong 1.004 f_R \tag{121}$$

The separation between the resonant and anti-resonant frequencies is therefore :—

$$\begin{aligned} f_A - f_R &= f_R \left(1 + \frac{C}{2C'} \right) - f_R \\ \text{i.e. } f_A - f_R &= f_R \cdot \frac{C}{2C'} = 0.4 \text{ per cent. of } f_R \end{aligned} \tag{122}$$

Stray capacity in parallel with the crystal has the effect of increasing the effective value of C' , so that $\frac{C}{C'} < \frac{1}{125}$; it therefore lowers the anti-resonant frequency f_A and reduces the separation ($f_A - f_R$).

If the dimensions of an X-cut quartz crystal slice be denoted by x , y , and z (in centimetres) in the directions of the X, Y, and Z axes respectively, the component values of the equivalent circuit

can be found approximately from the following empirical formulae:—

$$L = 115 \frac{xy}{z} \quad \text{Henries} \quad (123)$$

$$C = 0.0032 \frac{yz}{x} \quad \mu\mu\text{F} \quad (124)$$

$$C' = 0.40 \frac{yz}{x} \quad \mu\mu\text{F} \quad (125)$$

No useful formula can be given for R ; for although the actual value of R for the crystal may be very low, its effective value is considerably increased in practice by the mechanical damping of the crystal mounting. The inherent Q of a crystal slice is almost infinite; but even with the most careful mounting, in vacuo, with sprayed gold electrodes, this is reduced to several hundred thousand; and with normal mountings, it is of the order of 5000 to 20,000. Even these values, however, are appreciably higher than those obtainable from circuits using normal type inductances and capacities, which seldom yield a Q higher than about 200.

Example.—

A quartz crystal slice measures 0.2, 2.5, and 0.5 cm in the directions of the X , Y , and Z axes respectively (see Fig. 715a).

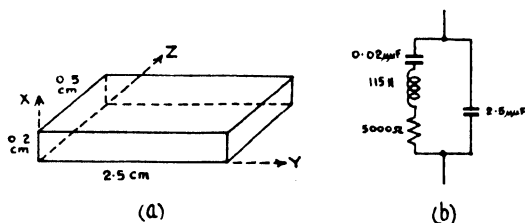


FIG. 715.—Dimensions and equivalent circuit of an actual crystal.

Find its equivalent circuit and its resonant and anti-resonant frequencies.

From equations 123, 124, and 125:—

$$L = 115 \frac{xy}{z} = 115 \cdot \frac{0.2 \cdot 2.5}{0.5} = 115 \text{ H}$$

$$C = 0.0032 \frac{yz}{x} = 0.0032 \cdot \frac{2.5 \cdot 0.5}{0.2} = 0.02 \mu\mu\text{F}$$

$$C' = 0.40 \frac{yz}{x} = 0.40 \cdot \frac{2.5 \cdot 0.5}{0.2} = 2.5 \mu\mu\text{F}$$

$$f_{\pi} = \frac{1}{2\pi \sqrt{LC}} = \frac{1}{2\pi \sqrt{115 \cdot 0.02 \cdot 10^{-12}}} = 104.8 \text{ kc/s}$$

$$f_A = \frac{1}{2\pi\sqrt{L \cdot \frac{CC'}{C+C'}}} = \frac{1}{2\pi\sqrt{115 \cdot \frac{0.02 \cdot 2.5 \cdot 10^{-12}}{2.52}}} = 105.2 \text{ kc/s}$$

This particular crystal slice was found to have a Q of 15,000, corresponding to an equivalent resistance of:—

$$R = \frac{\omega L}{Q} = \frac{2\pi \cdot 104.8 \cdot 10^3 \cdot 115}{15,000} = 5000 \Omega.$$

The equivalent circuit is then as shown in Fig. 715b.

Single-crystal filter

The simplest method of employing a crystal in a filter circuit is shown in Fig. 716a. Here the behaviour of the crystal may be determined by considering it to be replaced by its equivalent circuit (see Fig. 714b); thus it presents a low impedance at its resonant frequency, an almost infinite impedance at its anti-resonant frequency, and a high impedance at all other frequencies. The attenuation-frequency curve for this filter is therefore of the form shown in Fig. 716b.

The anti-resonant frequency f_A can be altered by varying the effective shunt capacity across the crystal (C' in Fig. 714b). This can conveniently be done by using a centre-tapped input transformer and a variable "balancing" condenser C_B , as shown in

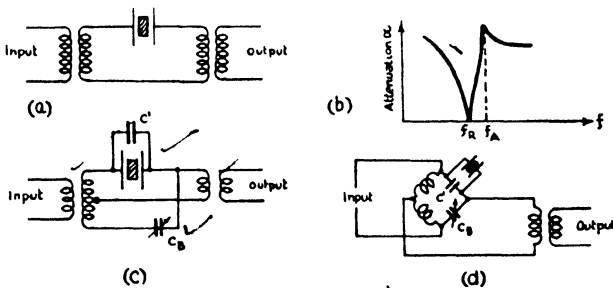


FIG. 716.—Single-crystal band-pass filter.

Fig. 716c, which can be looked upon as a bridge circuit as in Fig. 716d. If C_B be adjusted to zero capacity, the circuit is essentially the same as Fig. 716a, but with only half the input voltage utilised.

If C_B then be increased, some current will reach the output through it, approximately in anti-phase to that passing *via* C' ; the resulting current reaching the output is therefore less than that passing *via* C' , and the effect is the same as would be obtained if C' had been reduced. Anti-resonance occurs at that frequency for which the capacitive current passing *via* C' is equal in magnitude to the

inductive current passing *via* C , L , and R ; reduction of the current reaching the output *via* C' therefore causes the anti-resonance to occur at a frequency for which the inductive current through C , L , and R is less—*i.e.* at a higher frequency.

If C_B is increased until it is equal to C' , no anti-resonance will occur; while if it be further increased, the current reaching the output *via* C_B will be greater than that *via* C' , and the anti-resonance will occur at a frequency for which the current reaching the output *via* C , L , and R is capacitive—*i.e.*, at a frequency *below* f_B . Thus as C_B is increased from zero, the anti-resonant frequency f_A is first increased from its original value, and reaches infinity when $C_B = C'$; further increase of C_B raises f_A from zero frequency until it approaches f_B when C_B is made very large.

A filter of this type is especially useful when it is desired to transmit one particular frequency, and to attenuate a neighbouring frequency severely. For most communications purposes, however, comparatively wide bands of frequencies have to be passed, and for this purpose the response curve of Fig. 716*b* is unsuitable; for the frequency band over which the attenuation is low is extremely narrow. The width of the response curve can be modified to a certain extent by varying the impedance of the input and output circuits; for maximum sharpness (*i.e.*, highest Q and minimum bandwidth) both input and output impedances should be low, but for maximum output voltage at the resonant frequency the output impedance should be high. Even when its sharpness is reduced by increasing the input and output impedances, the response of a filter of this type is unsatisfactory for many purposes owing to its pointed nature. Various types of filter have therefore been developed in which advantage is taken of the extremely high Q of quartz crystals, to furnish a band-pass filter with a very low and constant attenuation in the pass bands, but with a sharpness of cut-off approaching that of "ideal" resistanceless filters.

Double-crystal band-pass filter

A filter circuit giving a pass band up to about 1 per cent. of the mid-band frequency is shown in Fig. 717*a*. The resonant frequencies of the two crystals Cr_1 and Cr_2 are at the lower and upper edges of the pass band respectively, while the input and output circuits are tuned to the mid-band frequency. At frequencies below the lower edge of the pass band, both crystals present a capacitive impedance; owing to the "push-pull" input and parallel output connections, the outputs from the two crystals are in anti-phase, so that the resultant output is less than that from one crystal alone. Between the resonant frequencies of the two crystals, Cr_1 presents an inductive and Cr_2 a capacitive impedance; but owing to the method of connection, the two outputs are additive, so that their combined output is greater than that obtained from either crystal alone. Above the higher edge of the pass band, both crystals present an inductive impedance, but

their outputs, being in anti-phase, tend to cancel out. Thus a low attenuation is obtained between the resonant frequencies (f_1 and f_2) of the two crystals, and a high attenuation outside this band.

If a balancing condenser C_b is so adjusted that the shunt capacities across the two crystals are equal, no anti-resonance occurs. But if this condenser be so adjusted that the shunt capacity across the higher-frequency crystal Cr_2 exceeds that across Cr_1 an anti-resonance occurs just above the resonant frequency f_2 of Cr_2 ; and a second anti-resonance occurs just below the resonant frequency f_1 of the lower-frequency crystal Cr_1 , as explained above in connection with the single-crystal filter. The attenuation-frequency curve then obtained is as shown in Fig. 717*b*, and it will

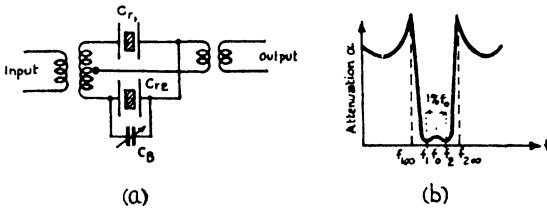


FIG. 717.—Double-crystal band-pass filter.

be noted that there is an increase in attenuation at the centre of the pass band; the wider the pass band, the more serious is this increase. For this reason, filters of this type are used only when the bandwidth required is less than about 1 per cent. of the mid-band frequency; thus for a bandwidth of 3000 c/s, this type of filter would be satisfactory for mid-band frequencies above 300 kc/s. In line communication, however, crystals are employed chiefly as the reactive elements in band-pass filter circuits of conventional type.

T type crystal filters

The T type crystal filter forms a good example of the use of crystals as the reactive elements in conventional filter circuits,

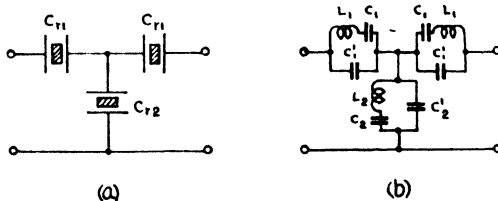


FIG. 718.—T type crystal band-pass filter.

and its analysis shows clearly how the reactance sketches for crystals used in this way are manipulated. This type of filter is shown in Fig. 718*a*, and its equivalent circuit (neglecting resistance) in Fig. 718*b*.

The crystals Cr_1 in the series arms are carefully selected to have a series resonant frequency exactly equal to the anti-resonant frequency of the crystal in the shunt arm. Let the resonant and anti-resonant frequencies of the series arms be f_{R1} and f_{A1} respectively, and those of the shunt arm f_{R2} and f_{A2} ; then $f_{R1} = f_{A2}$. Let the reactance of the series arm be X_1 , and that of the shunt arm be X_2 ; the variation with frequency of X_1 and X_2 is then as shown in Fig. 719a. From this can be drawn the reactance sketch for the filter, as in Fig. 719b.


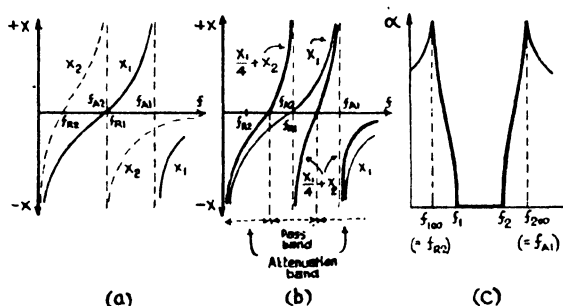


FIG. 719.—Reactance sketch for a T type crystal band-pass filter.

It will be seen that the filter has a band-pass characteristic, with a pass band from f_1 to f_2 , and frequencies of infinite attenuation at $f_{1\infty} = f_{R2}$ and $f_{2\infty} = f_{A1}$. The attenuation-frequency characteristic, shown in Fig. 719c, is seen to be of the same form as that of an m -derived band-pass section; while the bandwidth $(f_2 - f_1)$ is seen to be less than $(f_{A1} - f_{R2})$ —i.e., less than 0.8 per cent. of the mid-band frequency.

Lattice type crystal filters

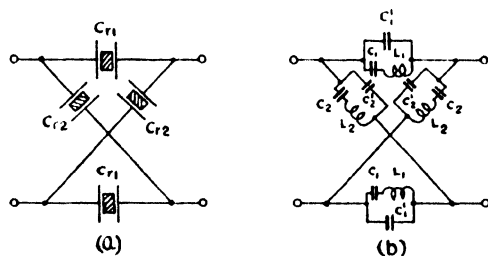Crystal filters are frequently made up in lattice form, as shown in Fig. 720a, with the equivalent circuit as in Fig. 720b.



Lattice crystal filter, with equivalent circuit.

FIG. 720.—Lattice crystal band-pass filter.

The crystals Cr_1 are a carefully matched pair, as also are Cr_2 . The crystals are so cut that the series resonant frequency of one pair corresponds with the anti-resonant frequency of the other. Using the method set out on page 686, the reactance sketch is shown in Fig. 721a, indicating that the filter has a band-pass characteristic. The pass band is seen to extend from $f_1 = f_{R1}$ to $f_2 = f_{A2}$, so that the bandwidth is 0.8 per cent. of the mid-band frequency $f_0 = f_{A1} = f_{R2}$. The corresponding attenuation-frequency characteristic is shown in Fig. 721b.

By suitable choice of the crystals in the series and lattice arms, the reactance curves may be made to cross as shown in Fig. 721c. The points of intersection correspond to equal impedances in

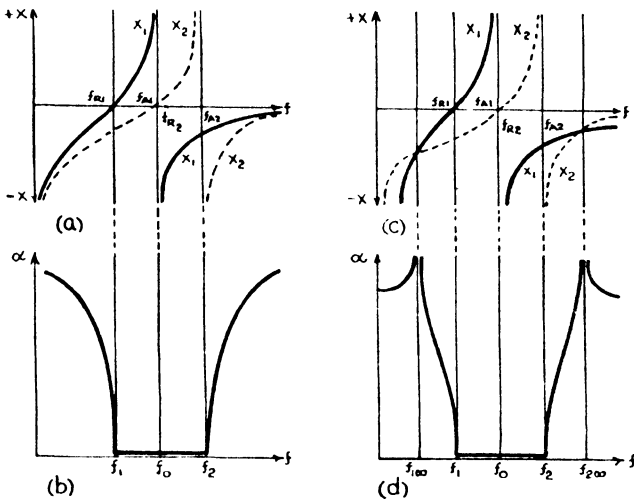


FIG. 721.—Reactance sketch for a lattice crystal band-pass filter.

the series and lattice arms, giving rise to frequencies of infinite attenuation $f_{1\infty}$ and $f_{2\infty}$, as shown in Fig. 721d, since the load would now be across the diagonal of a balanced bridge. Such an arrangement gives considerable discrimination against frequencies immediately outside the pass band.

In lattice crystal filter circuits, a pair of identical crystals are required in the two series arms, and a second pair in the two lattice arms. In practice, each such pair of identical crystals can be replaced by a single crystal slice with two independent pairs of terminals. Each face of the slice carries two metal coatings, usually of aluminium, insulated from each other, the two coatings on one end of the crystal slice being used for one arm of the circuit, and those on the other end for the opposite arm. The whole slice vibrates mechanically; but owing to the symmetrical disposition of the two identical crystals in a lattice filter section, no undesired

coupling between different parts of the circuit can occur. The use of one crystal slice to perform the two electrical functions in this way is not only economical and convenient, but also ensures that the two "opposite" crystals in the filter do, in fact, have identical characteristics.

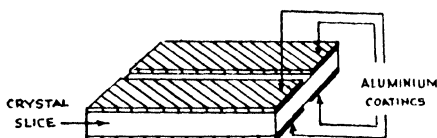


FIG. 722.—Use of a single crystal slice to provide a matched pair of crystal elements.

Crystals with series inductance

It has been seen that the bandwidth obtainable from a simple ladder or lattice filter using crystals as the reactive elements is limited, by the proximity of the resonant and anti-resonant frequencies, to about 1 per cent. of the mid-band frequency. It has also been seen that these frequencies can be brought nearer together by the addition of shunt capacity across the crystal, and that they can be separated by reducing the effective shunt capacity. There is, however, an irreducible minimum value to the shunt capacity of the crystal (C' in Fig. 714*b*); and in the case of a ladder or lattice type filter section, this capacity cannot conveniently be "balanced out", as it can in the case of the double-crystal filter shown in Fig. 717. The resonant and anti-resonant frequencies of a crystal can, however, be separated by the addition of inductance in series or in shunt with the crystal.

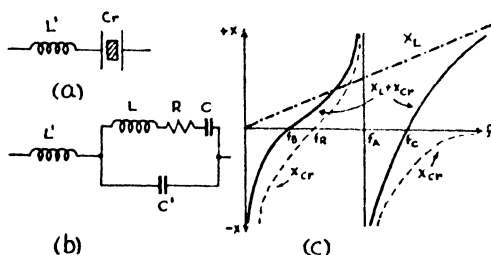


FIG. 723.—Effect of adding inductance in series with a crystal.

If an inductance L' be connected in series with a crystal C_r , as shown in Fig. 723*a*, the equivalent circuit is as given in Fig. 723*b*. The reactance X_{cr} of the crystal is given by the broken lines in Fig. 723*c*, with resonant and anti-resonant frequencies f_B and f_A ; while the reactance X_L of the added inductance is given by the chain-dotted line. The sum of these two gives the total reactance,

shown by the full-line curve, and is seen to exhibit an anti-resonance at f_A , and *two* series resonances, at f_B and f_C . The separation between f_B and f_A is clearly greater than that between f_B and f_C ; it can be shown that maximum bandwidth is obtained if the value of L' is so chosen that $(f_A - f_B) = (f_C - f_A)$, and in this case the separation $(f_A - f_B)$ is $4\frac{1}{2}$ per cent. of f_A . Thus from the point of view of maximum bandwidth, there is an optimum value of L' for any crystal.

Since any coil has an appreciable resistance, and a low value of Q compared with that of the crystal, it is at once apparent that the addition of an inductance L' in series with a crystal will adversely affect the performance of a filter. In certain cases, however, the added resistance can be made to appear outside the arms of the filter, and be combined with an external resistance to form an attenuator, which will give a constant increase in attenuation at all frequencies (*i.e.*, in both the pass and the attenuation bands), the increase being usually only a few decibels. This can best be seen by considering the addition of series inductances to a lattice filter section.

Broad-band lattice filter

Fig. 724a shows a lattice filter section with inductances L_1' , L_2' , added in series with each of the four crystals. The anti-resonant frequency f_{A1} of the series arms is made equal to the lower

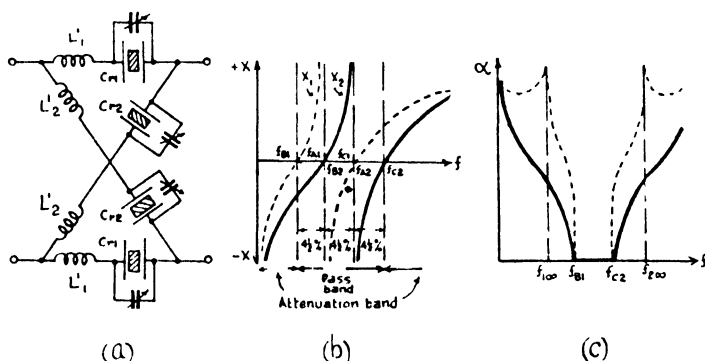


FIG. 724.—Broad-band lattice filter using series inductances.

series resonant frequency f_{B2} of the lattice arms; and the anti-resonant frequency f_{A2} of the lattice arms is made equal to the higher series resonant frequency f_{C1} of the series arms. The reactance sketch for this section is therefore as shown in Fig. 724b, and the attenuation-frequency characteristic as in Fig. 724c. The component values can, of course, be so chosen that the reactance curves X_1 and X_2 cross, giving rise to frequencies of infinite attenuation $f_{1\infty}$ and $f_{2\infty}$, and a response of the form shown dotted in Fig. 724c.

Since each of the three separations $(f_{A1} - f_{B1})$, $(f_{O1} - f_{A1}) = (f_{A2} - f_{B2})$, and $(f_{O2} - f_{A2})$ is approximately $4\frac{1}{2}$ per cent. of the mid-band frequency, the total bandwidth is $3 \cdot 4\frac{1}{2} = 13\frac{1}{2}$ per cent. of the mid-band frequency. If this is too wide, it may be reduced by connecting condensers in parallel with the crystals, and by this means any bandwidth from $13\frac{1}{2}$ per cent. down to $\frac{1}{2}$ per cent. of the mid-band frequency may be obtained. For bandwidths less than $\frac{1}{2}$ per cent., the loss caused by the resistance of the inductances becomes excessive; but below 1 per cent. bandwidth, the all-crystal filter can be used. For bandwidths greater than 13 per cent., ordinary inductance-and-condenser filters are satisfactory.

The inductances L_1' and L_2' in the series and lattice arms may all be made equal, and the anti-resonant frequencies adjusted for equality with the appropriate resonant frequencies by means of condensers C_B in parallel with the crystals as shown in Fig. 725*a*, where the inherent series resistance of each coil is shown as R' . Then, by the theorem given in Chapter 13 (page 598), the impedance formed by L' and R' in series can be subtracted from all four arms of the lattice, and placed in series with the input or output terminals

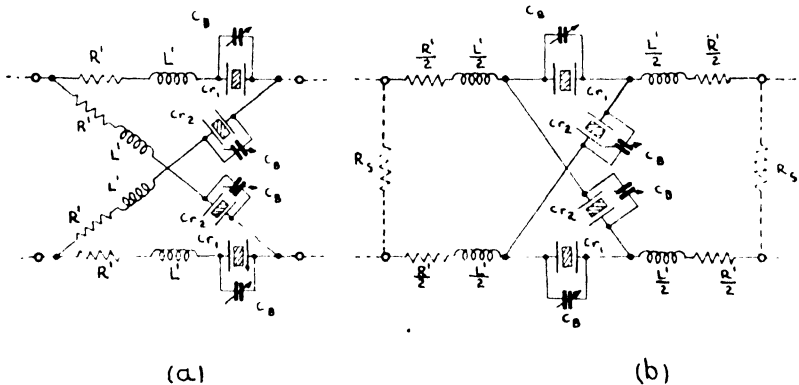


FIG. 725.—Showing how resistance of series inductances in lattice filter can be made to form an attenuator independent of frequency.

of the section as shown in Fig. 725*b*. If a resistance R_B be connected across the terminals of the resulting network, it will form, together with the resistances R' , an attenuator; and the value of R_B can be chosen to give correct impedance matching and minimum loss.

In a similar manner, a wideband filter can be obtained by connecting inductances in *parallel* with each crystal, and these added inductances, if equal, can be removed from the arms of the lattice and placed in parallel with the input or output terminals of the resulting network. A broad-band crystal filter with series inductances has a low characteristic impedance (of the order of 100Ω); while the corresponding filter with inductances added in parallel with the crystals has a high characteristic impedance, of the order of $100,000\Omega$.

CHAPTER 16

LINE TRANSMISSION

Line transmission is the theory of the propagation of electric waves along transmission lines. These transmission lines are assumed to consist of a pair of wires that are uniform throughout their whole length. Provided that this uniformity holds good, it is immaterial for the general theory whether the two wires are air-spaced on telegraph poles, are two conductors in an underground cable, or form a pair in a field quad cable.

Only steady-state currents and voltages will be considered, and the problem resolves itself into one of finding the current and voltage at any point along the length of the line, when a known voltage (or current) is continuously applied to the sending end.

In this chapter, the problem will be treated as far as possible in a non-mathematical manner; a more rigid mathematical treatment will be given in Chapter 17.

THE INFINITE LINE

The propagation of electric waves along any uniform and symmetrical transmission line may be deduced in terms of the results for a hypothetical line of infinite length having electrical constants per unit length identical to those of the line under consideration. For this reason, the propagation of electric waves along an infinite line will be considered first.



FIG. 726.—Infinite line.

When an alternating voltage is applied to the sending end of an infinite line (*see* Fig. 726), a finite current will flow due to the capacity and the leakage conductance between the two wires constituting the line. The value of this current will depend upon these two factors and others to be investigated later.

The ratio of the voltage applied, to the current flowing, will give the input impedance. This input impedance is known as the "characteristic impedance" of the line, and is denoted by Z_0 .

The characteristic impedance of any line is defined as the impedance looking into an infinite length of the line (*c.f.* characteristic impedance of a network, Chapter 13, page 561).

This characteristic impedance, in the case of a telephone line, is a vector quantity having a modulus $|Z_0|$ (usually between 200 and 1600 ohms), and an angle φ (usually lying between -45° and 0°). Since this angle lies in the fourth quadrant, it may be written either as $\angle -\varphi^\circ$ or as $\sphericalangle \varphi^\circ$. The modulus and angle of the characteristic impedance will, in general, vary with frequency; and the frequency at which the impedance has been measured should be stated. The following table shows the characteristic impedance of some typical army cables measured at 1600 c/s:—

TABLE XIX

Type of Cable	Z_0
Cable, electric, D 8, twisted	500 $\sphericalangle -32^\circ$
Cable, electric, D 8, single, 9 in. spacing.	1600 $\sphericalangle -30^\circ$
Field Quad (unloaded)	300 $\sphericalangle -37^\circ$

In addition to possessing an input impedance Z_0 , an infinite line has the following important properties:—

- (1) Since the line has infinite length, no waves will ever reach the distant end, hence there will be no possibility of reflection at the distant end and no reflected waves will return to the sending end.
- (2) For the same reason, when a voltage is applied to the sending end, the current flowing will depend only on the characteristic impedance Z_0 , and will be unaffected by the terminating impedance Z_B at the distant end.

It may be noted that in practice this last condition is approximately fulfilled by many long lines.

Short line terminated in Z_0

Consider an infinite line having input terminals 1 and 2 (see Fig. 727a). The impedance looking in at terminals 1 and 2 will, by definition, be Z_0 . Suppose that a short section AB at the near end of the line is now removed (Fig. 727b), so that the line now starts at terminals 3 and 4. The impedance looking in at terminals 3 and 4 will still be Z_0 , since the removal of the short section does not affect the infinite nature of the line. This means that the short section AB , from an electrical point of view, was originally terminated in an impedance Z_0 at B . If the short section AB is now terminated in an actual impedance Z_0 , the current and voltage at all points along its length will be exactly the same as if it were terminated in an infinite length of line.

It therefore follows that a short line terminated in Z_0 behaves

electrically, at all points along its length, as if it were an infinite line. In particular, this means that the input impedance will be Z_0 , and that there will be no reflection. Before a line can be thus

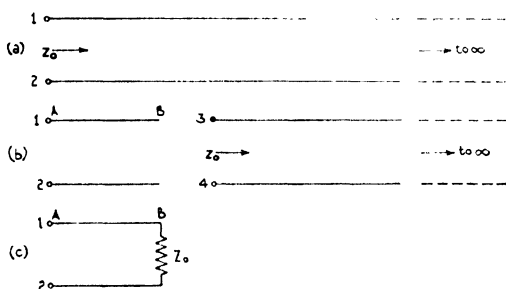


FIG. 727.—Short line terminated in Z_0 .

terminated, however, a method must be developed for the practical determination of Z_0 when only a short length of line is available.

Determination of Z_0 for a short line

A short line may be considered as a complex electrical network, and like any other network it may, at the frequency under consideration, be represented by a T section (see Fig. 728a). If the short

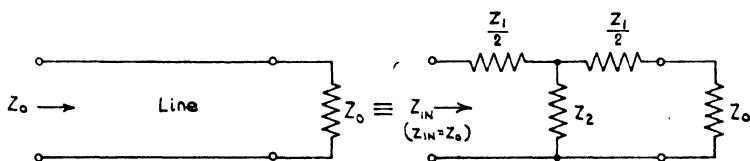


FIG. 728.—(a) Short line terminated in Z_0 —Equivalent T section.

line is terminated in Z_0 , it will behave as an infinite line, and have an input impedance Z_0 . Since the equivalent T section represents the line, it also must have an input impedance Z_0 when it is terminated in Z_0 .

Let the equivalent T section have series arms $\frac{Z_1}{2}$, $\frac{Z_1}{2}$, and shunt arm Z_2 (Fig. 728a).

Then
$$Z_{IN} = \frac{Z_1}{2} + \frac{Z_2 \left(\frac{Z_1}{2} + Z_0 \right)}{\frac{Z_1}{2} + Z_2 + Z_0}$$

But
$$Z_{IN} = Z_0$$

\therefore
$$Z_0^2 = \frac{Z_1^2}{4} + Z_1 Z_2 \tag{1}$$

$$\text{or } Z_0 = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2} \quad (2)$$

Thus Z_0 for the T section, and hence for the line, may be determined if Z_1 and Z_2 can be found. This will require two equations, which may be obtained by measuring the input impedance using two different terminating impedances. For convenience these terminations will be taken as infinity and zero.

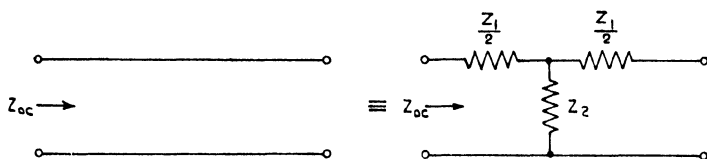


FIG. 728.—(b) Short line on open-circuit—Equivalent T section on open-circuit.

Let the input impedance with an infinite-impedance termination, *i.e.* open-circuit, be Z_{0c} .

Considering the equivalent T section on open-circuit (*see* Fig. 728b) :—

$$Z_{0c} = \frac{Z_1}{2} + Z_2 \quad (3)$$

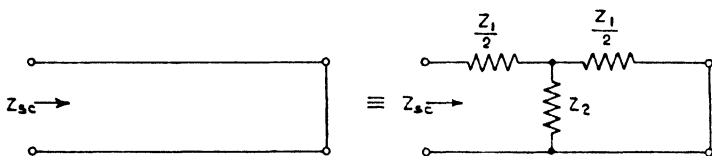


FIG. 728.—(c) Short line on short-circuit—Equivalent T section on short-circuit.

Let the input impedance with a zero-impedance termination, *i.e.*, short-circuit, be Z_{0s} .

Considering the equivalent T section on short-circuit (*see* Fig. 728c) :—

$$Z_{0s} = \frac{Z_1}{2} + \frac{\frac{Z_1 Z_2}{2}}{\frac{Z_1}{2} + Z_2}$$

$$\text{i.e. } Z_{0s} = \frac{\frac{Z_1^2}{4} + Z_1 Z_2}{\frac{Z_1}{2} + Z_2} \quad (4)$$

Equations 3 and 4 give two simultaneous equations from which Z_1 and Z_2 may be determined. At this stage, however, only Z_0 is

required, and this may be obtained directly by substituting equations 1 and 3 in equation 4 :—

$$Z_{so} = \frac{Z_0^2}{Z_{oo}}$$

i.e.
$$Z_0 = \sqrt{Z_{oo} \cdot Z_{so}} \quad (5)$$

The characteristic impedance of a line is therefore the geometric mean of the open- and short-circuit impedances.

This gives a very convenient method for the determination of the characteristic impedance of a practical line, since Z_{oo} and Z_{so} may readily be determined using an impedance bridge. The impedance bridges most frequently employed for such measurements

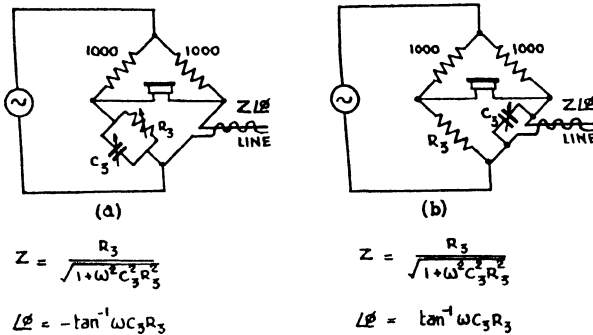


FIG. 729.—(a) Negative parallel bridge.
(b) Parallel resonance bridge.

are the inverted Wien (negative parallel) bridge (see Fig. 729a), for capacitive impedances, and the parallel resonance (negative parallel condenser-to-line) bridge (see Fig. 729b) for inductive impedances (see Chapter 5).

Example.—

The following measurements have been made on a line at 1600 c/s :—

$$Z_{oo} = 900 \Omega \angle -30^\circ$$

$$Z_{so} = 400 \Omega \angle -10^\circ$$

What is the characteristic impedance of the line at 1600 c/s ?

$$\begin{aligned} Z_0 &= \sqrt{Z_{oo} \cdot Z_{so}} \\ &= \sqrt{[900 \angle -30^\circ] [400 \angle -10^\circ]} \\ &= \sqrt{360,000 \angle -40^\circ} \\ &= 600 \angle -20^\circ \quad \text{Ans.} \end{aligned}$$



PLATE 35.—View of panel of typical impedance bridge.

CURRENTS AND VOLTAGES ALONG AN INFINITE LINE

Consider a current I_g applied to the sending end A of an infinite line (or a line terminated in Z_0) as in Fig. 730*a*. At the point B , at a distance of one mile down the line, let the current be I_1 .

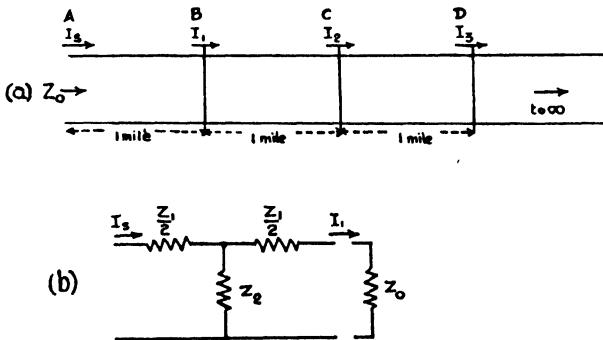


FIG. 730.—Currents along an infinite line.

Due to the loss introduced by the line, the current I_1 will be less than the current I_g ; and since, in addition, a phase-shift will be introduced, the ratio $\frac{I_g}{I_1}$ will be a vector quantity.

A convenient way of representing a vector quantity is in the form e^γ , where γ is a complex quantity.

$$\text{Hence let } \frac{I_s}{I_1} = e^\gamma$$

γ is known as the "propagation constant" per mile of the line.

Considering the equivalent T section for the first mile of the line, γ may be determined in terms of the arms $\frac{Z_1}{2}$ and Z_2 . From Fig. 730*b*, it will be seen that:—

$$I_1 = \frac{Z_2}{Z_2 + \frac{Z_1}{2} + Z_0} \cdot I_s$$

$$\text{Hence } e^\gamma = \frac{I_s}{I_1} = 1 + \frac{Z_1}{2Z_2} + \frac{Z_0}{Z_2} \quad (6)$$

$$\text{giving } \gamma = \log_e \left[1 + \frac{Z_1}{2Z_2} + \frac{Z_0}{Z_2} \right] \quad (7)$$

At a distance two miles down the line, at point *C*, let the current be I_2 . Since the section of the line between *B* and *C* is identical with that between *A* and *B*, it follows that it may be represented by the same equivalent T section.

$$\text{Thus } \frac{I_1}{I_2} = 1 + \frac{Z_1}{2Z_2} + \frac{Z_0}{Z_2} = e^\gamma$$

Similarly it will be seen that, for the section between *C* and *D*:—

$$\frac{I_2}{I_3} = e^\gamma$$

where I_3 is the current at *D*, three miles down the line. For the n^{th} section:—

$$\frac{I_{n-1}}{I_n} = e^\gamma$$

where I_{n-1} and I_n are the currents at distances $(n-1)$ and n miles down the line respectively.

$$\begin{aligned} \text{Now } \frac{I_s}{I_1} &= e^\gamma \\ \frac{I_s}{I_2} &= \frac{I_s}{I_1} \cdot \frac{I_1}{I_2} = e^{2\gamma} \\ \frac{I_s}{I_3} &= \frac{I_s}{I_1} \cdot \frac{I_1}{I_2} \cdot \frac{I_2}{I_3} = e^{3\gamma} \end{aligned}$$

and, in the general case:—

$$\frac{I_s}{I_n} = \frac{I_s}{I_1} \cdot \frac{I_1}{I_2} \cdot \dots \cdot \frac{I_{n-1}}{I_n} = e^{n\gamma}$$

From this, it follows that:—

$$I_n = I_s \cdot e^{-n\gamma} \quad (8)$$

This is the general equation for the current at a point distant n miles down an infinite line, in terms of the current at the sending end I_s , and the propagation constant per mile. It applies for any value of n .

A similar equation can be derived for voltage, since at all points along an infinite line the ratio of voltage to current is equal to the characteristic impedance Z_0 .

$$\text{Thus} \quad \frac{E_s}{I_s} = \frac{E_1}{I_1} = \frac{E_2}{I_2} = \frac{E_3}{I_3} = \dots = \frac{E_n}{I_n} = Z_0$$

$$\text{Hence} \quad \frac{E_s}{E_n} = \frac{I_s}{I_n}$$

$$\text{But} \quad \frac{I_s}{I_n} = e^{n\gamma}$$

$$\text{Therefore} \quad \frac{E_s}{E_n} = e^{n\gamma}$$

from which it follows that:—

$$E_n = E_s \cdot e^{-n\gamma} \quad (9)$$

Attenuation and phase constants

The propagation constant γ is a complex quantity; let it be equal to $\alpha + j\beta$.

Thus, for one mile of line:—

$$\begin{aligned} \frac{I_s}{I_1} &= e^\gamma = e^{\alpha + j\beta} \\ &= e^\alpha \angle \beta \end{aligned}$$

Hence $\left| \frac{I_s}{I_1} \right| = e^\alpha$, and the angle of $\frac{I_s}{I_1}$ is $\angle \beta$. It follows that $\alpha = \log_e \left| \frac{I_s}{I_1} \right|$. Note that e^α gives the ratio of the absolute value of the current sent, to that of the current received, while β gives the phase angle between the two currents.

α is known as the attenuation constant per mile of the line, and is measured in nepers per mile.

β is known as the phase constant or wavelength constant per mile of the line, and is measured in radians per mile.

If the length of the line is n miles:—

$$\begin{aligned} \frac{I_s}{I_n} &= e^{n\gamma} = e^{n\alpha + jn\beta} \\ &= e^{n\alpha} \angle n\beta \end{aligned}$$

The attenuation of such a line is thus $n\alpha$ nepers, and the phase-shift is $n\beta$ radians.

It must be noted that, throughout this chapter, the values obtained for attenuation and phase-shift are in nepers and radians. These results can be converted into the more convenient units for practical work, the decibel and the degree, by multiplying by 8.686 and 57.3 respectively, or by using the Conversion Tables on pages 800, 804, 838 and 839.

Conclusions.—

In the general case of an infinite line or a short line terminated in its characteristic impedance and having a propagation constant γ , the current I at any point distant x from the sending end will be given by :—

$$I = I_s \cdot e^{-\gamma x} \quad (10)$$

$$= I_s e^{-\alpha x} \angle -\beta x \quad (11)$$

where I_s is the sending-end current.

The voltage E at any point distant x from the sending end will be given by :—

$$E = E_s \cdot e^{-\gamma x} \quad (12)$$

$$= E_s e^{-\alpha x} \angle -\beta x \quad (13)$$

where E_s is the sending-end voltage.

Example.—

A twisted D8 cable has, at 1600 c/s, an attenuation of 3.0 db per mile and a phase constant of 0.319 radians per mile in dry weather. If 2 volts at 1600 c/s are applied to the sending end, what will be the voltage at a point 10 miles down the line when the line is correctly terminated (*i.e.* terminated in its characteristic impedance) ?

The voltage at a point distant x miles from the sending end is :—

$$E = E_s \cdot e^{-\gamma x}$$

$$= E_s \cdot e^{-\alpha x} \angle -\beta x$$

where α is in nepers per mile
and β is in radians per mile.

In this case, attenuation at 3.0 db/mile is equivalent to 3.0×0.115 nepers per mile, *i.e.* 0.345 nepers/mile.

$$\begin{aligned} \text{The required voltage } E &= 2 \cdot e^{-0.345 \times 10} \angle -0.319 \times 10 \\ &= 2 \cdot e^{-3.45} \angle -3.19 \\ &= 0.0635 \text{ volts, } \angle -3.19. \quad \text{Ans.} \end{aligned}$$

Thus the voltage at a point 10 miles from the sending end is 0.0635 volts, lagging 3.19 radians, *i.e.* $182^\circ 47'$, behind the sending end voltage.

Graphical representation of current and voltage distribution along an infinitely long line

Current.

It has been seen that the current I at any point distant x from the sending end of a line is given by:—

$$I = I_s \cdot e^{-\alpha x} \angle -\beta x$$

To represent this equation graphically would require a three-dimensional figure, because I_s itself is an alternating current, and therefore I varies both with the distance x and with the time t .

If I_s has a frequency f , it may be represented by a rotating vector of length I_{smax} rotating with angular velocity ω radians per second, where $\omega = 2\pi f$. The projection of this vector on to the vertical axis will give the instantaneous value of I_s (see Fig. 731).

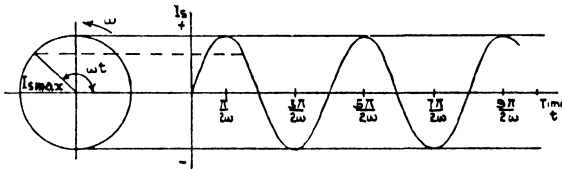


FIG. 731.—Rotating vector and graphical representation of I_s against time.

At a point distant x down the line, the current I will have the same frequency f , but, due to the attenuation of the line, the maximum amplitude will have been reduced from I_{smax} to $I_{smax} \cdot e^{-\alpha x}$. The current I will therefore vary sinusoidally between the limits $I_{smax} \cdot e^{-\alpha x}$ at the peak of the positive half-cycle and $-I_{smax} \cdot e^{-\alpha x}$ at the peak of the negative half-cycle (see Fig. 732).

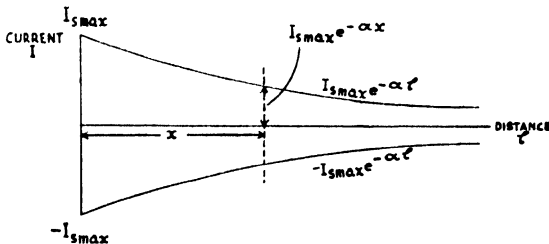


FIG. 732.—Decrease in amplitude of current along an infinite line.

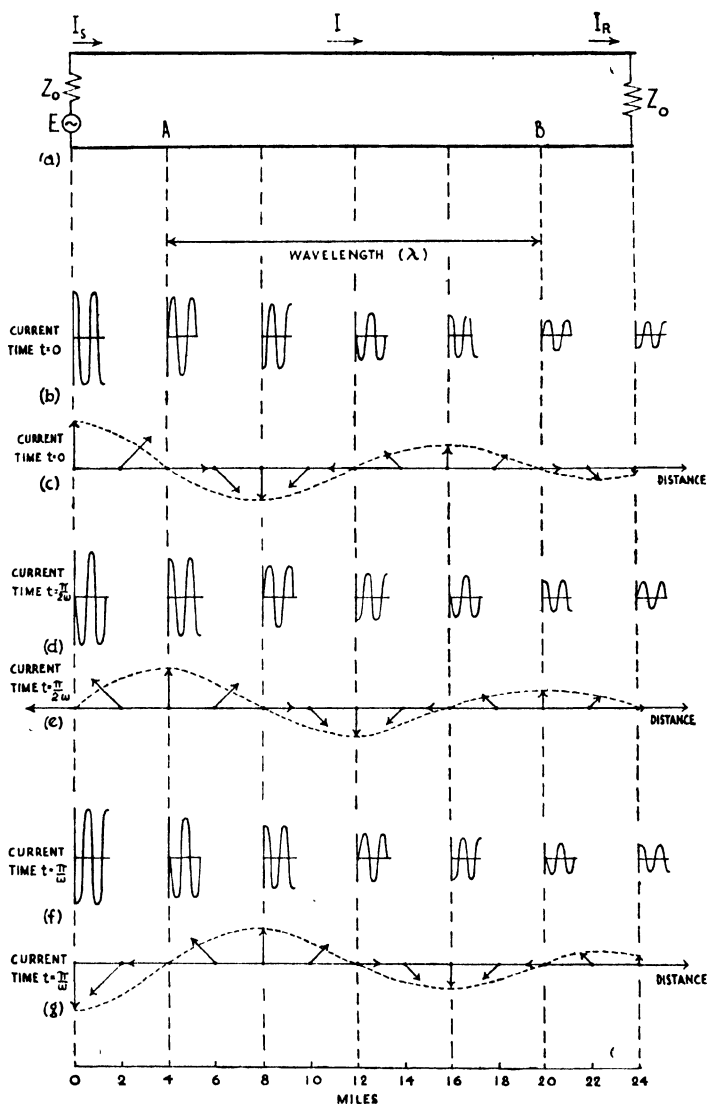


FIG. 733.—Magnitude and phase of current along an infinite line.

Due to the phase constant β , the current I will lag by a phase angle βx on the current I_s .

Both the magnitude and the phase of the current I at various points along the line (*see* Fig. 733*a*) may be seen from the sine waves in Fig. 733*b*; each of these represents the variation of current with time at the point on the line corresponding to the vertical line at the left of the sine wave.

In place of these sine waves, however, it is more convenient to consider their corresponding rotating vectors, as shown in Fig. 733*c*. These vectors are drawn to correspond with the instant at which I_s is at its positive peak; but it must be remembered that all these vectors are rotating in an anti-clockwise direction with angular velocity ω . Thus at a time $\frac{\pi}{2\omega}$ seconds later, I_s will be at zero and approaching its negative peak, and the corresponding sine wave and vector diagrams will be as shown in Figs. 733*d* and *e* respectively; while at a time $\frac{\pi}{\omega}$ seconds, I_s will be at its negative peak, and the corresponding sine wave and vector diagrams as in Figs. 733*f* and *g*.

Alternatively, if one instant of time be considered, a picture may be obtained of the current distribution along the line at that instant. Thus, corresponding to the vector diagram in Fig. 733*c*, which shows I_s at its positive peak, one can draw the dotted curve along the line. Similarly, the dotted curves of Figs. 733*e* and *g* show the current distribution at all points along the line at the instants when I_s is at zero and at its negative peak respectively.

Voltage.

The voltage at any point distance x from the sending end is given by:—

$$E = E_s \cdot e^{-\alpha x} \angle -\beta x$$

The ratio of voltage to current at all points down an infinite line is equal to Z_0 , the characteristic impedance of the line.

Thus if $Z_0 = |Z_0| \angle -\varphi$, the voltage at any point will lag on the current by the angle φ . Bearing in mind this difference in phase, the voltage may now be represented in a similar manner to the current.

Fig. 734*b* and *c* show the instantaneous distributions of current and voltage respectively along a line (*see* Fig. 734*a*) having a characteristic impedance $1000 \angle -45^\circ$.

The full curve in Fig. 734*d* shows the distribution of power $P = |E| \cdot |I| \cos \varphi$ along the line, while the broken line shows the same power distribution expressed in decibels referred to 1mW.

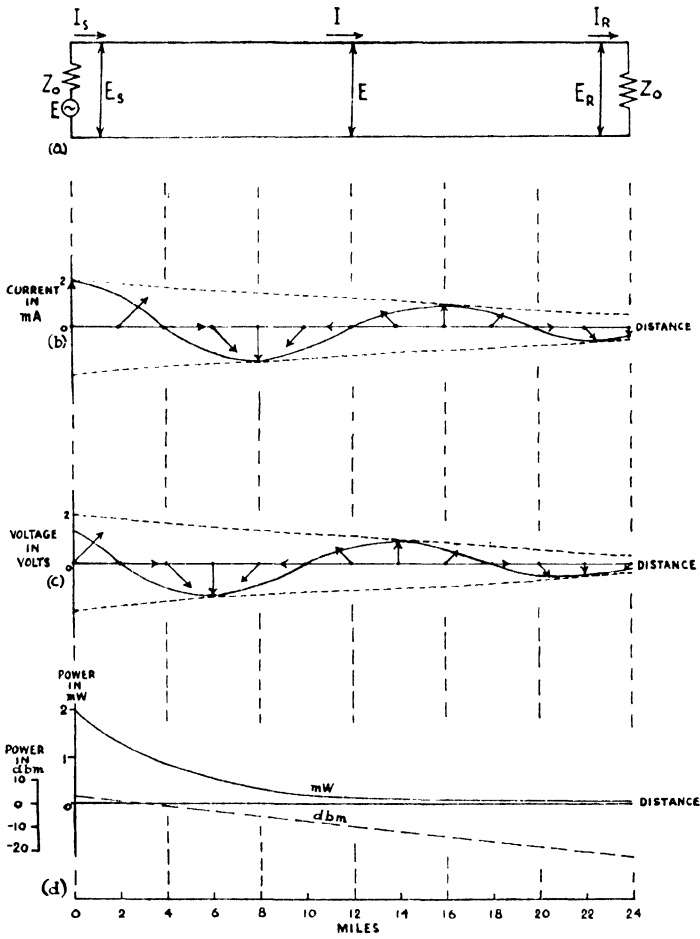


FIG. 734.—Distribution of current, voltage and power along a correctly terminated line.

Logarithmic spiral representation of current and voltage distribution along an infinite line

The diagrams dealt with so far refer to one instant of time only, and in order to obtain a complete picture of the current or voltage distribution at all instants one diagram would be required for each position of the I_s or E_s vectors.

Just as a waveform that varies in amplitude with time may be represented by a rotating vector, so may a waveform that varies in amplitude with distance. Thus the instantaneous picture given by the dotted curve in Fig. 733c may be represented by a vector of length $I_{smax} \cdot e^{-\alpha x}$ and angle $-\beta x$, as shown in Fig. 735. As x increases, this vector rotates in a clockwise direction; but at the same time, its modulus decreases logarithmically, and the locus of the vector is, in fact, a logarithmic spiral. The projection of

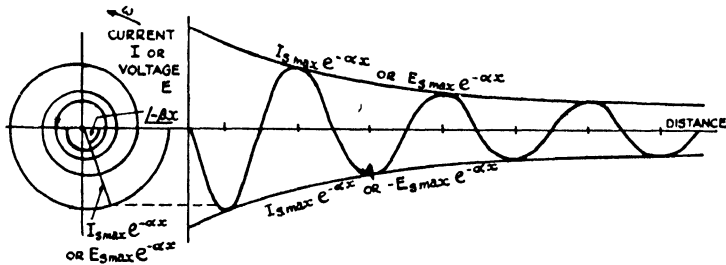


FIG. 735.—Logarithmic spiral representation of current and voltage at any point along a line and at any time.

the rotating vector on to the vertical axis will give the instantaneous value of current at the point down the line corresponding to the distance x .

If the complete logarithmic spiral is now rotated in an anti-clockwise direction with angular velocity ω radians per second, and the projection taken, the value of current or voltage will be obtained for all distances (x) down the line, and for all times (t).

Wavelength and velocity

The wavelength λ is the distance between any point and the next point along the line at which the current (or voltage) is in the same phase. In Fig. 733, A and B are two such points. Although the current at A reaches a maximum at the same instant as the current at B , the current at A is really leading by 2π radians on the current at B . The phase-shift along the line is β radians per mile. Hence the distance λ must be $\frac{2\pi}{\beta}$ miles, that is:—

$$\lambda = \frac{2\pi}{\beta}$$

The velocity* of propagation (v) = frequency \times wavelength

Thus
$$v = \frac{2\pi f}{\beta}$$

or
$$v = \frac{\omega}{\beta} \tag{15}$$

Example.—

At 1600 c/s, $\omega = 10,000$ radians/second.

For an airline $\beta = 0.055$ radians per mile.

$\therefore \lambda = \frac{2\pi}{0.055} = 114.2$ miles

and
$$v = \frac{10,000}{0.055} = 182,000$$
 miles/second.

Therefore the time taken for a wave of this frequency to travel 100 miles is 0.55 milliseconds.

For a loaded underground cable, $\beta = 1.0$ radian per mile at 1600 c/s.

$\therefore \lambda = 6.28$ miles

and
$$v = 10,000$$
 miles/second.

In this case, the time taken for a signal to travel 100 miles is 10 milliseconds.

LINE CONSTANTS

It has already been seen that a practical line has a characteristic impedance Z_0 , a propagation constant γ , an attenuation constant α , and a phase constant β . These are known as the "secondary line constants." Although they are referred to as constants it should be noted that, in general, all will vary if the frequency is changed.

The "primary line constants" (which, for the purpose of transmission theory, are assumed to be independent of frequency) are R , G , L , and C , where:—

R is the resistance per mile of the line, measured in ohms,

G is the leakance per mile of the line, measured in mhos,

L is the inductance per mile of the line, measured in henries,

C is the capacitance per mile of the line, measured in farads.

They are measured considering both conductors, *i.e.* per mile loop.

These primary constants may be obtained by measurements on a sample of the line.

* This is the phase or wave velocity. The group velocity (*i.e.*, the velocity at which the energy is transferred along the line) is $\frac{d\omega}{d\beta}$.

Relationship between primary and secondary line constants

Consider a short length of line l miles long. This short section will have a resistance Rl , a leakance Gl , an inductance Ll , and a capacitance Cl .

Its characteristic impedance will be Z_0 , the same as that of the complete line. Its propagation constant will be γl , where γ is the propagation constant per mile of the complete line.

This short section of line may be represented by a T network, as shown in Fig. 736b.

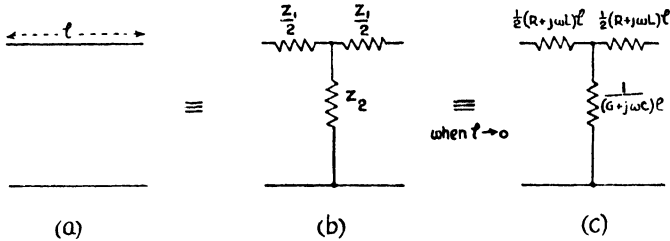


FIG. 736.—T sections equivalent to short length of line.

If the length of the section is very small, Z_1 will be approximately equal to the series impedance of the section, *i.e.* to $Rl + j\omega Ll$; and Z_2 will be approximately equal to the shunt impedance of the section, *i.e.* $\frac{1}{Gl + j\omega Cl}$.

The accuracy of this statement increases as l decreases, and in order to obtain an accurate answer it will be assumed that the section is so small that l tends to zero.

Determination of Z_0

It has been shown that for a T section:—

$$Z_0 = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2} \quad (\text{Equation 2})$$

Hence in this case, since $Z_1 = (R + j\omega L)l$ and $Z_2 = \frac{1}{(G + j\omega C)l}$,

$$\begin{aligned} \therefore Z_0 &= \sqrt{\frac{(R + j\omega L)^2 l^2}{4} + \frac{(R + j\omega L)l}{(G + j\omega C)l}} \\ &= \sqrt{\frac{R + j\omega L}{G + j\omega C} + \frac{(R + j\omega L)^2}{4} \cdot l^2} \end{aligned}$$

As $l \rightarrow 0$, terms containing l^2 may be neglected, giving:—

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} \quad (16)$$

This equation is very important, since it enables both the

modulus and the angle of Z_0 to be calculated from a knowledge of the primary line constants.

Example.—

A line has the following primary line constants:—

$$R = 100 \text{ ohms per mile.}$$

$$G = 1.5 \times 10^{-6} \text{ mhos per mile.}$$

$$L = 0.001 \text{ henries per mile.}$$

$$C = 0.062 \text{ microfarads per mile.}$$

Find the characteristic impedance in modulus-and-angle form at 1000 c/s.

$$\begin{aligned} R + j\omega L &= 100 + j \times 2\pi \times 1000 \times 0.001 \\ &= 100 + j6.283 \\ &= 100.2 \angle 3^\circ 36' \end{aligned}$$

$$\begin{aligned} G + j\omega C &= 1.5 \times 10^{-6} + j \times 2\pi \times 1000 \times 0.062 \times 10^{-6} \\ &= (1.5 + j389.5) \times 10^{-6} \\ &= 389.5 \times 10^{-6} \angle 89^\circ 48' \end{aligned}$$

$$\begin{aligned} Z_0 &= \sqrt{\frac{R + j\omega L}{G + j\omega C}} \\ &= \sqrt{\frac{100.2 \angle 3^\circ 36'}{389.5 \times 10^{-6} \angle 89^\circ 48'}} \\ &= 507 \angle -43^\circ 6' \text{ Ans.} \end{aligned}$$

Equation 16 can be expressed in the modulus and angle form:—

$$\begin{aligned} Z_0 &= \sqrt{\frac{R + j\omega L}{G + j\omega C}} \\ &= \left[\frac{R + j\omega L}{G + j\omega C} \right]^{\frac{1}{2}} \\ &= \left[\frac{\sqrt{R^2 + \omega^2 L^2}, \tan^{-1} \frac{\omega L}{R}}{\sqrt{G^2 + \omega^2 C^2}, \tan^{-1} \frac{\omega C}{G}} \right]^{\frac{1}{2}} \\ &= \left[\frac{\sqrt{R^2 + \omega^2 L^2}}{\sqrt{G^2 + \omega^2 C^2}}, \tan^{-1} \frac{\omega L}{R} - \tan^{-1} \frac{\omega C}{G} \right]^{\frac{1}{2}} \\ &= \sqrt[4]{\frac{R^2 + \omega^2 L^2}{G^2 + \omega^2 C^2}} \cdot \frac{1}{2} \left(\tan^{-1} \frac{\omega L}{R} - \tan^{-1} \frac{\omega C}{G} \right) \quad (17) \end{aligned}$$

Alternatively, since $Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$

it follows that $Z_0 = \sqrt{\frac{\omega L - jR}{\omega C - jG}}$ (multiplying by $\sqrt{\frac{-j}{-j}}$)

Hence, instead of equation 17, one can write :—


$$Z_0 = \sqrt{\frac{R^2 + \omega^2 L^2}{G^2 + \omega^2 C^2}} \cdot \frac{1}{2} \left[\tan^{-1} \frac{G}{\omega C} - \tan^{-1} \frac{R}{\omega L} \right] \quad (18)$$

It will be seen from equation 17 that :—

When ω is very small, $|Z_0| \rightarrow \sqrt{\frac{R}{G}}$

When ω is very large, $|Z_0| \rightarrow \sqrt{\frac{L}{C}}$

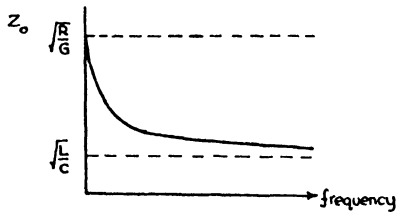Since $\frac{R}{G}$ is in all cases greater than $\frac{L}{C}$, the variation of Z_0 with frequency expected for a practical line will be as in Fig. 737.



Variation of Z_0 with frequency.

FIG. 737.—Characteristic impedance of a line.

Taking 70 lb Cd-Cu multi-airline as an example of an open-wire line, Fig. 738 shows how $|Z_0|$ and $\angle \varphi_0$ vary with frequency over the audio and carrier range for a practical line.

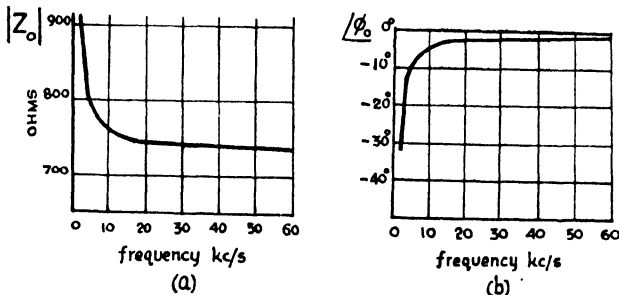


FIG. 738.—(a) Variation of $|Z_0|$ with frequency for Cd-Cu multi-airline.
(b) Variation of $\angle \varphi_0$ with frequency for Cd-Cu multi-airline.

Determination of γ

For the T section of Fig. 736*b*, the propagation constant is γl . Since the series and shunt arms of the T section are $\frac{Z_1}{2}$ and Z_2 respectively, it follows that :—

$$e^{\gamma l} = 1 + \frac{Z_1}{2Z_2} + \frac{Z_0}{Z_2}$$

But as $l \rightarrow 0$, $Z_1 = (R + j\omega L) l$

$$\text{and } Z_2 = \frac{1}{(G + j\omega C) l}$$

Hence

$$\begin{aligned} e^{\gamma l} &= 1 + \frac{(R + j\omega L)(G + j\omega C) l^2}{2} + Z_0(G + j\omega C) l \\ &= 1 + \frac{(R + j\omega L)(G + j\omega C) l^2}{2} \\ &\quad + \sqrt{\frac{R + j\omega L}{G + j\omega C}} (G + j\omega C) l \\ &= 1 + \sqrt{\frac{(R + j\omega L)(G + j\omega C) l}{(R + j\omega L)(G + j\omega C) l^2}} \\ &\quad + \frac{(R + j\omega L)(G + j\omega C) l^2}{2} \end{aligned} \tag{19}$$

But by the exponential series :—

$$e^{\gamma l} = 1 + \gamma l + \frac{\gamma^2 l^2}{2} + \dots \text{ to } \infty$$

As $l \rightarrow 0$, terms containing l^3 and higher may be neglected,

$$\therefore e^{\gamma l} = 1 + \gamma l + \frac{\gamma^2 l^2}{2} \tag{20}$$

Comparing equations 19 and 20, it is seen that :—

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)} \tag{21}$$

This equation is very important, since it enables γ to be calculated from a knowledge of the primary line constants.

Since $\gamma = \alpha + j\beta$,

$$\alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)} \tag{22}$$

If γ is to be calculated, equation 21 should be used, and the result obtained in rectangular notation ; then the real part will be the attenuation constant α , and the imaginary part the phase constant β .

If γ is obtained in the modulus-and-angle notation, say :—

$$\gamma = P \angle \theta \tag{23}$$

the attenuation and phase constants may be found from the equations :—

$$\alpha = P \cos \theta \tag{24}$$

$$\beta = P \sin \theta \tag{25}$$

The primary and secondary line constants for various types of line are given in Table XX.

Example.—

A sample of field quad cable has the following primary line constants :—

$$R = 78 \text{ ohms per mile loop.}$$

$$G = 62 \text{ micromhos per mile.}$$

$$L = 1.75 \text{ millihenries per mile loop.}$$

$$C = 0.0945 \text{ microfarads per mile.}$$

Required to calculate at 1600 c/s ($\omega \approx 10,000$ radians/second) the following :—

- (i) Characteristic impedance Z_0 .
- (ii) Attenuation constant (α), in nepers and decibels per mile.
- (iii) Phase constant (β), in radians and degrees per mile.
- (iv) Wavelength (λ), in miles.
- (v) Velocity (v) in miles per second.
- (vi) Time for a wave to travel 100 miles along the line, in milliseconds.

$$\begin{aligned} R + j\omega L &= 78 + j10,000 \times 1.75 \times 10^{-3} \\ &= 78 + j17.5 \\ &= 79.94 \angle 12^\circ 39' \end{aligned}$$

$$\begin{aligned} G + j\omega C &= 10^{-6} \times 62 + j10,000 \times 0.0945 \times 10^{-6} \\ &= 10^{-6} (62 + j945) \\ &= 10^{-6} \times 947 \angle 86^\circ 15' \end{aligned}$$

$$\begin{aligned} Z_0 &= \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \sqrt{\frac{79.94}{947 \times 10^{-6}}} \angle -36^\circ 48' \\ \text{i.e., } Z_0 &= 290 \angle -36^\circ 48' \quad \text{Ans. (i)} \end{aligned}$$

$$\begin{aligned} \gamma &= \sqrt{(R + j\omega L)(G + j\omega C)} = \sqrt{79.94 \times 10^{-6} \times 947} \angle 49^\circ 27' \\ \text{i.e., } \gamma &= 0.275 \angle 49^\circ 27' \end{aligned}$$

$$\text{i.e., } \gamma = 0.179 + j0.209$$

$$\alpha = 0.179 \text{ nepers per mile} \equiv 1.56 \text{ db per mile. Ans. (ii).}$$

$$\beta = 0.209 \text{ radians per mile} \equiv 11^\circ 58' \text{ per mile. Ans. (iii).}$$

$$\text{The wavelength } \lambda = \frac{2\pi}{\beta} = \frac{2\pi}{0.209} = 30 \text{ miles. Ans. (iv).}$$

$$\text{The velocity } v = \frac{\omega}{\beta} = \frac{10,000}{0.209} = 47,840 \text{ miles per second. Ans. (v).}$$

The time taken for a wave to travel 100 miles is :—

$$\begin{aligned} t &= \frac{100}{47,840} \text{ seconds} \\ &= 0.00209 \text{ seconds} \\ &= 2.09 \text{ milliseconds. Ans. (vi).} \end{aligned}$$

LINE CONSTANTS

723

TABLE XX
PRIMARY and SECONDARY LINE CONSTANTS (at 1600 c/s)

Type of Line	Loading	Cut-off fre- quency kc/s	R ohms per mile	L mH per mile	G μ -mhos per mile	C μ F per mile	$\frac{R}{\omega L}$	$\frac{G}{\omega C}$	Z_0 ohms	θ degrees	α db per mile	β radians per mile	λ miles	ν miles per sec.
300 lb. Cu. Airline ..	Unloaded	—	5.8	3.54	1	0.0089	0.164	0.0112	640	-4.3	0.043	0.056	112	179,000
200 lb. Cu. Airline ..	Unloaded	—	8.8	3.66	1	0.0086	0.24	0.0116	660	-6.4	0.061	0.0565	111	177,000
150 lb. Cu. Airline ..	Unloaded	—	11.7	3.76	1	0.0084	0.31	0.0119	685	-8.5	0.077	0.057	110	175,000
150 lb. Cd-Cu Airline ..	Unloaded	—	14	3.76	1	0.0084	0.37	0.0119	690	-10	0.092	0.057	110	175,000
70 lb. Cd-Cu Airline	Unloaded	—	30	4.07	1	0.0081	0.74	0.0124	790	-18	0.176	0.061	103	164,000
40 lb. Cd-Cu Airline	Unloaded	—	52.5	4.25	1	0.0079	1.24	0.0127	920	-25	0.274	0.066	95	152,000
40 lb. PCQT UG cable	Unloaded	—	44	1	1	0.065	4.4	0.00154	264	-38.7	0.93	0.134	47	74,500
40 lb. PCQT UG cable	88 mH/1.136 mile	3.93	47.3	78.5	1	0.065	0.06	0.00154	1100	-1.6	0.19	0.714	8.8	14,000
20 lb. PCQT UG cable	Unloaded	—	88	1	1	0.065	8.8	0.00154	368	-44.6	1.44	0.168	37.4	59,500
20 lb. PCQT UG cable	88 mH/1.136 mile	3.93	91.3	78.5	1	0.065	0.116	0.00154	1100	-3.2	0.362	0.714	9.8	14,000
Field quad cable ..	Unloaded	—	78	1.75	62	0.0945	4.45	0.00106	290	-36.8	1.56	0.209	30	48,000
D8 cable, spaced 9 in.	Unloaded	—	196	10	5	0.008	1.96	0.0125	1660	-29.7	0.64	0.111	56.5	90,000
D8 cable, twisted, dry	Unloaded	—	196	7.1	95	0.090	2.76	0.00111	480	-32	2.34	0.342	18.4	29,000
D8 cable, twisted, wet	Unloaded	—	196	7.1	365	0.206	2.76	0.000485	290	-30	4.0	0.55	11.5	18,000

Evaluation of α and β

Equation 21 may be converted into the modulus-and-angle notation, in which case:—

$$\gamma = \sqrt[4]{(R^2 + \omega^2 L^2)(G^2 + \omega^2 C^2)}, \frac{1}{2} \left[\tan^{-1} \frac{\omega L}{R} + \tan^{-1} \frac{\omega C}{G} \right] \quad (26)$$

$$\text{Hence } |\gamma| = \sqrt[4]{(R^2 + \omega^2 L^2)(G^2 + \omega^2 C^2)}$$

$$\text{But } \gamma = \alpha + j\beta$$

$$\therefore |\gamma| = \sqrt{\alpha^2 + \beta^2}$$

$$\text{Thus } \sqrt{\alpha^2 + \beta^2} = \sqrt[4]{(R^2 + \omega^2 L^2)(G^2 + \omega^2 C^2)}$$

Squaring both sides:—

$$\alpha^2 + \beta^2 = \sqrt{(R^2 + \omega^2 L^2)(G^2 + \omega^2 C^2)} \quad (27)$$

From equation 22:—

$$\alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

Squaring both sides:—

$$(\alpha + j\beta)^2 = (R + j\omega L)(G + j\omega C)$$

$$\alpha^2 + 2j\alpha\beta - \beta^2 = RG + j\omega LG + j\omega CR - \omega^2 LC$$

Equating real terms on both sides:—

$$\alpha^2 - \beta^2 = RG - \omega^2 LC \quad (28)$$

Adding equations 28 and 27:—

$$2\alpha^2 = \sqrt{(R^2 + \omega^2 L^2)(G^2 + \omega^2 C^2)} + (RG - \omega^2 LC)$$

$$\therefore \alpha = \sqrt{\frac{1}{2} [\sqrt{(R^2 + \omega^2 L^2)(G^2 + \omega^2 C^2)} + (RG - \omega^2 LC)]} \quad (29)$$

Subtracting 28 from 27:—

$$2\beta^2 = \sqrt{(R^2 + \omega^2 L^2)(G^2 + \omega^2 C^2)} - (RG - \omega^2 LC)$$

$$\therefore \beta = \sqrt{\frac{1}{2} [\sqrt{(R^2 + \omega^2 L^2)(G^2 + \omega^2 C^2)} - (RG - \omega^2 LC)]} \quad (30)$$

Practical formulæ for Z_0 , α , and β for unloaded cables

In practice, certain approximations are made to obtain simplified expressions for Z_0 , α and β . In the case of an underground cable, small diameter conductors are used in order to obtain the maximum number of conductors for a given overall diameter of the cable. An underground cable will, therefore, in general, have a fairly large resistance R per mile; and, due to the small spacing between the conductors, a large capacitance C and a small inductance L per mile. The leakance G per mile is very small, due to the good insulation between conductors in a well-laid and well-maintained cable.

To take a particular case, the constants for an air-spaced paper-insulated 20 lb. underground cable are given as $R = 88$ ohms per

mile, $G = 10^{-6}$ mhos per mile, $L = 0.001$ henries per mile and $C = 0.065 \mu\text{F}$ per mile. Thus, taking the extreme limits of the audio frequency band as 200 and 3200 c/s, it may be seen that in this band ωL is always less than 20 and ωC is always greater than 80×10^{-6} .

The permissible approximations for unloaded underground cables at audio frequencies are therefore that $\omega C \gg G$, and that $\omega L \ll R$. These approximations will clearly give more accurate results at the lower than at the higher audio frequencies.

Characteristic Impedance Z_0

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} \quad (\text{equation 16}).$$

When $R \gg \omega L$ and $\omega C \gg G$

$$\begin{aligned} Z_0 &\simeq \sqrt{\frac{R}{j\omega C}} = \sqrt{\frac{R}{\omega C}} \angle \frac{1}{2} (0^\circ - 90^\circ) \\ \text{i.e., } Z_0 &\simeq \sqrt{\frac{R}{\omega C}} \angle -45^\circ \end{aligned} \quad (31)$$

Propagation constant γ

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)} \quad (\text{equation 21})$$

When $R \gg \omega L$ and $\omega C \gg G$

$$\begin{aligned} \gamma &\simeq \sqrt{j\omega CR} = \sqrt{\omega CR} \angle 45^\circ \\ &= \sqrt{\omega CR} \cos 45^\circ + j \sqrt{\omega CR} \sin 45^\circ \\ &= \sqrt{\frac{\omega CR}{2}} + j \sqrt{\frac{\omega CR}{2}} \end{aligned}$$

$$\text{But } \gamma = \alpha + j\beta$$

$$\therefore \alpha \simeq \sqrt{\frac{\omega CR}{2}} \text{ nepers per mile} \quad (32)$$

$$\text{and } \beta \simeq \sqrt{\frac{\omega CR}{2}} \text{ radians per mile} \quad (33)$$

Example.—

An underground cable has the following constants :—

$$R = 44 \text{ ohms per mile loop,}$$

$$G = 1 \text{ micromho per mile,}$$

$$L = 0.001 \text{ henries per mile loop,}$$

$$C = 0.065 \text{ microfarads per mile.}$$

Find the approximate values of Z_0 , α and β at 400 c/s and 1600 c/s .

$$Z_0 \simeq \sqrt{\frac{R}{\omega C}} \angle -45^\circ$$

At 400 c/s, $\omega = 2500$ radians per second,

$$\therefore Z_0 \simeq \sqrt{\frac{44}{2500 \times 0.065 \times 10^{-6}}} \angle -45^\circ$$

$$\therefore Z_0 \simeq 520 \angle -45^\circ.$$

[Accurately, $Z_0 = 521 \angle -43^\circ 14'$]

At 1600 c/s, $\omega = 10,000$ radians per second,

$$\therefore Z_0 \simeq \sqrt{\frac{44}{10,000 \times 0.065 \times 10^{-6}}} \angle -45^\circ$$

$$\therefore Z_0 \simeq 260 \angle -45^\circ.$$

[Accurately, $Z_0 = 263 \angle -38^\circ 36'$]

It will be noted that the modulus of Z_0 for an unloaded underground cable approximates to a value that is inversely proportional to the square root of the frequency, whilst the angle approximates to $\angle -45^\circ$.

$$\alpha = \beta = \sqrt{\frac{\omega CR}{2}}.$$

At 400 c/s,

$$\alpha = \beta = \sqrt{\frac{2,500 \times 0.065 \times 10^{-6} \times 44}{2}} = 0.0598$$

Hence $\alpha = 0.0598$ nepers per mile.

$\beta = 0.0598$ radians per mile.

[Accurately, $\alpha = 0.0582$ nepers per mile

and $\beta = 0.0612$ radians per mile].

At 1600 c/s,

$$\alpha = \beta = \sqrt{\frac{10,000 \times 0.065 \times 10^{-6} \times 44}{2}} = 0.120$$

Hence $\alpha = 0.120$ nepers per mile.

$\beta = 0.120$ radians per mile.

[Accurately, $\alpha = 0.107$ nepers per mile

and $\beta = 0.134$ radians per mile].

It will be noted that for an unloaded underground cable at audio frequencies, α and β approximate to values directly proportional to the square root of the frequency.

LOADING OF LINES

Conditions for minimum attenuation

The attenuation constant α has been shown by equation 29 to be given by:—

$$\alpha = \sqrt{\frac{1}{2} [\sqrt{(R^2 + \omega^2 L^2)(G^2 + \omega^2 C^2)} + (RG - \omega^2 LC)]}$$

It will be seen that α depends on the four primary line constants in addition to the frequency under consideration.

Value of L for minimum attenuation.—To determine the value of L for minimum attenuation when L only may be varied, differentiate α with respect to L , and equate to zero.

$$\frac{d\alpha}{dL} = \frac{\frac{1}{2} \left[\frac{1}{2} \frac{2 \omega^2 L (G^2 + \omega^2 C^2)}{\sqrt{(R^2 + \omega^2 L^2) (G^2 + \omega^2 C^2)}} - \omega^2 C \right]}{\sqrt{\frac{1}{2} \left[\sqrt{(R^2 + \omega^2 L^2) (G^2 + \omega^2 C^2)} + (RG - \omega^2 LC) \right]}}$$

$$\therefore \frac{1}{2} \left[\frac{1}{2} \left\{ \frac{2 \omega^2 L (G^2 + \omega^2 C^2)}{\sqrt{(R^2 + \omega^2 L^2) (G^2 + \omega^2 C^2)}} - \omega^2 C \right\} \right] = 0.$$

Hence the condition for minimum attenuation is that:—

$$\frac{\omega^2 L (G^2 + \omega^2 C^2)}{\sqrt{(R^2 + \omega^2 L^2) (G^2 + \omega^2 C^2)}} - \omega^2 C = 0$$

i.e.,
$$\frac{L (G^2 + \omega^2 C^2)}{\sqrt{(R^2 + \omega^2 L^2) (G^2 + \omega^2 C^2)}} = C$$

i.e.,
$$\frac{L \sqrt{G^2 + \omega^2 C^2}}{\sqrt{R^2 + \omega^2 L^2}} = C$$

i.e.,
$$L \sqrt{G^2 + \omega^2 C^2} = C \sqrt{R^2 + \omega^2 L^2}$$

Squaring both sides:—

i.e.,
$$L^2 (G^2 + \omega^2 C^2) = C^2 (R^2 + \omega^2 L^2)$$

i.e.,
$$L^2 G^2 + \omega^2 C^2 L^2 = C^2 R^2 + \omega^2 C^2 L^2$$

i.e.,
$$L^2 G^2 = C^2 R^2$$

i.e.,
$$L = \frac{CR}{G} \quad (34)$$

Thus, if L is variable, the attenuation will be a minimum when:—

$$L = \frac{CR}{G} \text{ henries/mile}$$

This result is important because in practice L is normally less than this desired value, and hence the attenuation of a line can be reduced by artificially increasing L .

Value of C for minimum attenuation.—In a similar manner, if C is considered as the only variable, its value to give minimum attenuation may be determined by differentiating α with respect to C and equating to zero.

The result obtained in this case is:—

$$C = \frac{LG}{R} \text{ farads/mile} \quad (35)$$

In practice, C is normally already greater than the value given by $\frac{LG}{R}$, and to reduce the attenuation it would be necessary to decrease the capacity.

Values of R and G for minimum attenuation.—If either R or G is the only variable, no minimum is found by differentiating and equating to zero. When, however, $R = 0$ and $G = 0$, the attenuation is zero, as can be seen from equation 29; hence R and G should both be kept as small as possible.

Conditions for minimum distortion

If the received signal is not an exact replica of the transmitted signal, the signal is said to be "distorted."

There are three main causes of distortion along a transmission line. Distortion occurs when :—

- (1) The characteristic impedance of the line varies with frequency and the line is terminated in an impedance that does not vary with frequency in an identical manner.
- (2) The attenuation of the line varies with frequency, so that waves of different frequencies are attenuated by different amounts.
- (3) The velocity of propagation varies with frequency so that waves of different frequencies arrive at different times.

Distortion due to Z_0 varying with frequency.—It has been seen that :—

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} \quad (\text{equation 16})$$

$$\therefore Z_0 = \sqrt{\frac{R\left(1 + j\omega \frac{L}{R}\right)}{G\left(1 + j\omega \frac{C}{G}\right)}}$$

It will be seen that, when $LG = CR$, i.e., $\frac{L}{R} = \frac{C}{G}$, then .—

$$\left(1 + j\omega \frac{L}{R}\right) = \left(1 + j\omega \frac{C}{G}\right)$$

$$\therefore Z_0 = \sqrt{\frac{\bar{R}}{G} \angle 0^\circ} = \sqrt{\frac{\bar{L}}{C} \angle 0^\circ} \quad (41)$$

In such a case, Z_0 no longer depends on ω , is therefore independent of frequency, and is resistive.

Hence a line for which $\frac{L}{R} = \frac{C}{G}$ can readily be correctly terminated in its characteristic impedance at all frequencies, thus eliminating this form of distortion.

Distortion due to α varying with frequency.—It has been seen that :—

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)} \quad (\text{equation 21})$$

$$\therefore \gamma^2 = RG + j\omega (CR + LG) - \omega^2 LC \quad (42)$$

When $LG = CR$,

$$CR = LG = \sqrt{CRLG}$$

hence $(CR + LG) = 2\sqrt{CRLG}$

From equation 42:—

$$\gamma^2 = RG + 2j\omega \sqrt{RGLC} - \omega^2 LC$$

$$\therefore \gamma^2 = [\sqrt{RG} + j\omega \sqrt{LC}]^2$$

$$\therefore \gamma = \sqrt{RG} + j\omega \sqrt{LC}$$

$$\text{But } \gamma = \alpha + j\beta$$

Hence, when $LG = CR$,

$$\therefore \alpha = \sqrt{RG} \quad (43)$$

$$\text{and } \beta = \omega \sqrt{LC} \quad (44)$$

If $\alpha = \sqrt{RG}$, it is independent of frequency, hence there will be no distortion due to the attenuation varying with frequency.

Distortion due to velocity varying with frequency

The velocity of propagation $v = \frac{\omega}{\beta}$ (equation 15)

$$\text{When } \frac{L}{R} = \frac{C}{G}$$

$$\beta = \omega \sqrt{LC}$$

$$\text{Thus } v = \frac{\omega}{\omega \sqrt{LC}} = \frac{1}{\sqrt{LC}} \text{ miles per second.} \quad (45)$$

ω has now disappeared from the velocity equation, and hence v^* is independent of frequency.

The "distortionless condition"

$LG = CR$ is called the *distortionless condition* for a line; for when this relationship holds, the received signal is an exact replica of the sent signal, although reduced in amplitude and delayed by a constant time. It will be noted that this condition for minimum distortion is identical with that for minimum attenuation when either L or C may be varied. It is evident, then, that the transmission properties of a line can be greatly improved if either L can be increased or C decreased in order that this condition be fulfilled.

C depends on the construction of the line or the make-up of the cable and cannot readily be reduced. Attempts have therefore been concentrated on efforts to increase L . "Loading" is the

* When $\beta = \omega \sqrt{LC}$, the group velocity $\frac{d\omega}{d\beta}$ also equals $\frac{1}{\sqrt{LC}}$, and is therefore independent of frequency.

name given to the process whereby the inductance of the line is artificially increased to reduce the attenuation and distortion. There are two main types of loading in general use—continuous loading and lumped loading.

With regard to distortion alone, attempts have been made to satisfy the condition $LG = CR$ by increasing G . These have proved unsatisfactory, however, due to the fact that although increasing G reduces the distortion, it increases the attenuation.

Continuous loading

A tape of iron or some other magnetic material such as mumetal is wound round the conductor to be loaded, thus increasing the

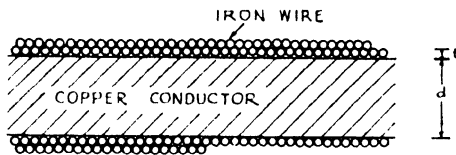


FIG. 739.—Continuous loading.

permeability of the surrounding medium and thereby increasing the inductance (see Fig. 739). It may be shown that the increase in inductance is:—

$$L \approx \frac{\mu}{\frac{d}{n \cdot t} + 1} \text{ mH}$$

where μ = permeability of iron wire.

d = diameter of copper conductor.

n = number of layers.

t = thickness per layer of iron wire.

If $\mu = 200$, $n = 2$, and $t = 0.005$ in., then the additional inductance per mile in terms of the diameter d of copper wire is given by Table XXI.


TABLE XXI

Type of conductor	d	Additional inductance per mile
40 lb. copper ..	0.05 in.	34 mH
70 lb. copper ..	0.066 in.	27 mH
100 lb. copper ..	0.079 in.	23.5 mH

This method may be used to give an increase in inductance up to approximately 100 millihenries per mile, but the cost is excessive due to the difficulties in construction. Further disadvantages are the large apparent increase in the primary constant R , due to eddy current losses and hysteresis losses in the magnetic material, and the fact that small differences in mechanical treatment or pressure between the tape and conductor cause large variations in the primary constants.

Continuous loading at the present time is used only on submarine cables, where the problem of making water-tight joints at loading points renders "lumped" loading difficult; further, repair of a break in the cable would probably result in an alteration in the loading coil spacing for that section and hence introduce irregularities.

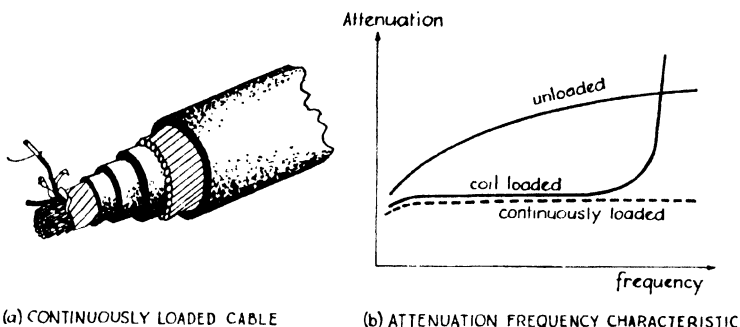The continuously loaded cable has the advantage over the lump-loaded cable, that its attenuation increases smoothly with increase in frequency; there is no "cut-off" frequency. (See Fig. 740b.)



(a) CONTINUOUSLY LOADED CABLE

(b) ATTENUATION FREQUENCY CHARACTERISTIC OF CABLE.

FIG. 740.

It has been found unnecessary to use continuous loading over the entire cable to obtain the required reduction in attenuation and distortion. Some submarine cables employ sections of continuously loaded cable separated by sections of unloaded cable, a typical length for the sections being 440 yds. In this way the benefits of continuous loading are obtained but the cost is greatly reduced. This system is known as "patch" loading.

Lumped loading

The inductance of a line may be increased by the introduction of inductance coils at uniform intervals along the line. Provided that the spacing is uniform the line behaves, at all frequencies up to a frequency called the "cut-off" frequency of the line, as if this added inductance were distributed uniformly along it. Above this cut-off frequency, the attenuation increases rapidly. The line, in fact, acts as if it were a low-pass filter.

Provided that a limited frequency range is permissible, this method of loading is more convenient than continuous loading. There is, however, a practical limit to the amount by which the inductance of the line may be increased to reduce attenuation: the inductance (or loading) coils have a certain resistance, and thus increasing L also increases R . Moreover, hysteresis and eddy current losses will occur in loading coils. These will cause a further apparent increase in R , and unless the coil is carefully designed, may introduce distortion. The resistances of several typical loading coils may be seen from Table XXII.

TABLE XXII
Characteristics of typical loading coils

Type	Inductance (mH)	Resistance (Ω)
Pots, loading, 2-coil, No. 2	4.6	2.3
Pots, loading, 2-coil, No. 3	88	10.0
G.P.O. type A88	88	3.0
G.P.O. type B88	88	4.3
G.P.O. type 506	250	5.6
G.P.O. type 582	250	10.5

Fig. 741*a* and *b* show the effect of loading on the attenuation and characteristic impedance of carrier quad cable at various frequencies. They also show the variation of attenuation and characteristic impedance with frequency for several other types of line.

Construction of loading coils

The most important features in loading coil design are low resistance, low core loss, maintenance of circuit balance, avoidance of interference between circuits, and (particularly for field work) small size.

The core is usually toroidal in shape, and made of permalloy or molybdenum-permalloy dust, bound by shellac. This form of core permits the construction of a coil of high inductance, having small dimensions, very low eddy current losses, and negligible external field which might otherwise cause interaction with neighbouring circuits.

The coil is wound of the largest gauge of wire consistent with small size, and each winding is divided into equal parts, so that exactly half the inductance can be inserted into each leg of the circuit. To avoid cross-talk, a high order of accuracy in balancing is necessary, and Fig. 742 shows the method of winding employed to ensure that the two parts of the winding are identical.

Loading coils are usually built into steel "pots," which are made in several standard sizes to accommodate one or more coils.

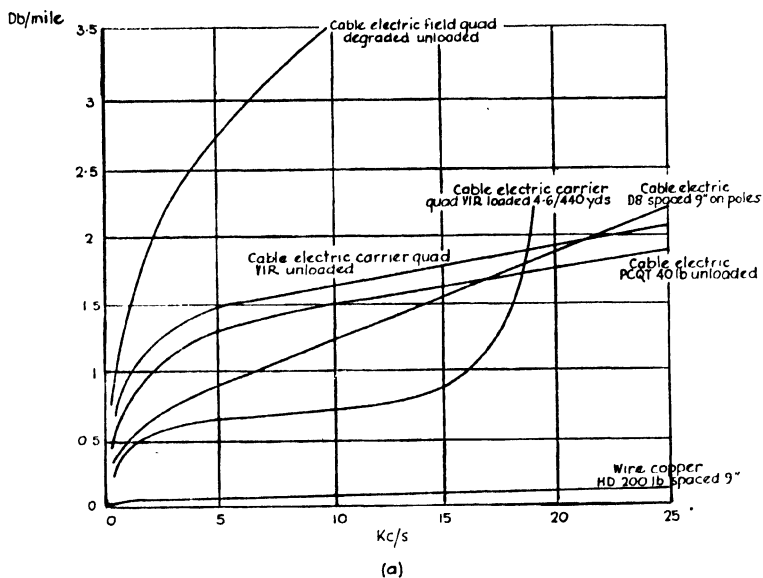


FIG. 741.—(a) Variation of attenuation with frequency for some army lines.

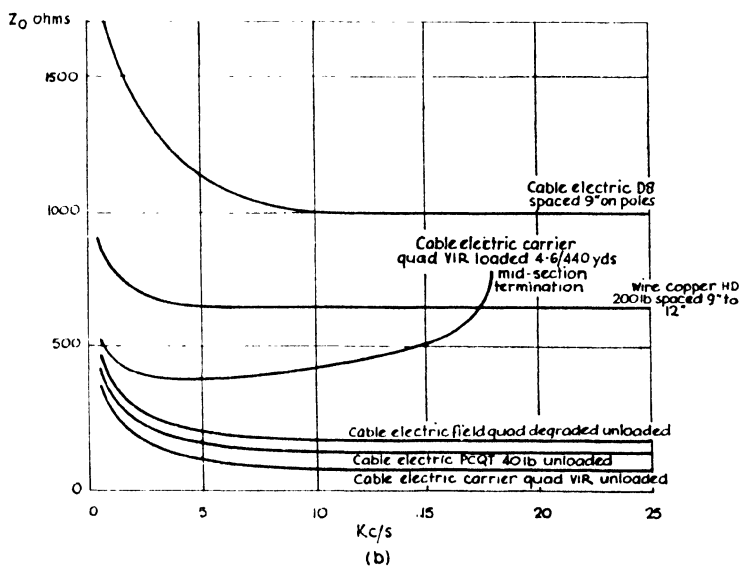


FIG. 741.—(b) Variation of $|Z_0|$ with frequency for some army lines.

LOADING

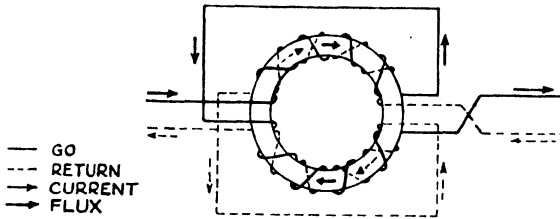


FIG. 742.—Winding of single loading coil, showing directions of current and flux.

In addition to giving the coils protection from the weather and from mechanical damage, the pots also screen the coils from external magnetic fields.

Important considerations in the use of loading coils

When installing loading coils, one must ensure not only that the circuit balance is maintained, but also that the inductances and spacings of the various coils on any circuit are all equal within fairly fine limits. In the case of repeated circuits, divergencies of more than about 2 per cent. from the mean value of inductance

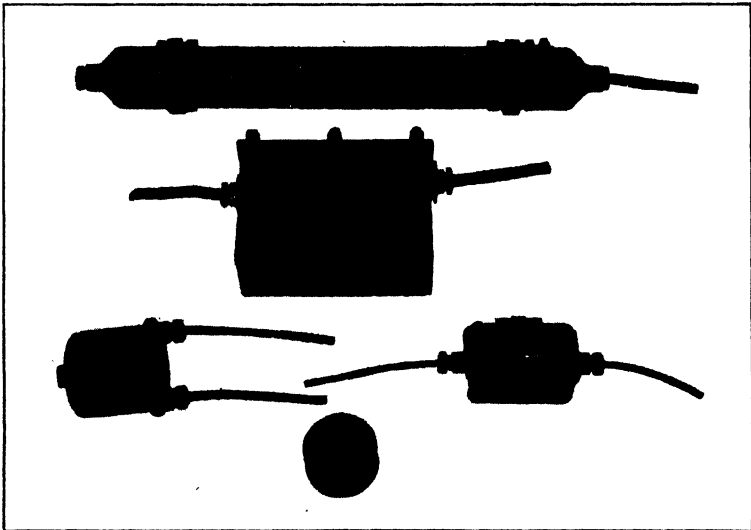


PLATE 36.—Loading coils.

or spacing will render the construction of accurate line balancing networks almost impossible, and so prevent the setting-up of a stable circuit with a good overall T.E., as explained in Chapter 21. When it is impossible to locate a coil at the correct distance, the effective length of a section of line may be artificially increased by a process of "building-out" as described below.

Care must always be taken that no winding is reversed, or it will neutralize the inductance of the other winding of the coil instead of adding to it.

When DC telegraphy is employed over a loaded circuit, the telegraph current must not exceed the maximum permissible for the coils in use, or permanent magnetisation may occur, causing a reduction in the effective inductance of the coils and also introducing distortion.

Building-out short loading circuits

When, for geographical and similar reasons, loading pots cannot be located at the correct spacing, short sections can be "built-out" to the correct electrical length. In the case of a long section, an additional loading point must be inserted, and the short section (or sections) resulting can then be built-out.

The principle of building-out is simply the addition of capacity and, if great precision is required, of resistance, at a convenient point in the section. The capacity must be added not only between the two legs of a pair, but also between all wires in a cable, and in

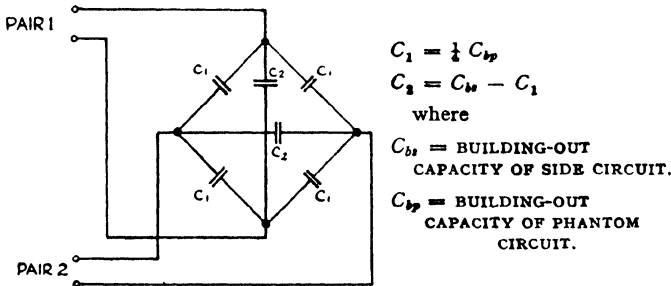


FIG. 743.—Building-out capacity.

the same proportion as the capacities of the cable. Thus, in the case of a quad, six capacities must be added as in Fig. 743.

The capacity C_b to be added is not simply equal to that of the "missing" portion of the section, but is given by the formula:—

$$C_b = C_s - d_1 C \tag{46}$$

where C_s is the lumped capacity that would simulate the distributed capacity per section,

d_1 is the length of the short section,

and C is the capacity per mile of the line.

In practice, the most convenient method of adding capacity is the use of "stub cables." These are short lengths of cable, usually made with a very high capacity, that can be bridged across or connected in series with the section to be built-out. Series connection adds resistance as well as capacity, but this is not usually necessary ; the parallel connection is the more common, as it permits convenient adjustment of the added capacity by varying the length of the "open" end of the stub. Separate resistance can, of course, be added in series with the conductors of the cable if required. When large values of capacity are to be added, several stubs may be connected in parallel to avoid excessive lengths of stub. In either case, the stub must be balanced against cross-talk in the same way as the main cable.

Side circuit and phantom circuit loading

Two metallic pairs between two places *A* and *B* may be utilized to provide three speech circuits by the use of the phantom circuit.

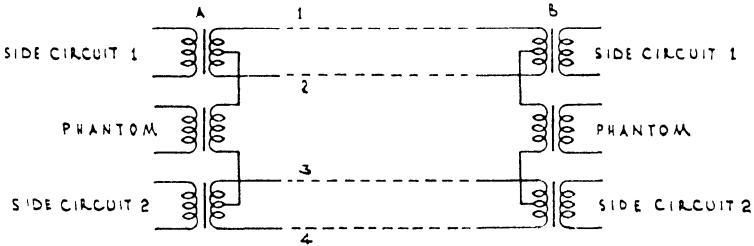


FIG. 744.—Side and phantom circuits.

This is usually tapped off at the line transformers at either end, as in Fig. 744.

Briefly, the reason that speech is possible on the phantom circuit without interference with the side circuits is that current arriving at the centre tap of the line transformer side circuit 1 at *A* splits equally, half travelling to *B* via line 1 and half via line 2. These two currents will produce no resultant magnetic flux in the iron

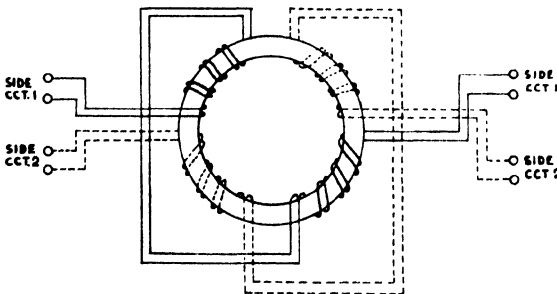


FIG. 745.—Windings of a phantom circuit loading coil.

cores of line transformers at either *A* or *B*, and hence no interference with the side circuit 1. The same applies to the return path *via* side circuit 2.

Since the two phantom currents in 1 and 2 are in the same direction, a loading coil such as is shown in Fig. 742 will have zero inductance since the two equal currents will produce equal and opposite magnetic fluxes. This loading coil, although satisfactory for the side circuit, will be useless as far as the phantom circuit is

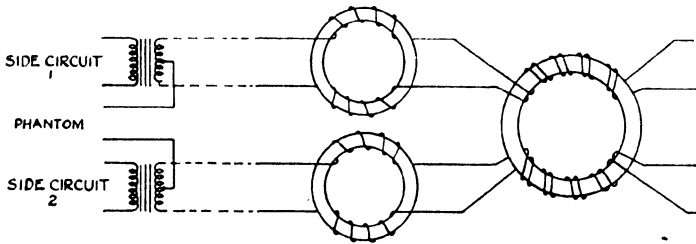


FIG. 746.—Arrangement of side and phantom loading coils.

concerned. If it is desired to load the phantom circuit, phantom loading coils must be used (see Fig. 745). When inserting such a loading coil, side circuit 1 would be treated as one line, and side circuit 2 as the other (see Fig. 746).

Cut-off frequency

A lump-loaded line acts as a low-pass filter, since the inductance is lumped instead of being uniformly distributed along the line.

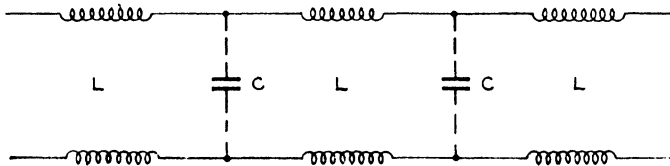


FIG. 747.—A loaded line shown as a low-pass filter.

The line can be represented approximately by Fig. 747. If the inductance of the line plus loading coil is L_s henries per loading coil section, and the capacity of the line per loading coil section is C_s , then the cut-off frequency f_c is given by :—

$$f_c = \frac{1}{\pi \sqrt{L_s C_s}} \tag{47}$$

Alternatively, if L is the apparent inductance of the line per mile after loading,

C is the capacity of the line per mile,
and d the loading coil spacing in miles.

$$\text{Then } L_s = Ld$$

$$C_s = Cd.$$

$$\text{Thus } f_c = \frac{1}{\pi d \sqrt{LC}} \quad (48)$$

Hence the coil spacing d must be less than $\frac{1}{\pi f \sqrt{LC}}$ where f is the highest working frequency.

It will be noted from equation 48 that :—

- (1) If the value of the loading coil inductance remains unchanged, the cut-off frequency is inversely proportional to the loading coil spacing.
- (2) If the loading coil spacing remains unchanged, the cut-off frequency is inversely proportional to the square root of the inductance of the loading coil (see Fig. 748).
- (3) If the loading coil inductance is multiplied by any amount and the spacing is divided by the same amount, there is no change in the cut-off frequency.
- (4) If the inductance of each coil, and the spacing between coils are both divided by a factor n , the cut-off frequency is increased by the same factor n .

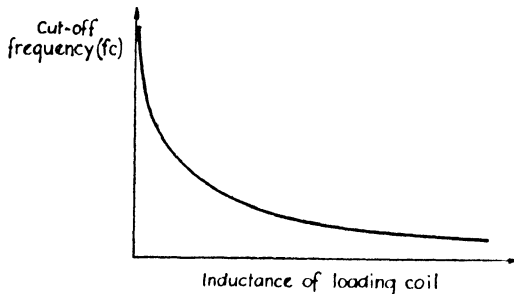


FIG. 748.—Effect on cut-off frequency of varying the inductance of the loading coils with fixed spacing.

Example.—Carrier quad cable, when loaded with 4.6 mH loading coils at 440 yds. spacing, has a cut-off frequency of 24,000 c/s.

- (a) What will be the cut-off frequency if the spacing is reduced to 110 yds? *Ans.* 48,000 c/s.
- (b) What will be the cut-off frequency if 18.4 mH loading coils are used at 440 yds. spacing? *Ans.* 12,000 c/s.
- (c) What will be the cut-off frequency if 18.4 mH loading coils are used at 110 yds. spacing? *Ans.* 24,000 c/s.
- (d) What will be the cut-off frequency if 2.3 mH loading coils are used at 220 yds. spacing? *Ans.* 48,000 c/s.

Half-coil and half-section terminations

It has been stated that a loaded line behaves in a similar manner to a low-pass filter. There will therefore be two methods of terminating such a line. If the line is terminated half-way along a loading coil section, an impedance Z_{02} will be obtained corresponding to $Z_{0\pi}$ for a low-pass filter. If the line is terminated in a loading coil having half the normal value, an impedance Z_{01} will be obtained corresponding to $Z_{0\pi}$ for a low-pass filter (see broken curves in Fig. 749).

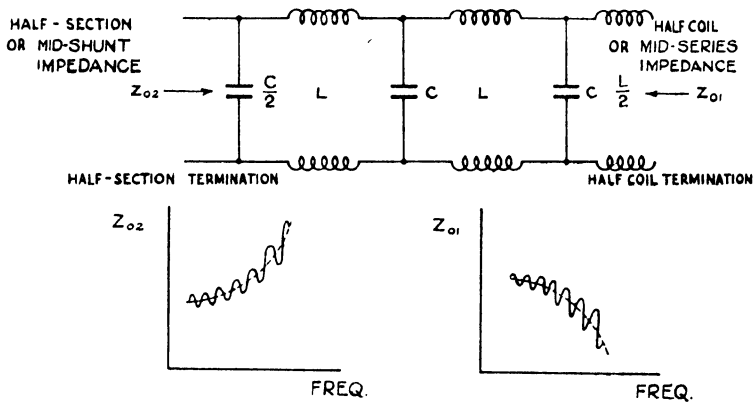


FIG. 749.—Variation in Z_{01} and Z_{02} with frequency.

In practice, the curves obtained for the input impedance of a loaded line, although having the same general shape as those corresponding to a low-pass filter, will not be smooth owing to the presence of points of reflection along the line (see full curves in Figs. 749).

Effect of lumped loading on a practical line

It is found in practice that lines can be made almost distortionless by loading only up to a fraction of the theoretical value, the final spacing and size of the coils being a compromise between the attempts to—

- (i) obtain a high cut-off frequency,
- (ii) use as few loading coils as possible,
- (iii) increase the resistance by as small amount as possible.

It has been shown that, to obtain a high cut-off frequency, small loading coils spaced at short intervals must be employed. If loading coil spacing is to be economical, this means that, for a given value of added inductance per mile, a definite limit is set to the cut-off frequency. For this reason loading is most commonly applied to underground cables carrying audio-frequency circuits. A typical form of loading in this case is the insertion of coils of 88 mH at

intervals of 2,000 yds., such a system being designated as "88 mH/2,000 yds." or "88 mH/1.136 miles." It should be noted that the value 88 mH is only a small fraction of that required to satisfy the distortionless condition $L = \frac{CR}{G}$.

Until recently, underground cables on main trunk routes were invariably loaded. In the case of multiple twin cables it was the usual practice to use and to load the phantom circuits. With starquad cables, the phantoms are seldom used, since the pair-to-pair capacity is too great for satisfactory lumped phantom loading.

With the introduction of carrier systems over underground cables, loading has ceased to be so important. At the higher frequencies used, even an unloaded line approaches the distortionless condition. In any case, all but the lightest of loading is out of the question owing to the high cut-off frequency required. The high attenuation of the unloaded cable is overcome by placing valve amplifiers (repeaters) at frequent intervals along the line. The distortion due to variation of attenuation with frequency is corrected by the use of "attenuation equalisers," and the distortion due to the variation of velocity with frequency is corrected by the use of "phase equalisers." Phase equalisers are used only on the highest grade circuits.

Airline is seldom loaded because the value of L is already approaching that required by the distortionless condition, and the introduction of loading would mean the introduction of further resistance into the circuit.

Loaded underground cables

If an underground cable were loaded up to the value $L = \frac{CR}{G}$,

then, as has been shown, Z_0 would be $\sqrt{\frac{R}{G}}$ and α would be \sqrt{RG} .

In practice such loading is impossible owing to the resistance of the loading coils and to the fact that in order to obtain a reasonable cut-off frequency, the loading coil spacing would be impracticable. Consider the example of an underground cable having the following constants:—

$$\begin{aligned} R &= 44 \text{ ohms per mile,} \\ G &= 1 \text{ micromho per mile,} \\ L &= 0.001 \text{ henries per mile,} \\ C &= 0.065 \text{ microfarads per mile.} \end{aligned}$$

In order to attain the distortionless condition, L must be increased to a value L' where:—

$$L' = \frac{0.065 \times 10^{-6} \times 44}{10^{-6}} = 2.86 \text{ henries per mile.}$$

This is more than 2,800 times the natural inductance of the line.

It is clearly impracticable to introduce such heavy loading ; for, supposing that this added inductance could be obtained with negligible added resistance, if it were added in the form of a single loading coil of 2.86 henries at one mile spacing, the cut-off frequency would be much too low for an audio circuit.

In this particular case,

$$f_0 = \frac{1}{\pi d \sqrt{L'C}} = \frac{1}{\pi \sqrt{2.86 \times 0.065 \times 10^{-6}}} = 740 \text{ c/s.}$$

In order to increase the inductance of the line by 2.86 henries per mile and still have a cut-off frequency of, say, 3000 c/s, it would be necessary to load the line using loading coils of 715 mH at intervals of 440 yards. Such heavy loading as this is, however, uneconomical, since a much lighter loading, such as 88 mH at intervals of 2,000 yards, will give a sufficient reduction both in distortion and in attenuation. In practice, the length of the loading section is usually standardised at 2,000 yards, and the loading coil inductance is standardised in several values ranging from 250 mH down to 2.3 mH, with 88 mH the most commonly used.

If the practical loading of 88 mH at 2,000 yard spacing is applied to the cable under consideration, the resultant inductance per mile is $\left(\frac{88}{1.136} + 1\right) = 78.5$ mH per mile, since the lumped inductance may be regarded as uniformly distributed.

In the range 400 to 3000 c/s :—

ωL varies between 200 and 1500, while $R = 44$ ohms.

ωC varies between 80×10^{-6} and 1250×10^{-6} , while

$G = 1 \times 10^{-6}$ mhos.

Thus $\omega L > R$, and $\omega C \gg G$ for a loaded underground cable, *i.e.*,

$\frac{R}{\omega L}$ and $\frac{G}{\omega C}$ are both small,—very small at high frequencies.

Under these conditions, approximate formulae may be found for Z_0 , α and β . These approximations are very useful in practice.

Practical formulae for Z_0 and γ for loaded underground cables

Characteristic Impedance Z_0

$$Z_0 = \sqrt[4]{\frac{R^2 + \omega^2 L^2}{G^2 + \omega^2 C^2}} \cdot \frac{1}{2} \left[\tan^{-1} \frac{G}{\omega C} - \tan^{-1} \frac{R}{\omega L} \right] \text{ (equation 18)}$$

$$\therefore Z_0 = \sqrt[4]{\frac{\omega^2 L^2 \left(1 + \frac{R^2}{\omega^2 L^2}\right)}{\omega^2 C^2 \left(1 + \frac{G^2}{\omega^2 C^2}\right)}} \cdot \frac{1}{2} \left[\tan^{-1} \frac{G}{\omega C} - \tan^{-1} \frac{R}{\omega L} \right]$$

$\frac{R}{\omega L}$ and $\frac{G}{\omega C}$ are both very small,

$$\therefore \left(1 + \frac{R^2}{\omega^2 L^2}\right) \simeq 1 \text{ and } \left(1 + \frac{G^2}{\omega^2 C^2}\right) \simeq 1$$

Also $\tan^{-1} \frac{R}{\omega L} \cong \frac{R}{\omega L}$ radians and $\tan^{-1} \frac{G}{\omega C} \cong \frac{G}{\omega C}$ radians

$$\begin{aligned} \therefore Z_0 &= \sqrt{\frac{\omega^2 L^2}{\omega^2 C^2}} / \frac{1}{2} \left(\frac{G}{\omega C} - \frac{R}{\omega L} \right) \\ \therefore Z_0 &= \sqrt{\frac{L}{C}} / \frac{1}{2} \left(\frac{G}{\omega C} - \frac{R}{\omega L} \right) \end{aligned} \quad (49)$$

The characteristic impedance will be seen to have a modulus that is independent of frequency, and to have only a very small angle.

More approximately, since the angle is very small :—

$$Z_0 \cong \sqrt{\frac{L}{C}} \angle 0^\circ \quad (50)$$

This last approximation is permissible for heavy loading ($\frac{G}{C} - \frac{R}{L} = 0$ is the distortionless condition), and also for the higher audio frequencies.

Propagation constant γ

$$\begin{aligned} \gamma &= \sqrt{(R + j\omega L)(G + j\omega C)} \quad (\text{equation 21}) \\ \text{i.e., } \gamma &= \sqrt{j\omega L \left(1 + \frac{R}{j\omega L}\right) j\omega C \left(1 + \frac{G}{j\omega C}\right)} \\ &= j\omega \sqrt{LC} \left[\left(1 + \frac{R}{j\omega L}\right) \left(1 + \frac{G}{j\omega C}\right) \right]^{\frac{1}{2}} \end{aligned}$$

Expanding by the binomial theorem,

$$\gamma = j\omega \sqrt{LC} \left[1 + \frac{R}{2j\omega L} + \dots \right] \left[1 + \frac{G}{2j\omega C} + \dots \right]$$

This is permissible because

$$\begin{aligned} \left| \frac{R}{j\omega L} \right| &= \frac{R}{\omega L} \ll 1 \\ \text{and } \left| \frac{G}{j\omega C} \right| &= \frac{G}{\omega C} \ll 1 \end{aligned}$$

Also, since $\frac{R}{\omega L}$ and $\frac{G}{\omega C}$ are small, second and higher order terms can be neglected, and therefore :—

$$\begin{aligned} \gamma &\cong j\omega \sqrt{LC} \left[1 + \frac{R}{2j\omega L} + \frac{G}{2j\omega C} \right] \\ \text{i.e., } \gamma &\cong \frac{R}{2} \sqrt{\frac{C}{L}} + \frac{G}{2} \sqrt{\frac{L}{C}} + j\omega \sqrt{LC} \end{aligned}$$

The attenuation α of a loaded cable is therefore :—

$$\alpha \cong \frac{R}{2} \sqrt{\frac{C}{L}} + \frac{G}{2} \sqrt{\frac{L}{C}} \text{ nepers per mile.} \quad (51)$$

Since ω no longer appears in the expression for α , the attenuation will be independent of frequency.

For loaded paper core cables (where G is negligible)

$$\alpha \simeq \frac{R}{2} \sqrt{\frac{C}{L}} = \frac{R}{2|Z_0|} \text{ nepers per mile.} \quad (52)$$

The phase constant β for a loaded cable is :—

$$\beta \simeq \omega \sqrt{LC} \text{ radians per mile.} \quad (53)$$

Thus velocity $v^* = \frac{1}{\sqrt{LC}}$, a value that is independent of frequency.

It will thus be seen from equations 51 and 53 that, although the loading is only a small fraction of the value required to make $L = \frac{CR}{G}$, the line approximates to the distortionless condition.

Example.—A 40 lb PCQT underground cable with constants :

$$R = 44 \text{ ohms per mile,}$$

$$G = 1 \text{ micromho per mile,}$$

$$L = 0.001 \text{ henries per mile,}$$

$$C = 0.065 \text{ microfarads per mile,}$$

is loaded with 88 mH loading coils of resistance 3.7 ohms at 2,000 yd. spacing. Find the approximate values of Z_0 , α and β .

The total inductance for 2,000 yds. is $(88 + 1.136)$ mH., *i.e.*, 89.14 mH.

Therefore the total inductance per mile is :—

$$L' = \frac{89.14}{1.136} = 78.5 \text{ mH.}$$

The total resistance per 2,000 yds. is $(44 \times 1.136 + 3.7)$ ohms, *i.e.*, 53.7 ohms.

Therefore the total resistance per mile is :—

$$R' = \frac{53.7}{1.136} = 47.3 \text{ ohms.}$$

Then $Z_0 \simeq \sqrt{\frac{L'}{C}} = \sqrt{\frac{78.5 \times 10^{-3}}{0.065 \times 10^{-6}}} = 1100$ ohms (using equation 50)

$$\alpha \simeq \frac{R'}{2} \sqrt{\frac{C}{L'}} + \frac{G}{2} \sqrt{\frac{L'}{C}} = \frac{47.3}{2 \times 1100} + 0.5 \times 10^{-6} \times 1100$$

i.e., $\alpha = 0.022$ nepers per mile = 0.191 db per mile

$$\text{and } \beta \simeq \omega \sqrt{L'C} = 10,000 \sqrt{78.5 \times 10^{-3} \times 0.065 \times 10^{-6}} \\ = 0.715 \text{ at } 1600 \text{ c/s.}$$

* In this case the group velocity $\frac{d\omega}{d\beta}$ is also $\frac{1}{\sqrt{LC}}$ and is independent of frequency.

i.e., $\beta = 0.715$ radians per mile at 1600 c/s

and $\beta = 0.179$ radians per mile at 400 c/s.

$$\therefore v = \frac{\omega}{\beta} = 14,000 \text{ miles/sec. at both frequencies.}$$

The following table shows these results for partial loading compared with those for the same line unloaded :—

TABLE XXIII

Freq.	Unloaded			Loaded 88 mH/2,000 yds.		
	Z_0	α Nepers/ mile	v miles/ sec.	Z_0	α Nepers/ mile	v miles/ sec.
400 c/s	520 \angle -43°	0.058	41,000	1100 \angle 0	0.022	14,000
1600 c/s	260 \angle -39°	0.107	74,000	1100 \angle 0	0.022	14,000

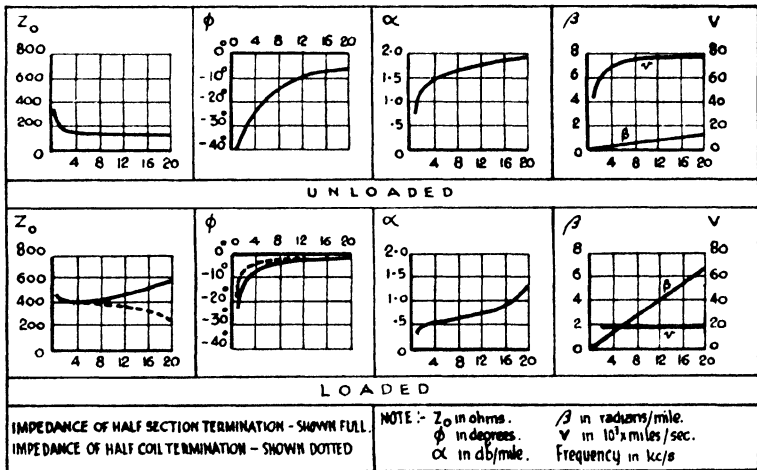


FIG. 750.—Secondary constants of carrier quad cable loaded 4.6 mH/440 yds.

Summary of effects of loading

The effects of loading on the secondary constants of a line may be summed up as follows :—

- (a) The characteristic impedance Z_0 is increased and becomes practically a pure resistance.

- (b) The attenuation constant α is reduced and becomes practically constant over the working range.
- (c) The phase constant β is increased, and the velocity of propagation is reduced to a value which is practically constant over the working range.

These effects may be seen from a comparison of the curves given in Fig. 750, which illustrate the secondary constants of carrier quad cable when unloaded and when loaded with 4.6 mH/440 yds.

REFLECTION

So far, current and voltage relationships have only been considered for infinite uniform lines, or uniform lines terminated in their characteristic impedances. If a line, at any point along its length, is joined to some impedance having a value other than Z_0 , part of the wave travelling down the line will be reflected back again from the point of discontinuity. In particular, if a line is uniform along its length but is terminated in an impedance Z_R , reflection will occur at the distant end. This reflection will be a maximum when the line is on open-circuit ($Z_R = \infty$) or short-circuit ($Z_R = 0$), and will be zero when $Z_R = Z_0$.

Before proceeding further to discuss the current and voltage relationships along such a line, the magnitude of the reflected wave will be considered in more detail in a general case.

Reflection coefficient

In general terms, it may be stated that reflection occurs wherever there is an impedance mis-match between two networks. Consider a generator network *A*, impedance Z_0 , working into a load network *B* impedance Z_R (see Fig. 751). According to the concept of reflection,

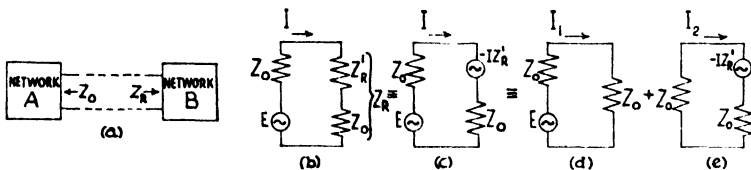


FIG. 751.

an "initial current" I_1 flows from the generator expecting to find a load equal to Z_0 . This current in a load Z_R produces a "reflected current" I_2 , flowing back from the load to the generator. The resultant current I in the steady state is therefore:—

$$I = I_1 + I_2$$

Applying Thévenin's Theorem, replace network *A* by a generator of EMF E and impedance Z_0 . Replace network *B* by the two

impedances Z_0 and Z'_R (Fig. 751b) such that:—

$$Z_0 + Z'_R = Z_R \quad (54)$$

Applying the Compensation Theorem, replace impedance Z'_R by a generator having zero internal impedance and an EMF equal at all times to $-IZ'_R$ (Fig. 751c).

$$\begin{aligned} \text{Thus} \quad \frac{E - IZ'_R}{2Z_0} &= I \\ \therefore \quad E &= I(2Z_0 + Z'_R) \end{aligned} \quad (55)$$

Applying the Superposition Theorem to Fig. 751c, the current may be considered as the sum of two currents: the current I_1 produced by the EMF E , and the current I_2 produced by the EMF $-IZ'_R$ (Figs. 751d and e).

From Fig. 751d:—

$$I_1 = \frac{E}{2Z_0} \quad (56)$$

From Fig. 751e:—

$$I_2 = \frac{-IZ'_R}{2Z_0} \quad (57)$$

Dividing (57) by (56):—

$$\frac{I_2}{I_1} = \frac{-IZ'_R}{E}$$

But from (55):—

$$\begin{aligned} E &= I(2Z_0 + Z'_R) \\ \therefore \quad \frac{I_2}{I_1} &= \frac{-IZ'_R}{I(2Z_0 + Z'_R)} \\ \therefore \quad \frac{I_2}{I_1} &= \frac{-Z'_R}{2Z_0 + Z'_R} \\ \therefore \quad \frac{I_2}{I_1} &= \frac{Z_0 - Z_R}{Z_0 + Z_R} \quad (\text{using equation 54}) \end{aligned} \quad (58)$$

$\frac{Z_0 - Z_R}{Z_0 + Z_R}$ is called the “reflection coefficient,” and gives the ratio of the “reflected” current to the “incident” current. In addition from equation (57),

$$\begin{aligned} \frac{I_2}{I} &= \frac{-Z'_R}{2Z_0} \\ &= \frac{Z_0 - Z_R}{2Z_0} \end{aligned} \quad (59)$$

Therefore $\frac{Z_0 - Z_R}{2Z_0}$ gives the ratio of reflected current to total current flowing.

Derivation of general line equations from reflection considerations

Consider a line of length l , and characteristic impedance Z_0 , that is terminated in Z_R at the distant end. Consider a generator of impedance Z_0 and EMF E connected to the sending end (Fig. 752);

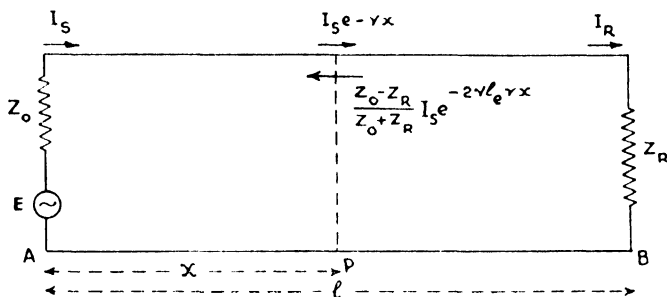


FIG. 752.—Reflected current in line terminated in Z_R .

let the sent current be I_s , and the received current be I_R . It is required to find the current and voltage at any point P distant x from the sending end.

The problem cannot be solved by using the infinite line equation directly because the line is neither infinitely long, nor terminated at the receiving end in Z_0 .

Consider the current at P .

The generator of EMF E may be considered to send a current wave along the line in the direction A to B , while a return current wave can be considered to be "reflected" back along the line from B to A . The current at P at any instant is the vector sum of these two currents.

Let the total current at P be I .

Let the incident current at P be I_1 , and the reflected current at P be I_2 .

Let γ be the propagation constant of the line.

Then :—

$$I_1 = I_s e^{-\gamma x}$$

$$= b e^{-\gamma x} \text{ where } b = I_s$$

Received current at B is given by :—

$$I_R = I_s e^{-\gamma l}$$

\therefore Reflected current at B is $\frac{Z_0 - Z_R}{Z_0 + Z_R} I_s e^{-\gamma l}$ (see equation 58)

$$\therefore I_2 = \frac{Z_0 - Z_R}{Z_0 + Z_R} I_s e^{-\gamma l} e^{-\gamma(l-x)}$$

$$= \frac{Z_0 - Z_R}{Z_0 + Z_R} I_s e^{-2\gamma l} e^{\gamma x}$$

$$\text{i.e. } I_2 = ae^{\gamma x} \text{ where } a = \frac{Z_0 - Z_R}{Z_0 + Z_R} I_s e^{-2\gamma l}$$

The total current I at point P is therefore :—

$$\begin{aligned} I &= I_1 + I_2 \\ \text{i.e. } I &= ae^{\gamma x} + be^{-\gamma x} \end{aligned}$$

$be^{-\gamma x}$ represents the wave starting from A and travelling towards B , and $ae^{\gamma x}$ represents the reflected wave starting from B and travelling towards A .

An expression of a similar general form can be derived for the voltage at P , but the mathematical treatment is rather more advanced. This will be considered from a different aspect in Chapter 17.

CHAPTER 17

MATHEMATICAL TREATMENT OF LINE TRANSMISSION

This chapter gives an alternative approach to some aspects of the subject of Line Transmission. In 1893 Kennelly and Steinmetz, working independently, introduced the use of hyperbolic functions of complex numbers in order to simplify the form of the results obtained. This chapter is intended to illustrate the use of these functions. It will be noted that many of the results obtained will have already been derived or assumed in the preceding chapter, but the use of hyperbolic functions will enable a more detailed study to be made.

DERIVATION OF THE GENERAL LINE EQUATIONS

It is required to obtain expressions for current, voltage and impedance, in the steady state, at any point along a line of any length having uniformly distributed electrical constants. Since the line may be terminated in an impedance not equal to its characteristic impedance, the result must take into account the possibility of reflection.

Let the line have length l , characteristic impedance Z_0 and propagation constant γ per mile.

Let R , G , L and C be the primary constants of the line per mile. It is assumed that they do not vary with frequency.

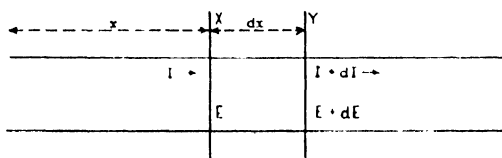


FIG. 753.—Short section XY , distant x from the sending end of a transmission line.

Consider a short section of line XY , of length dx , at a distance x from the sending end (*see* Fig. 753). By making dx very small, the current may be considered constant for voltage calculations, and the voltage constant for current calculations.

At X , let the voltage be E and the current I .

Then at Y , the voltage will be $E + dE$ and the current $I + dI$.

The series impedance of the small section dx will consist of

resistance Rdx and inductance Ldx . The shunt admittance will consist of leakage Gdx and capacitance Cdx .

Since dx is very small, the voltage drop from X to Y may be considered to be due to the current I flowing through the series impedance $Rdx + j\omega Ldx$. The decrease in current from X to Y may be considered to be due to the voltage E being applied to the shunt admittance $Gdx + j\omega Cdx$.

Consider voltage.

Potential difference between X and Y is due to current I flowing through series impedance elements Rdx and $j\omega Ldx$.

$$\begin{aligned} \text{Thus } E - (E + dE) &= IRdx + Ij\omega Ldx \\ \therefore -dE &= (R + j\omega L) I dx \\ \therefore -\frac{dE}{dx} &= (R + j\omega L) I \end{aligned} \quad (1)$$

Consider current.

Current difference between X and Y is due to voltage applied to shunt admittance elements Gdx and $j\omega Cdx$.

$$\begin{aligned} \text{Thus } I - (I + dI) &= EGdx + Ej\omega Cdx \\ \therefore -dI &= (G + j\omega C) E dx \\ \therefore -\frac{dI}{dx} &= (G + j\omega C) E \end{aligned} \quad (2)$$

To determine the current at distance x from sending end

Differentiate (2) with respect to x

$$\begin{aligned} -\frac{d^2I}{dx^2} &= (G + j\omega C) \frac{dE}{dx} \\ \therefore \frac{d^2I}{dx^2} &= (R + j\omega L) (G + j\omega C) I \quad [\text{from (1)}] \end{aligned} \quad (3)$$

To simplify notation,

$$\text{let } (R + j\omega L) (G + j\omega C) = P \text{ (say)} \quad (4)$$

Hence (3) becomes:—

$$\frac{d^2I}{dx^2} = P \cdot I \quad (5)$$

This is a differential equation the solution of which gives the value of current I at any point distance x down the line, its solution being:—

$$I = ae^{\sqrt{P}x} + be^{-\sqrt{P}x} \quad (6)$$

where a and b are constants.

This may be verified as follows:—

$$\begin{aligned} \text{If } I &= ae^{\sqrt{P}x} + be^{-\sqrt{P}x} \\ \frac{dI}{dx} &= a\sqrt{P}e^{\sqrt{P}x} - b\sqrt{P}e^{-\sqrt{P}x} \end{aligned}$$

$$\therefore \frac{d^2 I}{dx^2} = aPe^{\sqrt{P}x} + bPe^{-\sqrt{P}x}$$

$$\text{i.e., } \frac{d^2 I}{dx^2} = P [ae^{\sqrt{P}x} + be^{-\sqrt{P}x}]$$

$$\text{i.e., } \frac{d^2 I}{dx^2} = PI$$

Before proceeding to a general study of line transmission, some meaning must be given to the constants of equation 6. This can be done by considering a line of infinite length, since the current must become zero as the distance becomes infinite, i.e., $I \rightarrow 0$ as $x \rightarrow \infty$. Considering equation 6, this means $a = 0$, for the first term increases with x . Hence in an infinite line :—

$$I = be^{-\sqrt{P}x}$$

If the sending end current is I_s , then I must equal I_s when $x = 0$,

$$\therefore b = I_s$$

Hence the current at any point of an infinite line is :—

$$I = I_s e^{-\sqrt{P}x} \quad (7)$$

But the definition of the propagation constant γ of a line is such that, in an infinite line :—

$$I = I_s e^{-\gamma x} \quad (8)$$

Hence, comparing equations 7 and 8, it follows that :—

$$\gamma = \sqrt{P}$$

$$\text{Hence } \gamma = \sqrt{(R + j\omega L)(G + j\omega C)} \quad (9)$$

Thus γ may be determined from the values of the primary line constants. This verifies the result obtained by another method in the last chapter.

To determine the voltage at distance x from sending end

The voltage E can be obtained from equation 2.

$$\begin{aligned} E &= -\frac{1}{G + j\omega C} \cdot \frac{dI}{dx} \\ &= -\frac{1}{G + j\omega C} \cdot I_s (-\gamma) e^{-\gamma x} \\ &= I_s \cdot \frac{\gamma}{G + j\omega C} \cdot e^{-\gamma x} \end{aligned}$$

But $\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$ from equation 9.

$$\therefore E = I_s \sqrt{\frac{R + j\omega L}{G + j\omega C}} e^{-\gamma x} \quad (10)$$

The sending-end voltage E_s can be obtained by putting $x = 0$.

$$\text{hence } E_s = I_s \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$\text{i.e.,} \quad \frac{E_s}{I_s} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

But by definition the ratio $\frac{E_s}{I_s}$ in an infinite line is its characteristic impedance Z_0 .

$$\text{Hence} \quad Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} \quad (11)$$

This again verifies a previous result.

These results were obtained by considering an infinite line; the general case of a finite line is given by equation 6, which may now be written:—

$$I = ae^{\gamma x} + be^{-\gamma x} \quad (12)$$

Equation 12 can now be expressed using hyperbolic functions.

$$\text{Put } e^{\gamma x} = \cosh \gamma x + \sinh \gamma x$$

$$\text{and } e^{-\gamma x} = \cosh \gamma x - \sinh \gamma x.$$

Equation 12 therefore now becomes:—

$$I = (a + b) \cosh \gamma x + (a - b) \sinh \gamma x.$$

This may be further simplified by putting $a + b = A$, and $a - b = B$, giving

$$I = A \cosh \gamma x + B \sinh \gamma x. \quad (13)$$

The voltage may now be found in these terms from equation 2.

$$\begin{aligned} E &= -\frac{1}{G + j\omega C} \cdot \frac{dI}{dx} \\ &= -\frac{1}{G + j\omega C} (A\gamma \sinh \gamma x + B\gamma \cosh \gamma x) \\ &= -\frac{\gamma}{G + j\omega C} (A \sinh \gamma x + B \cosh \gamma x) \\ E &= -Z_0 (A \sinh \gamma x + B \cosh \gamma x) \end{aligned} \quad (14)$$

$$\text{since } \gamma = \sqrt{(R + j\omega L)(G + j\omega C)} \quad \text{and} \quad Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

Equations 13 and 14 may be used to find the current and voltage at any point along a line, if the constants A and B can be determined. This is usually done from a knowledge of the conditions at one end of the line.

Determination of constants A and B

(a) *If conditions at sending end of the line are known.*

Let I_s be the current at the sending end, and E_s be the voltage at the sending end.

But at sending end $x = 0$.

Thus equation 13 becomes:—

$$I_s = A \cosh \gamma 0 + B \sinh \gamma 0$$

$$\begin{aligned} \text{i.e.,} \quad I_s &= A \times 1 + B \times 0 \\ \text{i.e.,} \quad A &= I_s \end{aligned} \tag{15}$$

Similarly, equation 14 becomes :—

$$\begin{aligned} E_s &= -BZ_0 \cosh \gamma 0 - AZ_0 \sinh \gamma 0 \\ \text{i.e.,} \quad E_s &= -BZ_0 \times 1 - AZ_0 \times 0 \\ \text{i.e.,} \quad E_s &= -BZ_0 \\ \text{i.e.,} \quad B &= -\frac{E_s}{Z_0} \end{aligned} \tag{16}$$

Thus A and B are expressible in terms of the current and voltage at the sending end. Substituting these values for A and B in equations 13 and 14 gives :—

$$I = I_s \cosh \gamma x - \frac{E_s}{Z_0} \sinh \gamma x \tag{17}$$

$$\text{and } E = E_s \cosh \gamma x - I_s Z_0 \sinh \gamma x \tag{18}$$

(b) *If conditions at receiving end of the line are known.*

Let I_R be the current at the receiving end, and E_R the voltage at the receiving end.

But at the receiving end $x = l$.

Thus equation 13 becomes :—

$$I_R = A \cosh \gamma l + B \sinh \gamma l. \tag{19}$$

Similarly, equation 14 becomes :—

$$E_R = -BZ_0 \cosh \gamma l - AZ_0 \sinh \gamma l \tag{20}$$

From equations 19 and 20 :—

$$\frac{I_R - A \cosh \gamma l}{E_R + AZ_0 \sinh \gamma l} = \frac{B \sinh \gamma l}{-BZ_0 \cosh \gamma l}$$

$$\therefore -I_R Z_0 \cosh \gamma l + AZ_0 \cosh^2 \gamma l = E_R \sinh \gamma l + AZ_0 \sinh^2 \gamma l$$

$$\therefore A = \frac{E_R}{Z_0} \sinh \gamma l + I_R \cosh \gamma l \tag{21}$$

Similarly :—

$$\frac{I_R - B \sinh \gamma l}{E_R + BZ_0 \cosh \gamma l} = \frac{A \cosh \gamma l}{-AZ_0 \sinh \gamma l}$$

$$\therefore -I_R Z_0 \sinh \gamma l + BZ_0 \sinh^2 \gamma l = E_R \cosh \gamma l + BZ_0 \cosh^2 \gamma l$$

$$\therefore B = -I_R \sinh \gamma l - \frac{E_R}{Z_0} \cosh \gamma l \tag{22}$$

Substitute in equation 13 for A and B :—

$$\begin{aligned} I &= \left[I_R \cosh \gamma l + \frac{E_R}{Z_0} \sinh \gamma l \right] \cosh \gamma x \\ &\quad - \left[I_R \sinh \gamma l + \frac{E_R}{Z_0} \cosh \gamma l \right] \sinh \gamma x \end{aligned}$$

$$\text{i.e.,} \quad I = I_R \cosh \gamma (l - x) + \frac{E_R}{Z_0} \sinh \gamma (l - x) \quad (23)$$

Substitute in equation 14 for A and B :—

$$E = \left[I_R Z_0 \sinh \gamma l + E_R \cosh \gamma l \right] \cosh \gamma x \\ - \left[I_R Z_0 \cosh \gamma l + E_R \sinh \gamma l \right] \sinh \gamma x$$

$$\text{i.e.,} \quad E = E_R \cosh \gamma (l - x) + I_R Z_0 \sinh \gamma (l - x) \quad (24)$$

Equations 17 and 18 are the general line equations expressing respectively the current and voltage at a point distant x from the sending end in terms of the sent current and the sent voltage.

Equations 23 and 24 are the general line equations in another form, but this time the current and voltage at a point distant x from the sending end are expressed in terms of the received current and voltage. Clearly then, equations 23 and 24 can be applied only to a line of finite length, whilst equations 17 and 18 apply also to an infinite line.

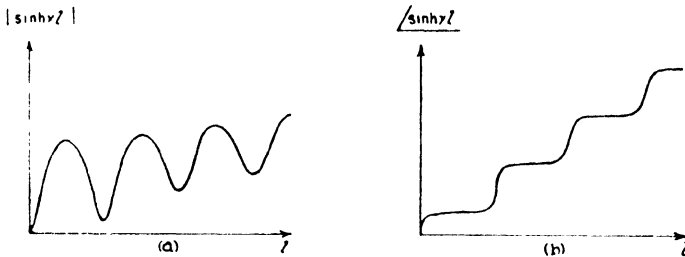


FIG. 754.—Curves of $|\sinh \gamma l|$ and $\angle \sinh \gamma l$ plotted against l .

Since γ is a complex quantity, both $|\sinh \gamma l|$ and $|\cosh \gamma l|$ will be curves of the characteristic shape shown in Figs. 754 and 755. For convenience in calculation, $\sinh \gamma l$ and $\cosh \gamma l$ may be evaluated in the form $A + jB$ by expanding :—

$$\sinh \gamma l = \sinh (\alpha + j\beta) l \\ = \sinh \alpha l \cdot \cosh j\beta l + \cosh \alpha l \cdot \sinh j\beta l \\ \text{i.e.,} \quad \sinh \gamma l = \sinh \alpha l \cdot \cos \beta l + j \cdot \cosh \alpha l \cdot \sin \beta l \quad (25)$$

$$\text{and} \quad \cosh \gamma l = \cosh (\alpha + j\beta) l \\ = \cosh \alpha l \cdot \cosh j\beta l + \sinh \alpha l \cdot \sinh j\beta l \\ \text{i.e.,} \quad \cosh \gamma l = \cosh \alpha l \cdot \cos \beta l + i \cdot \sinh \alpha l \cdot \sin \beta l \quad (26)$$

Example.—

$$\sinh (0.6 + j \cdot 2.9) = \sinh 0.6 \cdot \cos 2.9 + j \cdot \cosh 0.6 \cdot \sin 2.9 \\ = -0.6367 \cdot 0.9710 + j \cdot 1.1855 \cdot 0.2392 \\ = -0.6183 + j \cdot 0.2836 \quad \text{Ans.}$$

$$\begin{aligned} \cosh (0.6 + j.2.9) &= \cosh 0.6 . \cos 2.9 + j . \sinh 0.6 . \sin 2.9 \\ &= -1.1855 . 0.9710 + j . 0.6367 . 0.2392 \\ &= -1.152 + j . 0.1524 \quad \text{Ans.} \end{aligned}$$

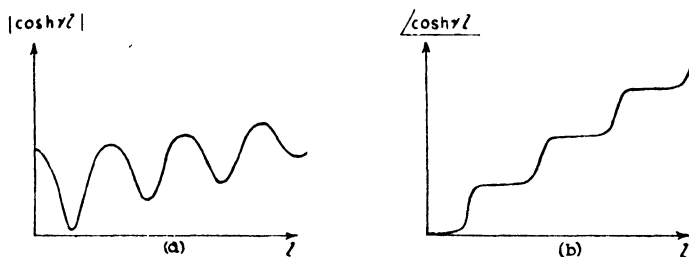


FIG. 755.—Curves of $|\cosh \gamma l|$ and $\angle \cosh \gamma l$ plotted against l .

Example.—

An open-wire line has, at 1000 c/s, a characteristic impedance Z_0 of $730 \angle -11^\circ$ and a propagation constant $\gamma = 0.012 + j.0.058$.

When 2 volts are applied to the sending end, a current of 4 milliamps flows. What will be the current at the distant end 50 miles away?

It will be noted that the value of the terminating impedance is not given. If required, it could be calculated from the information given. From equation 17 :—

$$\begin{aligned} I &= I_s \cosh \gamma x - \frac{E_s}{Z_0} \sinh \gamma x \\ \therefore I_R &= \frac{4}{1000} \cosh 50 (0.012 + j.0.058) \\ &\quad - \frac{2}{730 \angle -11^\circ} \sinh 50 (0.012 + j.0.058) \\ &= 0.004 . \cosh (0.6 + j.2.9) \\ &\quad - (0.002689 + j.0.0005229) . \sinh (0.6 + j.2.9) \\ &= 0.004 (-1.152 + j.0.1524) \\ &\quad - (0.002689 + j.0.0005229) . (-0.6183 + j.0.2836) \\ &= -0.002797 + j.0.00017 \\ &= 0.0028 \angle 176^\circ 35' \end{aligned}$$

Thus the current at the receiving end of the line is 2.8 milliamps, leading by $176^\circ 35'$ on the sent current. *Ans.*

APPLICATION OF THE GENERAL LINE EQUATIONS TO PARTICULAR CASES

Case (i). Finite line of length l , terminated in Z_0

At the distant end (*i.e.*, where $x = l$), let the current be I_R and the voltage E_R .

Now E_R can be found in terms of the sent current and voltage by substituting $x = l$ in equation 18.

$$\text{i.e., } E_R = E_s \cosh \gamma l - I_s Z_0 \sinh \gamma l \quad (27)$$

and I_R is found by putting $x = l$ in (17)

$$\text{i.e., } I_R = I_s \cosh \gamma l - \frac{E_s}{Z_0} \sinh \gamma l \quad (28)$$

$$\text{Thus } \frac{E_R}{I_R} = Z_0 \frac{E_s \cosh \gamma l - I_s Z_0 \sinh \gamma l}{I_s Z_0 \cosh \gamma l - E_s \sinh \gamma l}$$

But since the terminating impedance is Z_0 , it follows that:—

$$\begin{aligned} \frac{E_R}{I_R} &= Z_0 \\ \text{Thus } Z_0 \frac{E_s \cosh \gamma l - I_s Z_0 \sinh \gamma l}{I_s Z_0 \cosh \gamma l - E_s \sinh \gamma l} &= Z_0 \\ \therefore E_s \cosh \gamma l - I_s Z_0 \sinh \gamma l &= I_s Z_0 \cosh \gamma l - E_s \sinh \gamma l \\ \therefore \frac{E_s}{I_s} &= Z_0 \frac{\cosh \gamma l + \sinh \gamma l}{\cosh \gamma l + \sinh \gamma l} \\ \therefore \frac{E_s}{I_s} &= Z_0 \end{aligned} \quad (29)$$

But $\frac{E_s}{I_s}$ is the input impedance of the line.

$$\text{Thus } Z_{in} = Z_0 \quad (30)$$

That is to say, the input impedance of a finite line terminated in its characteristic impedance Z_0 is the characteristic impedance Z_0 .

Now consider the general equation for current I .

From equation 17:—

$$I = I_s \cosh \gamma x - \frac{E_s}{Z_0} \sinh \gamma x$$

$$\text{But } Z_0 = \frac{E_s}{I_s} \text{ (from equation 29)}$$

Substituting for Z_0 :—

$$\begin{aligned} I &= I_s \cosh \gamma x - E_s \cdot \frac{I_s}{E_s} \sinh \gamma x \\ &= I_s (\cosh \gamma x - \sinh \gamma x) \\ &= I_s \cdot e^{-\gamma x} \end{aligned} \quad (31)$$

This is the same expression as that giving the current at a point distant x along an infinite line.

Similarly, the general equation for the voltage E can be found:—

$$E = E_s \cosh \gamma x - I_s Z_0 \sinh \gamma x.$$

But $Z_0 = \frac{E_s}{I_s}$ (from equation 29)

$$\begin{aligned} \therefore E &= E_s \cosh \gamma x - I_s \cdot \frac{E_s}{I_s} \sinh \gamma x \\ &= E_s (\cosh \gamma x - \sinh \gamma x) \end{aligned}$$

$$\therefore E = E_s e^{-\gamma x} \tag{32}$$

which is the same expression as that giving the voltage at a point distant x along an infinite line.

Hence with regard to current, voltage and impedance, a short line terminated in its characteristic impedance behaves as an infinite line. This verifies the assumption made in the previous chapter.

Case (ii). Finite line of length l , open-circuited at distant end

In the case of an open-circuited line, the current at the distant end (I_R) is zero.

Thus when $x = l$, equation 17 becomes :—

$$0 = I_s \cosh \gamma l - \frac{E_s}{Z_0} \sinh \gamma l$$

$$\therefore \frac{E_s}{I_s} = Z_0 \frac{\cosh \gamma l}{\sinh \gamma l} = Z_0 \coth \gamma l$$

But $\frac{E_s}{I_s}$ is the input impedance of the line. In the special case of an open-circuited line call it Z_{oo} .

$$\text{Then } Z_{oo} = Z_0 \coth \gamma l. \tag{33}$$

Note that when γl is very large, $\coth \gamma l \rightarrow 1$. Hence Z_{oo} approaches Z_0 if l is made very large.

Case (iii). Finite line of length l , short-circuited at the distant end

In the case of a short-circuited line, the voltage at the distant end (E_R) is zero.

Thus when $x = l$, equation 27 becomes :—

$$0 = E_s \cosh \gamma l - I_s Z_0 \sinh \gamma l$$

$$\text{i.e., } \frac{E_s}{I_s} = Z_0 \frac{\sinh \gamma l}{\cosh \gamma l} = Z_0 \tanh \gamma l$$

But $\frac{E_s}{I_s}$ is the input impedance of the line. In the special case of a short-circuited line, call it Z_{so} .

$$\text{Then } Z_{so} = Z_0 \tanh \gamma l. \tag{34}$$

Note that when γl is very large, $\tanh \gamma l \rightarrow 1$. Hence Z_{so} approaches Z_0 if l is made very large.

Multiply equations 33 and 34 :—

$$Z_{oo} \cdot Z_{so} = Z_0^2 \coth \gamma l \cdot Z_0 \tanh \gamma l.$$

$$\therefore Z_{oo} \cdot Z_{so} = Z_0^2$$

$$\text{Hence } Z_0 = \sqrt{Z_{oo} \cdot Z_{so}} \quad (35)$$

Thus for any uniform and symmetrical line the characteristic impedance is the geometric mean of the open- and short-circuit impedances. This verifies the result obtained in the previous chapter.

Dividing equation 34 by equation 33 gives :—

$$\frac{Z_{so}}{Z_{oo}} = \frac{Z_0 \tanh \gamma l}{Z_0 \coth \gamma l} = \tanh^2 \gamma l$$

$$\therefore \tanh \gamma l = \sqrt{\frac{Z_{so}}{Z_{oo}}} \quad (36)$$

Example.—

A line 10 miles long has the following constants :—

$$Z_0 = 600 \angle 0^\circ$$

$$\alpha = 0.1 \text{ nepers per mile.}$$

$$\beta = 0.05 \text{ radians per mile.}$$

Find the received current and voltage when 20 milliamperes are sent into one end, and the receiving end is short-circuited.

The general line equation for voltage (equation 18) states :—

$$E = E_s \cdot \cosh \gamma x - I_s Z_0 \cdot \sinh \gamma x$$

But $E = 0$ at $x = 10$ miles, due to the short-circuit.

$$\therefore 0 = E_s \cdot \cosh \gamma \cdot 10 - I_s Z_0 \cdot \sinh \gamma \cdot 10$$

$$\therefore E_s = \frac{I_s Z_0 \cdot \sinh \gamma \cdot 10}{\cosh \gamma \cdot 10}$$

The general line equation for current (equation 17) states :—

$$\begin{aligned} I &= I_s \cdot \cosh \gamma \cdot x - \frac{E_s}{Z_0} \cdot \sinh \gamma \cdot x \\ &= 20 \cdot \cosh \gamma \cdot 10 - \frac{I_s Z_0 \cdot \sinh \gamma \cdot 10}{Z_0 \cdot \cosh \gamma \cdot 10} \cdot \sinh \gamma \cdot 10 \\ &= \frac{20}{\cosh \gamma \cdot 10} (\cosh^2 \gamma \cdot 10 - \sinh^2 \gamma \cdot 10) \\ &= \frac{20}{\cosh (1 + j \cdot 0.5)} \\ &= \frac{20}{1.354 + j \cdot 0.564} \\ &= 12.6 - j \cdot 5.25 \\ &= 13.65 \angle -22^\circ 30' \text{ Ans.} \end{aligned}$$

Thus the received voltage is zero, and the received current is 13.65 milliamperes, lagging behind the sent current by $22^\circ 30'$.

Practical application of the above formulae

Equations 35 and 36 enable the primary and secondary line constants of a transmission line to be calculated from the measured

values of the open- and short-circuit impedances of a known length of line.

For suppose the modulus and angle of both Z_{oo} and Z_{so} are found by measurement, then Z_0 will be determined from equation 35, which is a vector equation, and will give both the modulus and angle of Z_0 . Similarly, the right-hand side of equation 36 will be a vector quantity, which may be changed into the rectangular form. *i.e.*, $\tanh \gamma l = A + jB$ where A and B are known. (37)

It has been shown (Chapter 2, page 97) that in this case :—

$$\tanh 2\alpha l = \frac{2A}{1 + A^2 + B^2} \quad (38)$$

$$\text{and } \tan 2\beta l = \frac{2B}{1 - (A^2 + B^2)} \quad (39)$$

From equations 38 and 39 (*see also* Appendix II), αl and βl may be deduced, and if the length of the line is known, α and β may be found. αl may be determined from tables, or as follows :—

$$\text{Let } \tanh 2\alpha l = \frac{2A}{1 + A^2 + B^2} = C$$

$$\text{Then } \frac{e^{4\alpha l} - 1}{e^{4\alpha l} + 1} = C$$

$$\therefore e^{4\alpha l} (1 - C) = 1 + C$$

$$\therefore e^{4\alpha l} = \frac{1 + C}{1 - C}$$

$$\therefore \alpha l = \frac{1}{4} \log_e \left(\frac{1 + C}{1 - C} \right) \quad (40)$$

From β , the wavelength $\lambda (= \frac{2\pi}{\beta})$ and the velocity of propagation $v (= \frac{\omega}{\beta})$ may be calculated.

Further, γ is now known ($\gamma = \alpha + j\beta$), and multiplying equations 9 and 11 :—

$$Z_0 \gamma = R + j\omega L \quad (41)$$

Also, by dividing 9 by 11 :—

$$\frac{\gamma}{Z_0} = G + j\omega C \quad (42)$$

From 41 and 42 the four primary constants may be determined.

Example.—

Impedance measurements made on a 440-yard length of field quad cable at 1600 c/s ($\omega = 10,000$) under open-circuit and short-circuit conditions gave the following results :—

$$Z_{oc} = 2460 \angle -86^\circ 30'; \quad Z_{sc} = 21.5 \angle 14^\circ$$

Calculate Z_0 , α , β , R , G , L and C .

From (35) : $Z_0 = \sqrt{Z_{00} \cdot Z_{80}} = \sqrt{21.5 \times 2460} \angle -36^\circ 15'$
i.e., $Z_0 = 230 \angle -36^\circ 15'$

From (36) : $\tanh \gamma l = \sqrt{\frac{Z_{80}}{Z_{00}}} = \sqrt{\frac{21.5}{2460}} \angle 50^\circ 15' = 0.0935 \angle 50^\circ 15'$
 $= 0.0598 + j0.0719 = A + jB$

From (38) : $\tanh 2\alpha l = \frac{2A}{1 + A^2 + B^2} = \frac{0.1196}{1.009} = 0.1185$

\therefore From (40) : $\alpha l = \frac{1}{4} \log_e \frac{1+0.1185}{1-0.1185} = \frac{1}{4} \log_e \frac{1.1185}{0.8815} = 0.060$

But $l = 0.25$ miles

$\therefore \alpha = 0.240$ nepers/mile

From (39) : $\tan 2\beta l = \frac{2B}{1 - (A^2 + B^2)} = \frac{0.1438}{0.9912} = 0.1452$

$\therefore 2\beta l = 8^\circ 16' \pm n\pi$, where n is zero or a positive integer.

i.e., $2\beta l = 0.1443 \pm n\pi$ radians.

But $l = 0.25$ miles

$\therefore \beta = 0.289 \pm 2n\pi$ radians/mile.

In order to determine the correct value of n , it is necessary to make one more observation.

(i) *Either* estimate the approximate velocity of propagation in the cable at the frequency considered,

(ii) *or* estimate the loop resistance per mile of the line.

These two methods of approach will be taken in turn.

(i) The velocity of propagation for airline at 1600 c/s is approximately 170,000 miles per second, and for loaded cable approximately 10,000 miles per second. For field quad cable it will be somewhere between these values—estimate it at roughly 50,000 miles per second.

Since $v = \frac{\omega}{\beta}$, $v \simeq 50,000$, and $\omega = 10,000$,

$\therefore \beta = 0.2$ radians per mile (approx.)

$\therefore n = 0$, and the correct value of β is:—

$\beta = 0.289$ radians per mile.

(ii) Measuring the DC resistance of the 440 yard loop, the result was 20.4 ohms, giving a DC resistance of 81.6 ohms per mile loop.

The method is to calculate the AC loop resistance R using $\beta = 0.289 \pm 2n\pi$ and see which value of n gives the nearest agreement between R and the measured DC loop resistance.

$$\begin{aligned} \text{Thus } \gamma &= 0.240 + j(0.289 \pm 2n\pi) \\ Z_0 &= 230 \angle -36^\circ 15' = 186 - j136 \\ R + j\omega L &= \gamma Z_0 = [186 - j136] [0.240 + j(0.289 \pm 2n\pi)] \\ \therefore R &= 186 \cdot 0.240 + 136(0.289 \pm 2n\pi) \\ &= 44.6 + 39.3 \pm 854n \\ &= 83.9 \pm 854n \end{aligned}$$

Since the DC loop resistance is 81.6 ohms, the correct value of n is $n = 0$, giving $\beta = 0.289$ as before.

Having established the correct value of β , proceed as follows:—

$$\begin{aligned} \gamma &= 0.240 + j0.289 = 0.3756 \angle 50^\circ 26' \\ Z_0 &= 230 \angle -36^\circ 15' \\ \therefore R + j\omega L &= \gamma Z_0 = 230 \times 0.3756 \angle 14^\circ 11' \\ &= 83.8 + j21.0 \end{aligned}$$

Hence $R = 83.8$ ohms per mile

and $\omega L = 21.0$

$\therefore L = 2.1$ mH per mile.

Similarly:—

$$\begin{aligned} G + j\omega C &= \frac{\gamma}{Z_0} = \frac{0.3756}{230} \angle 86^\circ 41' \\ &= 0.000094 + j0.00163 \end{aligned}$$

$\therefore G = 0.000094$ mhos per mile.

and $\omega C = 0.00163$

$\therefore C = 0.163$ μ F per mile.

Thus, for the cable considered:—

$$\left. \begin{aligned} R &= 83.8 \text{ ohms per mile} \\ L &= 2.1 \text{ mH per mile} \\ G &= 94 \text{ } \mu\text{mhos per mile} \\ C &= 0.163 \text{ } \mu\text{F per mile.} \end{aligned} \right\} \text{Ans.}$$

GENERAL CASE OF A FINITE LINE TERMINATED IN AN IMPEDANCE Z_R

Consider the case of a finite line of length l , terminated in any impedance Z_R . Let the received current and voltage be I_R and E_R respectively.

Then, from equation 17, putting $x = l$:—

$$I_R = I_s \cosh \gamma l - \frac{E_R}{Z_0} \sinh \gamma l$$

and, from equation 18, when $x = l$:—

$$E_R = E_s \cosh \gamma l - I_s Z_0 \sinh \gamma l$$

But $\frac{E_R}{I_R} = Z_R$ since the line is terminated at the distant end in Z_R .

Thus
$$\frac{E_s \cosh \gamma l - I_s Z_0 \sinh \gamma l}{I_s \cosh \gamma l - \frac{E_s}{Z_0} \sinh \gamma l} = Z_R$$

$$\therefore I_s Z_R \cosh \gamma l - \frac{E_s Z_R}{Z_0} \sinh \gamma l = E_s \cosh \gamma l - I_s Z_0 \sinh \gamma l$$

$$\therefore I_s Z_0 Z_R \cosh \gamma l - E_s Z_R \sinh \gamma l = E_s Z_0 \cosh \gamma l - I_s Z_0^2 \sinh \gamma l$$

The input impedance Z_{IN} is given by :—

$$Z_{IN} = \frac{E_s}{I_s} = Z_0 \cdot \frac{Z_R \cosh \gamma l + Z_0 \sinh \gamma l}{Z_0 \cosh \gamma l + Z_R \sinh \gamma l} \quad (43)$$

Alternatively :—

$$Z_{IN} = Z_0 \cdot \frac{Z_R + Z_0 \tanh \gamma l}{Z_0 + Z_R \tanh \gamma l} \quad (44)$$

Variation of input impedance with frequency

Equation 43 may be written :—

$$Z_{IN} = Z_0 \cdot \frac{\cosh \gamma l + \frac{Z_0}{Z_R} \sinh \gamma l}{\frac{Z_0}{Z_R} \cosh \gamma l + \sinh \gamma l}$$

$$\text{Put } \frac{Z_0}{Z_R} = \tanh \theta = \tanh (p + jq)$$

This is permissible, since values of p and q can be found to give any value for $\tanh \theta$.

$$\begin{aligned} \text{Then } Z_{IN} &= Z_0 \cdot \frac{\cosh \gamma l + \tanh \theta \sinh \gamma l}{\tanh \theta \cosh \gamma l + \sinh \gamma l} \\ &= Z_0 \cdot \frac{\cosh \gamma l \cosh \theta + \sinh \gamma l \sinh \theta}{\cosh \gamma l \sinh \theta + \sinh \gamma l \cosh \theta} \\ &= Z_0 \frac{\cosh (\gamma l + \theta)}{\sinh (\gamma l + \theta)} \\ &= Z_0 \frac{\cosh [(\alpha l + p) + j(\beta l + q)]}{\sinh [(\alpha l + p) + j(\beta l + q)]} \end{aligned}$$

In Chapter 2, page 97, it was seen that :—

$$|\cosh (A + jB)| = \sqrt{\sinh^2 A + \cos^2 B}$$

$$\text{and } |\sinh (A + jB)| = \sqrt{\sinh^2 A + \sin^2 B}$$

$$\text{Thus } |Z_{IN}| = |Z_0| \frac{\sqrt{\sinh^2 (\alpha l + p) + \cos^2 (\beta l + q)}}{\sqrt{\sinh^2 (\alpha l + p) + \sin^2 (\beta l + q)}}$$

i.e., squaring $|Z_{IN}|^2 = |Z_o|^2 \frac{\sinh^2(\alpha l + p) + \cos^2(\beta l + q)}{\sinh^2(\alpha l + p) + \sin^2(\beta l + q)}$

Note that $\sin(\beta l + q)$ and $\cos(\beta l + q)$ are periodic functions, whereas $\sinh(\alpha l + p)$ is not.

$|Z_{IN}|^2$ will have a *maximum* value approximately when $\cos^2(\beta l + q) = 1$ and $\sin^2(\beta l + q) = 0$ simultaneously; *i.e.*, when $\beta l + q = \pi, 2\pi, 3\pi$, etc., or, in general, when $\beta l + q = n\pi$, where n is an integer. Similarly $|Z_{IN}|^2$ will have a *minimum* value when $\cos^2(\beta l + q) = 0$ and $\sin^2(\beta l + q) = 1$ simultaneously; *i.e.*, when $\beta l + q = \frac{\pi}{2}, \frac{3\pi}{2}, \frac{5\pi}{2}$, etc., or, in general, when $\beta l + q = (2n - 1)\frac{\pi}{2}$.

Thus $|Z_{IN}|$ will have a maximum value when :-

$$\beta l + q = n\pi$$

i.e., when $\beta = \frac{n\pi - q}{l}$ radians (45)

and the maxima will occur at frequencies for which β takes these values.

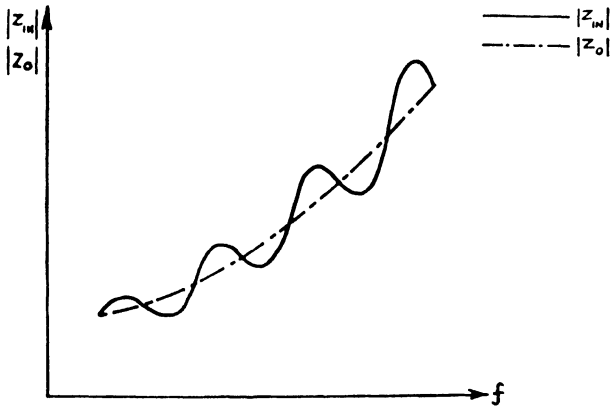


FIG. 756.—Impedance/frequency characteristics of an incorrectly terminated coil-loaded underground cable employing half-section terminations.

Similarly $|Z_{IN}|$ will have a minimum value when :-

$$\beta l + q = (2n - 1) \frac{\pi}{2}$$

i.e., when $\beta = \frac{(2n - 1) \frac{\pi}{2} - q}{l}$ radians (46)

Fig. 756 shows the impedance-frequency characteristic of an incorrectly terminated coil-loaded underground cable employing half-section terminations.

Particular case (i). Line on open-circuit

In this case $Z_R = \infty$, i.e., $\frac{Z_0}{Z_R} = \tanh \theta = 0$

i.e., $\tanh(p + jq) = 0$, i.e., $p = q = 0$

Maxima will occur at frequencies for which :—

$$\beta = \frac{n\pi}{l} \text{ radians} \quad (47)$$

Minima will occur at frequencies for which :—

$$\beta = \frac{(2n - 1) \frac{\pi}{2}}{l} \text{ radians} \quad (48)$$

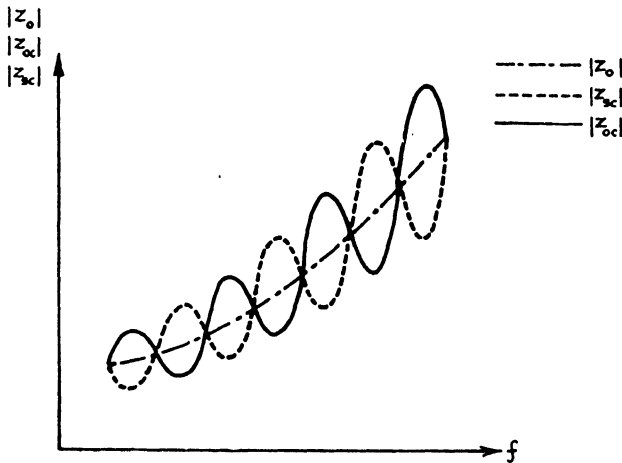


FIG. 757.—Impedance/frequency characteristics of a line.

Particular case (ii). Line on short-circuit

In this case $Z_R = 0$ $\therefore \frac{Z_0}{Z_R} = \infty$

Hence $\tanh(p + jq) = \infty$ and $p = 0$, $q = \frac{\pi}{2}$

Maxima occur at frequencies for which :—

$$\beta = \frac{n\pi - \frac{\pi}{2}}{l} = \frac{(2n - 1) \frac{\pi}{2}}{l} \text{ radians} \quad (49)$$

Minima occur at frequencies for which :—

$$\beta = \frac{(2n - 1) \frac{\pi}{2} - \frac{\pi}{2}}{l} = \frac{(n - 1) \frac{\pi}{2}}{l} \text{ radians}$$

or
$$\beta = \frac{n\pi}{l} \text{ radians} \tag{50}$$

since n is any integer.

Comparing equations 47 with 50, and 48 with 49, it will be seen that the frequencies at which maxima occur with the line on open-circuit are the same as those at which minima occur with the line

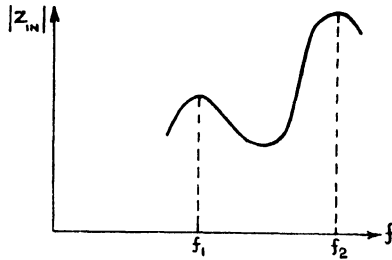


FIG. 758.—Two consecutive maxima on the input impedance/frequency characteristic of a faulty cable.

on short-circuit, and *vice versa* (see Fig. 757). In fact, the frequency difference between successive maxima or minima is independent of the value of the terminating impedance.

Fault location using variation of input impedance with frequency

Measurement of variation of input impedance with frequency gives a convenient method of fault location, particularly in the case of loaded underground cables, where trouble may be experienced due to faulty loading coils. An impedance-frequency run is made on the faulty line, and the frequency difference between two successive maxima (or minima) noted (see Fig. 758).

Let these frequencies be f_1 and f_2 , and let the corresponding values of β at these frequencies be β_1 and β_2 . Provided that the frequency difference is small, it may be assumed that the value of q in equation 45 remains unchanged.

At frequency f_1 , equation 45 becomes :—

$$\beta_1 = \frac{n\pi - q}{l} \tag{51}$$

At frequency f_2 , equation 45 becomes :—

$$\beta_2 = \frac{(n + 1)\pi - q}{l} \tag{52}$$

$\therefore \beta_2 - \beta_1 = \frac{\pi}{l}$

For a loaded underground cable :—

$$\beta = \omega \sqrt{LC}$$

$$\therefore \omega_2 \sqrt{LC} - \omega_1 \sqrt{LC} = \frac{\pi}{l}$$

or
$$l = \frac{1}{2\sqrt{LC} (f_2 - f_1)} \text{ miles} \quad (53)$$

This gives the distance in miles from the sending end to the point of discontinuity (the fault) and enables the fault to be localised.

EQUIVALENT NETWORKS

When interest lies only in the voltage and current at the two ends of a line, it is convenient to consider the equivalent network.

Equivalent T section

Let the T section shown in Fig. 759b represent a line of length l , characteristic impedance Z_0 and propagation constant γ .

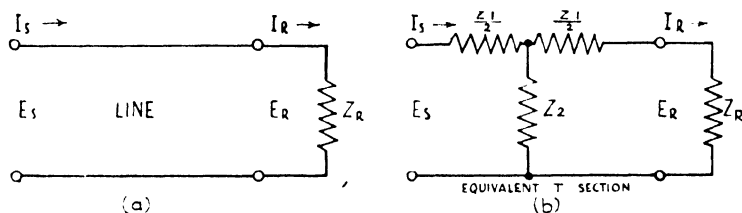


FIG. 759.—Transmission line and its equivalent T section.

Let the sent current and voltage be I_s and E_s , and let the received current and voltage be I_R and E_R .

From equation 17 :—

$$I_R = I_s \cosh \gamma l - \frac{E_s}{Z_0} \sinh \gamma l \quad (54)$$

Considering the T section :—

$$E_s = I_s \frac{Z_1}{2} + (I_s - I_R) Z_2$$

$$\therefore I_R Z_2 = \frac{I_s Z_1}{2} + I_s Z_2 - E_s$$

$$\therefore I_R = I_s \left(\frac{Z_1}{2Z_2} + 1 \right) - \frac{E_s}{Z_2} \quad (55)$$

Equation 55 must be identical with 54 if the T section is to represent the line.

$$\text{Hence } \frac{Z_1}{2Z_2} + 1 = \cosh \gamma l \quad (\text{coefficient of } I_s) \quad (56)$$

$$\text{and } -\frac{1}{Z_2} = -\frac{\sinh \gamma l}{Z_0} \quad (\text{coefficient of } E_s) \quad (57)$$

From equation 57 :—

$$Z_2 = \frac{Z_0}{\sinh \gamma l} \quad (58)$$

From equation 56 :—

$$\begin{aligned} \frac{Z_1}{2} &= Z_0 (\cosh \gamma l - 1) \\ &= Z_0 \frac{\cosh \gamma l - 1}{\sinh \gamma l} \end{aligned} \tag{59}$$

$$= Z_0 \tanh \frac{\gamma l}{2} \tag{60}$$

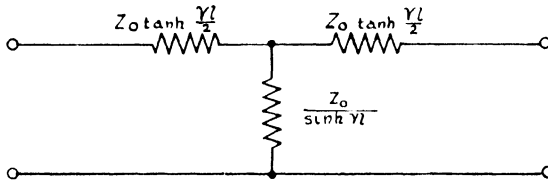


FIG. 760.—Equivalent T section of a uniform transmission line.

Hence the equivalent T section is as shown in Fig. 760.

Equivalent π section

In a similar manner, it can be shown that the equivalent π section is as shown in Fig. 761.

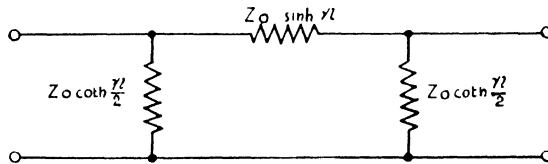


FIG. 761.—Equivalent π section of a uniform transmission line.

Equivalent lattice section

The equivalent lattice section is as shown in Fig. 762.

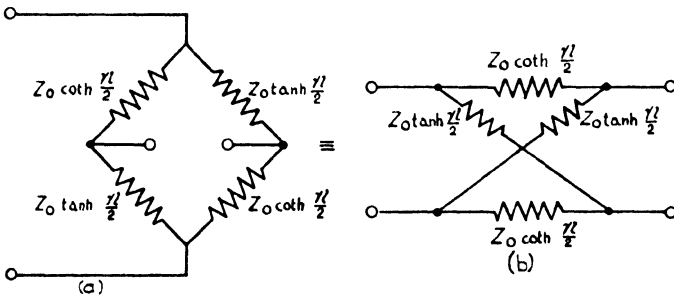


FIG. 762.—Equivalent lattice section of a uniform transmission line.

PROPAGATION CONSTANT OF A LUMP-LOADED LINE

The propagation constant of a lump-loaded line may be determined by considering the equivalent T section.

Let Z_0 be the characteristic impedance of the line before loading ;

Let γ be the propagation constant of the line before loading ;

Let Z_L be the impedance of the loading coil ;

Let d be the coil spacing ;

Let γ' be the propagation constant of the line after loading.

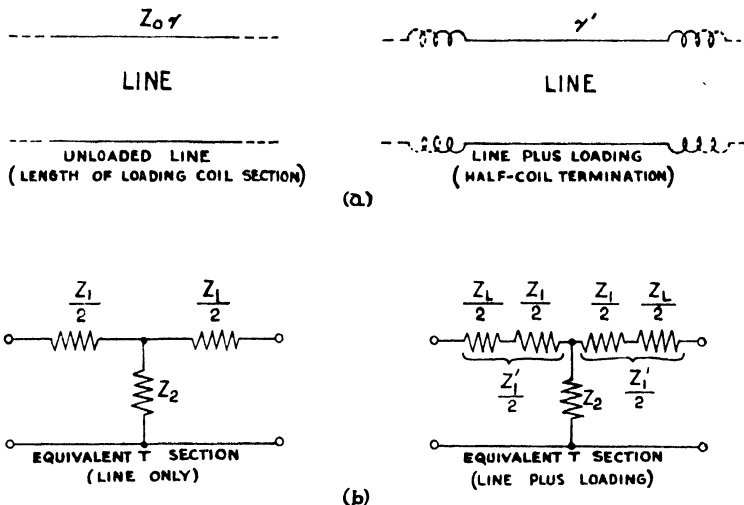


FIG. 763.—Equivalent circuits for unloaded and coil-loaded lines.

Consider the equivalent T section of a loading coil section (see Fig. 763).

$$\text{Let } \frac{Z_1}{2} + \frac{Z_L}{2} = \frac{Z'_1}{2}$$

But, from equation 59 :—

$$\frac{Z_1}{2} = Z_0 \frac{\cosh \gamma d - 1}{\sinh \gamma d}$$

$$\text{Hence } \frac{Z'_1}{2} = \frac{Z_L}{2} + Z_0 \frac{\cosh \gamma d - 1}{\sinh \gamma d}$$

From equation 58 :—

$$Z_2 = \frac{Z_0}{\sinh \gamma d}$$

From equation 56 :—

$$\cosh \gamma' d = 1 + \frac{Z'_1}{2Z_0} = 1 + \frac{\sinh \gamma d}{2Z_0} \left[Z_L + 2Z_0 \frac{\cosh \gamma d - 1}{\sinh \gamma d} \right]$$

$$= 1 + \frac{Z_L \sinh \gamma d}{2Z_0} + \cosh \gamma d - 1$$

$$i.e., \quad \cosh \gamma' d = \cosh \gamma d + \frac{Z_L}{2Z_0} \sinh \gamma d \quad (61)$$

This is known as Campbell's Formula for a loaded line, and it gives an expression for the propagation constant of a loaded section. The method by which this formula was obtained applies only for a loading section with a half-coil termination (see Fig. 749a). By applying a somewhat similar analysis to a loading section with a half-section termination, an identical expression is obtained. Campbell's Formula therefore applies in both cases.

It can be shown from Campbell's Formula that a loaded line has a low-pass filter characteristic; for on writing $\gamma' = \alpha' + j\beta'$ and replacing γ and Z_0 by their values in terms of the primary line constants (*i.e.*, equations 9 and 11 on pages 751-2), equation 61 becomes:—

$$\begin{aligned} & \cosh \alpha' d \cdot \cos \beta' d + j \cdot \sinh \alpha' d \cdot \sin \beta' d \\ &= \cosh \{d \sqrt{(R + j\omega L)(G + j\omega C)}\} \\ &+ \frac{Z_L}{2 \sqrt{\frac{R + j\omega L}{G + j\omega C}}} \cdot \sinh \{d \sqrt{(R + j\omega L)(G + j\omega C)}\} \quad (62) \end{aligned}$$

In order to determine the cut-off frequency, it is necessary to neglect the resistance and leakage and to consider a no-loss line; *i.e.*, putting $R = 0$, $G = 0$ and $Z_L = j\omega L_L$ in equation 62:—

$$\begin{aligned} \cosh \alpha' d \cdot \cos \beta' d + j \sinh \alpha' d \cdot \sin \beta' d &= \cos \omega d \sqrt{LC} \\ &- \frac{\omega L_L}{2} \sqrt{\frac{C}{L}} \cdot \sin \omega d \sqrt{LC} \end{aligned}$$

Equating real and imaginary parts:—

$$\cosh \alpha' d \cdot \cos \beta' d = \cos \omega d \sqrt{LC} - \frac{\omega L_L}{2} \sqrt{\frac{C}{L}} \sin \omega d \sqrt{LC} \quad (63)$$

$$\text{and } \sinh \alpha' d \cdot \sin \beta' d = 0 \quad (64)$$

These equations have a solution $\alpha' = 0$ if:—

$$\cos \beta' d = \cos \omega d \sqrt{LC} - \frac{\omega L_L}{2} \sqrt{\frac{C}{L}} \sin \omega d \sqrt{LC} \quad (65)$$

In the practical case $\omega d \sqrt{LC}$ is a small angle (being the phase shift in the loading coil section), so that in equation 65 the approximations:—

$$\sin \omega d \sqrt{LC} = \omega d \sqrt{LC}$$

$$\text{and } \cos \omega d \sqrt{LC} = 1$$

may be made without much loss of accuracy, giving:—

$$\cos \beta' d = 1 - \frac{\omega^2 L_L C d}{2} \quad (66)$$

This is possible for small values of ω , the limiting value ω_o being given when $\cos \beta'd = 1$

$$\text{i.e.,} \quad \omega_o = \frac{2}{\sqrt{L_L C d}} \quad (67)$$

This means that equations 63 and 64 have a solution $\alpha' = 0$ for all values of ω between $\omega = 0$ and $\omega = \omega_o$; in other words, the loaded line behaves like a low-pass filter, and ω_o gives the cut-off frequency.

Now suppose that the total inductance of the loaded section may be regarded as being uniformly distributed throughout the loading section; let the resultant inductance per mile be denoted by L' ; then:—

$$L'd = L_L + Ld \simeq L_L$$

Equation 67 becomes:—

$$\omega_o = \frac{2}{d \sqrt{L' C}} \quad (68)$$

$$\text{or} \quad f_o = \frac{1}{\pi d \sqrt{L' C}} \quad (69)$$

This formula for the cut-off frequency agrees very closely with observed results. In the same way, for calculating the characteristic impedance and the propagation constant of a loaded line, there is very little loss in accuracy if the "smoothing approximation" is made, *i.e.* if the added inductance is considered to be uniformly distributed along the line. The method by which Z_o and γ are normally calculated is demonstrated in the example on page 722 (Chapter 16), and this method gives perfectly satisfactory results over the normal working frequency range—that is, up to 0.7 of the cut-off frequency.

For frequencies near cut-off, the propagation constant may be computed more accurately by using Campbell's Formula (equation 61); but this is very tedious unless a graphical method (*see* Appendix II) is used for computing the complex hyperbolic functions, and in this case much of the accuracy is lost. For computing accurately the attenuation constant, certain formulae have been derived from Campbell's Formula that enable the attenuation per loading coil section to be calculated simply and accurately. The method given below (without proof) is a modification of a formula obtained by Mayer.

Let R , G , L and C be the primary constants per mile of the unloaded cable. Let L_L be the inductance, R_L the AC resistance, and C_L the shunt capacity of a loading coil, and d the length of the loading coil section in miles.

The following definitions are then made:—

$$L'd = L_L + Ld$$

where L' is the "smoothed" inductance per mile of the loaded cable.

$$C'd = C_L + Cd$$

where C' is the "smoothed" capacity per mile of the loaded cable.

TABLE XXIV

VALUES OF K_1 AND K_2 FOR USE IN EQUATIONS 71, 72 and 73
Propagation Constant of a Lump-loaded Line


x	K_1	K_2	x	K_1	K_2
0.30	0.5172	0.5502	0.65	0.4963	0.6909
0.31	0.5169	0.5523	0.66	0.4959	0.6988
0.32	0.5165	0.5544	0.67	0.4955	0.7072
0.33	0.5156	0.5560	0.68	0.4953	0.7161
0.34	0.5150	0.5581	0.69	0.4953	0.7256
0.35	0.5144	0.5602	0.70	0.4949	0.7350
0.36	0.5142	0.5628	0.71	0.4949	0.7455
0.37	0.5133	0.5649	0.72	0.4951	0.7565
0.38	0.5129	0.5675	0.73	0.4952	0.7681
0.39	0.5123	0.5702	0.74	0.4957	0.7807
0.40	0.5117	0.5728	0.75	0.4961	0.7938
0.41	0.5109	0.5754	0.76	0.4968	0.8080
0.42	0.5105	0.5786	0.77	0.4975	0.8227
0.43	0.5100	0.5817	0.78	0.4987	0.8390
0.44	0.5094	0.5849	0.79	0.5000	0.8583
0.45	0.5086	0.5880	0.80	0.5017	0.8752
0.46	0.5077	0.5912	0.81	0.5036	0.8951
0.47	0.5072	0.5948	0.82	0.5060	0.9172
0.48	0.5066	0.5985	0.83	0.5090	0.9413
0.49	0.5058	0.6022	0.84	0.5125	0.9676
0.50	0.5053	0.6064	0.85	0.5172	0.9965
0.51	0.5047	0.6106	0.86	0.5216	1.029
0.52	0.5039	0.6148	0.87	0.5276	1.065
0.53	0.5031	0.6190	0.88	0.5345	1.105
0.54	0.5025	0.6237	0.89	0.5434	1.151
0.55	0.5017	0.6284	0.90	0.5539	1.204
0.56	0.5012	0.6337	0.91	0.5670	1.266
0.57	0.5005	0.6389	0.92	0.5838	1.340
0.58	0.5001	0.6447	0.93	0.6048	1.428
0.59	0.4995	0.6505	0.94	0.6321	1.539
0.60	0.4988	0.6563	0.95	0.6694	1.681
0.61	0.4982	0.6626	0.96	0.7229	1.875
0.62	0.4978	0.6694	0.97	0.8106	2.160
0.63	0.4973	0.6762	0.98	0.9487	2.638
0.64	0.4965	0.6830	0.99	1.289	3.721
—	—	—	1.00	∞	∞

$$f_0 = \frac{1}{\pi d \sqrt{L'C'}}$$

i.e., f_0 is the cut-off frequency calculated in the normal manner using the smoothing approximation.

Let
$$Z_d = \sqrt{\frac{L'}{C'}}$$

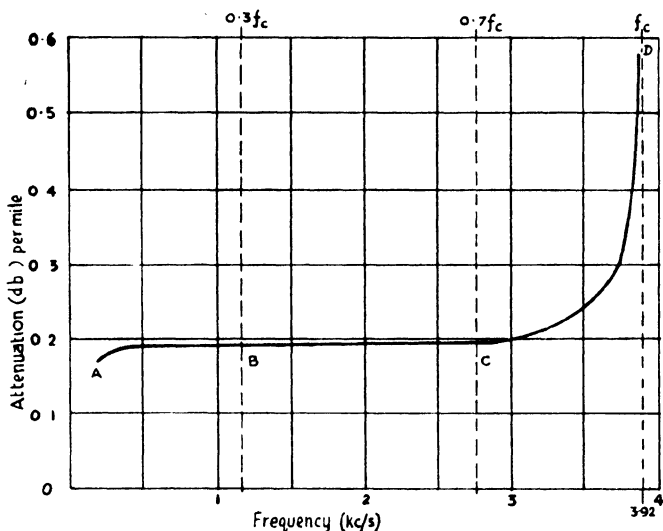and $x = \frac{f}{f_0}$, where f is the frequency at which the attenuation is to be determined.



CALCULATED ATTENUATION OF 40 lb. PCQT
LOADED 88 mH/2000 yds.

FIG. 764.—Attenuation-frequency characteristic of a 40 lb. PCQT line, loaded 88 mH/2000 yds.

The attenuation αd per loading coil section is then given by:—

$$\alpha d = \alpha_1 + \alpha_2 + \alpha_3 \quad (70)$$

where:—

α_1 is the conductor attenuation per loading coil section, and is given by:—

$$\alpha_1 = \frac{Rd}{Z_d} K_1 \text{ nepers} \quad (71)$$

α_2 is the "coil" attenuation per loading coil section, and is given by:—

$$\alpha_2 = \frac{R_L}{Z_d} \cdot K_1 \text{ nepers} \quad (72)$$

α_3 is the "leakance" attenuation per loading coil section, and is given by :—

$$\alpha_3 = d \cdot G \cdot Z_d \cdot K_2 \text{ nepers} \quad (73)$$

The quantities K_1 and K_2 are dependent on the ratio $x = \frac{f}{f_0}$ of the frequency considered to the cut-off frequency, and their values are tabulated in Table XXIV for values of x from 0.3 to 1.0.

Fig. 764 shows the attenuation-frequency curve for 40 lb. PCQT underground cable loaded 88mH/2,000 yds. (the cable specified in the example on page 743). The method of calculating this curve is as follows :—

- (i) From A to B , calculate α from $\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$ using the smoothing approximation.
- (ii) From B to D , calculate α from the method just given.

It will be noted that the flat portion of the curve from B to C is very close to the value obtained in the example on page 743, *i.e.*, 0.191 db per mile. Thus for frequencies up to 0.7 of the cut-off frequency, there is no advantage to be gained by the more accurate method; and, since a loaded cable is rarely worked at frequencies above this figure, the method of page 742 is the one generally employed.

APPENDIX I

MATHEMATICAL TABLES AND FORMULAE

Table No.		Page
	Reciprocals	776
2	Squares	778
3	Square roots (of numbers from 1 to 10)	780
4	Square roots (of numbers from 10 to 100)	782
5	Common logarithms (logarithms to base 10)	784
6	Antilogarithms	786
7	Hyperbolic (Napierian) logarithms	788
8	Positive powers of $e = 2.71828$ (values of e^x)	790
9	Negative powers of $e = 2.71828$ (values of e^{-x})	792
10	Natural hyperbolic sines (values of $\sinh x$)	794
11	Natural hyperbolic cosines (values of $\cosh x$)	796
12	Natural hyperbolic tangents (values of $\tanh x$)	798
13	Circular functions of radians	800
14	Degrees of radians	804
15	Natural sines	806
16	Natural cosines	808
17	Natural tangents	810
18	Logarithms of sines	812
19	Logarithms of cosines	814
20	Logarithms of tangents	816
21	Chords of angles	818
22	Useful numbers (with their logarithms to base 10)	820
23	Comparative table of circular and hyperbolic relationships	822
24	Complex hyperbolic identities	825
25	Common derivatives and integrals	826
26	Guides to the integration of awkward expressions	828

TABLE 1
RECIPROCAL

(To the first four figures, no account being taken of the position of the decimal point)

	0	1	2	3	4	5	6	7	8	9	Subtract :								
											1	2	3	4	5	6	7	8	9
10	1000	9901	9804	9709	9615	9524	9434	9346	9259	9174	9	18	27	36	45	55	64	73	82
11	9091	9009	8929	8850	8772	8696	8621	8547	8475	8403	8	15	23	30	38	45	53	61	68
12	8333	8264	8197	8130	8065	8000	7937	7874	7813	7752	6	13	19	26	32	38	45	51	58
13	7692	7634	7576	7519	7463	7407	7353	7299	7246	7194	5	11	16	22	27	33	38	44	49
14	7143	7092	7042	6993	6944	6897	6849	6803	6757	6711	5	10	14	19	24	29	33	38	43
15	6667	6623	6579	6536	6494	6452	6410	6369	6329	6289	4	8	13	17	21	25	29	33	38
16	6250	6211	6173	6135	6098	6061	6024	5988	5952	5917	4	7	11	15	18	22	26	29	33
17	5882	5848	5814	5780	5747	5714	5682	5650	5618	5587	3	7	10	13	16	20	23	26	29
18	5556	5525	5495	5464	5435	5405	5376	5348	5319	5291	3	6	9	12	15	18	21	23	26
19	5263	5236	5208	5181	5155	5128	5102	5076	5051	5025	3	5	8	11	13	16	18	21	24
20	5000	4975	4950	4926	4902	4878	4854	4831	4808	4785	2	5	7	10	12	14	17	19	21
21	4762	4739	4717	4695	4673	4651	4630	4608	4587	4566	2	4	7	9	11	13	15	17	20
22	4545	4525	4505	4484	4464	4444	4425	4405	4386	4367	2	4	6	8	10	12	14	16	18
23	4348	4329	4310	4292	4274	4255	4237	4219	4202	4184	2	4	5	7	9	11	13	14	16
24	4167	4149	4132	4115	4098	4082	4065	4049	4032	4016	2	3	5	7	8	10	12	13	15
25	4000	3984	3968	3953	3937	3922	3906	3891	3876	3861	2	3	5	6	8	9	11	12	14
26	3846	3831	3817	3802	3788	3774	3759	3745	3731	3717	1	3	4	6	7	9	10	11	13
27	3704	3690	3676	3663	3650	3636	3623	3610	3597	3584	1	3	4	5	7	8	9	11	12
28	3571	3559	3546	3534	3521	3509	3497	3484	3472	3460	1	2	4	5	6	7	9	10	11
29	3448	3436	3425	3413	3401	3390	3378	3367	3356	3344	1	2	3	5	6	7	8	9	10
30	3333	3322	3311	3300	3289	3279	3268	3257	3247	3236	1	2	3	4	5	6	7	9	10
31	3226	3215	3205	3195	3185	3175	3165	3155	3145	3135	1	2	3	4	5	6	7	8	9
32	3125	3115	3106	3096	3086	3077	3067	3058	3049	3040	1	2	3	4	5	6	7	8	9
33	3030	3021	3012	3003	2994	2985	2976	2967	2959	2950	1	2	3	4	4	5	6	7	8
34	2941	2933	2924	2915	2907	2899	2890	2882	2874	2865	1	2	3	3	4	5	6	7	8
35	2857	2849	2841	2833	2825	2817	2809	2801	2793	2786	1	2	2	3	4	5	6	6	7
36	2778	2770	2762	2755	2747	2740	2732	2725	2717	2710	1	2	2	3	4	5	5	6	7
37	2703	2695	2688	2681	2674	2667	2660	2653	2646	2639	1	1	2	3	4	4	5	6	6
38	2632	2625	2618	2611	2604	2597	2591	2584	2577	2571	1	1	2	3	3	4	4	5	6
39	2564	2558	2551	2545	2538	2532	2525	2519	2513	2506	1	1	2	3	3	4	4	5	6
40	2500	2494	2488	2481	2475	2469	2463	2457	2451	2445	1	1	2	2	3	4	4	5	5
41	2439	2433	2427	2421	2415	2410	2404	2398	2392	2387	1	1	2	2	3	3	4	5	5
42	2381	2375	2370	2364	2358	2353	2347	2342	2336	2331	1	1	2	2	3	3	4	4	5
43	2326	2320	2315	2309	2304	2299	2294	2288	2283	2278	1	1	2	2	3	3	4	4	5
44	2273	2268	2262	2257	2252	2247	2242	2237	2232	2227	1	1	2	2	3	3	4	4	5
45	2222	2217	2212	2208	2203	2198	2193	2188	2183	2179	0	1	1	2	2	3	3	4	4
46	2174	2169	2165	2160	2155	2151	2146	2141	2137	2132	0	1	1	2	2	3	3	4	4
47	2128	2123	2119	2114	2110	2105	2101	2096	2092	2088	0	1	1	2	2	3	3	4	4
48	2083	2079	2075	2070	2066	2062	2058	2053	2049	2045	0	1	1	2	2	3	3	4	4
49	2041	2037	2033	2028	2024	2020	2016	2012	2008	2004	0	1	1	2	2	3	3	4	4
50	2000	1996	1992	1988	1984	1980	1976	1972	1969	1965	0	1	1	2	2	3	3	4	4
51	1961	1957	1953	1949	1946	1942	1938	1934	1931	1927	0	1	1	2	2	3	3	4	4
52	1923	1919	1916	1912	1908	1905	1901	1896	1894	1890	0	1	1	2	2	3	3	4	4
53	1887	1883	1880	1876	1873	1869	1866	1862	1859	1855	0	1	1	2	2	3	3	4	4
54	1852	1848	1845	1842	1838	1835	1832	1828	1825	1821	0	1	1	2	2	3	3	4	4
55	1818	1815	1812	1808	1805	1802	1799	1795	1792	1789	0	1	1	2	2	3	3	4	4

TABLE 1
RECIPROCALLS

	0	1	2	3	4	5	6	7	8	9	Subtract :								
											1	2	3	4	5	6	7	8	9
55	1818	1815	1812	1808	1805	1802	1799	1795	1792	1789	0	1	1	1	2	2	2	3	3
56	1786	1783	1779	1776	1773	1770	1767	1764	1761	1757	0	1	1	1	2	2	2	3	3
57	1754	1751	1748	1745	1742	1739	1736	1733	1730	1727	0	1	1	1	2	2	2	3	3
58	1724	1721	1718	1715	1712	1709	1706	1704	1701	1698	0	1	1	1	2	2	2	3	3
59	1695	1692	1689	1686	1684	1681	1678	1675	1672	1669	0	1	1	1	2	2	2	3	3
60	1667	1664	1661	1658	1656	1653	1650	1647	1645	1642	0	1	1	1	2	2	2	2	2
61	1639	1637	1634	1631	1629	1626	1623	1621	1618	1616	0	1	1	1	2	2	2	2	2
62	1613	1610	1608	1605	1603	1600	1597	1595	1592	1590	0	1	1	1	2	2	2	2	2
63	1587	1585	1582	1580	1577	1575	1572	1570	1567	1565	0	0	1	1	1	2	2	2	2
64	1563	1560	1558	1555	1553	1550	1548	1546	1543	1541	0	0	1	1	1	2	2	2	2
65	1538	1536	1534	1531	1529	1527	1524	1522	1520	1517	0	0	1	1	1	2	2	2	2
66	1515	1513	1511	1508	1506	1504	1502	1499	1497	1495	0	0	1	1	1	2	2	2	2
67	1493	1490	1488	1486	1484	1481	1479	1477	1475	1473	0	0	1	1	1	2	2	2	2
68	1471	1468	1466	1464	1462	1460	1458	1456	1455	1451	0	0	1	1	1	2	2	2	2
69	1449	1447	1445	1443	1441	1439	1437	1435	1433	1431	0	0	1	1	1	2	2	2	2
70	1429	1427	1425	1422	1420	1418	1416	1414	1412	1410	0	0	1	1	1	2	2	2	2
71	1408	1406	1404	1403	1401	1399	1397	1395	1393	1391	0	0	1	1	1	2	2	2	2
72	1389	1387	1385	1383	1381	1379	1377	1376	1374	1372	0	0	1	1	1	2	2	2	2
73	1370	1368	1366	1364	1362	1361	1359	1357	1355	1353	0	0	1	1	1	2	2	2	2
74	1351	1350	1348	1346	1344	1342	1340	1339	1337	1335	0	0	1	1	1	2	2	2	2
75	1333	1332	1330	1328	1326	1325	1323	1321	1319	1318	0	0	1	1	1	2	2	2	2
76	1316	1314	1312	1311	1309	1307	1305	1304	1302	1300	0	0	1	1	1	2	2	2	2
77	1299	1297	1295	1294	1292	1290	1289	1287	1285	1284	0	0	0	1	1	2	2	2	2
78	1282	1280	1279	1277	1276	1274	1272	1271	1269	1267	0	0	0	1	1	2	2	2	2
79	1266	1264	1263	1261	1259	1258	1256	1255	1253	1252	0	0	0	1	1	2	2	2	2
80	1250	1248	1247	1245	1244	1242	1241	1239	1238	1236	0	0	0	1	1	2	2	2	2
81	1235	1233	1232	1230	1229	1227	1225	1224	1222	1221	0	0	0	1	1	2	2	2	2
82	1220	1218	1217	1215	1214	1212	1211	1209	1208	1206	0	0	0	1	1	2	2	2	2
83	1205	1203	1202	1200	1199	1198	1196	1195	1193	1192	0	0	0	1	1	2	2	2	2
84	1190	1189	1188	1186	1185	1183	1182	1181	1179	1178	0	0	0	1	1	2	2	2	2
85	1176	1175	1174	1172	1171	1170	1168	1167	1166	1164	0	0	0	1	1	2	2	2	2
86	1163	1161	1160	1159	1157	1156	1155	1153	1152	1151	0	0	0	1	1	2	2	2	2
87	1149	1148	1147	1145	1144	1143	1142	1140	1139	1138	0	0	0	1	1	2	2	2	2
88	1136	1135	1134	1133	1131	1130	1129	1127	1126	1125	0	0	0	1	1	2	2	2	2
89	1124	1122	1121	1120	1119	1117	1116	1115	1114	1112	0	0	0	1	1	2	2	2	2
90	1111	1110	1109	1107	1106	1105	1104	1103	1101	1100	0	0	0	1	1	2	2	2	2
91	1099	1098	1096	1095	1094	1093	1092	1091	1089	1088	0	0	0	1	1	2	2	2	2
92	1087	1086	1085	1083	1082	1081	1080	1079	1078	1076	0	0	0	1	1	2	2	2	2
93	1075	1074	1073	1072	1071	1070	1068	1067	1066	1065	0	0	0	1	1	2	2	2	2
94	1064	1063	1062	1060	1059	1058	1057	1056	1055	1054	0	0	0	1	1	2	2	2	2
95	1053	1052	1050	1049	1048	1047	1046	1045	1044	1043	0	0	0	1	1	2	2	2	2
96	1042	1041	1040	1038	1037	1036	1035	1034	1033	1032	0	0	0	1	1	2	2	2	2
97	1031	1030	1029	1028	1027	1026	1025	1024	1022	1021	0	0	0	1	1	2	2	2	2
98	1020	1019	1018	1017	1016	1015	1014	1013	1012	1011	0	0	0	1	1	2	2	2	2
99	1010	1009	1008	1007	1006	1005	1004	1003	1002	1001	0	0	0	1	1	2	2	2	2
100	1000	9990	9980	9970	9960	9950	9940	9930	9921	9911	0	0	0	1	1	2	2	2	2

TABLE 2
SQUARES

(To the first four figures, no account being taken of the position of the decimal point)

	0	1	2	3	4	5	6	7	8	9	Add :											
											1	2	3	4	5	6	7	8	9	1	2	3
10	1000	1020	1040	1061	1082	1103	1124	1145	1166	1188	2	4	6	8	11	13	15	17	19			
11	1210	1232	1254	1277	1300	1323	1346	1369	1392	1416	2	5	7	9	12	14	16	18	21			
12	1440	1464	1488	1513	1538	1563	1588	1613	1638	1664	3	5	8	10	13	15	18	20	23			
13	1690	1716	1742	1769	1796	1823	1850	1877	1904	1932	3	5	8	11	14	16	19	22	24			
14	1960	1988	2016	2045	2074	2103	2132	2161	2190	2220	3	6	9	12	15	17	20	23	26			
15	2250	2280	2310	2341	2372	2403	2434	2465	2496	2528	3	6	9	12	16	19	22	25	28			
16	2560	2592	2624	2657	2690	2723	2756	2789	2822	2856	3	7	10	13	17	20	23	26	30			
17	2890	2924	2958	2993	3028	3063	3098	3133	3168	3204	4	7	11	14	18	21	25	28	32			
18	3240	3276	3312	3349	3386	3423	3460	3497	3534	3572	4	7	11	15	19	22	26	30	33			
19	3610	3648	3686	3725	3764	3803	3842	3881	3920	3960	4	8	12	16	20	23	27	31	35			
20	4000	4040	4080	4121	4162	4203	4244	4285	4326	4368	4	8	12	16	21	25	29	33	37			
21	4410	4452	4494	4537	4580	4623	4666	4709	4752	4796	4	9	13	17	22	26	30	34	39			
22	4840	4884	4928	4973	5018	5063	5108	5153	5198	5244	5	9	14	18	23	27	32	36	41			
23	5290	5336	5382	5429	5476	5523	5570	5617	5664	5712	5	9	14	19	24	28	33	38	42			
24	5760	5808	5856	5905	5954	6003	6052	6101	6150	6200	5	10	15	20	25	29	34	39	44			
25	6250	6300	6350	6401	6452	6503	6554	6605	6656	6708	5	10	15	20	26	31	36	41	46			
26	6760	6812	6864	6917	6970	7023	7076	7129	7182	7236	5	11	16	21	27	32	37	42	48			
27	7290	7344	7398	7453	7508	7563	7618	7673	7728	7784	6	11	17	22	28	33	39	44	50			
28	7840	7896	7952	8009	8066	8123	8180	8237	8294	8352	6	11	17	23	29	34	40	46	51			
29	8410	8468	8526	8585	8644	8703	8762	8821	8880	8940	6	12	18	24	30	35	41	47	53			
30	9000	9060	9120	9181	9242	9303	9364	9425	9486	9548	6	12	18	24	31	37	43	49	55			
31	9610	9672	9734	9797	9860	9923	9986	1005	1011	1018	6	13	19	25	32	38	44	50	56			
31								1005	1011	1018	1	1	2	3	3	4	4	5	6			
32	1024	1030	1037	1043	1050	1056	1063	1069	1076	1082	1	1	2	3	3	4	5	5	6			
33	1089	1096	1102	1109	1116	1122	1129	1136	1142	1149	1	1	2	3	3	4	5	5	6			
34	1156	1163	1170	1176	1183	1190	1197	1204	1211	1218	1	1	2	3	3	4	5	5	6			
35	1225	1232	1239	1246	1253	1260	1267	1274	1282	1289	1	1	2	3	3	4	4	5	6			
36	1296	1303	1310	1318	1325	1332	1340	1347	1354	1362	1	1	2	3	3	4	4	5	6			
37	1369	1376	1384	1391	1399	1406	1414	1421	1429	1436	1	2	2	3	3	4	5	5	6			
38	1444	1452	1459	1467	1475	1482	1490	1498	1505	1513	1	2	2	3	3	4	5	5	6			
39	1521	1529	1537	1544	1552	1560	1568	1576	1584	1592	1	2	2	3	3	4	5	5	6			
40	1600	1608	1616	1624	1632	1640	1648	1656	1665	1673	1	2	2	3	3	4	5	6	7			
41	1681	1689	1697	1706	1714	1722	1731	1739	1747	1756	1	2	2	3	3	4	5	6	7			
42	1764	1772	1781	1789	1798	1806	1815	1823	1832	1840	1	2	3	3	4	5	6	7	8			
43	1849	1858	1866	1875	1884	1892	1901	1910	1918	1927	1	2	3	3	4	5	6	7	8			
44	1936	1945	1954	1962	1971	1980	1989	1998	2007	2016	1	2	3	3	4	5	6	7	8			
45	2025	2034	2043	2052	2061	2070	2079	2088	2098	2107	1	2	3	3	4	5	5	6	7			
46	2116	2125	2134	2144	2153	2162	2172	2181	2190	2200	1	2	3	3	4	5	6	7	8			
47	2209	2218	2228	2237	2247	2256	2266	2275	2285	2294	1	2	3	3	4	5	6	7	8			
48	2304	2314	2323	2333	2343	2352	2362	2372	2381	2391	1	2	3	3	4	5	6	7	8			
49	2401	2411	2421	2430	2440	2450	2460	2470	2480	2490	1	2	3	3	4	5	6	7	8			
50	2500	2510	2520	2530	2540	2550	2560	2570	2581	2591	1	2	3	3	4	5	6	7	8			
51	2601	2611	2621	2632	2642	2652	2663	2673	2683	2694	1	2	3	3	4	5	6	7	8			
52	2704	2714	2725	2735	2746	2756	2767	2777	2788	2798	1	2	3	3	4	5	6	7	8			
53	2809	2820	2830	2841	2852	2862	2873	2884	2894	2905	1	2	3	3	4	5	6	7	9			
54	2916	2927	2938	2948	2959	2969	2979	2989	2999	3003	1	2	3	3	4	5	7	8	9			
55	3025	3036	3047	3058	3069	3080	3091	3102	3114	3125	1	2	3	3	4	6	7	8	9			

TABLE 2
SQUARES

	0	1	2	3	4	5	6	7	8	9	Add :								
											1	2	3	4	5	6	7	8	9
55	3025	3036	3047	3058	3069	3080	3091	3102	3114	3125	1	2	3	4	6	7	8	9	10
56	3136	3147	3158	3170	3181	3192	3204	3215	3226	3238	1	2	3	5	6	7	8	9	10
57	3249	3260	3272	3283	3295	3306	3318	3329	3341	3352	1	2	3	5	6	7	8	9	10
58	3364	3376	3387	3399	3411	3422	3434	3446	3457	3469	1	2	4	5	6	7	8	9	11
59	3481	3493	3505	3516	3528	3540	3552	3564	3576	3588	1	2	4	5	6	7	8	10	11
60	3600	3612	3624	3636	3648	3660	3672	3684	3697	3709	1	2	4	5	6	7	8	10	11
61	3721	3733	3745	3758	3770	3782	3795	3807	3819	3832	1	2	4	5	6	7	9	10	11
62	3844	3856	3869	3881	3894	3906	3919	3931	3944	3956	1	3	4	5	6	8	9	10	11
63	3969	3982	3994	4007	4020	4032	4045	4058	4070	4083	1	3	4	5	6	8	9	10	11
64	4096	4109	4122	4134	4147	4160	4173	4186	4199	4212	1	3	4	5	6	8	9	10	12
65	4225	4238	4251	4264	4277	4290	4303	4316	4330	4343	1	3	4	5	7	8	9	10	12
66	4356	4369	4382	4396	4409	4422	4436	4449	4462	4476	1	3	4	5	7	8	9	11	12
67	4489	4502	4516	4529	4543	4556	4570	4583	4597	4610	1	3	4	5	7	8	9	11	12
68	4624	4638	4651	4665	4679	4692	4706	4720	4733	4747	1	3	4	5	7	8	10	11	12
69	4761	4775	4789	4802	4816	4830	4844	4858	4872	4886	1	3	4	6	7	8	10	11	13
70	4900	4914	4928	4942	4956	4970	4984	4998	5013	5027	1	3	4	6	7	8	10	11	13
71	5041	5055	5069	5084	5098	5112	5127	5141	5155	5170	1	3	4	6	7	9	10	11	13
72	5184	5198	5213	5227	5242	5256	5271	5285	5300	5314	1	3	4	6	7	9	10	12	13
73	5329	5344	5358	5373	5388	5402	5417	5432	5446	5461	1	3	4	6	7	9	10	12	13
74	5476	5491	5506	5520	5535	5550	5565	5580	5595	5610	1	3	4	6	7	9	10	12	13
75	5625	5640	5655	5670	5685	5700	5715	5730	5746	5761	2	3	5	6	8	9	11	12	14
76	5776	5791	5806	5822	5837	5852	5868	5883	5898	5914	2	3	5	6	8	9	11	12	14
77	5929	5944	5960	5975	5991	6006	6022	6037	6053	6068	2	3	5	6	8	9	11	12	14
78	6084	6100	6115	6131	6147	6162	6178	6194	6209	6225	2	3	5	6	8	9	11	13	14
79	6241	6257	6273	6288	6304	6320	6336	6352	6368	6384	2	3	5	6	8	10	11	13	14
80	6400	6416	6432	6448	6464	6480	6496	6512	6529	6545	2	3	5	6	8	10	11	13	14
81	6561	6577	6593	6610	6626	6642	6659	6675	6691	6708	2	3	5	7	8	10	11	13	15
82	6724	6740	6757	6773	6790	6806	6823	6839	6856	6872	2	3	5	7	8	10	12	13	15
83	6889	6906	6922	6939	6956	6972	6989	7006	7022	7039	2	3	5	7	8	10	12	13	15
84	7056	7073	7090	7106	7123	7140	7157	7174	7191	7208	2	3	5	7	8	10	12	14	15
85	7225	7242	7259	7276	7293	7310	7327	7344	7362	7379	2	3	5	7	9	10	12	14	15
86	7396	7413	7430	7448	7465	7482	7500	7517	7534	7552	2	3	5	7	9	10	12	14	16
87	7569	7586	7604	7621	7639	7656	7674	7691	7709	7726	2	4	5	7	9	11	12	14	16
88	7744	7762	7779	7797	7815	7832	7850	7868	7885	7903	2	4	5	7	9	11	12	14	16
89	7921	7939	7957	7974	7992	8010	8028	8046	8064	8082	2	4	5	7	9	11	13	14	16
90	8100	8118	8136	8154	8172	8190	8208	8226	8245	8263	2	4	5	7	9	11	13	14	16
91	8281	8299	8317	8336	8354	8372	8391	8409	8427	8446	2	4	5	7	9	11	13	15	16
92	8464	8482	8501	8519	8538	8556	8575	8593	8612	8630	2	4	6	7	9	11	13	15	17
93	8649	8668	8686	8705	8724	8742	8761	8780	8798	8817	2	4	6	7	9	11	13	15	17
94	8836	8855	8874	8892	8911	8930	8949	8968	8987	9006	2	4	6	8	9	11	13	15	17
95	9025	9044	9063	9082	9101	9120	9139	9158	9178	9197	2	4	6	8	10	11	13	15	17
96	9216	9235	9254	9274	9293	9312	9332	9351	9370	9390	2	4	6	8	10	12	14	15	17
97	9409	9428	9448	9467	9487	9506	9526	9545	9565	9584	2	4	6	8	10	12	14	16	18
98	9604	9624	9643	9663	9683	9702	9722	9742	9761	9781	2	4	6	8	10	12	14	16	18
99	9801	9821	9841	9860	9880	9900	9920	9940	9960	9980	2	4	6	8	10	12	14	16	18
100	1000	1002	1004	1006	1008	1010	1012	1014	1016	1018	0	0	1	1	1	1	2	2	2

TABLE 3
SQUARE ROOTS
of numbers from 1 to 10

	0	1	2	3	4	5	6	7	8	9	Add:			
											1 2 3	4 5 6	7 8 9	
1-0	1-000	1-005	1-010	1-015	1-020	1-025	1-030	1-034	1-039	1-044	0 1 1	2 2 3	3 4 4	
1-1	1-049	1-054	1-058	1-063	1-068	1-072	1-077	1-082	1-086	1-091	0 1 1	2 2 3	3 4 4	
1-2	1-095	1-100	1-105	1-109	1-114	1-118	1-122	1-127	1-131	1-136	0 1 1	2 2 3	3 4 4	
1-3	1-140	1-145	1-149	1-153	1-158	1-162	1-166	1-170	1-175	1-179	0 1 1	2 2 3	3 3 4	
1-4	1-183	1-187	1-192	1-196	1-200	1-204	1-208	1-212	1-217	1-221	0 1 1	2 2 2	3 3 4	
1-5	1-225	1-229	1-233	1-237	1-241	1-245	1-249	1-253	1-257	1-261	0 1 1	2 2 2	3 3 4	
1-6	1-265	1-269	1-273	1-277	1-281	1-285	1-288	1-292	1-296	1-300	0 1 1	2 2 2	3 3 3	
1-7	1-304	1-308	1-311	1-315	1-319	1-323	1-327	1-330	1-334	1-338	0 1 1	2 2 2	3 3 3	
1-8	1-342	1-345	1-349	1-353	1-356	1-360	1-364	1-367	1-371	1-375	0 1 1	1 2 2	3 3 3	
1-9	1-378	1-382	1-386	1-389	1-393	1-396	1-400	1-404	1-407	1-411	0 1 1	1 2 2	3 3 3	
2-0	1-414	1-418	1-421	1-425	1-428	1-432	1-435	1-439	1-442	1-446	0 1 1	1 2 2	2 3 3	
2-1	1-449	1-453	1-456	1-459	1-463	1-466	1-470	1-473	1-476	1-480	0 1 1	1 2 2	2 3 3	
2-2	1-483	1-487	1-490	1-493	1-497	1-500	1-503	1-507	1-510	1-513	0 1 1	1 2 2	2 3 3	
2-3	1-517	1-520	1-523	1-526	1-530	1-533	1-536	1-539	1-543	1-546	0 1 1	1 2 2	2 3 3	
2-4	1-549	1-552	1-556	1-559	1-562	1-565	1-568	1-572	1-575	1-578	0 1 1	1 2 2	2 3 3	
2-5	1-581	1-584	1-587	1-591	1-594	1-597	1-600	1-603	1-606	1-609	0 1 1	1 2 2	2 3 3	
2-6	1-612	1-616	1-619	1-622	1-625	1-628	1-631	1-634	1-637	1-640	0 1 1	1 2 2	2 2 3	
2-7	1-643	1-646	1-649	1-652	1-655	1-658	1-661	1-664	1-667	1-670	0 1 1	1 2 2	2 2 3	
2-8	1-678	1-676	1-679	1-682	1-685	1-688	1-691	1-694	1-697	1-700	0 1 1	1 1 2	2 2 3	
2-9	1-703	1-708	1-709	1-712	1-715	1-718	1-720	1-723	1-726	1-729	0 1 1	1 1 2	2 2 3	
3-0	1-732	1-735	1-738	1-741	1-744	1-746	1-749	1-752	1-755	1-758	0 1 1	1 1 2	2 2 3	
3-1	1-761	1-764	1-766	1-769	1-772	1-775	1-778	1-780	1-783	1-786	0 1 1	1 1 2	2 2 3	
3-2	1-789	1-792	1-794	1-797	1-800	1-803	1-806	1-808	1-811	1-814	0 1 1	1 1 2	2 2 2	
3-3	1-817	1-819	1-822	1-825	1-828	1-830	1-833	1-836	1-838	1-841	0 1 1	1 1 2	2 2 2	
3-4	1-844	1-847	1-849	1-852	1-855	1-857	1-860	1-863	1-865	1-868	0 1 1	1 1 2	2 2 2	
3-5	1-871	1-873	1-876	1-879	1-881	1-884	1-887	1-889	1-892	1-895	0 1 1	1 1 2	2 2 2	
3-6	1-897	1-900	1-903	1-905	1-908	1-910	1-913	1-916	1-918	1-921	0 1 1	1 1 2	2 2 2	
3-7	1-924	1-926	1-929	1-931	1-934	1-936	1-939	1-942	1-944	1-947	0 1 1	1 1 2	2 2 2	
3-8	1-949	1-952	1-954	1-957	1-960	1-962	1-965	1-967	1-970	1-972	0 1 1	1 1 2	2 2 2	
3-9	1-975	1-977	1-980	1-982	1-985	1-987	1-990	1-992	1-995	1-997	0 1 1	1 1 2	2 2 2	
4-0	2-000	2-002	2-005	2-007	2-010	2-012	2-015	2-017	2-020	2-022	0 0 1	1 1 1	2 2 2	
4-1	2-025	2-027	2-030	2-032	2-035	2-037	2-040	2-042	2-045	2-047	0 0 1	1 1 1	2 2 2	
4-2	2-049	2-052	2-054	2-057	2-059	2-062	2-064	2-066	2-069	2-071	0 0 1	1 1 1	2 2 2	
4-3	2-074	2-078	2-078	2-081	2-083	2-086	2-088	2-090	2-093	2-095	0 0 1	1 1 1	2 2 2	
4-4	2-098	2-100	2-102	2-105	2-107	2-110	2-112	2-114	2-117	2-119	0 0 1	1 1 1	2 2 2	
4-5	2-121	2-124	2-126	2-128	2-131	2-133	2-135	2-138	2-140	2-142	0 0 1	1 1 1	2 2 2	
4-6	2-145	2-147	2-149	2-152	2-154	2-156	2-159	2-161	2-163	2-166	0 0 1	1 1 1	2 2 2	
4-7	2-168	2-170	2-173	2-176	2-177	2-179	2-182	2-184	2-186	2-189	0 0 1	1 1 1	2 2 2	
4-8	2-191	2-193	2-195	2-198	2-200	2-202	2-205	2-207	2-209	2-211	0 0 1	1 1 1	2 2 2	
4-9	2-214	2-216	2-218	2-220	2-223	2-225	2-227	2-229	2-232	2-234	0 0 1	1 1 1	2 2 2	
5-0	2-236	2-238	2-241	2-243	2-245	2-247	2-249	2-252	2-254	2-256	0 0 1	1 1 1	2 2 2	
5-1	2-258	2-261	2-263	2-265	2-267	2-269	2-272	2-274	2-276	2-278	0 0 1	1 1 1	2 2 2	
5-2	2-280	2-283	2-285	2-287	2-289	2-291	2-293	2-296	2-298	2-300	0 0 1	1 1 1	2 2 2	
5-3	2-302	2-304	2-307	2-309	2-311	2-313	2-315	2-317	2-319	2-322	0 0 1	1 1 1	2 2 2	
5-4	2-324	2-326	2-328	2-330	2-332	2-335	2-337	2-339	2-341	2-343	0 0 1	1 1 1	1 2 2	
5-5	2-345	2-347	2-349	2-352	2-354	2-356	2-358	2-360	2-362	2-364	0 0 1	1 1 1	1 2 2	

TABLE 3
SQUARE ROOTS
of numbers from 1 to 10

	0	1	2	3	4	5	6	7	8	9	Add :		
											1 2 3	4 5 6	7 8 9
5-5	2-345	2-347	2-349	2-352	2-354	2-356	2-358	2-360	2-362	2-364	0 0 1	1 1 1	1 2 2
5-6	2-366	2-369	2-371	2-373	2-375	2-377	2-379	2-381	2-383	2-385	0 0 1	1 1 1	1 2 2
5-7	2-387	2-390	2-392	2-394	2-396	2-398	2-400	2-402	2-404	2-406	0 0 1	1 1 1	1 2 2
5-8	2-408	2-410	2-412	2-415	2-417	2-419	2-421	2-423	2-425	2-427	0 0 1	1 1 1	1 2 2
5-9	2-429	2-431	2-433	2-435	2-437	2-439	2-441	2-443	2-445	2-447	0 0 1	1 1 1	1 2 2
6-0	2-449	2-452	2-454	2-456	2-458	2-460	2-462	2-464	2-466	2-468	0 0 1	1 1 1	1 2 2
6-1	2-470	2-472	2-474	2-476	2-478	2-480	2-482	2-484	2-486	2-488	0 0 1	1 1 1	1 2 2
6-2	2-490	2-492	2-494	2-496	2-498	2-500	2-502	2-504	2-506	2-508	0 0 1	1 1 1	1 2 2
6-3	2-510	2-512	2-514	2-516	2-518	2-520	2-522	2-524	2-526	2-528	0 0 1	1 1 1	1 2 2
6-4	2-530	2-532	2-534	2-536	2-538	2-540	2-542	2-544	2-546	2-548	0 0 1	1 1 1	1 2 2
6-5	2-550	2-551	2-553	2-555	2-557	2-559	2-561	2-563	2-565	2-567	0 0 1	1 1 1	1 2 2
6-6	2-569	2-571	2-573	2-575	2-577	2-579	2-581	2-583	2-585	2-587	0 0 1	1 1 1	1 2 2
6-7	2-588	2-590	2-592	2-594	2-596	2-598	2-600	2-602	2-604	2-606	0 0 1	1 1 1	1 2 2
6-8	2-608	2-610	2-612	2-613	2-615	2-617	2-619	2-621	2-623	2-625	0 0 1	1 1 1	1 2 2
6-9	2-627	2-629	2-631	2-632	2-634	2-636	2-638	2-640	2-642	2-644	0 0 1	1 1 1	1 2 2
7-0	2-646	2-648	2-650	2-651	2-653	2-655	2-657	2-659	2-661	2-663	0 0 1	1 1 1	1 2 2
7-1	2-665	2-666	2-668	2-670	2-672	2-674	2-676	2-678	2-680	2-681	0 0 1	1 1 1	1 1 2
7-2	2-683	2-685	2-687	2-689	2-691	2-693	2-694	2-696	2-698	2-700	0 0 1	1 1 1	1 1 2
7-3	2-702	2-704	2-706	2-707	2-709	2-711	2-713	2-715	2-717	2-718	0 0 1	1 1 1	1 1 2
7-4	2-720	2-722	2-724	2-726	2-728	2-729	2-731	2-733	2-735	2-737	0 0 1	1 1 1	1 1 2
7-5	2-739	2-740	2-742	2-744	2-746	2-748	2-750	2-751	2-753	2-755	0 0 1	1 1 1	1 1 2
7-6	2-757	2-759	2-760	2-762	2-764	2-766	2-768	2-769	2-771	2-773	0 0 1	1 1 1	1 1 2
7-7	2-775	2-777	2-778	2-780	2-782	2-784	2-786	2-787	2-789	2-791	0 0 1	1 1 1	1 1 2
7-8	2-793	2-795	2-796	2-798	2-800	2-802	2-804	2-805	2-807	2-809	0 0 1	1 1 1	1 1 2
7-9	2-811	2-812	2-814	2-816	2-818	2-820	2-821	2-823	2-825	2-827	0 0 1	1 1 1	1 1 2
8-0	2-828	2-830	2-832	2-834	2-835	2-837	2-839	2-841	2-843	2-844	0 0 1	1 1 1	1 1 2
8-1	2-846	2-848	2-850	2-851	2-853	2-855	2-857	2-858	2-860	2-862	0 0 1	1 1 1	1 1 2
8-2	2-864	2-865	2-867	2-869	2-871	2-872	2-874	2-876	2-877	2-879	0 0 1	1 1 1	1 1 2
8-3	2-881	2-883	2-884	2-886	2-888	2-890	2-891	2-893	2-895	2-897	0 0 1	1 1 1	1 1 2
8-4	2-898	2-900	2-902	2-903	2-905	2-907	2-909	2-910	2-912	2-914	0 0 1	1 1 1	1 1 2
8-5	2-915	2-917	2-919	2-921	2-922	2-924	2-926	2-927	2-929	2-931	0 0 1	1 1 1	1 1 2
8-6	2-933	2-934	2-936	2-938	2-939	2-941	2-943	2-944	2-946	2-948	0 0 1	1 1 1	1 1 2
8-7	2-950	2-951	2-953	2-955	2-956	2-958	2-960	2-961	2-963	2-965	0 0 1	1 1 1	1 1 2
8-8	2-966	2-968	2-970	2-972	2-973	2-975	2-977	2-978	2-980	2-982	0 0 1	1 1 1	1 1 2
8-9	2-983	2-985	2-987	2-988	2-990	2-992	2-993	2-995	2-997	2-998	0 0 1	1 1 1	1 1 2
9-0	3-000	3-002	3-003	3-005	3-007	3-008	3-010	3-012	3-013	3-015	0 0 0	1 1 1	1 1 1
9-1	3-017	3-018	3-020	3-022	3-023	3-025	3-027	3-028	3-030	3-032	0 0 0	1 1 1	1 1 1
9-2	3-033	3-035	3-036	3-038	3-040	3-041	3-043	3-045	3-046	3-048	0 0 0	1 1 1	1 1 1
9-3	3-050	3-051	3-053	3-055	3-056	3-058	3-059	3-061	3-063	3-064	0 0 0	1 1 1	1 1 1
9-4	3-066	3-068	3-069	3-071	3-072	3-074	3-076	3-077	3-079	3-081	0 0 0	1 1 1	1 1 1
9-5	3-082	3-084	3-085	3-087	3-089	3-090	3-092	3-094	3-095	3-097	0 0 0	1 1 1	1 1 1
9-6	3-098	3-100	3-102	3-103	3-105	3-106	3-108	3-110	3-111	3-113	0 0 0	1 1 1	1 1 1
9-7	3-114	3-116	3-118	3-119	3-121	3-122	3-124	3-126	3-127	3-129	0 0 0	1 1 1	1 1 1
9-8	3-130	3-132	3-134	3-135	3-137	3-138	3-140	3-142	3-143	3-145	0 0 0	1 1 1	1 1 1
9-9	3-146	3-148	3-150	3-151	3-153	3-154	3-156	3-158	3-159	3-161	0 0 0	1 1 1	1 1 1
10-0	3-162	3-164	3-165	3-167	3-168	3-170	3-172	3-173	3-175	3-176	0 0 0	0 1 1	1 1 1

TABLE 4
SQUARE ROOTS
of numbers from 10 to 100

	0	1	2	3	4	5	6	7	8	9	Add :					
											1 2 3	4 5 6	7 8 9			
10	3-162	3-178	3-194	3-209	3-225	3-240	3-256	3-271	3-286	3-302	2 3 5	6 8 9	11 12 14			
11	3-317	3-332	3-347	3-362	3-376	3-391	3-406	3-421	3-435	3-450	1 3 4	6 7 9	10 12 13			
12	3-464	3-479	3-493	3-507	3-521	3-536	3-550	3-564	3-578	3-592	1 3 4	6 7 8	10 11 13			
13	3-606	3-619	3-633	3-647	3-661	3-674	3-688	3-701	3-715	3-728	1 3 4	5 7 8	10 11 12			
14	3-742	3-755	3-768	3-782	3-795	3-808	3-821	3-834	3-847	3-860	1 3 4	5 7 8	9 11 12			
15	3-873	3-886	3-899	3-912	3-924	3-937	3-950	3-962	3-975	3-987	1 3 4	5 6 8	9 10 11			
16	4-000	4-012	4-025	4-037	4-050	4-062	4-074	4-087	4-099	4-111	1 2 4	5 6 7	9 10 11			
17	4-123	4-135	4-147	4-159	4-171	4-183	4-195	4-207	4-219	4-231	1 2 4	5 6 7	8 10 11			
18	4-243	4-254	4-266	4-278	4-290	4-301	4-313	4-324	4-336	4-347	1 2 3	5 6 7	8 9 10			
19	4-359	4-370	4-382	4-393	4-405	4-416	4-427	4-438	4-450	4-461	1 2 3	5 6 7	8 9 10			
20	4-472	4-483	4-494	4-506	4-517	4-528	4-539	4-550	4-561	4-572	1 2 3	4 6 7	8 9 10			
21	4-583	4-593	4-604	4-615	4-626	4-637	4-648	4-658	4-669	4-680	1 2 3	4 5 6	8 9 10			
22	4-690	4-701	4-712	4-722	4-733	4-743	4-754	4-764	4-775	4-785	1 2 3	4 5 6	7 8 9			
23	4-796	4-806	4-817	4-827	4-837	4-848	4-858	4-868	4-879	4-889	1 2 3	4 5 6	7 8 9			
24	4-899	4-909	4-919	4-930	4-940	4-950	4-960	4-970	4-980	4-990	1 2 3	4 5 6	7 8 9			
25	5-000	5-010	5-020	5-030	5-040	5-050	5-060	5-070	5-079	5-089	1 2 3	4 5 6	7 8 9			
26	5-099	5-109	5-119	5-128	5-138	5-148	5-158	5-167	5-177	5-187	1 2 3	4 5 6	7 8 9			
27	5-196	5-206	5-215	5-225	5-235	5-244	5-254	5-263	5-273	5-282	1 2 3	4 5 6	7 8 9			
28	5-282	5-301	5-310	5-320	5-329	5-339	5-348	5-357	5-367	5-376	1 2 3	4 5 6	7 7 8			
29	5-385	5-394	5-404	5-413	5-422	5-431	5-441	5-450	5-459	5-468	1 2 3	4 5 5	6 7 8			
30	5-477	5-486	5-495	5-505	5-514	5-523	5-532	5-541	5-550	5-559	1 2 3	4 4 5	6 7 8			
31	5-568	5-577	5-586	5-595	5-604	5-612	5-621	5-630	5-639	5-648	1 2 3	3 4 5	6 7 8			
32	5-657	5-666	5-675	5-683	5-692	5-701	5-710	5-718	5-727	5-736	1 2 3	3 4 5	6 7 8			
33	5-745	5-753	5-762	5-771	5-779	5-788	5-797	5-805	5-814	5-822	1 2 3	3 4 5	6 7 8			
34	5-831	5-840	5-848	5-857	5-865	5-874	5-882	5-891	5-899	5-908	1 2 3	3 4 5	6 7 8			
35	5-916	5-925	5-933	5-941	5-950	5-958	5-967	5-975	5-983	5-992	1 2 2	3 4 5	6 7 8			
36	6-000	6-008	6-017	6-025	6-033	6-042	6-050	6-058	6-066	6-075	1 2 2	3 4 5	6 7 7			
37	6-083	6-091	6-099	6-107	6-116	6-124	6-132	6-140	6-148	6-156	1 2 2	3 4 5	6 7 7			
38	6-164	6-173	6-181	6-189	6-197	6-205	6-213	6-221	6-229	6-237	1 2 2	3 4 5	6 6 7			
39	6-245	6-253	6-261	6-269	6-277	6-285	6-293	6-301	6-309	6-317	1 2 2	3 4 5	6 6 7			
40	6-325	6-332	6-340	6-348	6-356	6-364	6-372	6-380	6-387	6-395	1 2 2	3 4 5	6 6 7			
41	6-403	6-411	6-419	6-427	6-434	6-442	6-450	6-458	6-465	6-473	1 2 2	3 4 5	5 6 7			
42	6-481	6-488	6-496	6-504	6-512	6-519	6-527	6-535	6-542	6-550	1 2 2	3 4 5	5 6 7			
43	6-557	6-565	6-573	6-580	6-588	6-595	6-603	6-611	6-618	6-626	1 2 2	3 4 5	5 6 7			
44	6-633	6-641	6-648	6-656	6-663	6-671	6-678	6-686	6-693	6-701	1 2 2	3 4 5	5 6 7			
45	6-708	6-716	6-723	6-731	6-738	6-745	6-753	6-760	6-768	6-775	1 1 2	3 4 4	5 6 7			
46	6-782	6-790	6-797	6-804	6-812	6-819	6-826	6-834	6-841	6-848	1 1 2	3 4 4	5 6 7			
47	6-856	6-863	6-870	6-877	6-885	6-892	6-899	6-907	6-914	6-921	1 1 2	3 4 4	5 6 7			
48	6-928	6-935	6-943	6-950	6-957	6-964	6-971	6-979	6-986	6-993	1 1 2	3 4 4	5 6 6			
49	7-000	7-007	7-014	7-021	7-029	7-036	7-043	7-050	7-057	7-064	1 1 2	3 4 4	5 6 6			
50	7-071	7-078	7-085	7-092	7-099	7-106	7-113	7-120	7-127	7-134	1 1 2	3 4 4	5 6 6			
51	7-141	7-148	7-155	7-162	7-169	7-176	7-183	7-190	7-197	7-204	1 1 2	3 4 4	5 6 6			
52	7-211	7-218	7-225	7-232	7-239	7-246	7-253	7-259	7-266	7-273	1 1 2	3 3 4	5 6 6			
53	7-280	7-287	7-294	7-301	7-308	7-314	7-321	7-328	7-335	7-342	1 1 2	3 3 4	5 5 6			
54	7-348	7-355	7-362	7-369	7-376	7-382	7-389	7-396	7-403	7-409	1 1 2	3 3 4	5 5 6			
55	7-416	7-423	7-430	7-436	7-443	7-450	7-457	7-463	7-470	7-477	1 1 2	3 3 4	5 5 6			

TABLE 4
 SQUARE ROOTS
 of numbers from 10 to 100

	0	1	2	3	4	5	6	7	8	9	Add :								
											1	2	3	4	5	6	7	8	9
55	7-416	7-423	7-430	7-436	7-443	7-450	7-457	7-463	7-470	7-477	1	1	2	3	3	4	5	5	6
56	7-483	7-490	7-497	7-503	7-510	7-517	7-523	7-530	7-537	7-543	1	1	2	3	3	4	5	5	6
57	7-550	7-556	7-563	7-570	7-576	7-583	7-589	7-596	7-603	7-609	1	1	2	3	3	4	5	5	6
58	7-616	7-622	7-629	7-635	7-642	7-649	7-655	7-662	7-668	7-675	1	1	2	3	3	4	5	5	6
59	7-681	7-688	7-694	7-701	7-707	7-714	7-720	7-727	7-733	7-740	1	1	2	3	3	4	5	5	6
60	7-746	7-752	7-759	7-765	7-772	7-778	7-785	7-791	7-797	7-804	1	1	2	3	3	4	5	5	6
61	7-810	7-817	7-823	7-829	7-836	7-842	7-849	7-855	7-861	7-868	1	1	2	3	3	4	5	5	6
62	7-874	7-880	7-887	7-893	7-899	7-906	7-912	7-918	7-925	7-931	1	1	2	3	3	4	5	5	6
63	7-937	7-944	7-950	7-956	7-962	7-969	7-975	7-981	7-987	7-994	1	1	2	3	3	4	5	5	6
64	8-000	8-006	8-012	8-019	8-025	8-031	8-037	8-044	8-050	8-056	1	1	2	2	3	4	4	5	6
65	8-062	8-068	8-075	8-081	8-087	8-093	8-099	8-106	8-112	8-118	1	1	2	2	3	4	4	5	6
66	8-124	8-130	8-136	8-142	8-149	8-155	8-161	8-167	8-173	8-179	1	1	2	2	3	4	4	5	5
67	8-185	8-191	8-198	8-204	8-210	8-216	8-222	8-228	8-234	8-240	1	1	2	2	3	4	4	5	5
68	8-246	8-252	8-258	8-264	8-270	8-276	8-283	8-289	8-295	8-301	1	1	2	2	3	4	4	5	5
69	8-307	8-313	8-319	8-325	8-331	8-337	8-343	8-349	8-355	8-361	1	1	2	2	3	4	4	5	5
70	8-367	8-373	8-379	8-385	8-390	8-396	8-402	8-408	8-414	8-420	1	1	2	2	3	4	4	5	5
71	8-426	8-432	8-438	8-444	8-450	8-456	8-462	8-468	8-473	8-479	1	1	2	2	3	4	4	5	5
72	8-485	8-491	8-497	8-503	8-509	8-515	8-521	8-526	8-532	8-538	1	1	2	2	3	4	4	5	5
73	8-544	8-550	8-556	8-562	8-567	8-573	8-579	8-585	8-591	8-597	1	1	2	2	3	4	4	5	5
74	8-602	8-608	8-614	8-620	8-626	8-631	8-637	8-643	8-649	8-654	1	1	2	2	3	4	4	5	5
75	8-660	8-666	8-672	8-678	8-683	8-689	8-695	8-701	8-706	8-712	1	1	2	2	3	4	4	5	5
76	8-718	8-724	8-729	8-735	8-741	8-746	8-752	8-758	8-764	8-769	1	1	2	2	3	4	4	5	5
77	8-775	8-781	8-786	8-792	8-798	8-803	8-809	8-815	8-820	8-826	1	1	2	2	3	4	4	5	5
78	8-832	8-837	8-843	8-849	8-854	8-860	8-866	8-871	8-877	8-883	1	1	2	2	3	4	4	5	5
79	8-888	8-894	8-899	8-905	8-911	8-916	8-922	8-927	8-933	8-939	1	1	2	2	3	4	4	5	5
80	8-944	8-950	8-955	8-961	8-967	8-972	8-978	8-983	8-989	8-994	1	1	2	2	3	4	4	5	5
81	9-000	9-006	9-011	9-017	9-022	9-028	9-033	9-039	9-044	9-050	1	1	2	2	3	4	4	5	5
82	9-055	9-061	9-066	9-072	9-077	9-083	9-088	9-094	9-099	9-105	1	1	2	2	3	4	4	5	5
83	9-110	9-116	9-121	9-127	9-132	9-138	9-143	9-149	9-154	9-160	1	1	2	2	3	4	4	5	5
84	9-165	9-171	9-176	9-182	9-187	9-192	9-198	9-203	9-209	9-214	1	1	2	2	3	4	4	5	5
85	9-220	9-225	9-230	9-236	9-241	9-247	9-252	9-257	9-263	9-268	1	1	2	2	3	4	4	5	5
86	9-274	9-279	9-284	9-290	9-295	9-301	9-306	9-311	9-317	9-322	1	1	2	2	3	4	4	5	5
87	9-327	9-333	9-338	9-343	9-349	9-354	9-359	9-365	9-370	9-375	1	1	2	2	3	4	4	5	5
88	9-381	9-386	9-391	9-397	9-402	9-407	9-413	9-418	9-423	9-429	1	1	2	2	3	4	4	5	5
89	9-434	9-439	9-445	9-450	9-455	9-460	9-466	9-471	9-476	9-482	1	1	2	2	3	4	4	5	5
90	9-487	9-492	9-497	9-503	9-508	9-513	9-518	9-524	9-529	9-534	1	1	2	2	3	4	4	5	5
91	9-539	9-545	9-550	9-555	9-560	9-566	9-571	9-576	9-581	9-586	1	1	2	2	3	4	4	5	5
92	9-592	9-597	9-602	9-607	9-612	9-618	9-623	9-628	9-633	9-638	1	1	2	2	3	4	4	5	5
93	9-644	9-649	9-654	9-659	9-664	9-670	9-675	9-680	9-685	9-690	1	1	2	2	3	4	4	5	5
94	9-695	9-701	9-706	9-711	9-716	9-721	9-726	9-731	9-737	9-742	1	1	2	2	3	4	4	5	5
95	9-747	9-752	9-757	9-762	9-767	9-772	9-778	9-783	9-788	9-793	1	1	2	2	3	4	4	5	5
96	9-798	9-803	9-808	9-813	9-818	9-823	9-829	9-834	9-839	9-844	1	1	2	2	3	4	4	5	5
97	9-849	9-854	9-859	9-864	9-869	9-874	9-879	9-884	9-889	9-894	1	1	2	2	3	4	4	5	5
98	9-899	9-905	9-910	9-915	9-920	9-925	9-930	9-935	9-940	9-945	0	1	2	2	3	4	4	5	5
99	9-950	9-955	9-960	9-965	9-970	9-975	9-980	9-985	9-990	9-995	0	1	2	2	3	4	4	5	5
100	10-000	10-005	10-010	10-015	10-020	10-024	10-029	10-034	10-039	10-044	0	1	2	2	3	4	4	5	5

TABLE 1
COMMON LOGARITHMS
(Logarithms to Base 10)

	0	1	2	3	4	5	6	7	8	9	Add :								
											1	2	3	4	5	6	7	8	9
10	0.0000	0043	0086	0128	0170	0212	0253	0294	0334	0374	4	8	12	17	21	25	29	33	37
11	0.0414	0453	0492	0531	0569	0607	0645	0682	0719	0755	4	8	11	15	19	23	26	30	34
12	0.0732	0828	0864	0899	0934	0969	1004	1038	1072	1106	3	7	10	14	17	21	24	28	31
13	0.1139	1173	1206	1239	1271	1303	1335	1367	1399	1430	3	6	10	13	16	19	23	26	29
14	0.1461	1492	1523	1553	1584	1614	1644	1673	1703	1732	3	6	9	12	15	18	21	24	27
15	0.1761	1790	1818	1847	1875	1903	1931	1959	1987	2014	3	6	8	11	14	17	20	22	25
16	0.2041	2068	2095	2122	2148	2175	2201	2227	2253	2279	3	5	8	11	13	16	18	21	24
17	0.2304	2330	2355	2380	2405	2430	2455	2480	2504	2529	2	5	7	10	12	15	17	20	22
18	0.2553	2577	2601	2625	2648	2672	2695	2718	2742	2765	2	5	7	9	12	14	16	19	21
19	0.2788	2810	2833	2856	2878	2900	2923	2945	2967	2989	2	4	7	9	11	13	16	18	20
20	0.3010	3032	3054	3075	3096	3118	3139	3160	3181	3201	2	4	6	8	11	13	15	17	19
21	0.3222	3243	3263	3284	3304	3324	3345	3365	3385	3404	2	4	6	8	10	12	14	16	18
22	0.3424	3444	3464	3483	3502	3522	3541	3560	3579	3598	2	4	6	8	10	12	14	15	17
23	0.3617	3636	3655	3674	3692	3711	3729	3747	3766	3784	2	4	6	7	9	11	13	15	17
24	0.3802	3820	3838	3856	3874	3892	3909	3927	3945	3962	2	4	5	7	9	11	12	14	16
25	0.3979	3997	4014	4031	4048	4065	4082	4099	4116	4133	2	3	5	7	9	10	12	14	15
26	0.4150	4166	4183	4200	4216	4232	4249	4265	4281	4298	2	3	5	7	8	10	11	13	15
27	0.4314	4330	4346	4362	4378	4393	4409	4425	4440	4456	2	3	5	6	8	9	11	13	14
28	0.4472	4487	4502	4518	4533	4548	4564	4579	4594	4609	2	3	5	6	8	9	11	12	14
29	0.4624	4639	4654	4669	4683	4698	4713	4728	4742	4757	1	3	4	6	7	9	10	12	13
30	0.4771	4786	4800	4814	4829	4843	4857	4871	4886	4900	1	3	4	6	7	9	10	11	13
31	0.4914	4928	4942	4955	4969	4983	4997	5011	5024	5038	1	3	4	6	7	8	10	11	12
32	0.5051	5065	5079	5092	5105	5119	5132	5145	5159	5172	1	3	4	5	7	8	9	11	12
33	0.5185	5198	5211	5224	5237	5250	5263	5276	5289	5302	1	3	4	5	6	8	9	10	12
34	0.5315	5328	5340	5353	5366	5378	5391	5403	5416	5428	1	3	4	5	6	8	9	10	11
35	0.5441	5453	5465	5478	5490	5502	5514	5527	5539	5551	1	2	4	5	6	7	9	10	11
36	0.5563	5575	5587	5599	5611	5623	5635	5647	5658	5670	1	2	4	5	6	7	8	10	11
37	0.5682	5694	5705	5717	5729	5740	5752	5763	5775	5786	1	2	3	5	6	7	8	9	10
38	0.5798	5809	5821	5832	5843	5855	5866	5877	5888	5899	1	2	3	5	6	7	8	9	10
39	0.5911	5922	5933	5944	5955	5966	5977	5988	5999	6010	1	2	3	4	5	7	8	9	10
40	0.6021	6031	6042	6053	6064	6075	6085	6096	6107	6117	1	2	3	4	5	6	8	9	10
41	0.6128	6138	6149	6160	6170	6180	6191	6201	6212	6222	1	2	3	4	5	6	7	8	9
42	0.6232	6243	6253	6263	6274	6284	6294	6304	6314	6325	1	2	3	4	5	6	7	8	9
43	0.6335	6345	6355	6365	6375	6385	6395	6405	6415	6425	1	2	3	4	5	6	7	8	9
44	0.6435	6444	6454	6464	6474	6484	6493	6503	6513	6522	1	2	3	4	5	6	7	8	9
45	0.6532	6542	6551	6561	6571	6580	6590	6599	6609	6618	1	2	3	4	5	6	7	8	9
46	0.6628	6637	6646	6656	6665	6675	6684	6693	6702	6712	1	2	3	4	5	6	7	7	8
47	0.6721	6730	6739	6749	6758	6767	6776	6785	6794	6803	1	2	3	4	5	5	6	7	8
48	0.6812	6821	6830	6839	6848	6857	6866	6875	6884	6893	1	2	3	4	4	5	6	7	8
49	0.6902	6911	6920	6928	6937	6946	6955	6964	6972	6981	1	2	3	4	4	5	6	7	8
50	0.6990	6998	7007	7016	7024	7033	7042	7050	7059	7067	1	2	3	3	4	5	6	7	8
51	0.7076	7084	7093	7101	7110	7118	7126	7135	7143	7152	1	2	3	3	4	5	6	7	8
52	0.7160	7168	7177	7185	7193	7202	7210	7218	7226	7235	1	2	2	3	4	5	6	7	7
53	0.7243	7251	7259	7267	7275	7284	7292	7300	7308	7316	1	2	2	3	4	5	6	6	7
54	0.7324	7332	7340	7348	7356	7364	7372	7380	7388	7396	1	2	2	3	4	5	6	6	7
55	0.7404	7412	7419	7427	7435	7443	7451	7459	7466	7474	1	2	2	3	4	5	5	6	7

TABLE 5
COMMON LOGARITHMS
(Logarithms to Base 10)

	0	1	2	3	4	5	6	7	8	9	Add :								
											1	2	3	4	5	6	7	8	9
55	0.7404	7412	7419	7427	7435	7443	7451	7459	7466	7474	1	2	2	3	4	5	5	6	7
56	0.7482	7490	7497	7505	7513	7520	7528	7536	7543	7551	1	2	2	3	4	5	5	6	7
57	0.7559	7566	7574	7582	7589	7597	7604	7612	7619	7627	1	2	2	3	4	5	5	6	7
58	0.7634	7642	7649	7657	7664	7672	7679	7686	7694	7701	1	1	2	3	4	4	5	6	7
59	0.7709	7716	7723	7731	7738	7745	7752	7760	7767	7774	1	1	2	3	4	4	5	6	7
60	0.7782	7789	7796	7803	7810	7818	7825	7832	7839	7846	1	1	2	3	4	4	5	6	6
61	0.7853	7860	7868	7875	7882	7889	7896	7903	7910	7917	1	1	2	3	4	4	5	6	6
62	0.7924	7931	7938	7945	7952	7959	7966	7973	7980	7987	1	1	2	3	3	4	5	6	6
63	0.7993	8000	8007	8014	8021	8028	8035	8041	8048	8055	1	1	2	3	3	4	5	5	6
64	0.8062	8069	8075	8082	8089	8096	8102	8109	8116	8122	1	1	2	3	3	4	5	5	6
65	0.8129	8136	8142	8149	8156	8162	8169	8176	8182	8189	1	1	2	3	3	4	5	5	6
66	0.8195	8202	8209	8215	8222	8228	8235	8241	8248	8254	1	1	2	3	3	4	5	5	6
67	0.8261	8267	8274	8280	8287	8293	8299	8306	8312	8319	1	1	2	3	3	4	5	5	6
68	0.8325	8331	8338	8344	8351	8357	8363	8370	8376	8382	1	1	2	3	3	4	4	5	6
69	0.8388	8395	8401	8407	8414	8420	8426	8432	8439	8445	1	1	2	2	3	4	4	5	6
70	0.8451	8457	8463	8470	8476	8482	8488	8494	8500	8506	1	1	2	2	3	4	4	5	6
71	0.8513	8519	8525	8531	8537	8543	8549	8555	8561	8567	1	1	2	2	3	4	4	5	5
72	0.8573	8579	8585	8591	8597	8603	8609	8615	8621	8627	1	1	2	2	3	4	4	5	5
73	0.8633	8639	8645	8651	8657	8663	8669	8675	8681	8686	1	1	2	2	3	4	4	5	5
74	0.8692	8698	8704	8710	8716	8722	8727	8733	8739	8745	1	1	2	2	3	4	4	5	5
75	0.8751	8756	8762	8768	8774	8779	8785	8791	8797	8802	1	1	2	2	3	3	4	5	5
76	0.8808	8814	8820	8825	8831	8837	8842	8848	8854	8859	1	1	2	2	3	3	4	5	5
77	0.8865	8871	8876	8882	8887	8893	8899	8904	8910	8915	1	1	2	2	3	3	4	4	5
78	0.8921	8927	8932	8938	8943	8949	8954	8960	8965	8971	1	1	2	2	3	3	4	4	5
79	0.8976	8982	8987	8993	8998	9004	9009	9015	9020	9025	1	1	2	2	3	3	4	4	5
80	0.9031	9036	9042	9047	9053	9058	9063	9069	9074	9079	1	1	2	2	3	3	4	4	5
81	0.9085	9090	9096	9101	9106	9112	9117	9122	9128	9133	1	1	2	2	3	3	4	4	5
82	0.9138	9143	9149	9154	9159	9165	9170	9175	9180	9186	1	1	2	2	3	3	4	4	5
83	0.9191	9196	9201	9206	9212	9217	9222	9227	9232	9238	1	1	2	2	3	3	4	4	5
84	0.9243	9248	9253	9258	9263	9269	9274	9279	9284	9289	1	1	2	2	3	3	4	4	5
85	0.9294	9299	9304	9309	9315	9320	9325	9330	9335	9340	1	1	2	2	3	3	4	4	5
86	0.9345	9350	9355	9360	9365	9370	9375	9380	9385	9390	1	1	2	2	3	3	4	4	5
87	0.9395	9400	9405	9410	9415	9420	9425	9430	9435	9440	0	1	1	2	2	3	3	4	4
88	0.9445	9450	9455	9460	9465	9469	9474	9479	9484	9489	0	1	1	2	2	3	3	4	4
89	0.9494	9499	9504	9509	9513	9518	9523	9528	9533	9538	0	1	1	2	2	3	3	4	4
90	0.9542	9547	9552	9557	9562	9566	9571	9576	9581	9586	0	1	1	2	2	3	3	4	4
91	0.9590	9595	9600	9605	9609	9614	9619	9624	9628	9633	0	1	1	2	2	3	3	4	4
92	0.9638	9643	9647	9652	9657	9661	9666	9671	9675	9680	0	1	1	2	2	3	3	4	4
93	0.9685	9689	9694	9699	9703	9708	9713	9717	9722	9727	0	1	1	2	2	3	3	4	4
94	0.9731	9736	9741	9745	9750	9754	9759	9763	9768	9773	0	1	1	2	2	3	3	4	4
95	0.9777	9782	9786	9791	9795	9800	9805	9809	9814	9818	0	1	1	2	2	3	3	4	4
96	0.9823	9827	9832	9836	9841	9845	9850	9854	9859	9863	0	1	1	2	2	3	3	4	4
97	0.9868	9872	9877	9881	9886	9890	9894	9899	9903	9908	0	1	1	2	2	3	3	4	4
98	0.9912	9917	9921	9926	9930	9934	9939	9943	9948	9952	0	1	1	2	2	3	3	4	4
99	0.9956	9961	9965	9969	9974	9978	9983	9987	9991	9996	0	1	1	2	2	3	3	4	4
100	0.0000	0004	0009	0013	0017	0022	0026	0030	0035	0039	0	1	1	2	2	3	3	4	4

TABLE 6
ANTILOGARITHMS

	0	1	2	3	4	5	6	7	8	9	Add :								
											1	2	3	4	5	6	7	8	9
·00	1000	1002	1005	1007	1009	1012	1014	1016	1019	1021	0 0 1	1 1 1	2 2 2						
·01	1023	1026	1028	1030	1033	1035	1038	1040	1042	1045	0 0 1	1 1 1	2 2 2						
·02	1047	1050	1052	1054	1057	1059	1062	1064	1067	1069	0 0 1	1 1 1	2 2 2						
·03	1072	1074	1076	1079	1081	1084	1086	1089	1091	1094	0 0 1	1 1 1	2 2 2						
·04	1096	1099	1102	1104	1107	1109	1112	1114	1117	1119	0 1 1	1 1 2	2 2 2						
·05	1122	1125	1127	1130	1132	1135	1138	1140	1143	1146	0 1 1	1 1 2	2 2 2						
·06	1148	1151	1153	1156	1159	1161	1164	1167	1169	1172	0 1 1	1 1 2	2 2 2						
·07	1175	1178	1180	1183	1186	1189	1191	1194	1197	1199	0 1 1	1 1 2	2 2 2						
·08	1202	1205	1208	1211	1213	1216	1219	1222	1225	1227	0 1 1	1 1 2	2 2 3						
·09	1230	1233	1236	1239	1242	1245	1247	1250	1253	1256	0 1 1	1 1 2	2 2 3						
·10	1259	1262	1265	1268	1271	1274	1276	1279	1282	1285	0 1 1	1 1 2	2 2 3						
·11	1288	1291	1294	1297	1300	1303	1306	1309	1312	1315	0 1 1	1 2 2	2 2 3						
·12	1318	1321	1324	1327	1330	1334	1337	1340	1343	1346	0 1 1	1 2 2	2 2 3						
·13	1349	1352	1355	1358	1361	1365	1368	1371	1374	1377	0 1 1	1 2 2	2 3 3						
·14	1380	1384	1387	1390	1393	1396	1400	1403	1406	1409	0 1 1	1 2 2	2 3 3						
·15	1413	1416	1419	1422	1426	1429	1432	1435	1439	1442	0 1 1	1 2 2	2 3 3						
·16	1445	1449	1452	1455	1459	1462	1466	1469	1472	1476	0 1 1	1 2 2	2 3 3						
·17	1479	1483	1486	1489	1493	1496	1500	1503	1507	1510	0 1 1	1 2 2	2 3 3						
·18	1514	1517	1521	1524	1528	1531	1535	1538	1542	1545	0 1 1	1 2 2	2 3 3						
·19	1549	1552	1556	1560	1563	1567	1570	1574	1578	1581	0 1 1	1 2 2	2 3 3						
·20	1585	1589	1592	1596	1600	1603	1607	1611	1614	1618	0 1 1	1 2 2	3 3 3						
·21	1622	1626	1629	1633	1637	1641	1644	1648	1652	1656	0 1 1	2 2 2	3 3 3						
·22	1660	1663	1667	1671	1675	1679	1683	1687	1690	1694	0 1 1	2 2 2	3 3 3						
·23	1698	1702	1706	1710	1714	1718	1722	1726	1730	1734	0 1 1	2 2 2	3 3 4						
·24	1738	1742	1746	1750	1754	1758	1762	1766	1770	1774	0 1 1	2 2 2	3 3 4						
·25	1778	1782	1786	1791	1795	1799	1803	1807	1811	1816	0 1 1	2 2 2	3 3 4						
·26	1820	1824	1828	1832	1837	1841	1845	1849	1854	1858	0 1 1	2 2 3	3 3 4						
·27	1862	1866	1871	1875	1879	1884	1888	1892	1897	1901	0 1 1	2 2 3	3 3 4						
·28	1905	1910	1914	1919	1923	1928	1932	1936	1941	1945	0 1 1	2 2 3	3 4 4						
·29	1950	1954	1959	1963	1968	1972	1977	1982	1986	1991	0 1 1	2 2 3	3 4 4						
·30	1995	2000	2004	2009	2014	2018	2023	2028	2032	2037	0 1 1	2 2 3	3 4 4						
·31	2042	2046	2051	2056	2061	2065	2070	2075	2080	2084	0 1 1	2 2 3	3 4 4						
·32	2089	2094	2099	2104	2109	2113	2118	2123	2128	2133	0 1 1	2 2 3	3 4 4						
·33	2138	2143	2148	2153	2158	2163	2168	2173	2178	2183	0 1 1	2 2 3	3 4 4						
·34	2188	2193	2198	2203	2208	2213	2218	2223	2228	2234	1 1 2	2 3 3	4 4 5						
·35	2239	2244	2249	2254	2259	2265	2270	2275	2280	2286	1 1 2	2 3 3	4 4 5						
·36	2291	2296	2301	2307	2312	2317	2323	2328	2333	2339	1 1 2	2 3 3	4 4 5						
·37	2344	2350	2355	2360	2366	2371	2377	2382	2388	2393	1 1 2	2 3 3	4 4 5						
·38	2399	2404	2410	2415	2421	2427	2432	2438	2443	2449	1 1 2	2 3 3	4 4 5						
·39	2455	2460	2466	2472	2477	2483	2489	2495	2500	2506	1 1 2	2 3 3	4 5 5						
·40	2512	2518	2523	2529	2535	2541	2547	2553	2559	2564	1 1 2	2 3 4	4 5 5						
·41	2570	2576	2582	2588	2594	2600	2606	2612	2618	2624	1 1 2	2 3 4	4 5 5						
·42	2630	2636	2642	2649	2655	2661	2667	2673	2679	2685	1 1 2	2 3 4	4 5 6						
·43	2692	2698	2704	2710	2716	2723	2729	2735	2742	2748	1 1 2	2 3 4	4 5 6						
·44	2754	2761	2767	2773	2780	2786	2793	2799	2805	2812	1 1 2	2 3 4	4 5 6						
·45	2818	2825	2831	2838	2844	2851	2858	2864	2871	2877	1 1 2	2 3 4	4 5 6						
·46	2884	2891	2897	2904	2911	2917	2924	2931	2938	2944	1 1 2	2 3 4	4 5 6						
·47	2951	2958	2965	2972	2979	2985	2992	2999	3006	3013	1 1 2	2 3 4	4 5 6						
·48	3020	3027	3034	3041	3048	3055	3062	3069	3076	3083	1 1 2	2 3 4	4 5 6						
·49	3090	3097	3105	3112	3119	3126	3133	3141	3148	3155	1 1 2	2 3 4	4 5 6						
·50	3162	3170	3177	3184	3192	3199	3206	3214	3221	3228	1 1 2	2 3 4	4 5 6 7						

ANTILOGARITHMS

	0	1	2	3	4	5	6	7	8	9	Add								
											1	2	3	4	5	6	7	8	9
·50	8162	8170	8177	8184	8192	8199	8206	8214	8221	8228	1	1	2	3	4	4	5	6	7
·51	8236	8243	8251	8258	8266	8273	8281	8289	8296	8304	1	2	2	3	4	5	5	6	7
·52	8311	8319	8327	8334	8342	8350	8357	8365	8373	8381	1	2	2	3	4	5	5	6	7
·53	8388	8396	8404	8412	8420	8428	8436	8443	8451	8459	1	2	2	3	4	5	6	6	7
·54	8467	8475	8483	8491	8499	8508	8516	8524	8532	8540	1	2	2	3	4	5	6	6	7
·55	3548	3556	3565	3573	3581	3589	3597	3606	3614	3622	1	2	2	3	4	5	6	7	7
·56	3631	3639	3648	3656	3664	3673	3681	3690	3698	3707	1	2	3	3	4	5	6	7	8
·57	3715	3724	3733	3741	3750	3758	3767	3776	3784	3793	1	2	3	3	4	5	6	7	8
·58	3802	3811	3819	3828	3837	3846	3855	3864	3873	3882	1	2	3	4	4	5	6	7	8
·59	3890	3899	3908	3917	3926	3936	3945	3954	3963	3972	1	2	3	4	5	5	6	7	8
·60	3981	3990	3999	4009	4018	4027	4036	4046	4055	4064	1	2	3	4	5	6	6	7	8
·61	4074	4083	4093	4102	4111	4121	4130	4140	4150	4159	1	2	3	4	5	6	7	8	9
·62	4169	4178	4188	4198	4207	4217	4227	4236	4246	4256	1	2	3	4	5	6	7	8	9
·63	4266	4276	4285	4295	4305	4315	4325	4335	4345	4355	1	2	3	4	5	6	7	8	9
·64	4865	4375	4385	4395	4406	4416	4426	4436	4446	4457	1	2	3	4	5	6	7	8	9
·65	4467	4477	4487	4498	4508	4519	4529	4539	4550	4560	1	2	3	4	5	6	7	8	9
·66	4571	4581	4592	4603	4613	4624	4634	4645	4656	4667	1	2	3	4	5	6	7	9	10
·67	4677	4688	4699	4710	4721	4732	4742	4753	4764	4775	1	2	3	4	5	7	8	9	10
·68	4786	4797	4808	4819	4831	4842	4853	4864	4875	4887	1	2	3	4	6	7	8	9	10
·69	4898	4909	4920	4932	4943	4955	4966	4977	4989	5000	1	2	3	5	6	7	8	9	10
·70	5012	5023	5035	5047	5058	5070	5082	5093	5105	5117	1	2	4	5	6	7	8	9	11
·71	5129	5140	5152	5164	5176	5188	5200	5212	5224	5236	1	2	4	5	6	7	8	10	11
·72	5248	5260	5272	5284	5297	5309	5321	5333	5346	5358	1	2	4	5	6	7	9	10	11
·73	5370	5383	5395	5408	5420	5433	5445	5458	5470	5483	1	3	4	5	6	8	9	10	11
·74	5495	5508	5521	5534	5546	5559	5572	5585	5598	5610	1	3	4	5	6	8	9	10	12
·75	5623	5636	5649	5662	5675	5689	5702	5715	5728	5741	1	3	4	5	7	8	9	10	12
·76	5754	5768	5781	5794	5808	5821	5834	5848	5861	5875	1	3	4	5	7	8	9	11	12
·77	5888	5902	5916	5929	5943	5957	5970	5984	5998	6012	1	3	4	5	7	8	10	11	12
·78	6026	6039	6053	6067	6081	6095	6109	6124	6138	6152	1	3	4	6	7	8	10	11	13
·79	6166	6180	6194	6209	6223	6237	6252	6266	6281	6295	1	3	4	6	7	9	10	11	13
·80	6310	6324	6339	6353	6368	6383	6397	6412	6427	6442	1	3	4	6	7	9	10	12	13
·81	6457	6471	6486	6501	6516	6531	6546	6561	6577	6592	2	3	5	6	8	9	11	12	14
·82	6607	6622	6637	6653	6668	6683	6699	6714	6730	6745	2	3	5	6	8	9	11	12	14
·83	6761	6776	6792	6808	6823	6839	6855	6871	6887	6902	2	3	5	6	8	9	11	13	14
·84	6918	6934	6950	6966	6982	6998	7015	7031	7047	7063	2	3	5	6	8	10	11	13	15
·85	7079	7096	7112	7129	7145	7161	7178	7194	7211	7228	2	3	5	7	8	10	12	13	15
·86	7244	7261	7278	7295	7311	7328	7345	7362	7379	7396	2	3	5	7	8	10	12	13	15
·87	7413	7430	7447	7464	7482	7499	7516	7534	7551	7568	2	3	5	7	9	10	12	14	16
·88	7586	7603	7621	7638	7656	7674	7691	7709	7727	7745	2	4	5	7	9	11	12	14	16
·89	7762	7780	7798	7816	7834	7852	7870	7889	7907	7925	2	4	5	7	9	11	13	14	16
·90	7943	7962	7980	7998	8017	8035	8054	8072	8091	8110	2	4	6	7	9	11	13	15	17
·91	8128	8147	8166	8185	8204	8222	8241	8260	8279	8299	2	4	6	8	9	11	13	15	17
·92	8318	8337	8356	8375	8395	8414	8433	8453	8472	8492	2	4	6	8	10	12	14	15	17
·93	8511	8531	8551	8570	8590	8610	8630	8650	8670	8690	2	4	6	8	10	12	14	16	18
·94	8710	8730	8750	8770	8790	8810	8831	8851	8872	8892	2	4	6	8	10	12	14	16	18
·95	8913	8933	8954	8974	8995	9016	9036	9057	9078	9099	2	4	6	8	10	12	15	17	19
·96	9120	9141	9162	9183	9204	9226	9247	9268	9290	9311	2	4	6	8	11	13	15	17	19
·97	9333	9354	9376	9397	9419	9441	9462	9484	9506	9528	2	4	7	9	11	13	15	17	20
·98	9550	9572	9594	9616	9638	9661	9683	9705	9727	9750	2	4	7	9	11	13	16	18	20
·99	9772	9795	9817	9840	9863	9886	9908	9931	9954	9977	2	5	7	9	11	14	16	18	20

HYPERBOLIC (NAPIERIAN) LOGARITHMS

(Logarithms to Base e)

No.	0	1	2	3	4	5	6	7	8	9	Subsidiary Table								
											No.	Hyp. Log.	No.	Hyp. Log.					
0-1	3-6974	7927	8797	9589	0339	1029	1674	2280	2852	3393	6	1-7918	40	3-6889					
0-2	2-3906	4393	4859	5303	5729	6137	6529	6907	7270	7621	7	1-9459	50	3-9120					
0-3	2-7960	8298	8606	8913	9212	9502	9783	0057	0324	0584	8	2-0794	60	4-0943					
0-4	1-0837	1084	1325	1560	1790	2015	2235	2450	2660	2866	9	2-1972	70	4-2485					
0-5	1-3068	3267	3461	3651	3838	4022	4202	4379	4553	4724	10	2-3026	80	4-3820					
0-6	1-4892	5057	5220	5380	5537	5692	5845	5995	6143	6289	20	2-9957	90	4-4998					
0-7	1-6433	6575	6715	6853	6989	7123	7256	7386	7515	7643	30	3-4012	100	4-6052					
0-8	1-7769	7893	8015	8137	8256	8375	8492	8607	8722	8835	Add :								
0-9	1-8946	9057	9166	9274	9381	9487	9592	9695	9798	9899									
1-0	0-0000	0100	0198	0296	0392	0488	0583	0677	0770	0862	1	2	3	4	5	6	7	8	9
1-1	0-0953	1044	1133	1222	1310	1398	1484	1570	1655	1740	9	17 26	35	44	52	61	70	78	
1-2	0-1823	1906	1989	2070	2151	2231	2311	2390	2469	2546	8	16 24	32	40	48	56	64	72	
1-3	0-2624	2700	2776	2852	2927	3001	3075	3148	3221	3293	7	15 22	30	37	45	52	59	67	
1-4	0-3365	3436	3507	3577	3646	3716	3784	3853	3920	3988	6	14 21	28	35	41	48	55	62	
1-5	0-4055	4121	4187	4253	4318	4383	4447	4511	4571	4637	5	13 19	26	32	39	45	52	58	
1-6	0-4700	4782	4824	4886	4947	5008	5068	5128	5188	5247	4	12 18	24	30	36	42	48	55	
1-7	0-5306	5365	5423	5481	5539	5596	5653	5710	5768	5822	3	11 17	23	29	34	40	46	52	
1-8	0-5878	5933	5988	6043	6098	6152	6206	6259	6313	6366	2	10 16	22	27	32	38	43	49	
1-9	0-6419	6471	6523	6575	6627	6678	6729	6780	6831	6881	1	9 15	20	26	31	36	41	46	
2-0	0-6931	6981	7031	7080	7129	7178	7227	7275	7324	7372	5	10 15	20	24	29	34	39	44	
2-1	0-7419	7467	7514	7561	7608	7655	7701	7747	7793	7839	4	9 14	19	23	28	33	37	42	
2-2	0-7885	7930	7975	8020	8065	8109	8154	8198	8242	8286	3	8 13	18	22	27	31	36	40	
2-3	0-8329	8372	8416	8459	8502	8544	8587	8629	8671	8713	2	7 13	17	21	26	30	34	38	
2-4	0-8755	8796	8838	8879	8920	8961	9002	9042	9083	9123	1	6 12	16	20	24	29	33	37	
2-5	0-9163	9203	9243	9282	9322	9361	9400	9439	9478	9517	4	8 12	16	20	24	27	31	35	
2-6	0-9555	9594	9632	9670	9708	9746	9783	9821	9858	9895	3	7 11	15	19	23	26	30	34	
2-7	0-9933	9969	0006	0043	0080	0116	0152	0188	0225	0260	2	6 11	15	18	22	26	29	33	
2-8	1-0296	0332	0367	0403	0438	0473	0508	0543	0578	0613	1	5 11	14	18	21	25	28	32	
2-9	1-0647	0682	0716	0750	0784	0818	0852	0886	0919	0953	3	7 10	14	17	20	24	27	31	
3-0	1-0986	1019	1053	1086	1119	1151	1184	1217	1249	1282	3	7 10	13	16	20	23	26	30	
3-1	1-1314	1346	1378	1410	1442	1474	1506	1537	1569	1600	2	6 10	13	16	19	22	25	29	
3-2	1-1632	1663	1694	1725	1756	1787	1817	1848	1878	1909	1	5 9	12	15	18	21	25	28	
3-3	1-1939	1969	2000	2030	2060	2090	2119	2149	2179	2208	3	6 9	12	15	18	21	24	27	
3-4	1-2238	2267	2296	2326	2355	2384	2413	2442	2470	2499	2	5 9	12	14	17	20	23	26	
3-5	1-2528	2556	2585	2613	2641	2669	2698	2726	2754	2782	1	4 8	11	14	17	20	22	25	
3-6	1-2809	2837	2865	2892	2920	2947	2975	3002	3029	3056	3	5 8	11	14	16	19	22	25	
3-7	1-3083	3110	3137	3164	3191	3218	3244	3271	3297	3324	2	4 8	11	13	16	19	21	24	
3-8	1-3350	3376	3403	3429	3455	3481	3507	3533	3558	3584	1	3 8	10	13	16	18	21	23	
3-9	1-3610	3635	3661	3686	3712	3737	3762	3788	3813	3838	3	5 8	10	13	15	18	20	23	
4-0	1-3883	3888	3913	3938	3962	3987	4012	4036	4061	4085	2	5 7	10	12	15	17	20	22	
4-1	1-4110	4134	4159	4183	4207	4231	4255	4279	4303	4327	2	5 7	10	12	14	17	19	22	
4-2	1-4351	4375	4398	4422	4446	4469	4493	4516	4540	4563	1	4 7	9	12	14	16	19	21	
4-3	1-4586	4609	4633	4656	4679	4702	4725	4748	4770	4793	2	5 7	9	11	14	16	18	21	
4-4	1-4816	4839	4861	4884	4907	4929	4951	4974	4996	5019	1	4 7	9	11	13	16	18	20	
4-5	1-5041	5063	5085	5107	5129	5151	5173	5195	5217	5239	2	4 7	9	11	13	15	18	20	
4-6	1-5261	5282	5304	5326	5347	5369	5390	5412	5433	5454	1	3 6	9	11	13	15	17	19	
4-7	1-5478	5497	5518	5539	5560	5581	5602	5623	5644	5665	2	4 6	8	11	13	15	17	19	
4-8	1-5688	5707	5728	5748	5769	5790	5810	5831	5851	5872	1	3 6	8	10	12	14	16	19	
4-9	1-5892	5913	5933	5953	5974	5994	6014	6034	6054	6074	2	4 6	8	10	12	14	16	18	
5-0	1-6094	6114	6134	6154	6174	6194	6214	6233	6253	6273	1	2 4 6	8	10	12	14	16	18	

HYPERBOLIC (NAPIERIAN) LOGARITHMS
(Logarithms to Base e)

No.	0	1	2	3	4	5	6	7	8	9	Add :			
											1 2 3	4 5 6	7 8 9	
5-0	1-6094	6114	6134	6154	6174	6194	6214	6233	6253	6273	2 4 6	8 10 12	14 16 18	
5-1	1-6292	6312	6332	6351	6371	6390	6409	6429	6448	6467	2 4 6	8 10 12	14 16 18	
5-2	1-6487	6506	6525	6544	6563	6582	6601	6620	6639	6658	2 4 6	8 10 11	13 15 17	
5-3	1-6677	6696	6715	6734	6752	6771	6790	6808	6827	6845	2 4 6	8 10 11	13 15 17	
5-4	1-6864	6882	6901	6919	6938	6956	6974	6993	7011	7029	2 4 6	8 10 11	13 15 17	
5-5	1-7047	7066	7084	7102	7120	7138	7156	7174	7192	7210	2 4 5	7 9 11	13 14 16	
5-6	1-7228	7246	7263	7281	7299	7317	7334	7352	7370	7387	2 4 5	7 9 11	12 14 16	
5-7	1-7405	7422	7440	7457	7475	7492	7509	7527	7544	7561	2 3 5	7 9 10	12 14 16	
5-8	1-7579	7596	7613	7630	7647	7664	7681	7699	7716	7733	2 3 5	7 9 10	12 14 16	
5-9	1-7750	7768	7783	7800	7817	7834	7851	7867	7884	7901	2 3 5	7 8 10	12 13 15	
6-0	1-7918	7934	7951	7967	7984	8001	8017	8034	8050	8066	2 3 5	7 8 10	12 13 15	
6-1	1-8083	8099	8116	8132	8148	8165	8181	8197	8213	8229	2 3 5	6 8 10	11 13 15	
6-2	1-8245	8262	8278	8294	8310	8326	8342	8358	8374	8390	2 3 5	6 8 10	11 13 14	
6-3	1-8405	8421	8437	8453	8469	8485	8500	8516	8532	8547	2 3 5	6 8 9	11 12 14	
6-4	1-8563	8579	8594	8610	8625	8641	8656	8672	8687	8703	2 3 5	6 8 9	11 12 14	
6-5	1-8718	8733	8749	8764	8779	8795	8810	8825	8840	8856	2 3 5	6 8 9	11 12 14	
6-6	1-8871	8886	8901	8916	8931	8946	8961	8976	8991	9006	2 3 5	6 8 9	11 12 14	
6-7	1-9021	9036	9051	9066	9081	9095	9110	9125	9140	9155	1 3 4	6 7 9	10 12 13	
6-8	1-9169	9184	9199	9213	9228	9242	9257	9272	9286	9301	1 3 4	6 7 9	10 12 13	
6-9	1-9315	9330	9344	9359	9373	9387	9402	9416	9430	9445	1 3 4	6 7 9	10 12 13	
7-0	1-9459	9473	9488	9502	9516	9530	9544	9559	9573	9587	1 3 4	6 7 9	10 11 13	
7-1	1-9601	9615	9629	9643	9657	9671	9685	9699	9713	9727	1 3 4	6 7 8	10 11 13	
7-2	1-9741	9755	9769	9782	9796	9810	9824	9838	9851	9865	1 3 4	6 7 8	10 11 12	
7-3	1-9879	9892	9906	9920	9933	9947	9961	9974	9988	9991	1 3 4	5 7 8	10 11 12	
7-4	2-0015	0028	0042	0055	0069	0082	0096	0109	0122	0136	1 3 4	5 7 8	9 11 12	
7-5	2-0149	0162	0176	0189	0202	0215	0229	0242	0255	0268	1 3 4	5 7 8	9 11 12	
7-6	2-0281	0295	0308	0321	0334	0347	0360	0375	0386	0399	1 3 4	5 6 8	9 10 12	
7-7	2-0412	0425	0438	0451	0464	0477	0490	0503	0516	0528	1 3 4	5 6 8	9 10 12	
7-8	2-0541	0554	0567	0580	0594	0605	0618	0631	0643	0656	1 3 4	5 6 8	9 10 11	
7-9	2-0669	0681	0694	0707	0719	0732	0744	0757	0769	0782	1 3 4	5 6 8	9 10 11	
8-0	2-0794	0807	0819	0832	0844	0857	0869	0882	0894	0906	1 3 4	5 6 7	9 10 11	
8-1	2-0919	0931	0943	0956	0968	0980	0992	1005	1017	1029	1 2 4	5 6 7	9 10 11	
8-2	2-1041	1054	1066	1078	1090	1102	1114	1126	1138	1150	1 2 4	5 6 7	9 10 11	
8-3	2-1163	1175	1187	1199	1211	1223	1235	1247	1258	1270	1 2 4	5 6 7	8 10 11	
8-4	2-1282	1294	1306	1318	1330	1342	1353	1365	1377	1389	1 2 4	5 6 7	8 9 11	
8-5	2-1401	1412	1424	1436	1448	1459	1471	1483	1494	1506	1 2 4	5 6 7	8 9 11	
8-6	2-1518	1529	1541	1552	1564	1576	1587	1599	1610	1622	1 2 3	5 6 7	8 9 10	
8-7	2-1633	1645	1656	1668	1679	1691	1702	1713	1725	1736	1 2 3	5 6 7	8 9 10	
8-8	2-1748	1759	1770	1782	1793	1804	1815	1827	1838	1849	1 2 3	5 6 7	8 9 10	
8-9	2-1861	1872	1883	1894	1905	1917	1928	1939	1950	1961	1 2 3	4 6 7	8 9 10	
9-0	2-1972	1983	1994	2006	2017	2028	2039	2050	2061	2072	1 2 3	4 6 7	8 9 10	
9-1	2-2083	2094	2105	2116	2127	2138	2148	2159	2170	2181	1 2 3	4 5 7	8 9 10	
9-2	2-2192	2203	2214	2225	2235	2246	2257	2268	2279	2289	1 2 3	4 5 6	8 9 10	
9-3	2-2300	2311	2322	2332	2343	2354	2364	2375	2386	2396	1 2 3	4 5 6	7 9 10	
9-4	2-2407	2418	2428	2439	2450	2460	2471	2481	2492	2502	1 2 3	4 5 6	7 8 10	
9-5	2-2513	2523	2534	2544	2555	2565	2576	2586	2597	2607	1 2 3	4 5 6	7 8 9	
9-6	2-2618	2628	2638	2649	2659	2670	2680	2690	2701	2711	1 2 3	4 5 6	7 8 9	
9-7	2-2721	2732	2742	2752	2762	2773	2783	2793	2803	2814	1 2 3	4 5 6	7 8 9	
9-8	2-2824	2834	2844	2854	2865	2875	2885	2895	2905	2915	1 2 3	4 5 6	7 8 9	
9-9	2-2925	2935	2946	2956	2966	2976	2986	2996	3006	3016	1 2 3	4 5 6	7 8 9	
10-0	2-3026	3036	3046	3056	3066	3076	3086	3096	3106	3116	1 2 3	4 5 6	7 8 9	

Hyperbolic Logarithms of 10^n and 10^{-n}

n	1	2	3	4	5	6	7	8	9
$\log_e 10^{+n}$	2-3026	4-6052	6-9078	9-2103	11-5129	13-8155	16-1181	18-4207	20-7233
$\log_e 10^{-n}$	3-6974	5-3948	7-0922	8-7897	10-4871	12-1845	14-8819	16-5793	18-2767

TABLE 8
 POSITIVE POWERS OF $e = 2.71828$
 (Values of e^x)

	0	1	2	3	4	5	6	7	8	9
0.0	1.0000	1.0101	1.0202	1.0305	1.0408	1.0513	1.0618	1.0725	1.0833	1.0942
0.1	1.1052	1.1163	1.1275	1.1388	1.1503	1.1618	1.1735	1.1853	1.1972	1.2092
0.2	1.2214	1.2337	1.2461	1.2586	1.2712	1.2840	1.2969	1.3100	1.3231	1.3364
0.3	1.3499	1.3634	1.3771	1.3910	1.4049	1.4191	1.4333	1.4477	1.4623	1.4770
0.4	1.4918	1.5068	1.5220	1.5373	1.5527	1.5683	1.5841	1.6000	1.6161	1.6323
0.5	1.6487	1.6653	1.6820	1.6989	1.7160	1.7333	1.7507	1.7683	1.7860	1.8040
0.6	1.8221	1.8404	1.8595	1.8776	1.8965	1.9155	1.9348	1.9542	1.9739	1.9937
0.7	2.0138	2.0340	2.0544	2.0751	2.0959	2.1170	2.1383	2.1598	2.1815	2.2034
0.8	2.2255	2.2479	2.2705	2.2933	2.3164	2.3396	2.3632	2.3869	2.4109	2.4351
0.9	2.4596	2.4843	2.5093	2.5345	2.5600	2.5857	2.6117	2.6379	2.6645	2.2912
1.0	2.7183	2.7456	2.7732	2.8011	2.8292	2.8577	2.8864	2.9154	2.9447	2.9743
1.1	3.0042	3.0344	3.0649	3.0957	3.1268	3.1582	3.1899	3.2220	3.2544	3.2871
1.2	3.3201	3.3535	3.3872	3.4212	3.4556	3.4903	3.5254	3.5609	3.5966	3.6328
1.3	3.6693	3.7062	3.7434	3.7810	3.8190	3.8574	3.8962	3.9354	3.9749	4.0149
1.4	4.0552	4.0960	4.1371	4.1787	4.2207	4.2631	4.3060	4.3492	4.3929	4.4371
1.5	4.4817	4.5267	4.5722	4.6182	4.6646	4.7115	4.7588	4.8066	4.8550	4.9037
1.6	4.9530	5.0028	5.0531	5.1039	5.1552	5.2070	5.2593	5.3122	5.3656	5.4195
1.7	5.4739	5.5290	5.5845	5.6407	5.6973	5.7546	5.8124	5.8709	5.9299	5.9895
1.8	6.0496	6.1104	6.1719	6.2339	6.2965	6.3598	6.4237	6.4883	6.5535	6.6194
1.9	6.6859	6.7531	6.8210	6.8895	6.9588	7.0287	7.0993	7.1707	7.2427	7.3155
2.0	7.3891	7.4633	7.5383	7.6141	7.6906	7.7679	7.8460	7.9248	8.0045	8.0849
2.1	8.1662	8.2482	8.3311	8.4149	8.4994	8.5849	8.6711	8.7583	8.8463	8.9352
2.2	9.0250	9.1157	9.2073	9.2999	9.3933	9.4877	9.5831	9.6794	9.7767	9.8749
2.3	9.9742	10.074	10.176	10.278	10.381	10.486	10.591	10.697	10.805	10.913
2.4	11.023	11.134	11.246	11.359	11.473	11.588	11.705	11.822	11.941	12.061
2.5	12.182	12.305	12.429	12.554	12.680	12.807	12.936	13.066	13.197	13.330
2.6	13.464	13.599	13.736	13.874	14.013	14.154	14.296	14.440	14.585	14.732
2.7	14.880	15.029	15.180	15.333	15.487	15.643	15.800	15.959	16.119	16.281
2.8	16.445	16.610	16.777	16.945	17.116	17.288	17.462	17.637	17.814	17.993
2.9	18.174	18.357	18.541	18.728	18.916	19.106	19.298	19.492	19.688	19.886
3.0	20.086	20.287	20.491	20.697	20.905	21.115	21.328	21.542	21.758	21.977
3.1	22.198	22.421	22.646	22.874	23.104	23.336	23.571	23.807	24.047	24.288
3.2	24.533	24.779	25.028	25.280	25.534	25.790	26.050	26.311	26.576	26.843
3.3	27.113	27.385	27.660	27.938	28.219	28.503	28.789	29.079	29.371	29.666
3.4	29.964	30.265	30.569	30.877	31.187	31.500	31.817	32.137	32.460	32.786
3.5	33.115	33.448	33.784	34.124	34.467	34.813	35.163	35.517	35.874	36.234
3.6	36.598	36.966	37.338	37.713	38.092	38.475	38.861	39.252	39.646	40.045
3.7	40.447	40.854	41.264	41.679	42.098	42.521	42.948	43.380	43.816	44.256
3.8	44.701	45.150	45.604	46.063	46.525	46.993	47.465	47.942	48.424	48.911
3.9	49.402	49.899	50.400	50.907	51.419	51.935	52.457	52.985	53.517	54.055
4.0	54.598	55.147	55.701	56.261	56.826	57.397	57.974	58.557	59.145	59.740
4.1	60.340	60.947	61.559	62.178	62.803	63.434	64.072	64.715	65.366	66.023
4.2	66.686	67.357	68.033	68.717	69.408	70.105	70.810	71.522	72.240	72.966
4.3	73.700	74.440	75.189	75.944	76.708	77.478	78.257	79.044	79.838	80.640
4.4	81.451	82.269	83.096	83.931	84.775	85.627	86.488	87.357	88.235	89.121
4.5	90.017	90.922	91.836	92.759	93.691	94.632	95.583	96.544	97.514	98.494
4.6	99.484	100.48	101.49	102.51	103.54	104.58	105.64	106.70	107.77	108.85
4.7	109.95	111.05	112.17	113.30	114.43	115.58	116.75	117.92	119.10	120.30
4.8	121.51	122.73	123.97	125.21	126.47	127.74	129.02	130.32	131.63	132.95
4.9	134.29	135.64	137.00	138.38	139.77	141.17	142.59	144.03	145.47	146.94

TABLE 8
 POSITIVE POWERS OF $e = 2.71828$
 (Values of e^x)

	0	1	2	3	4	5	6	7	8	9
5-0	148.41	149.90	151.41	152.93	154.47	156.02	157.59	159.17	160.77	162.39
5-1	164.02	165.67	167.34	169.02	170.72	172.43	174.16	175.91	177.68	179.47
5-2	181.27	183.09	184.93	186.79	188.67	190.57	192.48	194.42	196.37	198.34
5-3	200.34	202.35	204.38	206.44	208.51	210.61	212.72	214.86	217.02	219.20
5-4	221.41	223.63	225.88	228.15	230.44	232.76	235.10	237.46	239.85	242.26
5-5	244.69	247.15	249.64	252.14	254.68	257.24	259.82	262.43	265.07	267.74
5-6	270.43	273.14	275.89	278.66	281.46	284.29	287.15	290.03	292.95	295.89
5-7	298.87	301.87	304.90	307.97	311.06	314.19	317.35	320.54	323.76	327.01
5-8	330.30	333.62	336.97	340.36	343.78	347.23	350.72	354.25	357.81	361.41
5-9	365.04	368.71	372.41	376.15	379.93	383.75	387.61	391.51	395.44	399.41
6-0	403.43	407.48	411.58	415.72	419.89	424.11	428.38	432.58	437.03	441.42

$e^7 = 1096.6$	$e^{\frac{\pi}{4}} = 2.1933$	$e^{\frac{3\pi}{4}} = 111.32$
$e^8 = 2981.0$	$e^{\frac{\pi}{2}} = 4.8105$	$e^{2\pi} = 535.49$
$e^9 = 8103.1$	$e^{\frac{3\pi}{4}} = 10.557$	$e^{3\pi} = 12391.7$
$e^{10} = 22026.$	$e^{\pi} = 23.141$	$e^{4\pi} = 286752$

TABLE 9
 NEGATIVE POWERS OF $e = 2.71828$
 (Values of e^{-x})

	0	1	2	3	4	5	6	7	8	9
0.0	1.00000	99005	98020	97045	96079	95123	94176	93239	92312	91393
0.1	0.90484	89583	88692	87810	86936	86071	85214	84366	83527	82696
0.2	0.81873	81058	80252	79453	78663	77880	77105	76338	75578	74826
0.3	0.74082	73345	72615	71892	71177	70469	69768	69073	68386	67706
0.4	0.67032	66365	65705	65051	64404	63763	63128	62500	61878	61263
0.5	0.60653	60050	59452	58860	58275	57695	57121	56553	55990	55433
0.6	0.54881	54335	53794	53259	52729	52205	51685	51171	50662	50158
0.7	0.49659	49164	48675	48191	47711	47237	46767	46301	45841	45384
0.8	0.44933	44486	44043	43605	43171	42741	42316	41895	41478	41066
0.9	0.40657	40252	39852	39455	39063	38674	38289	37908	37531	37158
1.0	0.36788	36422	36059	35701	35345	34994	34646	34301	33960	33622
1.1	0.33287	32956	32628	32303	31982	31664	31349	31037	30728	30422
1.2	0.30119	29820	29523	29229	28938	28650	28365	28083	27804	27527
1.3	0.27253	26982	26714	26448	26185	25924	25666	25411	25158	24908
1.4	0.24680	24414	24171	23931	23693	23457	23224	22993	22764	22537
1.5	0.22313	22091	21871	21654	21438	21225	21014	20805	20598	20393
1.6	0.20190	19989	19790	19593	19398	19205	19014	18825	18637	18452
1.7	0.18268	18087	17907	17728	17552	17377	17204	17033	16864	16696
1.8	0.16530	16365	16203	16041	15882	15724	15567	15412	15259	15107
1.9	0.14957	14808	14661	14515	14370	14227	14086	13946	13807	13670
2.0	0.13534	13399	13266	13134	13003	12873	12745	12619	12493	12369
2.1	0.12246	12124	12003	11884	11765	11648	11533	11418	11304	11192
2.2	0.11080	10970	10861	10753	10646	10540	10435	10331	10228	10127
2.3	0.10026	09926	09827	09730	09633	09537	09442	09348	09255	09163
2.4	0.09072	08982	08892	08804	08716	08629	08543	08458	08374	08291
2.5	0.08208	08127	08046	07966	07887	07808	07730	07654	07577	07502
2.6	0.07427	07353	07280	07208	07136	07065	06995	06925	06856	06788
2.7	0.06721	06654	06587	06522	06457	06393	06329	06266	06204	06142
2.8	0.06081	06020	05961	05901	05843	05784	05727	05670	05613	05558
2.9	0.05502	05448	05393	05340	05287	05234	05182	05130	05079	05029
3.0	0.04979	04929	04880	04832	04783	04736	04689	04642	04596	04550
3.1	0.04505	04460	04416	04372	04328	04285	04243	04200	04159	04117
3.2	0.04076	04036	03996	03956	03916	03877	03839	03801	03763	03725
3.3	0.03688	03652	03615	03579	03544	03508	03474	03439	03405	03371
3.4	0.03337	03304	03271	03239	03206	03175	03143	03112	03081	03050
3.5	0.03020	02990	02960	02930	02901	02872	02844	02816	02788	02760
3.6	0.02732	02705	02678	02652	02625	02599	02573	02548	02522	02497
3.7	0.02472	02448	02423	02399	02375	02352	02328	02305	02282	02260
3.8	0.02237	02215	02193	02171	02149	02128	02107	02086	02065	02045
3.9	0.02024	02004	01984	01964	01945	01925	01906	01887	01869	01850
4.0	0.01832	01813	01795	01777	01760	01742	01725	01708	01691	01674
4.1	0.01657	01641	01624	01608	01592	01576	01561	01545	01530	01515
4.2	0.01500	01485	01470	01455	01441	01426	01412	01398	01384	01370
4.3	0.01357	01343	01330	01317	01304	01291	01278	01265	01253	01240
4.4	0.01228	01216	01203	01191	01180	01168	01156	01145	01133	01122
4.5	0.01111	01100	01089	01078	01067	01057	01046	01036	01025	01015
4.6	0.01005	00995	00985	00975	00966	00956	00947	00937	00928	00919
4.7	0.00910	00900	00892	00883	00874	00865	00857	00848	00840	00831
4.8	0.00823	00815	00807	00799	00791	00783	00775	00767	00760	00752
4.9	0.00745	00737	00730	00723	00715	00708	00701	00694	00687	00681

TABLE 9
NEGATIVE POWERS OF $e = 2.71828$
 (Values of e^{-x})

	0	1	2	3	4	5	6	7	8	9
5-0	0.00674	00667	00660	00654	00647	00641	00635	00628	00622	00616
5-1	0.00610	00604	00598	00592	00586	00580	00574	00568	00563	00557
5-2	0.00552	00546	00541	00535	00530	00525	00520	00514	00509	00504
5-3	0.00499	00494	00489	00484	00480	00475	00470	00465	00461	00456
5-4	0.00452	00447	00443	00438	00434	00430	00425	00421	00417	00413
5-5	0.00409	00405	00401	00397	00393	00389	00385	00381	00377	00374
5-6	0.00370	00366	00362	00359	00355	00352	00348	00345	00341	00338
5-7	0.00335	00331	00328	00325	00321	00318	00315	00312	00309	00306
5-8	0.00303	00300	00297	00294	00291	00288	00285	00282	00279	00277
5-9	0.00274	00271	00269	00266	00263	00261	00258	00255	00253	00250
6-0	0.00248	00245	00243	00241	00238	00236	00234	00231	00229	00227

$e^{-7} = 0.0009119$	$e^{-\frac{\pi}{4}} = 0.4559$	$e^{-\frac{3\pi}{2}} = 0.008983$
$e^{-8} = 0.0003355$	$e^{-\frac{\pi}{2}} = 0.20788$	$e^{-2\pi} = 0.001867$
$e^{-9} = 0.0001234$	$e^{-\frac{3\pi}{4}} = 0.09478$	$e^{-3\pi} = 0.000087$
$e^{-10} = 0.0000454$	$e^{-\pi} = 0.043214$	$e^{-4\pi} = 0.0000035$

TABLE 10
NATURAL HYPERBOLIC SINES

(Values of Sinh x)

	0	1	2	3	4	5	6	7	8	9
0.0	0.0000	0.0100	0.0200	0.0300	0.0400	0.0500	0.0600	0.0701	0.0801	0.0901
0.1	0.1002	0.1102	0.1203	0.1304	0.1405	0.1506	0.1607	0.1708	0.1810	0.1911
0.2	0.2013	0.2115	0.2218	0.2320	0.2423	0.2526	0.2629	0.2733	0.2837	0.2941
0.3	0.3045	0.3150	0.3255	0.3360	0.3466	0.3572	0.3678	0.3785	0.3892	0.4000
0.4	0.4108	0.4216	0.4325	0.4434	0.4543	0.4653	0.4764	0.4875	0.4986	0.5098
0.5	0.5211	0.5324	0.5438	0.5552	0.5666	0.5782	0.5897	0.6104	0.6131	0.6248
0.6	0.6367	0.6485	0.6605	0.6725	0.6846	0.6967	0.7090	0.7219	0.7336	0.7461
0.7	0.7586	0.7712	0.7838	0.7966	0.8094	0.8223	0.8353	0.8484	0.8615	0.8748
0.8	0.8881	0.9015	0.9150	0.9286	0.9423	0.9561	0.9700	0.9840	0.9981	1.0122
0.9	1.0265	1.0409	1.0554	1.0700	1.0847	1.0995	1.1144	1.1294	1.1446	1.1598
1.0	1.1752	1.1907	1.2063	1.2220	1.2379	1.2539	1.2700	1.2862	1.3025	1.3190
1.1	1.3356	1.3524	1.3693	1.3863	1.4035	1.4208	1.4382	1.4558	1.4735	1.4914
1.2	1.5095	1.5276	1.5460	1.5645	1.5831	1.6019	1.6209	1.6400	1.6593	1.6788
1.3	1.6984	1.7182	1.7381	1.7583	1.7786	1.7991	1.8198	1.8406	1.8617	1.8829
1.4	1.9043	1.9259	1.9477	1.9697	1.9919	2.0143	2.0369	2.0597	2.0827	2.1059
1.5	2.1293	2.1529	2.1768	2.2008	2.2251	2.2496	2.2743	2.2993	2.3245	2.3499
1.6	2.3756	2.4105	2.4276	2.4540	2.4806	2.5075	2.5346	2.5620	2.5896	2.6175
1.7	2.6456	2.6740	2.7027	2.7317	2.7609	2.7904	2.8202	2.8503	2.8806	2.9112
1.8	2.9422	2.9734	3.0049	3.0367	3.0689	3.1013	3.1340	3.1671	3.2005	3.2341
1.9	3.2682	3.3025	3.3372	3.3722	3.4075	3.4432	3.4792	3.5156	3.5523	3.5894
2.0	3.6269	3.6647	3.7028	3.7414	3.7803	3.8196	3.8593	3.8993	3.9398	3.9806
2.1	4.0219	4.0635	4.1056	4.1480	4.1909	4.2342	4.2779	4.3221	4.3666	4.4116
2.2	4.4571	4.5030	4.5494	4.5962	4.6434	4.6912	4.7394	4.7880	4.8372	4.8868
2.3	4.9370	4.9876	5.0387	5.0903	5.1425	5.1951	5.2483	5.3020	5.3562	5.4109
2.4	5.4662	5.5221	5.5785	5.6354	5.6929	5.7510	5.8097	5.8689	5.9288	5.9892
2.5	6.0502	6.1118	6.1741	6.2369	6.3004	6.3645	6.4293	6.4946	6.5607	6.6274
2.6	6.6947	6.7628	6.8315	6.9008	6.9709	7.0417	7.1132	7.1854	7.2583	7.3319
2.7	7.4063	7.4814	7.5572	7.6338	7.7112	7.7894	7.8683	7.9480	8.0285	8.1098
2.8	8.1919	8.2749	8.3586	8.4432	8.5287	8.6150	8.7021	8.7902	8.8791	8.9689
2.9	9.0596	9.1512	9.2437	9.3371	9.4315	9.5268	9.6231	9.7203	9.8185	9.9177
3.0	10.018	10.119	10.221	10.325	10.429	10.534	10.640	10.748	10.856	10.966
3.1	11.077	11.188	11.301	11.415	11.530	11.647	11.764	11.883	12.003	12.124
3.2	12.246	12.369	12.494	12.620	12.747	12.876	13.006	13.137	13.269	13.403
3.3	13.538	13.674	13.812	13.951	14.092	14.234	14.377	14.522	14.668	14.816
3.4	14.965	15.116	15.268	15.422	15.577	15.734	15.893	16.053	16.215	16.378
3.5	16.543	16.709	16.877	17.047	17.219	17.392	17.567	17.744	17.923	18.103
3.6	18.285	18.470	18.655	18.843	19.033	19.224	19.418	19.613	19.811	20.010
3.7	20.211	20.415	20.620	20.828	21.037	21.249	21.463	21.679	21.897	22.117
3.8	22.339	22.564	22.791	23.020	23.252	23.486	23.722	23.961	24.202	24.445
3.9	24.691	24.939	25.190	25.444	25.700	25.958	26.219	26.483	26.749	27.018
4.0	27.290	27.564	27.842	28.122	28.404	28.690	28.979	29.270	29.564	29.862
4.1	30.162	30.465	30.772	31.081	31.393	31.709	32.028	32.350	32.675	33.004
4.2	33.336	33.671	34.009	34.351	34.697	35.046	35.398	35.754	36.113	36.476
4.3	36.843	37.214	37.588	37.966	38.347	38.733	39.122	39.515	39.913	40.314
4.4	40.719	41.129	41.542	41.960	42.382	42.808	43.238	43.673	44.112	44.555
4.5	45.003	45.455	45.912	46.374	46.840	47.311	47.787	48.267	48.752	49.242
4.6	49.737	50.237	50.742	51.252	51.767	52.288	52.813	53.344	53.880	54.422
4.7	54.969	55.522	56.080	56.643	57.213	57.788	58.369	58.955	59.548	60.147
4.8	60.751	61.362	61.979	62.601	63.231	63.866	64.508	65.157	65.812	66.473
4.9	67.141	67.816	68.498	69.186	69.882	70.584	71.293	72.010	72.734	73.465

TABLE 10
NATURAL HYPERBOLIC SINES
 (Values of Sinh x)

	0	1	2	3	4	5	6	7	8	9
5.0	74.203	74.949	75.702	76.463	77.232	78.008	78.792	79.584	80.384	81.192
5.1	82.008	82.832	83.665	84.506	85.355	86.213	87.079	87.955	88.839	89.732
5.2	90.633	91.544	92.464	93.394	94.332	95.281	96.238	97.205	98.182	99.169
5.3	100.17	101.17	102.19	103.22	104.25	105.30	106.36	107.43	108.51	109.60
5.4	110.70	111.81	112.94	114.07	115.22	116.38	117.55	118.73	119.92	121.13
5.5	122.34	123.57	124.82	126.07	127.34	128.62	129.91	131.22	132.53	133.87
5.6	135.21	136.57	137.94	139.33	140.73	142.14	143.57	145.02	146.47	147.95
5.7	149.33	150.93	152.45	153.98	155.53	157.09	158.67	160.27	161.88	163.51
5.8	165.15	166.81	168.48	170.18	171.89	173.62	175.36	177.12	178.90	180.70
5.9	182.52	184.35	186.20	188.08	189.97	191.88	193.80	195.75	197.72	199.71
6.0	201.71	203.74	205.79	207.86	209.94	212.06	214.19	216.29	218.51	220.71

Note.—For values of x greater than 6, $\sinh x = \cosh x = \frac{1}{2}e^x$.

TABLE 11
NATURAL HYPERBOLIC COSINES
 (Values of Cosh x)

	0	1	2	3	4	5	6	7	8	9
0.0	1.0000	1.0001	1.0002	1.0005	1.0008	1.0013	1.0018	1.0025	1.0032	1.0041
0.1	1.0050	1.0061	1.0072	1.0085	1.0099	1.0113	1.0128	1.0145	1.0162	1.0181
0.2	1.0201	1.0221	1.0243	1.0266	1.0289	1.0314	1.0340	1.0367	1.0395	1.0423
0.3	1.0453	1.0484	1.0516	1.0549	1.0584	1.0619	1.0655	1.0692	1.0731	1.0770
0.4	1.0811	1.0852	1.0895	1.0939	1.0984	1.1030	1.1077	1.1125	1.1174	1.1223
0.5	1.1276	1.1329	1.1383	1.1438	1.1494	1.1551	1.1609	1.1669	1.1730	1.1792
0.6	1.1855	1.1919	1.1984	1.2051	1.2119	1.2188	1.2258	1.2330	1.2402	1.2476
0.7	1.2552	1.2628	1.2706	1.2785	1.2865	1.2947	1.3030	1.3114	1.3199	1.3286
0.8	1.3374	1.3464	1.3555	1.3647	1.3740	1.3835	1.3932	1.4029	1.4128	1.4229
0.9	1.4331	1.4434	1.4539	1.4645	1.4753	1.4862	1.4973	1.5085	1.5199	1.5314
1.0	1.5431	1.5549	1.5669	1.5790	1.5913	1.6038	1.6164	1.6292	1.6421	1.6552
1.1	1.6685	1.6820	1.6956	1.7093	1.7233	1.7374	1.7517	1.7662	1.7808	1.7957
1.2	1.8107	1.8258	1.8412	1.8568	1.8725	1.8884	1.9045	1.9208	1.9373	1.9540
1.3	1.9709	1.9880	2.0053	2.0228	2.0404	2.0583	2.0764	2.0947	2.1132	2.1320
1.4	2.1509	2.1700	2.1894	2.2090	2.2288	2.2488	2.2691	2.2896	2.3103	2.3312
1.5	2.3524	2.3738	2.3955	2.4174	2.4395	2.4619	2.4845	2.5073	2.5305	2.5538
1.6	2.5775	2.6013	2.6255	2.6499	2.6746	2.6995	2.7247	2.7502	2.7760	2.8020
1.7	2.8283	2.8549	2.8818	2.9090	2.9364	2.9642	2.9922	3.0206	3.0492	3.0781
1.8	3.1075	3.1371	3.1669	3.1972	3.2277	3.2585	3.2897	3.3212	3.3530	3.3852
1.9	3.4177	3.4506	3.4838	3.5173	3.5512	3.5855	3.6201	3.6551	3.6904	3.7261
2.0	3.7622	3.7987	3.8355	3.8727	3.9103	3.9483	3.9867	4.0255	4.0647	4.1043
2.1	4.1443	4.1847	4.2256	4.2669	4.3085	4.3507	4.3932	4.4362	4.4797	4.5236
2.2	4.5679	4.6128	4.6580	4.7037	4.7499	4.7966	4.8437	4.8914	4.9395	4.9881
2.3	5.0372	5.0868	5.1370	5.1876	5.2388	5.2905	5.3427	5.3954	5.4487	5.5028
2.4	5.5569	5.6119	5.6674	5.7235	5.7801	5.8373	5.8951	5.9535	6.0125	6.0721
2.5	6.1323	6.1931	6.2545	6.3166	6.3793	6.4426	6.5066	6.5712	6.6365	6.7024
2.6	6.7690	6.8363	6.9043	6.9729	7.0423	7.1123	7.1831	7.2546	7.3268	7.3998
2.7	7.4735	7.5479	7.6231	7.6991	7.7758	7.8533	7.9316	8.0106	8.0905	8.1712
2.8	8.2527	8.3351	8.4182	8.5022	8.5871	8.6728	8.7594	8.8469	8.9352	9.0244
2.9	9.1146	9.2056	9.2976	9.3905	9.4844	9.5791	9.6749	9.7716	9.8693	9.9680
3.0	10.068	10.168	10.270	10.373	10.477	10.581	10.687	10.794	10.902	11.011
3.1	11.122	11.233	11.345	11.459	11.574	11.689	11.807	11.925	12.044	12.165
3.2	12.287	12.410	12.534	12.660	12.786	12.915	13.044	13.175	13.307	13.440
3.3	13.575	13.711	13.848	13.987	14.127	14.269	14.412	14.556	14.702	14.850
3.4	14.999	15.149	15.301	15.455	15.610	15.766	15.924	16.084	16.245	16.408
3.5	16.573	16.739	16.907	17.077	17.248	17.421	17.596	17.772	17.951	18.131
3.6	18.313	18.497	18.682	18.870	19.059	19.250	19.444	19.639	19.836	20.035
3.7	20.236	20.439	20.644	20.852	21.061	21.272	21.486	21.702	21.919	22.140
3.8	22.362	22.586	22.813	23.042	23.274	23.507	23.743	23.982	24.222	24.466
3.9	24.711	24.960	25.210	25.463	25.719	25.977	26.238	26.502	26.768	27.037
4.0	27.308	27.583	27.860	28.139	28.422	28.707	28.996	29.287	29.581	29.878
4.1	30.178	30.482	30.788	31.097	31.409	31.725	32.044	32.365	32.691	33.019
4.2	33.351	33.686	34.024	34.366	34.711	35.060	35.412	35.768	36.127	36.490
4.3	36.857	37.227	37.601	37.979	38.360	38.746	39.135	39.528	39.925	40.326
4.4	40.732	41.141	41.554	41.972	42.393	42.819	43.250	43.684	44.123	44.566
4.5	45.014	45.466	45.923	46.385	46.851	47.321	47.797	48.277	48.762	49.252
4.6	49.747	50.247	50.752	51.262	51.777	52.297	52.823	53.354	53.890	54.431
4.7	54.978	55.531	56.089	56.652	57.222	57.796	58.377	58.964	59.556	60.155
4.8	60.759	61.370	61.987	62.609	63.239	63.874	64.516	65.164	65.819	66.481
4.9	67.149	67.823	68.505	69.193	69.889	70.591	71.300	72.017	72.741	73.472

TABLE 11
NATURAL HYPERBOLIC COSINES

(Values of Cosh x)

	0	1	2	3	4	5	6	7	8	9
5·0	74·210	74·956	75·710	76·470	77·238	78·014	78·798	79·590	80·390	81·198
5·1	82·014	82·838	83·671	84·512	85·361	86·219	87·085	87·960	88·844	89·737
5·2	90·639	91·550	92·470	93·399	94·338	95·286	96·243	97·211	98·188	99·174
5·3	100·17	101·18	102·19	103·22	104·26	105·31	106·36	107·43	108·51	109·60
5·4	110·71	111·82	112·94	114·08	115·22	116·38	117·55	118·73	119·93	121·13
5·5	122·35	123·58	124·82	126·07	127·34	128·62	129·91	131·22	132·54	133·87
5·6	135·22	136·57	137·95	139·33	140·73	142·15	143·58	145·02	146·48	147·95
5·7	149·44	150·94	152·45	153·99	155·53	157·10	158·68	160·27	161·88	163·51
5·8	165·15	166·81	168·49	170·18	171·89	173·62	175·36	177·13	178·91	180·70
5·9	182·52	184·35	186·21	188·08	189·97	191·88	193·81	195·75	197·72	199·71
6·0	201·72	203·74	205·79	207·86	209·95	212·06	214·19	216·29	218·52	220·71

Note.—For values greater than 6, $\cosh x = \sinh x = \frac{1}{2}e^x$.

TABLE 13
CIRCULAR FUNCTIONS OF RADIANs

Radian	Degree	Chord	Sine	Cosine	Tangent	Logarithm of		
						Sine	Cosine	Tangent
0.01	0.57	0.0100	0.0100	1.0000	0.0100	2.0000	0.0000	2.0000
0.02	1.15	0.0200	0.0200	0.9998	0.0200	2.3010	1.9999	2.3010
0.03	1.72	0.0300	0.0300	0.9996	0.0300	2.4771	1.9999	2.4771
0.04	2.29	0.0400	0.0400	0.9992	0.0400	2.6021	1.9997	2.6021
0.05	2.86	0.0500	0.0500	0.9987	0.0500	2.6990	1.9994	2.6990
0.06	3.44	0.0600	0.0600	0.9982	0.0600	2.7782	1.9992	2.7782
0.07	4.01	0.0700	0.0700	0.9976	0.0700	2.8451	1.9990	2.8451
0.08	4.58	0.0800	0.0799	0.9968	0.0801	2.9025	1.9986	2.9036
0.09	5.16	0.0900	0.0899	0.9959	0.0902	2.9538	1.9982	2.9552
0.10	5.73	0.1001	0.0998	0.9950	0.1003	2.9993	1.9978	1.0015
0.11	6.30	0.1099	0.1098	0.9940	0.1104	1.0405	1.9974	1.0431
0.12	6.88	0.1200	0.1197	0.9928	0.1206	1.0781	1.9969	1.0813
0.13	7.45	0.1300	0.1296	0.9916	0.1307	1.1127	1.9963	1.1164
0.14	8.02	0.1399	0.1395	0.9902	0.1409	1.1447	1.9957	1.1490
0.15	8.59	0.1499	0.1494	0.9888	0.1511	1.1745	1.9951	1.1794
0.16	9.17	0.1598	0.1593	0.9872	0.1614	1.2023	1.99 4	1.2078
0.17	9.74	0.1698	0.1692	0.9856	0.1717	1.2284	1.9937	1.2347
0.18	10.31	0.1798	0.1790	0.9838	0.1820	1.2529	1.9929	1.2600
0.19	10.89	0.1898	0.1889	0.9820	0.1923	1.2761	1.9921	1.2840
0.20	11.46	0.1997	0.1987	0.9801	0.2027	1.2981	1.9913	1.3069
0.21	12.03	0.2097	0.2085	0.9780	0.2131	1.3190	1.9904	1.3287
0.22	12.61	0.2198	0.2182	0.9759	0.2236	1.3389	1.9894	1.3495
0.23	13.18	0.2295	0.2280	0.9737	0.2341	1.3579	1.9884	1.3695
0.24	13.75	0.2400	0.2377	0.9713	0.2447	1.3760	1.9874	1.3887
0.25	14.32	0.2493	0.2474	0.9689	0.2553	1.3934	1.9863	1.4071
0.26	14.90	0.2600	0.2571	0.9664	0.2660	1.4101	1.9852	1.4249
0.27	15.47	0.2693	0.2667	0.9638	0.2768	1.4261	1.9840	1.4421
0.28	16.04	0.2798	0.2764	0.9611	0.2876	1.4415	1.9827	1.4587
0.29	16.62	0.2892	0.2860	0.9582	0.2984	1.4563	1.9815	1.4748
0.30	17.19	0.2989	0.2955	0.9553	0.3093	1.4706	1.9802	1.4904
0.31	17.76	0.3089	0.3051	0.9523	0.3203	1.4844	1.9788	1.5056
0.32	18.33	0.3196	0.3146	0.9492	0.3314	1.4977	1.9774	1.5203
0.33	18.91	0.3285	0.3240	0.9460	0.3425	1.5106	1.9759	1.5347
0.34	19.48	0.3396	0.3335	0.9428	0.3537	1.5231	1.9744	1.5487
0.35	20.05	0.3482	0.3429	0.9394	0.3650	1.5352	1.9728	1.5623
0.36	20.63	0.3596	0.3523	0.9359	0.3764	1.5469	1.9712	1.5757
0.37	21.20	0.3680	0.3616	0.9323	0.3879	1.5582	1.9696	1.5887
0.38	21.77	0.3795	0.3709	0.9287	0.3994	1.5693	1.9679	1.6014
0.39	22.35	0.3876	0.3802	0.9249	0.4111	1.5800	1.9661	1.6139
0.40	22.92	0.3973	0.3894	0.9211	0.4228	1.5904	1.9643	1.6261
0.41	23.49	0.4072	0.3986	0.9171	0.4346	1.6005	1.9624	1.6381
0.42	24.06	0.4168	0.4078	0.9131	0.4466	1.6104	1.9605	1.6499
0.43	24.64	0.4269	0.4169	0.9090	0.4586	1.6200	1.9585	1.6615
0.44	25.21	0.4366	0.4259	0.9048	0.4708	1.6293	1.9565	1.6728
0.45	25.78	0.4462	0.4350	0.9004	0.4831	1.6385	1.9545	1.6840
0.46	26.36	0.4561	0.4439	0.8961	0.4954	1.6473	1.9523	1.6950
0.47	26.93	0.4657	0.4529	0.8916	0.5080	1.6560	1.9502	1.7058
0.48	27.50	0.4754	0.4618	0.8870	0.5206	1.6644	1.9479	1.7165
0.49	28.07	0.4850	0.4706	0.8823	0.5334	1.6727	1.9456	1.7270

TABLE 13
CIRCULAR FUNCTIONS OF RADIANs

Radian	Degree	Chord	Sine	Cosine	Tangent	Logarithms of		
						Sine	Cosine	Tangent
0.50	28.65	0.4948	0.4794	0.8776	0.5463	I.6807	I.9433	I.7374
0.51	29.22	0.5045	0.4882	0.8727	0.5594	I.6886	I.9409	I.7477
0.52	29.79	0.5142	0.4969	0.8678	0.5726	I.6963	I.9384	I.7578
0.53	30.37	0.5240	0.5055	0.8628	0.5859	I.7037	I.9359	I.7678
0.54	30.94	0.5336	0.5141	0.8577	0.5994	I.7111	I.9333	I.7777
0.55	31.51	0.5430	0.5227	0.8525	0.6131	I.7182	I.9307	I.7875
0.56	32.09	0.5528	0.5312	0.8473	0.6269	I.7252	I.9280	I.7972
0.57	32.66	0.5625	0.5396	0.8419	0.6410	I.7321	I.9253	I.8068
0.58	33.23	0.5719	0.5480	0.8365	0.6552	I.7388	I.9224	I.8164
0.59	33.80	0.5815	0.5564	0.8309	0.6696	I.7454	I.9196	I.8258
0.60	34.38	0.5911	0.5646	0.8253	0.6841	I.7518	I.9166	I.8351
0.61	34.95	0.6008	0.5729	0.8196	0.6989	I.7581	I.9136	I.8444
0.62	35.52	0.6103	0.5810	0.8139	0.7139	I.7642	I.9106	I.8536
0.63	36.10	0.6197	0.5891	0.8080	0.7291	I.7702	I.9074	I.8628
0.64	36.67	0.6291	0.5972	0.8021	0.7445	I.7761	I.9042	I.8719
0.65	37.24	0.6385	0.6052	0.7961	0.7602	I.7819	I.9010	I.8809
0.66	37.82	0.6483	0.6131	0.7900	0.7761	I.7875	I.8976	I.8899
0.67	38.39	0.6577	0.6210	0.7838	0.7923	I.7931	I.8942	I.8989
0.68	38.96	0.6670	0.6288	0.7776	0.8087	I.7985	I.8907	I.9078
0.69	39.53	0.6764	0.6365	0.7712	0.8253	I.8038	I.8872	I.9166
0.70	40.11	0.6858	0.6442	0.7648	0.8423	I.8090	I.8836	I.9255
0.71	40.68	0.6952	0.6518	0.7584	0.8595	I.8141	I.8799	I.9343
0.72	41.25	0.7045	0.6594	0.7518	0.8771	I.8191	I.8761	I.9430
0.73	41.83	0.7140	0.6669	0.7452	0.8949	I.8240	I.8723	I.9518
0.74	42.40	0.7234	0.6743	0.7385	0.9131	I.8288	I.8683	I.9605
0.75	42.97	0.7303	0.6816	0.7317	0.9316	I.8336	I.8643	I.9692
0.76	43.54	0.7418	0.6889	0.7248	0.9505	I.8382	I.8602	I.9779
0.77	44.12	0.7511	0.6961	0.7179	0.9697	I.8427	I.8561	I.9866
0.78	44.69	0.7605	0.7033	0.7109	0.9893	I.8471	I.8518	I.9953
0.79	45.26	0.7696	0.7104	0.7038	1.0092	I.8515	I.8475	0.0040
0.80	45.84	0.7784	0.7174	0.6967	1.0296	I.8557	I.8430	0.0127
0.81	46.41	0.7881	0.7243	0.6895	1.0505	I.8599	I.8385	0.0214
0.82	46.98	0.7972	0.7311	0.6822	1.0717	I.8640	I.8339	0.0301
0.83	47.56	0.8066	0.7379	0.6749	1.0934	I.8680	I.8292	0.0388
0.84	48.13	0.8156	0.7446	0.6675	1.1156	I.8719	I.8244	0.0475
0.85	48.70	0.8246	0.7513	0.6600	1.1383	I.8758	I.8195	0.0563
0.86	49.27	0.8336	0.7578	0.6524	1.1616	I.8796	I.8145	0.0650
0.87	49.85	0.8423	0.7643	0.6448	1.1853	I.8833	I.8094	0.0738
0.88	50.42	0.8519	0.7707	0.6372	1.2097	I.8869	I.8042	0.0827
0.89	50.99	0.8609	0.7771	0.6294	1.2346	I.8905	I.7989	0.0915
0.90	51.57	0.8699	0.7833	0.6216	1.2602	I.8939	I.7935	0.1004
0.91	52.14	0.8790	0.7895	0.6137	1.2864	I.8974	I.7880	0.1094
0.92	52.71	0.8880	0.7956	0.6058	1.3133	I.9007	I.7823	0.1184
0.93	53.29	0.8970	0.8016	0.5978	1.3409	I.9040	I.7766	0.1274
0.94	53.86	0.9059	0.8076	0.5898	1.3692	I.9072	I.7707	0.1365
0.95	54.43	0.9147	0.8134	0.5817	1.3984	I.9103	I.7647	0.1456
0.96	55.00	0.9235	0.8192	0.5735	1.4284	I.9134	I.7585	0.1548
0.97	55.58	0.9324	0.8249	0.5653	1.4592	I.9164	I.7523	0.1641
0.98	56.15	0.9413	0.8305	0.5570	1.4910	I.9193	I.7459	0.1735
0.99	56.72	0.9501	0.8360	0.5487	1.5237	I.9222	I.7393	0.1829

TABLE 13
CIRCULAR FUNCTIONS OF RADIANs

Radian	Degree	Chord	Sine	Cosine	Tangent	Logarithms of		
						Sine	Cosine	Tangent
1·00	57·30	0·9589	0·8415	0·5403	1·5574	I·9250	I·7326	0·1924
1·01	57·87	0·9678	0·8468	0·5319	1·5922	I·9278	I·7258	0·2020
1·02	58·44	0·9764	0·8521	0·5234	1·6281	I·9305	I·7188	0·2117
1·03	59·01	0·9850	0·8573	0·5148	1·6652	I·9331	I·7117	0·2215
1·04	59·59	0·9939	0·8624	0·5062	1·7036	I·9357	I·7043	0·2314
1·05	60·16	1·0003	0·8674	0·4976	1·7433	I·9382	I·6969	0·2414
1·06	60·73	1·0112	0·8724	0·4889	1·7844	I·9407	I·6892	0·2515
1·07	61·31	1·0198	0·8772	0·4801	1·8270	I·9431	I·6814	0·2617
1·08	61·88	1·0283	0·8820	0·4713	1·8712	I·9454	I·6733	0·2721
1·09	62·45	1·0369	0·8866	0·4625	1·9171	I·9477	I·6651	0·2826
1·10	63·03	1·0455	0·8912	0·4536	1·9648	I·9500	I·6567	0·2933
1·11	63·60	1·0540	0·8957	0·4447	2·014	I·9522	I·6480	0·3041
1·12	64·17	1·0621	0·9001	0·4357	2·066	I·9543	I·6392	0·3151
1·13	64·74	1·0709	0·9044	0·4267	2·120	I·9564	I·6301	0·3263
1·14	65·32	1·0794	0·9086	0·4176	2·176	I·9584	I·6208	0·3376
1·15	65·89	1·0866	0·9128	0·4085	2·234	I·9604	I·6112	0·3492
1·16	66·46	1·0961	0·9168	0·3993	2·296	I·9623	I·6013	0·3609
1·17	67·04	1·1045	0·9208	0·3902	2·360	I·9641	I·5912	0·3729
1·18	67·61	1·1129	0·9246	0·3809	2·427	I·9660	I·5808	0·3851
1·19	68·18	1·1211	0·9284	0·3717	2·498	I·9677	I·5701	0·3976
1·20	68·75	1·1292	0·9320	0·3624	2·572	I·9694	I·5591	0·4103
1·21	69·33	1·1376	0·9356	0·3530	2·650	I·9711	I·5478	0·4233
1·22	69·90	1·1458	0·9391	0·3436	2·733	I·9727	I·5361	0·4366
1·23	70·47	1·1539	0·9425	0·3342	2·820	I·9743	I·5241	0·4502
1·24	71·05	1·1621	0·9458	0·3248	2·912	I·9758	I·5116	0·4642
1·25	71·62	1·1702	0·9490	0·3153	3·010	I·9773	I·4988	0·4785
1·26	72·19	1·1783	0·9521	0·3058	3·113	I·9787	I·4855	0·4932
1·27	72·77	1·1865	0·9551	0·2963	3·224	I·9800	I·4717	0·5083
1·28	73·34	1·1945	0·9580	0·2867	3·341	I·9814	I·4575	0·5239
1·29	73·91	1·2023	0·9608	0·2771	3·467	I·9826	I·4427	0·5400
1·30	74·48	1·2104	0·9636	0·2675	3·602	I·9839	I·4273	0·5566
1·31	75·06	1·2183	0·9662	0·2579	3·747	I·9851	I·4114	0·5737
1·32	75·63	1·2259	0·9687	0·2482	3·903	I·9862	I·3948	0·5914
1·33	76·20	1·2341	0·9711	0·2385	4·072	I·9873	I·3774	0·6098
1·34	76·78	1·2421	0·9735	0·2288	4·256	I·9883	I·3594	0·6290
1·35	77·35	1·2498	0·9757	0·2190	4·455	I·9893	I·3405	0·6489
1·36	77·92	1·2575	0·9779	0·2092	4·673	I·9903	I·3208	0·6696
1·37	78·50	1·2654	0·9799	0·1994	4·913	I·9912	I·2998	0·6914
1·38	79·07	1·2731	0·9819	0·1896	5·177	I·9920	I·2779	0·7141
1·39	79·64	1·2803	0·9837	0·1798	5·471	I·9929	I·2548	0·7380
1·40	80·21	1·2882	0·9854	0·1700	5·798	I·9936	I·2304	0·7633
1·41	80·79	1·2962	0·9871	0·1601	6·165	I·9944	I·2044	0·7900
1·42	81·36	1·3037	0·9887	0·1502	6·581	I·9950	I·1767	0·8183
1·43	81·93	1·3112	0·9901	0·1403	7·055	I·9957	I·1472	0·8485
1·44	82·51	1·3189	0·9915	0·1304	7·602	I·9963	I·1154	0·8809
1·45	83·08	1·3263	0·9927	0·1205	8·238	I·9968	I·0810	0·9154
1·46	83·65	1·3338	0·9939	0·1106	8·989	I·9973	I·0436	0·9537
1·47	84·22	1·3412	0·9949	0·1006	9·887	I·9978	I·0027	0·9951
1·48	84·80	1·3487	0·9959	0·0907	10·984	I·9982	I·9575	1·0407
1·49	85·37	1·3559	0·9967	0·0807	12·350	I·9986	I·9069	1·0917

TABLE 13
CIRCULAR FUNCTIONS OF RADIAN

Radian	Degree	Chord	Sine	Cosine	Tangent	Logarithm of		
						Sine	Cosine	Tangent
1.50	85.94	1.3633	0.9975	0.0707	14.101	I.9989	Z.8496	1.1493
1.51	86.52	1.3707	0.9982	0.0608	16.428	I.9992	Z.7836	1.2156
1.52	87.09	1.3778	0.9987	0.0508	19.670	I.9994	Z.7056	1.2938
1.53	87.66	1.3851	0.9992	0.0408	24.498	I.9996	Z.6105	1.3891
1.54	88.24	1.3924	0.9995	0.0308	32.461	I.9998	Z.4884	1.5114
1.55	88.81	1.3984	0.9998	0.0208	48.078	I.9999	Z.3180	1.6820
1.56	89.38	1.4066	0.9999	0.0108	92.620	0.0000	Z.0333	1.9667
1.57	89.95	1.4136	1.0000	0.0008	1255.766	0.0000	Z.9011	3.0989
2	114.59	1.6829	0.9093	-0.4161	-2.1850	I.9587	I.6193	0.3395
3	171.89	1.9962	0.1411	-0.9900	-0.1425	I.1496	I.9956	I.1540
4	229.18	1.8186	-0.7568	-0.6536	1.1578	I.9790	I.8153	0.0636
5	286.48	1.1969	-0.9589	0.2837	-3.3806	I.9818	I.4528	0.5290
6	343.77	0.2822	-0.2794	0.9602	-0.2910	I.4462	I.9824	I.4639
7	401.07	0.7016	0.6570	0.7579	0.8715	I.8175	I.8773	I.9402
8	458.37	1.3073	0.9894	-0.1455	-6.7994	I.9954	I.1629	0.8325
9	515.66	0.4216	0.4121	-0.9111	-0.4523	I.6150	I.9596	I.6554
10	572.96	1.9178	-0.5440	-0.8391	0.6484	I.7356	I.9238	1.8118
$\pi/2$	90.00	1.4142	1.0000	0.0000	$+\infty$	0.0000	$-\infty$	$+\infty$
$2\pi/3$	120	1.7321	0.8660	-0.5000	-1.7321	I.9375	I.6990	0.2386
$3\pi/4$	135	1.8478	0.7071	-0.7071	-1.0000	I.8495	I.8495	0.0000
π	180	2.0000	0.0000	-1.0000	0.0000	$-\infty$	0.0000	$-\infty$
$3\pi/2$	270	1.4142	-1.0000	0.0000	$-\infty$	0.0000	$-\infty$	$+\infty$
2π	360	0.0000	0.0000	1.0000	0.0000	$-\infty$	0.0000	$-\infty$

TABLE 14
DEGREES TO RADIANs

Degrees	0'	6'	12'	18'	24'	30'	36'	42'	48'	54'	Add:				
	0-0°	0-1°	0-2°	0-3°	0-4°	0-5°	0-6°	0-7°	0-8°	0-9°	1'	2'	3'	4'	5'
0	0.0000	0017	0035	0052	0070	0087	0105	0122	0140	0157	3	6	9	12	15
1	0.0175	0192	0209	0227	0244	0262	0279	0297	0314	0332	3	6	9	12	15
2	0.0349	0367	0384	0401	0419	0436	0454	0471	0489	0506	3	6	9	12	15
3	0.0524	0541	0559	0576	0593	0611	0628	0646	0663	0681	3	6	9	12	15
4	0.0698	0716	0733	0750	0768	0785	0803	0820	0838	0855	3	6	9	12	15
5	0.0873	0890	0908	0925	0942	0960	0977	0995	1012	1030	3	6	9	12	15
6	0.1047	1065	1082	1100	1117	1134	1152	1169	1187	1204	3	6	9	12	15
7	0.1222	1239	1257	1274	1292	1309	1326	1344	1361	1379	3	6	9	12	15
8	0.1396	1414	1431	1449	1466	1484	1501	1518	1536	1553	3	6	9	12	15
9	0.1571	1588	1606	1623	1641	1658	1676	1693	1710	1728	3	6	9	12	15
10	0.1745	1763	1780	1798	1815	1833	1850	1868	1885	1902	3	6	9	12	15
11	0.1920	1937	1955	1972	1990	2007	2025	2042	2060	2077	3	6	9	12	15
12	0.2094	2112	2129	2147	2164	2182	2199	2217	2234	2251	3	6	9	12	15
13	0.2269	2286	2304	2321	2339	2356	2374	2391	2409	2426	3	6	9	12	15
14	0.2443	2461	2478	2496	2513	2531	2548	2566	2583	2601	3	6	9	12	15
15	0.2618	2635	2653	2670	2688	2705	2723	2740	2758	2775	3	6	9	12	15
16	0.2793	2810	2827	2845	2862	2880	2897	2915	2932	2950	3	6	9	12	15
17	0.2967	2985	3002	3019	3037	3054	3072	3089	3107	3124	3	6	9	12	15
18	0.3142	3159	3176	3194	3211	3229	3246	3264	3281	3299	3	6	9	12	15
19	0.3316	3334	3351	3368	3386	3403	3421	3438	3456	3473	3	6	9	12	15
20	0.3491	3508	3526	3543	3560	3578	3595	3613	3630	3648	3	6	9	12	15
21	0.3665	3783	3700	3718	3735	3752	3770	3787	3805	3822	3	6	9	12	15
22	0.3840	3857	3875	3892	3910	3927	3944	3962	3979	3997	3	6	9	12	15
23	0.4014	4032	4049	4067	4084	4102	4119	4136	4154	4171	3	6	9	12	15
24	0.4189	4206	4224	4241	4259	4276	4294	4311	4328	4346	3	6	9	12	15
25	0.4363	4381	4398	4416	4433	4451	4468	4485	4503	4520	3	6	9	12	15
26	0.4538	4555	4573	4590	4608	4625	4643	4660	4677	4695	3	6	9	12	15
27	0.4712	4730	4747	4765	4782	4800	4817	4835	4852	4869	3	6	9	12	15
28	0.4887	4904	4922	4939	4957	4974	4992	5009	5027	5044	3	6	9	12	15
29	0.5061	5079	5096	5114	5131	5149	5166	5184	5201	5219	3	6	9	12	15
30	0.5236	5253	5271	5288	5306	5323	5341	5358	5376	5393	3	6	9	12	15
31	0.5411	5428	5445	5463	5480	5498	5515	5533	5550	5568	3	6	9	12	15
32	0.5585	5603	5620	5637	5655	5672	5690	5707	5725	5742	3	6	9	12	15
33	0.5760	5777	5794	5812	5829	5847	5864	5882	5899	5917	3	6	9	12	15
34	0.5934	5952	5969	5986	6004	6021	6039	6056	6074	6091	3	6	9	12	15
35	0.6109	6126	6144	6161	6178	6196	6213	6231	6248	6266	3	6	9	12	15
36	0.6283	6301	6318	6336	6353	6370	6388	6405	6423	6440	3	6	9	12	15
37	0.6458	6475	6493	6510	6528	6545	6562	6580	6597	6615	3	6	9	12	15
38	0.6632	6650	6667	6685	6702	6720	6737	6754	6772	6789	3	6	9	12	15
39	0.6807	6824	6842	6859	6877	6894	6912	6929	6946	6964	3	6	9	12	15
40	0.6981	6999	7016	7034	7051	7069	7086	7103	7121	7138	3	6	9	12	15
41	0.7156	7173	7191	7208	7226	7243	7261	7278	7295	7313	3	6	9	12	15
42	0.7330	7348	7365	7383	7400	7418	7435	7453	7470	7487	3	6	9	12	15
43	0.7505	7522	7540	7557	7575	7592	7610	7627	7645	7662	3	6	9	12	15
44	0.7679	7697	7714	7732	7749	7767	7784	7802	7819	7837	3	6	9	12	15
45	0.7854	7871	7889	7906	7924	7941	7959	7976	7994	8011	3	6	9	12	15

Degrees	Radians	Degrees	Radians
180	$\pi = 3.141593$	1080	$6\pi = 18.849556$
360	$2\pi = 6.283185$	1260	$7\pi = 21.991149$
540	$3\pi = 9.424778$	1440	$8\pi = 25.132741$
720	$4\pi = 12.566371$	1620	$9\pi = 28.274334$
900	$5\pi = 15.707963$	1800	$10\pi = 31.415927$

TABLE 14
DEGREES TO RADIANs

Degrees	0	6'	12'	18'	24'	30'	36'	42'	48'	54'	Add :				
	0-0°	0-1°	0-2°	0-3°	0-4°	0-5°	0-6°	0-7°	0-8°	0-9°	1'	2'	3'	4'	5'
45	0.7854	7871	7889	7906	7924	7941	7959	7976	7994	8011	3	6	9	12	15
46	0.8029	8046	8063	8081	8098	8116	8133	8151	8168	8186	3	6	9	12	15
47	0.8203	8221	8238	8255	8273	8290	8308	8325	8343	8360	3	6	9	12	15
48	0.8378	8395	8412	8430	8447	8465	8482	8500	8517	8535	3	6	9	12	15
49	0.8552	8570	8587	8604	8622	8639	8657	8674	8692	8709	3	6	9	12	15
50	0.8727	8744	8762	8779	8796	8814	8831	8849	8866	8884	3	6	9	12	15
51	0.8901	8919	8936	8954	8971	8988	9006	9023	9041	9058	3	6	9	12	15
52	0.9076	9093	9111	9128	9146	9163	9180	9198	9215	9233	3	6	9	12	15
53	0.9250	9268	9285	9303	9320	9338	9355	9372	9390	9407	3	6	9	12	15
54	0.9425	9442	9460	9477	9495	9512	9529	9547	9564	9582	3	6	9	12	15
55	0.9599	9617	9634	9652	9669	9687	9704	9721	9739	9756	3	6	9	12	15
56	0.9774	9791	9809	9826	9844	9861	9879	9896	9913	9931	3	6	9	12	15
57	0.9948	9966	9983	0001	0018	0036	0053	0071	0088	0105	3	6	9	12	15
58	1-0123	0140	0158	0175	0193	0210	0228	0245	0263	0280	3	6	9	12	15
59	1-0297	0315	0332	0350	0367	0385	0402	0420	0437	0455	3	6	9	12	15
60	1-0472	0489	0507	0524	0542	0559	0577	0594	0612	0629	3	6	9	12	15
61	1-0647	0664	0681	0699	0716	0734	0751	0769	0786	0804	3	6	9	12	15
62	1-0821	0838	0856	0873	0891	0908	0926	0943	0961	0978	3	6	9	12	15
63	1-0996	1013	1030	1048	1065	1083	1100	1118	1135	1153	3	6	9	12	15
64	1-1170	1188	1205	1222	1240	1257	1275	1292	1310	1327	3	6	9	12	15
65	1-1345	1362	1380	1397	1414	1432	1449	1467	1484	1502	3	6	9	12	15
66	1-1519	1537	1554	1572	1589	1606	1624	1641	1659	1676	3	6	9	12	15
67	1-1694	1711	1729	1746	1764	1781	1798	1816	1833	1851	3	6	9	12	15
68	1-1868	1886	1903	1921	1938	1956	1973	1990	2008	2025	3	6	9	12	15
69	1-2043	2060	2078	2095	2113	2130	2147	2165	2182	2200	3	6	9	12	15
70	1-2217	2235	2252	2270	2287	2305	2322	2339	2357	2374	3	6	9	12	15
71	1-2392	2409	2427	2444	2462	2479	2497	2514	2531	2549	3	6	9	12	15
72	1-2566	2584	2601	2619	2636	2654	2671	2689	2706	2723	3	6	9	12	15
73	1-2741	2758	2776	2793	2811	2828	2846	2863	2881	2898	3	6	9	12	15
74	1-2915	2933	2950	2968	2985	3003	3020	3038	3055	3073	3	6	9	12	15
75	1-3090	3107	3125	3142	3160	3177	3195	3212	3230	3247	3	6	9	12	15
76	1-3265	3282	3299	3317	3334	3352	3369	3387	3404	3422	3	6	9	12	15
77	1-3439	3456	3474	3491	3509	3526	3544	3561	3579	3596	3	6	9	12	15
78	1-3614	3631	3648	3666	3683	3701	3718	3736	3753	3771	3	6	9	12	15
79	1-3788	3806	3823	3840	3858	3875	3893	3910	3928	3945	3	6	9	12	15
80	1-3963	3980	3998	4015	4032	4050	4067	4085	4102	4120	3	6	9	12	15
81	1-4137	4155	4172	4190	4207	4224	4242	4259	4277	4294	3	6	9	12	15
82	1-4312	4329	4347	4364	4382	4399	4416	4434	4451	4469	3	6	9	12	15
83	1-4486	4504	4521	4539	4556	4573	4591	4608	4626	4643	3	6	9	12	15
84	1-4661	4678	4696	4713	4731	4748	4765	4783	4800	4818	3	6	9	12	15
85	1-4835	4853	4870	4888	4905	4923	4940	4957	4975	4992	3	6	9	12	15
86	1-5010	5027	5045	5062	5080	5097	5115	5132	5149	5167	3	6	9	12	15
87	1-5184	5202	5219	5237	5254	5272	5289	5307	5324	5341	3	6	9	12	15
88	1-5359	5376	5394	5411	5429	5446	5464	5481	5499	5516	3	6	9	12	15
89	1-5533	5551	5568	5586	5603	5621	5638	5656	5673	5691	3	6	9	12	15
90	1-5708	5726	5743	5761	5778	5796	5813	5831	5848	5865	3	6	9	12	15

Degrees	Radians	Degrees	Radians
1980	11π=34.557519	2880	16π=50.265482
2160	12π=37.699112	3060	17π=53.407075
2340	13π=40.840704	3240	18π=56.548668
2520	14π=43.982297	3420	19π=59.690260
2700	15π=47.123890	3600	20π=62.831853

TABLE 15
NATURAL SINES

Radian.	Degree.	0°	6°	12°	18°	24°	30°	36°	42°	48°	54°	Add :				
		0-0°	0-1°	0-2°	0-3°	0-4°	0-5°	0-6°	0-7°	0-8°	0-9°	1'	2'	3'	4'	5'
0-0000	0	0-0000	0017	0035	0052	0070	0087	0105	0122	0140	0157	3	6	9	12	15
0-0175	1	0-0175	0192	0209	0227	0244	0262	0279	0297	0314	0332	3	6	9	12	15
0-0349	2	0-0349	0366	0384	0401	0419	0436	0454	0471	0488	0506	3	6	9	12	15
0-0524	3	0-0523	0541	0558	0576	0593	0610	0628	0645	0663	0680	3	6	9	12	15
0-0698	4	0-0698	0715	0732	0750	0767	0785	0802	0819	0837	0854	3	6	9	12	14
0-0873	5	0-0872	0889	0906	0924	0941	0958	0976	0993	1011	1028	3	6	9	12	14
0-1047	6	0-1045	1063	1080	1097	1115	1132	1149	1167	1184	1201	3	6	9	12	14
0-1222	7	0-1219	1236	1253	1271	1288	1305	1323	1340	1357	1374	3	6	9	12	14
0-1396	8	0-1392	1409	1426	1444	1461	1478	1495	1513	1530	1547	3	6	9	12	14
0-1571	9	0-1564	1582	1599	1616	1633	1650	1668	1685	1702	1719	3	6	9	12	14
0-1745	10	0-1736	1754	1771	1788	1805	1822	1840	1857	1874	1891	3	6	9	11	14
0-1920	11	0-1908	1925	1942	1959	1977	1994	2011	2028	2045	2062	3	6	9	11	14
0-2094	12	0-2079	2096	2113	2130	2147	2164	2181	2198	2215	2233	3	6	9	11	14
0-2269	13	0-2250	2267	2284	2300	2317	2334	2351	2368	2385	2402	3	6	8	11	14
0-2443	14	0-2419	2436	2453	2470	2487	2504	2521	2538	2554	2571	3	6	8	11	14
0-2618	15	0-2588	2605	2622	2639	2656	2672	2689	2706	2723	2740	3	6	8	11	14
0-2793	16	0-2756	2773	2790	2807	2823	2840	2857	2874	2890	2907	3	6	8	11	14
0-2967	17	0-2924	2940	2957	2974	2990	3007	3024	3040	3057	3074	3	6	8	11	14
0-3142	18	0-3090	3107	3123	3140	3156	3173	3190	3206	3223	3239	3	6	8	11	14
0-3316	19	0-3256	3272	3289	3305	3322	3338	3355	3371	3387	3404	3	5	8	11	14
0-3491	20	0-3420	3437	3453	3469	3486	3502	3518	3535	3551	3567	3	5	8	11	14
0-3665	21	0-3584	3600	3616	3633	3649	3665	3681	3697	3714	3730	3	5	8	11	14
0-3840	22	0-3748	3762	3778	3795	3811	3827	3843	3859	3875	3891	3	5	8	11	14
0-4014	23	0-3907	3923	3939	3955	3971	3987	4003	4019	4035	4051	3	5	8	11	14
0-4189	24	0-4067	4083	4099	4115	4131	4147	4163	4179	4195	4210	3	5	8	11	13
0-4363	25	0-4226	4242	4258	4274	4289	4305	4321	4337	4352	4368	3	5	8	11	13
0-4538	26	0-4384	4399	4415	4431	4446	4462	4478	4493	4509	4524	3	5	8	10	13
0-4712	27	0-4540	4555	4571	4586	4602	4617	4633	4648	4664	4679	3	5	8	10	13
0-4887	28	0-4695	4710	4726	4741	4756	4772	4787	4802	4818	4833	3	5	8	10	13
0-5061	29	0-4848	4863	4879	4894	4909	4924	4939	4955	4970	4985	3	5	8	10	13
0-5236	30	0-5000	5015	5030	5045	5060	5075	5090	5105	5120	5135	3	5	8	10	13
0-5411	31	0-5150	5165	5180	5195	5210	5225	5240	5255	5270	5284	2	5	7	10	12
0-5585	32	0-5299	5314	5329	5344	5358	5373	5388	5402	5417	5432	2	5	7	10	12
0-5760	33	0-5446	5461	5476	5490	5505	5519	5534	5548	5563	5577	2	5	7	10	12
0-5934	34	0-5592	5606	5621	5635	5650	5664	5678	5693	5707	5721	2	5	7	10	12
0-6109	35	0-5736	5750	5764	5779	5793	5807	5821	5835	5850	5864	2	5	7	9	12
0-6283	36	0-5878	5892	5906	5920	5934	5948	5962	5976	5990	6004	2	5	7	9	12
0-6458	37	0-6018	6032	6046	6060	6074	6088	6101	6115	6129	6143	2	5	7	9	12
0-6632	38	0-6157	6170	6184	6198	6211	6225	6239	6252	6266	6280	2	5	7	9	11
0-6807	39	0-6293	6307	6320	6334	6347	6361	6374	6388	6401	6414	2	4	7	9	11
0-6981	40	0-6428	6441	6455	6468	6481	6494	6508	6521	6534	6547	2	4	7	9	11
0-7156	41	0-6561	6574	6587	6600	6613	6626	6639	6652	6665	6678	2	4	7	9	11
0-7330	42	0-6699	6704	6717	6730	6743	6756	6769	6782	6794	6807	2	4	6	9	11
0-7505	43	0-6820	6833	6845	6858	6871	6884	6896	6909	6921	6934	2	4	6	8	11
0-7679	44	0-6947	6959	6972	6984	6997	7009	7022	7034	7046	7059	2	4	6	8	10
0-7854	45	0-7071	7083	7096	7108	7120	7133	7145	7157	7169	7181	2	4	6	8	10

Radian=0017 | 0035 | 0052 | 0070 | 0087 | 0105 | 0122 | 0140 | 0157 |

TABLE 15
NATURAL SINES

Radian.	Degree.	0°	6'	12'	18'	24'	30'	36'	42'	48'	54'	Add:				
		0-0°	0-1'	0-2'	0-3'	0-4'	0-5'	0-6'	0-7'	0-8'	0-9'	1'	2'	3'	4'	5'
0.7854	45	0.7071	7083	7096	7108	7120	7133	7145	7157	7169	7181	2	4	6	8	10
0.8029	46	0.7193	7206	7218	7230	7242	7254	7266	7278	7290	7302	2	4	6	8	10
0.8203	47	0.7314	7325	7337	7349	7361	7373	7385	7396	7408	7420	2	4	6	8	10
0.8378	48	0.7431	7443	7455	7466	7478	7490	7501	7513	7524	7536	2	4	6	8	10
0.8552	49	0.7547	7559	7570	7581	7593	7604	7615	7627	7638	7649	2	4	6	8	9
0.8727	50	0.7660	7672	7683	7694	7705	7716	7727	7738	7749	7760	2	4	6	7	9
0.8901	51	0.7771	7782	7793	7804	7815	7826	7837	7848	7859	7869	2	4	5	7	9
0.9076	52	0.7880	7891	7902	7912	7923	7934	7944	7955	7965	7976	2	4	5	7	9
0.9250	53	0.7986	7997	8007	8018	8028	8039	8049	8059	8070	8080	2	3	5	7	9
0.9425	54	0.8090	8100	8111	8121	8131	8141	8151	8161	8171	8181	2	3	5	7	8
0.9599	55	0.8192	8202	8211	8221	8231	8241	8251	8261	8271	8281	2	3	5	7	8
0.9774	56	0.8290	8300	8310	8320	8329	8339	8348	8358	8368	8377	2	3	5	6	8
0.9948	57	0.8387	8396	8406	8415	8425	8434	8443	8453	8462	8471	2	3	5	6	8
1.0123	58	0.8480	8490	8499	8508	8517	8526	8535	8545	8554	8563	2	3	5	6	8
1.0297	59	0.8572	8581	8590	8599	8607	8616	8625	8634	8643	8652	1	3	4	6	7
1.0472	60	0.8660	8669	8678	8686	8695	8704	8712	8721	8729	8738	1	3	4	6	7
1.0647	61	0.8746	8755	8763	8771	8780	8788	8796	8805	8813	8821	1	3	4	6	7
1.0821	62	0.8829	8838	8846	8854	8862	8870	8878	8886	8894	8902	1	3	4	5	7
1.0996	63	0.8910	8918	8926	8934	8942	8949	8957	8965	8973	8980	1	3	4	5	6
1.1170	64	0.8988	8996	9003	9011	9018	9026	9033	9041	9048	9056	1	3	4	5	6
1.1345	65	0.9063	9070	9078	9085	9092	9100	9107	9114	9121	9128	1	2	4	5	6
1.1519	66	0.9135	9143	9150	9157	9164	9171	9178	9184	9191	9198	1	2	3	5	6
1.1694	67	0.9205	9212	9219	9225	9232	9239	9245	9252	9259	9265	1	2	3	4	6
1.1868	68	0.9272	9278	9285	9291	9298	9304	9311	9317	9323	9330	1	2	3	4	5
1.2043	69	0.9336	9342	9348	9354	9361	9367	9373	9379	9385	9391	1	2	3	4	5
1.2217	70	0.9397	9403	9409	9415	9421	9426	9432	9438	9444	9449	1	2	3	4	5
1.2392	71	0.9455	9461	9466	9472	9478	9483	9489	9494	9500	9505	1	2	3	4	5
1.2566	72	0.9511	9516	9521	9527	9532	9537	9542	9548	9553	9558	1	2	3	3	4
1.2741	73	0.9563	9568	9573	9578	9583	9588	9593	9598	9603	9608	1	2	2	3	4
1.2915	74	0.9613	9617	9622	9627	9632	9636	9641	9646	9650	9655	1	2	2	3	4
1.3090	75	0.9659	9664	9668	9673	9677	9681	9686	9690	9694	9699	1	1	2	3	4
1.3265	76	0.9703	9707	9711	9715	9720	9724	9728	9732	9736	9740	1	1	2	3	3
1.3439	77	0.9744	9748	9751	9755	9759	9763	9767	9770	9774	9778	1	1	2	3	3
1.3614	78	0.9781	9785	9789	9792	9796	9799	9803	9806	9810	9813	1	1	2	2	3
1.3788	79	0.9816	9820	9823	9826	9829	9833	9836	9839	9842	9845	1	1	2	2	3
1.3963	80	0.9848	9851	9854	9857	9860	9863	9866	9869	9871	9874	0	1	1	2	2
1.4137	81	0.9877	9880	9882	9885	9888	9890	9893	9895	9898	9900	0	1	1	2	2
1.4312	82	0.9903	9905	9907	9910	9912	9914	9917	9919	9921	9923	0	1	1	2	2
1.4486	83	0.9925	9928	9930	9932	9934	9936	9938	9940	9942	9943	0	1	1	1	2
1.4661	84	0.9945	9947	9949	9951	9952	9954	9956	9957	9959	9960	0	1	1	1	1
1.4835	85	0.9962	9963	9965	9966	9968	9969	9971	9972	9973	9974	0	0	1	1	1
1.5010	86	0.9976	9977	9978	9979	9980	9981	9982	9983	9984	9985	0	0	1	1	1
1.5184	87	0.9986	9987	9988	9989	9990	9990	9991	9992	9993	9993	0	0	0	1	1
1.5359	88	0.9994	9995	9995	9996	9996	9997	9997	9997	9998	9998	0	0	0	0	0
1.5533	89	0.9998	9999	9999	9999	9999	1.000	1.000	1.000	1.000	1.000	0	0	0	0	0
1.5708	90	1.0000														

Radian = 0017 | 0035 | 0052 | 0070 | 0087 | 0105 | 0122 | 0140 | 0157 |

TABLE 16
NATURAL COSINES

Radian.	Degree.	0°	6°	12°	18°	24°	30°	36°	42°	48°	54°	Subtract :				
		0-0°	0-1°	0-2°	0-3°	0-4°	0-5°	0-6°	0-7°	0-8°	0-9°	1'	2'	3'	4'	5'
0-0000	0	1-0000	0000	0000	0000	0000	0000	9999	9999	9999	9999	0	0	0	0	0
0-0175	1	0-9998	9998	9998	9997	9997	9997	9996	9996	9995	9995	0	0	0	0	0
0-0349	2	0-9994	9993	9993	9992	9991	9990	9990	9989	9988	9987	0	0	0	1	1
0-0524	3	0-9986	9985	9984	9983	9982	9981	9980	9979	9978	9977	0	0	1	1	1
0-0698	4	0-9976	9974	9973	9972	9971	9969	9968	9968	9965	9963	0	0	1	1	1
0-0873	5	0-9962	9960	9959	9957	9956	9954	9952	9951	9949	9947	0	1	1	1	1
0-1047	6	0-9945	9943	9942	9940	9938	9936	9934	9932	9930	9928	0	1	1	1	2
0-1222	7	0-9925	9923	9921	9919	9917	9914	9912	9910	9907	9905	0	1	1	2	2
0-1396	8	0-9903	9900	9898	9895	9893	9890	9888	9885	9882	9880	0	1	1	2	2
0-1571	9	0-9877	9874	9871	9869	9866	9863	9860	9857	9854	9851	0	1	1	2	2
0-1745	10	0-9848	9845	9842	9839	9836	9833	9829	9826	9823	9820	1	1	2	2	3
0-1920	11	0-9816	9813	9810	9806	9803	9799	9796	9792	9789	9785	1	1	2	2	3
0-2094	12	0-9781	9778	9774	9770	9767	9763	9759	9755	9751	9748	1	1	2	3	3
0-2269	13	0-9744	9740	9736	9732	9728	9724	9720	9715	9711	9707	1	1	2	3	3
0-2443	14	0-9703	9699	9694	9690	9686	9681	9677	9673	9668	9664	1	1	2	3	4
0-2618	15	0-9659	9655	9650	9646	9641	9636	9632	9627	9622	9617	1	2	2	3	4
0-2793	16	0-9613	9608	9603	9598	9593	9588	9583	9578	9573	9568	1	2	2	3	4
0-2967	17	0-9563	9558	9553	9548	9542	9537	9532	9527	9521	9516	1	2	3	3	4
0-3142	18	0-9511	9505	9500	9494	9489	9483	9478	9472	9466	9461	1	2	3	4	5
0-3316	19	0-9455	9449	9444	9438	9432	9426	9421	9415	9409	9403	1	2	3	4	5
0-3491	20	0-9397	9391	9385	9379	9373	9367	9361	9354	9348	9342	1	2	3	4	5
0-3665	21	0-9336	9330	9323	9317	9311	9304	9298	9291	9285	9278	1	2	3	4	5
0-3840	22	0-9272	9265	9259	9252	9245	9239	9232	9225	9219	9212	1	2	3	4	6
0-4014	23	0-9205	9198	9191	9184	9178	9171	9164	9157	9150	9143	1	2	3	5	6
0-4189	24	0-9135	9128	9121	9114	9107	9100	9092	9085	9078	9070	1	2	4	5	6
0-4363	25	0-9063	9056	9048	9041	9033	9026	9018	9011	9003	8996	1	3	4	5	6
0-4538	26	0-8988	8980	8973	8965	8957	8949	8942	8934	8926	8918	1	3	4	5	6
0-4712	27	0-8910	8902	8894	8886	8878	8870	8862	8854	8846	8838	1	3	4	5	7
0-4887	28	0-8829	8821	8813	8805	8796	8788	8780	8771	8763	8755	1	3	4	6	7
0-5061	29	0-8746	8738	8729	8721	8712	8704	8695	8686	8678	8669	1	3	4	6	7
0-5236	30	0-8660	8652	8643	8634	8625	8616	8607	8599	8590	8581	1	3	4	6	7
0-5411	31	0-8572	8563	8554	8545	8536	8526	8517	8508	8499	8490	2	3	5	6	8
0-5585	32	0-8480	8471	8462	8453	8443	8434	8425	8415	8406	8396	2	3	5	6	8
0-5760	33	0-8387	8377	8368	8358	8348	8339	8329	8320	8310	8300	2	3	5	6	8
0-5934	34	0-8290	8281	8271	8261	8251	8241	8231	8221	8211	8202	2	3	5	7	8
0-6109	35	0-8192	8181	8171	8161	8151	8141	8131	8121	8111	8100	2	3	5	7	8
0-6283	36	0-8090	8080	8070	8059	8049	8039	8028	8018	8007	7997	2	3	5	7	9
0-6458	37	0-7986	7976	7965	7955	7944	7934	7923	7912	7902	7891	2	4	5	7	9
0-6632	38	0-7880	7869	7859	7848	7837	7826	7815	7804	7793	7782	2	4	5	7	9
0-6807	39	0-7771	7760	7749	7738	7727	7716	7705	7694	7683	7672	2	4	6	7	9
0-6981	40	0-7660	7649	7638	7627	7615	7604	7593	7581	7570	7559	2	4	6	8	9
0-7156	41	0-7547	7536	7524	7513	7501	7490	7478	7466	7455	7443	2	4	6	8	10
0-7330	42	0-7431	7420	7408	7396	7385	7373	7361	7349	7337	7325	2	4	6	8	10
0-7505	43	0-7314	7302	7290	7278	7266	7254	7242	7230	7218	7206	2	4	6	8	10
0-7679	44	0-7193	7181	7169	7157	7145	7133	7120	7108	7096	7083	2	4	6	8	10
0-7854	45	0-7071	7059	7046	7034	7022	7009	6997	6984	6972	6959	2	4	6	8	10

Radian = 0017 0035 0052 0070 0087 0105 0122 0140 0157

TABLE 16
NATURAL COSINES

Radian.	Degree.	0'	6'	12'	18'	24'	30'	36'	42'	48'	54'	Subtract :				
		0-0°	0-1°	0-2°	0-3°	0-4°	0-5°	0-6°	0-7°	0-8°	0-9°	1'	2'	3'	4'	5'
0.7854	45	0.7071	7059	7046	7034	7022	7009	6997	6984	6972	6959	2	4	6	8	10
0.8029	46	0.6947	6934	6921	6909	6896	6884	6871	6858	6845	6833	2	4	6	8	11
0.8203	47	0.6820	6807	6794	6782	6769	6756	6743	6730	6717	6704	2	4	6	9	11
0.8378	48	0.6691	6678	6665	6652	6639	6626	6613	6600	6587	6574	2	4	7	9	11
0.8552	49	0.6561	6547	6534	6521	6508	6494	6481	6468	6455	6441	2	4	7	9	11
0.8727	50	0.6428	6414	6401	6388	6374	6361	6347	6334	6320	6307	2	4	7	9	11
0.8901	51	0.6293	6280	6266	6252	6239	6225	6211	6198	6184	6170	2	5	7	9	11
0.9076	52	0.6157	6143	6129	6115	6101	6088	6074	6060	6046	6032	2	5	7	9	12
0.9250	53	0.6018	6004	5990	5976	5962	5948	5934	5920	5906	5892	2	5	7	9	12
0.9425	54	0.5878	5864	5850	5835	5821	5807	5793	5779	5764	5750	2	5	7	9	12
0.9599	55	0.5763	5721	5707	5693	5678	5664	5650	5635	5621	5606	2	5	7	10	12
0.9774	56	0.5592	5577	5563	5548	5534	5519	5505	5490	5476	5461	2	5	7	10	12
0.9943	57	0.5446	5432	5417	5402	5388	5373	5358	5344	5329	5314	2	5	7	10	12
1.0123	58	0.5299	5284	5270	5255	5240	5225	5210	5195	5180	5165	2	5	7	10	12
1.0297	59	0.5150	5135	5120	5105	5090	5075	5060	5045	5030	5015	3	5	8	10	13
1.0472	60	0.5000	4985	4970	4955	4939	4924	4909	4894	4879	4863	3	5	8	10	13
1.0647	61	0.4848	4833	4818	4802	4787	4772	4756	4741	4726	4710	3	5	8	10	13
1.0821	62	0.4695	4679	4664	4648	4633	4617	4602	4586	4571	4555	3	5	8	10	13
1.0996	63	0.4540	4524	4509	4493	4478	4462	4446	4431	4415	4399	3	5	8	10	13
1.1170	64	0.4384	4368	4352	4337	4321	4305	4289	4274	4258	4242	3	5	8	11	13
1.1345	65	0.4226	4210	4195	4179	4163	4147	4131	4115	4099	4083	3	5	8	11	13
1.1519	66	0.4067	4051	4035	4019	4003	3987	3971	3955	3939	3923	3	5	8	11	14
1.1694	67	0.3907	3891	3875	3859	3843	3827	3811	3795	3778	3762	3	5	8	11	14
1.1868	68	0.3746	3730	3714	3697	3681	3665	3649	3633	3616	3600	3	5	8	11	14
1.2043	69	0.3584	3567	3551	3535	3518	3502	3486	3469	3453	3437	3	5	8	11	14
1.2217	70	0.3420	3404	3387	3371	3355	3338	3322	3305	3289	3272	3	5	8	11	14
1.2392	71	0.3256	3239	3223	3206	3190	3173	3156	3140	3123	3107	3	6	8	11	14
1.2566	72	0.3090	3074	3057	3040	3024	3007	2990	2974	2957	2940	3	6	8	11	14
1.2741	73	0.2924	2907	2890	2874	2857	2840	2823	2807	2790	2773	3	6	8	11	14
1.2915	74	0.2756	2740	2723	2706	2689	2672	2656	2639	2622	2605	3	6	8	11	14
1.3090	75	0.2588	2571	2554	2538	2521	2504	2487	2470	2453	2436	3	6	8	11	14
1.3265	76	0.2419	2402	2385	2368	2351	2334	2317	2300	2284	2267	3	6	8	11	14
1.3439	77	0.2250	2233	2215	2198	2181	2164	2147	2130	2113	2096	3	6	9	11	14
1.3614	78	0.2079	2062	2045	2028	2011	1994	1977	1959	1942	1925	3	6	9	11	14
1.3788	79	0.1908	1891	1874	1857	1840	1822	1805	1788	1771	1754	3	6	9	11	14
1.3963	80	0.1736	1719	1702	1685	1668	1650	1633	1616	1599	1582	3	6	9	12	14
1.4137	81	0.1564	1547	1530	1513	1495	1478	1461	1444	1426	1409	3	6	9	12	14
1.4312	82	0.1392	1374	1357	1340	1323	1305	1288	1271	1253	1236	3	6	9	12	14
1.4486	83	0.1219	1201	1184	1167	1149	1132	1115	1097	1080	1063	3	6	9	12	14
1.4661	84	0.1045	1028	1011	0993	0976	0958	0941	0924	0906	0889	3	6	9	12	14
1.4835	85	0.0872	0854	0837	0819	0802	0785	0767	0750	0732	0715	3	6	9	12	14
1.5010	86	0.0698	0680	0663	0645	0628	0610	0593	0576	0558	0541	3	6	9	12	15
1.5184	87	0.0523	0506	0488	0471	0454	0436	0419	0401	0384	0366	3	6	9	12	15
1.5359	88	0.0349	0332	0314	0297	0279	0262	0244	0227	0209	0192	3	6	9	12	15
1.5533	89	0.0175	0157	0140	0122	0105	0087	0070	0052	0035	0017	3	6	9	12	15
1.5708	90	0.0000														

Radian = 0017 | 0035 | 0052 | 0070 | 0087 | 0105 | 0122 | 0140 | 0157

TABLE 17
NATURAL TANGENTS

Radian.	Degree.											Add :				
		0°	6'	12'	18'	24'	30'	36'	42'	48'	54'	1'	2'	3'	4'	5'
		0-0°	0-1°	0-2°	0-3°	0-4°	0-5°	0-6°	0-7°	0-8°	0-9°					
0-0000	0	0-0000	0017	0035	0052	0070	0087	0105	0122	0140	0157	3	6	9	12	15
0-0175	1	0-0175	0192	0209	0227	0244	0262	0279	0297	0314	0332	3	6	9	12	15
0-0349	2	0-0349	0367	0384	0402	0419	0437	0454	0472	0489	0507	3	6	9	12	15
0-0524	3	0-0524	0542	0559	0577	0594	0612	0629	0647	0664	0682	3	6	9	12	15
0-0698	4	0-0699	0717	0734	0752	0769	0787	0805	0822	0840	0857	3	6	9	12	15
0-0873	5	0-0875	0892	0910	0928	0945	0963	0981	0998	1016	1033	3	6	9	12	15
0-1047	6	0-1051	1069	1086	1104	1122	1139	1157	1175	1192	1210	3	6	9	12	15
0-1222	7	0-1228	1246	1263	1281	1299	1317	1334	1352	1370	1388	3	6	9	12	15
0-1396	8	0-1405	1423	1441	1459	1477	1495	1512	1530	1548	1566	3	6	9	12	15
0-1571	9	0-1584	1602	1620	1638	1655	1673	1691	1709	1727	1745	3	6	9	12	15
0-1745	10	0-1763	1781	1799	1817	1835	1853	1871	1890	1908	1926	3	6	9	12	15
0-1920	11	0-1944	1962	1980	1998	2016	2035	2053	2071	2089	2107	3	6	9	12	15
0-2094	12	0-2126	2144	2162	2180	2199	2217	2235	2254	2272	2290	3	6	9	12	15
0-2269	13	0-2309	2327	2345	2364	2382	2401	2419	2438	2456	2475	3	6	9	12	15
0-2443	14	0-2493	2512	2530	2549	2568	2586	2605	2623	2642	2661	3	6	9	12	16
0-2618	15	0-2679	2698	2717	2736	2754	2773	2792	2811	2830	2849	3	6	9	13	16
0-2793	16	0-2867	2886	2905	2924	2943	2962	2981	3000	3019	3038	3	6	9	13	16
0-2967	17	0-3057	3076	3096	3115	3134	3153	3172	3191	3211	3230	3	6	10	13	16
0-3142	18	0-3249	3269	3289	3307	3327	3346	3365	3385	3404	3424	3	6	10	13	16
0-3316	19	0-3443	3463	3482	3502	3522	3541	3561	3581	3600	3620	3	7	10	13	16
0-3491	20	0-3640	3659	3679	3699	3719	3739	3759	3779	3799	3819	3	7	10	13	17
0-3665	21	0-3839	3859	3879	3899	3919	3939	3959	3979	4000	4020	3	7	10	13	17
0-3840	22	0-4040	4061	4081	4101	4122	4142	4163	4183	4204	4224	3	7	10	14	17
0-4014	23	0-4245	4265	4286	4307	4327	4348	4369	4390	4411	4431	3	7	10	14	17
0-4189	24	0-4452	4473	4494	4515	4536	4557	4578	4599	4621	4642	4	7	11	14	18
0-4363	25	0-4663	4684	4706	4727	4748	4770	4791	4813	4834	4856	4	7	11	14	18
0-4538	26	0-4877	4899	4921	4942	4964	4986	5008	5029	5051	5073	4	7	11	15	18
0-4712	27	0-5095	5117	5139	5161	5184	5206	5228	5250	5272	5295	4	7	11	15	18
0-4887	28	0-5317	5340	5362	5384	5407	5430	5452	5475	5498	5520	4	8	11	15	19
0-5061	29	0-5543	5566	5589	5612	5635	5658	5681	5704	5727	5750	4	8	12	15	19
0-5236	30	0-5774	5797	5820	5844	5867	5890	5914	5938	5961	5985	4	8	12	16	20
0-5411	31	0-6009	6032	6056	6080	6104	6128	6152	6176	6200	6224	4	8	12	16	20
0-5585	32	0-6249	6273	6297	6322	6346	6371	6395	6420	6445	6469	4	8	12	16	20
0-5760	33	0-6494	6519	6544	6569	6594	6619	6644	6669	6694	6720	4	8	13	17	21
0-5934	34	0-6745	6771	6796	6822	6847	6873	6899	6924	2950	6976	4	9	13	17	21
0-6109	35	0-7002	7028	7054	7080	7107	7133	7159	7186	7212	7239	4	9	13	18	22
0-6283	36	0-7265	7292	7319	7346	7373	7400	7427	7454	7481	7508	5	9	14	18	23
0-6458	37	0-7536	7563	7590	7618	7646	7673	7701	7729	7757	7785	5	9	14	18	23
0-6632	38	0-7813	7841	7869	7898	7926	7954	7983	8012	8040	8069	5	9	14	19	24
0-6807	39	0-8098	8127	8156	8185	8214	8243	8273	8302	8332	8361	5	10	15	20	24
0-6981	40	0-8391	8421	8451	8481	8511	8541	8571	8601	8632	8662	5	10	15	20	25
0-7156	41	0-8693	8724	8754	8785	8816	8847	8878	8910	8941	8972	5	10	16	21	26
0-7330	42	0-9004	9036	9067	9099	9131	9163	9195	9228	9260	9293	5	11	16	21	27
0-7505	43	0-9325	9358	9391	9424	9457	9490	9523	9556	9590	9623	6	11	17	22	28
0-7679	44	0-9657	9691	9725	9759	9793	9827	9861	9896	9930	9965	6	11	17	23	29
0-7854	45	1-0000	0035	0070	0105	0141	0176	0212	0247	0283	0319	6	12	18	24	30

Radian = 0017 | 0035 | 0052 | 0070 | 0087 | 0105 | 0122 | 0140 | 0157 |

TABLE 17
NATURAL TANGENTS

Radian.	Degree.											Add :					
		0'	6'	12'	18'	24'	30'	36'	42'	48'	54'	1'	2'	3'	4'	5'	
0.7854	45	1.0000	0035	0070	0105	0141	0176	0212	0247	0283	0319	6	12	18	24	30	
0.8029	46	1.0355	0392	0428	0464	0501	0538	0575	0612	0649	0686	6	12	18	25	31	
0.8203	47	1.0724	0761	0799	0837	0875	0913	0951	0990	1028	1067	6	13	19	25	32	
0.8378	48	1.1106	1145	1184	1224	1263	1303	1343	1383	1423	1463	7	13	20	27	33	
0.8552	49	1.1504	1544	1585	1626	1667	1708	1750	1792	1833	1875	7	14	21	28	34	
0.8727	50	1.1918	1960	2002	2045	2088	2131	2174	2218	2261	2305	7	14	22	29	36	
0.8901	51	1.2349	2393	2437	2482	2527	2572	2617	2662	2708	2753	8	15	23	30	38	
0.9076	52	1.2799	2846	2892	2938	2985	3032	3079	3127	3175	3222	8	16	24	31	39	
0.9250	53	1.3270	3319	3367	3416	3465	3514	3564	3613	3663	3713	8	16	25	33	41	
0.9425	54	1.3764	3814	3865	3916	3968	4019	4071	4124	4176	4229	9	17	26	34	43	
0.9599	55	1.4281	4335	4388	4442	4496	4550	4605	4659	4715	4770	9	18	27	36	45	
0.9774	56	1.4826	4882	4938	4994	5051	5108	5166	5224	5282	5340	10	19	29	38	48	
0.9948	57	1.5399	5458	5517	5577	5637	5697	5757	5818	5880	5941	10	20	30	40	50	
1.0123	58	1.6003	6066	6128	6191	6255	6319	6383	6447	6512	6577	11	21	32	43	53	
1.0297	59	1.6643	6709	6775	6842	6909	6977	7045	7113	7182	7251	11	23	34	45	56	
1.0472	60	1.7321	7391	7461	7532	7603	7675	7747	7820	7893	7966	12	24	36	48	60	
1.0647	61	1.8040	8115	8190	8265	8341	8418	8495	8572	8650	8728	13	26	38	51	64	
1.0821	62	1.8807	8887	8967	9047	9128	9210	9292	9375	9458	9542	14	27	41	55	68	
1.0996	63	1.9626	9711	9797	9883	9970	0057	0145	0233	0323	0413	15	29	44	58	73	
1.1170	64	2.0503	0594	0686	0778	0872	0965	1060	1155	1251	1348	16	31	47	63	78	
1.1345	65	2.1445	1543	1642	1742	1842	1943	2045	2148	2251	2355	17	34	51	68	85	
1.1519	66	2.2460	2566	2673	2781	2889	2998	3109	3220	3332	3445	18	37	55	73	92	
1.1694	67	2.3559	3673	3789	3906	4023	4142	4262	4383	4504	4627	20	40	60	79	99	
1.1868	68	2.4751	4876	5002	5129	5257	5386	5517	5649	5782	5916	22	43	65	87	108	
1.2043	69	2.6051	6187	6325	6464	6605	6746	6889	7034	7179	7326	24	47	71	95	119	
1.2217	70	2.7475	7625	7776	7929	8083	8239	8397	8556	8716	8878	26	52	78	104	131	
1.2392	71	2.9042	9208	9375	9544	9714	9887	0061	0237	0415	0595	29	58	87	116	145	
1.2566	72	3.0777	0961	1146	1334	1524	1716	1910	2106	2305	2506	32	64	96	129	161	
1.2741	73	3.2709	2914	3122	3332	3544	3759	3977	4197	4420	4646	36	72	108	144	180	
1.2915	74	3.4874	5105	5339	5576	5816	6059	6305	6554	6806	7062	41	81	122	163	204	
1.3090	75	3.7321	7583	7848	8118	8391	8667	8947	9232	9520	9812	46	93	139	186	232	
1.3265	76	4.0108	0408	0713	1022	1335	1653	1976	2303	2635	2972						
1.3439	77	4.3315	3662	4015	4373	4737	5107	5483	5864	6252	6646						
1.3614	78	4.7046	7453	7867	8288	8718	9152	9594	0045	0504	0970						
1.3788	79	5.1446	1829	2422	2924	3435	3955	4486	5026	5578	6140						
1.3963	80	5.6713	7297	7894	8502	9124	9758	0405	1066	1742	2432						
1.4137	81	6.3138	3859	4596	5350	6122	6912	7720	8548	9395	0264	Interpolation is no longer suffi- ciently accurate.					
1.4312	82	7.1154	2066	3002	3962	4947	5958	6996	8062	9158	0285						
1.4486	83	8.1443	2636	3863	5126	6427	7769	9152	0579	2052	3572						
1.4661	84	9.5144	9.877	9.845	10.02	10.20	10.39	10.58	10.78	10.99	11.20						
1.4835	85	11.43	11.66	11.91	12.16	12.43	12.71	13.00	13.30	13.62	13.95						
1.5010	86	14.30	14.67	15.06	15.46	15.89	16.35	16.83	17.34	17.89	18.46						
1.5184	87	19.08	19.74	20.45	21.20	22.02	22.90	23.86	24.90	26.03	27.27						
1.5359	88	28.64	30.14	31.82	33.69	35.80	38.19	40.92	44.07	47.74	52.08						
1.5533	89	57.29	63.66	71.62	81.85	95.49	114.6	143.2	191.0	286.5	573.0						
1.5708	90	∞															

TABLE 18
LOGARITHMS OF SINES

Radian.	Degree.											Add:				
		0°	6'	12'	18'	24'	30'	36'	42'	48'	54'	1'	2'	3'	4'	5'
0-0000	0	— ∞	3.2419	5429	7190	8439	9408	0200	0870	1450	1961	Interpolation is not sufficiently accurate.				
0-0175	1	2.2419	2832	3210	3558	3880	4179	4459	4723	4971	5206					
0-0349	2	2.5528	5640	5842	6035	6220	6397	6567	6731	6889	7041					
0-0524	3	2.7188	7330	7463	7602	7731	7857	7979	8098	8213	8326					
0-0698	4	2.8436	8543	8647	8749	8849	8946	9042	9135	9226	9315	16	32	48	64	80
0-0873	5	2.9403	9489	9573	9655	9736	9816	9894	9970	0046	0120	13	26	39	52	65
0-1047	6	3.0192	0264	0334	0403	0472	0539	0605	0670	0734	0797	11	22	33	44	55
0-1222	7	3.0859	0920	0981	1040	1099	1157	1214	1271	1326	1381	10	19	29	38	48
0-1396	8	3.1436	1489	1542	1594	1646	1697	1747	1797	1847	1895	8	17	25	34	42
0-1571	9	3.1943	1991	2038	2085	2131	2176	2221	2266	2310	2353	8	15	23	30	38
0-1745	10	3.2397	2439	2482	2524	2565	2606	2647	2687	2727	2767	7	14	20	27	34
0-1920	11	3.2806	2845	2883	2921	2959	2997	3034	3070	3107	3143	6	12	19	25	31
0-2094	12	3.3179	3214	3250	3284	3319	3353	3387	3421	3455	3488	6	11	17	23	28
0-2269	13	3.3521	3554	3588	3618	3650	3682	3713	3745	3775	3806	5	11	16	21	26
0-2443	14	3.3837	3867	3897	3927	3957	3986	4015	4044	4073	4102	5	10	15	20	24
0-2618	15	3.4130	4158	4186	4214	4242	4269	4296	4323	4350	4377	5	9	14	18	23
0-2793	16	3.4403	4490	4456	4482	4508	4533	4559	4584	4609	4634	4	9	13	17	21
0-2967	17	3.4659	4684	4709	4733	4757	4781	4805	4829	4853	4876	4	8	12	16	20
0-3142	18	3.4900	4923	4946	4969	4992	5015	5037	5060	5082	5104	4	8	11	15	19
0-3316	19	3.5126	5148	5170	5192	5213	5235	5256	5278	5299	5320	4	7	11	14	18
0-3491	20	3.5341	5361	5382	5402	5423	5443	5463	5484	5504	5523	3	7	10	14	17
0-3665	21	3.5543	5563	5583	5602	5621	5641	5660	5679	5698	5717	3	6	10	13	16
0-3840	22	3.5736	5754	5773	5792	5810	5828	5847	5865	5883	5901	3	6	9	12	15
0-4014	23	3.5919	5937	5954	5972	5990	6007	6024	6042	6059	6076	3	6	9	12	15
0-4189	24	3.6093	6110	6127	6144	6161	6177	6194	6210	6227	6243	3	6	8	11	14
0-4363	25	3.6259	6276	6292	6308	6324	6340	6356	6371	6387	6403	3	5	8	11	13
0-4538	26	3.6418	6434	6449	6465	6480	6495	6510	6526	6541	6556	3	5	8	10	13
0-4712	27	3.6570	6585	6600	6615	6629	6644	6659	6673	6687	6702	2	5	7	10	12
0-4887	28	3.6716	6730	6744	6759	6773	6787	6801	6814	6828	6842	2	5	7	9	12
0-5061	29	3.6856	6869	6883	6896	6910	6923	6937	6950	6963	6977	2	4	7	9	11
0-5236	30	3.6990	7003	7016	7029	7042	7055	7068	7080	7093	7106	2	4	6	9	11
0-5411	31	3.7118	7131	7144	7156	7168	7181	7193	7205	7218	7230	2	4	6	8	10
0-5585	32	3.7242	7254	7266	7278	7290	7302	7314	7326	7338	7349	2	4	6	8	10
0-5760	33	3.7361	7373	7384	7396	7407	7419	7430	7442	7453	7464	2	4	6	8	10
0-5934	34	3.7476	7487	7498	7509	7520	7531	7542	7553	7564	7575	2	4	6	7	9
0-6109	35	3.7588	7597	7607	7618	7629	7640	7650	7661	7671	7682	2	4	5	7	9
0-6283	36	3.7692	7703	7713	7723	7734	7744	7754	7764	7774	7785	2	3	5	7	9
0-6458	37	3.7795	7805	7815	7825	7835	7844	7854	7864	7874	7884	2	3	5	7	8
0-6632	38	3.7893	7903	7913	7922	7932	7941	7951	7960	7970	7979	2	3	5	6	8
0-6807	39	3.7989	7998	8007	8017	8026	8035	8044	8053	8063	8072	2	3	5	6	8
0-6981	40	3.8081	8090	8099	8108	8117	8125	8134	8143	8152	8161	1	3	4	6	7
0-7156	41	3.8169	8178	8187	8195	8204	8213	8221	8230	8238	8247	1	3	4	6	7
0-7330	42	3.8255	8264	8272	8280	8289	8297	8305	8313	8322	8330	1	3	4	6	7
0-7505	43	3.8338	8346	8354	8362	8370	8378	8386	8394	8402	8410	1	3	4	5	7
0-7679	44	3.8418	8426	8433	8441	8449	8457	8464	8472	8480	8487	1	3	4	5	6
0-7854	45	3.8495	8502	8510	8517	8525	8532	8540	8547	8555	8562	1	2	4	5	6

TABLE 18
LOGARITHMS OF SINES

Radian.	Degree.	0'	6'	12'	18'	24'	30'	36'	42'	48'	54'	Add :				
		0-0'	0-1'	0-2'	0-3'	0-4'	0-5'	0-6'	0-7'	0-8'	0-9'	1'	2'	3'	4'	5'
0.7854	45	I-8495	8502	8510	8517	8525	8532	8540	8547	8555	8562	1	2	4	5	6
0.8029	46	I-8569	8577	8584	8591	8598	8606	8613	8620	8627	8634	1	2	4	5	6
0.8203	47	I-8641	8648	8655	8662	8669	8676	8683	8690	8697	8704	1	2	3	5	6
0.8378	48	I-8711	8718	8724	8731	8738	8745	8751	8758	8765	8771	1	2	3	4	6
0.8552	49	I-8778	8784	8791	8797	8804	8810	8817	8823	8830	8836	1	2	3	4	5
0.8727	50	I-8848	8849	8855	8862	8868	8874	8880	8887	8893	8899	1	2	3	4	5
0.8901	51	I-8905	8911	8917	8923	8929	8935	8941	8947	8953	8959	1	2	3	4	5
0.9076	52	I-8965	8971	8977	8983	8989	8995	9000	9006	9012	9018	1	2	3	4	5
0.9250	53	I-9023	9029	9035	9041	9046	9052	9057	9063	9069	9074	1	2	3	4	5
0.9425	54	I-9080	9085	9091	9096	9101	9107	9112	9118	9123	9128	1	2	3	4	5
0.9599	55	I-9134	9139	9144	9149	9155	9160	9165	9170	9175	9181	1	2	3	3	4
0.9774	56	I-9186	9191	9196	9201	9206	9211	9216	9221	9226	9231	1	2	3	3	4
0.9948	57	I-9236	9241	9246	9251	9255	9260	9265	9270	9275	9279	1	2	2	3	4
1.0123	58	I-9284	9289	9294	9298	9303	9308	9312	9317	9322	9326	1	2	2	3	4
1.0297	59	I-9331	9335	9340	9344	9349	9353	9358	9362	9367	9371	1	1	2	3	4
1.0472	60	I-9375	9380	9384	9388	9393	9397	9401	9406	9410	9414	1	1	2	3	4
1.0647	61	I-9418	9422	9427	9431	9435	9439	9443	9447	9451	9455	1	1	2	3	3
1.0821	62	I-9459	9463	9467	9471	9475	9479	9483	9487	9491	9495	1	1	2	3	3
1.0996	63	I-9499	9503	9506	9510	9514	9518	9522	9525	9529	9533	1	1	2	3	3
1.1170	64	I-9537	9540	9544	9548	9551	9555	9558	9562	9566	9569	1	1	2	2	3
1.1345	65	I-9573	9576	9580	9583	9587	9590	9594	9597	9601	9604	1	1	2	2	3
1.1519	66	I-9607	9611	9614	9617	9621	9624	9627	9631	9634	9637	1	1	2	2	3
1.1694	67	I-9640	9643	9647	9650	9653	9656	9659	9662	9666	9669	1	1	2	2	3
1.1868	68	I-9672	9675	9678	9681	9684	9687	9690	9693	9696	9699	0	1	1	2	2
1.2043	69	I-9702	9704	9707	9710	9713	9716	9719	9722	9724	9727	0	1	1	2	2
1.2217	70	I-9730	9733	9735	9738	9741	9743	9746	9749	9751	9754	0	1	1	2	2
1.2392	71	I-9757	9759	9762	9764	9767	9770	9772	9775	9777	9780	0	1	1	2	2
1.2566	72	I-9782	9785	9787	9789	9792	9794	9797	9799	9801	9804	0	1	1	2	2
1.2741	73	I-9806	9808	9811	9813	9815	9817	9820	9822	9824	9826	0	1	1	2	2
1.2915	74	I-9828	9831	9833	9835	9837	9839	9841	9843	9845	9847	0	1	1	1	2
1.3090	75	I-9849	9851	9853	9855	9857	9859	9861	9863	9865	9867	0	1	1	1	2
1.3265	76	I-9869	9871	9873	9875	9876	9878	9880	9882	9884	9885	0	1	1	1	2
1.3439	77	I-9887	9889	9891	9892	9894	9896	9897	9899	9901	9902	0	1	1	1	1
1.3614	78	I-9904	9906	9907	9909	9910	9912	9913	9915	9916	9918	0	1	1	1	1
1.3788	79	I-9919	9921	9922	9924	9925	9927	9928	9929	9931	9932	0	0	1	1	1
1.3963	80	I-9934	9935	9936	9937	9939	9940	9941	9943	9944	9945	0	0	1	1	1
1.4137	81	I-9946	9947	9949	9950	9951	9952	9953	9954	9955	9956	0	0	1	1	1
1.4312	82	I-9958	9959	9960	9961	9962	9963	9964	9965	9966	9967	0	0	0	1	1
1.4486	83	I-9963	9968	9969	9970	9971	9972	9973	9974	9975	9976	0	0	0	1	1
1.4661	84	I-9976	9977	9978	9978	9979	9980	9981	9981	9982	9983	0	0	0	0	1
1.4835	85	I-9983	9984	9985	9985	9986	9987	9987	9988	9988	9989	0	0	0	0	0
1.5010	86	I-9989	9990	9990	9991	9991	9992	9992	9993	9993	9994	0	0	0	0	0
1.5184	87	I-9994	9994	9995	9995	9996	9996	9996	9996	9997	9997	0	0	0	0	0
1.5359	88	I-9997	9998	9998	9998	9998	9999	9999	9999	9999	9999	0	0	0	0	0
1.5533	89	I-9999	9999	0000	0000	0000	0000	0000	0000	0000	0000	0	0	0	0	0
1.5708	90	0-0000														

Radian= 0017 0085 0052 0070 0087 0105 0122 0140 0157

TABLE 19
LOGARITHMS OF COSINES

Radian.	Degree.											Subtract:						
		0°	1'	2'	3'	4'	5'	6'	7'	8'	9'	1'	2'	3'	4'	5'		
0.0000	0	0.0000	0000	0000	0000	0000	0000	0000	0000	0000	0000	0000	9999	0	0	0	0	0
0.0175	1	I.9999	9999	9999	9999	9999	9999	9999	9998	9998	9998	9998	9998	0	0	0	0	0
0.0349	2	I.9997	9997	9997	9996	9996	9996	9996	9995	9995	9995	9995	9994	0	0	0	0	0
0.0524	3	I.9994	9994	9993	9993	9992	9992	9991	9991	9990	9990	9990	9990	0	0	0	0	0
0.0698	4	I.9989	9989	9988	9988	9987	9987	9986	9985	9985	9984	9984	9984	0	0	0	0	0
0.0873	5	I.9983	9983	9982	9981	9981	9980	9979	9978	9978	9977	9977	9977	0	0	0	0	1
0.1047	6	I.9976	9975	9975	9974	9973	9972	9971	9970	9969	9968	9968	9968	0	0	0	1	1
0.1222	7	I.9968	9967	9966	9965	9964	9963	9962	9961	9960	9959	9959	9959	0	0	0	1	1
0.1396	8	I.9958	9956	9955	9954	9953	9952	9951	9950	9949	9947	9947	9947	0	0	1	1	1
0.1571	9	I.9946	9945	9944	9943	9941	9940	9939	9937	9936	9935	9935	9935	0	0	1	1	1
0.1745	10	I.9934	9932	9931	9929	9928	9927	9925	9924	9922	9921	9921	9921	0	0	1	1	1
0.1920	11	I.9919	9918	9916	9915	9913	9912	9910	9909	9907	9906	9906	9906	0	1	1	1	1
0.2094	12	I.9904	9902	9901	9899	9897	9896	9894	9892	9891	9889	9889	9889	0	1	1	1	1
0.2269	13	I.9887	9885	9884	9882	9880	9878	9876	9875	9873	9871	9871	9871	0	1	1	1	2
0.2443	14	I.9869	9867	9865	9863	9861	9859	9857	9855	9853	9851	9851	9851	0	1	1	1	2
0.2618	15	I.9849	9847	9845	9843	9841	9839	9837	9835	9833	9831	9831	9831	0	1	1	1	2
0.2793	16	I.9828	9826	9824	9822	9820	9817	9815	9813	9811	9808	9808	9808	0	1	1	2	2
0.2967	17	I.9806	9804	9801	9799	9797	9794	9792	9789	9787	9785	9785	9785	0	1	1	2	2
0.3142	18	I.9782	9780	9777	9775	9772	9770	9767	9764	9762	9759	9759	9759	0	1	1	2	2
0.3316	19	I.9757	9754	9751	9749	9746	9743	9741	9738	9735	9733	9733	9733	0	1	1	2	2
0.3491	20	I.9730	9727	9724	9722	9719	9716	9713	9710	9707	9704	9704	9704	0	1	1	2	2
0.3665	21	I.9702	9699	9696	9693	9690	9687	9684	9681	9678	9675	9675	9675	0	1	1	2	2
0.3840	22	I.9672	9669	9666	9662	9659	9656	9653	9650	9647	9643	9643	9643	1	1	2	2	3
0.4014	23	I.9640	9637	9634	9631	9627	9624	9621	9617	9614	9611	9611	9611	1	1	2	2	3
0.4189	24	I.9607	9604	9601	9597	9594	9590	9587	9583	9580	9576	9576	9576	1	1	2	2	3
0.4363	25	I.9573	9569	9566	9562	9558	9555	9551	9548	9544	9540	9540	9540	1	1	2	2	3
0.4538	26	I.9537	9533	9529	9525	9522	9518	9514	9510	9506	9503	9503	9503	1	1	2	3	3
0.4712	27	I.9499	9495	9491	9487	9483	9479	9475	9471	9467	9463	9463	9463	1	1	2	3	3
0.4887	28	I.9459	9455	9451	9447	9443	9439	9435	9431	9427	9422	9422	9422	1	1	2	3	3
0.5061	29	I.9418	9414	9410	9406	9401	9397	9393	9388	9384	9380	9380	9380	1	1	2	3	4
0.5236	30	I.9375	9371	9367	9362	9358	9353	9349	9344	9340	9335	9335	9335	1	1	2	3	4
0.5411	31	I.9331	9326	9322	9317	9312	9308	9303	9298	9294	9289	9289	9289	1	2	2	3	4
0.5585	32	I.9284	9279	9275	9270	9265	9260	9255	9251	9246	9241	9241	9241	1	2	2	3	4
0.5760	33	I.9236	9231	9226	9221	9216	9211	9206	9201	9196	9191	9191	9191	1	2	3	3	4
0.5934	34	I.9186	9181	9175	9170	9165	9160	9155	9149	9144	9139	9139	9139	1	2	3	3	4
0.6109	35	I.9134	9128	9123	9118	9112	9107	9101	9096	9091	9085	9085	9085	1	2	3	4	5
0.6283	36	I.9080	9074	9069	9063	9057	9052	9046	9041	9035	9029	9029	9029	1	2	3	4	5
0.6458	37	I.9023	9018	9012	9006	9000	8995	8989	8983	8977	8971	8971	8971	1	2	3	4	5
0.6632	38	I.8965	8959	8953	8947	8941	8935	8929	8923	8917	8911	8911	8911	1	2	3	4	5
0.6807	39	I.8905	8899	8893	8887	8880	8874	8868	8862	8855	8849	8849	8849	1	2	3	4	5
0.6981	40	I.8843	8836	8830	8823	8817	8810	8804	8797	8791	8784	8784	8784	1	2	3	4	5
0.7156	41	I.8778	8771	8765	8758	8751	8745	8738	8731	8724	8718	8718	8718	1	2	3	5	6
0.7330	42	I.8711	8704	8697	8690	8683	8676	8669	8662	8655	8648	8648	8648	1	2	3	5	6
0.7505	43	I.8641	8634	8627	8620	8613	8606	8598	8591	8584	8577	8577	8577	1	2	4	5	6
0.7679	44	I.8569	8562	8555	8547	8540	8532	8525	8517	8510	8502	8502	8502	1	2	4	5	6
0.7854	45	I.8495	8487	8480	8472	8464	8457	8449	8441	8433	8426	8426	8426	1	3	4	5	6

Radian = 0017 | 0035 | 0052 | 0070 | 0087 | 0105 | 0122 | 0140 | 0157

TABLE 19
LOGARITHMS OF COSINES

Radian.	Degree.											Subtract :				
		0	6'	12'	18'	24'	30'	36'	42'	48'	54'	1'	2'	3'	4'	5'
		0° 0'	0° 1'	0° 2'	0° 3'	0° 4'	0° 5'	0° 6'	0° 7'	0° 8'	0° 9'					
0.7854	45	I-8495	8487	8480	8472	8464	8457	8449	8441	8433	8426	1	3	4	5	6
0.8029	46	I-8418	8410	8402	8394	8386	8378	8370	8362	8354	8346	1	3	4	5	7
0.8203	47	I-8338	8330	8322	8313	8305	8297	8289	8280	8272	8264	1	3	4	6	7
0.8378	48	I-8255	8247	8238	8230	8221	8213	8204	8195	8187	8178	1	3	4	6	7
0.8552	49	I-8169	8161	8152	8143	8134	8125	8117	8108	8099	8090	1	3	4	6	7
0.8727	50	I-8081	8072	8063	8053	8044	8035	8026	8017	8007	7998	2	3	5	6	8
0.8901	51	I-7989	7979	7970	7960	7951	7941	7932	7922	7913	7903	2	3	5	6	8
0.9076	52	I-7893	7884	7874	7864	7854	7844	7835	7825	7815	7805	2	3	5	7	8
0.9250	53	I-7795	7785	7774	7764	7754	7744	7734	7723	7713	7703	2	3	5	7	9
0.9425	54	I-7692	7682	7671	7661	7650	7640	7629	7618	7607	7597	2	4	5	7	9
0.9599	55	I-7586	7575	7564	7553	7542	7531	7520	7509	7498	7487	2	4	6	7	9
0.9774	56	I-7476	7464	7453	7442	7430	7419	7407	7396	7384	7373	2	4	6	8	10
0.9948	57	I-7361	7349	7338	7326	7314	7302	7290	7278	7266	7254	2	4	6	8	10
1.0123	58	I-7242	7230	7218	7205	7193	7181	7168	7156	7144	7131	2	4	6	8	10
1.0297	59	I-7118	7106	7093	7080	7068	7055	7042	7029	7016	7003	2	4	6	9	11
1.0472	60	I-6990	6977	6963	6950	6937	6923	6910	6896	6883	6869	2	4	7	9	11
1.0647	61	I-6856	6842	6828	6814	6801	6787	6773	6759	6744	6730	2	5	7	9	12
1.0821	62	I-6716	6702	6687	6673	6659	6644	6629	6615	6600	6585	2	5	7	10	12
1.0996	63	I-6570	6556	6541	6526	6510	6495	6480	6465	6449	6434	3	5	8	10	13
1.1170	64	I-6418	6403	6387	6371	6356	6340	6324	6308	6292	6276	3	5	8	11	13
1.1345	65	I-6259	6243	6227	6210	6194	6177	6161	6144	6127	6110	3	6	8	11	14
1.1519	66	I-6093	6076	6059	6042	6024	6007	5990	5972	5954	5937	3	6	9	12	15
1.1694	67	I-5919	5901	5883	5865	5847	5828	5810	5792	5773	5754	3	6	9	12	15
1.1868	68	I-5736	5717	5698	5679	5660	5641	5621	5602	5583	5563	3	6	10	13	16
1.2043	69	I-5543	5523	5504	5484	5463	5443	5423	5402	5382	5361	3	7	10	14	17
1.2217	70	I-5341	5320	5299	5278	5256	5235	5213	5192	5170	5148	4	7	11	14	18
1.2392	71	I-5128	5104	5082	5060	5037	5015	4992	4969	4946	4923	4	8	11	15	19
1.2566	72	I-4900	4876	4853	4829	4805	4781	4757	4733	4709	4684	4	8	12	16	20
1.2741	73	I-4659	4634	4609	4584	4559	4533	4508	4482	4456	4430	4	9	13	17	21
1.2915	74	I-4403	4377	4350	4323	4296	4269	4242	4214	4186	4158	5	9	14	18	23
1.3090	75	I-4130	4102	4073	4044	4015	3986	3957	3927	3897	3867	5	10	15	20	24
1.3265	76	I-3837	3808	3775	3745	3713	3682	3650	3618	3586	3554	5	11	16	21	26
1.3439	77	I-3521	3488	3455	3421	3387	3353	3319	3284	3250	3214	6	11	17	23	28
1.3614	78	I-3179	3143	3107	3070	3034	2997	2959	2921	2883	2845	6	12	19	25	31
1.3788	79	I-2806	2767	2727	2687	2647	2606	2565	2524	2482	2439	7	14	20	27	34
1.3963	80	I-2397	2353	2310	2266	2221	2176	2131	2085	2038	1991	8	15	23	30	38
1.4137	81	I-1943	1895	1847	1797	1747	1697	1646	1594	1542	1489	8	17	25	34	42
1.4312	82	I-1436	1381	1326	1271	1214	1157	1099	1040	981	920	10	19	29	38	48
1.4486	83	I-0859	0797	0734	0607	0605	0539	0472	0403	0334	0264	11	22	33	44	55
1.4661	84	I-0192	0120	0046	9970	9894	9816	9736	9655	9573	9489	13	26	39	52	66
1.4835	85	2-9403	9315	9226	9135	9042	8946	8849	8749	8647	8543	16	32	48	64	80
1.5010	86	2-8436	8326	8213	8098	7979	7857	7731	7602	7468	7330	Interpolation is no longer suffi- ciently accurate.				
1.5184	87	2-7188	7041	6889	6731	6567	6397	6220	6035	5842	5640					
1.5359	88	2-5428	5206	4971	4723	4459	4179	3880	3558	3210	2832					
1.5533	89	2-2419	1961	1450	0870	0200	2408	2439	2190	2429	2419					
1.5708	90	-∞														

Radian— 0017 | 0085 | 0052 | 0070 | 0087 | 0105 | 0122 | 0140 | 0157 |

TABLE 20
LOGARITHMS OF TANGENTS

Radian.	Degree.											Add:				
		0°	6'	12'	18'	24'	30'	36'	42'	48'	54'	1'	2'	3'	4'	5'
0.0000	0	— ∞	3.2419	5429	7190	8439	9409	1200	1870	1450	1962	Interpolation is not sufficiently accurate.				
0.0175	1	2.2419	2833	3211	3559	3881	4181	4461	4725	4973	5208					
0.0349	2	2.5431	5643	5845	6038	6223	6401	6571	6736	6894	7046					
0.0524	3	2.7184	7337	7475	7609	7739	7865	7988	8107	8223	8336					
0.0698	4	2.8446	8554	8659	8762	8862	8960	9056	9150	9241	9331	13	26	40	53	66
0.0873	5	2.9420	9506	9591	9674	9756	9836	9915	9992	10068	10143	11	22	34	45	56
0.1047	6	3.0216	10289	10360	10430	10499	10567	10633	10699	10764	10828	10	20	29	39	49
0.1222	7	3.0891	10954	11015	11076	11135	11194	11252	11310	11367	11423	9	17	26	35	43
0.1396	8	3.1478	11533	11587	11640	11693	11745	11797	11848	11898	11948	8	16	23	31	39
0.1571	9	3.1997	12046	12094	12142	12189	12236	12282	12328	12374	12419	7	14	21	28	35
0.1745	10	3.2463	12507	12551	12594	12637	12680	12722	12764	12805	12846	6	13	19	26	32
0.1920	11	3.2887	12927	12967	13006	13046	13085	13123	13162	13200	13237	5	10	16	22	28
0.2094	12	3.3275	13312	13349	13385	13422	13458	13494	13529	13564	13599	4	9	13	18	22
0.2269	13	3.3634	13668	13702	13736	13770	13804	13837	13870	13903	13935	3	7	11	15	19
0.2443	14	3.3968	14000	14032	14064	14095	14127	14158	14189	14220	14250	2	5	10	16	21
0.2618	15	3.4281	14311	14341	14371	14400	14430	14459	14488	14517	14546	1	4	8	12	16
0.2793	16	3.4575	14603	14632	14660	14688	14716	14744	14771	14799	14826	5	9	14	19	23
0.2967	17	3.4853	14880	14907	14934	14961	14987	15014	15040	15066	15092	4	8	13	18	22
0.3142	18	3.5118	15143	15169	15195	15220	15245	15270	15295	15320	15345	3	7	11	17	21
0.3316	19	3.5370	15394	15419	15443	15467	15491	15516	15539	15563	15587	2	5	10	16	20
0.3491	20	3.5611	15634	15658	15681	15704	15727	15750	15773	15796	15819	1	4	8	12	15
0.3665	21	3.5842	15864	15887	15909	15932	15954	15976	15998	16020	16042	4	7	11	15	19
0.3840	22	3.6064	16086	16108	16129	16151	16172	16194	16215	16236	16257	3	7	11	14	18
0.4014	23	3.6279	16300	16321	16341	16362	16383	16404	16424	16445	16465	2	5	10	14	17
0.4189	24	3.6486	16506	16527	16547	16567	16587	16607	16627	16647	16667	1	4	8	12	16
0.4363	25	3.6687	16706	16726	16746	16765	16785	16804	16824	16843	16863	3	7	10	13	16
0.4538	26	3.6882	16901	16920	16939	16958	16977	16996	17015	17034	17053	2	6	9	13	16
0.4712	27	3.7072	17090	17109	17128	17146	17165	17183	17202	17220	17238	1	5	8	12	15
0.4887	28	3.7257	17275	17293	17311	17330	17348	17366	17384	17402	17420	3	6	9	12	15
0.5061	29	3.7438	17455	17473	17491	17509	17526	17544	17562	17579	17597	2	5	8	12	15
0.5236	30	3.7614	17632	17649	17667	17684	17701	17719	17736	17753	17771	1	4	8	12	14
0.5411	31	3.7788	17805	17822	17839	17856	17873	17890	17907	17924	17941	3	6	9	11	14
0.5585	32	3.7958	17975	17992	18008	18025	18042	18059	18075	18092	18109	2	5	8	11	14
0.5760	33	3.8125	18142	18158	18175	18191	18208	18224	18241	18257	18274	1	4	8	11	14
0.5934	34	3.8290	18306	18323	18339	18355	18371	18388	18404	18420	18436	3	5	8	11	14
0.6109	35	3.8452	18468	18484	18501	18517	18533	18549	18565	18581	18597	2	5	8	11	13
0.6283	36	3.8613	18629	18644	18660	18676	18692	18708	18724	18740	18755	1	4	8	11	13
0.6458	37	3.8771	18787	18803	18818	18834	18850	18865	18881	18897	18912	3	5	8	10	13
0.6632	38	3.8928	18944	18959	18975	18990	19006	19022	19037	19053	19068	2	5	8	10	13
0.6807	39	3.9084	19099	19115	19130	19146	19161	19176	19192	19207	19223	1	4	8	10	13
0.6981	40	3.9238	19254	19269	19284	19300	19315	19330	19346	19361	19376	3	5	8	10	13
0.7156	41	3.9392	19407	19422	19438	19453	19468	19483	19499	19514	19529	2	5	8	10	13
0.7330	42	3.9544	19560	19575	19590	19605	19621	19636	19651	19666	19681	1	4	8	10	13
0.7505	43	3.9697	19712	19727	19742	19757	19772	19788	19803	19818	19833	3	5	8	10	13
0.7679	44	3.9848	19864	19879	19894	19909	19924	19939	19955	19970	19985	2	5	8	10	13
0.7854	45	0.0000	0015	0030	0045	0061	0076	0091	0106	0121	0136	1	4	8	10	13

Radian = 0.017 0035 0052 0070 0087 0105 0122 0140 0157

TABLE 20
LOGARITHMS OF TANGENTS

Radian	Degree.	0'	6'	12'	18'	24'	30'	36'	42'	48'	54'	Add :				
		0-0'	0-1'	0-2'	0-3'	0-4'	0-5'	0-6'	0-7'	0-8'	0-9'	1'	2'	3'	4'	5'
0.7854	45	0.0000	0015	0030	0045	0061	0076	0091	0106	0121	0136	3	5	8	10	13
0.8029	46	0.0152	0167	0182	0197	0212	0228	0243	0258	0273	0288	3	5	8	10	13
0.8203	47	0.0303	0319	0334	0349	0364	0379	0395	0410	0425	0440	3	5	8	10	13
0.8378	48	0.0456	0471	0486	0501	0517	0532	0547	0562	0578	0593	3	5	8	10	13
0.8552	49	0.0608	0624	0639	0654	0670	0685	0700	0716	0731	0746	3	5	8	10	13
0.8727	50	0.0762	0777	0793	0808	0824	0839	0854	0870	0885	0901	3	5	8	10	13
0.8901	51	0.0916	0932	0947	0963	0978	0994	1010	1025	1041	1056	3	5	8	10	13
0.9076	52	0.1072	1088	1103	1119	1135	1150	1166	1182	1197	1213	3	5	8	10	13
0.9250	53	0.1229	1245	1260	1276	1292	1308	1324	1340	1356	1371	3	5	8	11	13
0.9425	54	0.1387	1403	1419	1435	1451	1467	1483	1499	1516	1532	3	5	8	11	13
0.9599	55	0.1548	1564	1580	1596	1612	1629	1645	1661	1677	1694	3	5	8	11	14
0.9774	56	0.1710	1726	1743	1759	1776	1792	1809	1825	1842	1858	3	5	8	11	14
0.9948	57	0.1875	1891	1908	1925	1941	1958	1975	1992	2008	2025	3	6	8	11	14
1.0123	58	0.2042	2059	2076	2093	2110	2127	2144	2161	2178	2195	3	6	9	11	14
1.0297	59	0.2212	2229	2247	2264	2281	2299	2316	2333	2351	2368	3	6	9	12	14
1.0472	60	0.2386	2403	2421	2438	2456	2474	2491	2509	2527	2545	3	6	9	12	15
1.0647	61	0.2562	2580	2598	2616	2634	2652	2670	2688	2707	2725	3	6	9	12	15
1.0821	62	0.2743	2762	2780	2798	2817	2835	2854	2872	2891	2910	3	6	9	12	15
1.0996	63	0.2928	2947	2966	2985	3004	3023	3042	3061	3080	3099	3	6	9	13	16
1.1170	64	0.3118	3137	3157	3176	3196	3215	3235	3254	3274	3294	3	6	10	13	16
1.1345	65	0.3313	3333	3353	3373	3393	3413	3433	3453	3473	3494	3	7	10	13	17
1.1519	66	0.3514	3535	3555	3576	3596	3617	3638	3659	3679	3700	3	7	10	14	17
1.1694	67	0.3721	3743	3764	3785	3806	3828	3849	3871	3892	3914	4	7	11	14	18
1.1868	68	0.3936	3958	3980	4002	4024	4046	4068	4091	4113	4136	4	7	11	15	19
1.2043	69	0.4158	4181	4204	4227	4250	4273	4296	4319	4342	4366	4	8	12	15	19
1.2217	70	0.4389	4413	4437	4461	4484	4509	4533	4557	4581	4606	4	8	12	16	20
1.2392	71	0.4630	4655	4680	4705	4730	4755	4780	4805	4831	4857	4	8	13	17	21
1.2566	72	0.4882	4908	4934	4960	4986	5013	5039	5066	5093	5120	4	9	13	18	22
1.2741	73	0.5147	5174	5201	5229	5256	5284	5312	5340	5368	5397	5	9	14	19	23
1.2915	74	0.5425	5454	5483	5512	5541	5570	5600	5629	5659	5689	5	10	15	20	25
1.3090	75	0.5719	5750	5780	5811	5842	5873	5905	5936	5968	6000	5	10	16	21	26
1.3265	76	0.6032	6065	6097	6130	6163	6196	6230	6264	6298	6332	6	11	17	22	28
1.3439	77	0.6366	6401	6436	6471	6507	6542	6578	6615	6651	6688	6	12	18	24	30
1.3614	78	0.6725	6763	6800	6838	6877	6915	6954	6994	7033	7073	6	13	19	26	32
1.3788	79	0.7113	7154	7195	7236	7278	7320	7363	7406	7449	7493	7	14	21	28	35
1.3963	80	0.7537	7581	7626	7672	7718	7764	7811	7858	7906	7954	8	16	23	31	39
1.4137	81	0.8003	8052	8102	8152	8203	8255	8307	8360	8413	8467	9	17	26	35	43
1.4312	82	0.8522	8577	8633	8690	8748	8806	8865	8924	8985	9046	10	20	29	39	49
1.4486	83	0.9109	9172	9236	9301	9367	9433	9501	9570	9640	9711	11	22	34	45	56
1.4661	84	0.9784	9857	9932	10008	10085	10164	10244	10326	10409	10494	13	26	40	53	66
1.4835	85	1.0580	0669	0759	0850	0944	1040	1138	1238	1341	1446	16	32	48	64	81
1.5010	86	1.1554	1664	1777	1893	2012	2135	2261	2391	2525	2663	Interpolation is no longer suffi- ciently accurate.				
1.5184	87	1.2806	2954	3106	3264	3429	3599	3777	3962	4155	4357					
1.5359	88	1.4569	4792	5027	5275	5539	5819	6119	6441	6789	7167					
1.5533	89	1.7581	8038	8550	9130	9800	10591	11511	12610	13911	15411					
1.5708	90	+ ∞														

Radian— 0017 | 0035 | 0052 | 0070 | 0087 | 0105 | 0122 | 0140 | 0157 |

TABLE 21
CHORDS OF ANGLES

	0'	20'	40'		0'	20'	40'		0'	20'	40'
0	0-0000	0-0058	0-0116	50	0-8452	0-8505	0-8558	100	1-5321	1-5358	1-5395
1	0-0175	0-0233	0-0291	51	0-8610	0-8663	0-8715	101	1-5432	1-5469	1-5506
2	0-0349	0-0407	0-0465	52	0-8767	0-8820	0-8872	102	1-5543	1-5579	1-5616
3	0-0524	0-0582	0-0640	53	0-8924	0-8976	0-9028	103	1-5652	1-5688	1-5724
4	0-0698	0-0756	0-0814	54	0-9080	0-9132	0-9183	104	1-5760	1-5796	1-5832
5	0-0872	0-0931	0-0989	55	0-9235	0-9287	0-9338	105	1-5867	1-5902	1-5938
6	0-1047	0-1105	0-1163	56	0-9389	0-9441	0-9492	106	1-5973	1-6008	1-6042
7	0-1221	0-1279	0-1337	57	0-9543	0-9594	0-9645	107	1-6077	1-6112	1-6146
8	0-1395	0-1453	0-1511	58	0-9696	0-9747	0-9798	108	1-6180	1-6214	1-6248
9	0-1569	0-1627	0-1685	59	0-9848	0-9899	0-9950	109	1-6282	1-6316	1-6350
10	0-1743	0-1801	0-1859	60	1-0000	1-0050	1-0101	110	1-6383	1-6416	1-6450
11	0-1917	0-1975	0-2033	61	1-0151	1-0201	1-0251	111	1-6483	1-6515	1-6548
12	0-2091	0-2148	0-2206	62	1-0301	1-0351	1-0400	112	1-6581	1-6613	1-6646
13	0-2264	0-2322	0-2380	63	1-0450	1-0500	1-0549	113	1-6678	1-6710	1-6742
14	0-2437	0-2495	0-2553	64	1-0598	1-0648	1-0697	114	1-6773	1-6805	1-6838
15	0-2611	0-2668	0-2726	65	1-0746	1-0795	1-0844	115	1-6868	1-6899	1-6930
16	0-2783	0-2841	0-2899	66	1-0893	1-0942	1-0990	116	1-6961	1-6992	1-7022
17	0-2956	0-3014	0-3071	67	1-1039	1-1087	1-1136	117	1-7053	1-7083	1-7113
18	0-3129	0-3186	0-3244	68	1-1184	1-1232	1-1280	118	1-7143	1-7173	1-7203
19	0-3301	0-3358	0-3416	69	1-1328	1-1376	1-1424	119	1-7233	1-7262	1-7291
20	0-3473	0-3530	0-3587	70	1-1472	1-1519	1-1567	120	1-7321	1-7350	1-7378
21	0-3645	0-3702	0-3759	71	1-1614	1-1661	1-1709	121	1-7407	1-7436	1-7464
22	0-3816	0-3873	0-3930	72	1-1756	1-1803	1-1850	122	1-7492	1-7521	1-7549
23	0-3987	0-4044	0-4101	73	1-1896	1-1943	1-1990	123	1-7576	1-7604	1-7632
24	0-4158	0-4215	0-4272	74	1-2036	1-2083	1-2129	124	1-7659	1-7686	1-7713
25	0-4329	0-4386	0-4442	75	1-2175	1-2221	1-2267	125	1-7740	1-7767	1-7794
26	0-4499	0-4556	0-4612	76	1-2313	1-2359	1-2405	126	1-7820	1-7846	1-7873
27	0-4669	0-4725	0-4782	77	1-2450	1-2496	1-2541	127	1-7899	1-7925	1-7950
28	0-4838	0-4895	0-4951	78	1-2586	1-2632	1-2677	128	1-7976	1-8001	1-8027
29	0-5008	0-5064	0-5120	79	1-2722	1-2766	1-2811	129	1-8052	1-8077	1-8101
30	0-5176	0-5233	0-5289	80	1-2856	1-2900	1-2945	130	1-8126	1-8151	1-8175
31	0-5345	0-5401	0-5457	81	1-2989	1-3033	1-3077	131	1-8199	1-8223	1-8247
32	0-5513	0-5569	0-5625	82	1-3121	1-3165	1-3209	132	1-8271	1-8294	1-8318
33	0-5680	0-5736	0-5792	83	1-3252	1-3296	1-3339	133	1-8341	1-8364	1-8387
34	0-5847	0-5903	0-5959	84	1-3383	1-3426	1-3469	134	1-8410	1-8433	1-8455
35	0-6014	0-6070	0-6125	85	1-3512	1-3555	1-3597	135	1-8478	1-8500	1-8522
36	0-6180	0-6236	0-6291	86	1-3640	1-3682	1-3725	136	1-8544	1-8565	1-8587
37	0-6346	0-6401	0-6456	87	1-3767	1-3809	1-3851	137	1-8608	1-8630	1-8651
38	0-6511	0-6566	0-6621	88	1-3893	1-3935	1-3977	138	1-8672	1-8692	1-8713
39	0-6676	0-6731	0-6786	89	1-4018	1-4060	1-4101	139	1-8733	1-8754	1-8774
40	0-6840	0-6895	0-6950	90	1-4142	1-4183	1-4224	140	1-8794	1-8814	1-8833
41	0-7004	0-7059	0-7113	91	1-4265	1-4306	1-4346	141	1-8853	1-8872	1-8891
42	0-7167	0-7222	0-7276	92	1-4387	1-4427	1-4467	142	1-8910	1-8929	1-8948
43	0-7330	0-7384	0-7438	93	1-4507	1-4547	1-4587	143	1-8966	1-8985	1-9003
44	0-7492	0-7546	0-7600	94	1-4627	1-4667	1-4706	144	1-9021	1-9039	1-9057
45	0-7654	0-7707	0-7761	95	1-4746	1-4785	1-4824	145	1-9074	1-9092	1-9109
46	0-7815	0-7868	0-7922	96	1-4863	1-4902	1-4941	146	1-9126	1-9143	1-9160
47	0-7975	0-8028	0-8082	97	1-4979	1-5018	1-5056	147	1-9176	1-9193	1-9208
48	0-8135	0-8188	0-8241	98	1-5094	1-5132	1-5170	148	1-9225	1-9241	1-9257
49	0-8294	0-8347	0-8400	99	1-5208	1-5246	1-5283	149	1-9273	1-9288	1-9303
50	0-8452	0-8505	0-8558	100	1-5321	1-5358	1-5395	150	1-9319	1-9333	1-9348

TABLE 21
CHORDS OF ANGLES

	0'	20'	40'		0'	20'	40'		0'	20'	40'
150	1.9319	1.9333	1.9348	160	1.9396	1.9706	1.9716	170	1.9924	1.9929	1.9934
151	1.9363	1.9377	1.9392	161	1.9726	1.9735	1.9745	171	1.9938	1.9943	1.9947
152	1.9406	1.9420	1.9434	162	1.9754	1.9763	1.9772	172	1.9951	1.9955	1.9959
153	1.9447	1.9461	1.9474	163	1.9780	1.9789	1.9797	173	1.9963	1.9966	1.9969
154	1.9487	1.9500	1.9513	164	1.9805	1.9813	1.9821	174	1.9973	1.9976	1.9978
155	1.9526	1.9538	1.9551	165	1.9829	1.9836	1.9844	175	1.9981	1.9983	1.9986
156	1.9563	1.9575	1.9587	166	1.9851	1.9858	1.9865	176	1.9988	1.9990	1.9992
157	1.9598	1.9610	1.9621	167	1.9871	1.9878	1.9884	177	1.9993	1.9995	1.9996
158	1.9633	1.9644	1.9654	168	1.9890	1.9896	1.9902	178	1.9997	1.9998	1.9999
159	1.9665	1.9676	1.9686	169	1.9908	1.9913	1.9919	179	1.9999	2.0000	2.0000
160	1.9696	1.9706	1.9716	170	1.9924	1.9929	1.9934	180	2.0000	2.0000	2.0000

TABLE 22
USEFUL NUMBERS
with their logarithms to base 10

WEIGHTS AND MEASURES

1 metre	= 39.370113 inches	<i>logarithm</i>	1.59517
	= 3.280843 feet		0.51599
	= 1.0936 yards		0.03886
1 Kilometre	= 0.62137 miles		$\bar{1}$.79335
1 (metre) ³	= 10.7639 (feet) ³		1.03197
	= 1.196 (yards) ³		0.07773
1 (Kilometre) ³	= 0.2861 (miles) ³		$\bar{1}$.58670
1 hectare	= 2.47106 acres		0.39288
1 (metre) ³	= 1.308 (yards) ³		0.11659
1 litre	= 61.0239 (inches) ³		1.78550
	= 1.76 pints		0.24546
	= 0.22 gallons		$\bar{1}$.34237
1 gram	= 15.43236 grains		1.18843
	= 0.03527 oz. (avoir.)		$\bar{2}$.54740
1 Kilogram	= 2.20462 pounds		0.34333
<hr/>			
1 inch	= 2.5400 centimetres	<i>logarithm</i>	0.40483
1 foot	= 30.4800 centimetres		1.48401
1 yard	= 0.9144 metres		$\bar{1}$.96114
1 mile	= 1.6093 Kilometres		0.20665
1 (inch) ³	= 6.4516 (centimetres) ³		0.80967
1 (yard) ³	= 0.8361 (metres) ³		$\bar{1}$.92227
1 (mile) ³	= 2.59 (Kilometres) ³		0.41330
1 acre	= 0.4047 hectares		$\bar{1}$.69712
1 (yard) ³	= 0.7646 (metres) ³		1.88341
1 (inch) ³	= 16.387 (centimetres) ³		1.21450
1 pint	= 0.568 litres		$\bar{1}$.75454
1 gallon	= 4.546 litres		0.65763
1 grain	= 0.0648 grams		$\bar{2}$.81157
1 ounce (avoir.)	= 28.350 grams		1.45255
1 pound	= 0.4536 Kilograms		$\bar{1}$.65667
<hr/>			
1 radian	= $180/\pi$ degrees	<i>logarithm</i>	1.75812
	= 57.2958°		
	= 57° 17' 44.8"		

TABLE 22
MATHEMATICAL CONSTANTS



π	$= 3.14159265$	<i>logarithm</i>	0.49715
	$\approx \frac{22}{7}$		
π^{-1}	$= 0.318310$	$\bar{1}$.	50285
$\frac{1}{2}\pi$	$= 1.57080$		0.19612
$\frac{1}{4}\pi$	$= 0.78540$	$\bar{1}$.	89509
$\frac{\pi}{180}$	$= 0.01745$	$\bar{2}$.	24188
$\pi^{\frac{1}{2}}$	$= 1.77245$		0.24857
$\pi^{-\frac{1}{2}}$	$= 0.56419$	$\bar{1}$.	75143
$\pi^{\frac{2}{3}}$	$= 9.86960$		0.99430
$\pi^{-\frac{2}{3}}$	$= 0.10132$	$\bar{1}$.	00570
<hr/>			
e	$= 2.7182818$	<i>logarithm</i>	0.43429
$\log_e 10$	$= 2.3025851$		—
$e^{\frac{1}{2}}$	$= 4.8105$		0.68219
e^{-1}	$= 0.36788$	$\bar{1}$.	56571

For powers of e , see Tables on p. 790–793.

DYNAMIC CONSTANTS

g	$= 32.2 \text{ ft.}/(\text{sec.})^2$	<i>logarithm</i>	1.50786
	$= 981 \text{ cm.}/(\text{sec.})^2$		2.99167
1 lb.-wt.	$= 4.45 \times 10^6 \text{ dynes}$		5.64836
1 ft.-lb.	$= 0.1383 \text{ Kg.-m.}$	$\bar{1}$.	14068
	$= 1.356 \times 10^7 \text{ ergs}$		7.13245
1 erg	$= 7.371 \times 10^{-8} \text{ ft.-lb.}$	$\bar{8}$.	86755
1 dyne	$= 2.247 \times 10^{-6} \text{ lb.-wt.}$	$\bar{6}$.	35164
1 Kg.-m.	$= 7.233 \text{ ft.-lb.}$		0.85932
<hr/>			
1 atmosphere of pressure	$= 1.014 \times 10^6 \text{ dynes}/(\text{cm.})^2$	<i>logarithm</i>	6.00604
	$= 14.7 \text{ lb.-wt.}/(\text{in.})^2$		1.16732
	$= 1.034 \text{ Kg.-wt.}/(\text{cm.})^2$		0.01437
1 lb.-wt./(\text{in.}) ²	$= 70.31 \text{ gram-wt.}/(\text{cm.})^2$		1.84700
1 Kg.-wt./(\text{cm.}) ²	$= 14.223 \text{ lb.-wt.}/(\text{in.})^2$		1.15300

TABLE 23
COMPARATIVE TABLE OF CIRCULAR AND HYPERBOLIC RELATIONSHIPS

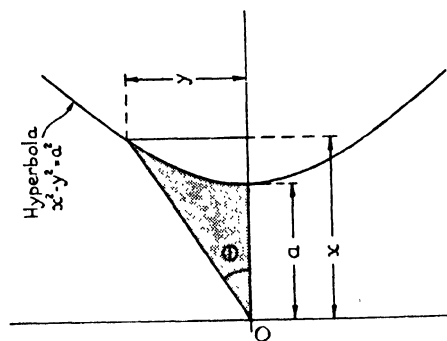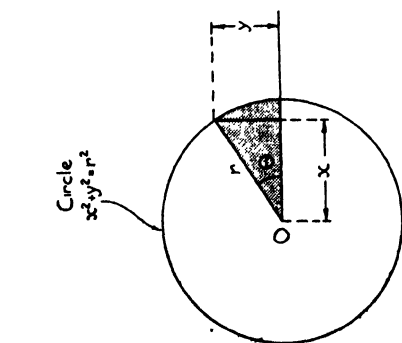

$$\theta = \frac{2 \times \text{area of sector}}{a^2} \quad \text{"hyperbolic radians"}$$

$$\begin{aligned} \sinh \theta &= \frac{y}{a} = \frac{e^\theta - e^{-\theta}}{2} = -\sinh(-\theta) \\ &= \theta + \frac{\theta^3}{3} + \frac{\theta^5}{5} + \frac{\theta^7}{7} + \dots \\ &= -j \sin j\theta \end{aligned}$$

$$\theta = \frac{2 \times \text{area of sector}}{r^2} \quad \text{radians}$$

$$\begin{aligned} \sin \theta &= \frac{y}{r} = \frac{e^{j\theta} - e^{-j\theta}}{2j} = -\sin(-\theta) \\ &= \theta - \frac{\theta^3}{3} + \frac{\theta^5}{5} - \frac{\theta^7}{7} + \dots \\ &= -j \sinh \theta = \cos\left(\frac{\pi}{2} - \theta\right) \end{aligned}$$

TABLE 23—continued

$\cosh \theta = \frac{x}{a} = \frac{e^{\theta} + e^{-\theta}}{2} = \cosh(-\theta) = \cosh j\theta$ $= 1 + \frac{\theta^2}{2!} + \frac{\theta^4}{4!} + \frac{\theta^6}{6!} + \dots$ $\tanh \theta = \frac{y}{x} = \frac{e^{\theta} - e^{-\theta}}{e^{\theta} + e^{-\theta}} = -\tanh(-\theta) = -j \tanh j\theta$	$\cosh \theta = \frac{x}{a} = \frac{e^{\theta} + e^{-\theta}}{2} = \cosh(-\theta) = \cosh j\theta$ $= 1 + \frac{\theta^2}{2!} + \frac{\theta^4}{4!} + \frac{\theta^6}{6!} + \dots$ $\tanh \theta = \frac{y}{x} = \frac{e^{\theta} - e^{-\theta}}{e^{\theta} + e^{-\theta}} = -\tanh(-\theta) = -j \tanh j\theta$
$\sin j\theta = j \sinh \theta$ $\cos j\theta = \cosh \theta$ $\tan j\theta = j \tanh \theta$	$\sinh j\theta = j \sin \theta$ $\cosh j\theta = \cos \theta$ $\tanh j\theta = j \tan \theta$
$\sin \frac{1}{2}\theta = \sqrt{\frac{1}{2}(1 - \cos \theta)}$ $\cos \frac{1}{2}\theta = \sqrt{\frac{1}{2}(1 + \cos \theta)}$ $\tan \frac{1}{2}\theta = \frac{\sin \theta}{1 + \cos \theta}$	$\sinh \frac{1}{2}\theta = \sqrt{\frac{1}{2}(\cosh \theta - 1)}$ $\cosh \frac{1}{2}\theta = \sqrt{\frac{1}{2}(\cosh \theta + 1)}$ $\tanh \frac{1}{2}\theta = \frac{\sinh \theta}{\cosh \theta - 1} = \frac{\sinh \theta}{\cosh \theta + 1}$
$\sin 2\theta = 2 \cdot \cos \theta \cdot \sin \theta$ $\cos 2\theta = \cos^2 \theta - \sin^2 \theta$ $\tan 2\theta = \frac{2 \tan \theta}{1 - \tan^2 \theta}$	$\sinh 2\theta = 2 \cdot \cosh \theta \cdot \sinh \theta$ $\cosh 2\theta = \cosh^2 \theta + \sinh^2 \theta$ $\tanh 2\theta = \frac{2 \tanh \theta}{1 + \tanh^2 \theta}$
$1 = \cos^2 \theta + \sin^2 \theta = \sec^2 \theta - \tan^2 \theta = \operatorname{cosec}^2 \theta - \cot^2 \theta$ $\cos \theta \pm \sin \theta = \sqrt{1 \pm \sin 2\theta}$	$1 = \cosh^2 \theta - \sinh^2 \theta = \operatorname{sech}^2 \theta + \tanh^2 \theta = \operatorname{coth}^2 \theta - \operatorname{cosech}^2 \theta$ $\cosh \theta \pm \sinh \theta = \sqrt{\cosh 2\theta \pm \sinh 2\theta} = e^{\pm \theta}$
$\sin^2 \theta = \frac{1 - \cos^2 \theta}{1 + \cos 2\theta} = \frac{1}{2}(1 - \cos 2\theta)$ $\cos^2 \theta = \frac{1 + \sin^2 \theta}{1 - \cos 2\theta} = \frac{1}{2}(1 + \cos 2\theta)$ $\tan^2 \theta = \frac{1 - \cos 2\theta}{1 + \cos 2\theta}$	$\sinh^2 \theta = \frac{\cosh^2 \theta - 1}{\cosh 2\theta - 1} = \frac{1}{2}(\cosh 2\theta - 1)$ $\cosh^2 \theta = \frac{\sinh^2 \theta + 1}{\cosh 2\theta + 1} = \frac{1}{2}(\cosh 2\theta + 1)$ $\tanh^2 \theta = \frac{\cosh 2\theta - 1}{\cosh 2\theta + 1}$
$a \cdot \sin \theta \pm b \cdot \cos \theta = \sqrt{a^2 + b^2} \sin \left(\theta \pm \tan^{-1} \frac{b}{a} \right)$ $= \pm \sqrt{a^2 + b^2} \cos \left(\theta \mp \tan^{-1} \frac{a}{b} \right)$	$a \cdot \sinh \theta \pm b \cdot \cosh \theta = \sqrt{a^2 - b^2} \sinh \left(\theta \pm \tanh^{-1} \frac{b}{a} \right)$ $= \pm \sqrt{b^2 - a^2} \cosh \left(\theta \pm \tanh^{-1} \frac{a}{b} \right)$

(continued on page 824)

TABLE 23—continued

$\sin(A \pm B) = \sin A \cos B \pm \cos A \sin B$ $\cos(A \pm B) = \cos A \cos B \mp \sin A \sin B$ $\tan(A \pm B) = \frac{\tan A \pm \tan B}{1 \mp \tan A \tan B}$ $\cot(A \pm B) = \frac{\cot A \cot B \mp 1}{\cot B \pm \cot A} = \frac{1 \mp \tan A \tan B}{\tan A \pm \tan B}$	$\sin(A \pm B) = \sinh A \cosh B \pm \cosh A \sinh B$ $\cosh(A \pm B) = \cosh A \cosh B \pm \sinh A \sinh B$ $\tanh(A \pm B) = \frac{\tanh A \pm \tanh B}{1 \pm \tanh A \tanh B}$ $\coth(A \pm B) = \frac{\coth A \coth B \pm 1}{\coth B \pm \coth A} = \frac{1 \pm \tanh A \tanh B}{\tanh A \pm \tanh B}$
$\sin(A + B) + \sin(A - B) = 2 \sin A \cos B$ $\sin(A + B) - \sin(A - B) = 2 \cos A \sin B$ $\cos(A + B) + \cos(A - B) = 2 \cos A \cos B$ $\cos(A + B) - \cos(A - B) = -2 \sin A \sin B$ $\tan(A + B) + \tan(A - B) = \frac{\cos 2A + \cos 2B}{2 \sin 2B}$ $\tan(A + B) - \tan(A - B) = \frac{\cos 2A + \cos 2B}{-2 \sin 2A}$ $\cot(A + B) + \cot(A - B) = \frac{-2 \sin 2A}{\cos 2A - \cos 2B}$ $\cot(A + B) - \cot(A - B) = \frac{2 \sin 2B}{\cos 2A - \cos 2B}$	$\sinh(A + B) + \sinh(A - B) = 2 \sinh A \cosh B$ $\sinh(A + B) - \sinh(A - B) = 2 \cosh A \sinh B$ $\cosh(A + B) + \cosh(A - B) = 2 \cosh A \cosh B$ $\cosh(A + B) - \cosh(A - B) = 2 \sinh A \sinh B$ $\tanh(A + B) + \tanh(A - B) = \frac{\cosh 2A + \cosh 2B}{2 \sinh 2A}$ $\tanh(A + B) - \tanh(A - B) = \frac{\cosh 2A + \cosh 2B}{-2 \sinh 2B}$ $\coth(A + B) + \coth(A - B) = \frac{\cosh 2A - \cosh 2B}{-2 \sinh 2B}$ $\coth(A + B) - \coth(A - B) = \frac{\cosh 2A - \cosh 2B}{2 \sinh 2A}$
$\sin A + \sin B = 2 \sin \frac{1}{2}(A + B) \cos \frac{1}{2}(A - B)$ $\sin A - \sin B = 2 \cos \frac{1}{2}(A + B) \sin \frac{1}{2}(A - B)$ $\cos A + \cos B = 2 \cos \frac{1}{2}(A + B) \cos \frac{1}{2}(A - B)$ $\cos A - \cos B = -2 \sin \frac{1}{2}(A + B) \sin \frac{1}{2}(A - B)$ $\tan A \pm \tan B = \frac{\sin(A \pm B)}{\cos A \cos B}$ $\cot A \pm \cot B = \frac{-\sin(A \pm B)}{\sin A \sin B}$	$\sinh A + \sinh B = 2 \sinh \frac{1}{2}(A + B) \cosh \frac{1}{2}(A - B)$ $\sinh A - \sinh B = 2 \cosh \frac{1}{2}(A + B) \sinh \frac{1}{2}(A - B)$ $\cosh A + \cosh B = 2 \cosh \frac{1}{2}(A + B) \cosh \frac{1}{2}(A - B)$ $\cosh A - \cosh B = 2 \sinh \frac{1}{2}(A + B) \sinh \frac{1}{2}(A - B)$ $\tanh A \pm \tanh B = \frac{\sinh(A \pm B)}{\cosh A \cosh B}$ $\coth A \pm \coth B = \frac{-\sinh(A \pm B)}{\sinh A \sinh B}$
$\sin^2 A + \sin^2 B = 1 - \cos(A + B) \cos(A - B)$ $\sin^2 A - \sin^2 B = \sin(A + B) \sin(A - B)$ $\cos^2 A + \sin^2 B = 1 - \sin(A + B) \sin(A - B)$ $\cos^2 A - \sin^2 B = \cos(A + B) \cos(A - B)$ $\cos^2 A + \cos^2 B = 1 + \cos(A + B) \cos(A - B)$ $\cos^2 A - \cos^2 B = -\sin(A + B) \sin(A - B)$	$\sinh^2 A + \sinh^2 B = 1 + \cosh(A + B) \cosh(A - B)$ $\sinh^2 A - \sinh^2 B = \sinh(A + B) \sinh(A - B)$ $\cosh^2 A + \sinh^2 B = \cosh(A + B) \cosh(A - B)$ $\cosh^2 A - \sinh^2 B = 1 + \sinh(A + B) \sinh(A - B)$ $\cosh^2 A + \cosh^2 B = 1 + \cosh(A + B) \cosh(A - B)$ $\cosh^2 A - \cosh^2 B = \sinh(A + B) \sinh(A - B)$

COMPLEX HYPERBOLIC IDENTITIES*

$$\begin{array}{ll} \sinh(\theta \pm j2n\pi) = \sinh \theta & \sinh(\theta \pm j\frac{\pi}{2}) = \pm j \cosh \theta \\ \cosh(\theta \pm j2n\pi) = \cosh \theta & \cosh(\theta \pm j\frac{\pi}{2}) = \pm j \sinh \theta \\ \tanh(\theta \pm jn\pi) = \tanh \theta & \tanh(\theta \pm j\frac{\pi}{2}) = \coth \theta \end{array}$$

$$\begin{aligned} \sinh(\alpha \pm j\beta) &= \sinh \alpha \cos \beta \pm j \cosh \alpha \sin \beta \\ &= \sqrt{\sinh^2 \alpha + \sin^2 \beta} / \pm \tan^{-1}(\coth \alpha \cdot \tan \beta) \\ &= \sqrt{\cosh^2 \alpha - \cos^2 \beta} / \pm \tan^{-1}(\coth \alpha \cdot \tan \beta) \end{aligned}$$

$$\begin{aligned} \cosh(\alpha \pm j\beta) &= \cosh \alpha \cos \beta \pm j \sinh \alpha \sin \beta \\ &= \sqrt{\sinh^2 \alpha + \cos^2 \beta} / \pm \tan^{-1}(\tanh \alpha \cdot \tan \beta) \\ &= \sqrt{\cosh^2 \alpha - \sin^2 \beta} / \pm \tan^{-1}(\tanh \alpha \cdot \tan \beta) \end{aligned}$$

$$\tanh(\alpha \pm j\beta) = \frac{\sinh 2\alpha \pm j \sin 2\beta}{\cosh 2\alpha + \cos 2\beta}$$

If $\sinh(\alpha + j\beta) = A + jB$

Then $\alpha = \cosh^{-1} \left\{ \frac{\sqrt{(1+B)^2 + A^2} + \sqrt{(1-B)^2 + A^2}}{2} \right\}$

and $\beta = \sin^{-1} \left\{ \frac{\sqrt{(1+B)^2 + A^2} - \sqrt{(1-B)^2 + A^2}}{2} \right\}$

If $\cosh(\alpha + j\beta) = A + jB$

Then $\alpha = \cosh^{-1} \left\{ \frac{\sqrt{(1+A)^2 + B^2} + \sqrt{(1-A)^2 + B^2}}{2} \right\}$

and $\beta = \cos^{-1} \left\{ \frac{\sqrt{(1+A)^2 + B^2} - \sqrt{(1-A)^2 + B^2}}{2} \right\}$

If $\tanh(\alpha + j\beta) = A + jB$

Then $\alpha = \frac{1}{2} \log_e \left\{ \frac{(1+A)^2 + B^2}{(1-A)^2 + B^2} \right\}$
 $= \frac{1}{2} \tanh^{-1} \left\{ \frac{2A}{1+A^2+B^2} \right\}$

and $\beta = \frac{\pi}{2} - \frac{1}{2} \tan^{-1} \left\{ \frac{A+1}{B} \right\} + \frac{1}{2} \tan^{-1} \left\{ \frac{A-1}{B} \right\}$
 $= \frac{1}{2} \tan^{-1} \left\{ \frac{2B}{1-(A^2+B^2)} \right\}$

* See also Graphical Calculators—Appendix II

COMMON DERIVATIVES AND INTEGRALS

y	$\frac{dy}{dx}$	$\int y dx$
C	0	$Cx + D$
$a \cdot f(x)$	$a \cdot \frac{d}{dx} f(x)$	$a \cdot \int f(x) dx$
x^n	nx^{n-1}	$\frac{1}{n+1} x^{n+1}$ when $n \neq -1$
x^{-1}	$-x^{-2}$	$\log_e x$
e^{ax}	ae^{ax}	$\frac{1}{a} e^{ax}$
$x \cdot e^x$	$e^x (x+1)$	$e^x (x-1)$
a^x	$a^x \log_e a$	$a^x / \log_e a$
$\log_e x$	x^{-1}	$x (\log_e x - 1)$
$\log_a x$	$\frac{1}{x} \log_a e$	$x \log_a \left(\frac{x}{e}\right)$
$u \cdot v$	$v \cdot du + u \cdot dv$	$u \int v \cdot dx - \int \left(\int v \cdot dx \right) du$
$\frac{u}{v}$	$\frac{v \cdot du - u \cdot dv}{v^2}$	$u \int \frac{1}{v} \cdot dx - \int \left(\int \frac{1}{v} dx \right) du$
$\sin ax$	$a \cos ax$	$-\frac{1}{a} \cos ax$
$\cos ax$	$-a \sin ax$	$+\frac{1}{a} \sin ax$
$\tan ax$	$a \sec^2 ax$	$-\frac{1}{a} \log_e \cos ax$
$\sin^{-1} \frac{x}{a}$	$\frac{1}{\sqrt{a^2 - x^2}}$	$x \cdot \sin^{-1} \frac{x}{a} + \sqrt{a^2 - x^2}$
$\cos^{-1} \frac{x}{a}$	$\frac{-1}{\sqrt{a^2 - x^2}}$	$x \cdot \cos^{-1} \frac{x}{a} - \sqrt{a^2 - x^2}$
$\tan^{-1} \frac{x}{a}$	$\frac{a}{a^2 + x^2}$	$x \cdot \tan^{-1} \frac{x}{a} - \frac{1}{a} \log_e \sqrt{a^2 + x^2}$
$\sinh ax$	$a \cosh ax$	$\frac{1}{a} \cosh ax$
$\cosh ax$	$a \sinh ax$	$\frac{1}{a} \sinh ax$
$\tanh ax$	$a \operatorname{sech}^2 ax$	$\frac{1}{a} \log_e \cosh ax$

y	$\frac{dy}{dx}$	$\int y dx$
$\sinh^{-1} \frac{x}{a}$	$\frac{1}{\sqrt{a^2 + x^2}}$	$x \cdot \sinh^{-1} \frac{x}{a} - \sqrt{x^2 + a^2}$
$\cosh^{-1} \frac{x}{a}$	$\frac{1}{\sqrt{x^2 - a^2}}$	$x \cdot \cosh^{-1} \frac{x}{a} - \sqrt{x^2 - a^2}$
$\tanh^{-1} \frac{x}{a}$	$\frac{a}{a^2 - x^2}$	$x \cdot \tanh^{-1} \frac{x}{a} + a \cdot \log_e \sqrt{a^2 - x^2}$
$\frac{1}{\sin x}$	$-\frac{\cos x}{\sin^2 x}$	$\log_e \tan \frac{x}{2}$
$\frac{1}{\cos x}$	$+\frac{\sin x}{\cos^2 x}$	$\log_e \tan \left(\frac{x}{2} + \frac{\pi}{4} \right)$ $= \log_e (\tan x + \sec x)$
$\sin^2 ax$	$a \sin 2ax$	$\left(\frac{x}{2} - \frac{\sin ax \cos ax}{2a} \right) = \left(\frac{x}{2} - \frac{\sin 2ax}{4a} \right)$
$\cos^2 ax$	$-a \sin 2ax$	$\left(\frac{x}{2} + \frac{\sin ax \cos ax}{2a} \right) = \left(\frac{x}{2} + \frac{\sin 2ax}{4a} \right)$
$e^{\alpha x} \cdot \sin \beta x$		$\frac{\alpha \cdot e^{\alpha x} \cdot \sin \beta x - \beta \cdot e^{\alpha x} \cdot \cos \beta x}{\alpha^2 + \beta^2}$
$e^{\alpha x} \cdot \cos \beta x$		$\frac{\alpha \cdot e^{\alpha x} \cdot \cos \beta x + \beta \cdot e^{\alpha x} \cdot \sin \beta x}{\alpha^2 + \beta^2}$
$e^{\alpha x} \cdot \sinh \beta x$		$\frac{\alpha \cdot e^{\alpha x} \cdot \sinh \beta x - \beta \cdot e^{\alpha x} \cdot \cosh \beta x}{\alpha^2 - \beta^2}$
$e^{\alpha x} \cdot \cosh \beta x$		$\frac{\alpha \cdot e^{\alpha x} \cdot \cosh \beta x + \beta \cdot e^{\alpha x} \cdot \sinh \beta x}{\alpha^2 - \beta^2}$
$\sinh \alpha x \cdot \sin \beta x$		$\frac{\alpha \cdot \cosh \alpha x \cdot \sin \beta x - \beta \cdot \sinh \alpha x \cdot \cos \beta x}{\alpha^2 + \beta^2}$
$\cosh \alpha x \cdot \sin \beta x$		$\frac{\alpha \cdot \sinh \alpha x \cdot \sin \beta x - \beta \cdot \cosh \alpha x \cdot \cos \beta x}{\alpha^2 + \beta^2}$
$\sinh \alpha x \cdot \cos \beta x$		$\frac{\alpha \cdot \cosh \alpha x \cdot \cos \beta x + \beta \cdot \sinh \alpha x \cdot \sin \beta x}{\alpha^2 + \beta^2}$
$\cosh \alpha x \cdot \cos \beta x$		$\frac{\alpha \cdot \sinh \alpha x \cdot \cos \beta x + \beta \cdot \cosh \alpha x \cdot \sin \beta x}{\alpha^2 + \beta^2}$

GUIDES TO THE INTEGRATION OF AWKWARD EXPRESSIONS

1. Integration by parts.—A product $u \cdot v$ of two functions of x can be integrated as :—

$$\int u \cdot v \cdot dx = u \cdot \int v \cdot dx - \int (v \cdot dx) \cdot du$$

or $\int u \cdot dw = u \cdot w - \int w \cdot du$, where $w = \int v \cdot dx$.

2. Reduction to the form $\int \frac{1}{z} dz$.—When the numerator of a fraction is, or can be changed into, the differential coefficient of the denominator, then the integral is equal to log to base e of the denominator, e.g. :—

$$\int \frac{x \cdot dx}{x^2 + 1} = \frac{1}{2} \int \frac{2x \cdot dx}{x^2 + 1} = \frac{1}{2} \int \frac{d(x^2 + 1)}{(x^2 + 1)} = \frac{1}{2} \log_e (x^2 + 1) = \log_e \sqrt{x^2 + 1}$$

3. Reduction to the form $\int \frac{1}{z^n} dz$.—When the numerator of a fraction is, or can be changed into, the differential coefficient of a function, of which the denominator is a power, equate the function to z ; then

$$\int z^n dz = \frac{1}{n+1} z^{n+1} \text{ (provided } n \neq -1 \text{), e.g. :—}$$

$$\begin{aligned} \int \frac{x \cdot dx}{(x^2 - 1)^2} &= \frac{1}{2} \int \frac{2x \cdot dx}{(x^2 - 1)^2} = \frac{1}{2} \int (x^2 - 1)^{-2} d(x^2 - 1) = -\frac{1}{2} (x^2 - 1)^{-1} \\ &= \frac{-1}{2(x^2 - 1)} \end{aligned}$$

4. Very involved fractions will normally split up into “partial fractions”.

5. Trigonometrical or hyperbolic substitutions frequently facilitate the integration of expressions of the form : $1/(x^2 + bx + c)$.

Example 1.—

$$\int \frac{dx}{\sqrt{5 - 4x - x^2}} = \int \frac{dx}{\sqrt{3^2 - (x + 2)^2}}$$

Putting $(x + 2) = 3 \sin \theta$, $dx = 3 \cos \theta d\theta$

$$\begin{aligned} \int &= \int \frac{3 \cos \theta d\theta}{\sqrt{3^2 - 3^2 \sin^2 \theta}} = \int \frac{3 \cos \theta d\theta}{\sqrt{3^2(1 - \sin^2 \theta)}} = \int \frac{3 \cos \theta d\theta}{3 \cos \theta} \\ &= \int d\theta = \theta = \sin^{-1} \left(\frac{x + 2}{3} \right) \end{aligned}$$

Example 2.—

$$\int \frac{dx}{\sqrt{13 + 4x + x^2}} = \int \frac{dx}{\sqrt{3^2 + (x + 2)^2}}$$

Putting $(x + 2) = 3 \sinh \theta$, $dx = 3 \cosh \theta d\theta$

$$\begin{aligned} \int &= \int \frac{3 \cosh \theta d\theta}{\sqrt{3^2 + 3^2 \sinh^2 \theta}} = \int \frac{3 \cosh \theta d\theta}{\sqrt{3^2(1 + \sinh^2 \theta)}} = \int \frac{3 \cosh \theta d\theta}{3 \cosh \theta} \\ &= \int d\theta = \theta = \sinh^{-1} \left(\frac{x + 2}{3} \right) \end{aligned}$$

APPENDIX II

GRAPHICAL CALCULATORS

GRAPHICAL CALCULATOR FOR $\tanh(\alpha + j\beta)$

If the values of α and β are known, then the real and imaginary parts of the function $\tanh(\alpha + j\beta) \equiv A + jB$ may be determined, for $A \equiv \frac{\sinh 2\alpha}{\cosh 2\alpha + \cos 2\beta}$ and $B \equiv \frac{\sin 2\beta}{\cosh 2\alpha + \cos 2\beta}$. The converse problem, namely, to find α and β if A and B are known, involves the solution of the equations:—

$$A^2 + B^2 - 2A \cdot \coth 2\alpha + 1 = 0 \quad (1)$$

$$A^2 + B^2 + 2B \cdot \cot 2\beta - 1 = 0 \quad (2)$$

If, however, values of A and B are taken along rectangular axes, equation 1 represents a system of circles, one circle corresponding to every value of α . These circles have their centres on the A -axis, and are called a "system of co-axial circles". Equation 2 also represents a system of co-axial circles, one member of the system corresponding to every value of β , and the centres all lying on the B -axis. These two co-axial systems have the property, that every point in the $[A, B]$ plane is the intersection of one member of one system with one member of the other.

Fig. 765 shows these co-axial systems. The values of α and β are given in nepers (hyperbolic radians) and radians respectively. A conversion table of nepers to decibels is given on page 839, while a conversion table from radians to degrees is given on page 838. Fig. 765 gives the complete chart for all values of α above 0.1 neper, but it is too cramped to permit accuracy for values of α above about 0.4 nepers; for this reason, Fig. 766 and 767 are given, to show enlargements of the portion of Fig. 765 around the point $[A = 1, B = 0]$, for values of α from 0.4 to 0.8, and 0.8 to 2.0 nepers respectively.

Negative values of A have not been shown, since they do not occur in any applications of line transmission theory. Moreover, values of A greater than 10, and of B greater than 6, are not given. This means that values of α less than 0.1 neper cannot be read, but measurements below this value are unlikely to be encountered in practice.

To find A and B , given α and β

To find the values of A and B , given the values of α and β , one must look for the intersection of the appropriate " α " and " β " circles. The co-ordinates of this point of intersection are the associated values of A and B .

Example.—

Given that $\alpha = 0.2$ nepers, $\beta = 0.40\pi$, find $\tanh \gamma$ in rectangular form, where $\gamma = \alpha + j\beta$.

This can be determined from Fig. 765 by finding the intersection of the circle marked " $\alpha = 0.2$ " with that marked " $\beta = 0.4\pi$ ". This occurs at the point where $A = 1.51$ and $B = 2.16$. The result is therefore :—

$$\tanh \gamma = 1.51 + j.2.16. \quad \text{Ans.}$$

To find α and β , given A and B

Conversely, to find α and β , given A and B , one must reverse this process and find the point specified by the co-ordinates given (*i.e.*, by A and B); and then see which circles pass through this point (or interpolate between the circles).

Example 1.—

Given that $\tanh \gamma = 2.3 - j.0.6$, find γ in rectangular form, and hence α and β .

Reference to Fig. 765 shows that the point corresponding to $A = 2.3$, $B = -0.6$, lies within the outer rectangle, so that Fig. 766 is the most convenient chart. One must therefore find the point $A = 2.3$, $B = -0.6$ on Fig. 766, and see which circles pass through this point. The circle $\beta = 0.54\pi$ passes very near to the point, and the two nearest " α " circles are $\alpha = 0.40$ and $\alpha = 0.45$; by interpolating, the value of α is seen to be approximately 0.425. The value of γ is therefore :—

$$\gamma = 0.425 + j.0.54\pi$$

$$\text{whence } \alpha = 0.425 \text{ nepers} \equiv 3.69 \text{ db}$$

$$\text{and } \beta = \underline{\underline{97.2^\circ}} \text{ Ans.}$$

$$\tanh(\alpha + j\beta) = A + jB$$

Example 2.—

Open- and short-circuit impedance measurements were made on 4 miles of unloaded carrier quad at 1600 c/s ($\omega = 10^4$), giving :—

$$Z_{oc} = 185 \angle -60^\circ \text{ and } Z_{sc} = 190 \angle -6^\circ.$$

Find $|Z_o|$, φ , α , β , λ and v at this frequency, and calculate the primary constants of the line.

$$Z_o = \sqrt{Z_{oc} \cdot Z_{sc}} = \sqrt{185 \times 190} \angle \frac{-60^\circ - 6^\circ}{2} = 188 \angle -33^\circ$$

$$\therefore |Z_o| = 188 \text{ and } \varphi = -33^\circ \text{ Ans (i)}$$

$$\tanh \gamma l = \tanh(\alpha + j\beta)l = \sqrt{\frac{Z_{sc}}{Z_{oc}}} = \sqrt{\frac{190}{185}} \angle \frac{-6^\circ - (-60^\circ)}{2}$$

$$= 1.01 \angle 27^\circ = 1.01 \cos 27^\circ + j1.01 \sin 27^\circ$$

$$= 0.90 + j0.46$$

$$\text{i.e. } A = 0.90, \quad B = 0.46$$

Hence, using Fig. 766 :—

$$\alpha l = 0.71 \text{ nepers} = 6.2 \text{ db,}$$

$$\beta l = 0.256\pi = 0.80 \text{ radians} = 46^\circ.$$

Since $l = 4$, this gives :—

$$\alpha = 0.18 \text{ nepers per mile} = 1.55 \text{ db per mile. Ans (ii)}$$

$$\text{and } \beta = 0.2 \text{ radians per mile} = 11.5^\circ \text{ per mile. Ans (iii)}$$

$$\lambda = \frac{2\pi}{\beta} = 31.4 \text{ miles Ans (iv)}$$

$$v = \frac{\omega}{\beta} = 50,000 \text{ miles/sec Ans (v)}$$

$$\gamma = 0.18 + j0.2 = 0.268 \angle 48^\circ.$$

$$\therefore R + j\omega L = Z_o \gamma = 188 \cdot 0.268 \angle 48^\circ - 33^\circ = 50.3 \angle 15^\circ$$

$$\therefore R = 50.3 \cos 15^\circ = 48.6 \text{ ohms/mile Ans (vi)}$$

$$\omega L = 50.3 \sin 15^\circ = 13.15, \quad \therefore L = 1.32 \text{ mH/mile Ans (vii)}$$

$$\text{Also } G + j\omega C = \frac{\gamma}{Z_o} = \frac{0.268}{188} \angle 48^\circ - (-33^\circ) = 1.43 \cdot 10^{-3} \angle 81^\circ$$


$$\therefore G = 1.43 \cdot 10^{-3} \cos 81^\circ = 220 \text{ } \mu\text{mhos/mile Ans (viii)}$$

$$\omega C = 1.43 \cdot 10^{-3} \sin 81^\circ = 1.42 \cdot 10^{-3}, \quad \therefore C = 0.142 \text{ } \mu\text{F/mile Ans (ix)}$$

Note that small errors in measuring the angles of Z_{oc} and Z_{sc} will result in comparatively large errors in the value of G .

Fig. 765.—Graphical calculator for $\text{Tanh}(a + j\beta)$

Fig. 765a

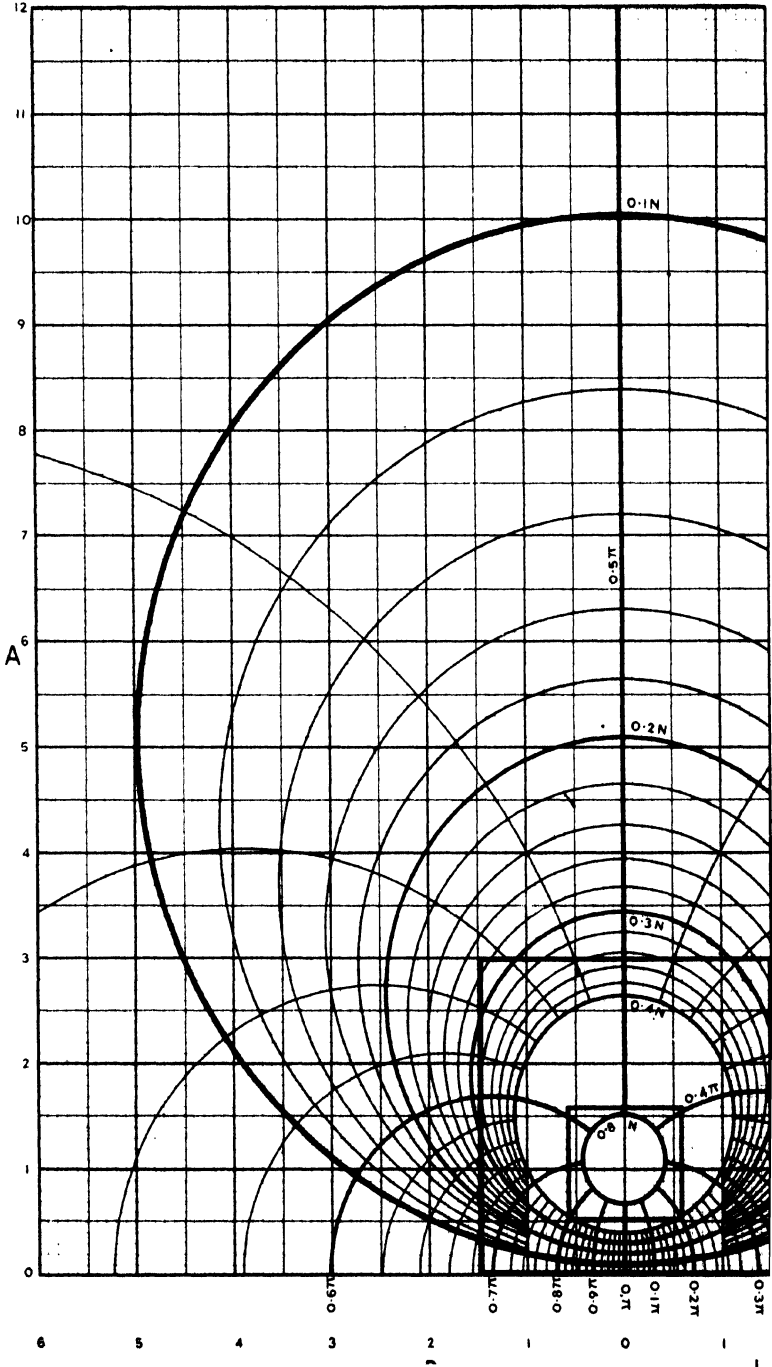

$\equiv A + jB$ for values of a from 0.1 to 0.4 nepers.

Fig. 765b

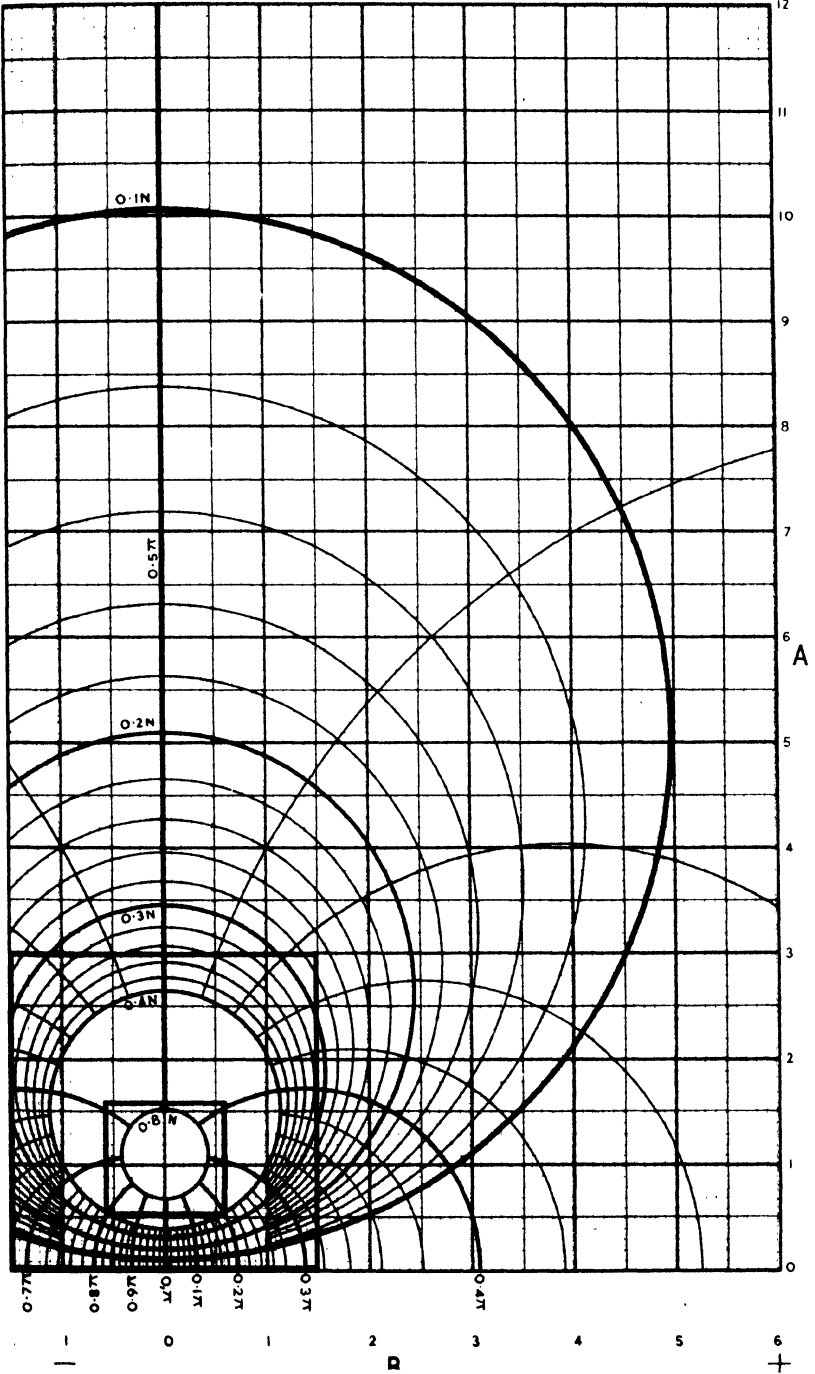


Fig. 766a

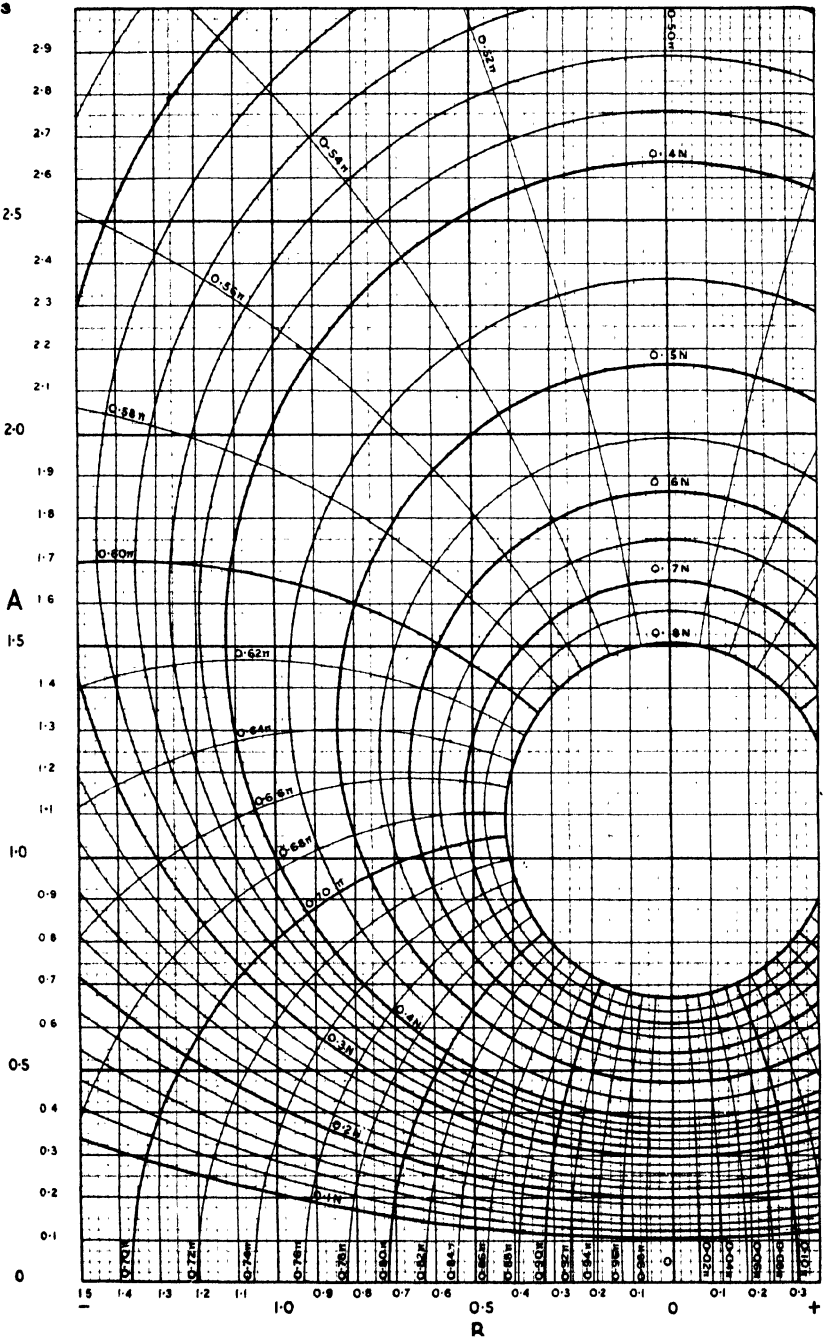


Fig. 766b


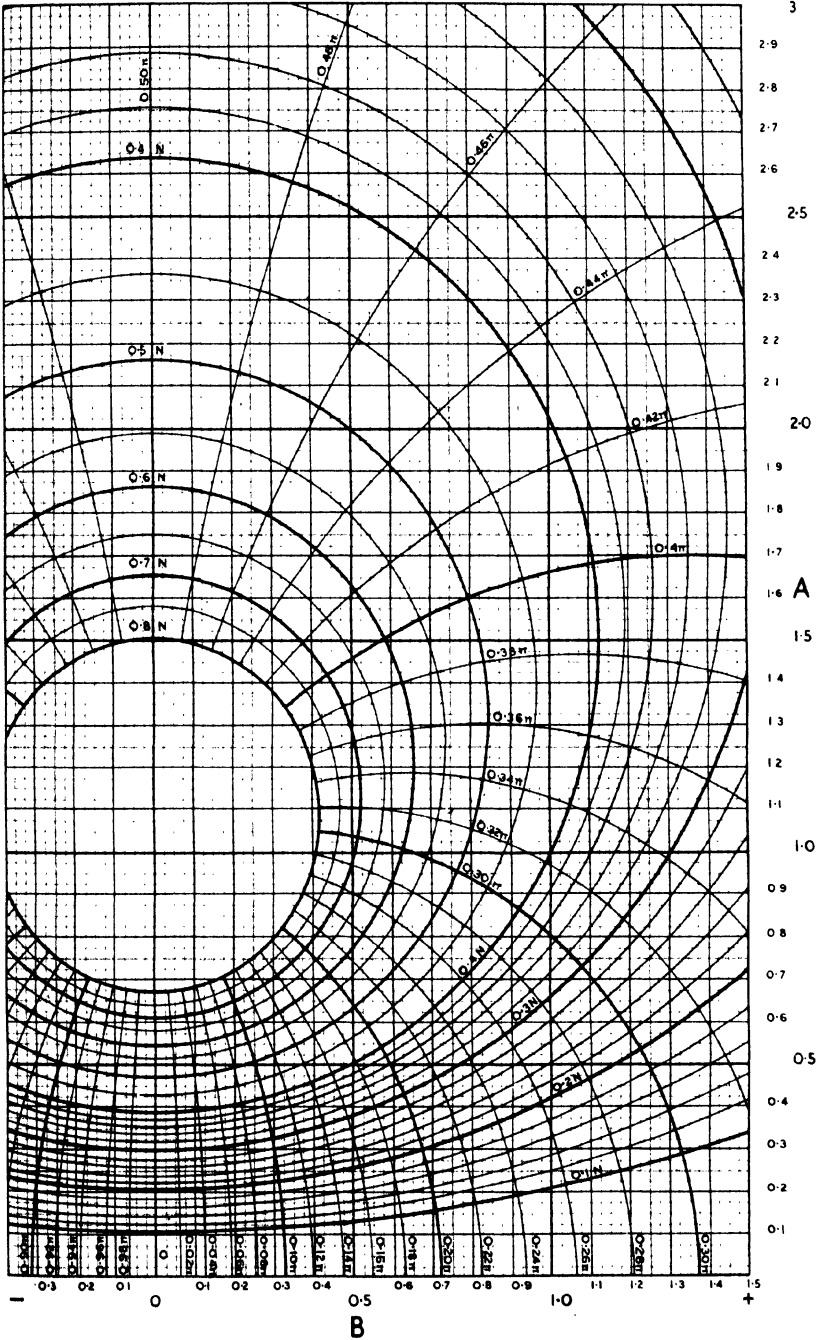


Fig. 767.—Graphical calculator for $\text{Tanh} (\alpha + \beta)$

Fig. 767a

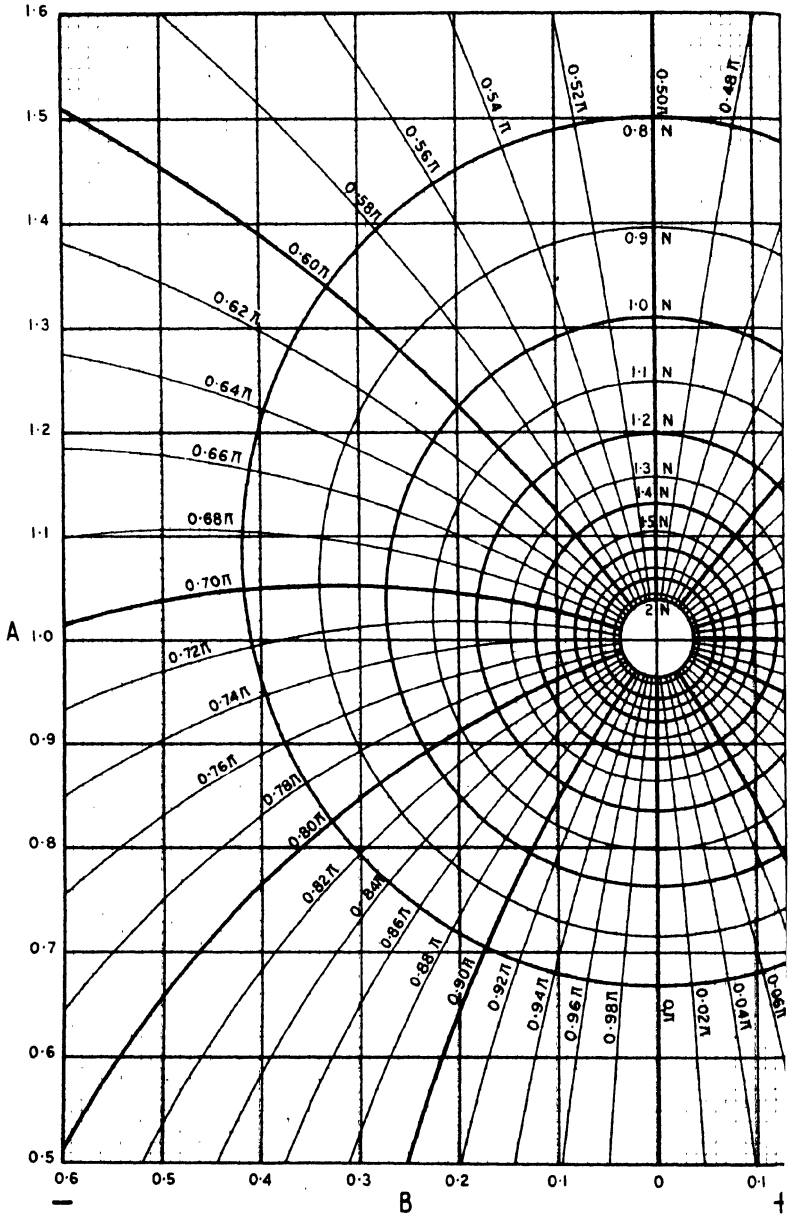

$\equiv A + jB$ for values of a from 0.8 to 2 nepers.

Fig. 767b

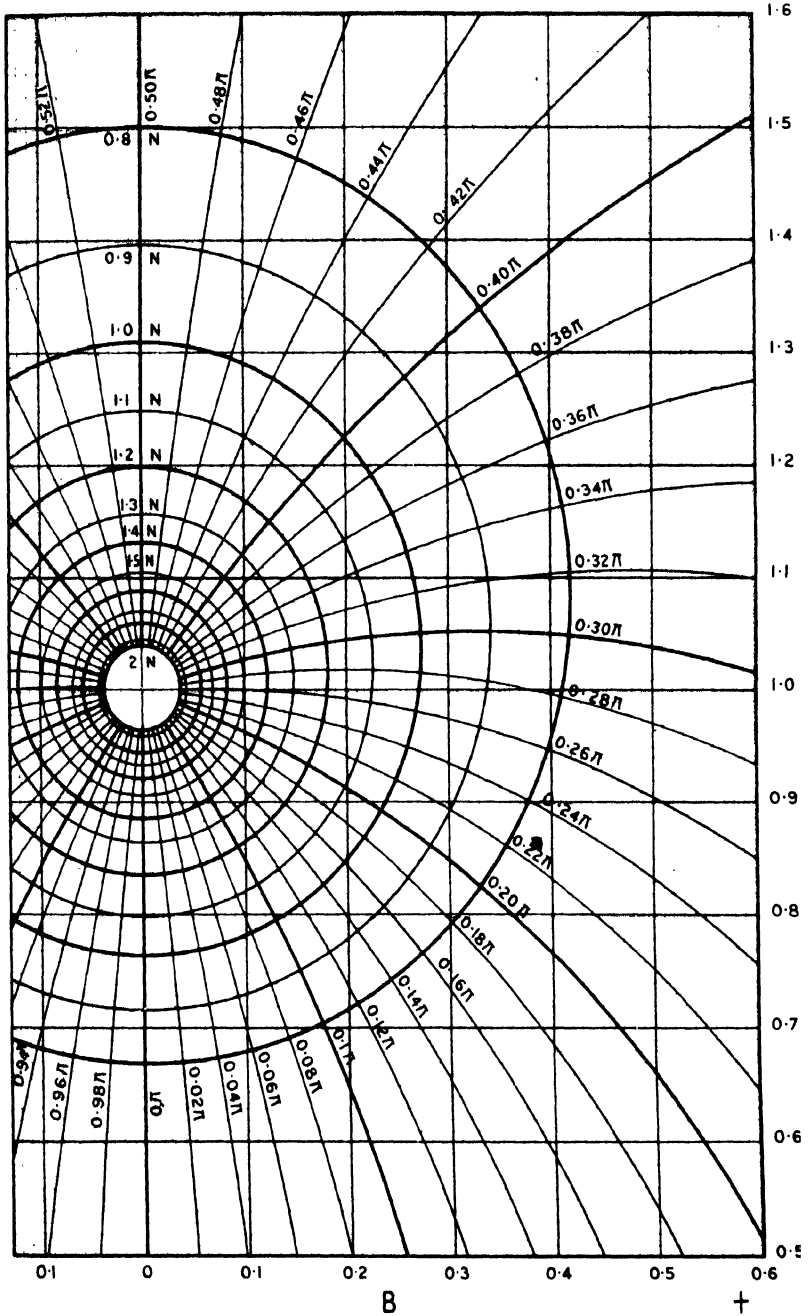


TABLE XXV

Table converting radians to degrees, for use with Figs. 765-767

Radians	Degrees	Radians	Degrees
$0.00.\pi = 0.0000$	0.0°	$0.50.\pi = 1.5708$	90.0°
$0.02.\pi = 0.0628$	3.6°	$0.52.\pi = 1.6336$	93.6°
$0.04.\pi = 0.1257$	7.2°	$0.54.\pi = 1.6965$	97.2°
$0.06.\pi = 0.1885$	10.8°	$0.56.\pi = 1.7593$	100.8°
$0.08.\pi = 0.2513$	14.4°	$0.58.\pi = 1.8221$	104.4°
$0.10.\pi = 0.3142$	18.0°	$0.60.\pi = 1.8850$	108.0°
$0.12.\pi = 0.3770$	21.6°	$0.62.\pi = 1.9478$	111.6°
$0.14.\pi = 0.4398$	23.2°	$0.64.\pi = 2.0106$	115.2°
$0.16.\pi = 0.5026$	28.8°	$0.66.\pi = 2.0734$	118.8°
$0.18.\pi = 0.5655$	32.4°	$0.68.\pi = 2.1363$	122.4°
$0.20.\pi = 0.6283$	36.0°	$0.70.\pi = 2.1991$	126.0°
$0.22.\pi = 0.6912$	39.6°	$0.72.\pi = 2.2619$	129.6°
$0.24.\pi = 0.7540$	43.2°	$0.74.\pi = 2.3248$	133.2°
$0.26.\pi = 0.8168$	46.8°	$0.76.\pi = 2.3876$	136.8°
$0.28.\pi = 0.8796$	50.4°	$0.78.\pi = 2.4504$	140.4°
$0.30.\pi = 0.9425$	54.0°	$0.80.\pi = 2.5133$	144.0°
$0.32.\pi = 1.0053$	57.6°	$0.82.\pi = 2.5761$	147.6°
$0.34.\pi = 1.0681$	61.2°	$0.84.\pi = 2.6389$	151.2°
$0.36.\pi = 1.1310$	64.8°	$0.86.\pi = 2.7018$	154.8°
$0.38.\pi = 1.1938$	68.4°	$0.88.\pi = 2.7646$	158.4°
$0.40.\pi = 1.2566$	72.0°	$0.90.\pi = 2.8274$	162.0°
$0.42.\pi = 1.3195$	75.6°	$0.92.\pi = 2.8903$	165.6°
$0.44.\pi = 1.3823$	79.2°	$0.94.\pi = 2.9531$	169.2°
$0.46.\pi = 1.4451$	82.8°	$0.96.\pi = 3.0159$	172.8°
$0.48.\pi = 1.5080$	86.4°	$0.98.\pi = 3.0788$	176.4°
$0.50.\pi = 1.5708$	90.0°	$1.00.\pi = 3.1416$	180.0°

TABLE XXVI
Conversion Table, Nepers to Decibels.

Nepers	.00	.01	.02	.03	.04	.05	.06	.07	.08	.09	1	2	3	4	5	6	7	8	9
0.0	0.0000	0869	1737	2606	3474	4343	5212	6080	6949	7817	87	174	261	347	434	521	608	695	782
0.1	0.8686	9554	0423	1292	2160	3029	3897	4766	5635	6503	87	174	261	347	434	521	608	695	782
0.2	1.7372	8340	9109	9977	0846	1715	2583	3452	4320	5189	87	174	261	347	434	521	608	695	782
0.3	2.6058	6926	7795	8663	9532	0401	1269	2138	3006	3875	87	174	261	347	434	521	608	695	782
0.4	3.4744	5612	6481	7351	8218	9087	9955	0824	1692	2561	87	174	261	347	434	521	608	695	782
0.5	4.3429	4298	5166	6035	6904	7772	8641	9510	0378	1247	87	174	261	347	434	521	608	695	782
0.6	5.2115	2984	3853	4721	5590	6458	7327	8195	9064	9933	87	174	261	347	434	521	608	695	782
0.7	6.0801	1670	2539	3407	4276	5144	6013	6881	7750	8619	87	174	261	347	434	521	608	695	782
0.8	6.9487	0356	1224	2093	2961	3830	4703	5587	6436	7304	87	174	261	347	434	521	608	695	782
0.9	7.8173	9042	9910	0779	1648	2516	3385	4253	5122	5990	87	174	261	347	434	521	608	695	782
1.0	8.6858	7727	8596	9465	0332	1202	2070	2939	3808	4676	87	174	261	347	434	521	608	695	782

TABLE XXVII
Conversion Table, Decibels to Nepers.

db	.0	.1	.2	.3	.4	.5	.6	.7	.8	.9	1	2	3	4	5	6	7	8	9
0	0.0000	0115	0230	0345	0461	0576	0691	0806	0921	1036	11	23	34	46	58	69	81	92	104
1	0.1151	1266	1382	1497	1612	1727	1842	1957	2072	2187	11	23	34	46	58	69	81	92	104
2	0.2303	2418	2533	2648	2763	2878	2993	3108	3224	3339	11	23	34	46	58	69	81	92	104
3	0.3454	3569	3684	3799	3914	4030	4145	4260	4375	4490	11	23	34	46	58	69	81	92	104
4	0.4605	4720	4835	4951	5066	5181	5296	5411	5526	5641	11	23	34	46	58	69	81	92	104
5	0.5756	5872	5987	6102	6217	6332	6447	6562	6678	6793	11	23	34	46	58	69	81	92	104
6	0.6908	7023	7138	7253	7368	7483	7598	7714	7829	7944	11	23	34	46	58	69	81	92	104
7	0.8059	8174	8289	8404	8520	8635	8750	8865	8980	9095	11	23	34	46	58	69	81	92	104
8	0.9210	9325	9441	9556	9671	9786	9901	0016	0134	0249	11	23	34	46	58	69	81	92	104
9	1.0362	0477	0592	0707	0822	0935	1052	1168	1283	1398	11	23	34	46	58	69	81	92	104
10	1.1513	1628	1743	1858	1973	2088	2204	2319	2434	2549	11	23	34	46	58	69	81	92	104

Values outside the range of the tables may be found by multiplication and division by 10,

e.g., 2.83 Nepers = 10 × 0.283 Nepers
 = 10 × (2.4320 + 0.0261) db
 = 10 × 2.4581 db
 = 24.581 db

GRAPHICAL CALCULATOR FOR $\cosh(\alpha + j\beta)$

If the values of α and β are known, then the real and imaginary parts of the function $\cosh(\alpha + j\beta) \equiv A + jB$ may readily be determined, for $A \equiv \cosh \alpha \cos \beta$, and $B \equiv \sinh \alpha \sin \beta$.

The converse problem, namely, to find α and β if A and B are known, is more difficult, involving the solution of the equations:—

$$\frac{A^2}{\cosh^2 \alpha} + \frac{B^2}{\sinh^2 \alpha} = 1 \quad (3)$$

and
$$\frac{A^2}{\cos^2 \beta} - \frac{B^2}{\sin^2 \beta} = 1 \quad (4)$$

If, however, values of A and B are taken along rectangular axes, equation 3 represents a family of ellipses, one corresponding to every value of α , and equation 4 represents a family of hyperbolae, one for every value of β . These curves are given in Fig. 768, where for convenience α has been expressed in db, and β in degrees. The two families form what is known as a "confocal system of conic sections", which has the important property that every point of the $[A, B]$ plane is the intersection of two curves—one ellipse (or α -curve) and one hyperbola (or β -curve). Thus, given A and B , one point in the plane is determined, and the associated values of α and β are those corresponding to the curves that intersect in that point. Conversely, if α and β are known, the two curves corresponding to these values intersect in a point whose co-ordinates are the associated values of A and B . *Values of α and β expressed in nepers and radians must be converted into db and degrees before Fig. 768 is used.*

Example.—

Find $\cosh(\alpha + j\beta)$, if $\alpha = 12$ db and $\beta = 10^\circ$.


Look for the intersection of the curves $\alpha = 12$ db and $\beta = 10^\circ$.

This gives the point whose co-ordinates are $A = 2.04$ and $B = 0.34$.

Hence $\cosh(\alpha + j\beta) = 2.04 + j0.34$. *Ans.*

An illustration is now given of the application of this diagram to network theory.

Fig. 768.—Graphical calculator for Cosh ($\alpha + j\beta$) $\equiv A + jB$, where α is expressed in db and β in degrees.

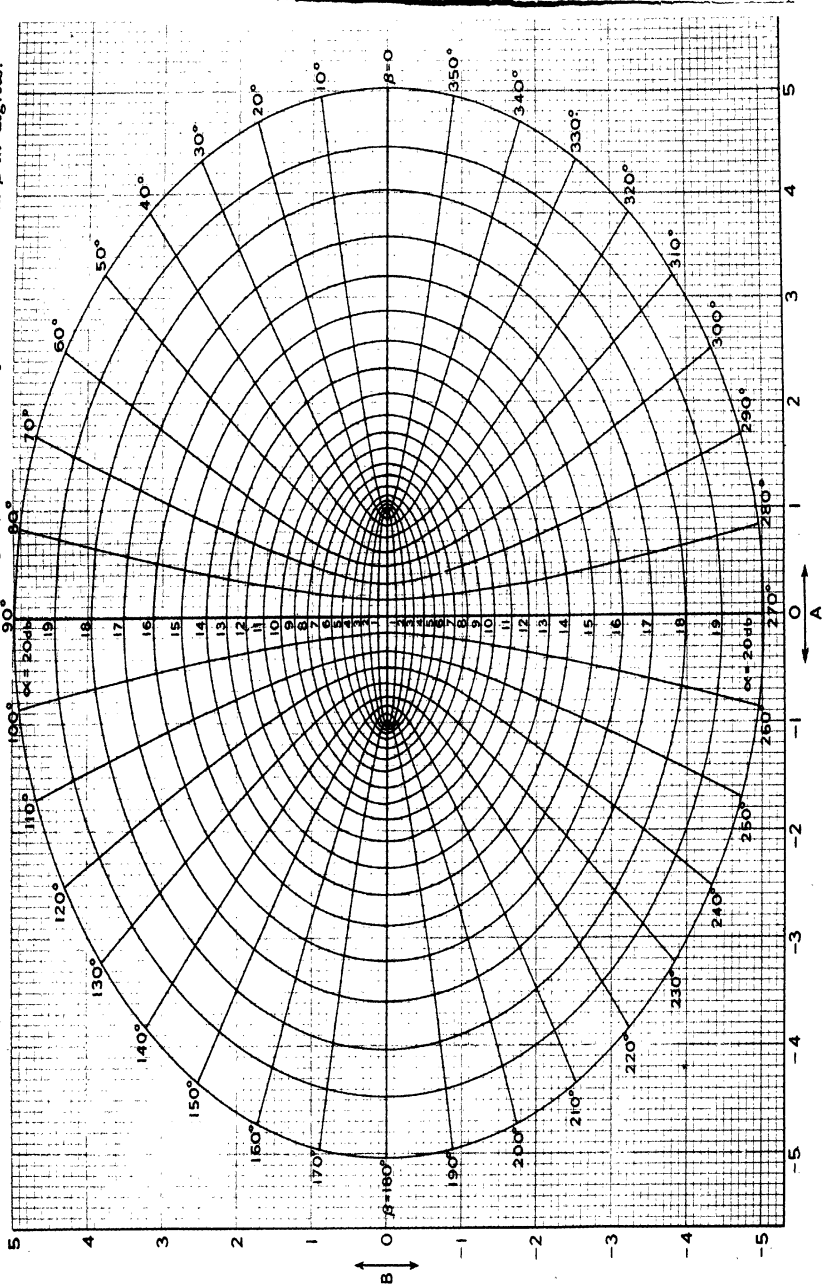

Example:—Find the attenuation and phase-shift of the network shown in Fig. 769 at 160 c/s ($\omega = 1000$).

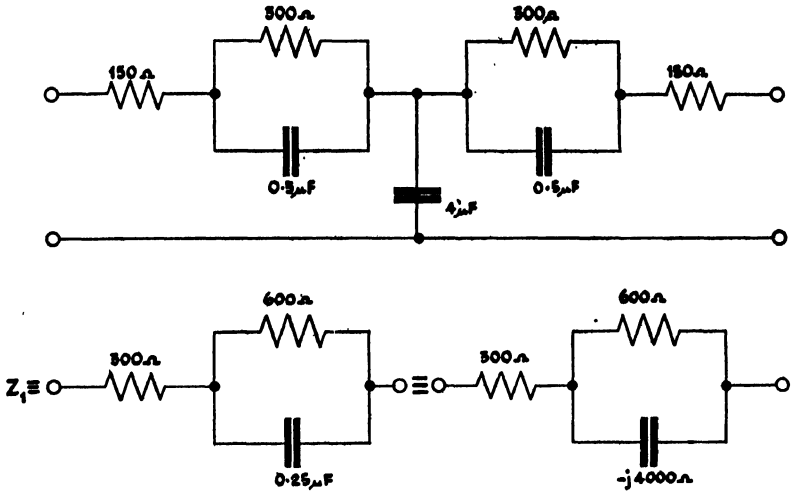


FIG. 769.

$$Z_1 = 300 - \frac{600 \times j4000}{600 - j4000} = 300 - \frac{j24000}{6 - j40}$$

Rationalising :—

$$\begin{aligned} Z_1 &= 300 - \frac{j24000(6 + j40)}{6^2 + 40^2} \\ &= 300 - 24000 \frac{(j6 - 40)}{1636} \\ &= 300 + 590 - j88 \\ &= 890 - j88 \end{aligned}$$

and

$$Z_2 = -j250$$

Now

$$\begin{aligned} \cosh \gamma &= 1 + \frac{Z_1}{2Z_2} \\ \therefore \cosh \gamma &= 1 + \frac{890 - j88}{-j500} = 1 + j1.78 + 0.176 \\ &= 1.176 + j1.78 \end{aligned}$$

This gives

$$\alpha = 12.8 \text{ db}, \beta = 59^\circ \text{ Ans.}$$

$$\text{Cosh } (\alpha + j\beta) = A + jB$$

If $\alpha > 20$ db, the point will lie outside the range of the diagram ; in such a case, an approximation can be made which gives α in nepers, viz. :—

$$\text{if } \alpha > 20 \text{ db, } \cosh \alpha \simeq \sqrt{A^2 + B^2} \text{ and } \tan \beta \simeq \frac{B}{A}.$$

Example.—Find α and β , if $\cosh (\alpha + j\beta) = 6.54 + j9.75$.

The point [$A = 6.54, B = 9.75$] lies outside the curve $\alpha = 20$ db, so that the approximation may be used :—

$$\cosh \alpha \simeq \sqrt{A^2 + B^2} = \sqrt{44 + 95} = \sqrt{139} = 11.8$$

$$\text{giving } \alpha \simeq 3.16 \text{ nepers} \equiv 27.5 \text{ db}$$

$$\text{and } \tan \beta \simeq \frac{B}{A} = \frac{9.75}{6.54} = 1.49$$

$$\text{giving } \beta \simeq 56^\circ. \text{ Ans.}$$

SUPPLEMENT

VOLUME 1

GRAPHICAL CALCULATORS

Graphical calculator for Sinh ($\alpha + j\beta$) = $A + jB$, where α is expressed in db and β in degrees.

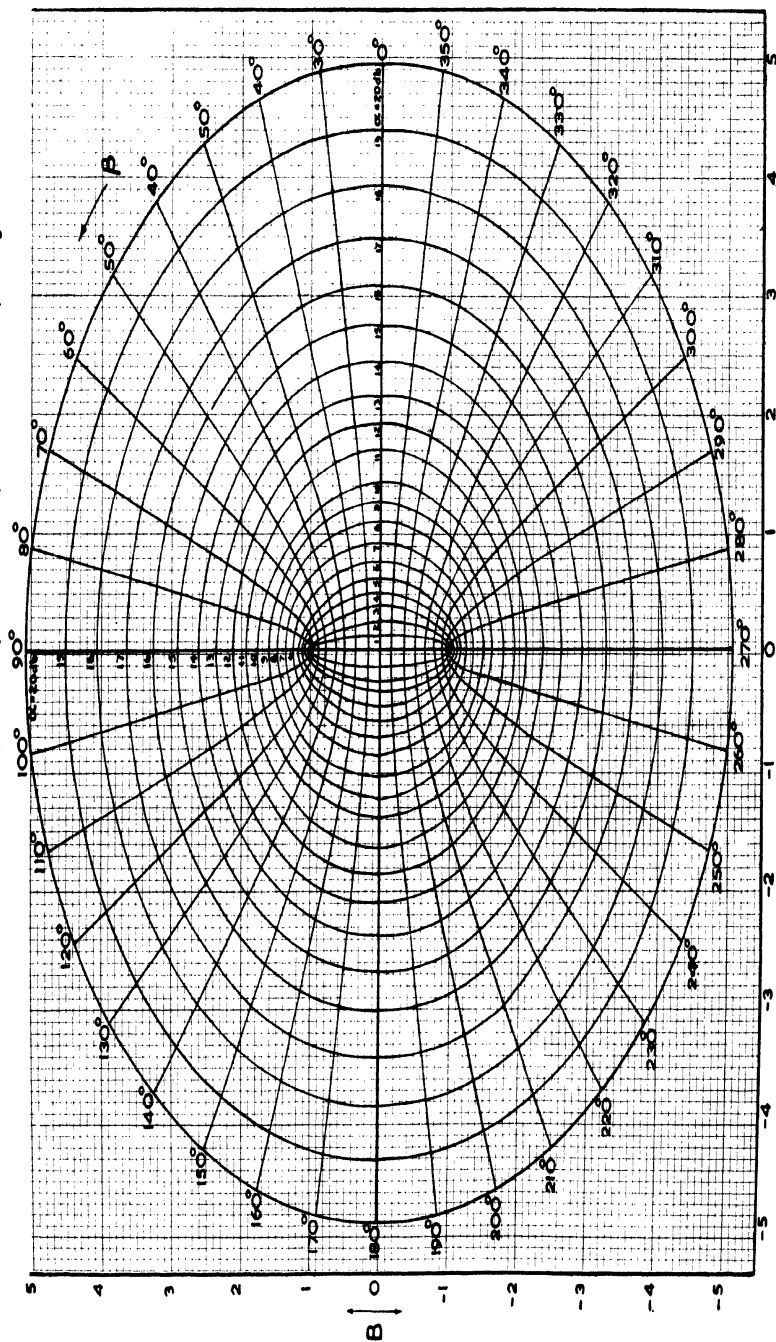


FIG. 5-1.—Graphical calculator for sinh ($\alpha + j\beta$) = $A + jB$.

GRAPHICAL CALCULATOR FOR $\sinh(\alpha + j\beta)$

If the values of α and β are known, then the real and imaginary parts of the function $\sinh(\alpha + j\beta) = A + jB$ may be readily determined, for $A = \sinh \alpha \cdot \cos \beta$ and $B = \cosh \alpha \cdot \sin \beta$.

The converse problem, namely to find α and β if A and B are known, involves the solution of the equations :

$$\frac{A^2}{\sinh^2 \alpha} + \frac{B^2}{\cosh^2 \alpha} = 1 \quad (5)$$

$$\text{and } \frac{B^2}{\sin^2 \beta} + \frac{A^2}{\cos^2 \beta} = 1 \quad (6)$$

If values of A and B are taken along rectangular axes, equation 5 represents a family of ellipses, one corresponding to each value of α , and equation 4 represents a family of hyperbolae, one corresponding to each value of β . These families form a confocal system of conic sections similar to that of Fig. 768, and are plotted in Fig. S-1. Given A and B , one point in the plane is determined, and the associated values of α and β are those corresponding to the curves that intersect in that point. Note that Fig. S-1 is drawn for values of α in db and values of β in degrees.

Example.—

Find α and β if $\sinh(\alpha + j\beta) = 2 + j \cdot 3 \cdot 5$

Look for the point whose co-ordinates are $A = 2$, $B = 3 \cdot 5$. This point is at the intersection of the curves $\alpha = 18$ db and $\beta = 60^\circ$.

Hence $2 + j \cdot 3 \cdot 5 = \sinh(18\text{db} + j \cdot 60^\circ)$
 $= \sinh(2 \cdot 07 + j \cdot 1 \cdot 047)$ *Ans.*

GRAPHICAL CALCULATOR FOR $\sqrt{\alpha + j\beta}$

If the values of A and B are known, where $A + jB = \sqrt{\alpha + j\beta}$, then α and β may be readily evaluated, for $\alpha + j\beta = (A + jB)^2$, giving $\alpha = A^2 - B^2$ and $\beta = 2AB$.

The converse problem, namely to find A and B if α and β are given, involves the solution of the equations :

$$4A^4 - 4\alpha \cdot A^2 - \beta^2 = 0 \quad (7)$$

$$\text{and } 4B^4 + 4\alpha \cdot B^2 - \beta^2 = 0 \quad (8)$$

The solutions to these equations for A and B are somewhat laborious ; A and B may, however, be found graphically. Consider the corresponding equations for α and β , namely :—

$$\alpha = A^2 - B^2 \quad (9)$$

$$\text{and } \beta = 2AB \quad (10)$$

If values of A and B are taken along rectangular axes, equations 9 and 10 represent two families of hyperbolae, one curve of the first

family corresponding to each value of α , and one curve of the second family corresponding to each value of β . These curves are plotted in Fig. S-2. Then, given A and B , one point in the plane is determined, and the associated values of α and β are those corresponding to the curves that intersect at that point.

Conversely, when α and β are known, the corresponding values of A and B are given by the co-ordinates of the points of intersection of the appropriate α and β curves. It must be noted, however, that for any pair of values of α and β , two intersections will be found, corresponding to the two roots.

Example.—

Find $\sqrt{12 + j \cdot 16}$

Look for the intersections of the curves $\alpha = +12$ and $\beta = +16$. These will be found at the points ($A = +4$, $B = +2$) and ($A = -4$, $B = -2$).

Hence $\sqrt{12 + j \cdot 16} = \pm(4 + j \cdot 2)$ Ans.

GRAPHICAL CALCULATOR FOR $r \angle \theta = x + jy$

If the values of the polar co-ordinates (r , θ) of a vector are given, the corresponding rectangular co-ordinates (x , y) are given by :

$$x = r \cdot \cos \theta \quad (11)$$

$$y = r \cdot \sin \theta \quad (12)$$

Similarly, if the rectangular co-ordinates (x , y) are given, the polar co-ordinates (r , θ) are given by :

$$r = \sqrt{x^2 + y^2} \quad (13)$$

$$\theta = \tan^{-1}\left(\frac{y}{x}\right) \quad (14)$$

In either case, the calculations involved are straightforward. Nevertheless, on occasions, when great accuracy is not required, time can be saved by the use of the chart given in Fig. S-3. Here values of x and y are taken along rectangular axes, values of r are represented by portions of concentric circles centred on ($x = 0$, $y = 0$), and values of θ are represented by the angle between radial lines radiating from ($x = 0$, $y = 0$) and the x -axis.

Given x and y , a straight-edge is placed so as to join the origin (0 , 0) with the point (x , y); this edge, when extended so as to intersect the curved θ -scale at the right-hand side of the chart, will do so at the appropriate value of θ . The value of r is given by the radial distance of the point (x , y) from the origin; it may be estimated with the aid of the concentric r -curves, or measured more accurately if the straight-edge be marked with a centimetre scale, and the zero of this scale arranged to coincide with the origin.

Conversely, given r and θ , a straight-edge is placed so as to join the origin with the appropriate value of θ on the curved scale; at a distance r from the origin along this straight-edge is the point (r , θ), whose rectangular co-ordinates (x , y) can be read off the rectangular axes.

The chart is drawn only for the first quadrant, in which x and y are both positive, *i.e.* $0 < \theta < \frac{\pi}{2}$; its use may be extended to vectors lying in other quadrants by adding multiples of $\frac{\pi}{2}$ and adjusting signs as necessary, as explained below.

Example 1.—

Express $10 \angle 30^\circ$ in rectangular co-ordinates.

At a distance 10 units along the radial line $\theta = 30^\circ$ is the point given by $x = 8.66, y = 5$.

Hence $10 \angle 30 = 8.66 + j.5$ *Ans.*

Example 2.—

Express $12 + j.5$ in polar form.

First find the point $x = 12, y = 5$. A centimetre scale joining the origin to this point shows the point to be 13 cm from the origin; this scale when extended cuts the θ scale at 22.5° , or $\frac{\pi}{8}$ radians.

Thus $12 + j.5 = 13 \angle \pi/8$ *Ans.*

Example 3.—

Express $1.2 = j.0.5$ in polar form.

In this case, 0.5 is too small to be read on the y scale, but both 1.2 and 0.5 , when multiplied by 10 , yield figures within the ranges of the x and y scales.

$$\begin{aligned} \text{Then } 1.2 + j.0.5 &= \frac{12 + j.5}{10} \\ &= \frac{13 \angle \pi/8}{10} \\ &= 1.3 \angle \pi/8 \quad \text{Ans.} \end{aligned}$$

Example 4.—

Express $120 \angle 30^\circ$ in rectangular form.

120 lies outside the range of values of r covered by the chart, but $120 \angle 30^\circ = 10 \times (12 \angle 30^\circ)$. Look for the intersection of the lines $r = 12$ and $\theta = 30^\circ$; this gives $x = 10.4, y = 6.0$.

$$\begin{aligned} \text{Thus } 120 \angle 30^\circ &= 10 \times (10.4 + j.6.0) \\ &= 104 + j.60 \quad \text{Ans.} \end{aligned}$$

Vectors outside the first quadrant


Since the chart of Fig. S-3 shows only vectors in the first quadrant, for which $0 < \theta < \frac{\pi}{2}$, and x and y are both positive, vectors outside this quadrant must be dealt with by finding a corresponding vector in the first quadrant which can be found on the chart.

Vectors in the second quadrant ($\frac{\pi}{2} < \theta < \pi$; x negative, y positive).—A vector in the second quadrant is most easily dealt with by considering that vector which has the same magnitude r

Graphical Calculator

for
$$r/\theta = X + jY$$

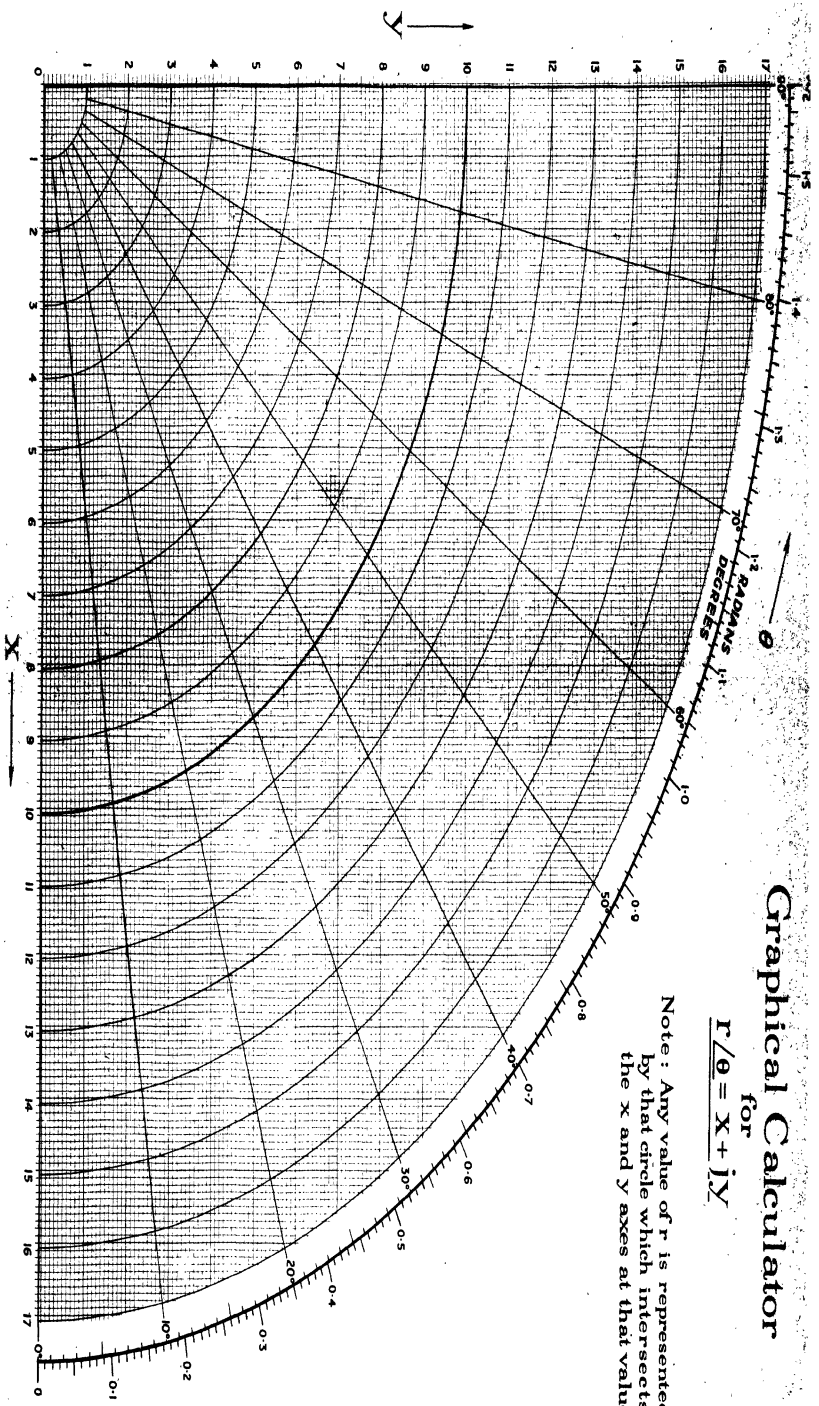Note: Any value of r is represented by that circle which intersects the x and y axes at that value



Graphical calculator for $\sqrt{a^2 + b^2} = A + jB$

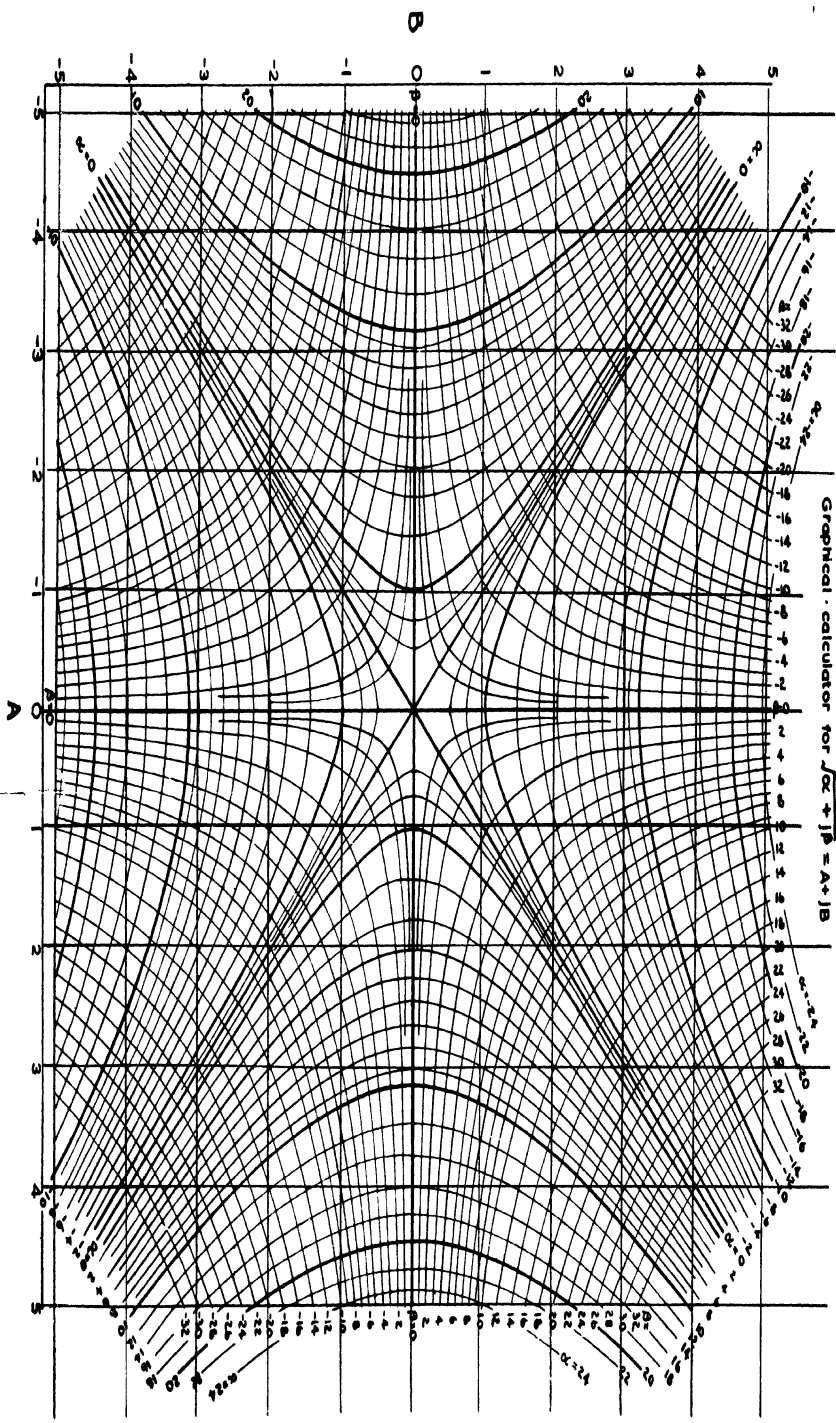


Fig. S-2.—Graphical calculator for $\sqrt{a + jb} = A + jB$.

but an angle $(\pi - \theta)$. This vector $r \angle \pi - \theta$ will have an x -component equal in magnitude but opposite in sign to that of the original vector $r \angle \theta$, and it will have the same y -component.

Example 5.—

Express $12 \angle 150^\circ$ in rectangular form.

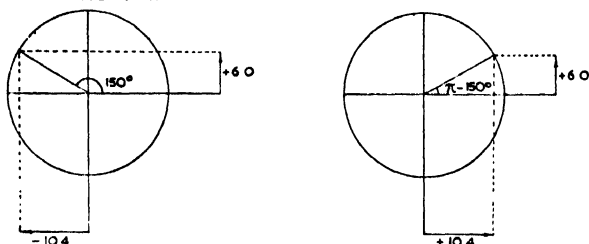


Fig. S-4.—Vector in second quadrant ($90^\circ < \theta < 180^\circ$).

From Fig. S-4, it can be seen that the x -component of $12 \angle (\pi - 150^\circ)$, *i.e.* of $12 \angle 30^\circ$, is equal in magnitude but opposite in sign to that of $12 \angle 150^\circ$, while the y -component is the same in each case.

From the chart, $12 \angle 30^\circ = 10.4 + j \cdot 6.0$

Hence $12 \angle 150^\circ = -10.4 + j \cdot 6.0$ *Ans.*

Vectors in the third quadrant ($\pi < \theta < \frac{3\pi}{2}$; x and y both negative). A vector in the third quadrant is most easily dealt with by considering that vector which has the same magnitude r but an angle $(\theta - \pi)$. Both x - and y -components of this vector $r \angle \theta - \pi$ will then be equal in magnitude but opposite in sign to those of the original vector $r \angle \theta$.

Example 6.—

Express $12 \angle 210^\circ$ in rectangular form.

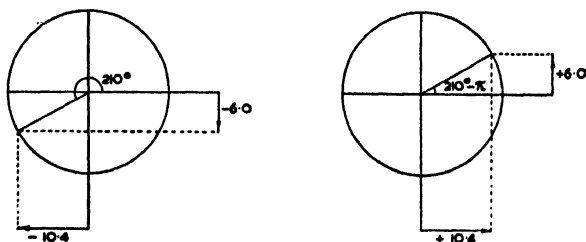


Fig. S-5.—Vector in third quadrant ($180^\circ < \theta < 270^\circ$).

From Fig. S-5, it can be seen that the x -component of $12 \angle (210^\circ - \pi)$, *i.e.*, of $12 \angle 30^\circ$, is the negative of the x -component of $12 \angle 210^\circ$, and that the y -component of $12 \angle 30^\circ$ is the negative of the x -component of $12 \angle 210^\circ$.

Hence $12 \angle 210^\circ = -10.4 - j \cdot 6.0$ *Ans.*

Vectors in the fourth quadrant ($\frac{3\pi}{2} < \theta < 2\pi$; x positive, y negative). A vector in the third quadrant is most easily dealt with by considering that vector which has the same magnitude r but an angle $(2\pi - \theta)$. This vector $r \angle (2\pi - \theta)$ will have an x -component equal to that of the original vector $r \angle \theta$, and it will have a y -component equal in magnitude but opposite in sign to that of the original vector.

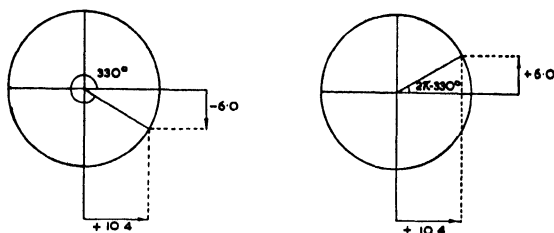


Fig. S-6.—Vector in fourth quadrant ($270^\circ < \theta < 360^\circ$).

Example 7.—

Express $10.4 - j 6.0$ in polar form.

$$\begin{aligned} \text{Let} \quad & 10.4 - j 6.0 = r \angle \theta \\ \text{Then} \quad & 10.4 + j 6.0 = r \angle 2\pi - \theta \\ \text{From the chart} \quad & 10.4 + j 6.0 = 12 \angle 30^\circ \\ \text{Thus} \quad & r \angle 2\pi - \theta = 12 \angle 30^\circ \\ \text{Hence} \quad & r \angle \theta = 12 \angle 330^\circ \\ \text{i.e.} \quad & 10.4 - j 6.0 = 12 \angle 330^\circ \quad \text{Ans.} \end{aligned}$$

RECIPROcity THEOREM

In any network consisting of linear impedances, if the circuit be broken at any point P and an EMF E applied in series with the circuit at P , and if the current I_1 at any point Q in the network be measured, then the "transfer impedance" Z_{PQ} (i.e., the ratio of E to I_1) is the same as the transfer impedance Z_{QP} (i.e., the ratio of E to I_2) obtained if the EMF E be applied at Q and the current I_2 at P be measured.

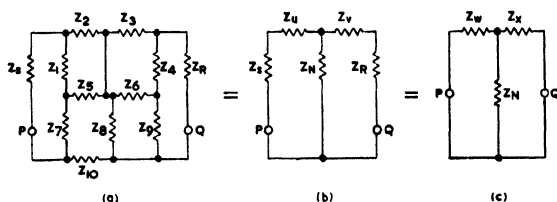


FIG. S-7.—Complex network (a) reduced to simple T-section (b). At (c), the terminal impedances Z_s and Z_R are included within the T-section

Any network consisting of linear impedances, with the circuit broken at two points P and Q , may be looked upon as a four-terminal network, and this, as seen on p. 594, can be replaced at any one frequency by an equivalent T section.

Consider, for example, the network of Fig. S-7a. This particular network was shown in Chapter 13 (Fig. 600, p. 595) to be equivalent to the arrangement of Fig. S-7b. By combining Z_S and Z_R with the series arms of the T section, this can be further simplified to the simple arrangement of Fig. S-7c, where $Z_W = Z_S + Z_V$ and $Z_X = Z_V + Z_R$. Thus the whole of the complex network of Fig. S-7a linking points P and Q has been replaced by a single T section.

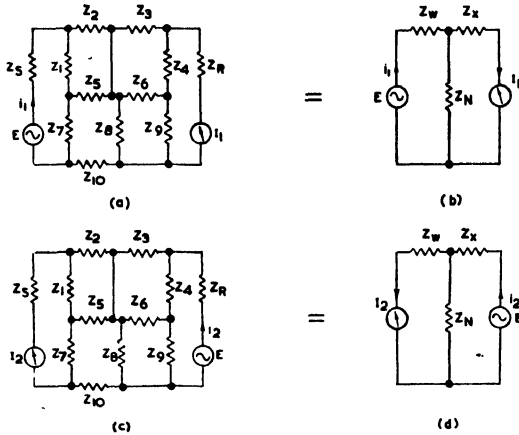


FIG. S-8.—Complex network (a) between generator and load, replaced at (b) by equivalent simple T-section; and (c and d) the same with positions of generator and load interchanged, to illustrate the Reciprocity theorem.

When an EMF E is applied in series with P , as in Fig. S-8a, the current I_1 flowing at Q may be found by considering the equivalent circuit shown in Fig. S-8b.

The current i_1 flowing from the generator at P is:—

$$i_1 = \frac{E}{Z_W + \frac{Z_X \cdot Z_H}{Z_X + Z_H}}$$

The current at Q is therefore:—

$$I_1 = \frac{i_1 \cdot Z_H}{Z_X + Z_H} = E \cdot \frac{Z_H}{Z_W Z_H + Z_X Z_H + Z_H Z_W}$$

The transfer impedance Z_{PQ} is therefore:—

$$Z_{PQ} = \frac{E}{I_1} = \frac{Z_W Z_X + Z_X Z_H + Z_H Z_W}{Z_H}$$

When the EMF E is applied in series with Q , as in Fig. S-8c, the current I_2 flowing at P may be found by considering the equivalent circuit shown in Fig. S-8d.

The current i_2 flowing from the generator at Q is:—

$$i_2 = \frac{E}{Z_X + \frac{Z_H \cdot Z_W}{Z_H + Z_W}}$$

The current I_2 at P is therefore :—

$$I_2 = \frac{i_2 \cdot Z_H}{Z_W + Z_H} = E \cdot \frac{Z_H}{Z_W Z_X + Z_X Z_H + Z_H Z_W} = I_1$$

The transfer impedance Z_{QP} is therefore :—

$$Z_{QP} = \frac{E}{I_1} = \frac{Z_W Z_X + Z_X Z_H + Z_H Z_W}{Z_H} = Z_{PQ}$$

It must be noted, in the application of this theorem, that no impedances are transferred in the interchange of point of application of EMF and point of measurement of current. The theorem can thus be applied to the interchange of a generator of finite impedance, and a load impedance, only when these two impedances are equal ; in this particular case, the theorem shows that a network of linear impedances will transmit equally effectively in either direction.

BARTLETT'S BISECTION THEOREM

Consider a symmetrical network (see Fig. S-9a) of characteristic impedance Z_0 and propagation constant γ , having within it n terminals $T_1 T_2 T_3 \dots T_n$ such that when these terminals are open-circuited the network is split into two exactly similar halves (see Fig. S-9b) ; this theorem states that the impedance Z_{sc} measured at the input terminals of one half of such a network with terminals $T_1 T_2 T_3 \dots T_n$ all connected together (Fig. S-9c) will be $Z_0 \cdot \tanh \frac{\gamma l}{2}$ and the impedance Z_{oc} with $T_1 T_2 T_3 \dots T_n$ all disconnected (Fig. S-9d) will be $Z_0 \cdot \coth \frac{\gamma l}{2}$.

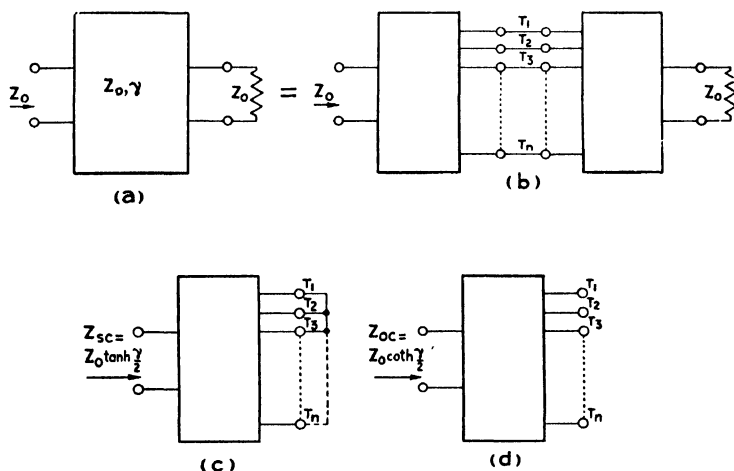


FIG. S-9.—Bartlett's bisection theorem :

- (a) Symmetrical network having characteristic impedance Z_0 and propagation constant γ .
- (b) Network of Fig. S-9a, split at $T_1 \dots T_n$ into two identical halves.
- (c) One-half of network, with terminals $T_1 \dots T_n$ short-circuited.
- (d) One-half of network, with terminals $T_1 \dots T_n$ open-circuited.

As a corollary to this theorem, it follows from equations 56 and 62 of Chapter 13 that any symmetrical network having a characteristic impedance Z_0 and a propagation constant γ can be represented by a lattice section having series arms each equal to $Z_0 \cdot \tanh \frac{\gamma}{2}$ and lattice arms each equal to $Z_0 \cdot \coth \frac{\gamma}{2}$.

It has been seen that any network can be represented (at any single frequency) by a simple T or π section (*see* p. 594). Since the network postulated above is symmetrical, it follows that it can be represented by a symmetrical T or π section. Let it therefore be represented by the symmetrical T section shown in Fig. S-10*a*, which shows how it may be split into two exactly similar halves at terminals T_1 and T_2 .

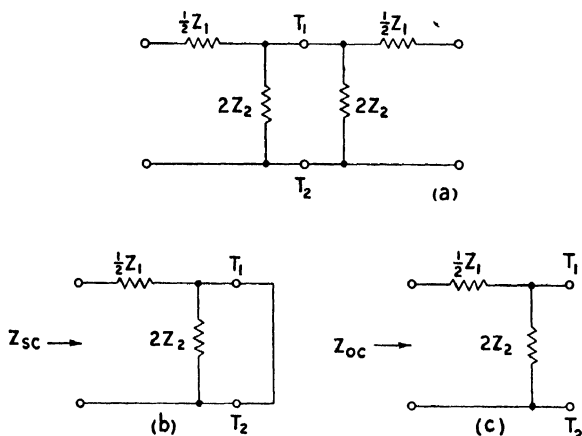


FIG. S-10.—Bartlett's bisection theorem applied to T-section :

- (a) Symmetrical network split at T_1 T_2 into two identical halves.
 (b) One-half of network, with terminals T_1 T_2 short-circuited.
 (c) One-half of network, with terminals T_1 T_2 open-circuited.

For the complete T section of Fig. S-10*a*, the characteristic impedance Z_0 and propagation constant γ are given in terms of the component impedances (*see* Chapter 13, eq. 10, p. 570 and eq. 24, p. 575) by :—

$$Z_0 = \sqrt{\frac{1}{4}Z_1^2 + Z_1 \cdot Z_2}$$

$$\tanh \frac{\gamma}{2} = \frac{Z_1}{2Z_0}$$

For one-half of the section with T_1 T_2 $T_3 \dots T_n$ connected together (*see* Fig. S-10*b*) :—

$$Z_{sc} = \frac{1}{2}Z_1 = Z_0 \cdot \frac{Z_1}{2Z_0} = Z_0 \cdot \tanh \frac{\gamma}{2}$$

For one-half of the section with $T_1, T_2, T_3, \dots, T_n$ all disconnected (see Fig. S-10c) :—

$$\begin{aligned} Z_{oo} &= \frac{1}{2}Z_1 + 2Z_2 = \frac{2}{Z_1} \left(\frac{1}{2}Z_1^2 + Z_1Z_2 \right) = \frac{2}{Z_1} \cdot Z_0^2 \\ &= Z_0 \cdot \frac{2 \cdot Z_0}{Z_1} = Z_0 \cdot \coth \frac{\gamma}{2} \end{aligned}$$

The impedances Z_{oo} and Z_{oo} are thus seen to have the values required.

Corollary

Fig. S-11 shows the lattice section with series arms Z_A each equal to $Z_0 \cdot \tanh \frac{\gamma}{2}$ and lattice arms Z_B each equal to $Z_0 \cdot \coth \frac{\gamma}{2}$. It is required to prove that this section is equivalent to the original network of Fig. S-9a.

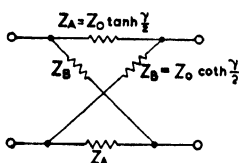


FIG. S-11.—Lattice section, equivalent to the original section of Fig. S-9a, as yielded by Bartlett's bisection theorem.

Let the characteristic impedance and propagation constant of the lattice section be Z_0' and γ' . Then, by eq. 56 of Chapter 13 (p. 587) and eq. 63 (p. 588), these are given by :—

$$\begin{aligned} Z_0' &= \sqrt{Z_A \cdot Z_B} = \sqrt{Z_0 \cdot \tanh \frac{\gamma}{2} \cdot Z_0 \cdot \coth \frac{\gamma}{2}} = Z_0 \\ \tanh \frac{\gamma'}{2} &= \sqrt{\frac{Z_A}{Z_B}} = \sqrt{\frac{Z_0 \cdot \tanh \frac{\gamma}{2}}{Z_0 \cdot \coth \frac{\gamma}{2}}} = \tanh \frac{\gamma}{2} \end{aligned}$$

Thus the lattice section of Fig. S-11 is seen to have the same characteristic impedance Z_0 and propagation constant γ as the original network of Fig. S-9a; the two networks are therefore equivalent.

This result may be compared with that of pp. 599–600, where the T section shown in Fig. S-12a is shown to be equivalent to the lattice section of Fig. S-12b and may therefore be used to replace it in any network.

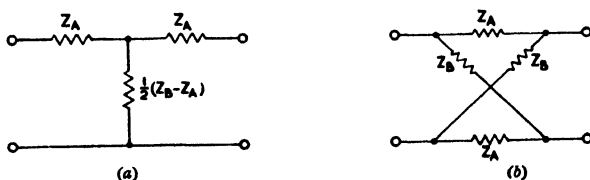


FIG. S-12.—T section and equivalent lattice section.

Applying Bartlett's bisection theorem to the T section of Fig. S-12a, to find the equivalent lattice section :—

$$\begin{aligned} Z_0 &= \sqrt{\frac{1}{4}(2Z_A)^2 + 2Z_A \cdot \frac{1}{2}(Z_B - Z_A)} \\ &= \sqrt{Z_A^2 + Z_A \cdot Z_B - Z_A^2} \\ &= \sqrt{Z_A \cdot Z_B} \\ \tanh \frac{\gamma}{2} &= \frac{2Z_A}{2\sqrt{Z_A \cdot Z_B}} = \sqrt{\frac{Z_A}{Z_B}} \\ \therefore \coth \frac{\gamma}{2} &= \sqrt{\frac{Z_B}{Z_A}} \end{aligned}$$

The series arms of the equivalent lattice section as given by Bartlett's bisection theorem will therefore be :—

$$Z_0 \cdot \tanh \frac{\gamma}{2} = \sqrt{Z_A \cdot Z_B} \cdot \sqrt{\frac{Z_A}{Z_B}} = Z_A$$

and the lattice arms :—

$$Z_0 \cdot \coth \frac{\gamma}{2} = \sqrt{Z_A \cdot Z_B} \cdot \sqrt{\frac{Z_B}{Z_A}} = Z_B$$

Thus Bartlett's bisection theorem also yields, as the lattice equivalent of the T section of Fig. S-12a, the section shown in Fig. S-12b.

Example of use of Bartlett's bisection theorem.—Find a lattice section equivalent to the bridged-T section of Fig. S-13a.

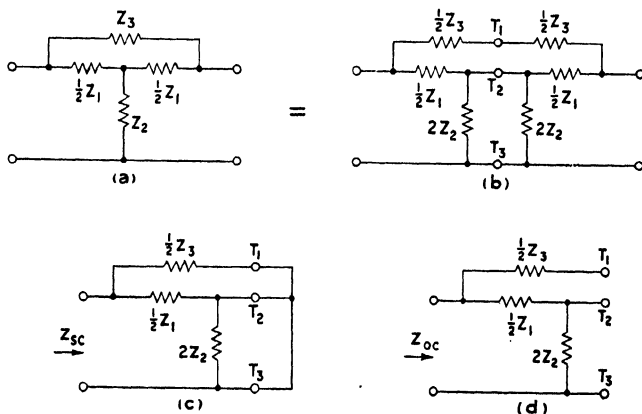


FIG. S-13.—Bridged T-section (a), shown at (b) split into two identical halves ; with one-half on short-circuit (c) and on open-circuit (d).

The bridged-T section of Fig. S-13a can be split into two identical halves at terminals T_1 , T_2 , T_3 , as shown in Fig. S-13b. With terminals T_1 - T_3 connected together, as in Fig. S-13c, the input impedance of one-half of the section is :—

$$Z_{sc} = \frac{\frac{1}{2}Z_1 \cdot \frac{1}{2}Z_3}{\frac{1}{2}Z_1 + \frac{1}{2}Z_3} = \frac{1}{2} \cdot \frac{Z_1 \cdot Z_3}{Z_1 + Z_3}$$

Similarly, with terminals T_1-T_3 open-circuited, as in Fig. S-13d, the input impedance of one-half of the section is :—

$$Z_{oc} = \frac{1}{2}Z_1 + 2Z_2$$

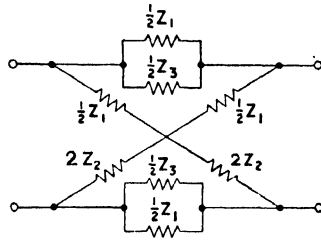


FIG. S-14.—Lattice section equivalent to the bridged-T section of Fig. S-13a, as yielded by Bartlett's bisection theorem.

Hence the bridged-T section of Fig. S-13a can be represented by the lattice section of Fig. S-14, which is completely equivalent to it. This may easily be verified by comparing the characteristic impedance and propagation constant for each section.

Extension to Bartlett's bisection theorem

Certain networks, when split into two identical halves at the terminals $T_1 \dots T_n$, do not exhibit a one-to-one correspondence between these terminals as illustrated in Fig. S-9b, but rather exhibit

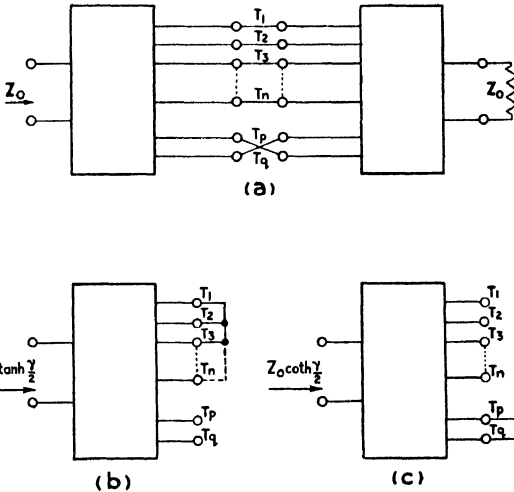


FIG. S-15.—Extension to Bartlett's bisection theorem :

- (a) Symmetrical network split into two identical halves at the straight interconnections $T_1 \dots T_n$ and the crossed terminal-pair $T_p T_q$.
- (b) Half of network, with terminals $T_1 \dots T_n$ short-circuited, and terminal-pair $T_p T_q$ open-circuited.
- (c) Half of network, with terminals $T_1 \dots T_n$ open-circuited, and terminal-pair $T_p T_q$ short-circuited.

a form of skew-symmetry such that the interconnections between certain pairs of terminals must be crossed, as shown at $T_p T_q$ in Fig. S-15a. Such "crossed" terminal pairs are in many ways akin to

the lattice arms of a lattice section, which behave in an inverse manner to the series arms. From this it follows, as can easily be proved, that the short-circuit and open-circuit impedances of one-half of the network will still obey the theorem, provided that each pair of crossed terminals is treated in the inverse manner to the remaining n terminals. Thus the input impedance of one-half of the section is $Z_{sc} = Z_0 \cdot \tanh \frac{\gamma}{2}$ when terminals $T_1 \dots T_n$ are all connected together and the crossed terminal-pairs $T_p T_q$ etc. are all open-circuited, as in Fig. S-15b. Similarly, the input impedance of one-half of the section is $Z_{oc} = Z_0 \cdot \coth \frac{\gamma}{2}$ when terminals $T_1 \dots T_n$ are all open-circuited and each terminal-pair $T_p T_q$ is short-circuited, as in Fig. S-15c.

Example.—To illustrate the use of this extension to Bartlett's bisection theorem, find a simple lattice section equivalent to the section shown in Fig. S-16a.

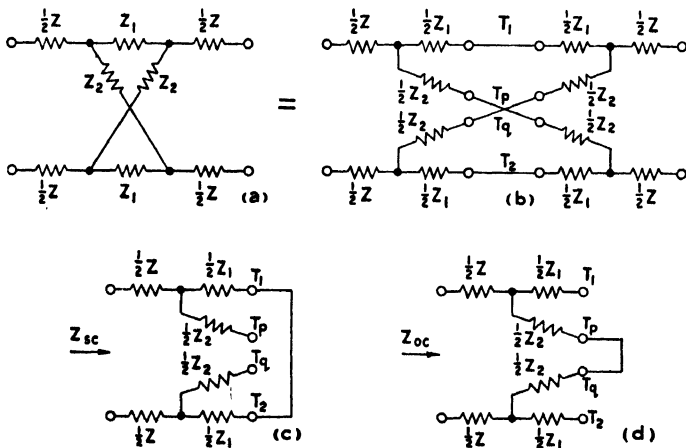


FIG. S-16.—Original network (a), shown at (b) split unto two identical halves at the straight interconnections $T_1 \dots T_n$ and the crossed terminal-pair $T_p T_q$; with one half on short-circuit (c), and on open-circuit (d).

This section can be redrawn in the form of two identical halves (see Fig. S-16b) with two straight interconnections $T_1 T_2$, and one pair of crossed interconnections $T_p T_q$.

With $T_1 T_2$ short-circuited and $T_p T_q$ open-circuited, as in Fig. S-16c, the short-circuit input impedance of one-half of the section is:—

$$Z_{sc} = Z_0 \cdot \tanh \frac{\gamma}{2} = \frac{1}{2}Z + \frac{1}{2}Z_1 + \frac{1}{2}Z_1 + \frac{1}{2}Z = Z + Z_1$$

Similarly, with T_1T_2 open-circuited and T_pT_q short-circuited, as in Fig. S-16*d*, the open-circuit impedance is :—

$$Z_{oc} = Z_0 \cdot \coth \frac{\gamma}{2} = \frac{1}{2}Z + \frac{1}{2}Z_2 + \frac{1}{2}Z_2 + \frac{1}{2}Z = Z + Z_2$$

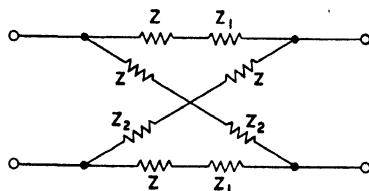


FIG. S-17.—Lattice section equivalent to the network of Fig. S-16*a*, as yielded by Bartlett's Bisection Theorem.

Hence a lattice section having series arms $(Z + Z_1)$ and lattice arms $(Z + Z_2)$, as shown in Fig. S-17, will be equivalent to the original section of Fig. S-16*a*. This confirms a result obtained in Chapter 13 (see Fig. 605, p. 599).

MILLMAN'S THEOREM

If any number n of constant-voltage generators, each of EMF E_r and finite internal admittance Y_r , be connected in parallel, as in Fig. S-18, then the resulting PD across the paralleled terminals is given by :—

$$E = \frac{\sum_{r=1}^{r=n} E_r Y_r}{\sum_{r=1}^{r=n} Y_r}$$

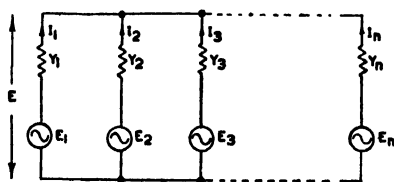


FIG. S-18.—Millman's theorem : n constant-voltage generators connected in parallel.

Referring to Fig. S-18, the PD E across the paralleled terminals is seen, by Kirchhoff's Law, to be :—

$$E = E_1 - \frac{I_1}{Y_1} = E_2 - \frac{I_2}{Y_2} = \dots = E_n - \frac{I_n}{Y_n}$$

$$\therefore E \cdot Y_1 = E_1 \cdot Y_1 - I_1$$

$$E \cdot Y_2 = E_2 \cdot Y_2 - I_2$$

$$\vdots$$

$$E \cdot Y_n = E_n \cdot Y_n - I_n$$

On adding these equations :—

$$E \cdot \sum_{r=1}^{r=n} Y_r = \sum_{r=1}^{r=n} E_r \cdot Y_r - \sum_{r=1}^{r=n} I_r$$

But by Kirchoff's First Law (see p. 126), $\sum_{r=1}^{r=n} I_r = 0$

$$\therefore E \sum_{r=1}^{r=n} Y_r = \sum_{r=1}^{r=n} E_r \cdot Y_r$$

$$\therefore E = \frac{\sum_{r=1}^{r=n} E_r \cdot Y_r}{\sum_{r=1}^{r=n} Y_r}$$

DUAL OF MILLMAN'S THEOREM

If any number n of constant-current generators, each of current I_r and finite parallel impedance Z_r , be connected in series to form a single closed loop, as in Fig. S-19, then the resulting current I through that closed loop is given by :—

$$I = \frac{\sum_{r=1}^{r=n} I_r \cdot Z_r}{\sum_{r=1}^{r=n} Z_r}$$

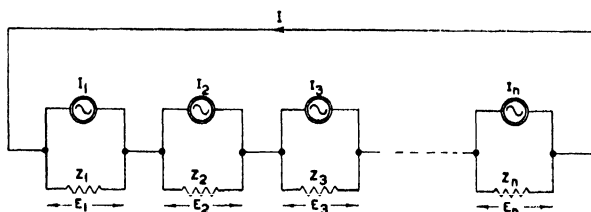


FIG. S-19.—Dual of Millman's theorem: n constant-current generators connected in series.

Referring to Fig. S-19, the current I through the series network is seen to be :—

$$I = I_1 - \frac{E_1}{Z_1} = I_2 - \frac{E_2}{Z_2} = \dots = I_n - \frac{E_n}{Z_n}$$

$$\therefore \begin{aligned} I \cdot Z_1 &= I_1 \cdot Z_1 - E_1 \\ I \cdot Z_2 &= I_2 \cdot Z_2 - E_2 \\ &\vdots \\ I \cdot Z_n &= I_n \cdot Z_n - E_n \end{aligned}$$

On adding these equations :—

$$I \cdot \sum_{r=1}^{r=n} Z_r = \sum_{r=1}^{r=n} I_r \cdot Z_r - \sum_{r=1}^{r=n} E_r$$

But by Kirchhoff's Second Law, $\sum_{r=1}^{r=n} E_r = 0$

$$\therefore I \cdot \sum_{r=1}^{r=n} Z_r = \sum_{r=1}^{r=n} I_r \cdot Z_r$$

$$\therefore I = \frac{\sum_{r=1}^{r=n} I_r \cdot Z_r}{\sum_{r=1}^{r=n} Z_r}$$

FOSTER'S REACTANCE THEOREM

The impedance of a two-terminal network consisting of purely reactive elements is uniquely specified by the location of the internal zeros and poles (*i.e.*, the frequencies at which the impedance is zero and infinity), plus one additional piece of information, which is usually the value of the impedance at one definite frequency. Expressed analytically :—

Any two-terminal network containing only pure reactances has, at frequency $\frac{\omega}{2\pi}$, an impedance Z of the form :

$$Z = \lambda \cdot H \cdot \frac{(\omega_a^2 - \omega^2)(\omega_c^2 - \omega^2) \dots (\omega_{2k \pm 1}^2 - \omega^2)}{(\omega_b^2 - \omega^2)(\omega_d^2 - \omega^2) \dots (\omega_{2k}^2 - \omega^2)} \quad (1)$$

where : $\lambda = +j \cdot \omega$ or $-\frac{j}{\omega}$

$$H = L \text{ or } \frac{1}{C}$$

k is a positive integer,

$$\text{and } 0 \leq \omega_a \leq \omega_b \leq \omega_c \leq \omega_d \dots \leq \infty \quad (2)$$

The frequencies $\omega_a, \omega_c \dots$ appearing in the numerator of (1) are the "zeros" of Z (*i.e.*, the frequencies for which the impedance is zero), while the frequencies $\omega_b, \omega_d \dots$ in the denominator are the "poles" of Z (*i.e.*, the frequencies for which the impedance is infinite).

This theorem is of great importance to the designers of filters and similar devices built up from reactive networks, since it gives a clear insight into the relation between the impedance/frequency characteristic and the structure of any two-terminal reactive network. As expressed above, the theorem is perfectly general, but this very generality obscures its meaning and makes it too vague to be useful for many purposes. However, the theorem can be re-expressed in the form of several simpler statements of direct application to practical problems. In the same way, eq. 1 can be expressed in a form more useful for practical application, as four less general equations, which between them cover all possible cases of (1).

Statement 1.—The vector reactance of an impedance containing only pure reactances always increases with frequency. In the case of a single inductance, $\frac{d}{d\omega}(\omega L) = +L$, which must always be positive, as may be seen from inspection of the reactance sketch in Fig. S-20a. In the case of a single capacity, $\frac{d}{d\omega}\left(-\frac{1}{\omega C}\right) = +\frac{1}{\omega^2 C}$, which again must always be positive; inspection of the reactance sketch of Fig. S-20b shows that, although the reactance of a capacity is negative and its magnitude decreases with frequency, nevertheless

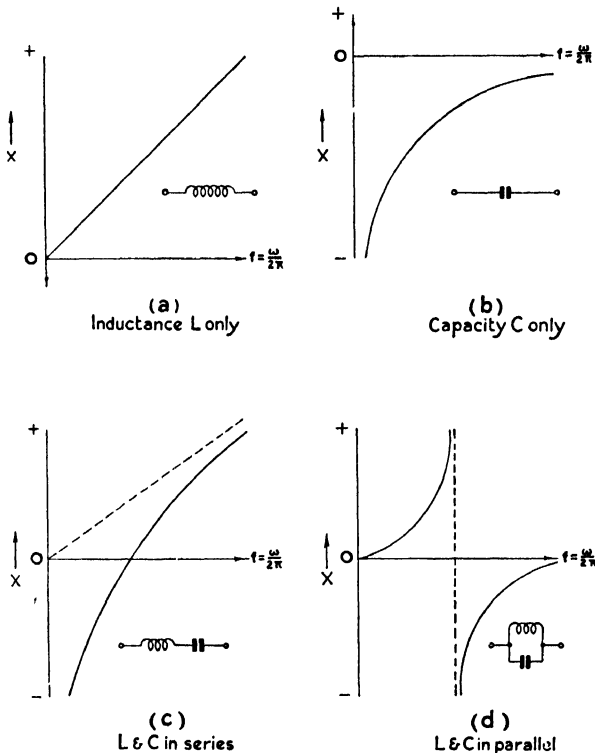


FIG. S-20.—Simple circuits containing only reactances, showing how vector reactance always increases with frequency.

the slope of the curve is always positive, which means that the vector reactance is always increasing. In the same way, for an inductance and capacity in series (see Fig. S-20c),

$$\frac{dX}{d\omega} = \frac{d}{d\omega}\left(\omega L - \frac{1}{\omega C}\right) = L + \frac{1}{\omega^2 C},$$

and for an inductance and capacity in parallel (see Fig. S-20d),

$$\frac{dX}{d\omega} = \frac{d}{d\omega}\left(\frac{\omega L}{1 - \omega^2 LC}\right) = L \cdot \frac{1 + \omega^2 LC}{(1 - \omega^2 LC)^2},$$

both of which expressions also must always be positive. It can be proved, either by inductive reasoning from these examples, or alternatively by an entirely independent method, that the derivative of the reactance of any purely reactive network is always positive, *i.e.*, that the vector reactance always increases with frequency.

Note that this does not apply when resistance is present; for example, the reactance of a parallel tuned circuit containing resistance decreases with increasing frequency in the neighbourhood of resonance (*see* Fig. 169, p. 217).

Statement 2.—The resonant frequencies or “zeros”, and anti-resonant frequencies or “poles”, of a reactive network must occur alternately with increasing frequency. This follows from statement (1); for if the reactance at any frequency is zero, then with increasing frequency the reactance must increase and remain positive until it reaches $+\infty$; it must then increase from $-\infty$ and remain negative until it reaches zero, after which it will again be positive until it reaches $+\infty$. Thus the reactance sketch for any reactive network must be of one of the four types shown in Fig. S-21, the choice between the four types (a), (b), (c) and (d) being governed by whether the impedance is zero or infinity at $\omega = 0$ and at $\omega = \infty$.


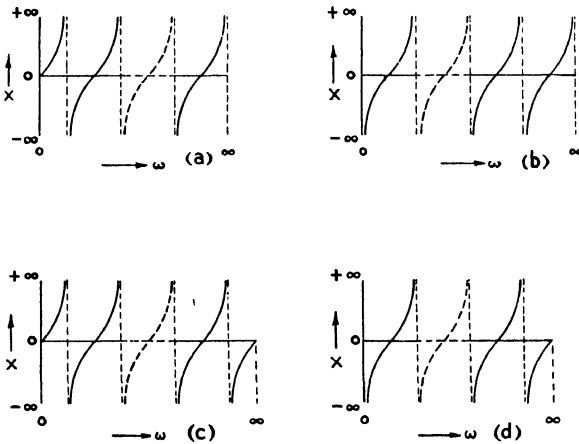


FIG. S-21.—The four possible types of reactance sketch for purely reactive networks, showing how zeros and poles must occur alternately with increasing frequency.

It can be shown that the impedance of any network having a finite number of elements must be expressible as the quotient of two polynomials, obtained from the solution of a number of linear equations given by Kirchhoff's Laws. The factors of the polynomial in the numerator must be determined by the zeros, and the factors of the denominator by the poles. Equation (1) satisfies this requirement, and also shows that the zeros ($Z = 0$) occur at frequencies $\omega_a, \omega_c, \dots, \omega_{2k\pm 1}$, and the poles ($Z = \infty$) at $\omega_b, \omega_d, \dots, \omega_{2k}$, while equation (2) shows that these must be interlaced.

Statement 3.—Any two-terminal network containing only pure reactances can be represented exactly either by a series arrangement of parallel tuned circuits, as in Fig. S-22a, with perhaps an additional series capacity C_0 and/or inductance L_q ; or alternatively, by a parallel arrangement of series tuned circuits, as in Fig. S-22b, with perhaps one capacity C_1 and/or inductance L_p omitted. Either of these arrangements yields a reactance sketch of one of the types shown in Fig. S-21, the choice between zeros and poles at $\omega = 0$ and at $\omega = \infty$ being governed by the inclusion or omission of the "odd" capacity (C_0 or C_1) and inductance (L_q or L_p). Networks of these two types are often called "Foster networks", after the originator of this theorem.

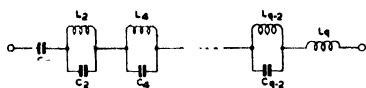

(a) Series arrangement of parallel tuned circuits.

Poles occur at frequencies given by:

$$\omega_0^2 = 0$$

$$\omega_2^2 = \frac{1}{L_2 C_2}$$

$$\omega_4^2 = \frac{1}{L_4 C_4}$$

⋮


$$\omega_{q-2}^2 = \frac{1}{L_{q-2} C_{q-2}}$$

$$\omega_q^2 = \infty$$

(where q is even).

For zero at origin ($\omega_1 = \omega_0 = 0$), put $C_0 = \infty$.

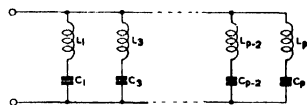For zero at infinity ($\omega_{q-1} = \omega_q = \infty$), put $L_q = 0$.



(b) Parallel arrangement of series tuned circuits.

Zeros occur at frequencies given by:

$$\omega_1^2 = \frac{1}{L_1 C_1}$$

$$\omega_3^2 = \frac{1}{L_3 C_3}$$

⋮

$$\omega_{p-2}^2 = \frac{1}{L_{p-2} C_{p-2}}$$

$$\omega_p^2 = \frac{1}{L_p C_p}$$

(where p is odd).

For zero at origin ($\omega_1 = \omega_0 = 0$), put $C_1 = \infty$.

For zero at infinity ($\omega_p = \omega_{p+1} = \infty$), put $L_p = 0$.

FIG. S-22.—Representation of any two-terminal network containing only pure reactances by a "Foster network".

Statement 4.—The minimum number m of components (inductances and capacities) required in the construction of a network having a given reactance-frequency response, is equal to one plus the number of internal zeros plus the number of internal poles (*i.e.*, the zeros and poles for which $0 < \omega < \infty$). If the sum of the numbers of internal zeros and poles be represented by n , this may be written as:

$$m = 1 + n \quad (3)$$

The "Foster" networks described in statement (3) require just this minimum number m of components. Other networks may be constructed to yield the required reactance-frequency curve, but they will in general require a larger number of components.

Statement 5.—If two impedances have the same resonant and anti-resonant frequencies, then one of these impedances must be a constant times the other at all frequencies.

This follows from statement (3), and from the fact that resonant (or anti-resonant) frequency is dependent on the product ($L \cdot C$) of inductance and capacity, while impedance is independent of this product. Consider, for example, a tuned circuit consisting of inductance L_1 and capacity C_1 ; this will have a resonant frequency given by $\omega_1^2 = L_1 \cdot C_1$, and an impedance at any frequency $\frac{\omega}{2\pi}$ given by $Z_1 = j \left(\omega L_1 - \frac{1}{\omega C_1} \right)$. Consider now a second tuned circuit, consisting of an inductance $L_2 = \alpha \cdot L_1$ and a capacity C_2 , and having the same resonant frequency $\frac{\omega_1}{2\pi}$. Since $L_2 \cdot C_2 = \omega_1^2 = L_1 C_1$, it follows that $C_2 = \frac{1}{\alpha} \cdot C_1$. The impedance of the second circuit is therefore given by :

$$Z_2 = j \left(\omega L_2 - \frac{1}{\omega C_2} \right) = j \left(\omega \cdot \alpha L_1 - \frac{\alpha}{\omega C_1} \right) = \alpha \cdot Z_1$$

Thus the second tuned circuit has the same resonant frequency as the first, but its impedance $Z_2 = \alpha \cdot Z_1$.

If, now, all the inductances in a Foster network of either type shown in Fig. S-22 be altered by a factor α , and all the capacities by a factor $\frac{1}{\alpha}$, then the locations of all the poles and zeros will be unchanged, but the impedance at any frequency will be altered by a factor α .

Note that all the inductances must be altered by the same factor α , and all the capacities by the same factor $\frac{1}{\alpha}$, if the locations of both poles and zeros are to remain unchanged. Suppose, for example, that the components L_2 and C_2 of one tuned circuit in Fig. S-22a be altered by factors α and $\frac{1}{\alpha}$ respectively, and that the components L_4 and C_4 of the next tuned circuit altered by some other factors β and $\frac{1}{\beta}$ respectively, and so on; then the anti-resonant frequencies $\omega_2, \omega_4, \dots$ will be unchanged, but unless $\alpha = \beta = \dots$, the resonant frequencies $\omega_3, \omega_5, \dots$ will not remain the same.

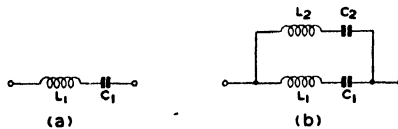


FIG. S-23.—Simple two-terminal reactive networks :

- (a) Impedance Z_1 consisting of inductance L_1 and capacity C_1 in series.
- (b) Inductance L_2 and capacity C_2 in series, added in parallel with Z_1 .

Physical explanation of Eq. 1.

Consider an impedance Z_1 , consisting of an inductance L_1 and a capacity C_1 in series, as in Fig. S-23a. The impedance is given by:—

$$Z_1 = j\omega L_1 + \frac{1}{j\omega C_1} = \frac{1 + (j\omega)^2 L_1 C_1}{(j\omega) C_1}$$

If now a second impedance Z_2 , consisting of an inductance L_2 and a capacity C_2 in series, be connected in parallel with Z_1 , as in Fig. S-23b, the resulting impedance Z is given by:—

$$Z = \frac{Z_1 \cdot Z_2}{Z_1 + Z_2} = \frac{1 + (j\omega)^2 (L_1 C_1 + L_2 C_2) + (j\omega)^4 L_1 L_2 C_1 C_2}{j\omega (C_1 + C_2) + (j\omega)^3 (L_1 C_1 C_2 + L_2 C_1 C_2)}$$

In general, when a complex reactive network is built up and analysed in this way, it is found that the numerator contains only even powers of $(j\omega)$, and the denominator only odd powers, or *vice versa*. On substituting $j^2 = -1$, one may write the general equation for the impedance, at frequency $\frac{\omega}{2\pi}$, of any reactive network in the form:—

$$Z = X \cdot \frac{a_0 - a_2 \omega^2 + a_4 \omega^4 - a_6 \omega^6 + \dots}{b_0 - b_2 \omega^2 + b_4 \omega^4 - b_6 \omega^6 + \dots} \quad (4)$$

where the coefficient X contains one " $j\omega$ ", *i.e.*, X is either of the form $j\omega \cdot A$, or of the form $\frac{1}{j\omega} \cdot A = -\frac{j}{\omega} A$, and the a 's and b 's are constants, dependent on the values of the circuit components. Equation 4, with the a 's and b 's written out in full in terms of the L 's and C 's, can be factorised into one of the four following forms:—

$$Z = +j\omega \cdot L \cdot \frac{(\omega_3^2 - \omega^2)(\omega_5^2 - \omega^2) \dots (\omega_{m-1}^2 - \omega^2)}{(\omega_2^2 - \omega^2)(\omega_4^2 - \omega^2) \dots (\omega_{m-1}^2 - \omega^2)} \quad (5a)$$

$$Z = -\frac{j}{\omega} \cdot L \cdot \frac{(\omega_1^2 - \omega^2)(\omega_3^2 - \omega^2) \dots (\omega_{m-1}^2 - \omega^2)}{(\omega_2^2 - \omega^2) \dots (\omega_{m-1}^2 - \omega^2)} \quad (5b)$$

$$Z = +j\omega \cdot \frac{1}{C} \cdot \frac{(\omega_3^2 - \omega^2) \dots (\omega_{m-1}^2 - \omega^2)}{(\omega_2^2 - \omega^2)(\omega_4^2 - \omega^2) \dots (\omega_{m-1}^2 - \omega^2)} \quad (5c)$$

$$Z = -\frac{j}{\omega} \cdot \frac{1}{C} \cdot \frac{(\omega_1^2 - \omega^2)(\omega_3^2 - \omega^2) \dots (\omega_{m-1}^2 - \omega^2)}{(\omega_2^2 - \omega^2)(\omega_4^2 - \omega^2) \dots (\omega_{m-1}^2 - \omega^2)} \quad (5d)$$

where $\omega_1, \omega_3, \omega_5, \dots$ are the zeros of Z , and $\omega_2, \omega_4, \omega_6, \dots$ are the poles of Z ; m is the minimum number of components, as defined in equation 3.

These four equations (5) are the four possible cases of equation (1), and apply respectively to networks having the four types of reactance sketch shown in Fig. S-21. Both forms of Foster network having each of these types of reactance sketch are shown in Fig. S-24, together with the corresponding equation (5) for Z ; while a simple example of each type is shown in Fig. S-25.

FOSTER'S REACTANCE THEOREM

[To face page 864.]

A			
<p>Inductive at Low Frequencies Inductive at High Frequencies m is Odd, n is Even $m_1 = m, m_0 = +1$ $Z = \frac{a_0 s^2 + a_2 s^4 + \dots + (a_{2m-2} s^{2m-2} + a_{2m} s^{2m})}{(b_0 s^2 + b_2 s^4 + \dots + (b_{2n-2} s^{2n-2} + b_{2n} s^{2n}))}$</p>			
<p>Capacitive at Low Frequencies Inductive at High Frequencies m is Even, n is Odd $m_1 = m, m_0 = 0$ $Z = \frac{a_1 s + a_3 s^3 + \dots + (a_{2m-1} s^{2m-1} + a_{2m+1} s^{2m+1})}{(b_0 s^2 + b_2 s^4 + \dots + (b_{2n-2} s^{2n-2} + b_{2n} s^{2n}))}$</p>			
<p>Inductive at Low Frequencies Capacitive at High Frequencies m is Even, n is Odd $m_1 = m, m_0 = 0$ $Z = \frac{a_0 s^2 + a_2 s^4 + \dots + (a_{2m-2} s^{2m-2} + a_{2m} s^{2m})}{(b_1 s + b_3 s^3 + \dots + (b_{2n-1} s^{2n-1} + b_{2n+1} s^{2n+1}))}$</p>			
<p>Capacitive at Low Frequencies Capacitive at High Frequencies m is Odd, n is Even $m_1 = m, m_0 = +1$ $Z = \frac{a_1 s + a_3 s^3 + \dots + (a_{2m-1} s^{2m-1} + a_{2m+1} s^{2m+1})}{(b_1 s + b_3 s^3 + \dots + (b_{2n-1} s^{2n-1} + b_{2n+1} s^{2n+1}))}$</p>			

Fig. S-24.—General cases of Foster networks of each type.

INSERTION LOSS OF A FOUR-TERMINAL NETWORK

In Chapter 13, an expression is given without proof (eq. 7, p. 566) for the insertion loss N of a four-terminal network, viz:—

$$N = A + \log_e \left| \frac{(Z_g + Z_{01})}{2 \sqrt{Z_g Z_{01}}} \right| + \log_e \left| \frac{(Z_L + Z_{02})}{2 \sqrt{Z_L Z_{02}}} \right| - \log_e \left| \frac{(Z_g + Z_L)}{2 \sqrt{Z_g Z_L}} \right| + \log_e \left| 1 - \frac{(Z_g - Z_{01})}{(Z_g + Z_{01})} \cdot \frac{(Z_L - Z_{02})}{(Z_L + Z_{02})} \right| \cdot e^{-2\theta}$$

nepers ... (1)

where :

$$N = \log_e \left| \frac{I_0}{I_R} \right| = \text{insertion loss of network} \quad (2)$$

$\theta = A + jB$ = image transfer constant of network

Z_{01} and Z_{02} = image impedances of network

Z_g = impedance of generator

Z_L = impedance of load

$$I_0 = \frac{E}{Z_g + Z_L} \quad (3)$$

= current that flows when a generator of EMF E is connected directly to the load, as in Fig. S-26.

I_R = current that flows through the load when the network is interposed between the generator and the load, as in Fig. S-27.

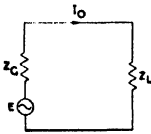


FIG. S-26.—Generator connected directly to load.

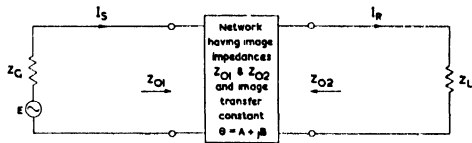


FIG. S-27.—Generator connected to load through network having image impedances Z_{01} , Z_{02} , and image transfer constant $\theta = A + jB$.

This expression (1) can be derived by the direct application of Kirchhoff's Laws, or by evaluation of reflection currents in the manner used on p. 745 in Chapter 15. The former method, although somewhat tedious, is the more straightforward, and is the safer method to employ in the analysis of unfamiliar circuits. The second method, however, shows more clearly the origin and the physical significance of each individual term in (1). Both methods will therefore be given, and the significance of the terms in (1) will then be explained.

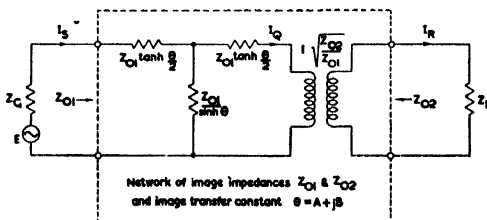


FIG. S-28.—Network of Fig. S-27 represented by a symmetrical T section and a perfect transformer.

Analysis by Kirchhoff's Laws.

The network having the properties postulated (namely, image impedances Z_{01} and Z_{02} , and image transfer constant $\theta = A + jB$) may be represented by the symmetrical T-section and perfect transformer shown in Fig. S-28. For, by equations 21 and 24 of Chapter 13 (pp. 574-5), the T-section shown will have the required image transfer constant θ , and the image impedance at its left-hand (input) terminals will be Z_{01} ; the image impedance at the right-hand (output)

terminals of the network of Fig. S-28 will be $Z_{01} \times \left(\sqrt{\frac{Z_{02}}{Z_{01}}} \right)^2 = Z_{02}$.

Applying Kirchhoff's Law to the left-hand mesh in Fig. S-28 :—

$$E = I_s \cdot \left\{ Z_g + Z_{01} \left(\tanh \frac{\theta}{2} + \frac{1}{\sinh \theta} \right) \right\} - I_q \cdot \frac{Z_{01}}{\sinh \theta} \quad (4)$$

Applying Kirchhoff's Law to the centre mesh in Fig. S-28 :—

$$0 = -I_s \cdot \frac{Z_{01}}{\sinh \theta} + I_q \cdot \left\{ Z_L \cdot \frac{Z_{01}}{Z_{02}} + Z_{01} \left(\tanh \frac{\theta}{2} + \frac{1}{\sinh \theta} \right) \right\} \quad (5)$$

Applying the transformer current equation :—

$$I_R = \sqrt{\frac{Z_{01}}{Z_{02}}} \cdot I_q \quad (6)$$

From (5) :—

$$I_s = I_q \cdot \sinh \theta \cdot \left\{ \frac{Z_L}{Z_{02}} + \tanh \frac{\theta}{2} + \frac{1}{\sinh \theta} \right\}$$

Substituting in (4) :—

$$\begin{aligned} \frac{E}{I_q} &= \left\{ \frac{Z_g}{Z_{02}} \cdot \sinh \theta + \tanh \frac{\theta}{2} \cdot \sinh \theta + 1 \right\} \cdot \\ &\quad \left\{ Z_g + Z_{01} \left(\tanh \frac{\theta}{2} + \frac{1}{\sinh \theta} \right) \right\} - \frac{Z_{01}}{\sinh \theta} \\ &= \frac{Z_g Z_L}{Z_{02}} \sinh \theta + Z_{01} \left(\sinh \theta \cdot \tanh^2 \frac{\theta}{2} + 2 \tanh \frac{\theta}{2} \right) + \\ &\quad + Z_g \left(1 + \sinh \theta \cdot \tanh \frac{\theta}{2} \right) + \frac{Z_L Z_{01}}{Z_{02}} \left(1 + \sinh \theta \cdot \tanh \frac{\theta}{2} \right) \\ &= \frac{(Z_g Z_L + Z_{01} Z_{02}) \sinh \theta + (Z_g Z_{02} + Z_L Z_{01}) \cosh \theta}{Z_{02}} \end{aligned}$$

Hence, from (6) :—

$$\begin{aligned} \frac{E}{I_R} &= \frac{(Z_g Z_L + Z_{01} Z_{02}) \sinh \theta + (Z_g Z_{02} + Z_L Z_{01}) \cosh \theta}{\sqrt{Z_{01} Z_{02}}} \\ \therefore I_R &= \frac{E \cdot \sqrt{Z_{01} Z_{02}}}{(Z_g Z_L + Z_{01} Z_{02}) \sinh \theta + (Z_g Z_{02} + Z_L Z_{01}) \cosh \theta} \quad (7) \end{aligned}$$

By manipulation of this equation, expressions may be obtained, both for I_R and for $\frac{I_0}{I_R}$, that show the physical effect of the network. Expressing $\sinh \theta$ and $\cosh \theta$ in terms of powers of e :—

$$\begin{aligned}
 I_R &= \frac{E \cdot 2\sqrt{Z_{01}Z_{02}}}{(Z_g Z_L + Z_{01}Z_{02} + Z_g Z_{02} + Z_L Z_{01}) \cdot e^\theta - \frac{E \cdot 2\sqrt{Z_{01}Z_{02}}}{(Z_g Z_L + Z_{01}Z_{02} - Z_g Z_{02} - Z_L Z_{01}) \cdot e^{-\theta}}} \\
 &= \frac{E \cdot 2\sqrt{Z_{01}Z_{02}}}{(Z_g + Z_{01})(Z_L + Z_{02}) \cdot e^\theta - (Z_g - Z_{01})(Z_L - Z_{02}) \cdot e^{-\theta}} \\
 &= \frac{E}{(Z_g + Z_L)} \cdot e^{-\theta} \cdot \frac{(Z_g + Z_L) \cdot 2\sqrt{Z_{01}Z_{02}}}{1} \\
 &\quad \left\{ 1 - \frac{(Z_g - Z_{01})}{(Z_g + Z_{01})} \cdot \frac{(Z_L - Z_{02})}{(Z_L + Z_{02})} \cdot e^{-2\theta} \right\}
 \end{aligned}$$

Hence :

$$\begin{aligned}
 I_R &= I_0 \cdot e^{-\theta} \cdot \frac{2\sqrt{Z_g Z_{01}}}{(Z_g + Z_{01})} \cdot \frac{2\sqrt{Z_L Z_{02}}}{(Z_L + Z_{02})} \cdot \frac{(Z_g + Z_L)}{2\sqrt{Z_g Z_L}} \\
 &\quad \left\{ 1 - \frac{(Z_g - Z_{01})}{(Z_g + Z_{01})} \cdot \frac{(Z_L - Z_{02})}{(Z_L + Z_{02})} \cdot e^{-2\theta} \right\} \tag{8}
 \end{aligned}$$

And :

$$\begin{aligned}
 \frac{I_0}{I_R} &= e^\theta \cdot \frac{(Z_g + Z_{01})}{2\sqrt{Z_g Z_{01}}} \cdot \frac{(Z_L + Z_{02})}{2\sqrt{Z_L Z_{02}}} \cdot \frac{2\sqrt{Z_g Z_L}}{(Z_g + Z_L)} \\
 &\quad \left\{ 1 - \frac{(Z_g - Z_{01})}{(Z_g + Z_{01})} \cdot \frac{(Z_L - Z_{02})}{(Z_L + Z_{02})} \cdot e^{-2\theta} \right\} \tag{9}
 \end{aligned}$$

Reflection considerations

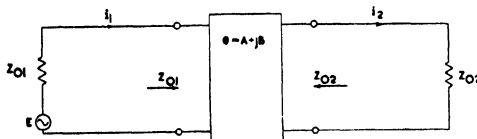


FIG. S-29.—Network having image impedances Z_{01} , Z_{02} , and image transfer constant θ , connected to generator of impedance Z_{01} and to load of impedance Z_{02} so that impedance matching obtains.


Let the network having image impedances Z_{01} and Z_{02} and transfer constant θ be connected to a generator of impedance Z_{01} and EMF E , and to a load of impedance Z_{02} , as in Fig. S-29, so that

impedance matching obtains. The input and output currents i_1 and i_2 that then flow are given by :


$$i_1 = \frac{E}{2Z_{01}} \quad (10)$$

$$i_2 = i_1 \cdot \sqrt{\frac{Z_{01}}{Z_{02}}} \cdot e^{-\theta} = \frac{E}{2\sqrt{Z_{01}Z_{02}}} \cdot e^{-\theta} \quad (11)$$

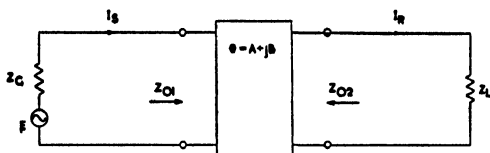Now consider the network connected to the generator of impedance Z_g and the load of impedance Z_L , as in Fig. S-27, which is repeated in Fig. S-30a, and let the input and output currents again be I_g and I_R .



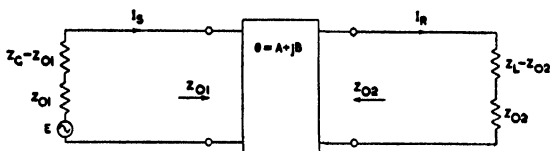
- (a) Network having image impedances Z_{01} , Z_{02} , and image transfer constant θ , connected between generator of impedance Z_g and load of impedance Z_L .



- (b) Generator and load impedances split into two components :

$$Z_g = Z_{01} + (Z_g - Z_{01})$$

$$Z_L = Z_{02} + (Z_L - Z_{02})$$

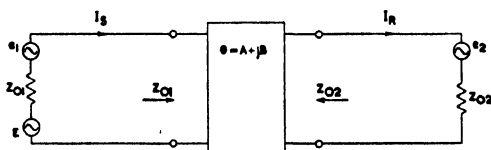

- (c) Impedances $(Z_g - Z_{01})$ and $(Z_L - Z_{02})$ replaced by equivalent generators.

FIG. S-30.—Derivation of insertion loss formula from reflection considerations.

The generator impedance Z_g may be replaced by two impedances, Z_{01} and $(Z_g - Z_{01})$, in series, and the load impedance by Z_{02} and $(Z_L - Z_{02})$, as in Fig. S-30b.

Applying the Compensation theorem, the impedance $(Z_g - Z_{01})$ may now be replaced, as in Fig. S-30c, by a zero-impedance generator of EMF e_1 , such that :—

$$e_1 = -I_g (Z_g - Z_{01}) \quad (12)$$

and the impedance $(Z_L - Z_{02})$ by a generator of EMF e_2 such that:—

$$e_2 = -I_R (Z_L - Z_{02}) \quad (13)$$

Referring to Fig. S-30c, the input and output currents I_s and I_R may each be seen (by application of the Superposition theorem) to consist of three components, due respectively to the three EMFs acting in the circuit, viz.— E , e_1 , and e_2 .

Thus :

$$\begin{aligned}
 I_s &= i_1 + \frac{e_1}{2Z_{01}} + \frac{e_2}{2Z_{02}} \cdot \sqrt{\frac{Z_{02}}{Z_{01}}} \cdot e^{-\theta} \\
 &= i_2 \frac{\sqrt{Z_{01}Z_{02}}}{Z_{01}} \cdot e^{-\theta} - I_s \cdot \frac{Z_{\sigma} - Z_{01}}{2Z_{01}} - I_R \cdot \frac{(Z_L - Z_{02})}{2\sqrt{Z_{01}Z_{02}}} \cdot e^{-\theta} \\
 \therefore I_s \cdot \left\{ 1 + \frac{(Z_{\sigma} - Z_{01})}{2Z_{01}} \right\} &= i_2 \cdot \frac{\sqrt{Z_{01}Z_{02}}}{Z_{01}} \cdot e^{-\theta} - I_R \cdot \frac{(Z_L - Z_{02})}{2\sqrt{Z_{01}Z_{02}}} \cdot e^{-\theta} \\
 \therefore I_s &= \frac{2Z_{01}}{Z_{\sigma} + Z_{01}} \cdot \left\{ i_2 \cdot \frac{Z_{01}Z_{02}}{2Z_{01}} \cdot e^{-\theta} - I_R \cdot \frac{(Z_L - Z_{02})}{2\sqrt{Z_{01}Z_{02}}} \cdot e^{-\theta} \right\} \quad (14)
 \end{aligned}$$

And similarly :

$$\begin{aligned}
 I_R &= i_2 + \frac{e_1}{2Z_{01}} \cdot \sqrt{\frac{Z_{01}}{Z_{02}}} \cdot e^{-\theta} + \frac{e_2}{2Z_{02}} \\
 &= i_2 - I_s \cdot \frac{(Z_{\sigma} - Z_{01})}{2\sqrt{Z_{01}Z_{02}}} \cdot e^{-\theta} - I_R \cdot \frac{(Z_L - Z_{02})}{2Z_{02}}
 \end{aligned}$$

Substituting for I_s from (14) :—

$$\begin{aligned}
 I_R &= i_2 - i_2 \frac{(Z_{\sigma} - Z_{01})}{(Z_{\sigma} + Z_{01})} + I_R \frac{(Z_{\sigma} - Z_{01})}{(Z_{\sigma} + Z_{01})} \cdot \frac{(Z_L - Z_{02})}{2Z_{02}} \cdot e^{-2\theta} \\
 &\quad - I_R \cdot \frac{(Z_L - Z_{02})}{2Z_{02}} \\
 \therefore I_R \cdot \left\{ 1 + \frac{(Z_L - Z_{02})}{2 \cdot Z_{02}} - \frac{(Z_{\sigma} - Z_{01})(Z_L - Z_{02})}{(Z_{\sigma} + Z_{01}) \cdot 2Z_{02}} \cdot e^{-2\theta} \right\} \\
 &= i_2 \left\{ 1 - \frac{Z_{\sigma} - Z_{01}}{(Z_{\sigma} + Z_{01})} \right\} \\
 \therefore I_R \cdot \left\{ 1 - \frac{(Z_{\sigma} - Z_{01})}{(Z_{\sigma} + Z_{01})} \cdot \frac{(Z_L - Z_{02})}{(Z_L + Z_{02})} \cdot e^{-2\theta} \right\} &= \frac{4Z_{01}Z_{02}}{(Z_{\sigma} + Z_{01})(Z_L + Z_{02})} \cdot i_2 \\
 &= \frac{4Z_{01}Z_{02}}{(Z_{\sigma} + Z_{01})(Z_L + Z_{02})} \cdot \frac{E}{2\sqrt{Z_{01}Z_{02}}} \cdot e^{-\theta}
 \end{aligned}$$

Hence

$$\begin{aligned}
 I_R &= \frac{E}{(Z_{\sigma} + Z_L)} \cdot e^{-\theta} \cdot \frac{2\sqrt{Z_{\sigma}Z_{01}}}{(Z_{\sigma} + Z_{01})} \cdot \frac{2\sqrt{Z_LZ_{02}}}{(Z_L + Z_{02})} \cdot \frac{(Z_{\sigma} + Z_L)}{2\sqrt{Z_{\sigma}Z_L}} \times \\
 &\quad \frac{1}{\left\{ 1 - \frac{(Z_{\sigma} - Z_{01})}{(Z_{\sigma} + Z_{01})} \cdot \frac{(Z_L - Z_{02})}{(Z_L + Z_{02})} \cdot e^{-2\theta} \right\}} \quad (15)
 \end{aligned}$$

$$\therefore \frac{I_0}{I_R} = e^{\theta} \cdot \frac{(Z_G + Z_{01})}{2 \sqrt{Z_G Z_{01}}} \cdot \frac{(Z_L + Z_{02})}{2 \sqrt{Z_L Z_{02}}} \cdot \frac{2 \sqrt{Z_G Z_L}}{(Z_G + Z_L)} \times \left\{ 1 - \frac{(Z_G - Z_{01})}{(Z_G + Z_{01})} \cdot \frac{(Z_L - Z_{02})}{(Z_L + Z_{02})} \cdot e^{-2\theta} \right\} \quad (16)$$

which is the same as (9) obtained by another method.

Hence the insertion loss N is given by :

$$N = \log_e \left| \frac{I_0}{I_R} \right| = A + \log_e \left| \frac{(Z_G + Z_{01})}{2 \sqrt{Z_G Z_{01}}} \right| + \log_e \left| \frac{(Z_L + Z_{02})}{2 \sqrt{Z_L Z_{02}}} \right| - \log_e \left| \frac{(Z_G + Z_L)}{2 \sqrt{Z_G Z_L}} \right| + \log_e \left| 1 - \frac{(Z_G - Z_{01})}{(Z_G + Z_{01})} \cdot \frac{(Z_L - Z_{02})}{(Z_L + Z_{02})} \cdot e^{-2\theta} \right| \quad (17)$$

Significance of individual terms

In equations 8 and 15 for I_R , the first factor $\frac{E}{Z_G + Z_L}$ represents the current I_0 that would flow in the absence of the network, *i.e.*, with the generator connected directly to the load, as in Fig. S-26.

The second factor, $e^{-\theta}$, expresses the effects of the transfer constant, *i.e.*, the attenuation and phase-shift, which are defined to be independent of the impedance conditions obtaining at the input and output terminals of the network.

The third factor $\frac{2 \sqrt{Z_G Z_{01}}}{(Z_G + Z_{01})}$ is the "reflection factor" of the impedances Z_G and Z_{01} , and is a measure of the transmission loss due to the impedance mismatch at the input terminals of the network.

The fourth factor $\frac{2 \sqrt{Z_L Z_{02}}}{(Z_L + Z_{02})}$ is the reflection factor of the impedances Z_L and Z_{02} , and is a measure of the transmission loss due to the impedance mismatch at the output terminals of the network.

The fifth factor $\frac{(Z_G + Z_L)}{2 \sqrt{Z_G \cdot Z_L}}$ is the reciprocal of the reflection factor of the impedances Z_G and Z_L , and it allows for the mismatching that occurs when the generator is connected directly to the load as in Fig. S-26. This has to be taken into account, because of the nature of the definition of N (eq. 2), and the definition of I_0 (eq. 3).

The sixth and last term in the equation for I_R , *viz.*,

$$\left\{ 1 - \frac{(Z_G - Z_{01})}{(Z_G + Z_{01})} \cdot \frac{(Z_L - Z_{02})}{(Z_L + Z_{02})} \cdot e^{-2\theta} \right\},$$

is called the "interaction factor", and is frequently designated by σ . It expresses the effects of the multiple reflections that occur

within the network, *i.e.*, current that travels from one end of the network to the other, is reflected, and travels back to its starting point, where it is reflected again, and so on, suffering at each journey the attenuation and phase-shift of the network. The effects of the interaction factor are usually small: if approximate impedance matching obtains at the input and output terminals, or if the attenuation of the network is large, the effect of this factor will be of only secondary importance; while if both these conditions hold, its effects are likely to be altogether negligible.

The various factors of equations 9 and 16 for $\frac{I_0}{I_R}$ are the reciprocals of factors 2 to 6 above, and the terms of equations 1 and 17 for N are the natural logarithms of the moduli of these. Thus, for example, the first term in (1) is:

$$\log_e |e^\theta| = \text{real part of } \theta = A$$

Example.—

A generator of internal impedance 300Ω is connected to a 400Ω load. If a symmetrical 600Ω 10 db pad is interposed between the generator and the load, by how much will the power reaching the load be reduced?

Here

$$\begin{aligned} Z_g &= 300\Omega \\ Z_L &= 400\Omega \\ Z_{01} &= Z_{02} = 600\Omega \\ A &= 10 \text{ db} = 1.1513 \text{ nepers} \end{aligned}$$

Hence the insertion loss N of the pad is given by:—

$$\begin{aligned} N &= 1.1513 + \log_e \left\{ \frac{Z_g + Z_{01}}{2\sqrt{Z_g Z_{01}}} \cdot \frac{Z_L + Z_{02}}{2\sqrt{Z_L Z_{02}}} \cdot \frac{2\sqrt{Z_g Z_L}}{Z_g + Z_L} \right. \\ &\quad \left. \left[1 - \frac{Z_g - Z_{01}}{Z_g + Z_{01}} \cdot \frac{Z_L - Z_{02}}{Z_L + Z_{02}} \cdot e^{-2.3026} \right] \right\} \\ &= 1.1513 + \log_e \left\{ \frac{300 + 600}{2\sqrt{180000}} \cdot \frac{400 + 600}{2\sqrt{240000}} \cdot \frac{2\sqrt{120000}}{300 + 400} \right. \\ &\quad \left. \left[1 - \frac{300 - 600}{300 + 600} \cdot \frac{400 - 600}{400 + 600} \cdot e^{-2.3026} \right] \right\} \\ &= 1.1513 + \log_e (1.0606 \cdot 1.0205 \cdot 0.9898 \cdot 0.09933) \\ &= 1.1513 + \log_e 1.064 \\ &= 1.1513 + 0.0621 \\ &= 1.2134 \text{ nepers} \\ &= 1.2134 \cdot 8.686 = 10.54 \text{ db.} \end{aligned}$$

Conversion to decibels simply by multiplying by 8.686 is justified, because the insertion loss is obtained in terms of the ratio of two currents through the same impedance (Z_L).

Example 2.—

What would be the effect of inserting the pad in the previous example, if the impedance of the load had been 1200Ω ?

In this case,

$$Z_g = 300\Omega$$

$$Z_L = 1200\Omega$$

$$Z_{01} = Z_{02} = 600\Omega$$

$$A = 10 \text{ db} = 1.1513 \text{ nepers}$$

Hence :

$$\begin{aligned} N &= 1.1513 + \log_e \left\{ \frac{300 + 600}{2\sqrt{180000}} \cdot \frac{1200 + 600}{2\sqrt{720000}} \cdot \frac{2\sqrt{360000}}{300 + 1200} \cdot \left[1 - \frac{300 - 600}{300 + 600} \cdot \frac{1200 - 600}{1200 + 600} \cdot e^{-2 \cdot 3026} \right] \right\} \\ &= 1.1513 + \log_e (1.0606 \cdot 1.0606 \cdot 0.80 \cdot 1.1011) \\ &= 1.1513 + \log_e 0.90999 \\ &= 1.1513 + \bar{1}.9057 \\ &= 1.057 \text{ nepers} \\ &= 9.180 \text{ db.} \end{aligned}$$

It will be noticed that the insertion loss in this case is less than the attenuation A of the pad. This results from the definition of insertion loss as the reduction in power in the load caused by the introduction of the network, and from the fact that, in this example, introduction of the network avoids the extreme mismatch that occurs when a 300Ω generator is connected directly to a 1200Ω load.

INDEX

VOLUME I

Pages 1 — 842

A

	Page
AC bridges	268
AC circuits	231
AC meters,	288
frequency errors of	293
temperature errors of	293
AC resistance of valve	335
Addition of two sine waves	493
Admittance	200
After-glow of fluorescent screen	535
AGC,	398
delayed	399
Agitation, thermal	405
Airline, loading of	740
Algebra	20, 48
Alternating currents,	187
in a condenser	198
in an inductance	198
in a resistance	197
Alternating voltages,	168, 189
addition of	196
Ammeters,	173
rectifier	292
Amplification factor	333
Amplifiers,	14, 376
buffer	473
class A	405
class AB	417
class B	416
class C	419
conditionally stable	495
deflection	549
feedback	421
gain control	379
input transformer	394
L-C coupled	387
pentode	361
power	405
push-pull	413
R-C coupled	376
stability	454
transformer-coupled	389
triode	338
triode, equivalent circuit of	344
tuned	394
voltage	376
Amplitude, control	548
distortion	404
modulation	498, 529
Analysis, harmonic	101
harmonic of square waveform	104
of input and output curves	112
12-ordinate	107

	Page
Angles,	35
general forms	39
negative	38
particular	39
small	39
Angular measure	35
Angular velocity	64, 189
Anode	325
Anode characteristics	333
Anode decoupling	374
Antilogarithms,	25
tables	786
Anti-resonance	215
Apparent power	208
Application of, CRO	553
line equations	756
NFB	439, 444, 461
Areas, formulae	21
Argument	56
Arithmetical progression	27
Asymmetrical networks,	561, 564
image impedance	565
image transfer constant	565
iterative impedance	564
Asymptotes	31
ATMITE	296
Atomic, structure	118
numbers	119
weights	119
Attenuating networks	606
Attenuation,	13, 605
band, filters	635
conditions for minimum	726
constant, filters	636
constant, networks	563
constant, line transmission	710
distortion,	403
distortion, effect of NFB on	427
equalisers	740
frequency of infinite	652
Attenuators,	606
bridged-T	612
design of	614
design, π type	621
design, T type	620
L type	610
π type	611
T type	607
variable	295, 622
Auto exchange	13
Auto transformer	264
AVC	398
Axes, graphical	28
quartz crystal	691

B

	Page
Balanced, circuit	18
L section	612
modulators	507, 512, 515, 527
π section	612
section	612
section, equivalence to unbalanced	569
symmetrical filters	635
T section	612
Ballistic meters	177
Band-pass coupling	396
Band-pass filters,	664, 672
band-width	667
design for VF telegraphy	681
double crystal	696
impedance transformation	679
lattice-type crystal	698
<i>m</i> -derived	669
mid-band frequency	667
pass-band	666
prototype, design of	668
single crystal	695
T-type crystal	697
Bands, side	499
Band-stop filters,	673, 677
band-width	674
<i>m</i> -derived	676
mid-band frequency	675
prototype design	675
Barretter	319
Barrier layer	275
Battery bias	368
Beam forming plate	355
Beam tetrode	355
Beat frequency,	494
oscillator	486
Beat notes	494
B-H curve	155, 160, 266
Bias,	367
battery	368
cathode	369
cut-off	333
filament current	368
grid leak	370, 469
Biassing of rectifiers	294
Binomial theorem	48
Bridge circuit,	268
rectification	285
lamp	633
Wheatstone's	129
Bridge ring modulator	512, 515

	Page
Bridged-T network,	568, 612
characteristic impedance	588
equivalent of lattice filter	689
open- and short-circuit impedances	589
propagation constant	590
Bridges, AC	268
impedance	268, 707
Brilliance of trace	534
Broad-band crystal filter	701
Buffer amplifier	473
Building-out	785

C

C section	567
Cables, loaded	726
loaded, practical formulae for	741
submarine	731
underground, loading of	740
unloaded, practical formulae for	724
Calculus, differential	67
integral	81
notation	68
Calibration of TMS	633
Call, multiple	9
loop	13
Campbell's formula	769
Capacitance of transmission line	717
Capacity,	135
between two parallel wires	141
inter-electrode	348
parallel plate condenser	135
two co-axial cylinders	138
Carbon-pile regulator	313
Carrier,	498
leak	507
suppressed	502
telephony	19
Cathode,	323
bias	369
construction of	324
follower	455
Cathode ray oscilloscope,	532
amplitude control	548
applications of	553
current measurements	553
deflection amplifiers	549
frequency comparison	554
phase-shift measurements	555
shift controls	553
voltage measurements	553

	Page
Cathode ray tube,	533
distortion in	553
power supply for	553
CB exchange	11
CBS system	11
Cells, Weston cadmium	122
Central battery signalling	11
Ceramic condensers	142
Characteristic impedance,	561
bridged-T section	588
determination from line constants	718
filters	636
lattice section	586
π section	577
T section	570
transmission line	703, 749
Characteristics, impedance-frequency, of transmission line	763
valve	331
Charge and discharge of condenser	145
Choke-capacity coupled amplifier	387
Choke-input filter	301
Chords of angles, tables	818
Circuit, balanced	18
containing L R & C	183
four-wire	15
phantom	18
physical	17
two-wire	14
Circular functions	35, 90, 822
Class, A amplifier	405
AB amplifiers	417
B amplifiers	413
C amplifiers	419
Cobalt alloys	266
Codes, telegraph	2
Coefficient of reflection	745
Coercivity	157
Coil-loaded line	768
Coils, loading	732
self-inductance of	169
Cold-cathode	320
Colpitt's oscillator	467
Common battery exchange	11
Common logarithms, tables	784
Compensating networks	679
Compensation theorem	236
Complementary Functions	101
Complex hyperbolic functions	95, 825, 829
Composite negative feedback	445

	Page
Condenser-input filter	301
Condensers,	136
alternating currents in	198
ceramic	142
charge and discharge of	145
electrolytic	142
impedance of	200
in parallel	144
in series	144
mica	142
paper	142
time constant of	148
Conditionally stable amplifiers	459
Conditions for minimum, attenuation	726
distortion	728
Conductance,	125, 222
mutual	334
Conductors, definition of	121
Constant, attenuation	563, 710
image transfer	565
phase	564, 710
propagation	562, 709
wave-length	710
Constant-current generator	235, 345, 361
Constant- h filter section	639
Constant-voltage generator	233, 345
Constants, primary line	717, 749
secondary line	703, 717, 749
valve	331
Contact noise	405
Continuous loading	730
Co-planar grid valve	365
Copper losses	256
Copper-oxide rectifiers	275
Core materials	265
Cosine	36, 40
tables	808
Coulomb	118, 131
Coulomb's theorem	137
Counter electrode	275
Couple	166, 173
Coupling,	
R-C	376
L-C	387
transformer	389
band-pass	396

	Page
Cowan modulator	511
Crash limiter	296
Critical distance tetrode	353
CRO (<i>see</i> Cathode ray oscilloscope)	
Cross-talk	13
Crystal filters,	691
broad-band lattice	701
double	696
lattice	698
single	695
T type	697
Crystal quartz,	691
addition of series inductance to	700
matched pair	700
X-cut	692
Current, distribution transmission line	712, 750
grid	346
negative feedback	440
screen	351
stabilisers	319
Currents, alternating	187
Conditions for maximum	227
Currents, direct	118
Cut-off bias	333
Cut-off frequency, filters	635
loaded line	731, 737, 769

D

Damping	175
Damped oscillations	186
Dashpot	177, 313
db	238, 605
dbm	241
DC meters	174
Decibel,	238, 605
meters	623
Decoupling,	372
anode	374
grid	372
Definite integrals	87
Deflection, amplifiers	549
electrostatic	540
electromagnetic	532
of electron beam	539
Degrees	35, 800, 804
Demodulation,	502
in suppressed carrier systems	526
Demodulators	520, 526

	Page
Derivatives,	69
partial	80
Derivation of line equations	749
Design impedance, filters	640
Design of, attenuators	614
band-pass filters	668
band-stop filters	675
high-pass filters	649
low-pass filters	645
pads	614
Detection, linear	520
square law	524
Detector, use of diode	327, 522
use of metal rectifier	524
Diamagnetism	159
Dielectric, breakdown	142
constant	141
strength	142
Dielectrics	142
Differential, calculus	67
equations	98
Differentiation,	68
partial	80
Diode,	324
detector	322, 327
double	328
saturation current	327
voltage doubler	328
Dissymmetrical networks	561
Distortion,	13, 403, 728
amplitude	404
attenuation	403
cathode ray tubes	553
effect of NFB on	427
harmonic	404
intermodulation	404
non-linear	403
phase	403
transmission line	728
Distortionless condition	729
Distribution of voltage and current along line	712, 750
Double-balanced modulators	512, 515
Double band-pass filter	639
Double-beam oscilloscope	550
Double-crystal band-pass filter	696
Double-diode	328
Double-phantom	18
Dust core	266
Dynamic characteristics	339
Dynatron oscillator	352, 480

B

	Page
Earth-return Phantom Circuit	17
Eddy current,	175
loss	255
Effects of loading	744
Effects of lumped loading	739
Efficiency of power amplifiers	409
Electrical axis of quartz crystal	691
Electrolytic condensers	142
Electromagnetic, deflection of electron beam	539
focusing	537
induction	166
units	130
Electromagnetism	160
Electro-motive force	122
Electron	118, 323
Electron-coupled oscillator	474
Electronic theory	118
Electrostatic deflection of electron beam	540
Electrostatic focusing	537
Electrostatics	133
Electrostatic units	130
Elementary filter sections	636
Elements	118
Emission, secondary	348
thermionic	323
Equalisers,	13, 15
attenuation	740
phase	740
Equations, commonly occurring curves	33, 34
differential	98
general line	754
linear	29
quadratic	24
simultaneous	23
solution by graphs	30
Equations, line, derivation of	749
general case	761
hyperbolic functions	752
particular applications	756
Equivalence, of balanced and unbalanced sections	569
complex networks to 3-element configuration	584
theorems for networks	590
Equivalent bridged-T sections of lattice filters	689
quivalent circuit, coil loaded line	768
quartz crystal	692
RC coupled amplifier	377
triode amplifier	344
Equivalent lattice section of a line	767

	Page
Equivalent networks, line	766
Equivalent π and T sections of a perfect transformer	596
Equivalent π section of a line	767
Equivalent T section of a line	705, 767
Erg	132
Exchange, auto	13
CB	11
purpose of	8
signalling	11
Exponential series	48

F

Factorial	48
Factorisation	23
Farad	136
Faraday's Law	166
Fault location, use of input impedance-frequency curve for	765
Feedback,	421
composite	445
current	440
factor	422
instability	423
negative	425
oscillation	423
oscillators	426
parallel	453
positive	421
series	451
voltage	434
Ferromagnetism	159
Field strength	134
Field, at centre of a coil	161
at centre of a solenoid	162
rotation of coil in	167
Field strength, magnetic	151
Filament current bias	368
Filters,	635
band-pass	664, 678
band-stop	673
compensating networks	679
constant- k section	639
cut-off frequency	638
crystal	691
crystal, lattice section	698
design impedance	640
effect of resistance on	662
general characteristics	636
high-pass	636, 646, 655
impedance matching of	656
impedance transformation in	682

	Page
Filters—contd.	
insertion loss	566, 687
lattice section	684
low-pass	636, 640, 650, 652, 658, 686, 690
<i>m</i> -derived	669, 676
mismatch loss	660
prototype sections	640
termination of	677
Fleming's left-hand rule	163
Fleming's right-hand rule	167
Fluorescent screen,	532
afterglow	541
Flux, density	152
leakage loss	256
Flyback	541
Focusing, electromagnetic	537
electrostatic	537
gas	536
Form factor	192
Formulae, Campbell's	769
double angle	44
multiple angle	42
solution of triangles	46
Four-terminal network, insertion loss	566
Four-wire circuit	15
Fourier's theorem,	101, 189
particular cases of symmetry	115
analysis of common waveforms	117
Free grid, effect of	348
Frequency,	187
bridges	269
changer valves	364
comparison using CRO	554
coverage of variable frequency oscillator	484
cut-off, of filters	638
cut-off, of transmission line	731, 737, 769
effect on gain of R-C amplifier	378
impedance characteristic of transmission line	763
of infinite attenuation	652
modulation	530
reactance curve of filters	639
spectrum	187
stability of oscillators	472
synchronisation	496
Full phantom circuit	18
Fullerphone	16
Full-wave rectification,	285
wave form	117, 300
Functional notation	28
Functions, circular	89
complementary	101
complex	95
hyperbolic	91
inverse	38
rate of change of	67

G

	Page
Gain control	397
Gain, variation with frequency	378
Gain, measurement of	630
Gain of NFB amplifier	426
Gas, effect on triode	347
focusing in CRO	536
relays	545
General line equations	747, 754
Geometrical progression	27
Geometry,	21
co-ordinate	34
Graphical calculators	829
Graphs,	28
general rules for plotting	31
Grid,	328
bias	469
coplanar	365
current	346
decoupling	372
leak bias	370
modulation	505
screen	350
suppressor	358

H

H section	567
Half-coil termination	739, 769
Half-section	580
Half-section filters, image impedance	657
impedance matching	656
<i>m</i> -derived	658
π terminating	660
T terminating	660
terminating	657
Half-section, image impedance	582
iterative impedance	581
loading termination	739
open- and short-circuit impedances	583
termination	769
Half-wave rectification	284
waveform	117, 300
Harmonic,	189
analysis	101
analysis of square waveform	104
Harmonic distortion,	404
Class A amplifier	410
Hartley oscillator	467
Henry	169

	Page
Heptode	365
Heptode, triode-	365
Hexode	365
Hexode, triode-	365
High-frequency time bases	548
High-pass filters,	636
<i>m</i> -derived	655
prototype	646
prototype design	649
Horse power	132
Hot-wire meters	179, 289
Hum	404
Hybrid transformer	14
Hyperbolic cosine,	91
tables	796
Hyperbolic functions,	91, 822
differential coefficients of	95
complex	95, 754, 825
identities	93
line equations	752
Hyperbolic sine,	91
tables	794
Hyperbolic tangent,	93
tables	798
Hypernik	266
Hysteresis,	155
coefficient	159
distortion	266
loss	155, 255
Hysteresis curve,	155
plotting with CRO	559

I

Ideal transformer	244
Identities, hyperbolic	93, 94
Identities, trigonometrical	40
Image attenuation constant	566
Image impedance,	565, 607
half-section	582
half-section filter	657
L section	585
Image phase constant	566
Image transfer constant,	565
Impedance,	199
bridges	269, 707
calculation of	201
conditions for maximum	227

	Page
Impedance—contd.	
conditions for minimum	227
design of filters	640
frequency characteristics of transmission line	763
image	565, 582, 585, 607, 657
matching of filters	656
of condenser	200
of inductance	200
of parallel circuit at resonance	216
of resistance	200
of series circuit at resonance	212
Impedance, characteristic,	607
determination from line constants	718
of a filter	636
of a transmission line	703, 706, 749, 757
Impedance, input, effect of NFB on	452
transmission line	762
Impedance, output, effect of voltage NFB on	435
effect of current NFB on	441
effect of composite NFB on	447
Impedance transformation,	247
in filters	679, 682
Incident current, reflection in transmission line	746
Indicator, supervisory	11
Indices	22
Inductance,	169
alternating current in	198
construction of	170
impedance of	200
series, of crystal filters	700
transmission line	717
two parallel wires	170
Induction, lines of	152
Induction, magnetic	153
Infinite transmission line	703, 0
Input impedance, fault location	765
series feedback	452
parallel feedback	454
T section having a high attenuation	576
T section terminated in Z_0	575
Input transformers, amplifiers	394
Insertion loss, four-terminal network	536
lattice filters	687
Instability, effect of feedback	423
of NFB amplifiers	457
Instantaneous power	208
Instantaneous values	189
Insulators, definition of	121
Integral, definite	87
particular	101
Integrals of harmonic functions	102

	Page
Integration,	81, 826, 828
area under curve	86
by algebraic substitution	84
by expansion	82
by partial fractions	83
Interelectrode capacity	348
Intermodulation distortion	404
International units	131
Interwinding capacities	267
Inverse functions	38, 73
Ions	120
Iron cores	265
Iron losses	255
Isotopes	120
Iterative impedance, asymmetrical network	564
half-section	581
L section	585

J

Joule	133
Junction lines	9

K

k-section, filters	639
Kirchhoff's laws	126, 231

L

L-C circuit oscillator	464
L-C coupled amplifier	388
L section,	567, 584
image impedance	585
iterative impedance	585
attenuator	610
Ladder networks	567
Lamp bridge	273, 633
stabilisation	478
Laplace's law	160
Lattice filter section,	684
crystal	698
crystal broad-band	701
equivalent bridged-T network	698
insertion loss	687
Lattice network	568

	Page
Lattice section,	586
characteristic impedance	586
equivalence to a π section	603
equivalence to a T section	599
equivalent of line	766
open- and short-circuit impedance	587
propagation constant	587
with series impedance	598
with shunt impedance	600
Laws, Faraday's	166
Laplace's	160
Lenz's	166
Ohm's	123
Leakance of transmission line	717
Left-hand rule	163
Lenz's Law	166
Level measurement	624
Level, power, measurement of	624
Limiters, voltage	296
Line constants, primary	717, 758
relationship	718
secondary	717, 758
table	723
Line equations,	756
derivation of	749
general case	761
hyperbolic functions	752
particular applications	756
Line, loaded	726, 768
Campbell's formula	769
Line transformers	262
Line transmission,	703
constants	749
equivalent networks	766
mathematical treatment	749
minimum distortion	728
Linear detection	520
Linear equations	29, 99
Linear impedance	231
Linear time-base	542
Lines of force	150
Lines of induction	152
Lissajous figures	557
Load lines,	341
L-C amplifiers	389
R-C amplifiers	386
Loaded line,	726, 768
Campbell's formula	769
equivalent circuit	768
propagation constant	768
Loading,	726, 768
airline	740
coils	732

	Page
Loading— <i>contd.</i>	
continuous	730
cut-off frequency	731, 737
effects	744
half-coil termination	739
half-section termination	739
lumped	731, 739
patch	731
phantom circuit	736
pots	732
side circuits	736
stub cables	736
underground	740
Location of faults, by input impedance	765
Logarithms,	25
charge of base	25
common, tables	784
multiplication by	25
Napierian	50, 788
units	240
Logarithmic spiral	716
Loop gain	423
Loose coupling	256
Loss, due to insertion of filter	687
due to mismatch of filter	660
insertion	566
" Loss " measurement	625
Losses, measurement of	630
Low-pass filter,	636
<i>m</i> -derived	652
prototype	640
prototype design	645
prototype mathematical treatment	644
Lower sideband	499
Lumped loading	731, 739, 768

M

<i>m</i> -derived filters,	650
band-pass	669
band-stop	676
high-pass	655
low-pass	652
π section	652
T section	651
terminating half-sections	657
Maclaurin's theorem	89
Magnetic, field strength	151
flux	155
induction	153
moment	152
Magnetising coefficient	255
Magnetism,	149
para-	159
dia-	159
electro	160

	Page
Magneto, signalling	11
Magnets, permanent	149
Mains transformers,	259
power loss	261
temperature rise	261
Matched pair crystal filters	700
Matching, impedance	250, 461, 656
of filters	656
Mathematical tables	775
Mathematical treatment of, line transmission	749
low-pass filter	644
tuned-anode oscillator	470
Maxima and minima	76
Maximum current	227
Maximum impedance	227
Maximum power transfer	249
Maximum power transfer theorem	132, 236
Maximum voltage	227
Maxwell Bridge	271
Mean, arithmetic	28
geometric	28
values of sine waves	189
Measurements of, gain	630
loss	630
resistance	128
Measurements, " Level "	624
" Loss "	625
" Terminating "	625
" Through "	625
" Transmission "	625
Measuring sets, transmission	631
Mechanical axis, quartz crystal	691
Mesh	590
Mesotron	120
Metal rectifiers,	275
as detectors	524
as modulators	504
characteristics of	276
effect of temperature on	283
markings of	283
self-capacity of	284
Meters, AC	288
ballistic	177
db-	626
DC	174
decibel-	626
high current ranges	292
hot-wire	179, 289
low voltage ranges	288
moving coil	174, 288
moving iron	289
rectifier	289
rectifier as shunt	181, 289
thermocouple	182, 299
shunts for	5
Microphone	5

	Page
Microphonic noise	404
Miller effect	350
Milliammeter, rectifier	292
Minimum attenuation, transmission line	726
Minimum distortion, transmission line	728
Minimum impedance	227
Mismatch loss, filters	660
Modulation,	493
amplitude	529
factor	499
frequency	530
grid	505
phase	530
suppressed carrier	506
Modulators,	503
balanced	507
balanced for demodulation	527
bridge ring	512, 515
Cowan	511
double-balanced	512, 515
double-balanced for demodulation	528
metal rectifier	524
non-linear	503
thermionic valve	504
Modulus	56
Molecule	118
Morse code	2
Moving coil meters	174, 288
Moving iron meters	177, 288
Mu-metal	179, 266
Multi-channel, carrier systems	19
VF telegraphy	18
VF telegraphy, filters	681
Multiple calls	9
Multivibrator	490
Murray code	2
Mutual, conductance	334
inductance	169, 256

N

Napierian logarithms	50
Niches	788
Negative feedback,	425, 433
Negative bias	426
amplifiers, instability	459
amplifier	445
cutoff	440
effect of large amount	425
effect on distortion	427
effect on gain	425
effect on output impedance	435

	Page
Negative feedback—<i>contd.</i>	
parallel	453
practical applications	439, 444, 450, 455
series	451
voltage	434
Negative resistance,	352
oscillators	478
Neon stabiliser,	320
for oscillator	476
Neon tube	320, 477
Neper	564, 605
Network theorems	231
Networks,	126, 561, 606, 635, 705, 766
asymmetrical	561, 564
balanced	569, 612
bridged-T	568, 588, 612
compensating, for filters	679
dissymmetrical	561, 564
equivalence theorems	590
equivalent to line	766
four-terminal	561
L type	567, 584
ladder	567
lattice	568, 598, 614, 767
π type	567, 577, 767
recurrent	567
symmetrical	561, 607
T type	567, 569
three-element	594, 767
unbalanced	569, 612, 635
Networks, attenuating	606
asymmetrical	607
balanced	612
bridged-T type	612
L type	610
lattice type	614
π type	611
symmetrical	607
T type	607
unbalanced	612
Neutron	120
NFB (<i>see</i> Negative feedback)	
Nickel-iron alloys	266
Noise,	404
contact	404
effect of NFB on	432
hum	404
thermal agitation	405
valve	405
Non-linear distortion,	403
effect of NFB on	428
Non-linear impedance modulator	503
Norton's theorem	235
Notes, beat	494
Nyquist's condition	461

O

	Page
O section	567
Octave	187
Ohm's law	123
Open-circuit impedance of transmission line	706, 757
Optical axis, quartz crystal	691
Oscillation, conditions for	463
Nyquist's condition	461
parasitic	483
Oscillators,	463
beat frequency	484
Colpitt's	468
dynatron	352, 480
electron-coupled	474
feedback	423, 463
Hartley	467
L-C circuit	464
negative resistance	478
output voltage	475
push-pull	468
R-C	486, 489
relaxation	463
resistance-capacity	486, 489
resistance stabilised	473
stabilisation of output voltage	475
stability	471
transitron	481
tuned-anode	464, 470
tuned-anode tuned-grid	482
tuned-grid	466
variable frequency	484
Oscilloscope, cathode ray	532
Output impedance, effect of NFB on	435, 441, 447
Output tetrode	357
Output voltage of oscillator	475

P

Pad,	606
asymmetrical	607
balanced	612
bridged-T	612
design	614
L type	610
lattice type	614
π type	611
symmetrical	607
T type	607
unbalanced	612
Parallel circuit, currents at resonance	612
impedance at resonance	216
resonant at all frequencies	220
Parallel resonance,	215, 229
bridge	272, 707

	Page
Parallel feedback	453
Paramagnetism	159
Parasitic oscillation	483
Partial differentiation	80
Particular integral	101
Pass band of filter	635, 666
Patch loading	731
Perfect transformer, equivalent T and π section	244 596
Permalloy	266
Permanent magnets	149
Permeability	151, 169
Perminvar	266
Pentode,	358
as amplifier	361
as power amplifier	408
as R-C amplifier	379
variable- μ	360
Phantom circuits,	17
loading	736
Phase,	63, 192
constant	564, 710
difference	192, 194
distortion	403
distortion, effect of NFB on	431
ellipse	556
equalisers	740
-shift in amplifiers	380
-shift, measurement using CRO	558
-shift in filters	636
Physical circuits	17
π section,	567, 577
attenuator or pad	611
attenuator, design of	621
characteristic impedance of	577
equivalent of transmission line	766
filters	635
filters m-derived	652
open and short circuit impedance of	578
propagation constant	579
Piezo-electric effect	691
Pole strength	151
Pollard's theorem	233
Positive feedback	421
Positron	120
Post Office box	130
Potential,	134
difference	134
Pots loading	782

	Page
Power,	132
AC circuits	208
amplifier	339, 405
apparent	208
factor	208
hysteresis loss	157
instantaneous	208
level in decibels	241
level measurement	624
maximum transfer theorem	133
pure reactance	208
ratios	238
ratios in decibels	240
reference level	241
supplies	299
supply for CRO	553
supply units	313
transformer losses	254, 261
transmission measurements	623
true	208
Practical units	131
Primary line constants,	717, 749
determination of	758
Progression, arithmetical	27
geometrical	27
Propagation constant,	562, 709
Propagation constant, bridged-T section	588
filters	636
lattice section	587
lump loaded line	768
π section	579
symmetrical networks	562
T section	572
transmission line	709, 731, 749
Propagation, velocity of	716
Proton	120
Prototype filter sections,	640
band-pass	664
band-pass, design of	668
band-stop	672
band-stop, design of	675
characteristics	650
high-pass	646
high-pass, design of	649
low-pass	640
low-pass, design of	645
Puckle's time base	548
Push-pull amplifier, class A	413
class AB	417
class B	416
Push-pull oscillators	468
Q	
Q factor	213
Quadratic equations	24

	Page
Quartz crystal,	691
filters	691
equivalent circuit of	692
X-cut	692

E

Radian	35, 800, 804
Radiometal	266
Rationalisation	22
Ratios trigonometrical	35, 37
angles greater than 90°	37
differential coefficients of	73
graphs of	40
particular angles	40
Reactance-frequency curves of filters	639
Reactance sketches,	222
filters	639
Receiver, telephone	8
Reciprocals, tables	776
Rectification circuits	284
Rectifier, biasing of	293
Rectifier, diode	327
metal	275
metal as detector	524
metal as modulator	504
meters	289
-type db meters	626
Recurrent networks	567
Reference power for transmission measurements	623
Reflected current	745
Reflected impedance	258
Reflection, coefficient	745
current in transmission lines	746
in transmission lines	717
Regeneration	421
Regulation voltage	300
Relaxation oscillator	463
Relay slugging using rectifier	299
Repeaters	13
Reservoir condenser	301
Resistance, alternating current in	197
AC of triode	335
-capacity coupled amplifiers	376
-capacity oscillator	484, 489
impedance of	200
lamps	319
measurement of	128
specific	125

	Page
Resistance— <i>contd.</i>	
stabilisation of oscillator	473
temperature coefficient of	125
transmission line	717
Resonance,	211
anti-	215
conditions for	212
current in parallel circuit at	216
impedance of parallel circuit at	216
impedance of series circuit at	212
parallel	215
series	212
summary of conditions for	227
voltages in series circuit at	212
Resonant circuits,	212, 215
having two resonant frequencies	224
selectivity of	219
Response curves of R-C amplifier	382
Retentivity	157
Right-hand rule	166
Ripple	300
RMS values of sine waves	189
Rotary transformers	311
Rotating vectors	63, 193
Rotation of coil in field	167
S	
Saturation current, diode	327
Saw-toothed waveform	117, 541
Saw-tooth oscillator	545
Screen, current	351
grid	350
Secondary emission	384
Secondary line constants,	717
determination of	758
Sections, asymmetrical	607
attenuating	606
balanced	612
bridged-T type	588, 612
equivalent to line	766
filter prototype	640
half-	580
half-, terminating	769
half-, loading termination	739
L type	584, 610
lattice type	586, 598, 614
<i>m</i> -derived	650
<i>m</i> -derived half-	658
π type	577, 611
symmetrical	607
T type	569, 607
T and π filter	635
unbalanced	612

	Page
Selectivity of resonant circuits	219
Selector	13
Selenium rectifiers	275, 280
Self-inductance of a coil	169
Self-capacity	256, 284
Series,	27, 48, 89
exponential	48
Series feedback	451
Series resonance	212, 227
Shift controls on CRO	553
Short-circuit impedance	757
Shunts, meter	182, 299
Sidebands	499
Side-circuit,	17
loading	736
Signalling, CBS	11
magneto	11
voice frequency	15
Signs, mathematical	20
Silicon-iron alloys	265
Simultaneous equations	23
Sine,	36, 40
tables	806
Sine-waves,	41, 63, 101, 189
addition of two	64, 193, 493
Single crystal filter	692
Single loading coils	734
Single stage amplifier with, composite NFB	448
current NFB	442
voltage NFB	436
Sinusoidal waveforms,	41, 63, 101, 189
instantaneous values of	189
mean values of	189
representation by vectors	193
RMS values of	189
sum of two	64, 193, 493
Smoothing circuits	300
Solenoid	157, 162
Solution of triangles, formulae	46
Sound, pitch	5, 187
quality	5
speed	5
Space charge	325
Spark quench	299
Spark transmitter	480
Specific resistance	125
Spiral, logarithmic	716

	Page
Square roots, tables	780
Squares tables	778
Square law detection	524
Squegging	469
Stabilisation of output voltage	475
Stabilisation, resistance, of oscillator	473
Stabiliser, current	319
lamp bridge	477
neon	476
voltage	320
Stability of oscillators	471
Stable amplifiers, conditionally	459
Stage gain	345, 362, 378
Star	590
Star-mesh conversion	590
Stub-cables	736
Submarine cables	731
Summations	27
Superposing	16
Superposition theorem	231
Supervisory indicator	11
Suppressed carrier, modulation	506
demodulation	526
Suppressor grid	358
Surds	22
Susceptance	222
Susceptibility	155
Surfaces, areas of	21
Swamp resistors	177
Switchboard,	9
requirements of	10
Symmetrical filters	635
Symmetrical networks	561, 607
Symmetrical waveforms	115
Synchronisation of time bases	543, 547
Synchronising two audio frequencies	496
Synchronous vibrators	306
Systems, multi-channel carrier	19

T

T section,	567, 569
characteristic impedance	570
equivalent to transmission line	705, 766
input impedance	575
open- and short-circuit impedance	570
propagation constant	572

	Page
T section filter,	635
bridged-, equivalent of lattice filter	689
<i>m</i> -derived filter	651
T type attenuator,	607
balanced	612
bridged	612
design of	620
unbalanced	612
T type crystal filter	697
Tables, mathematical	775
Tandem, networks in	239
Tangent	36, 40, 810
Telegraph codes	2
Telegraphs, multi-channel	18
filter design	681
Telegraphy	1
VF	18
Telephone	5, 8
Telephone exchanges	8
Telephony,	3
carrier	19
Temperature coefficient of resistance	125
Terminating measurement	625
Terminating half-section, filter	657
Terminations, half-coil loading	739, 769
half-section loading	739, 769
of filters	677
Tetrode,	350
beam	355
critical distance	353
output	357
power amplifier	408
Theorems, Binomial	48
Fourier's	101, 189
Fourier's, analysis of common wave forms	117
Maclaurin's	89
Pythagoras'	21
Thévenin's	233
Thermal agitation	405
Thermionic Emission	323
Thermionic valves,	323
as modulators	504
Thermo-couple meters	181, 289
Thévenin's theorem	233
Three-phase voltages	316
" Through " measurement	624
Thyratron	542
Time bases,	541
high frequency	548
linear	542
Puckle's	548
synchronisation of	542, 547
transitron saw-tooth oscillator	545

	Page
Time constant, of capacitive circuit	148
of inductive circuit	173
Toroidal loading coils	732
Transformation of impedance, in filter	679, 682
Transformer-coupled amplifier	389
Transformers,	244
audio frequency	262
auto-	264
capacity of windings	256, 267
core materials	265
current equation	252
current ratio	247
equivalent circuits	255
hybrid	14
impedance ratio	247
input	263, 394
intervalve	264
line	262
loose coupling	256
losses of,	254
mains	259
multi-winding	252
output	264
PO line	262
perfect	244, 258
rotary	311
voltage equation	252
voltage ratio	246
Transitron oscillator	481, 545
Transmission line,	703
characteristic impedance	703
constants	717, 749
current and voltage distribution	712, 750
equivalent networks	766
equivalent T section	705
half-coil terminations	739, 769
half-section terminations	739, 769
impedance-frequency characteristics	763
mathematical treatment	749
reflection	745
" Trans " measurement	625
Transmission measurements,	623
reference power	623
Transmission measuring sets,	631
calibration	633
Transmitter, spark	480
Triangular waveform	117
Trigger control	547, 549
Trigonometry	20, 35
Trigonometrical ratios	35
differential coefficients of	73
graphs of	40

	Page
Triode	328
A.C. resistance of	335
amplifier	338
amplifier equivalent circuits	344
constants	331
cut-off bias	333
effect of gas	347
-heptode	365
-hexode	365
power amplifier	406
variable-mu	334
True power	208
Tuned-anode oscillator	464, 470
Tuned-anode tuned-grid oscillator	482
Tuned class C amplifier	419
Tuned-grid oscillator	466
Tuned voltage amplifier	394
Twelve ordinate analysis	107
Two-wire circuit	14

U

Unbalanced, T L and π sections	612
symmetrical filters	635
Underground cables, loading of	740
Unloaded cables, practical formulae	724
Uniform transmission line, equivalent section of	766
Universal response curves R-C amplifiers	382
Units, electrostatic	130
electromagnetic	130
international	131
practical	131
Upper sideband	500
Useful numbers	820

V

Valve characteristics,	331
measurement of, using CRO	558
Valve constants	331
Valve noise	405
Valve type decibelmeter	628
Valves, co-planar grid	365
diode	324
frequency-changer	364
hexode	358
tetrode	350
triode	328

	Page
Variable attenuators	295, 622
Variable frequency oscillators	484
Variable, independent	80
Variable-mu triode	334
Variable-mu pentode	360
Vector representation of, sine waves	193
addition of voltages	196
Vectors, addition of	51
conjugates of	62
conversion from rectangular to polar co-ordinates and <i>vice versa</i>	58, 59
definition	51
exponential notation	62
logarithm of	63
multiplication and division of	59
multiplication by numbers	54
negative	53
polar notation	56
powers of	60
rationalisation of	62
rectangular notation	55
roots of	61
rotating	63
rotation of	54
Velocity of propagation	716
VF -(see Voice-frequency).	
Vibrators	304
construction of	309
interference suppression	308
series drive type	306
shunt drive type	304
synchronous	306
Voice-frequency signalling	15
telegraphy	18
Voltage,	190
alternating	168, 189
distribution along transmission line	714, 751
doubler circuits	286, 328
limiter	296
measurement of	173, 288
measurement using CRO	553
negative feedback	434
quadrupler	288
regulation	306
stabilisers	320
Voltage amplifiers,	338, 376
pentode	361
triode	339
tuned	394
Voltages, conditions for maximum	227
Voltmeter,	173, 288
rectifier	290, 292
Volumes, formulae for calculating	21
VU	242

	Page
W	
Wavelength,	716
constant	710
Weston cadmium cell	122
Wheatstone bridge	129, 268
Wide-band crystal filters	701
Width of band, band-pass filters	667
band-stop filters	674
Wien frequency bridge	271
X	
X-axis	28
X-axis of quartz crystal	691
X-cut quartz crystal.. .. .	692
Y	
Y-axis	28
Y-axis of quartz crystal	691
Z	
Z-axis of quartz crystal	691

CENTRAL LIBRARY
BIRLA INSTITUTE OF TECHNOLOGY AND SCIENCE
PILANI (Rajasthan)

Class No. 621.38

Book No. G.24

Acc. No. 55.391

Duration of loan	{	Students/Spl/'C'		Teachers—'	
		Text Books — 3 days			One month
		Technical Books — 7 days			General Books — 14 days

FROM THE DATE OF ISSUE

--	--	--	--

